
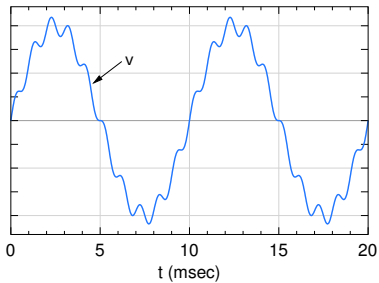




Introduction to filters

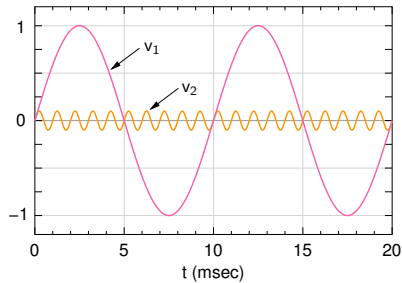Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.



Introduction to filters


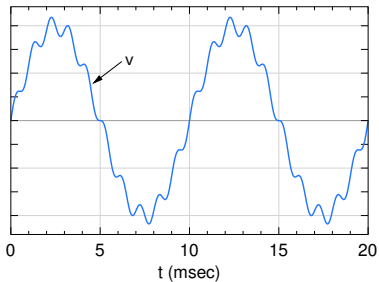
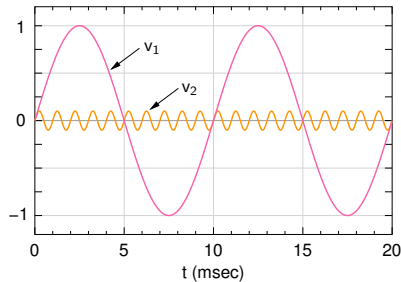
Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.



A low-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the low-frequency component $v_1(t)$ and remove the high-frequency component $v_2(t)$.

Introduction to filters

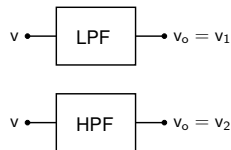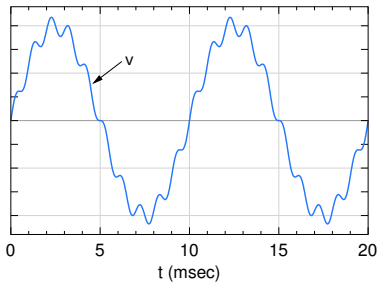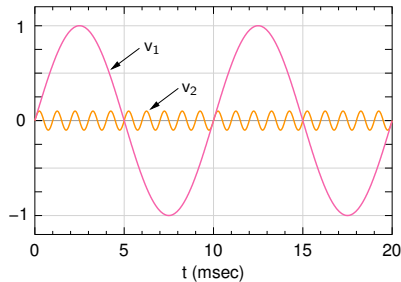Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.






A low-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the low-frequency component $v_1(t)$ and remove the high-frequency component $v_2(t)$.

A high-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the high-frequency component $v_2(t)$ and remove the low-frequency component $v_1(t)$.

Introduction to filters

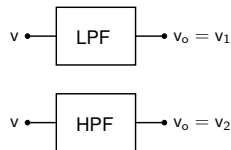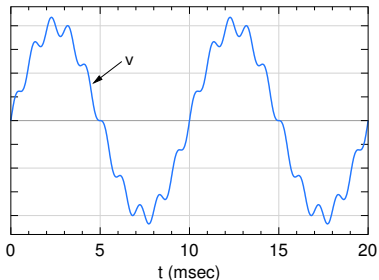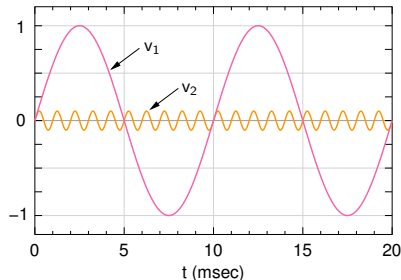Consider $v(t) = v_1(t) + v_2(t) = V_{m1} \sin \omega_1 t + V_{m2} \sin \omega_2 t$.





A low-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the low-frequency component $v_1(t)$ and remove the high-frequency component $v_2(t)$.

A high-pass filter with a cut-off frequency $\omega_1 < \omega_c < \omega_2$ will pass the high-frequency component $v_2(t)$ and remove the low-frequency component $v_1(t)$.




There are some other types of filters, as we will see.

Ideal low-pass filter

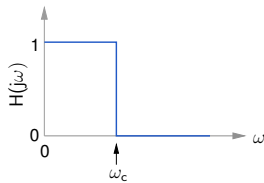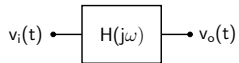


$$V_o(j\omega) = H(j\omega) V_i(j\omega).$$

Ideal low-pass filter

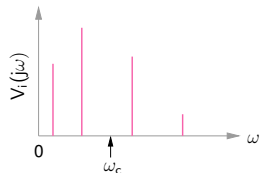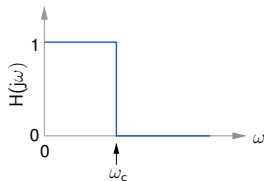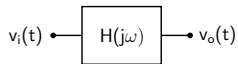


LPF

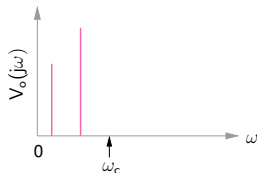

$$V_o(j\omega) = H(j\omega) V_i(j\omega).$$

Ideal low-pass filter

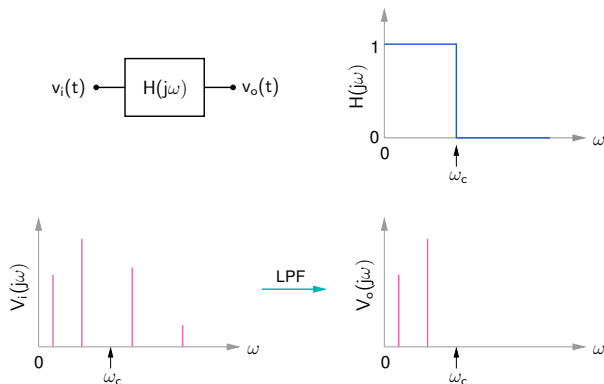


$$V_o(j\omega) = H(j\omega) V_i(j\omega).$$



All components with $\omega < \omega_c$ appear at the output without attenuation.

All components with $\omega > \omega_c$ get eliminated.



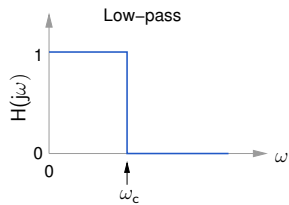
(Note that the ideal low-pass filter has $\angle H(j\omega) = 1$, i.e., $H(j\omega) = 1 + j0$.)







Ideal filters


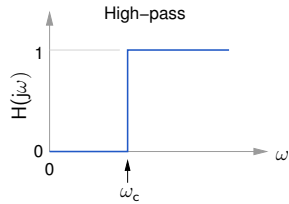
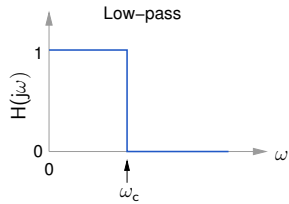


Ideal filters

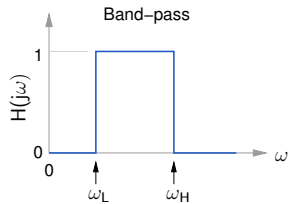
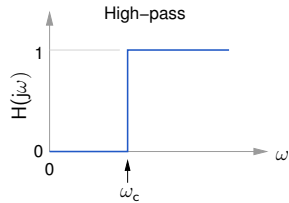
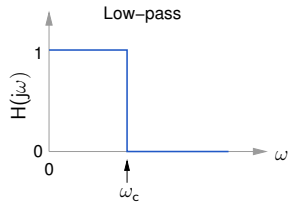


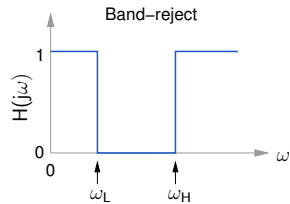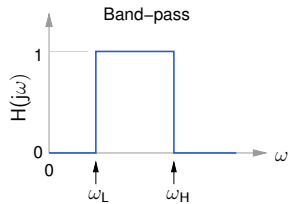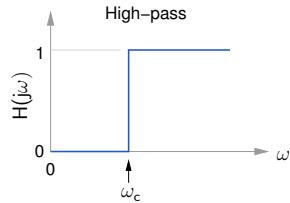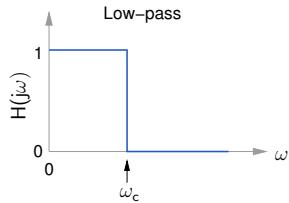




Ideal low-pass filter: example

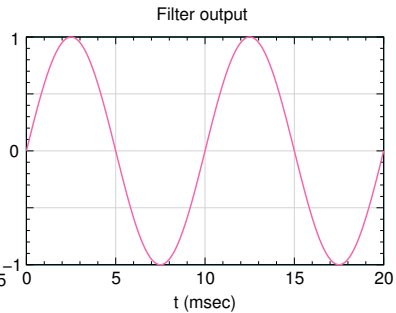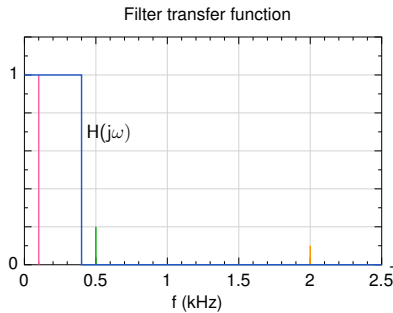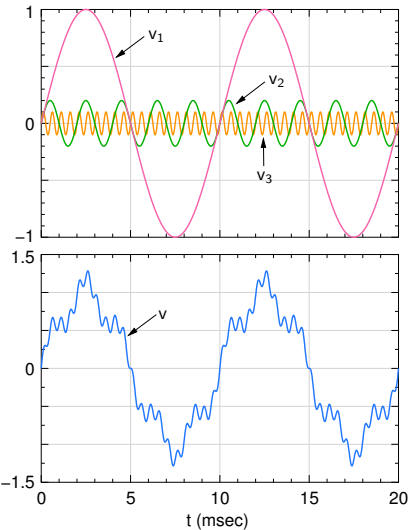



Ideal high-pass filter: example

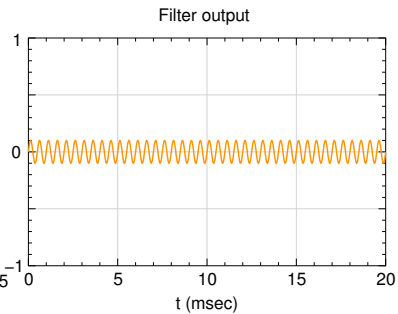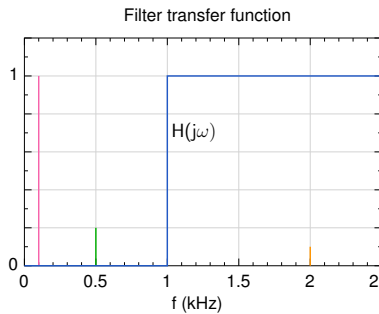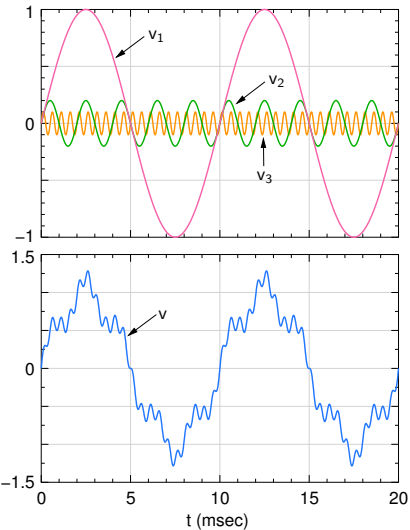

Ideal band-pass filter: example

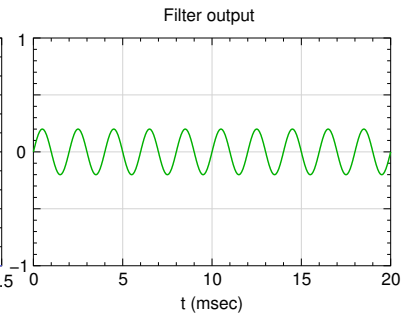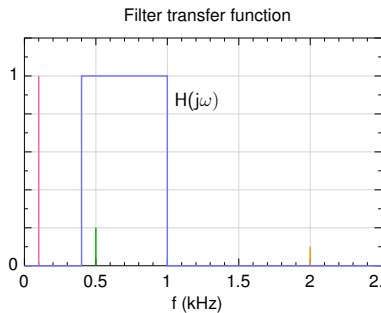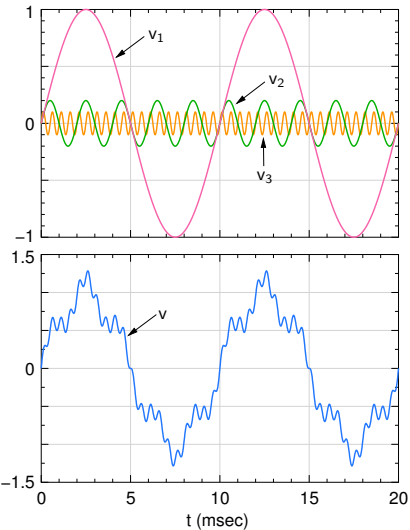

Ideal band-reject filter: example

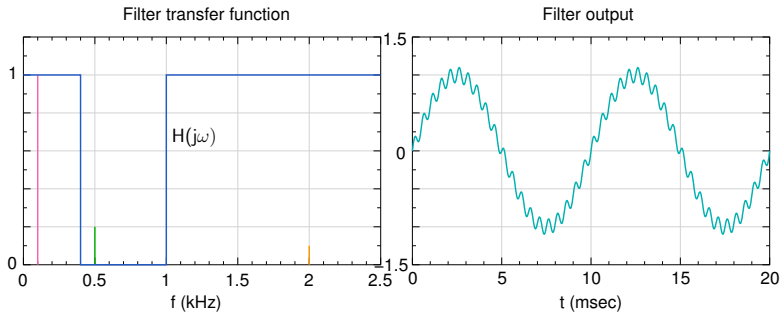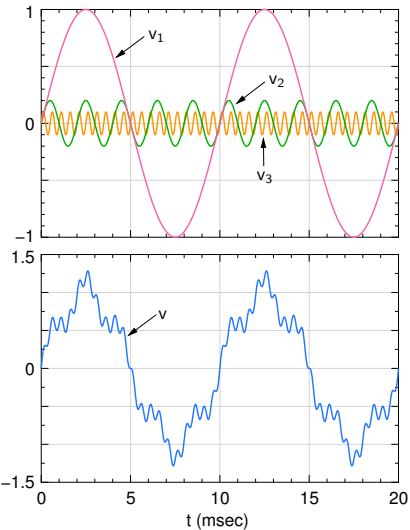

- * In practical filter circuits, the ideal filter response is approximated with a suitable $H(j\omega)$ that can be obtained with circuit elements. For example,

$$H(s) = \frac{1}{a_5 s^5 + a_4 s^4 + a_3 s^3 + a_2 s^2 + a_1 s + a_0}$$

represents a 5th-order low-pass filter.

- * In practical filter circuits, the ideal filter response is approximated with a suitable $H(j\omega)$ that can be obtained with circuit elements. For example,

$$H(s) = \frac{1}{a_5 s^5 + a_4 s^4 + a_3 s^3 + a_2 s^2 + a_1 s + a_0}$$

represents a 5th-order low-pass filter.

- * Some commonly used approximations (polynomials) are the Butterworth, Chebyshev, Bessel, and elliptic functions.


- * In practical filter circuits, the ideal filter response is approximated with a suitable $H(j\omega)$ that can be obtained with circuit elements. For example,

$$H(s) = \frac{1}{a_5 s^5 + a_4 s^4 + a_3 s^3 + a_2 s^2 + a_1 s + a_0}$$


represents a 5th-order low-pass filter.

- * Some commonly used approximations (polynomials) are the Butterworth, Chebyshev, Bessel, and elliptic functions.
- * Coefficients for these filters are listed in filter handbooks. Also, programs for filter design are available on the internet.

Practical filters

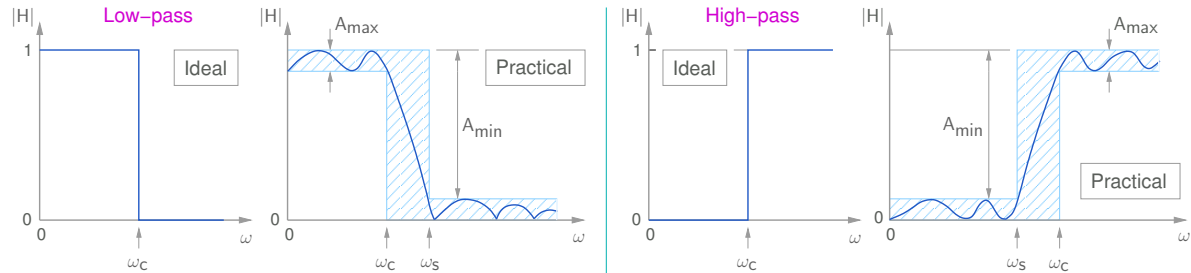


Practical filters

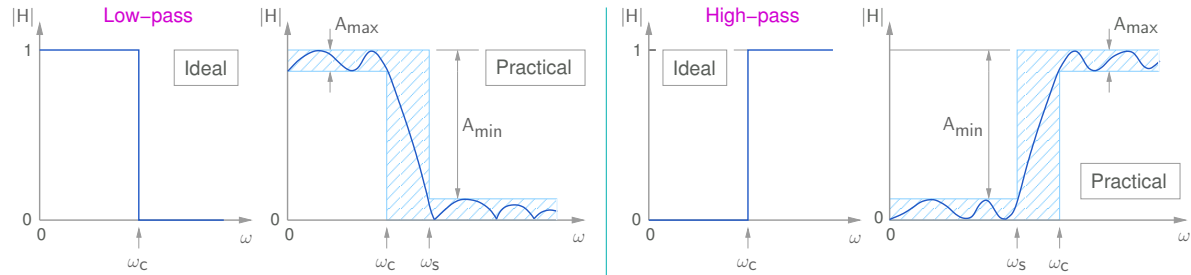


* A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.

Practical filters

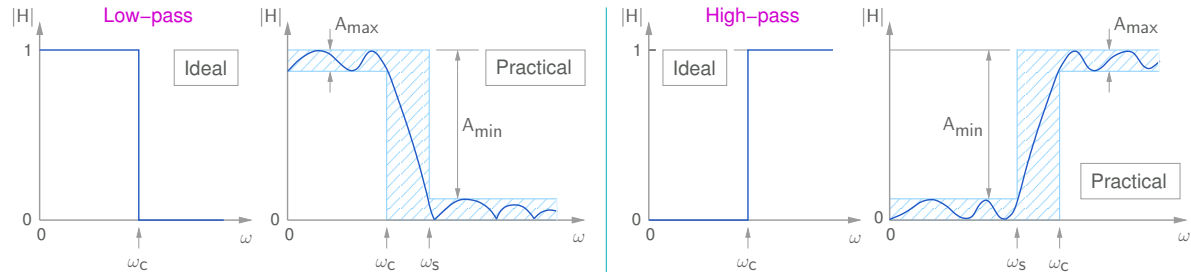


- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.

Practical filters

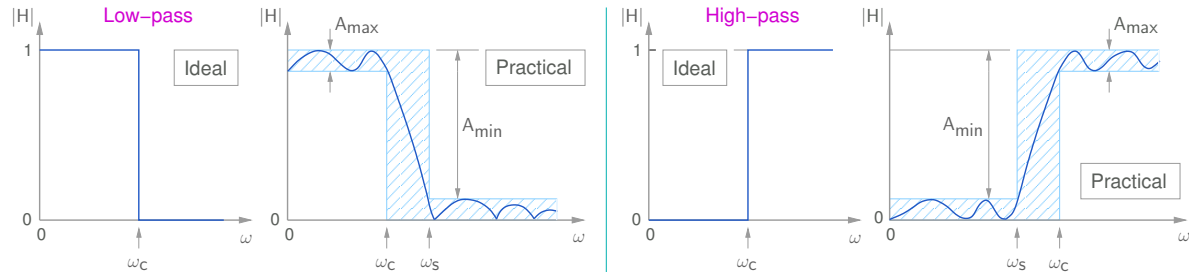


- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.
- * ω_s : edge of the stop band.

Practical filters

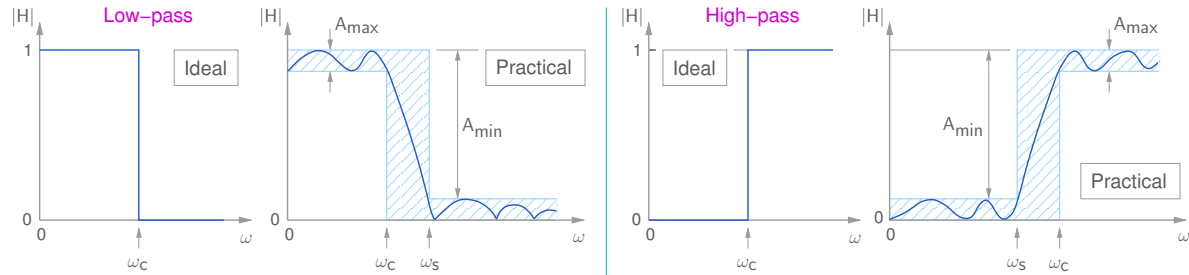

- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.
- * ω_s : edge of the stop band.
- * ω_s/ω_c (for a low-pass filter): selectivity factor, a measure of the sharpness of the filter.

Practical filters

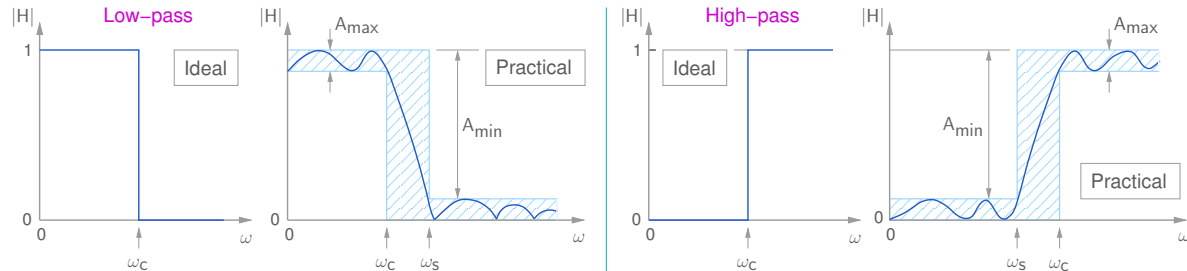

- * A practical filter may exhibit a ripple. A_{\max} is called the maximum passband ripple, e.g., $A_{\max} = 1$ dB.
- * A_{\min} is the minimum attenuation to be provided by the filter, e.g., $A_{\min} = 60$ dB.
- * ω_s : edge of the stop band.
- * ω_s/ω_c (for a low-pass filter): selectivity factor, a measure of the sharpness of the filter.
- * $\omega_c < \omega < \omega_s$: transition band.

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

Butterworth filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 (\omega/\omega_c)^{2n}}}.$$

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

Butterworth filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 (\omega/\omega_c)^{2n}}}.$$

Chebyshev filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2(\omega/\omega_c)}} \quad \text{where}$$

$$C_n(x) = \cos [n \cos^{-1}(x)] \quad \text{for } x \leq 1,$$

$$C_n(x) = \cosh [n \cosh^{-1}(x)] \quad \text{for } x \geq 1,$$

For a low-pass filter, $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$.

Coefficients (a_i) for various types of filters are tabulated in handbooks. We now look at $|H(j\omega)|$ for two commonly used filters.

Butterworth filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 (\omega/\omega_c)^{2n}}}.$$

Chebyshev filters:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2(\omega/\omega_c)}} \quad \text{where}$$



$$C_n(x) = \cos [n \cos^{-1}(x)] \quad \text{for } x \leq 1,$$

$$C_n(x) = \cosh [n \cosh^{-1}(x)] \quad \text{for } x \geq 1,$$



$H(s)$ for a high-pass filter can be obtained from $H(s)$ of the corresponding low-pass filter by $(s/\omega_c) \rightarrow (\omega_c/s)$.

Practical filters (low-pass)

Butterworth filters:

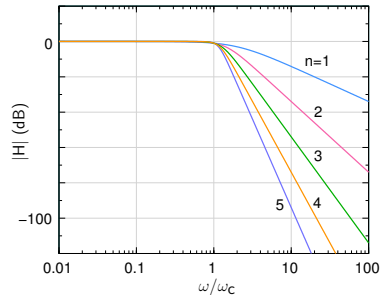
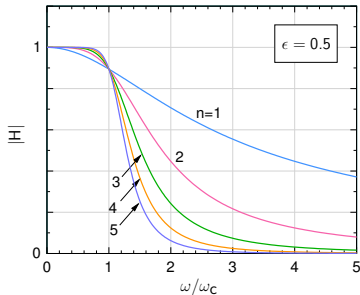


Chebyshev filters:

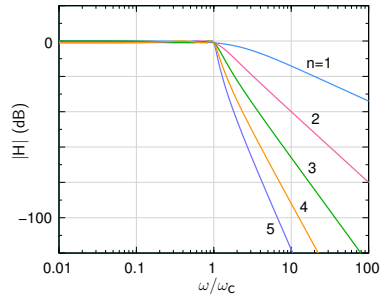
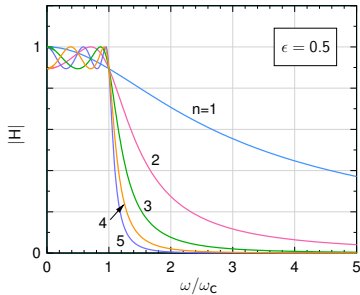


Practical filters (high-pass)


Butterworth filters:

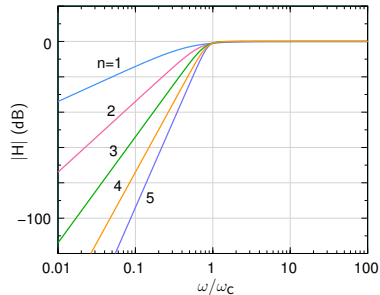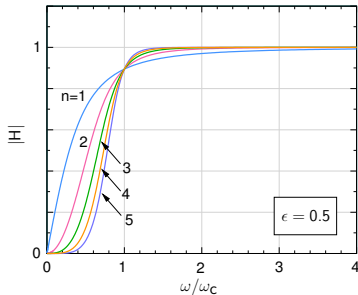


Chebyshev filters:

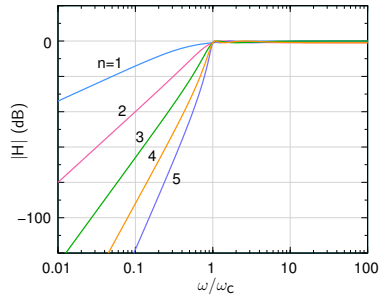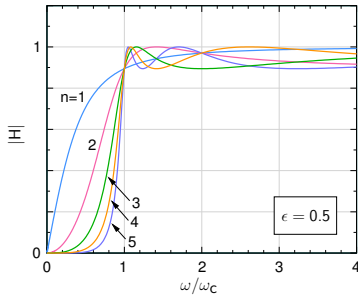

Passive filter example

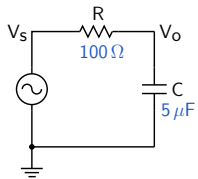

Passive filter example

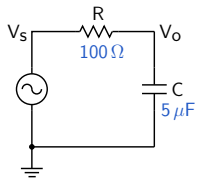


$$H(s) = \frac{(1/sC)}{R + (1/sC)} = \frac{1}{1 + (s/\omega_0)},$$

$$\text{with } \omega_0 = 1/RC \rightarrow f_0 = \omega_0/2\pi = 318\text{ Hz}$$

(Low-pass filter)


Passive filter example

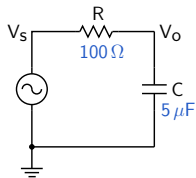

$$H(s) = \frac{(1/sC)}{R + (1/sC)} = \frac{1}{1 + (s/\omega_0)},$$


$$\text{with } \omega_0 = 1/RC \rightarrow f_0 = \omega_0/2\pi = 318\text{ Hz}$$

(Low-pass filter)

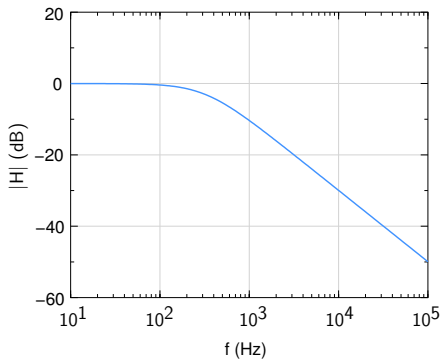


(SEQUEL file: ee101_rc_ac_2.sqproj)

Passive filter example

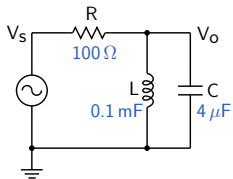

Passive filter example

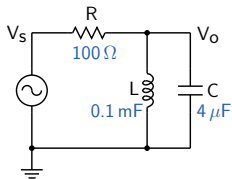


$$H(s) = \frac{(sL) \parallel (1/sC)}{R + (sL) \parallel (1/sC)} = \frac{s(L/R)}{1 + s(L/R) + s^2LC}$$

$$\text{with } \omega_0 = 1/\sqrt{LC} \rightarrow f_0 = \omega_0/2\pi = 7.96\ \text{kHz}$$

(Band-pass filter)


Passive filter example

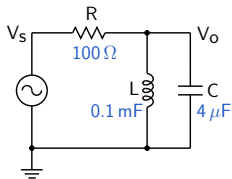

$$H(s) = \frac{(sL) \parallel (1/sC)}{R + (sL) \parallel (1/sC)} = \frac{s(L/R)}{1 + s(L/R) + s^2 LC}$$

$$\text{with } \omega_0 = 1/\sqrt{LC} \rightarrow f_0 = \omega_0/2\pi = 7.96\ \text{kHz}$$

(Band-pass filter)

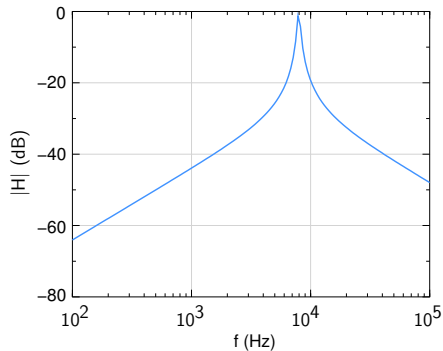

(SEQUEL file: ee101_rlc_3.sqproj)


- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.

- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.
- * With op-amps, a filter circuit can be designed with a pass-band gain.


- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.
- * With op-amps, a filter circuit can be designed with a pass-band gain.
- * Op-amp filters can be easily incorporated in an integrated circuit.

- * Op-amp filters can be designed without using inductors. This is a significant advantage since inductors are bulky and expensive. Inductors also exhibit nonlinear behaviour (arising from the core properties) which is undesirable in a filter circuit.
- * With op-amps, a filter circuit can be designed with a pass-band gain.
- * Op-amp filters can be easily incorporated in an integrated circuit.
- * However, there are situations in which passive filters are still used.
 - high frequencies at which op-amps do not have sufficient gain
 - high power which op-amps cannot handle

Op-amp filters: example

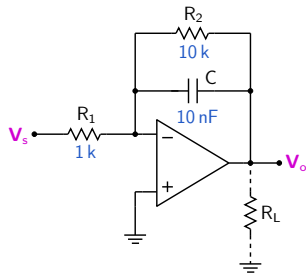

Op-amp filters: example

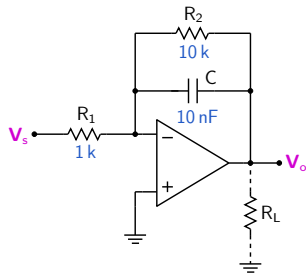


Op-amp filters are designed for op-amp operation in the linear region

→ Our analysis of the inverting amplifier applies, and we get,

$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

Op-amp filters: example

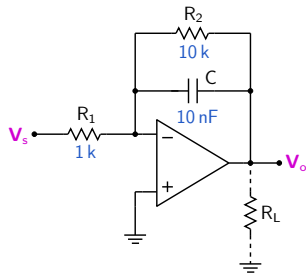

Op-amp filters are designed for op-amp operation in the linear region



→ Our analysis of the inverting amplifier applies, and we get,

$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

This is a low-pass filter, with $\omega_0 = 1/R_2C$ (i.e., $f_0 = \omega_0/2\pi = 1.59 \text{ kHz}$).

Op-amp filters: example

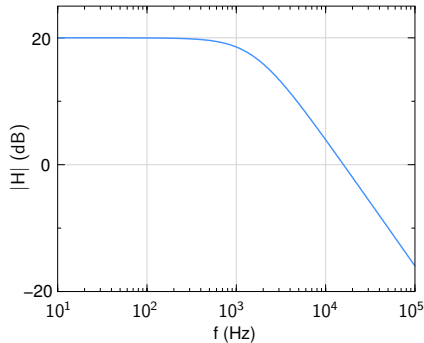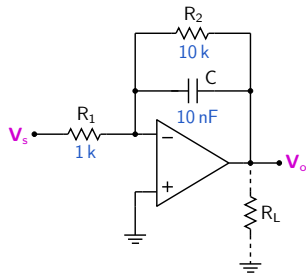

Op-amp filters are designed for op-amp operation in the linear region



→ Our analysis of the inverting amplifier applies, and we get,

$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

This is a low-pass filter, with $\omega_0 = 1/R_2C$ (i.e., $f_0 = \omega_0/2\pi = 1.59 \text{ kHz}$).

Op-amp filters: example

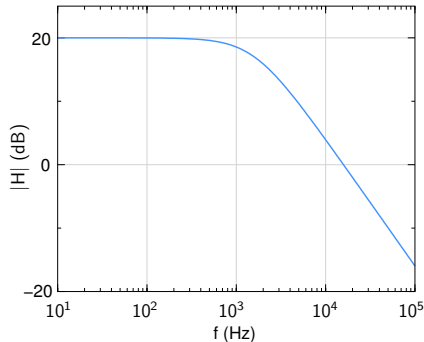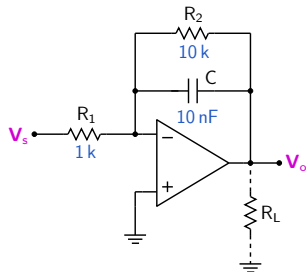

Op-amp filters are designed for op-amp operation in the linear region

→ Our analysis of the inverting amplifier applies, and we get,


$$\mathbf{V}_o = -\frac{R_2 \parallel (1/sC)}{R_1} \mathbf{V}_s \quad (\mathbf{V}_s \text{ and } \mathbf{V}_o \text{ are phasors})$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$


This is a low-pass filter, with $\omega_0 = 1/R_2C$ (i.e., $f_0 = \omega_0/2\pi = 1.59\text{ kHz}$).

(SEQUEL file: ee101_op_filter_1.sqproj)

Op-amp filters: example

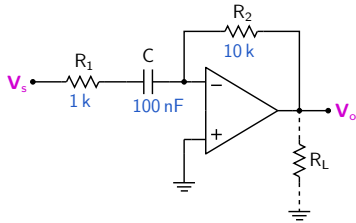


Op-amp filters: example

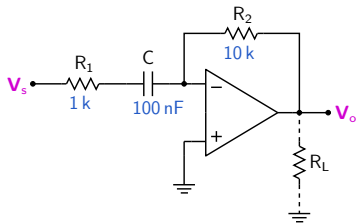

$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$



Op-amp filters: example

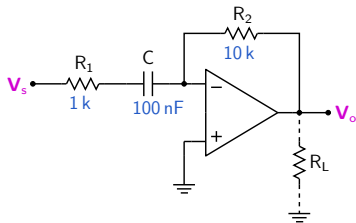

$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$



This is a high-pass filter, with $\omega_0 = 1/R_1C$ (i.e., $f_0 = \omega_0/2\pi = 1.59$ kHz).

Op-amp filters: example

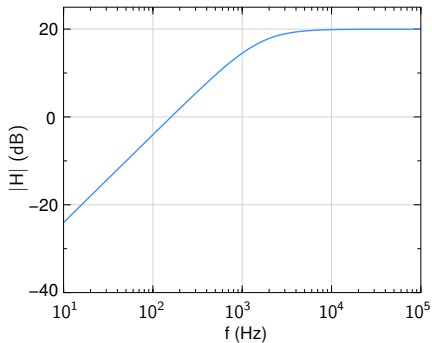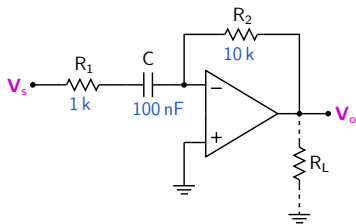

$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$

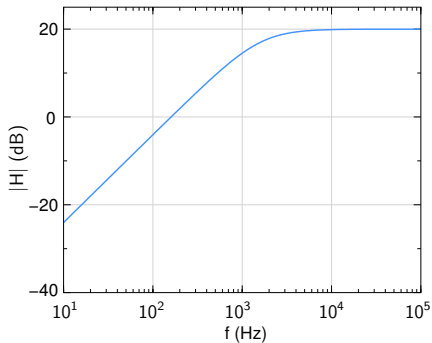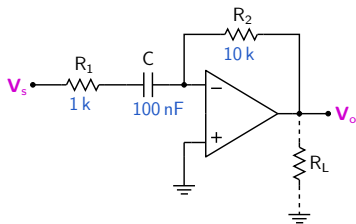This is a high-pass filter, with $\omega_0 = 1/R_1C$ (i.e., $f_0 = \omega_0/2\pi = 1.59$ kHz).




$$H(s) = -\frac{R_2}{R_1 + (1/sC)} = -\frac{sR_2C}{1 + sR_1C}.$$


This is a high-pass filter, with $\omega_0 = 1/R_1C$ (i.e., $f_0 = \omega_0/2\pi = 1.59$ kHz).

(SEQUEL file: ee101_op_filter_2.sqproj)

Op-amp filters: example

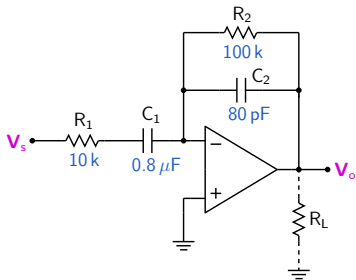


Op-amp filters: example

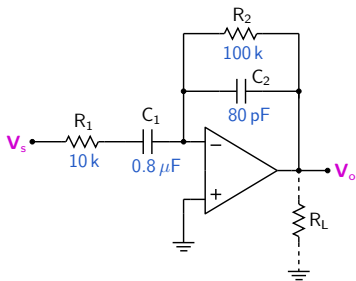

$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}.$$

Op-amp filters: example


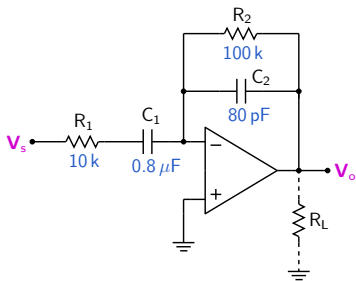


$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}.$$

This is a band-pass filter, with $\omega_L = 1/R_1 C_1$ and $\omega_H = 1/R_2 C_2$.

$\rightarrow f_L = 20\text{ Hz}$, $f_H = 20\text{ kHz}$.

Op-amp filters: example

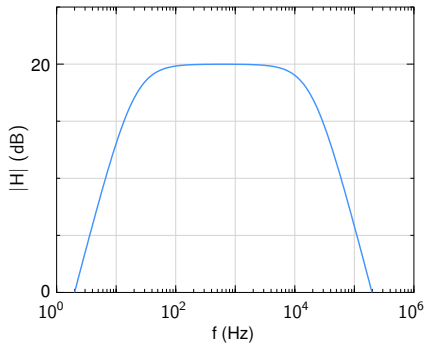
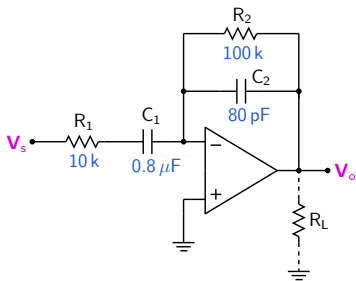


$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1C_1}{(1 + sR_1C_1)(1 + sR_2C_2)}.$$

This is a band-pass filter, with $\omega_L = 1/R_1C_1$ and $\omega_H = 1/R_2C_2$.

$\rightarrow f_L = 20\text{ Hz}$, $f_H = 20\text{ kHz}$.

Op-amp filters: example

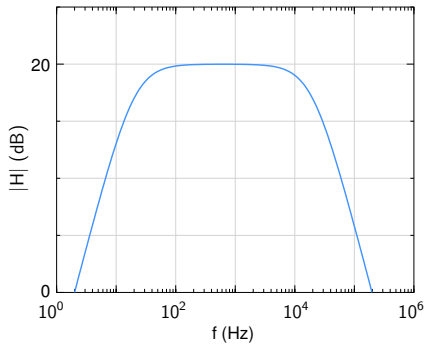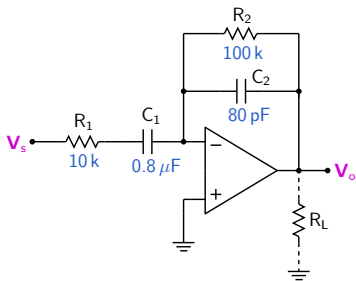



$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}.$$

This is a band-pass filter, with $\omega_L = 1/R_1 C_1$ and $\omega_H = 1/R_2 C_2$.

$\rightarrow f_L = 20$ Hz, $f_H = 20$ kHz.



(SEQUEL file: ee101_op_filter_3.sqproj)

Graphic equalizer

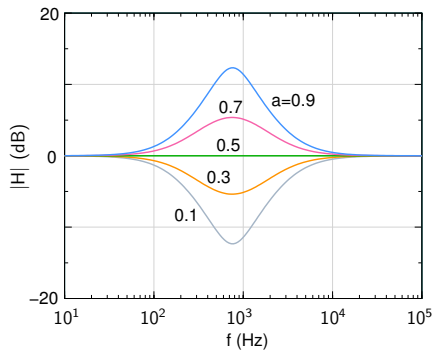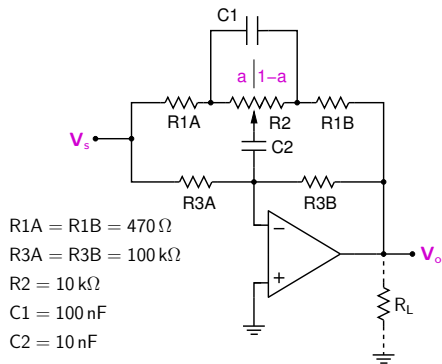



(Ref.: S. Franco, "Design with Op Amps and analog ICs")

Graphic equalizer

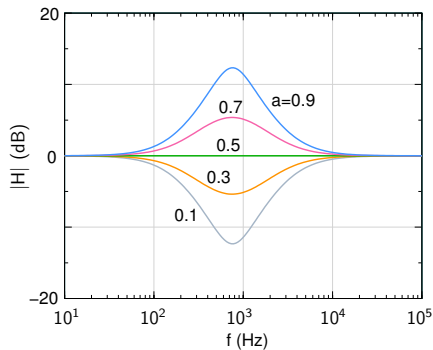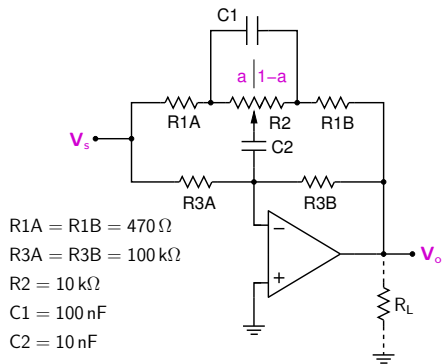

(Ref.: S. Franco, "Design with Op Amps and analog ICs")

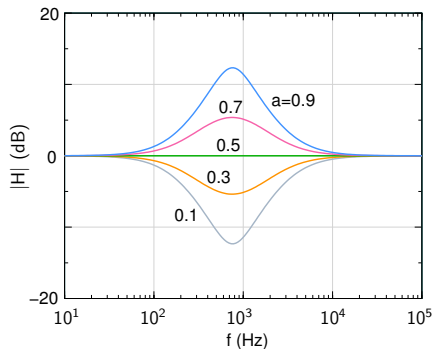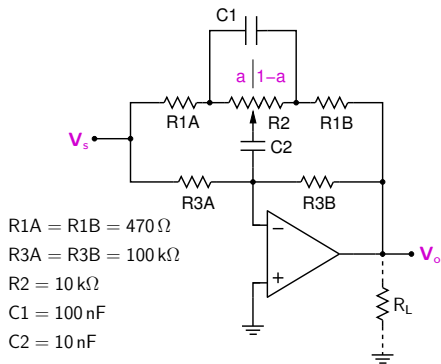- * Equalizers are implemented as arrays of narrow-band filters, each with an adjustable gain (attenuation) around a centre frequency.




(Ref.: S. Franco, "Design with Op Amps and analog ICs")

- * Equalizers are implemented as arrays of narrow-band filters, each with an adjustable gain (attenuation) around a centre frequency.
- * The circuit shown above represents one of the equalizer sections.
(SEQUEL file: ee101_op_filter_4.sqproj)



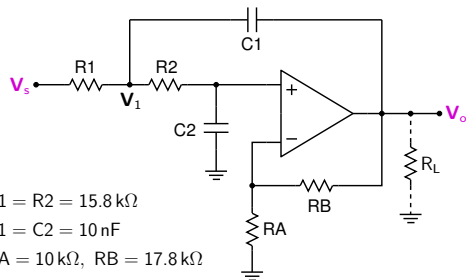Sallen-Key filter example (2nd order, low-pass)




$$R_1 = R_2 = 15.8 \text{ k}\Omega$$


$$C_1 = C_2 = 10 \text{ nF}$$

$$R_A = 10 \text{ k}\Omega, R_B = 17.8 \text{ k}\Omega$$

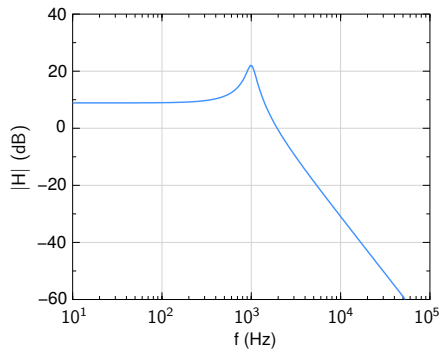(Ref.: S. Franco, "Design with Op Amps and analog ICs")



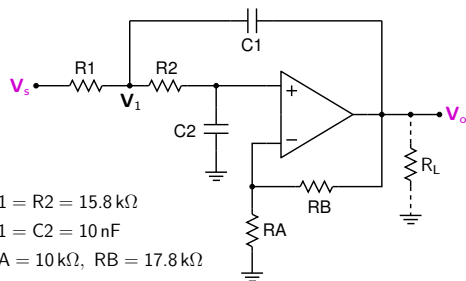Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$


$$R_A = 10 \text{ k}\Omega, R_B = 17.8 \text{ k}\Omega$$

(Ref.: S. Franco, "Design with Op Amps and analog ICs")
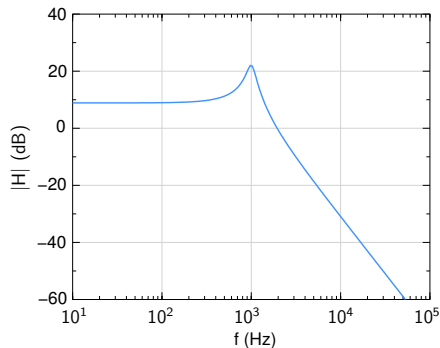
$$V_+ = V_- = V_o \frac{R_A}{R_A + R_B} \equiv V_o / K.$$



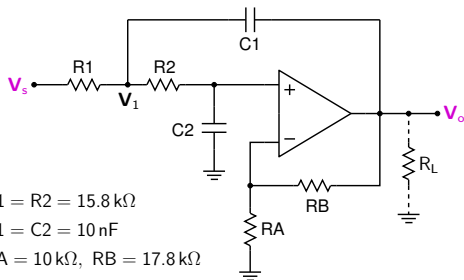Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$

$$R_A = 10 \text{ k}\Omega, R_B = 17.8 \text{ k}\Omega$$

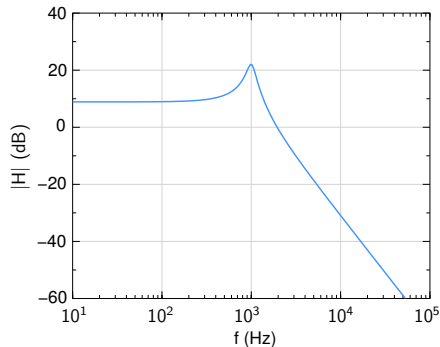
(Ref.: S. Franco, "Design with Op Amps and analog ICs")



$$\mathbf{V}_+ = \mathbf{V}_- = \mathbf{V}_o \frac{R_A}{R_A + R_B} \equiv \mathbf{V}_o / K .$$

$$\text{Also, } \mathbf{V}_+ = \frac{(1/sC_2)}{R_2 + (1/sC_2)} \mathbf{V}_1 = \frac{1}{1 + sR_2C_2} \mathbf{V}_1 .$$

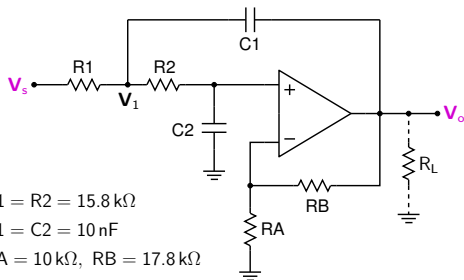Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$

$$R_A = 10 \text{ k}\Omega, R_B = 17.8 \text{ k}\Omega$$

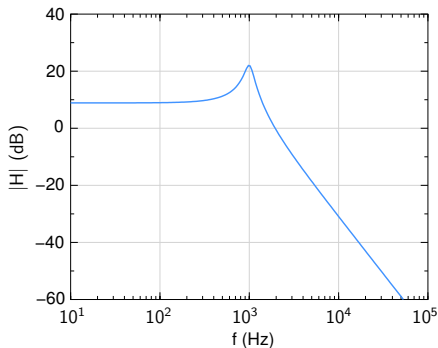(Ref.: S. Franco, "Design with Op Amps and analog ICs")




$$\mathbf{V}_+ = \mathbf{V}_- = \mathbf{V}_o \frac{R_A}{R_A + R_B} \equiv \mathbf{V}_o / K .$$

$$\text{Also, } \mathbf{V}_+ = \frac{(1/sC_2)}{R_2 + (1/sC_2)} \mathbf{V}_1 = \frac{1}{1 + sR_2C_2} \mathbf{V}_1 .$$

$$\text{KCL at } \mathbf{V}_1 \rightarrow \frac{1}{R_1} (\mathbf{V}_s - \mathbf{V}_1) + sC_1 (\mathbf{V}_o - \mathbf{V}_1) + \frac{1}{R_2} (\mathbf{V}_+ - \mathbf{V}_1) = 0 .$$

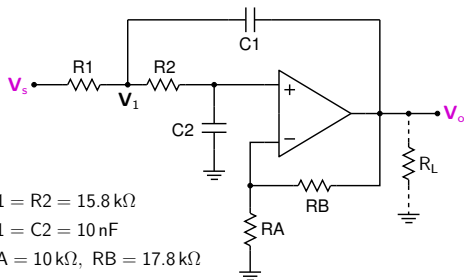Sallen-Key filter example (2nd order, low-pass)




$$R1 = R2 = 15.8 \text{ k}\Omega$$

$$C1 = C2 = 10 \text{ nF}$$

$$RA = 10 \text{ k}\Omega, RB = 17.8 \text{ k}\Omega$$

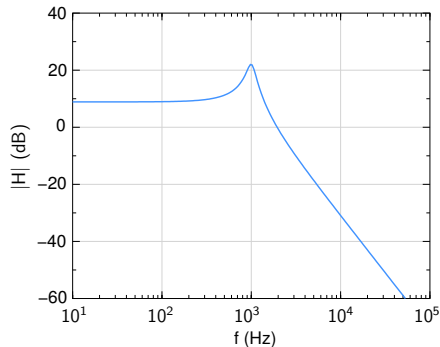(Ref.: S. Franco, "Design with Op Amps and analog ICs")



$$\mathbf{V}_+ = \mathbf{V}_- = \mathbf{V}_o \frac{R_A}{R_A + R_B} \equiv \mathbf{V}_o / K.$$



$$\text{Also, } \mathbf{V}_+ = \frac{(1/sC_2)}{R_2 + (1/sC_2)} \mathbf{V}_1 = \frac{1}{1 + sR_2C_2} \mathbf{V}_1.$$

$$\text{KCL at } \mathbf{V}_1 \rightarrow \frac{1}{R_1}(\mathbf{V}_s - \mathbf{V}_1) + sC_1(\mathbf{V}_o - \mathbf{V}_1) + \frac{1}{R_2}(\mathbf{V}_+ - \mathbf{V}_1) = 0.$$

$$\text{Combining the above equations, } H(s) = \frac{K}{1 + s[(R_1 + R_2)C_2 + (1 - K)R_1C_1] + s^2R_1C_1R_2C_2}.$$

(SEQUEL file: ee101_op_filter_5.sqproj)

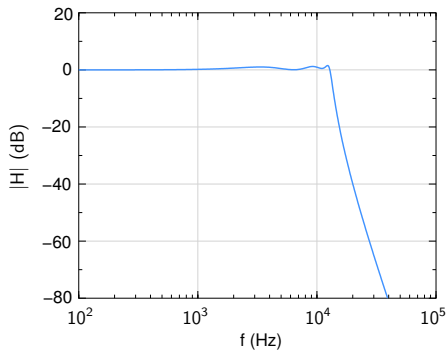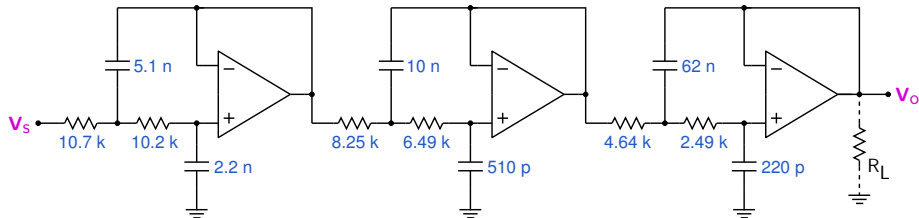
Sixth-order Chebyshev low-pass filter (cascade design)



(Ref.: S. Franco, "Design with Op Amps and analog ICs")


SEQUEL file: ee101_op_filter_6.sqproj

Third-order Chebyshev high-pass filter

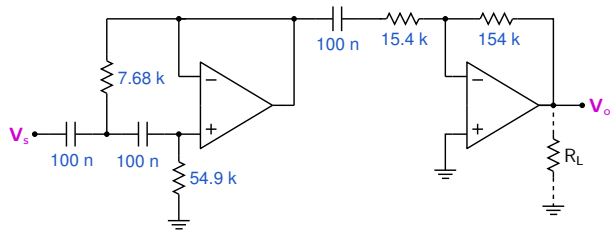


(Ref.: S. Franco, "Design with Op Amps and analog ICs")

SEQUEL file: ee101_op_filter_7.sqproj

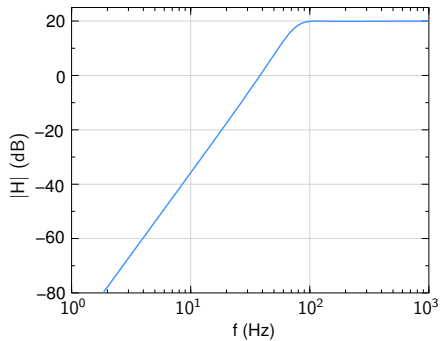


Band-pass filter example

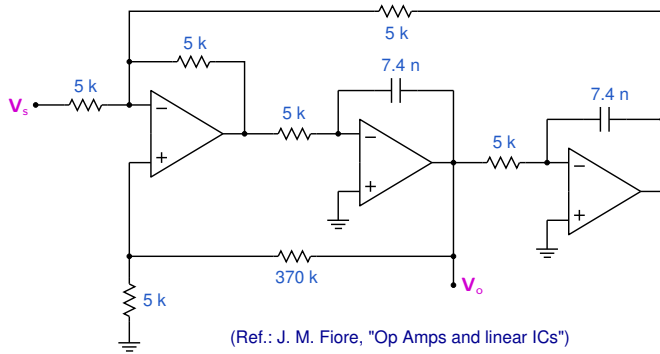


(Ref.: J. M. Fiore, "Op Amps and linear ICs")

SEQUEL file: ee101_op_filter_8.sqproj

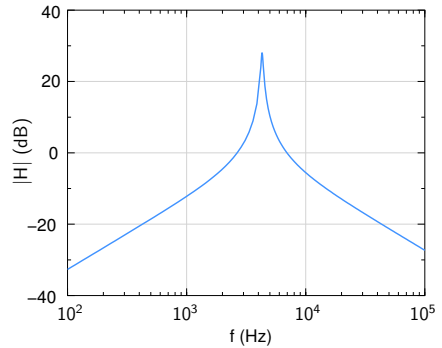


Notch filter example

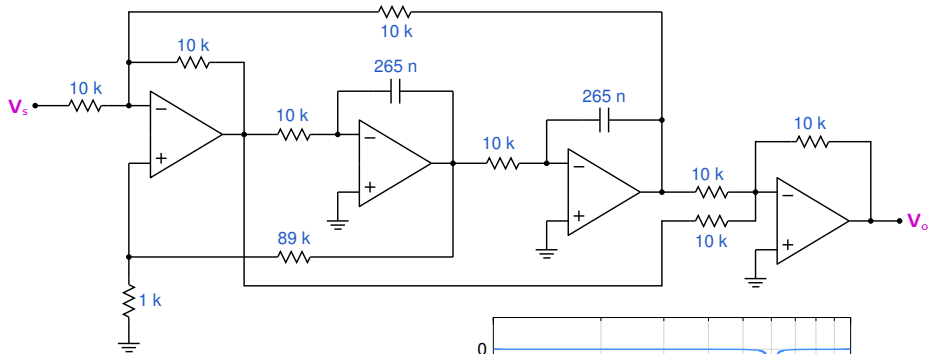


(Ref.: J. M. Fiore, "Op Amps and linear ICs")



SEQUEL file: ee101_op_filter_9.sqproj

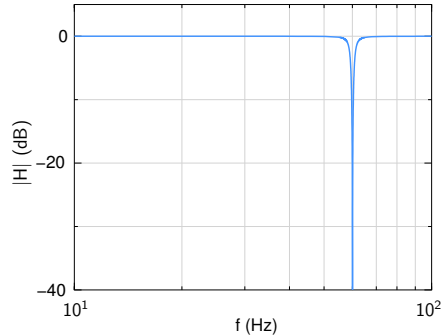




Half-wave rectifier

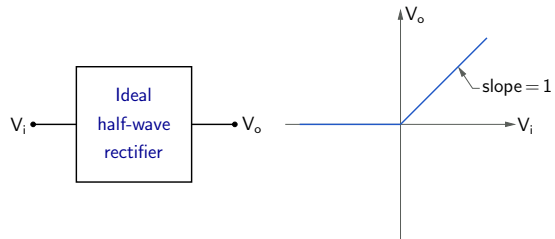







Half-wave rectifier

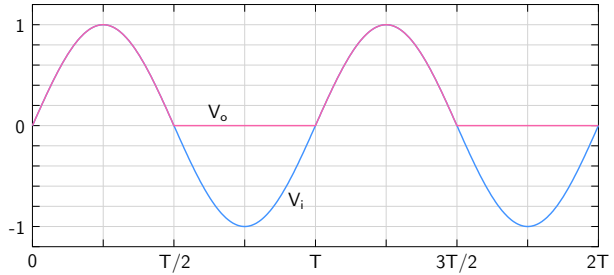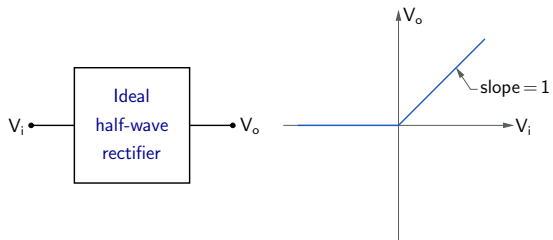




Half-wave rectifier

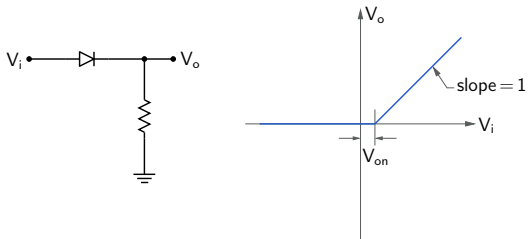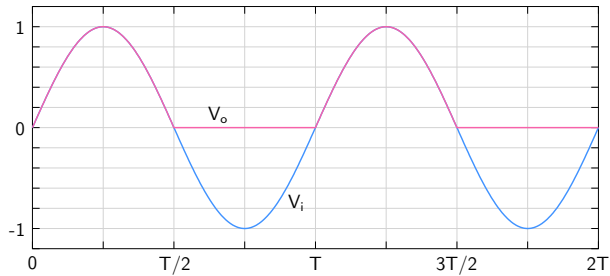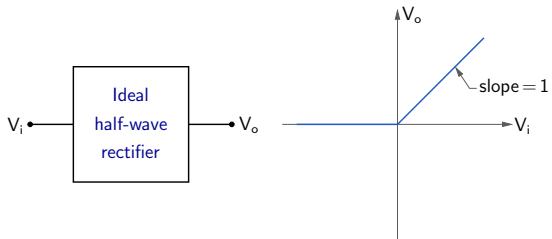


Half-wave rectifier

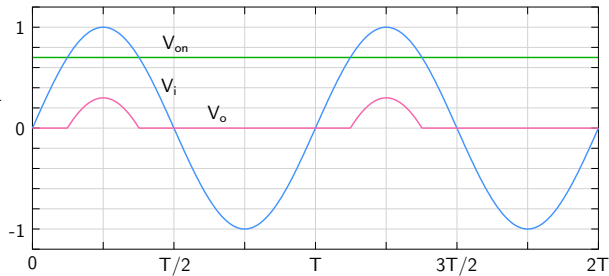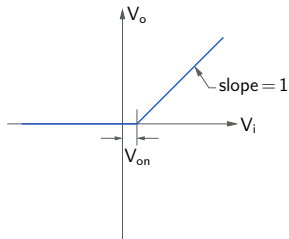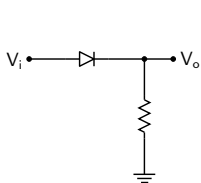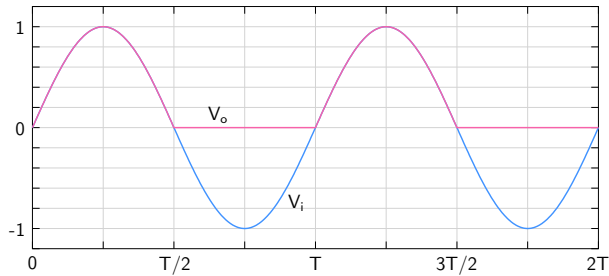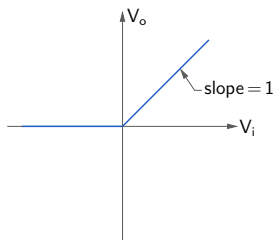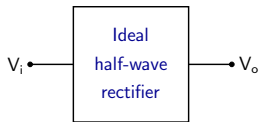


Half-wave rectifier

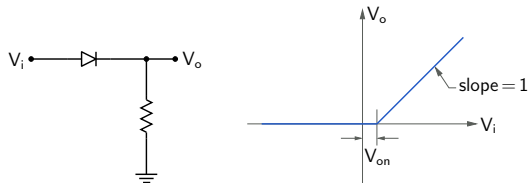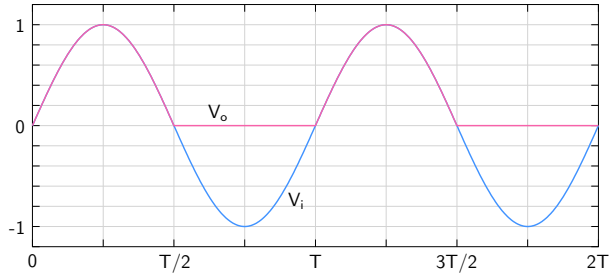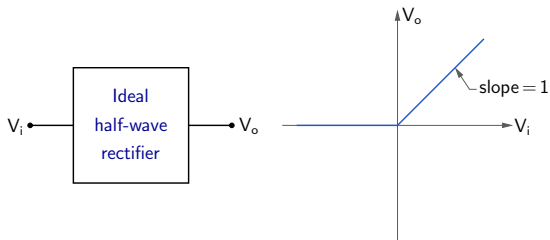


→ need an improved circuit

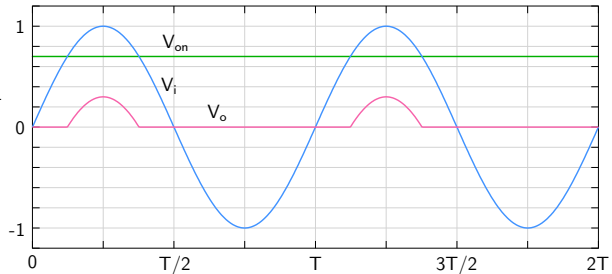

Half-wave precision rectifier

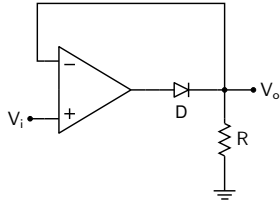


Half-wave precision rectifier

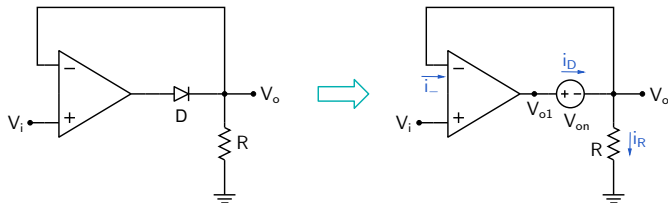

Consider two cases:

- (i) D is conducting: The feedback loop is closed, and the circuit looks like (except for the diode drop) the buffer we have seen earlier.

Half-wave precision rectifier

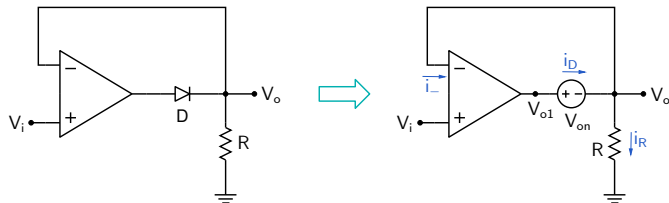


Consider two cases:

- (i) D is conducting: The feedback loop is closed, and the circuit looks like (except for the diode drop) the buffer we have seen earlier.

Since the input current $i_- \approx 0$, $i_R = i_D$.

$$V_+ - V_- = \frac{V_{o1}}{A_V} = \frac{V_o + 0.7 \text{ V}}{A_V} \approx 0 \text{ V} \rightarrow V_o = V_- \approx V_+ = V_i.$$

Half-wave precision rectifier

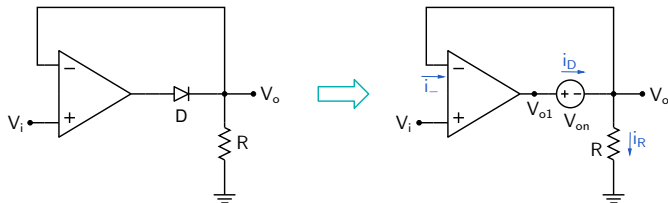

Consider two cases:


- (i) D is conducting: The feedback loop is closed, and the circuit looks like (except for the diode drop) the buffer we have seen earlier.

Since the input current $i_- \approx 0$, $i_R = i_D$.

$$V_+ - V_- = \frac{V_{o1}}{A_V} = \frac{V_o + 0.7 \text{ V}}{A_V} \approx 0 \text{ V} \rightarrow V_o = V_- \approx V_+ = V_i.$$

This situation arises only if $i_D > 0$ (since the diode can only conduct in the forward direction), i.e., $i_R > 0 \rightarrow V_o = i_R R > 0$, and therefore $V_i = V_o > 0 \text{ V}$.

Half-wave precision rectifier

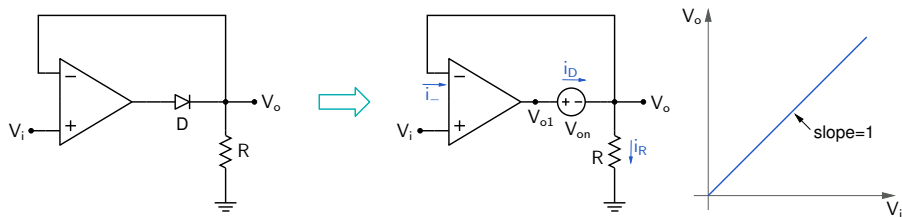

Consider two cases:


- (i) D is conducting: The feedback loop is closed, and the circuit looks like (except for the diode drop) the buffer we have seen earlier.

Since the input current $i_- \approx 0$, $i_R = i_D$.

$$V_+ - V_- = \frac{V_{o1}}{A_V} = \frac{V_o + 0.7 \text{ V}}{A_V} \approx 0 \text{ V} \rightarrow V_o = V_- \approx V_+ = V_i.$$

This situation arises only if $i_D > 0$ (since the diode can only conduct in the forward direction), i.e., $i_R > 0 \rightarrow V_o = i_R R > 0$, and therefore $V_i = V_o > 0 \text{ V}$.

Half-wave precision rectifier

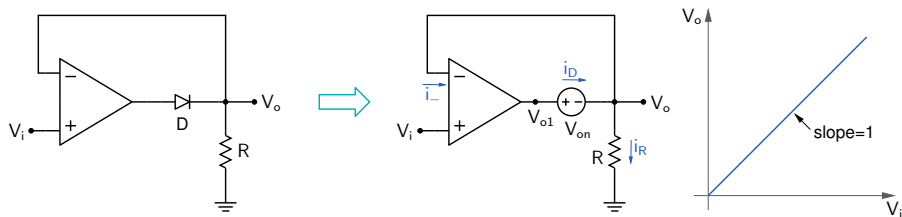

Consider two cases:

- (i) D is conducting: The feedback loop is closed, and the circuit looks like (except for the diode drop) the buffer we have seen earlier.


Since the input current $i_- \approx 0$, $i_R = i_D$.

$$V_+ - V_- = \frac{V_{o1}}{A_V} = \frac{V_o + 0.7 \text{ V}}{A_V} \approx 0 \text{ V} \rightarrow V_o = V_- \approx V_+ = V_i.$$


This situation arises only if $i_D > 0$ (since the diode can only conduct in the forward direction), i.e., $i_R > 0 \rightarrow V_o = i_R R > 0$, and therefore $V_i = V_o > 0 \text{ V}$.

Note: V_{on} does not appear in the graph.

Half-wave precision rectifier

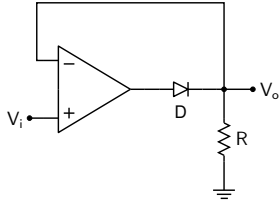


Half-wave precision rectifier

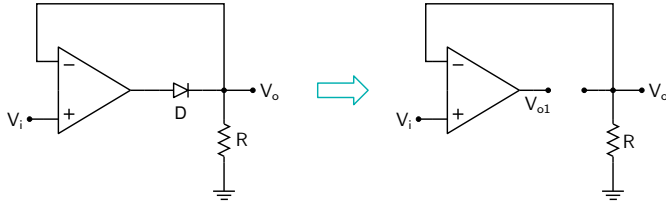

(ii) D is not conducting $\rightarrow V_o = 0\text{ V}$.

Half-wave precision rectifier

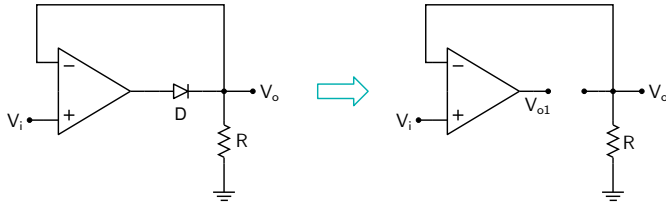


(ii) D is not conducting $\rightarrow V_o = 0\text{ V}$.

What about V_{o1} ?

Since the op-amp is now in the open-loop configuration, a very small V_i is enough to drive it to saturation.

Half-wave precision rectifier

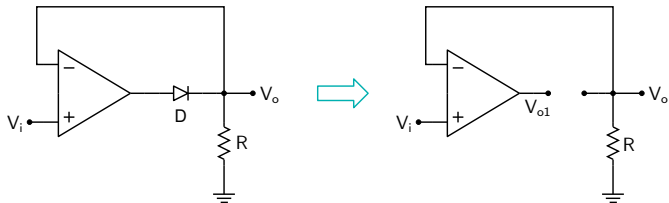


(ii) D is not conducting $\rightarrow V_o = 0\text{ V}$.

What about V_{o1} ?

Since the op-amp is now in the open-loop configuration, a very small V_i is enough to drive it to saturation.

Note that Case (ii) occurs when $V_i < 0\text{ V}$ (we have already looked at $V_i > 0$). Since $V_+ - V_- = V_i - 0 = V_i$ is negative, V_{o1} is driven to $-V_{\text{sat}}$.

Half-wave precision rectifier

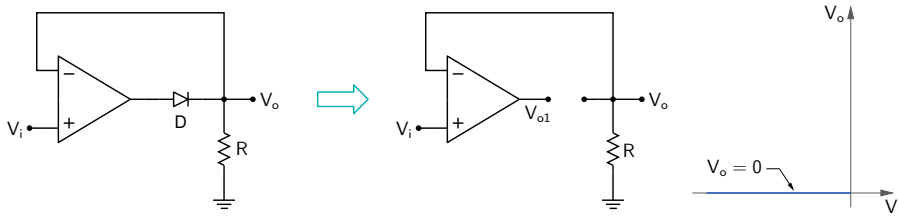


(ii) D is not conducting $\rightarrow V_o = 0\text{ V}$.

What about V_{o1} ?


Since the op-amp is now in the open-loop configuration, a very small V_i is enough to drive it to saturation.

Note that Case (ii) occurs when $V_i < 0\text{ V}$ (we have already looked at $V_i > 0$). Since $V_+ - V_- = V_i - 0 = V_i$ is negative, V_{o1} is driven to $-V_{\text{sat}}$.

Half-wave precision rectifier

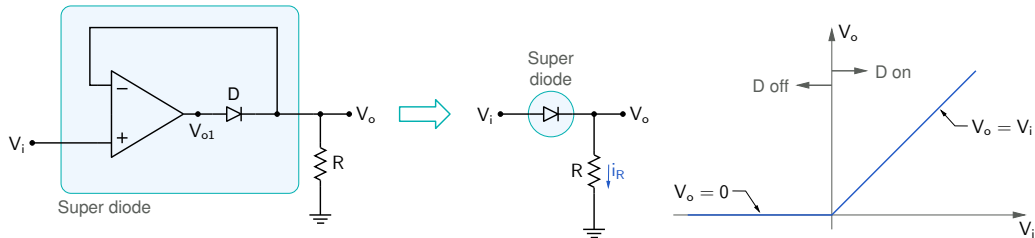


Half-wave precision rectifier

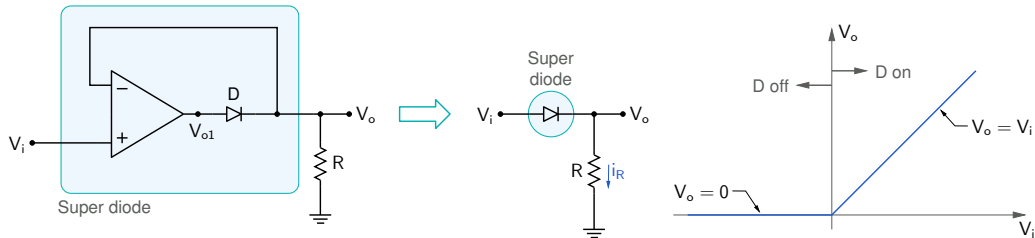


* The circuit is called "super diode" (an ideal diode with $V_{on} = 0\text{ V}$).

Half-wave precision rectifier

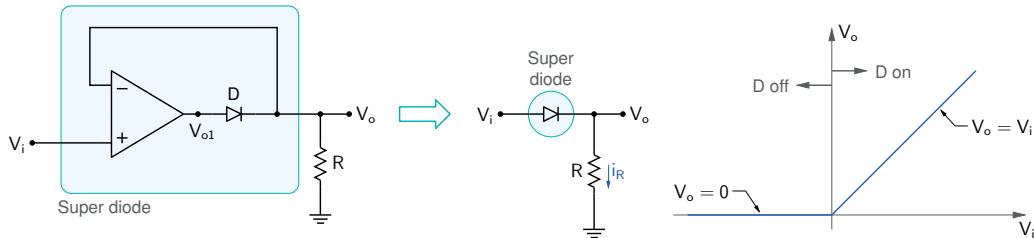


- * The circuit is called “super diode” (an ideal diode with $V_{on} = 0\text{ V}$).
- * When D conducts, the op-amp operates in the linear region, and we have $V_+ \approx V_-$.

Half-wave precision rectifier

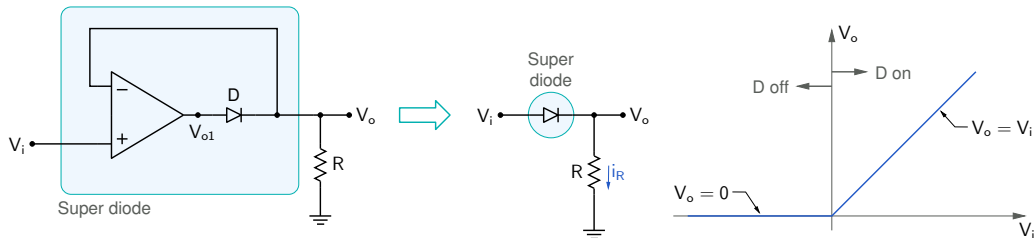

- * The circuit is called “super diode” (an ideal diode with $V_{on} = 0\text{ V}$).
- * When D conducts, the op-amp operates in the linear region, and we have $V_+ \approx V_-$.
- * When D is off, the op-amp operates in the saturation region, $V_- = 0$, $V_+ = V_i$, and $V_{o1} = -V_{sat}$.


Half-wave precision rectifier

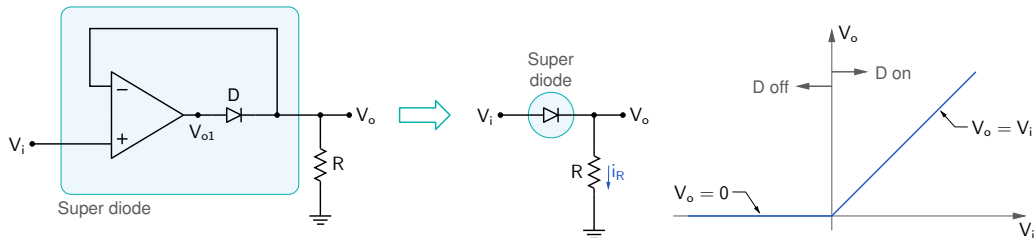

- * The circuit is called “super diode” (an ideal diode with $V_{on} = 0\text{ V}$).
- * When D conducts, the op-amp operates in the linear region, and we have $V_+ \approx V_-$.
- * When D is off, the op-amp operates in the saturation region, $V_- = 0$, $V_+ = V_i$, and $V_{o1} = -V_{sat}$.
- * Where does i_R come from?

$A = 1$
 $M = 0.3$
 $f_c = 200 \text{ kHz}$
 $f_m = 10 \text{ kHz}$

Application: AM demodulation

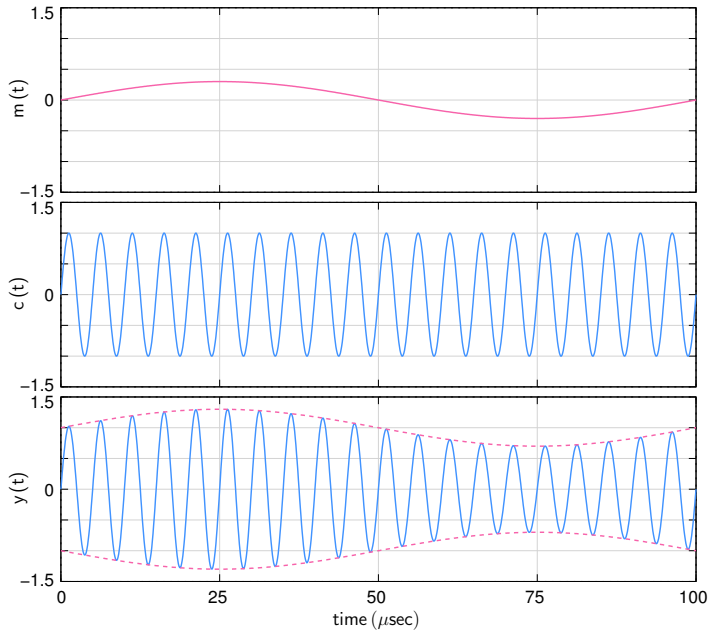


$$\begin{aligned} A &= 1 \\ M &= 0.3 \\ f_c &= 200 \text{ kHz} \\ f_m &= 10 \text{ kHz} \end{aligned}$$

Application: AM demodulation

Carrier wave:

$$c(t) = A \sin(2\pi f_c t)$$

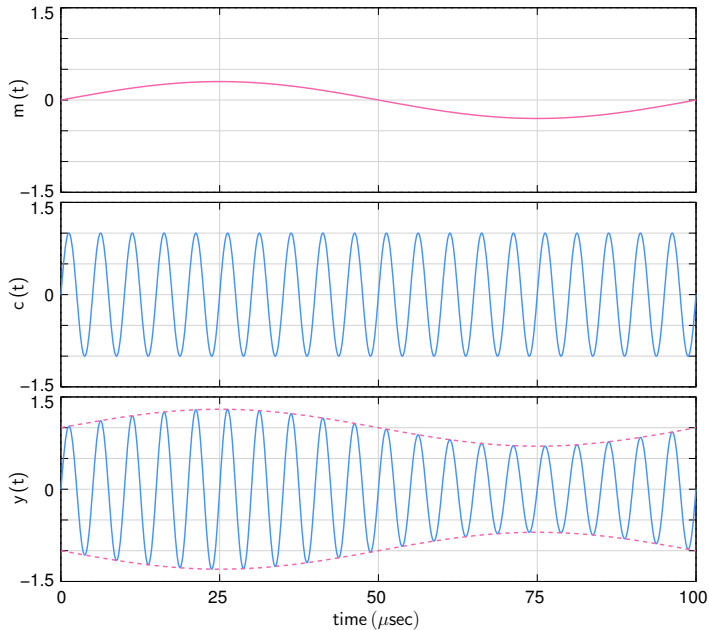

$$\begin{aligned} A &= 1 \\ M &= 0.3 \\ f_c &= 200 \text{ kHz} \\ f_m &= 10 \text{ kHz} \end{aligned}$$


Application: AM demodulation

Carrier wave:

$$c(t) = A \sin(2\pi f_c t)$$

Signal (e.g., audio):

$$m(t) = M \sin(2\pi f_m t + \phi)$$

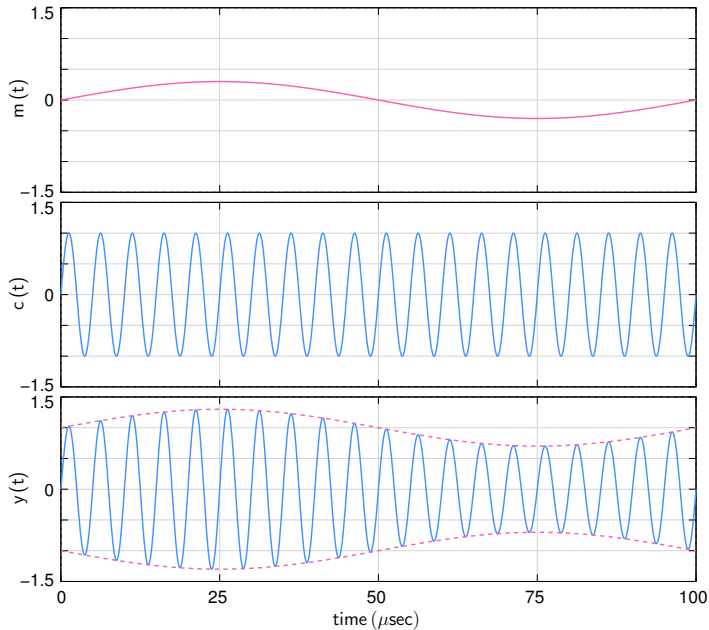

$$\begin{aligned} A &= 1 \\ M &= 0.3 \\ f_c &= 200 \text{ kHz} \\ f_m &= 10 \text{ kHz} \end{aligned}$$

Application: AM demodulation

Carrier wave:

$$c(t) = A \sin(2\pi f_c t)$$


Signal (e.g., audio):

$$m(t) = M \sin(2\pi f_m t + \phi)$$

AM wave:

$$y(t) = [1 + m(t)] c(t)$$

(Assume $M < 1$)

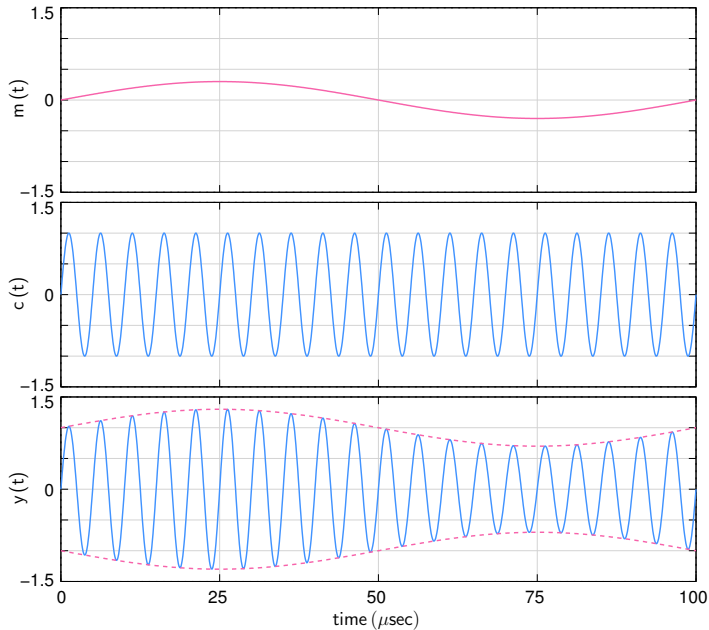

$$\begin{aligned} A &= 1 \\ M &= 0.3 \\ f_c &= 200 \text{ kHz} \\ f_m &= 10 \text{ kHz} \end{aligned}$$

Application: AM demodulation

Carrier wave:

$$c(t) = A \sin(2\pi f_c t)$$

Signal (e.g., audio):

$$m(t) = M \sin(2\pi f_m t + \phi)$$

AM wave:


$$y(t) = [1 + m(t)] c(t)$$

(Assume $M < 1$)


e.g., Vividh Bharati:

$$f_c = 1188 \text{ kHz},$$


$$f_m \simeq 10 \text{ kHz (audio).}$$

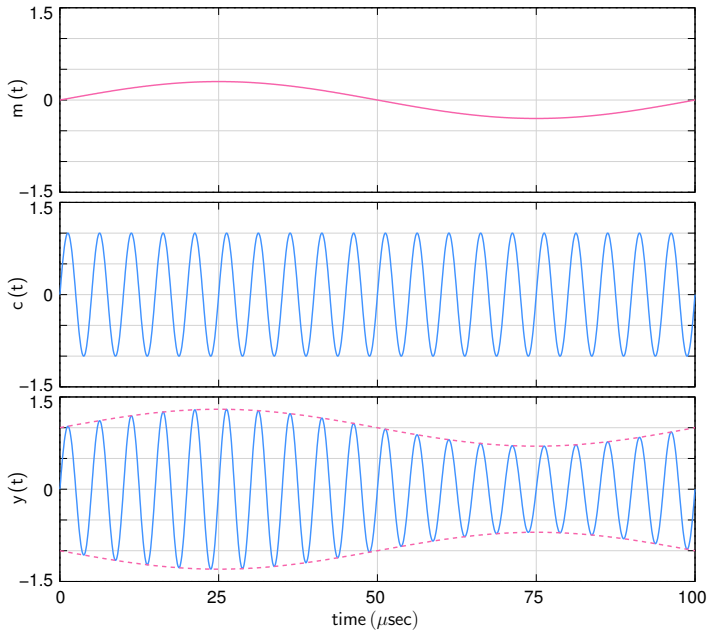

AM demodulation using a peak detector

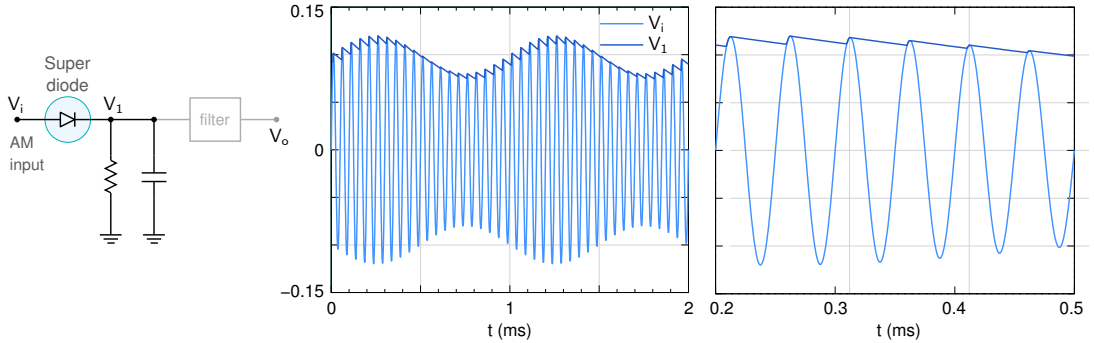


AM demodulation using a peak detector

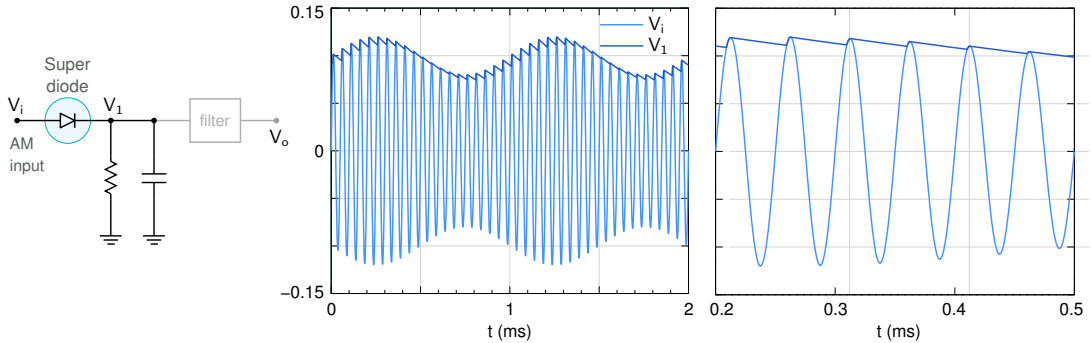


* charging through super diode, discharging through resistor

AM demodulation using a peak detector

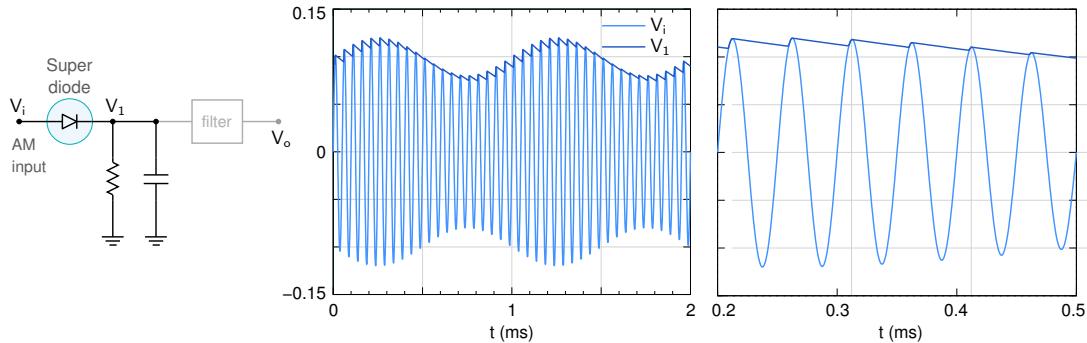

- * charging through super diode, discharging through resistor
- * The time constant (RC) needs to be carefully selected.





AM demodulation using a peak detector

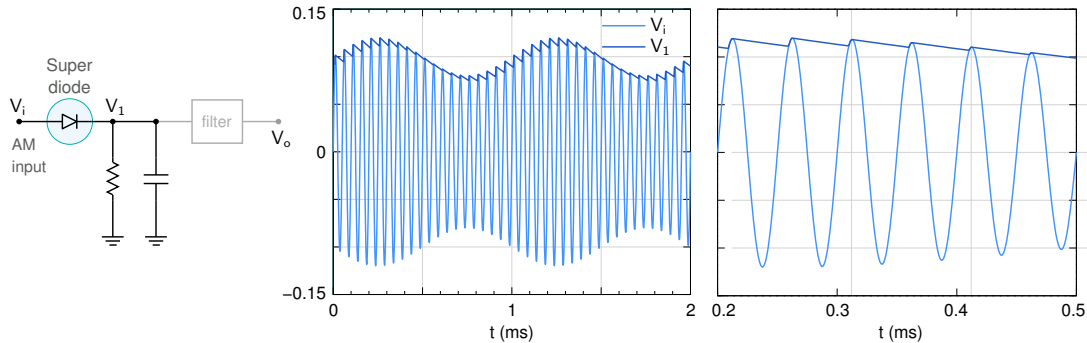

- * charging through super diode, discharging through resistor
- * The time constant (RC) needs to be carefully selected.





SEQUEL file: `super_diode.sqproj`

Clipping and clamping

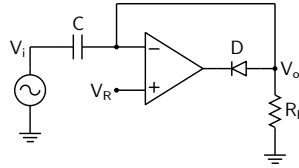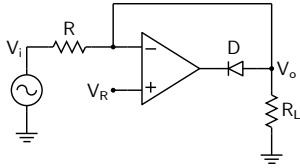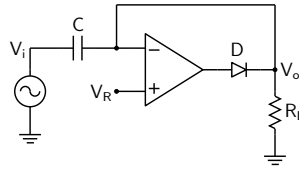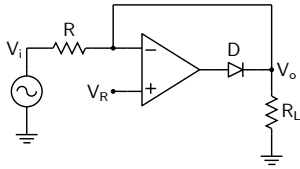


* What is the function provided by each circuit?


Clipping and clamping

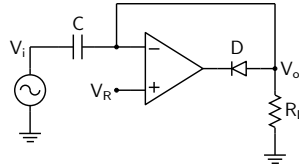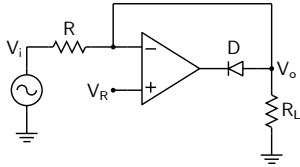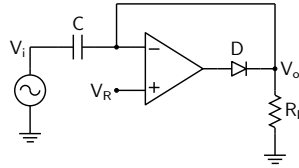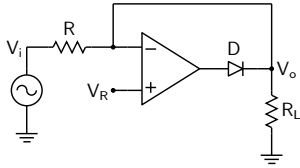

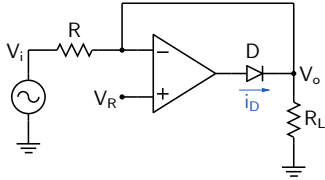- * What is the function provided by each circuit?
- * Verify with simulation (and in the lab).




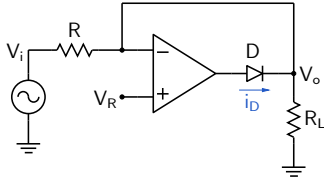When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.



When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

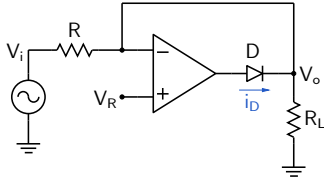
$$\text{KCL: } i_D = \frac{V_R}{R_L} + \frac{V_R - V_i}{R}.$$



When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D = \frac{V_R}{R_L} + \frac{V_R - V_i}{R}.$$
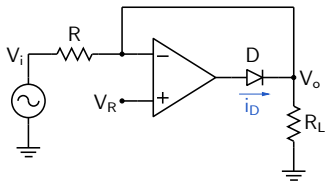
$$\text{Since } i_D > 0, \quad V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) > \frac{V_i}{R} \rightarrow V_i < V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$





When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D = \frac{V_R}{R_L} + \frac{V_R - V_i}{R}.$$

$$\text{Since } i_D > 0, \quad V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) > \frac{V_i}{R} \rightarrow V_i < V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$
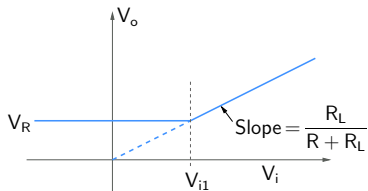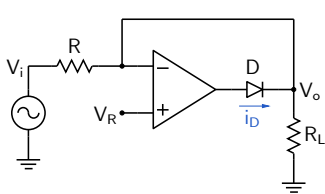
$$\text{For } V_i > V_{i1}, D \text{ does not conduct} \rightarrow V_o = \frac{R_L}{R + R_L} V_i.$$





When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D = \frac{V_R}{R_L} + \frac{V_R - V_i}{R}.$$

$$\text{Since } i_D > 0, \quad V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) > \frac{V_i}{R} \rightarrow V_i < V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$
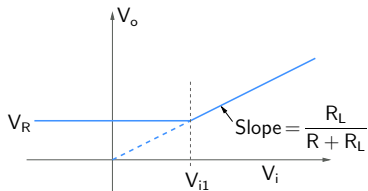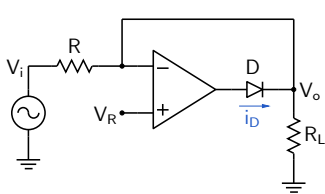
$$\text{For } V_i > V_{i1}, D \text{ does not conduct} \rightarrow V_o = \frac{R_L}{R + R_L} V_i.$$




When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D = \frac{V_R}{R_L} + \frac{V_R - V_i}{R}.$$


$$\text{Since } i_D > 0, \quad V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) > \frac{V_i}{R} \rightarrow V_i < V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$

$$\text{For } V_i > V_{i1}, D \text{ does not conduct} \rightarrow V_o = \frac{R_L}{R + R_L} V_i.$$

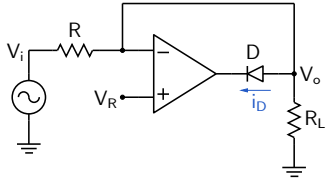If $R_L \gg R$, $V_{i1} = R$, and slope = 1 for $V_i > V_{i1}$.




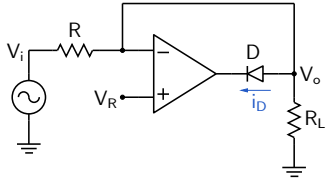When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.



When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

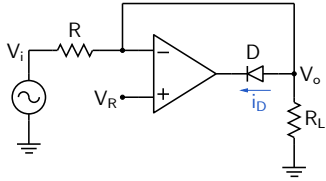
$$\text{KCL: } i_D + \frac{V_R}{R_L} + \frac{V_R - V_i}{R} = 0.$$



When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D + \frac{V_R}{R_L} + \frac{V_R - V_i}{R} = 0.$$
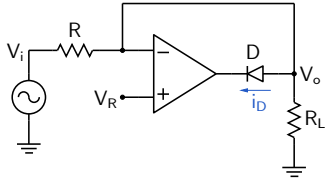
$$\text{Since } i_D > 0, \quad -V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) + \frac{V_i}{R} > 0 \rightarrow V_i > V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$





When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D + \frac{V_R}{R_L} + \frac{V_R - V_i}{R} = 0.$$

$$\text{Since } i_D > 0, -V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) + \frac{V_i}{R} > 0 \rightarrow V_i > V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$
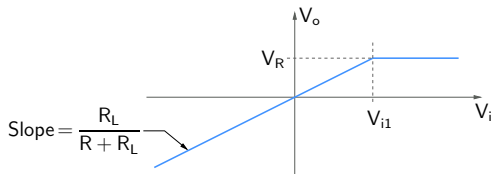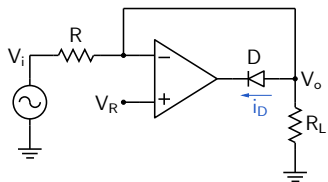
$$\text{For } V_i < V_{i1}, D \text{ does not conduct} \rightarrow V_o = \frac{R_L}{R + R_L} V_i.$$





When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D + \frac{V_R}{R_L} + \frac{V_R - V_i}{R} = 0.$$

$$\text{Since } i_D > 0, -V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) + \frac{V_i}{R} > 0 \rightarrow V_i > V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$
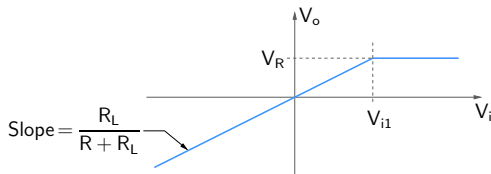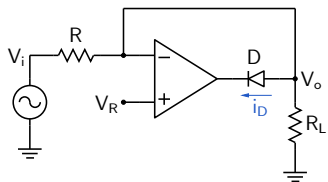
$$\text{For } V_i < V_{i1}, D \text{ does not conduct} \rightarrow V_o = \frac{R_L}{R + R_L} V_i.$$




When D conducts, feedback path is closed $\rightarrow V_- \approx V_+ = V_R \rightarrow V_o = V_R$.

$$\text{KCL: } i_D + \frac{V_R}{R_L} + \frac{V_R - V_i}{R} = 0.$$

$$\text{Since } i_D > 0, -V_R \left(\frac{1}{R_L} + \frac{1}{R} \right) + \frac{V_i}{R} > 0 \rightarrow V_i > V_R \left(\frac{R + R_L}{R_L} \right) \equiv V_{i1}.$$


$$\text{For } V_i < V_{i1}, D \text{ does not conduct} \rightarrow V_o = \frac{R_L}{R + R_L} V_i.$$

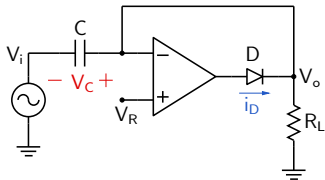If $R_L \gg R$, $V_{i1} = R$, and slope = 1 for $V_i < V_{i1}$.



Time constant for the discharging process is $R_L C$.

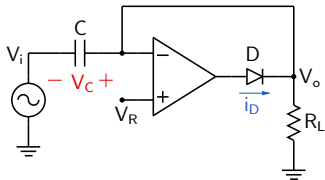Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).




Time constant for the discharging process is $R_L C$.

Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).

When D conducts, $V_- \approx V_R$, and $V_C(t) = V_R - V_m \sin \omega t$.

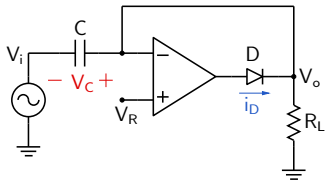$\rightarrow V_C^{\max} = V_R - (-V_m) = V_R + V_m$.




Time constant for the discharging process is $R_L C$.

Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).

When D conducts, $V_- \approx V_R$, and $V_C(t) = V_R - V_m \sin \omega t$.

$\rightarrow V_C^{\max} = V_R - (-V_m) = V_R + V_m$.

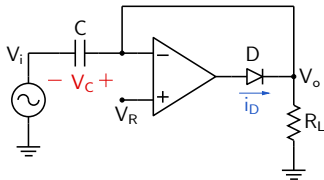In steady state, V_C remains equal to $V_C^{\max} \rightarrow V_o(t) = V_i(t) + V_C^{\max} = V_m \sin \omega t + V_R + V_m$.



Time constant for the discharging process is $R_L C$.



Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).

When D conducts, $V_- \approx V_R$, and $V_C(t) = V_R - V_m \sin \omega t$.

$\rightarrow V_C^{\max} = V_R - (-V_m) = V_R + V_m$.

In steady state, V_C remains equal to $V_C^{\max} \rightarrow V_o(t) = V_i(t) + V_C^{\max} = V_m \sin \omega t + V_R + V_m$.

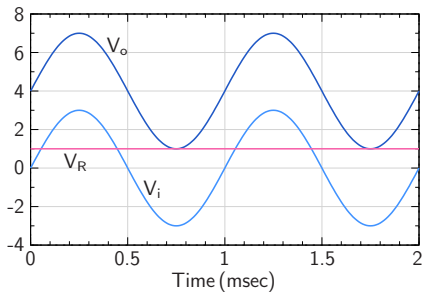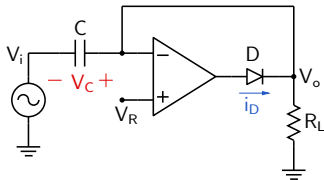Note: V_{on} of the diode does not appear in the expression for $V_o(t)$.



Time constant for the discharging process is $R_L C$.


Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).

When D conducts, $V_- \approx V_R$, and $V_C(t) = V_R - V_m \sin \omega t$.

$$\rightarrow V_C^{\max} = V_R - (-V_m) = V_R + V_m.$$


In steady state, V_C remains equal to $V_C^{\max} \rightarrow V_o(t) = V_i(t) + V_C^{\max} = V_m \sin \omega t + V_R + V_m$.

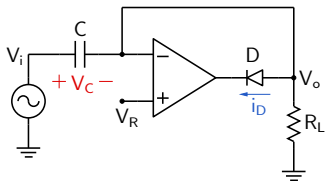Note: V_{on} of the diode does not appear in the expression for $V_o(t)$.



Time constant for the discharging process is $R_L C$.

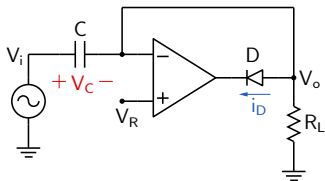Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).




Time constant for the discharging process is $R_L C$.

Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).

When D conducts, $V_- \approx V_R$, and $V_C(t) = V_m \sin \omega t - V_R$.

$\rightarrow V_C^{\max} = V_m - V_R$.

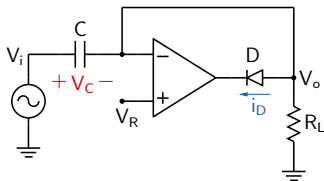


Time constant for the discharging process is $R_L C$.

Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).

When D conducts, $V_- \approx V_R$, and $V_C(t) = V_m \sin \omega t - V_R$.

$\rightarrow V_C^{\max} = V_m - V_R$.

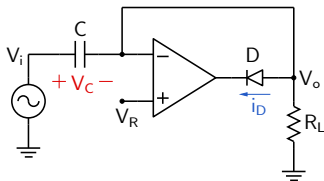In steady state, V_C remains equal to $V_C^{\max} \rightarrow V_o(t) = V_i(t) - V_C^{\max} = V_m \sin \omega t + V_R - V_m$.



Time constant for the discharging process is $R_L C$.



Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).

When D conducts, $V_- \approx V_R$, and $V_C(t) = V_m \sin \omega t - V_R$.

$\rightarrow V_C^{\max} = V_m - V_R$.

In steady state, V_C remains equal to $V_C^{\max} \rightarrow V_o(t) = V_i(t) - V_C^{\max} = V_m \sin \omega t + V_R - V_m$.

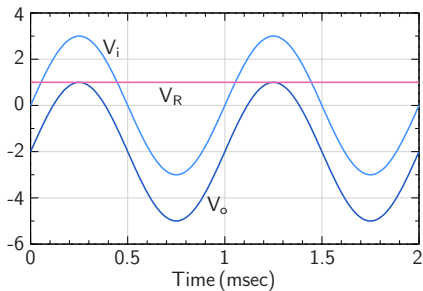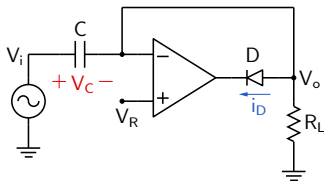Note: V_{on} of the diode does not appear in the expression for $V_o(t)$.



Time constant for the discharging process is $R_L C$.

Assume $R_L C \gg T \rightarrow V_C$ can only increase (in one cycle).




When D conducts, $V_- \approx V_R$, and $V_C(t) = V_m \sin \omega t - V_R$.

$\rightarrow V_C^{\max} = V_m - V_R$.


In steady state, V_C remains equal to $V_C^{\max} \rightarrow V_o(t) = V_i(t) - V_C^{\max} = V_m \sin \omega t + V_R - V_m$.

Note: V_{on} of the diode does not appear in the expression for $V_o(t)$.


Half-wave precision rectifier

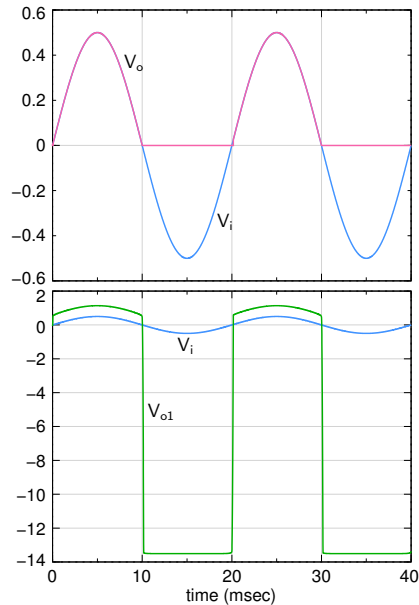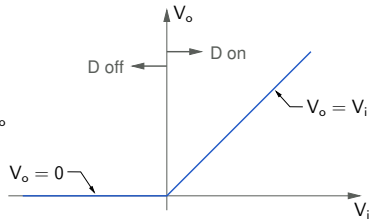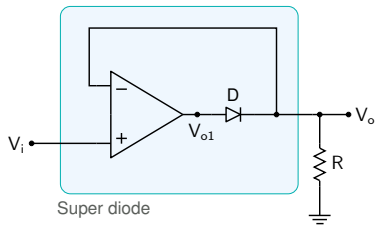


Half-wave precision rectifier

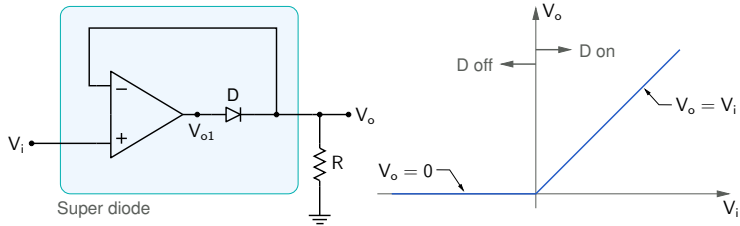

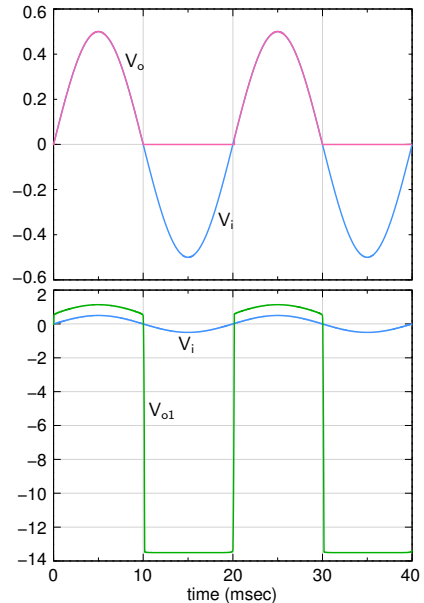
* When $V_i > 0$, the op-amp operates in the linear region, and $V_{o1} = V_o + V_{on}$.




Half-wave precision rectifier

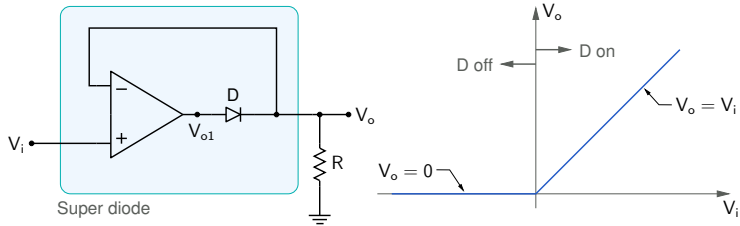

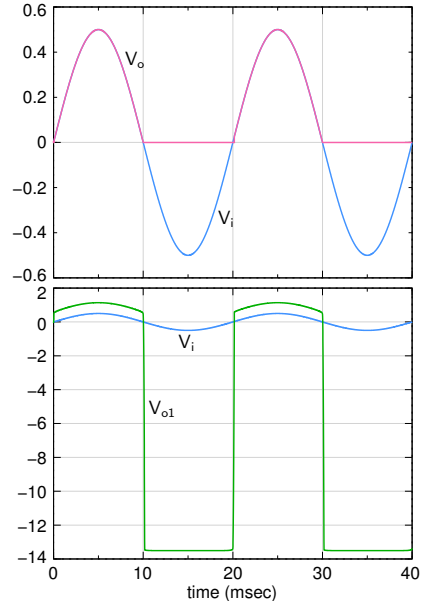
- * When $V_i > 0$, the op-amp operates in the linear region, and $V_{o1} = V_o + V_{on}$.
- * When $V_i < 0$, the op-amp operates in the open-loop configuration, leading to saturation, and $V_{o1} = -V_{sat}$.




Half-wave precision rectifier

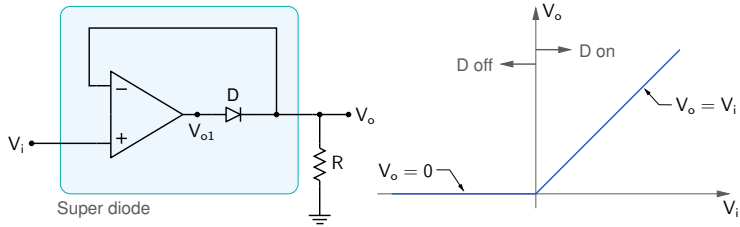

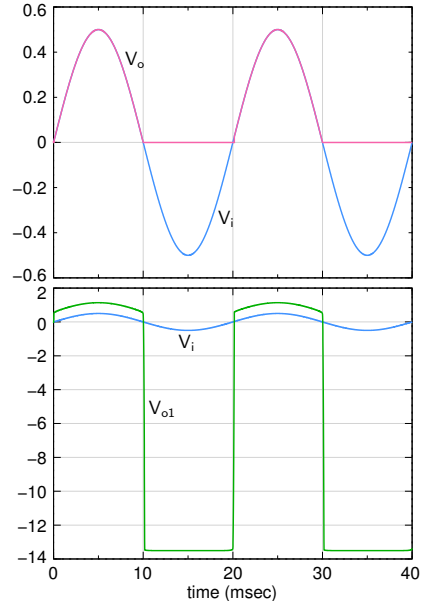- * When $V_i > 0$, the op-amp operates in the linear region, and $V_{o1} = V_o + V_{on}$.
- * When $V_i < 0$, the op-amp operates in the open-loop configuration, leading to saturation, and $V_{o1} = -V_{sat}$.
- * The $V_i < 0$ to $V_i > 0$ transition requires the op-amp to come out of saturation. This is a relatively slow process and is limited by the op-amp slew rate.




Half-wave precision rectifier

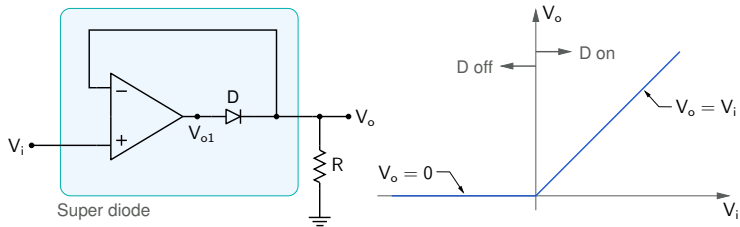


- * When $V_i > 0$, the op-amp operates in the linear region, and $V_{o1} = V_o + V_{on}$.
- * When $V_i < 0$, the op-amp operates in the open-loop configuration, leading to saturation, and $V_{o1} = -V_{sat}$.
- * The $V_i < 0$ to $V_i > 0$ transition requires the op-amp to come out of saturation. This is a relatively slow process and is limited by the op-amp slew rate.

SEQUEL file: ee101_super_diode.1.sqproj



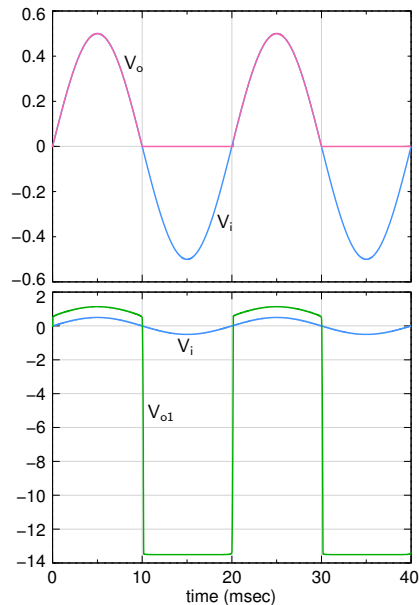


Half-wave precision rectifier

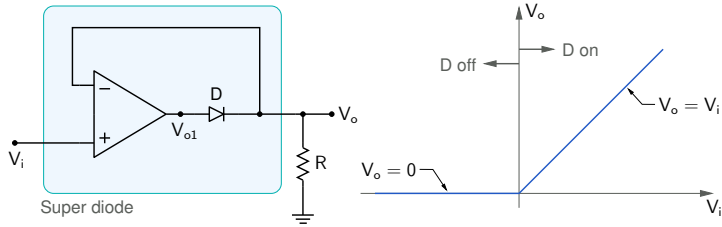




- * The time taken by the op-amp to come out of saturation can be neglected at low signal frequencies.

Half-wave precision rectifier

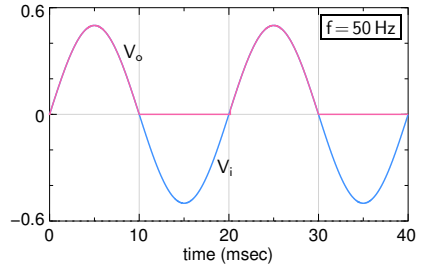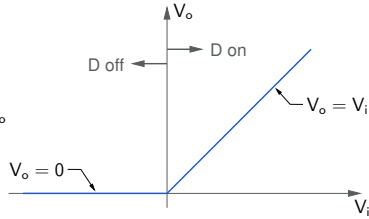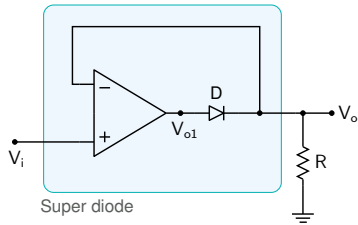





- * The time taken by the op-amp to come out of saturation can be neglected at low signal frequencies.

Half-wave precision rectifier

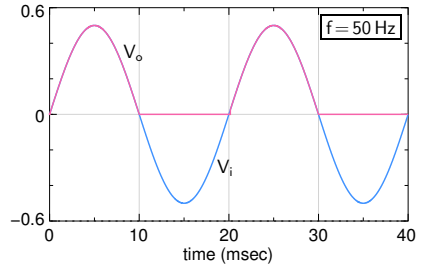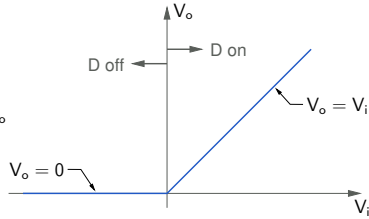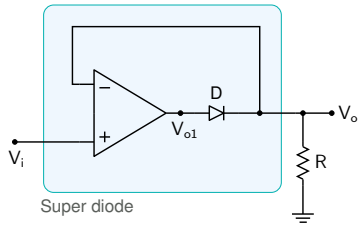




- * The time taken by the op-amp to come out of saturation can be neglected at low signal frequencies.
- * At high signal frequencies, it leads to distortion in the output waveform.

Half-wave precision rectifier

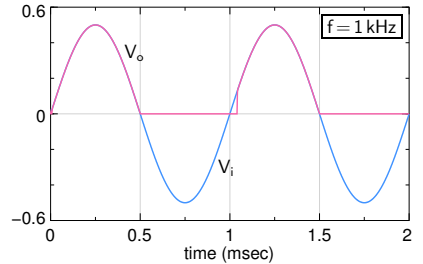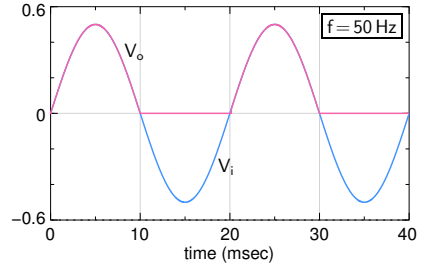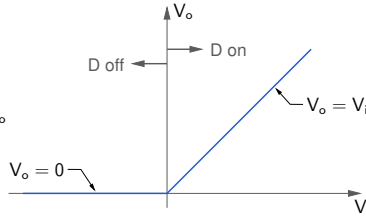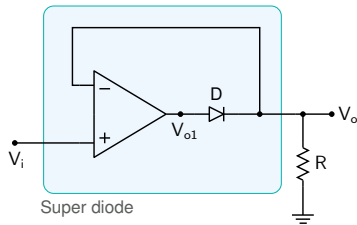


- * The time taken by the op-amp to come out of saturation can be neglected at low signal frequencies.
- * At high signal frequencies, it leads to distortion in the output waveform.


Half-wave precision rectifier

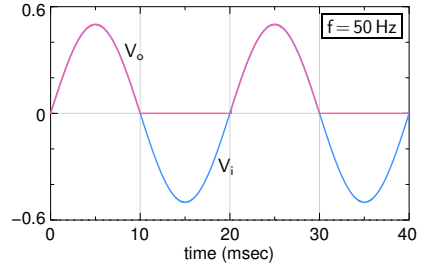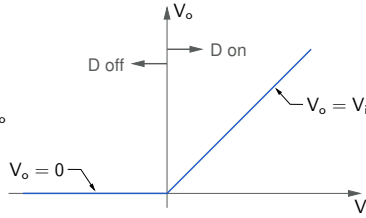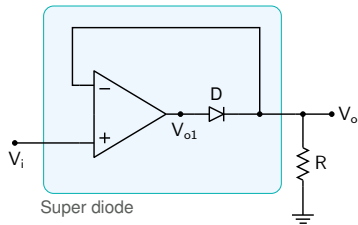

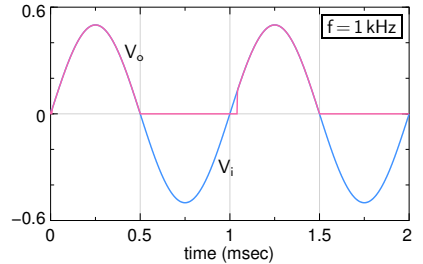
- * The time taken by the op-amp to come out of saturation can be neglected at low signal frequencies.
- * At high signal frequencies, it leads to distortion in the output waveform.
- * Hook up the circuit in the lab, and check it out!



Improved half-wave precision rectifier

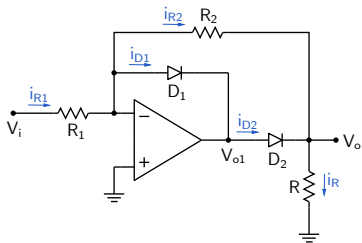


Improved half-wave precision rectifier

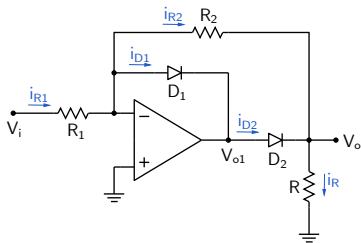

(i) D_1 conducts: $V_- = V_+ = 0\text{ V}$, $V_{o1} = -V_{D1} \approx -0.7\text{ V}$.

Improved half-wave precision rectifier

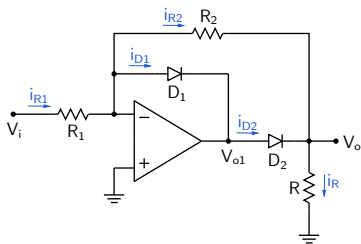


(i) D_1 conducts: $V_- = V_+ = 0\text{ V}$, $V_{o1} = -V_{D1} \approx -0.7\text{ V}$.

D_2 cannot conduct (show that, if it did, KCL is not satisfied at V_o).

$\rightarrow i_{R2} = 0$, $V_o = V_- = 0\text{ V}$.

Improved half-wave precision rectifier

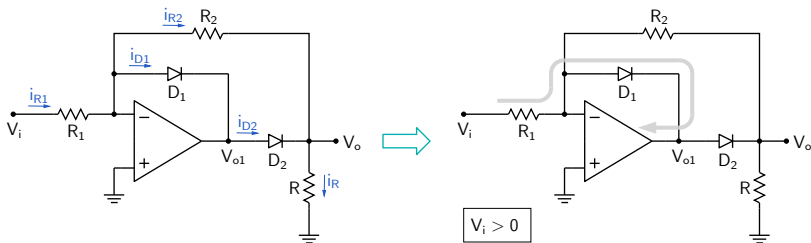


(i) D_1 conducts: $V_- = V_+ = 0\text{ V}$, $V_{o1} = -V_{D1} \approx -0.7\text{ V}$.

D_2 cannot conduct (show that, if it did, KCL is not satisfied at V_o).

$\rightarrow i_{R2} = 0$, $V_o = V_- = 0\text{ V}$.

Improved half-wave precision rectifier

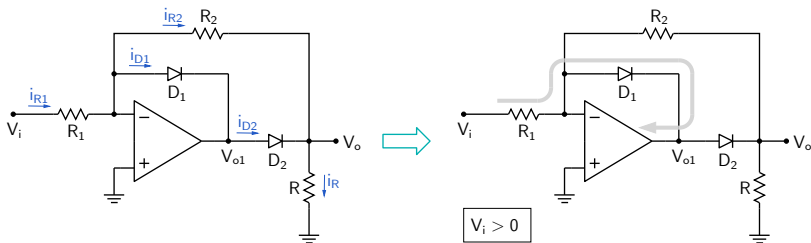


(i) D_1 conducts: $V_- = V_+ = 0\text{ V}$, $V_{o1} = -V_{D1} \approx -0.7\text{ V}$.

D_2 cannot conduct (show that, if it did, KCL is not satisfied at V_o).

$\rightarrow i_{R2} = 0$, $V_o = V_- = 0\text{ V}$.

$i_{R1} = i_{D1}$ which can only be positive $\Rightarrow V_i > 0\text{ V}$.

Improved half-wave precision rectifier

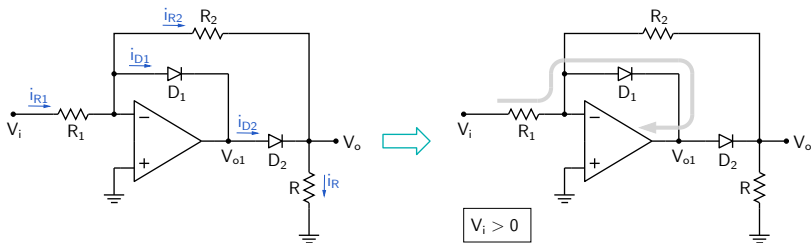

(i) D_1 conducts: $V_- = V_+ = 0\text{ V}$, $V_{o1} = -V_{D1} \approx -0.7\text{ V}$.


D_2 cannot conduct (show that, if it did, KCL is not satisfied at V_o).

$\rightarrow i_{R2} = 0$, $V_o = V_- = 0\text{ V}$.

$i_{R1} = i_{D1}$ which can only be positive $\Rightarrow V_i > 0\text{ V}$.

(ii) D_1 is off; this will happen when $V_i < 0\text{ V}$.

Improved half-wave precision rectifier

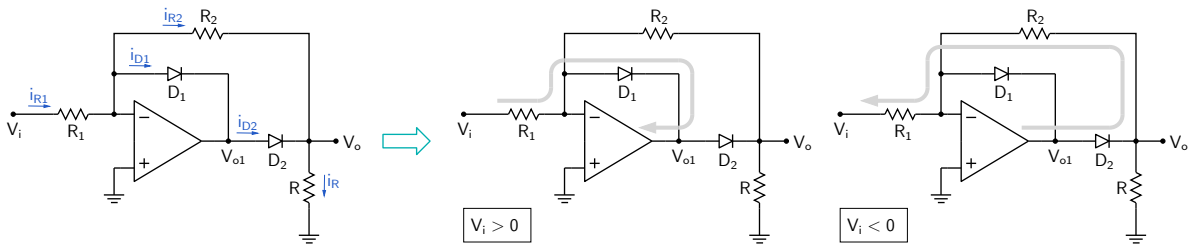

(i) D_1 conducts: $V_- = V_+ = 0\text{ V}$, $V_{o1} = -V_{D1} \approx -0.7\text{ V}$.

D_2 cannot conduct (show that, if it did, KCL is not satisfied at V_o).


$\rightarrow i_{R2} = 0$, $V_o = V_- = 0\text{ V}$.

$i_{R1} = i_{D1}$ which can only be positive $\Rightarrow V_i > 0\text{ V}$.

(ii) D_1 is off; this will happen when $V_i < 0\text{ V}$.

In this case, D_2 conducts and closes the feedback loop through R_2 .

Improved half-wave precision rectifier

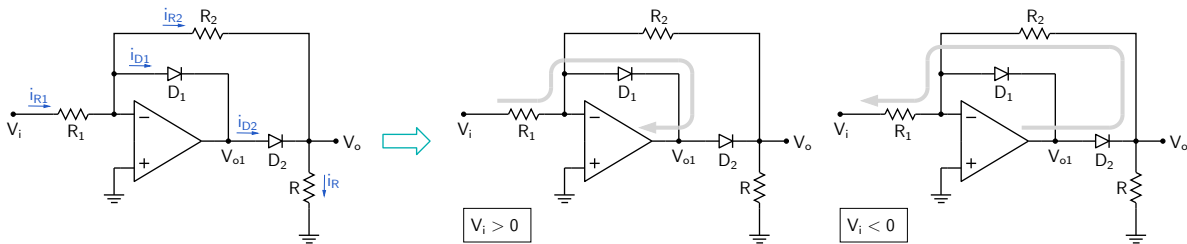

(i) D_1 conducts: $V_- = V_+ = 0 \text{ V}$, $V_{o1} = -V_{D1} \approx -0.7 \text{ V}$.

D_2 cannot conduct (show that, if it did, KCL is not satisfied at V_o).

$\rightarrow i_{R2} = 0$, $V_o = V_- = 0 \text{ V}$.




$i_{R1} = i_{D1}$ which can only be positive $\Rightarrow V_i > 0 \text{ V}$.

(ii) D_1 is off; this will happen when $V_i < 0 \text{ V}$.





In this case, D_2 conducts and closes the feedback loop through R_2 .

$$V_o = V_- + i_{R2}R_2 = 0 + \left(\frac{0 - V_i}{R_1} \right) R_2 = -\frac{R_2}{R_1} V_i.$$





Improved half-wave precision rectifier

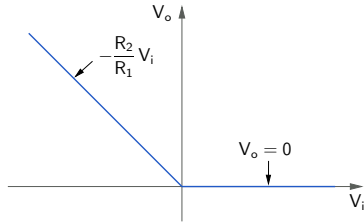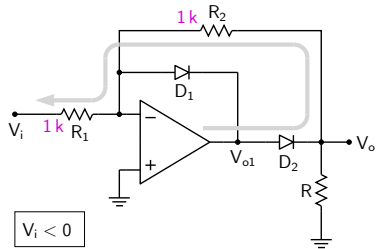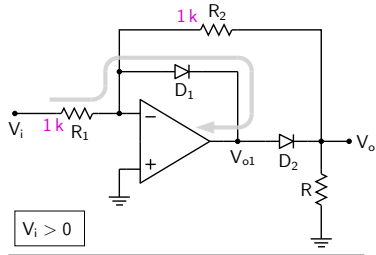





Improved half-wave precision rectifier

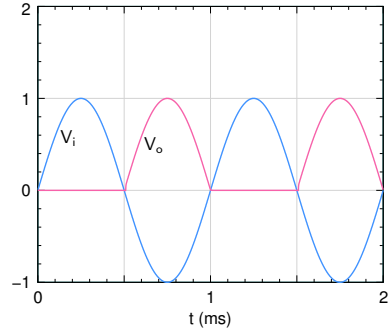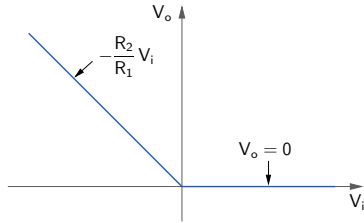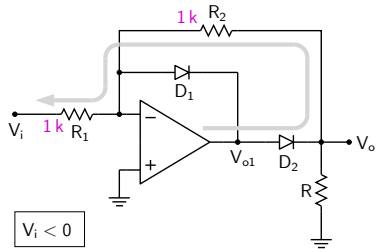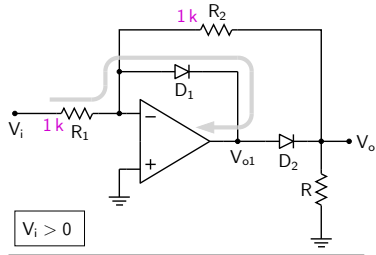

Improved half-wave precision rectifier

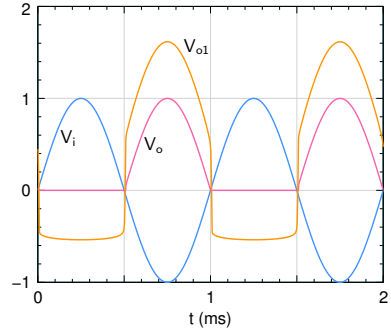
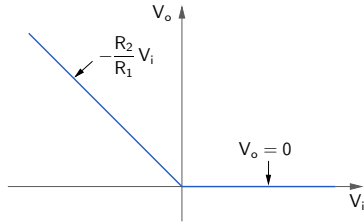
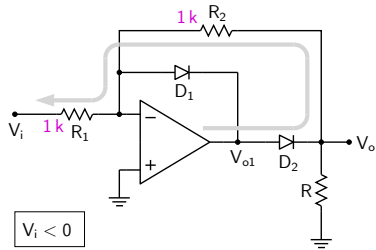
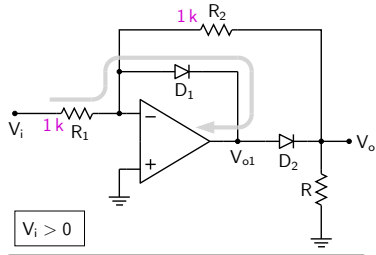


Improved half-wave precision rectifier

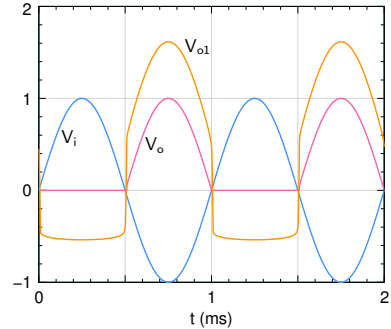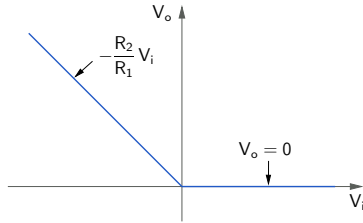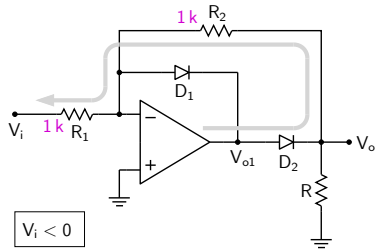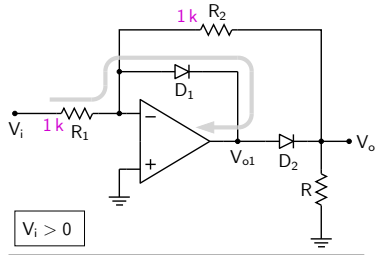

* Note that the op-amp does not enter saturation since a feedback path is available for $V_i > 0$ V and $V_i < 0$ V.



Improved half-wave precision rectifier

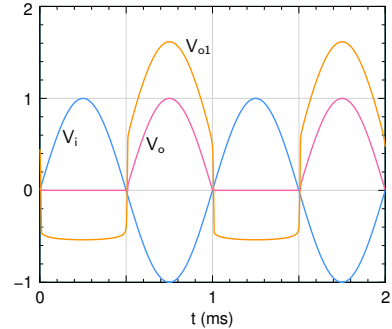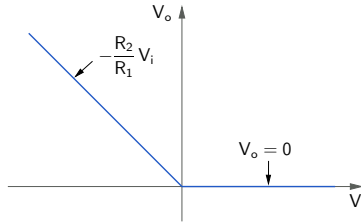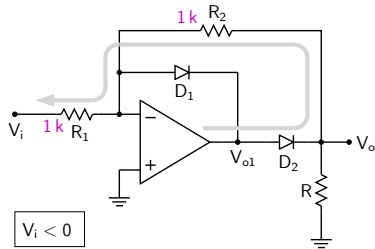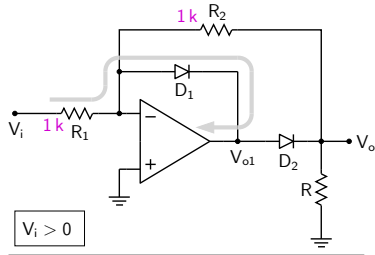

- * Note that the op-amp does not enter saturation since a feedback path is available for $V_i > 0$ V and $V_i < 0$ V.



SEQUEL file: precision_half_wave.sqproj

Improved half-wave precision rectifier

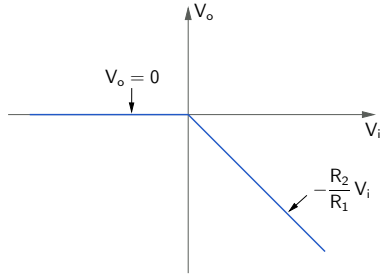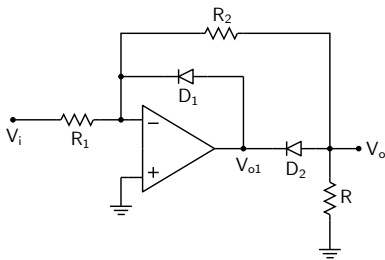

The diodes are now reversed.



Improved half-wave precision rectifier

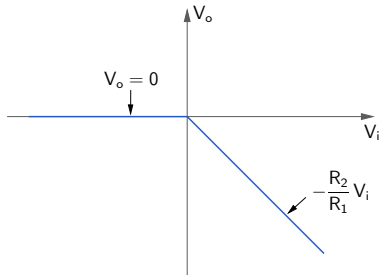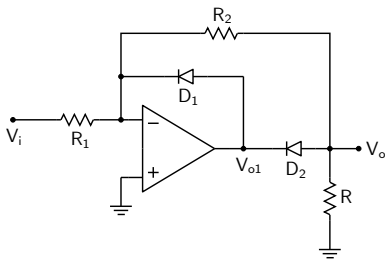

The diodes are now reversed.

By considering two cases: (i) D_1 on, (ii) D_1 off, the V_o versus V_i relationship shown in the figure is obtained (show this).

Improved half-wave precision rectifier

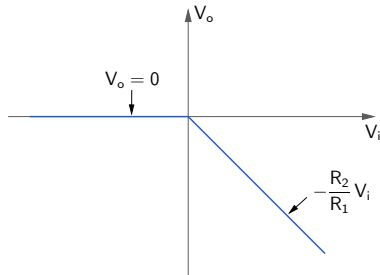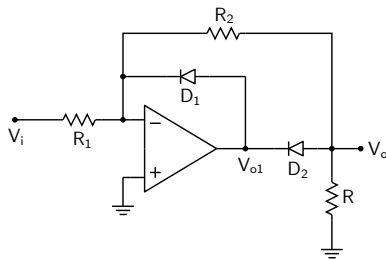


The diodes are now reversed.



By considering two cases: (i) D_1 on, (ii) D_1 off, the V_o versus V_i relationship shown in the figure is obtained (show this).

SEQUEL file: precision_half_wave_2.sqproj

Full-wave precision rectifier



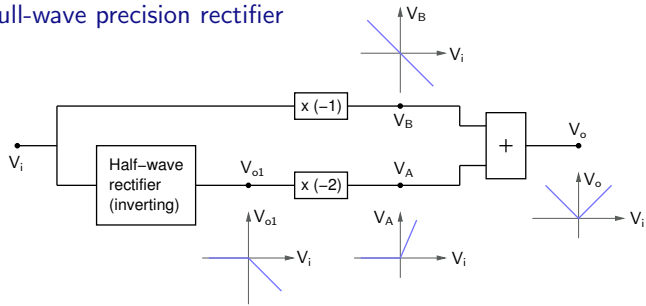


Full-wave precision rectifier

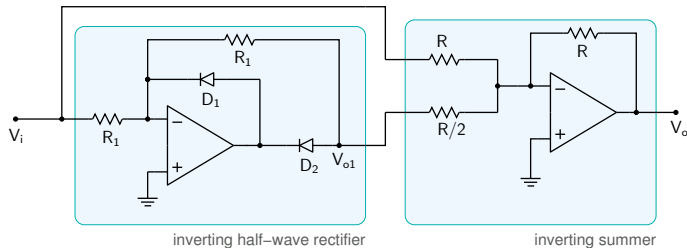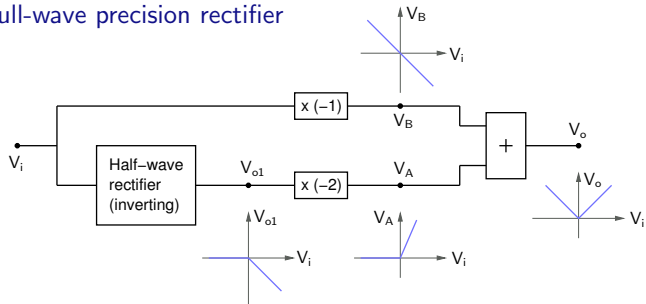


(SEQUEL file: [precision_full_wave.sqproj](#))

Full-wave precision rectifier

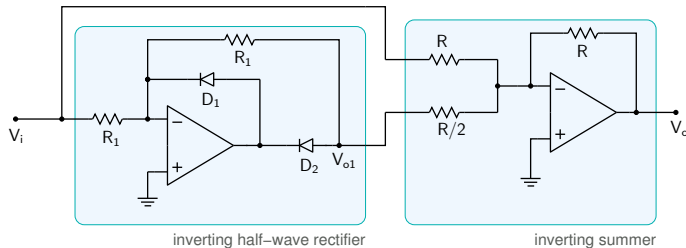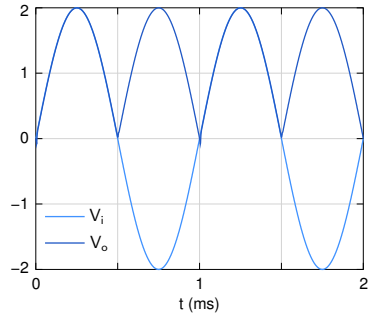
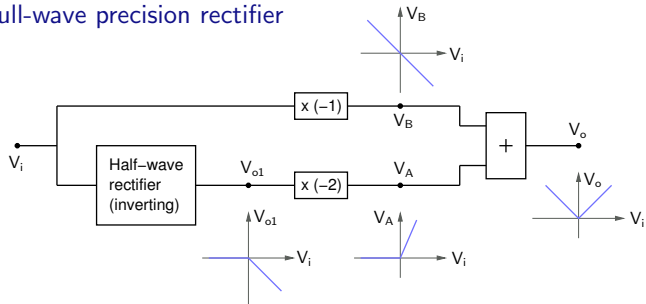


(SEQUEL file: [precision_full_wave.sqproj](#))



Wave shaping with diodes

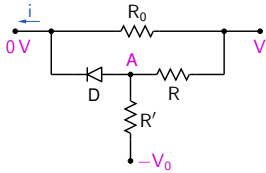

Wave shaping with diodes

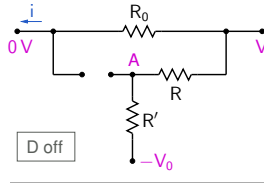
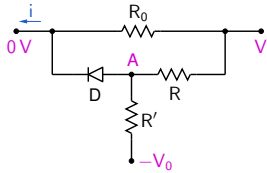


Wave shaping with diodes

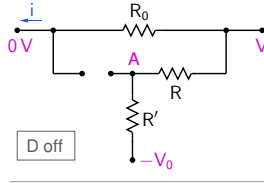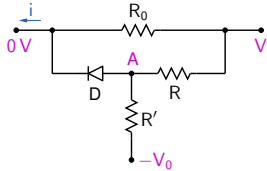

When D is off, $i = \frac{V}{R_0}$, and V_A is (by superposition), $V_A = V \frac{R'}{R + R'} - V_0 \frac{R}{R + R'}$.


Wave shaping with diodes

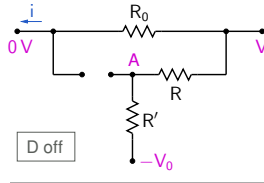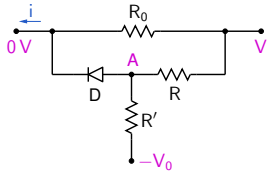

When D is off, $i = \frac{V}{R_0}$, and V_A is (by superposition), $V_A = V \frac{R'}{R + R'} - V_0 \frac{R}{R + R'}$.

For D to turn on, $V_A = V_{\text{on}} \approx 0.7 \text{ V} \rightarrow V \equiv V_{\text{break}} = \frac{R}{R'} (V_0 + V_{\text{on}}) + V_{\text{on}}$.


Wave shaping with diodes

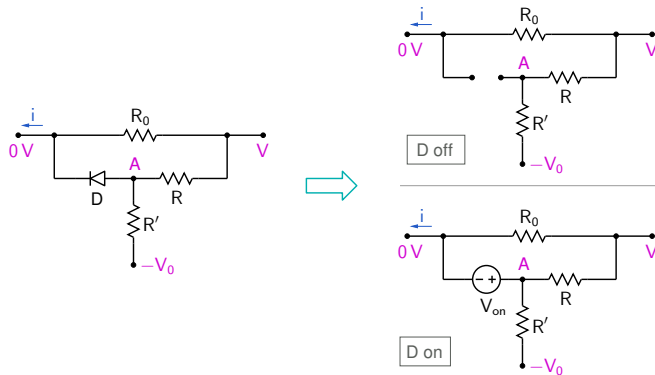

When D is off, $i = \frac{V}{R_0}$, and V_A is (by superposition), $V_A = V \frac{R'}{R + R'} - V_0 \frac{R}{R + R'}$.

For D to turn on, $V_A = V_{on} \approx 0.7V \rightarrow V \equiv V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$.

Wave shaping with diodes

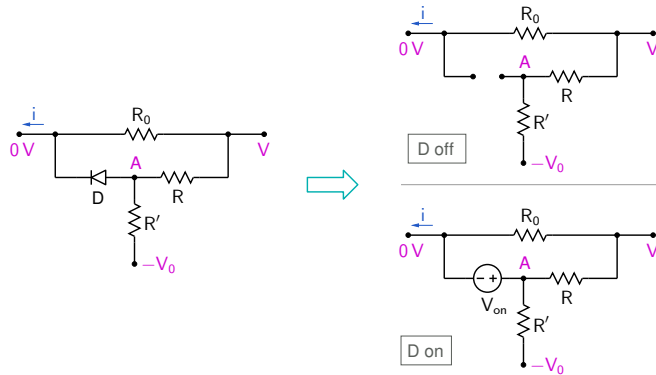


When D is off, $i = \frac{V}{R_0}$, and V_A is (by superposition), $V_A = V \frac{R'}{R + R'} - V_0 \frac{R}{R + R'}$.

For D to turn on, $V_A = V_{on} \approx 0.7V \rightarrow V \equiv V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$.

When D is on, $i = \frac{V}{R_0} + \frac{V - V_{on}}{R} + \frac{-V_0 - V_{on}}{R'} = V \left[\frac{1}{R_0} + \frac{1}{R} \right] + (\text{constant})$

Wave shaping with diodes

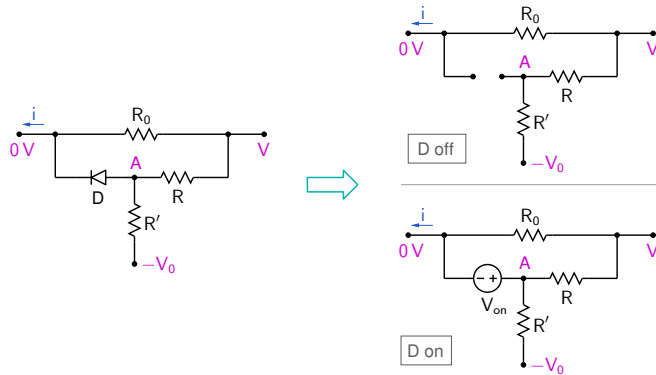


When D is off, $i = \frac{V}{R_0}$, and V_A is (by superposition), $V_A = V \frac{R'}{R + R'} - V_0 \frac{R}{R + R'}$.

For D to turn on, $V_A = V_{on} \approx 0.7V \rightarrow V \equiv V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$.

When D is on, $i = \frac{V}{R_0} + \frac{V - V_{on}}{R} + \frac{-V_0 - V_{on}}{R'} = V \left[\frac{1}{R_0} + \frac{1}{R} \right] + (\text{constant})$

i.e., $V = (R_0 \parallel R) i + (\text{constant})$.

Wave shaping with diodes

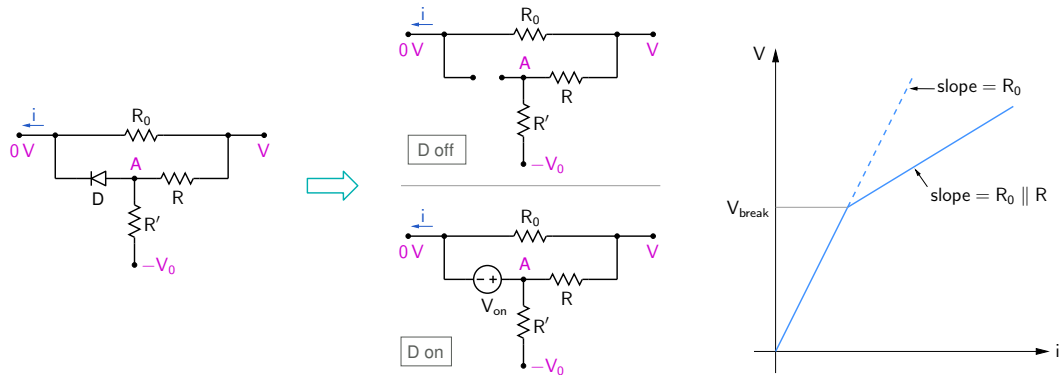


When D is off, $i = \frac{V}{R_0}$, and V_A is (by superposition), $V_A = V \frac{R'}{R + R'} - V_0 \frac{R}{R + R'}$.

For D to turn on, $V_A = V_{on} \approx 0.7 V \rightarrow V \equiv V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$.

When D is on, $i = \frac{V}{R_0} + \frac{V - V_{on}}{R} + \frac{-V_0 - V_{on}}{R'} = V \left[\frac{1}{R_0} + \frac{1}{R} \right] + (\text{constant})$


i.e., $V = (R_0 \parallel R) i + (\text{constant})$.

Wave shaping with diodes

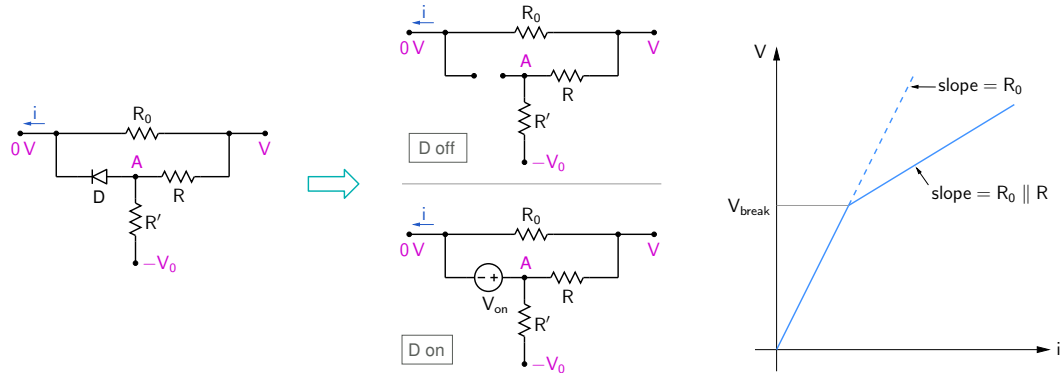

(a) $V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$. (b) When D is on, $V = (R_0 \parallel R) i + (\text{constant})$.


Wave shaping with diodes

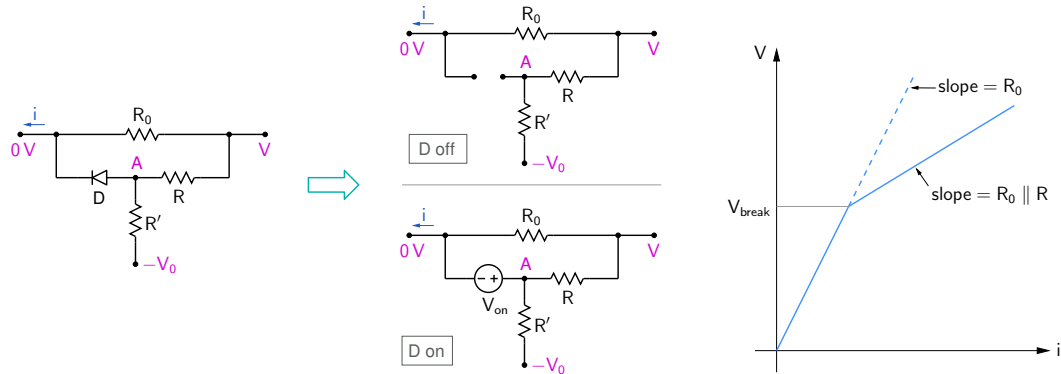

(a) $V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$. (b) When D is on, $V = (R_0 \parallel R) i + (\text{constant})$.


* V_{break} depends on the ratio R/R' .

Wave shaping with diodes

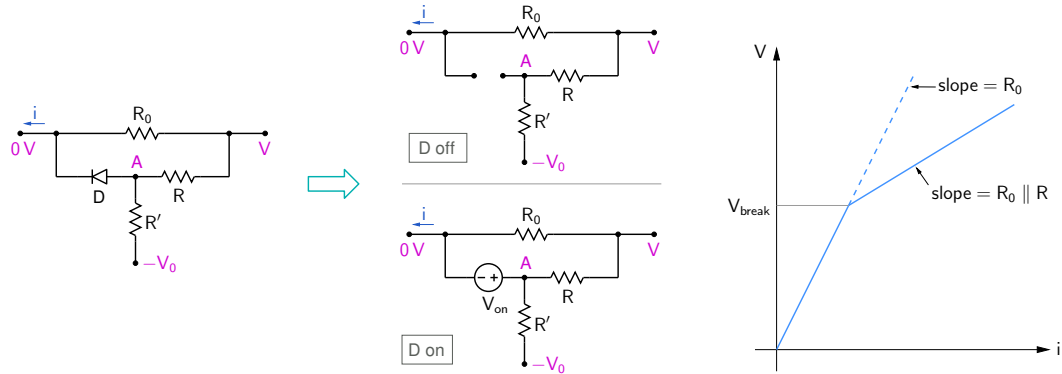

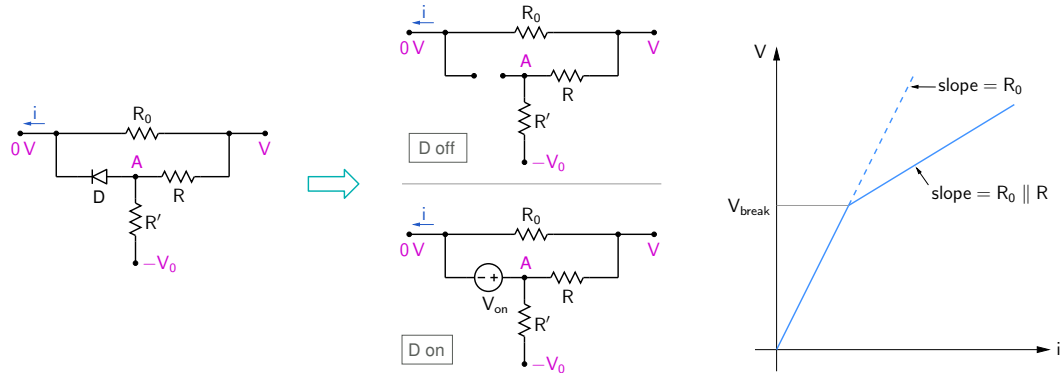
(a) $V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$. (b) When D is on, $V = (R_0 \parallel R) i + (\text{constant})$.

- * V_{break} depends on the ratio R/R' .
- * The slope $R_0 \parallel R$ depends on the resistance values.





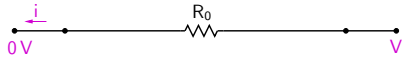(a) $V_{break} = \frac{R}{R'} (V_0 + V_{on}) + V_{on}$. (b) When D is on, $V = (R_0 \parallel R) i + (\text{constant})$.



- * V_{break} depends on the ratio R/R' .
- * The slope $R_0 \parallel R$ depends on the resistance values.
- * Given the break point and the two slopes, the resistance values can be easily determined.





Wave shaping with diodes

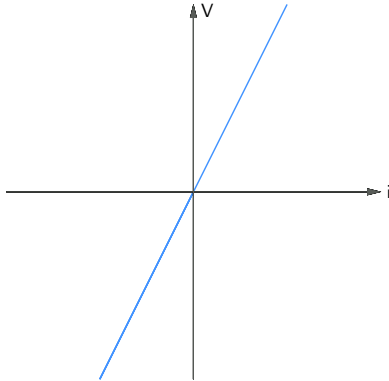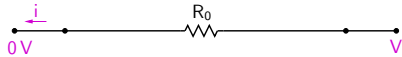



Wave shaping with diodes

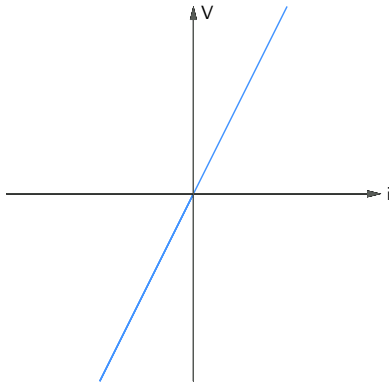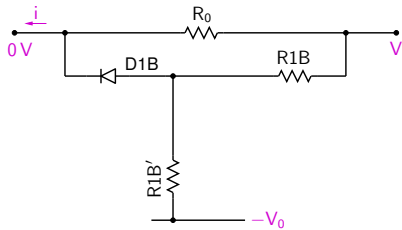



Wave shaping with diodes

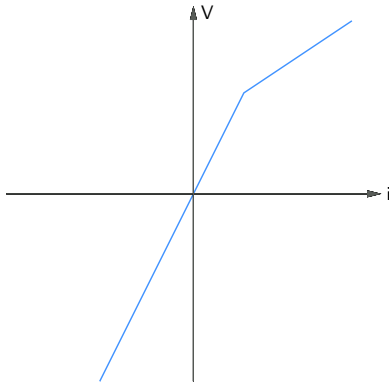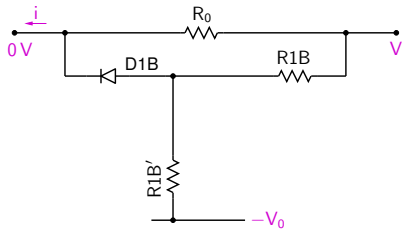



Wave shaping with diodes

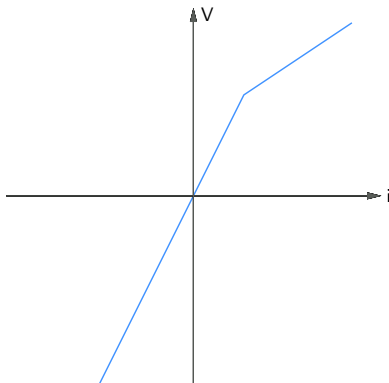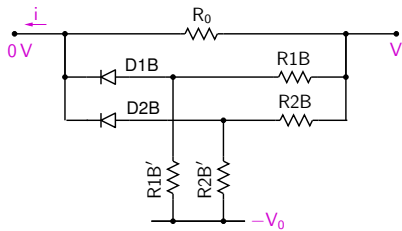



Wave shaping with diodes

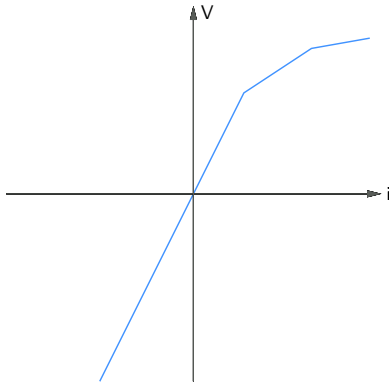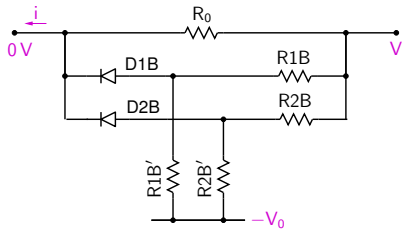



Wave shaping with diodes

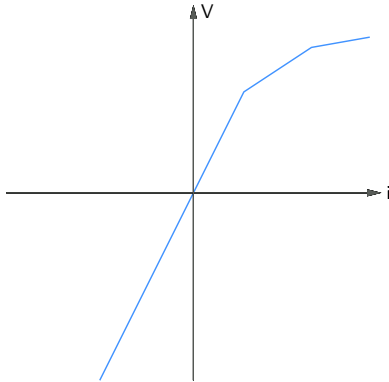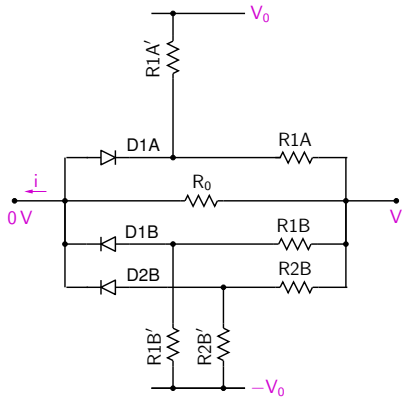



Wave shaping with diodes

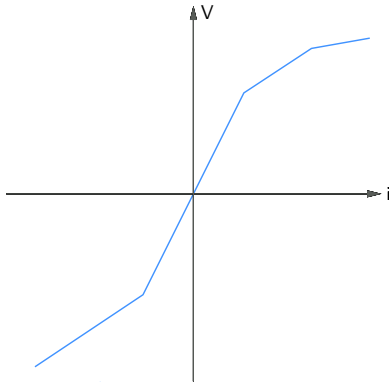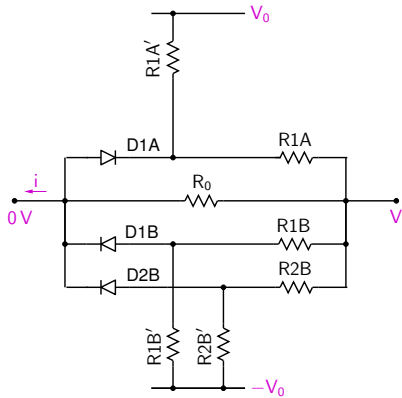

Wave shaping with diodes

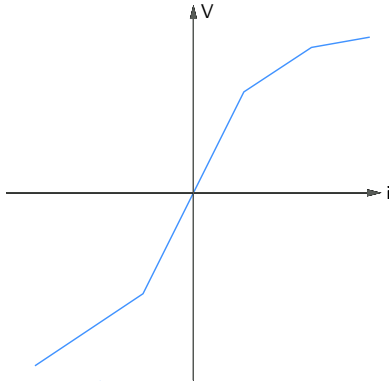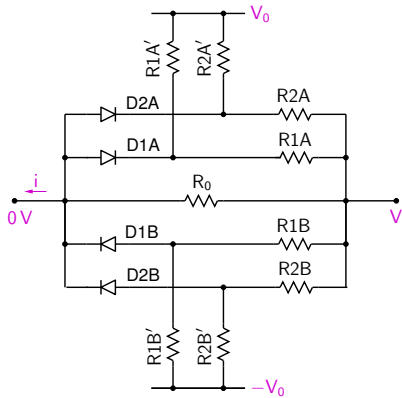

Wave shaping with diodes

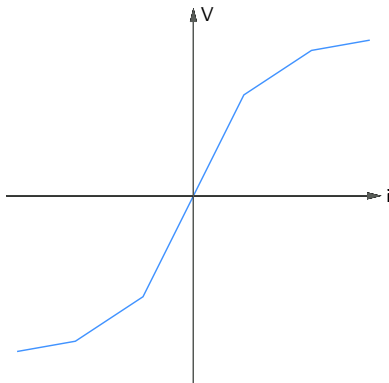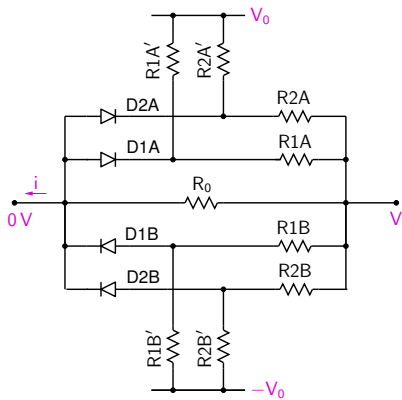

Wave shaping with diodes

$$R_a = 5 \text{ k}$$

$$R_0 = 20 \text{ k}$$



$$R_{1A} = R_{1B} = 15 \text{ k}$$

$$R_{2A} = R_{2B} = 5 \text{ k}$$



$$R_{1A'} = R_{1B'} = 60 \text{ k}$$

$$R_{2A'} = R_{2B'} = 10 \text{ k}$$

$$V_0 = 15 \text{ V}$$


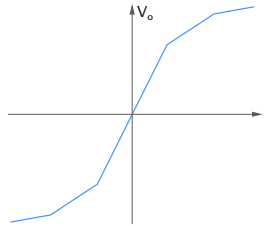
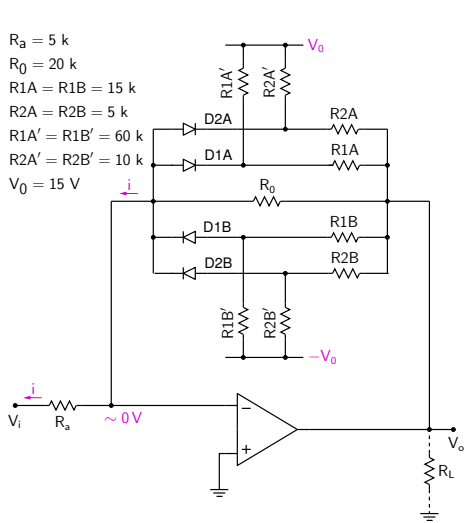


Wave shaping with diodes

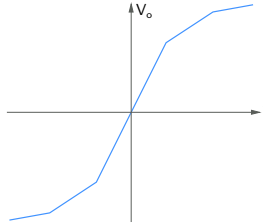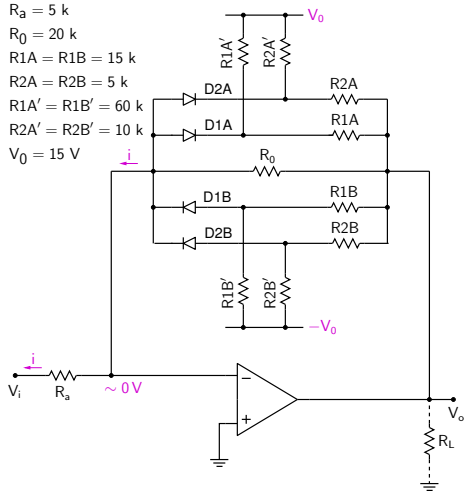





Since $V_i = -R_a i$, the V_o versus V_i plot is similar to the V versus i plot, except for the $(-R_a)$ factor.

Wave shaping with diodes

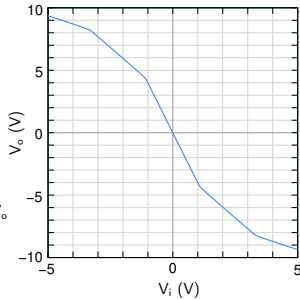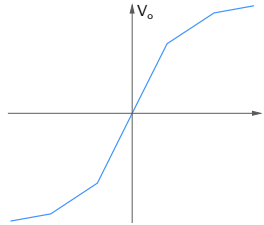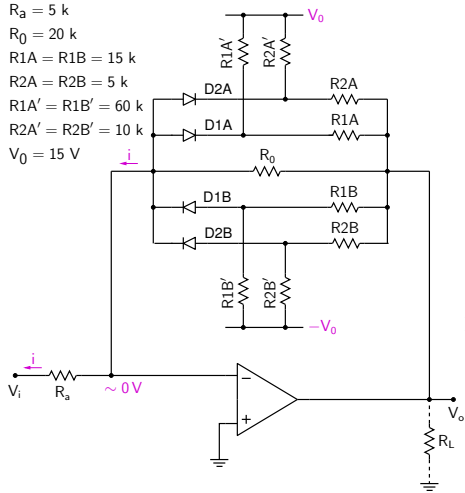





Since $V_i = -R_a i$, the V_o versus V_i plot is similar to the V versus i plot, except for the $(-R_a)$ factor.

Wave shaping with diodes

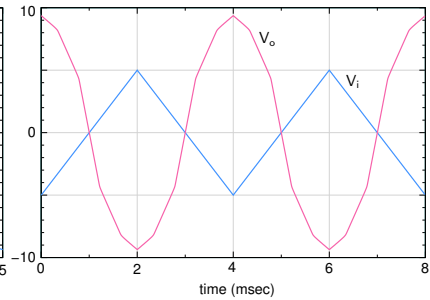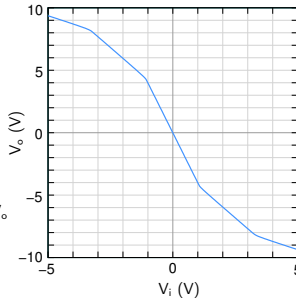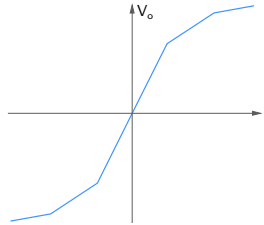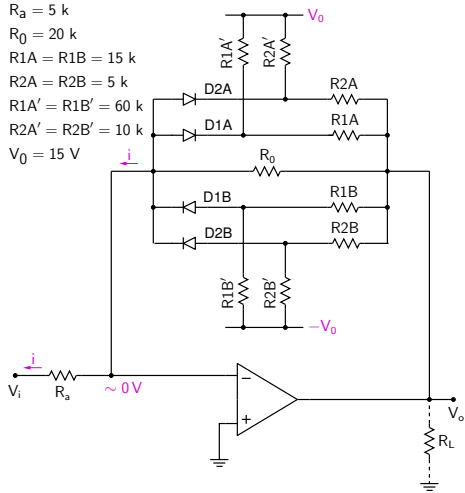

Since $V_i = -R_a i$, the V_o versus V_i plot is similar to the V versus i plot, except for the $(-R_a)$ factor.



Wave shaping with diodes

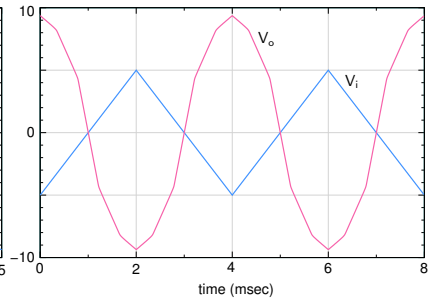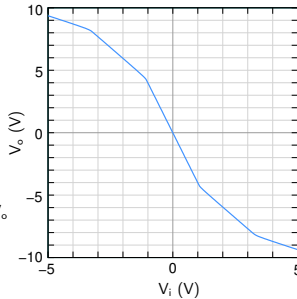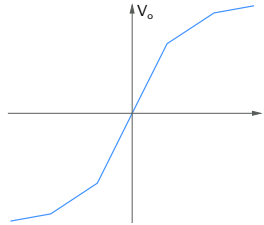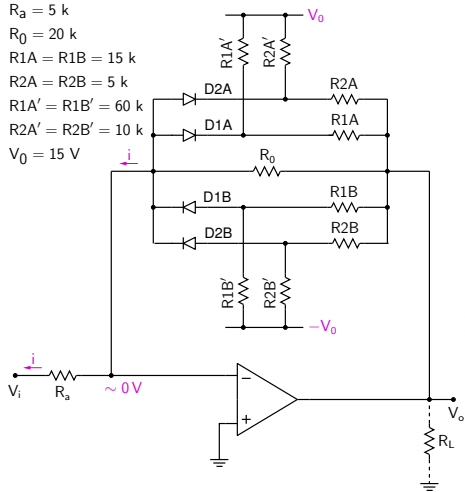

Since $V_i = -R_a i$, the V_o versus V_i plot is similar to the V versus i plot, except for the $(-R_a)$ factor.

SEQUEL file: ee101_wave_shaper.sqproj

Wave shaping with diodes: spectrum

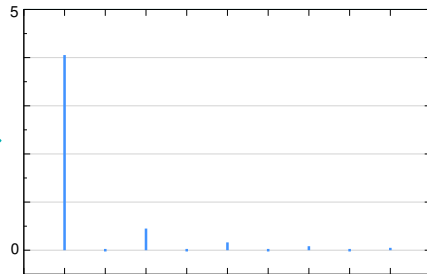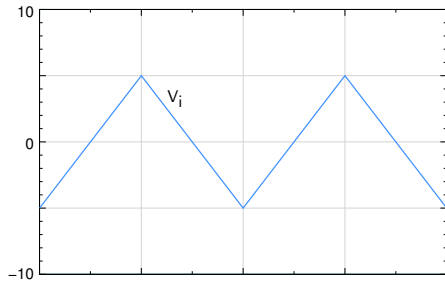

Wave shaping with diodes: spectrum

