


- * The digital circuits we have seen so far (gates, multiplexer, demultiplexer, encoders, decoders) are *combinatorial* in nature, i.e., the output(s) depends only on the *present* values of the inputs and *not* on their past values.

- * The digital circuits we have seen so far (gates, multiplexer, demultiplexer, encoders, decoders) are *combinatorial* in nature, i.e., the output(s) depends only on the *present* values of the inputs and *not* on their past values.
- * In *sequential* circuits, the “state” of the circuit is crucial in determining the output values. For a given input combination, a sequential circuit may produce different output values, depending on its previous state.

- * The digital circuits we have seen so far (gates, multiplexer, demultiplexer, encoders, decoders) are *combinatorial* in nature, i.e., the output(s) depends only on the *present* values of the inputs and *not* on their past values.
- * In *sequential* circuits, the “state” of the circuit is crucial in determining the output values. For a given input combination, a sequential circuit may produce different output values, depending on its previous state.
- * In other words, a sequential circuit has a *memory* (of its past state) whereas a combinatorial circuit has no memory.

- * The digital circuits we have seen so far (gates, multiplexer, demultiplexer, encoders, decoders) are *combinatorial* in nature, i.e., the output(s) depends only on the *present* values of the inputs and *not* on their past values.
- * In *sequential* circuits, the “state” of the circuit is crucial in determining the output values. For a given input combination, a sequential circuit may produce different output values, depending on its previous state.
- * In other words, a sequential circuit has a *memory* (of its past state) whereas a combinatorial circuit has no memory.
- * Sequential circuits (together with combinatorial circuits) make it possible to build several useful applications, such as counters, registers, arithmetic/logic unit (ALU), all the way to microprocessors.


NAND latch (RS latch)

 

A	B	X_1	X_2
1	0		
0	1		
1	1		
0	0		

* A, B : inputs, X_1, X_2 : outputs


NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0		
0	1		
1	1		
0	0		

- * A, B : inputs, X_1, X_2 : outputs
- * Consider $A = 1, B = 0$.

NAND latch (RS latch)

 


A	B	X ₁	X ₂
1	0		
0	1		
1	1		
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$B = 0 \Rightarrow X_2 = 1$

NAND latch (RS latch)

 


A	B	X ₁	X ₂
1	0		
0	1		
1	1		
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$B = 0 \Rightarrow X_2 = 1$

NAND latch (RS latch)

 


A	B	X ₁	X ₂
1	0		
0	1		
1	1		
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{AX_2} = \overline{1 \cdot 1} = 0.$$

NAND latch (RS latch)

 


A	B	X ₁	X ₂
1	0		
0	1		
1	1		
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{AX_2} = \overline{1 \cdot 1} = 0.$$

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1		
1	1		
0	0		


* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{AX_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have $X_1 = 0, X_2 = 1$.


NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1		
1	1		
0	0		

- * A, B : inputs, X_1, X_2 : outputs
- * Consider $A = 1, B = 0$.
 $B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{AX_2} = \overline{1 \cdot 1} = 0$.
Overall, we have $X_1 = 0, X_2 = 1$.
- * Consider $A = 0, B = 1$.


NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1		
0	0		

- * A, B : inputs, X_1, X_2 : outputs
- * Consider $A = 1, B = 0$.
 $B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{AX_2} = \overline{1 \cdot 1} = 0$.
Overall, we have $X_1 = 0, X_2 = 1$.
- * Consider $A = 0, B = 1$.
 $\rightarrow X_1 = 1, X_2 = 0$.


NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1		
0	0		

- * A, B : inputs, X_1, X_2 : outputs
- * Consider $A = 1, B = 0$.
 $B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{AX_2} = \overline{1 \cdot 1} = 0$.
Overall, we have $X_1 = 0, X_2 = 1$.
- * Consider $A = 0, B = 1$.
 $\rightarrow X_1 = 1, X_2 = 0$.
- * Consider $A = B = 1$.

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1		
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{A X_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have $X_1 = 0, X_2 = 1$.


* Consider $A = 0, B = 1$.

$$\rightarrow X_1 = 1, X_2 = 0.$$

* Consider $A = B = 1$.

$$X_1 = \overline{A X_2} = \overline{X_2}, X_2 = \overline{B X_1} = \overline{X_1} \Rightarrow \boxed{X_1 = \overline{X_2}}$$

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{A X_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have $X_1 = 0, X_2 = 1$.


* Consider $A = 0, B = 1$.

$$\rightarrow X_1 = 1, X_2 = 0.$$

* Consider $A = B = 1$.

$$X_1 = \overline{A X_2} = \overline{X_2}, X_2 = \overline{B X_1} = \overline{X_1} \Rightarrow \boxed{X_1 = \overline{X_2}}$$

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{A X_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have $X_1 = 0, X_2 = 1$.

* Consider $A = 0, B = 1$.


$$\rightarrow X_1 = 1, X_2 = 0.$$

* Consider $A = B = 1$.

$$X_1 = \overline{A X_2} = \overline{X_2}, X_2 = \overline{B X_1} = \overline{X_1} \Rightarrow \boxed{X_1 = \overline{X_2}}$$

If $X_1 = 1, X_2 = 0$ previously, the circuit continues to "hold" that state.

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{A X_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have $X_1 = 0, X_2 = 1$.

* Consider $A = 0, B = 1$.

$$\rightarrow X_1 = 1, X_2 = 0.$$


* Consider $A = B = 1$.

$$X_1 = \overline{A X_2} = \overline{X_2}, X_2 = \overline{B X_1} = \overline{X_1} \Rightarrow \boxed{X_1 = \overline{X_2}}$$

If $X_1 = 1, X_2 = 0$ previously, the circuit continues to “hold” that state.

Similarly, if $X_1 = 0, X_2 = 1$ previously, the circuit continues to “hold” that state.

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0		

* A, B : inputs, X_1, X_2 : outputs

* Consider $A = 1, B = 0$.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{A X_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have $X_1 = 0, X_2 = 1$.

* Consider $A = 0, B = 1$.

$$\rightarrow X_1 = 1, X_2 = 0.$$

* Consider $A = B = 1$.


$$X_1 = \overline{A X_2} = \overline{X_2}, X_2 = \overline{B X_1} = \overline{X_1} \Rightarrow \boxed{X_1 = \overline{X_2}}$$

If $X_1 = 1, X_2 = 0$ previously, the circuit continues to “hold” that state.

Similarly, if $X_1 = 0, X_2 = 1$ previously, the circuit continues to “hold” that state.

The circuit has “latched in” the previous state.

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0		

* A, B: inputs, X₁, X₂: outputs

* Consider A = 1, B = 0.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{A X_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have X₁ = 0, X₂ = 1.

* Consider A = 0, B = 1.

$$\rightarrow X_1 = 1, X_2 = 0.$$

* Consider A = B = 1.

$$X_1 = \overline{A X_2} = \overline{X_2}, X_2 = \overline{B X_1} = \overline{X_1} \Rightarrow \boxed{X_1 = \overline{X_2}}$$


If X₁ = 1, X₂ = 0 previously, the circuit continues to “hold” that state.

Similarly, if X₁ = 0, X₂ = 1 previously, the circuit continues to “hold” that state.

The circuit has “latched in” the previous state.

* For A = B = 0, X₁ and X₂ are both 1. This combination of A and B is *not* allowed for reasons that will become clear later.

NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0	1	1

* A, B: inputs, X₁, X₂: outputs

* Consider A = 1, B = 0.

$$B = 0 \Rightarrow X_2 = 1 \Rightarrow X_1 = \overline{A X_2} = \overline{1 \cdot 1} = 0.$$

Overall, we have X₁ = 0, X₂ = 1.

* Consider A = 0, B = 1.

$$\rightarrow X_1 = 1, X_2 = 0.$$

* Consider A = B = 1.

$$X_1 = \overline{A X_2} = \overline{X_2}, X_2 = \overline{B X_1} = \overline{X_1} \Rightarrow \boxed{X_1 = \overline{X_2}}$$


If X₁ = 1, X₂ = 0 previously, the circuit continues to “hold” that state.

Similarly, if X₁ = 0, X₂ = 1 previously, the circuit continues to “hold” that state.

The circuit has “latched in” the previous state.


* For A = B = 0, X₁ and X₂ are both 1. This combination of A and B is *not* allowed for reasons that will become clear later.

NAND latch (RS latch)

 

A	B	X_1	X_2
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	


NAND latch (RS latch)

 

A	B	X_1	X_2
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

* The combination $A=1, B=0$ serves to *reset* X_1 to 0 (*irrespective of* the previous state of the latch).


NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

- * The combination $A=1, B=0$ serves to *reset* X_1 to 0 (*irrespective of the previous state of the latch*).
- * The combination $A=0, B=1$ serves to *set* X_1 to 1 (*irrespective of the previous state of the latch*).


NAND latch (RS latch)

 

A	B	X ₁	X ₂
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

- * The combination $A=1, B=0$ serves to *reset* X_1 to 0 (*irrespective of the previous state of the latch*).
- * The combination $A=0, B=1$ serves to *set* X_1 to 1 (*irrespective of the previous state of the latch*).
- * In other words,
 - $A=1, B=0 \rightarrow$ latch gets reset to 0.
 - $A=0, B=1 \rightarrow$ latch gets set to 1.


NAND latch (RS latch)

 

A	B	X_1	X_2
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

- * The combination $A=1, B=0$ serves to *reset* X_1 to 0 (*irrespective of* the previous state of the latch).
- * The combination $A=0, B=1$ serves to *set* X_1 to 1 (*irrespective of* the previous state of the latch).
- * In other words,
 $A=1, B=0 \rightarrow$ latch gets reset to 0.
 $A=0, B=1 \rightarrow$ latch gets set to 1.
- * The A input is therefore called the RESET (R) input, and B is called the SET (S) input of the latch.


NAND latch (RS latch)

 


A	B	X_1	X_2
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

- * The combination $A=1, B=0$ serves to *reset* X_1 to 0 (*irrespective of* the previous state of the latch).
- * The combination $A=0, B=1$ serves to *set* X_1 to 1 (*irrespective of* the previous state of the latch).
- * In other words,
 $A=1, B=0 \rightarrow$ latch gets reset to 0.
 $A=0, B=1 \rightarrow$ latch gets set to 1.
- * The A input is therefore called the RESET (R) input, and B is called the SET (S) input of the latch.
- * X_1 is denoted by Q , and X_2 (which is $\overline{X_1}$ in all cases except for $A=B=0$) is denoted by \overline{Q} .

NAND latch (RS latch)

 


A	B	X_1	X_2
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

- * The combination $A=1, B=0$ serves to *reset* X_1 to 0 (*irrespective of the previous state of the latch*).
- * The combination $A=0, B=1$ serves to *set* X_1 to 1 (*irrespective of the previous state of the latch*).
- * In other words,
 $A=1, B=0 \rightarrow$ latch gets reset to 0.
 $A=0, B=1 \rightarrow$ latch gets set to 1.
- * The A input is therefore called the RESET (R) input, and B is called the SET (S) input of the latch.
- * X_1 is denoted by Q , and X_2 (which is $\overline{X_1}$ in all cases except for $A=B=0$) is denoted by \overline{Q} .


NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


* Up to $t = t_1$, $R = 0$, $S = 1 \rightarrow Q = 1$.

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


- * Up to $t = t_1$, $R = 0$, $S = 1 \rightarrow Q = 1$.
- * At $t = t_1$, R goes high $\rightarrow R = S = 1$, and the latch holds its previous state \rightarrow no change at the output.

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


- * Up to $t = t_1$, $R = 0$, $S = 1 \rightarrow Q = 1$.
- * At $t = t_1$, R goes high $\rightarrow R = S = 1$, and the latch holds its previous state \rightarrow no change at the output.
- * At $t = t_2$, S goes low $\rightarrow R = 1$, $S = 0 \rightarrow Q = 0$.

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


- * Up to $t = t_1$, $R=0$, $S=1 \rightarrow Q=1$.
- * At $t = t_1$, R goes high $\rightarrow R=S=1$, and the latch holds its previous state \rightarrow no change at the output.
- * At $t = t_2$, S goes low $\rightarrow R=1$, $S=0 \rightarrow Q=0$.
- * At $t = t_3$, S goes high $\rightarrow R=S=1$, and the latch holds its previous state \rightarrow no change at the output.


NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

- It makes $Q = \bar{Q} = 1$, i.e., Q and \bar{Q} are not inverse of each other any more.

NAND latch (RS latch)

 


R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

- It makes $Q = \overline{Q} = 1$, i.e., Q and \overline{Q} are not inverse of each other any more.
- More importantly, when R and S both become 1 simultaneously (starting from $R = S = 0$), the final outputs Q and \overline{Q} cannot be uniquely determined. We could have $Q = 0$, $\overline{Q} = 1$ or $Q = 1$, $\overline{Q} = 0$, depending on the delays associated with the two NAND gates.

NAND latch (RS latch)

 


R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

- It makes $Q = \overline{Q} = 1$, i.e., Q and \overline{Q} are not inverse of each other any more.
- More importantly, when R and S both become 1 simultaneously (starting from $R = S = 0$), the final outputs Q and \overline{Q} cannot be uniquely determined. We could have $Q = 0$, $\overline{Q} = 1$ or $Q = 1$, $\overline{Q} = 0$, depending on the delays associated with the two NAND gates.

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

- It makes $Q = \bar{Q} = 1$, i.e., Q and \bar{Q} are not inverse of each other any more.
- More importantly, when R and S both become 1 simultaneously (starting from $R = S = 0$), the final outputs Q and \bar{Q} cannot be uniquely determined. We could have $Q = 0, \bar{Q} = 1$ or $Q = 1, \bar{Q} = 0$, depending on the delays associated with the two NAND gates.

NAND latch (RS latch)

 


R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

- It makes $Q = \overline{Q} = 1$, i.e., Q and \overline{Q} are not inverse of each other any more.
- More importantly, when R and S both become 1 simultaneously (starting from $R = S = 0$), the final outputs Q and \overline{Q} cannot be uniquely determined. We could have $Q = 0, \overline{Q} = 1$ or $Q = 1, \overline{Q} = 0$, depending on the delays associated with the two NAND gates.

NAND latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

 - It makes $Q = \bar{Q} = 1$, i.e., Q and \bar{Q} are not inverse of each other any more.
- More importantly, when R and S both become 1 simultaneously (starting from $R = S = 0$), the final outputs Q and \bar{Q} cannot be uniquely determined. We could have $Q = 0, \bar{Q} = 1$ or $Q = 1, \bar{Q} = 0$, depending on the delays associated with the two NAND gates.




R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


Why not allow $R = S = 0$?

- It makes $Q = \bar{Q} = 1$, i.e., Q and \bar{Q} are not inverse of each other any more.
- More importantly, when R and S both become 1 simultaneously (starting from $R = S = 0$), the final outputs Q and \bar{Q} cannot be uniquely determined. We could have $Q = 0, \bar{Q} = 1$ or $Q = 1, \bar{Q} = 0$, depending on the delays associated with the two NAND gates.

NOR latch (RS latch)

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
0	0	previous	
1	1	invalid	

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
0	0	previous	
1	1	invalid	

 - * The NOR latch is similar to the NAND latch:
When $R=1$, $S=0$, the latch gets *reset* to $Q=0$.
When $R=0$, $S=1$, the latch gets *set* to $Q=1$.




R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
0	0	previous	
1	1	invalid	

 - * The NOR latch is similar to the NAND latch:
When $R=1$, $S=0$, the latch gets *reset* to $Q=0$.
When $R=0$, $S=1$, the latch gets *set* to $Q=1$.
- * For $R=S=0$, the latch retains its previous state (i.e., the previous values of Q and \overline{Q}).




R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
0	0	previous	
1	1	invalid	

 - * The NOR latch is similar to the NAND latch:
When $R = 1$, $S = 0$, the latch gets *reset* to $Q = 0$.
When $R = 0$, $S = 1$, the latch gets *set* to $Q = 1$.
- * For $R = S = 0$, the latch retains its previous state (i.e., the previous values of Q and \overline{Q}).
- * $R = S = 1$ is not allowed for reasons similar to those discussed in the context of the NAND latch.




R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
0	0	previous	
1	1	invalid	

NAND latch: alternative node names

 


R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

NAND latch: alternative node names

 


R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Active low input nodes:

 


\overline{S}	\overline{R}	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 Chatter (bouncing) due to a mechanical switch




 Chatter (bouncing) due to a mechanical switch




- * When the switch is thrown from A to B, V_o is expected to go from 0 V to V_s (say, 5 V).

 Chatter (bouncing) due to a mechanical switch




* When the switch is thrown from A to B, V_o is expected to go from 0 V to V_s (say, 5 V).

 Chatter (bouncing) due to a mechanical switch




- * When the switch is thrown from A to B, V_o is expected to go from 0 V to V_s (say, 5 V).
- * However, mechanical switches suffer from “chatter” or “bouncing,” i.e., the transition from A to B is not a single, clean one. As a result, V_o oscillates between 0 V and 5 V before settling to its final value (5 V).

 Chatter (bouncing) due to a mechanical switch




- * When the switch is thrown from A to B, V_o is expected to go from 0 V to V_s (say, 5 V).
- * However, mechanical switches suffer from “chatter” or “bouncing,” i.e., the transition from A to B is not a single, clean one. As a result, V_o oscillates between 0 V and 5 V before settling to its final value (5 V).

 Chatter (bouncing) due to a mechanical switch




- * When the switch is thrown from A to B, V_o is expected to go from 0 V to V_s (say, 5 V).
- * However, mechanical switches suffer from “chatter” or “bouncing,” i.e., the transition from A to B is not a single, clean one. As a result, V_o oscillates between 0 V and 5 V before settling to its final value (5 V).
- * In some applications, this chatter can cause malfunction → need a way to remove the chatter.

 
Chatter (bouncing) due to a mechanical switch




R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 

 Chatter (bouncing) due to a mechanical switch




R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 


- * Because of the chatter, the S and R inputs may have multiple transitions when the switch is thrown from A to B.

 Chatter (bouncing) due to a mechanical switch



R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 

- * Because of the chatter, the S and R inputs may have multiple transitions when the switch is thrown from A to B.
- * However, for $S = R = 1$, the previous value of Q is retained, causing a *single* transition in Q , as desired.

The “clock”


- * Complex digital circuits are generally designed for *synchronous* operation, i.e., transitions in the various signals are synchronised with the *clock*.

The “clock”

- * Complex digital circuits are generally designed for *synchronous* operation, i.e., transitions in the various signals are synchronised with the *clock*.
- * Synchronous circuits are easier to design and troubleshoot because the voltages at the nodes (both output nodes and internal nodes) can change only at specific times.


The “clock”

- * Complex digital circuits are generally designed for *synchronous* operation, i.e., transitions in the various signals are synchronised with the *clock*.
- * Synchronous circuits are easier to design and troubleshoot because the voltages at the nodes (both output nodes and internal nodes) can change only at specific times.
- * A clock is a periodic signal, with a positive-going transition and a negative-going transition.

 

The “clock”


- * Complex digital circuits are generally designed for *synchronous* operation, i.e., transitions in the various signals are synchronised with the *clock*.
- * Synchronous circuits are easier to design and troubleshoot because the voltages at the nodes (both output nodes and internal nodes) can change only at specific times.
- * A clock is a periodic signal, with a positive-going transition and a negative-going transition.

 

- * The clock frequency determines the overall speed of the circuit. For example, a processor that operates with a 1 GHz clock is 10 times faster than one that operates with a 100 MHz clock.

The “clock”

- * Complex digital circuits are generally designed for *synchronous* operation, i.e., transitions in the various signals are synchronised with the *clock*.
- * Synchronous circuits are easier to design and troubleshoot because the voltages at the nodes (both output nodes and internal nodes) can change only at specific times.
- * A clock is a periodic signal, with a positive-going transition and a negative-going transition.

 


- * The clock frequency determines the overall speed of the circuit. For example, a processor that operates with a 1 GHz clock is 10 times faster than one that operates with a 100 MHz clock.

Intel 80286 (IBM PC-AT): 6 MHz


Modern CPU chips: 2 to 3 GHz.

Clocked RS latch

 

Clocked RS latch


CLK	R	S	Q	\overline{Q}
0	X	X	previous	
1	1	0	0	1
1	0	1	1	0
1	0	0	previous	
1	1	1	invalid	

 

NAND RS latch


A	B	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Clocked RS latch

 

Clocked RS latch


CLK	R	S	Q	\overline{Q}
0	X	X	previous	
1	1	0	0	1
1	0	1	1	0
1	0	0	previous	
1	1	1	invalid	

 

NAND RS latch


A	B	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 * When clock is inactive (0), $A = B = 1$, and the latch holds the previous state.



Clocked RS latch


CLK	R	S	Q	\overline{Q}
0	X	X	previous	
1	1	0	0	1
1	0	1	1	0
1	0	0	previous	
1	1	1	invalid	

 

NAND RS latch


A	B	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

 - * When clock is inactive (0), $A = B = 1$, and the latch holds the previous state.
- * When clock is active (1), $A = \overline{S}$, $B = \overline{R}$. Using the truth table for the NAND RS latch (right), we can construct the truth table for the clocked RS latch.



Clocked RS latch

CLK	R	S	Q	\overline{Q}
0	X	X	previous	
1	1	0	0	1
1	0	1	1	0
1	0	0	previous	
1	1	1	invalid	

 


NAND RS latch


A	B	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

- * When clock is inactive (0), $A = B = 1$, and the latch holds the previous state.
- * When clock is active (1), $A = \overline{S}$, $B = \overline{R}$. Using the truth table for the NAND RS latch (right), we can construct the truth table for the clocked RS latch.
- * Note that the above table is sensitive to the *level* of the clock (i.e., whether CLK is 0 or 1).

Clocked RS latch

 

CLK	R	S	Q	\overline{Q}
0	X	X	previous	
1	1	0	0	1
1	0	1	1	0
1	0	0	previous	
1	1	1	invalid	


 


- * The clocked RS latch seen previously is *level-sensitive*, i.e., if the clock is active ($\text{CLK} = 1$), the flip-flop output is allowed to change, depending on the R and S inputs.

- * The clocked RS latch seen previously is *level-sensitive*, i.e., if the clock is active ($\text{CLK} = 1$), the flip-flop output is allowed to change, depending on the R and S inputs.
- * In an *edge-sensitive* flip-flop, the output can change only at the active clock *edge* (i.e., CLK transition from 0 to 1 or from 1 to 0).

Edge-triggered flip-flops

  
- * The clocked RS latch seen previously is *level-sensitive*, i.e., if the clock is active ($\text{CLK} = 1$), the flip-flop output is allowed to change, depending on the R and S inputs.
- * In an *edge-sensitive* flip-flop, the output can change only at the active clock *edge* (i.e., CLK transition from 0 to 1 or from 1 to 0).
- * Edge-sensitive flip-flops are denoted by the following symbols:



JK flip-flop: introduction


R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.

JK flip-flop: introduction

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)


Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.

JK flip-flop: introduction

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)

Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
- * When $CLK = 1$:

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)

Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
- * When $CLK = 1$:
 - $J = K = 0 \rightarrow R = S = 1$, RS latch holds previous Q , i.e., $Q_{n+1} = Q_n$, where n denotes the n^{th} clock pulse (This notation will become clear shortly).

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)

Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
- * When $CLK = 1$:
 - $J = K = 0 \rightarrow R = S = 1$, RS latch holds previous Q , i.e., $Q_{n+1} = Q_n$, where n denotes the n^{th} clock pulse (This notation will become clear shortly).

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)

Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
- * When $CLK = 1$:
 - $J = K = 0 \rightarrow R = S = 1$, RS latch holds previous Q , i.e., $Q_{n+1} = Q_n$, where n denotes the n^{th} clock pulse (This notation will become clear shortly).
 - $J = 0, K = 1 \rightarrow R = 1, S = \overline{Q_n}$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)

Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
- * When $CLK = 1$:
 - $J = K = 0 \rightarrow R = S = 1$, RS latch holds previous Q , i.e., $Q_{n+1} = Q_n$, where n denotes the n^{th} clock pulse (This notation will become clear shortly).
 - $J = 0, K = 1 \rightarrow R = 1, S = \overline{Q_n}$.
Case (i): $Q_n = 0 \rightarrow S = 1$ (i.e., $R = S = 1$) $\rightarrow Q_{n+1} = Q_n = 0$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)

Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
- * When $CLK = 1$:
 - $J = K = 0 \rightarrow R = S = 1$, RS latch holds previous Q , i.e., $Q_{n+1} = Q_n$, where n denotes the n^{th} clock pulse (This notation will become clear shortly).
 - $J = 0, K = 1 \rightarrow R = 1, S = \overline{Q_n}$.
 - Case (i): $Q_n = 0 \rightarrow S = 1$ (i.e., $R = S = 1$) $\rightarrow Q_{n+1} = Q_n = 0$.
 - Case (ii): $Q_n = 1 \rightarrow S = 0$ (i.e., $R = 1, S = 0$) $\rightarrow Q_{n+1} = 0$.

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)

Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
- * When $CLK = 1$:
 - $J = K = 0 \rightarrow R = S = 1$, RS latch holds previous Q , i.e., $Q_{n+1} = Q_n$, where n denotes the n^{th} clock pulse (This notation will become clear shortly).
 - $J = 0, K = 1 \rightarrow R = 1, S = \bar{Q}_n$.
 - Case (i): $Q_n = 0 \rightarrow S = 1$ (i.e., $R = S = 1$) $\rightarrow Q_{n+1} = Q_n = 0$.
 - Case (ii): $Q_n = 1 \rightarrow S = 0$ (i.e., $R = 1, S = 0$) $\rightarrow Q_{n+1} = 0$.
 In either case, $Q_{n+1} = 0 \rightarrow$ For $J = 0, K = 1, Q_{n+1} = 0$.

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0


Truth table for JK flip-flop

- * When $CLK = 0$, we have $R = S = 1$, and the RS latch holds the previous Q . In other words, nothing happens as long as $CLK = 0$.
 - * When $CLK = 1$:
 - $J = K = 0 \rightarrow R = S = 1$, RS latch holds previous Q , i.e., $Q_{n+1} = Q_n$, where n denotes the n^{th} clock pulse (This notation will become clear shortly).
 - $J = 0, K = 1 \rightarrow R = 1, S = \bar{Q}_n$.
 - Case (i): $Q_n = 0 \rightarrow S = 1$ (i.e., $R = S = 1$) $\rightarrow Q_{n+1} = Q_n = 0$.
 - Case (ii): $Q_n = 1 \rightarrow S = 0$ (i.e., $R = 1, S = 0$) $\rightarrow Q_{n+1} = 0$.
- In either case, $Q_{n+1} = 0 \rightarrow$ For $J = 0, K = 1, Q_{n+1} = 0$.

JK flip-flop: introduction

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0

Truth table for JK flip-flop

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0


Truth table for JK flip-flop

* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0

Truth table for JK flip-flop


* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.

Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0

Truth table for JK flip-flop

* When CLK = 1:


- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.

Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.

Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0


Truth table for JK flip-flop

* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.
 Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.
 \rightarrow For $J = 1, K = 0, Q_{n+1} = 1$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1


Truth table for JK flip-flop

* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.
 Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.
 \rightarrow For $J = 1, K = 0, Q_{n+1} = 1$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1


Truth table for JK flip-flop

* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.
 Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.
 \rightarrow For $J = 1, K = 0, Q_{n+1} = 1$.
- Consider $J = 1, K = 1 \rightarrow R = Q_n, S = \overline{Q_n}$.

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1


Truth table for JK flip-flop

* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.
 Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.
 \rightarrow For $J = 1, K = 0, Q_{n+1} = 1$.
- Consider $J = 1, K = 1 \rightarrow R = Q_n, S = \overline{Q_n}$.
 Case (i): $Q_n = 0 \rightarrow R = 0, S = 1 \rightarrow Q_{n+1} = 1$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1


Truth table for JK flip-flop

* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{Q_n} = Q_n$.
 Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.
 \rightarrow For $J = 1, K = 0, Q_{n+1} = 1$.
- Consider $J = 1, K = 1 \rightarrow R = Q_n, S = \overline{Q_n}$.
 Case (i): $Q_n = 0 \rightarrow R = 0, S = 1 \rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1, S = 0 \rightarrow Q_{n+1} = 0$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 

CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1


Truth table for JK flip-flop

* When CLK = 1:

- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.
 Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.
 \rightarrow For $J = 1, K = 0, Q_{n+1} = 1$.
- Consider $J = 1, K = 1 \rightarrow R = Q_n, S = \overline{Q_n}$.
 Case (i): $Q_n = 0 \rightarrow R = 0, S = 1 \rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1, S = 0 \rightarrow Q_{n+1} = 0$.
 \rightarrow For $J = 1, K = 1, Q_{n+1} = \overline{Q_n}$.

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
1	1	previous	
0	0	invalid	

Truth table for RS latch

 


CLK	J	K	Q (Q_{n+1})
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1
1	1	1	toggles ($\overline{Q_n}$)

Truth table for JK flip-flop

* When CLK = 1:


- Consider $J = 1, K = 0 \rightarrow S = 1, R = \overline{\overline{Q_n}} = Q_n$.
 Case (i): $Q_n = 0 \rightarrow R = 0$ (i.e., $R = 0, S = 1$) $\rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1$ (i.e., $R = 1, S = 1$) $\rightarrow Q_{n+1} = Q_n = 1$.
 \rightarrow For $J = 1, K = 0, Q_{n+1} = 1$.
- Consider $J = 1, K = 1 \rightarrow R = Q_n, S = \overline{Q_n}$.
 Case (i): $Q_n = 0 \rightarrow R = 0, S = 1 \rightarrow Q_{n+1} = 1$.
 Case (ii): $Q_n = 1 \rightarrow R = 1, S = 0 \rightarrow Q_{n+1} = 0$.
 \rightarrow For $J = 1, K = 1, Q_{n+1} = \overline{Q_n}$.

 

CLK	J	K	$Q(Q_{n+1})$
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1
1	1	1	toggles (\bar{Q}_n)

Truth table for JK flip-flop

Consider $J = K = 1$ and $CLK = 1$.

 


CLK	J	K	$Q(Q_{n+1})$
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1
1	1	1	toggles ($\overline{Q_n}$)

Truth table for JK flip-flop

Consider $J = K = 1$ and $CLK = 1$.

 As long as $CLK = 1$, Q will keep toggling! (The frequency will depend on the delay values of the various gates).



CLK	J	K	$Q(Q_{n+1})$
0	X	X	previous (Q_n)
1	0	0	previous (Q_n)
1	0	1	0
1	1	0	1
1	1	1	toggles ($\overline{Q_n}$)


Truth table for JK flip-flop

Consider $J = K = 1$ and $CLK = 1$.


As long as $CLK = 1$, Q will keep toggling! (The frequency will depend on the delay values of the various gates).

→ Use the “Master-slave” configuration.

JK flip-flop (Master-Slave)

 


JK flip-flop (Master-Slave)

 


- * When CLK goes high, only the first latch is affected; the second latch retains its previous value (because $\overline{CLK} = 0 \rightarrow R_2 = S_2 = 1$).

JK flip-flop (Master-Slave)

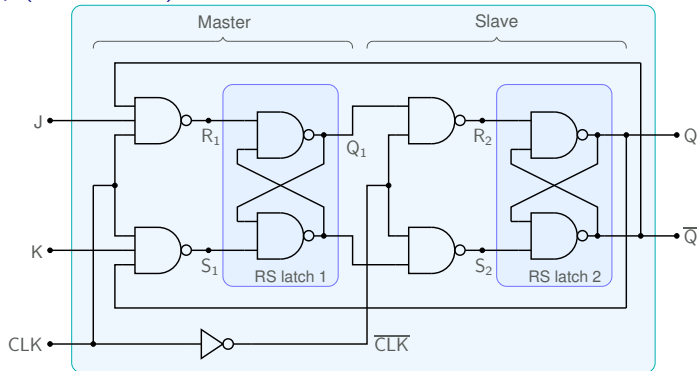


- * When CLK goes high, only the first latch is affected; the second latch retains its previous value (because $\overline{\text{CLK}} = 0 \rightarrow R_2 = S_2 = 1$).
- * When CLK goes low, the output of the first latch (Q_1) is retained (since $R_1 = S_1 = 1$), and Q_1 can now affect Q .

JK flip-flop (Master-Slave)

 

- * When CLK goes high, only the first latch is affected; the second latch retains its previous value (because $\overline{\text{CLK}} = 0 \rightarrow R_2 = S_2 = 1$).
- * When CLK goes low, the output of the first latch (Q_1) is retained (since $R_1 = S_1 = 1$), and Q_1 can now affect Q .
- * In other words, the effect of any changes in J and K appears at the output Q only when CLK makes a transition from 1 to 0.
This is therefore a negative edge-triggered flip-flop.


JK flip-flop (Master-Slave)

 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

- * When CLK goes high, only the first latch is affected; the second latch retains its previous value (because $\overline{\text{CLK}} = 0 \rightarrow R_2 = S_2 = 1$).
- * When CLK goes low, the output of the first latch (Q_1) is retained (since $R_1 = S_1 = 1$), and Q_1 can now affect Q .
- * In other words, the effect of any changes in J and K appears at the output Q only when CLK makes a transition from 1 to 0.
This is therefore a negative edge-triggered flip-flop.


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

- * When CLK goes high, only the first latch is affected; the second latch retains its previous value (because $\overline{CLK} = 0 \rightarrow R_2 = S_2 = 1$).
- * When CLK goes low, the output of the first latch (Q_1) is retained (since $R_1 = S_1 = 1$), and Q_1 can now affect Q .
- * In other words, the effect of any changes in J and K appears at the output Q only when CLK makes a transition from 1 to 0.
This is therefore a negative edge-triggered flip-flop.
- * Note that the JK flip-flop allows all four input combinations.


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

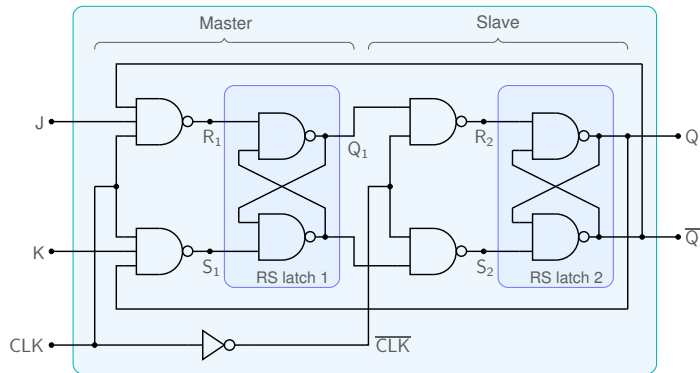


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

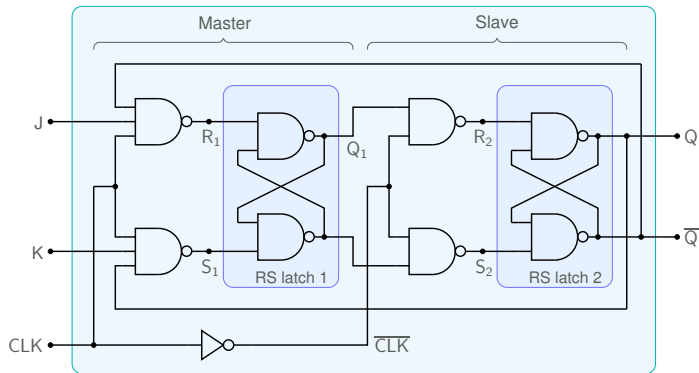


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


JK flip-flop (Master-Slave)

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


 


positive edge-triggered JK flip-flop

 

negative edge-triggered JK flip-flop


 


positive edge-triggered JK flip-flop


 


negative edge-triggered JK flip-flop

  - * Both negative (e.g., 74ALS112A, CD54ACT112) and positive (e.g., 74ALS109A, CD4027) edge-triggered JK flip-flops are available as ICs.





  Consider a negative edge-triggered JK flip-flop.





Consider a negative edge-triggered JK flip-flop.

  - * As seen earlier, when CLK is high (i.e., $t_{1A} < t < t_{1B}$, etc.), the input J and K determine the Master latch output Q_1 .
During this time, *no change* is visible at the flip-flop output Q .





Consider a negative edge-triggered JK flip-flop.

  - * As seen earlier, when CLK is high (i.e., $t_{1A} < t < t_{1B}$, etc.), the input J and K determine the Master latch output Q_1 .
During this time, *no change* is visible at the flip-flop output Q .
- * When the clock goes low, the Slave flip-flop becomes active, making it possible for Q to change.



Consider a negative edge-triggered JK flip-flop.

- * As seen earlier, when CLK is high (i.e., $t_{1A} < t < t_{1B}$, etc.), the input J and K determine the Master latch output Q_1 .
During this time, *no change* is visible at the flip-flop output Q .
- * When the clock goes low, the Slave flip-flop becomes active, making it possible for Q to change.
- * In short, although the flip-flop output Q can only change *after* the active edge, (t_{1B} , t_{2B} , etc.), the new Q value is determined by J and K values just *before* the active edge.

  


Consider a negative edge-triggered JK flip-flop.

- * As seen earlier, when CLK is high (i.e., $t_{1A} < t < t_{1B}$, etc.), the input J and K determine the Master latch output Q_1 .
During this time, *no change* is visible at the flip-flop output Q .
- * When the clock goes low, the Slave flip-flop becomes active, making it possible for Q to change.
- * In short, although the flip-flop output Q can only change *after* the active edge, (t_{1B} , t_{2B} , etc.), the new Q value is determined by J and K values just *before* the active edge.


This is a very important point!

JK flip-flop

 


CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

positive edge-triggered JK flip-flop


 


JK flip-flop

 


CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

positive edge-triggered JK flip-flop

  


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

negative edge-triggered JK flip-flop

 


JK flip-flop

 $J_1 = K_1 = 1$. Assume $Q_1 = Q_2 = 0$ initially.




CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

 


JK flip-flop

 $J_1 = K_1 = 1$. Assume $Q_1 = Q_2 = 0$ initially.




CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

 


* Since $J_1 = K_1 = 1$, Q_1 toggles after every active clock edge.

JK flip-flop

 $J_1 = K_1 = 1$. Assume $Q_1 = Q_2 = 0$ initially.





CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

 

* Since $J_1 = K_1 = 1$, Q_1 toggles after every active clock edge.

JK flip-flop

  $J_1 = K_1 = 1$. Assume $Q_1 = Q_2 = 0$ initially.




CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

* Since $J_1 = K_1 = 1$, Q_1 toggles after every active clock edge.


* $J_2 = Q_1$, $K_2 = \overline{Q_1}$. We need to look at J_2 and K_2 values *just before* the active edge, to determine the next value of Q_2 .

JK flip-flop

 $J_1 = K_1 = 1$. Assume $Q_1 = Q_2 = 0$ initially.




CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

 


- * Since $J_1 = K_1 = 1$, Q_1 toggles after every active clock edge.
- * $J_2 = Q_1$, $K_2 = \overline{Q_1}$. We need to look at J_2 and K_2 values *just before* the active edge, to determine the next value of Q_2 .
- * It is convenient to construct a table listing J_2 and K_2 to figure out the next Q_2 value.

JK flip-flop

 $J_1 = K_1 = 1$. Assume $Q_1 = Q_2 = 0$ initially.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

 


t	$J_2(t = t_k^-)$	$K_2(t = t_k^-)$	$Q_2(t = t_k^+)$
t_1	0	1	0
t_2	1	0	1
t_3	0	1	0
t_4	1	0	1
t_5	0	1	0


- * Since $J_1 = K_1 = 1$, Q_1 toggles after every active clock edge.
- * $J_2 = Q_1$, $K_2 = \overline{Q_1}$. We need to look at J_2 and K_2 values *just before* the active edge, to determine the next value of Q_2 .
- * It is convenient to construct a table listing J_2 and K_2 to figure out the next Q_2 value.

JK flip-flop

 $J_1 = K_1 = 1$. Assume $Q_1 = Q_2 = 0$ initially.




CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

 



t	$J_2(t = t_k^-)$	$K_2(t = t_k^-)$	$Q_2(t = t_k^+)$
t_1	0	1	0
t_2	1	0	1
t_3	0	1	0
t_4	1	0	1
t_5	0	1	0

 - * Since $J_1 = K_1 = 1$, Q_1 toggles after every active clock edge.
- * $J_2 = Q_1$, $K_2 = \overline{Q_1}$. We need to look at J_2 and K_2 values *just before* the active edge, to determine the next value of Q_2 .
- * It is convenient to construct a table listing J_2 and K_2 to figure out the next Q_2 value.




CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1			
t_2												
t_3												
t_4												
t_5												

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	0	
t_2												
t_3												
t_4												
t_5												

 


 

CLK	J	K	Q _{n+1}
↓	0	0	Q _n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q ₀	Q ₁	Q ₂	J ₀	K ₀	J ₁	K ₁	J ₂	K ₂	Q ₀	Q ₁	Q ₂
t ₁	0	0	0	1	0	1	1	0	1	1	0	
t ₂	1	1	0	1	0	0	0	1	0			
t ₃												
t ₄												
t ₅												

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	0	
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3												
t_4												
t_5												

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	0	
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3	1	1	1	1	1	0	0	1	0			
t_4												
t_5												

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	0	
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3	1	1	1	1	1	0	0	1	0	0	1	1
t_4												
t_5												

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	1	0
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3	1	1	1	1	1	0	0	1	0	0	1	1
t_4	0	1	1	1	1	1	1	0	0			
t_5												

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	1	0
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3	1	1	1	1	1	0	0	1	0	0	1	1
t_4	0	1	1	1	1	1	1	0	0	1	0	1
t_5												

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	1	0
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3	1	1	1	1	1	0	0	1	0	0	1	1
t_4	0	1	1	1	1	1	1	0	0	1	0	1
t_5	1	0	1	1	1	0	0	1	1			

 


 

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$


	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	1	0
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3	1	1	1	1	1	0	0	1	0	0	1	1
t_4	0	1	1	1	1	1	1	0	0	1	0	1
t_5	1	0	1	1	1	0	0	1	1	0	0	0

 

 


CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	$\overline{Q_n}$

	t_k^-									t_k^+		
t	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2	Q_0	Q_1	Q_2
t_1	0	0	0	1	0	1	1	0	1	1	1	0
t_2	1	1	0	1	0	0	0	1	0	1	1	1
t_3	1	1	1	1	1	0	0	1	0	0	1	1
t_4	0	1	1	1	1	1	1	0	0	1	0	1
t_5	1	0	1	1	1	0	0	1	1	0	0	0

 


JK flip-flop: asynchronous inputs

 

S_d	R_d	CLK	J	K	Q_{n+1}
0	1	X	X	X	0
1	0	X	X	X	1
1	1	X	X	X	invalid
0	0	\uparrow	0	0	Q_n
0	0	\uparrow	0	1	0
0	0	\uparrow	1	0	1
0	0	\uparrow	1	1	$\overline{Q_n}$

} normal operation

JK flip-flop: asynchronous inputs

 


S_d	R_d	CLK	J	K	Q_{n+1}
0	1	X	X	X	0
1	0	X	X	X	1
1	1	X	X	X	invalid
0	0	↑	0	0	Q_n
0	0	↑	0	1	0
0	0	↑	1	0	1
0	0	↑	1	1	$\overline{Q_n}$

} normal operation

- * Clocked flip-flops are also provided with *asynchronous* or *direct* Set and Reset inputs, S_d and R_d , (also called Preset and Clear, respectively) which override all other inputs (J, K, CLK).

JK flip-flop: asynchronous inputs

 


S_d	R_d	CLK	J	K	Q_{n+1}
0	1	X	X	X	0
1	0	X	X	X	1
1	1	X	X	X	invalid
0	0	↑	0	0	Q_n
0	0	↑	0	1	0
0	0	↑	1	0	1
0	0	↑	1	1	$\overline{Q_n}$

} normal operation

- * Clocked flip-flops are also provided with *asynchronous* or *direct* Set and Reset inputs, S_d and R_d , (also called Preset and Clear, respectively) which override all other inputs (J, K, CLK).
- * The S_d and R_d inputs may be active low; in that case, they are denoted by $\overline{S_d}$ and $\overline{R_d}$.

JK flip-flop: asynchronous inputs

 


S_d	R_d	CLK	J	K	Q_{n+1}
0	1	X	X	X	0
1	0	X	X	X	1
1	1	X	X	X	invalid
0	0	\uparrow	0	0	Q_n
0	0	\uparrow	0	1	0
0	0	\uparrow	1	0	1
0	0	\uparrow	1	1	$\overline{Q_n}$

} normal operation




- * Clocked flip-flops are also provided with *asynchronous* or *direct* Set and Reset inputs, S_d and R_d , (also called Preset and Clear, respectively) which override all other inputs (J, K, CLK).
- * The S_d and R_d inputs may be active low; in that case, they are denoted by $\overline{S_d}$ and $\overline{R_d}$.
- * The asynchronous inputs are convenient for starting up a circuit in a known state.

D flip-flop

 



CLK	D	Q_{n+1}
↑	0	0
↑	1	1

positive edge-triggered D flip-flop

   


CLK	D	Q_{n+1}
↓	0	0
↓	1	1

negative edge-triggered D flip-flop


 
 


D flip-flop

 



CLK	D	Q_{n+1}
↑	0	0
↑	1	1

positive edge-triggered D flip-flop

   


CLK	D	Q_{n+1}
↓	0	0
↓	1	1

negative edge-triggered D flip-flop

  




* The D flip-flop can be used to *delay* the Data (D) signal by one clock period.

D flip-flop

 



CLK	D	Q_{n+1}
↑	0	0
↑	1	1

positive edge-triggered D flip-flop

   


CLK	D	Q_{n+1}
↓	0	0
↓	1	1

negative edge-triggered D flip-flop

  




- * The D flip-flop can be used to *delay* the Data (D) signal by one clock period.
- * With $J = D$, $K = \overline{D}$, we have either $J = 0$, $K = 1$ or $J = 1$, $K = 0$; the next Q is 0 in the first case, 1 in the second case.

D flip-flop

 



CLK	D	Q_{n+1}
↑	0	0
↑	1	1

positive edge-triggered D flip-flop

   


CLK	D	Q_{n+1}
↓	0	0
↓	1	1

negative edge-triggered D flip-flop

 
 


- * The D flip-flop can be used to *delay* the Data (D) signal by one clock period.
- * With $J = D$, $K = \overline{D}$, we have either $J = 0$, $K = 1$ or $J = 1$, $K = 0$; the next Q is 0 in the first case, 1 in the second case.
- * Instead of a JK flip-flop, an RS flip-flop can also be used to make a D flip-flop, with $S = D$, $R = \overline{D}$.



Shift register

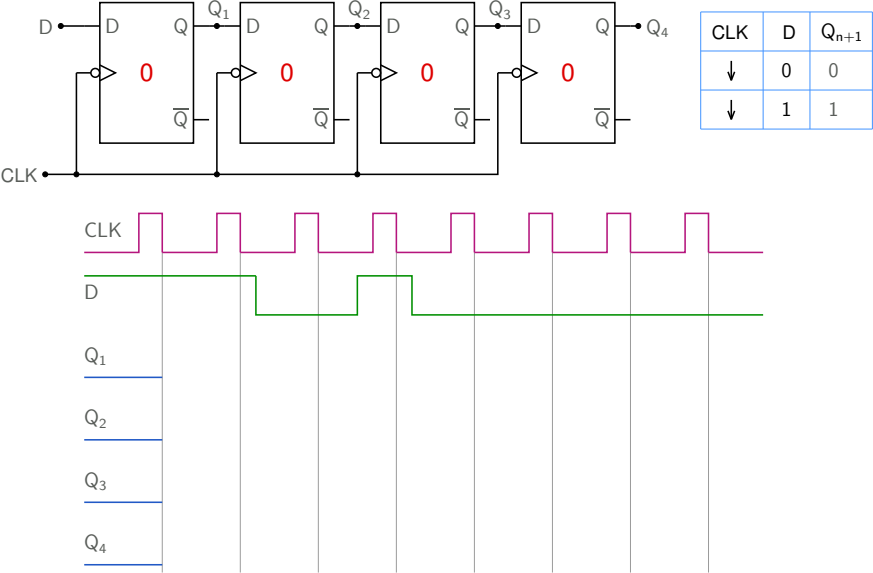



Shift register

  



Shift register

  



Shift register

  



Shift register

  



Shift register

  



Shift register

  



Shift register

  

Shift register

  


Shift register

  


SEQUEL file: ee101_shift_reg_1.sqproj

 
Parallel transfer between shift registers




Register A

 

Register B

 


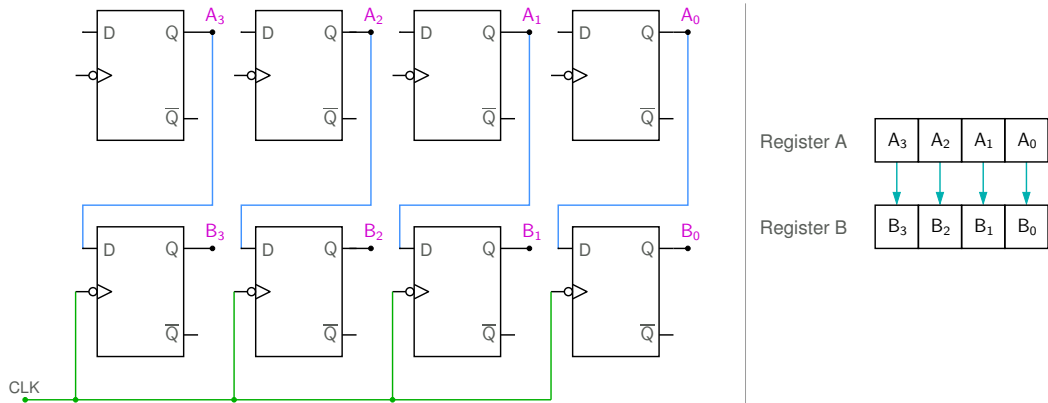Parallel transfer between shift registers




* After the active clock edge, the contents of the A register ($A_3A_2A_1A_0$) are copied to the B register.

Bidirectional shift register

 


Bidirectional shift register

 


- * When the mode input (M) is 1, we have
 $D_0 = D_R, D_1 = Q_0, D_2 = Q_1, D_3 = Q_2$.

Bidirectional shift register

 

- * When the mode input (M) is 1, we have $D_0 = D_R, D_1 = Q_0, D_2 = Q_1, D_3 = Q_2$.
- * When the mode input (M) is 0, we have $D_0 = Q_1, D_1 = Q_2, D_2 = Q_3, D_3 = D_L$.

Bidirectional shift register

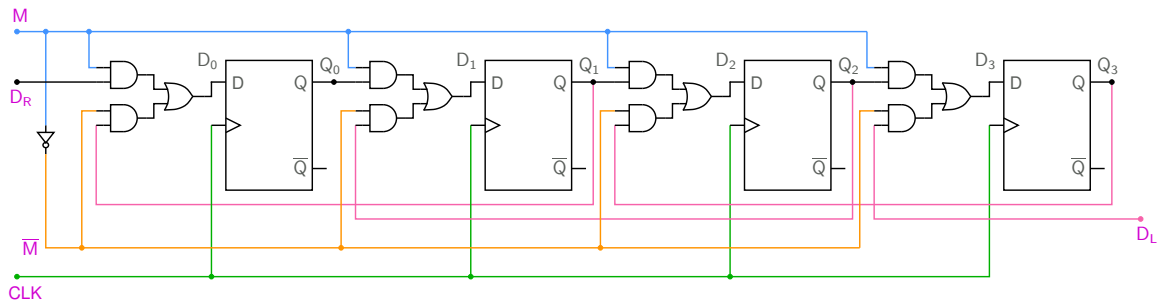

- * When the mode input (M) is 1, we have
 $D_0 = D_R$, $D_1 = Q_0$, $D_2 = Q_1$, $D_3 = Q_2$.
- * When the mode input (M) is 0, we have
 $D_0 = Q_1$, $D_1 = Q_2$, $D_2 = Q_3$, $D_3 = D_L$.
- * $M = 1 \rightarrow$ shift right operation.
 $M = 0 \rightarrow$ shift left operation.

Shift left operation

	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0		
original number	0	0	0	0	1	1	0	1	0	dec. 13

Shift left operation

	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0		
original number	0	0	0	0	1	1	0	1	0	dec. 13
after shift left	0	0	0	1	1	0	1	0		dec. 26

Shift left operation

	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0		
original number	0	0	0	0	1	1	0	1	0	dec. 13
after shift left	0	0	0	1	1	0	1	0		dec. 26

Shift left $\rightarrow \times 2$

Multiplication using shift and add


	1	0	1	1	$A_3A_2A_1A_0$	(decimal 11)				
\times	1	1	0	1	$B_3B_2B_1B_0$	(decimal 13)				
<hr/>										
+		1	0	1	1	since $B_0 = 1$				
		0	0	0	0	since $B_1 = 0$				
<hr/>										
+		0	1	0	1	1	addition			
	1	0	1	1	Z	Z	since $B_2 = 1$			
<hr/>										
+		1	1	0	1	1	1	addition		
	1	0	1	1	Z	Z	Z	since $B_3 = 1$		
<hr/>										
	1	0	0	0	1	1	1	1	addition	(decimal 143)

Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.

Multiplication using shift and add

	1	0	1	1	$A_3A_2A_1A_0$	(decimal 11)
\times	1	1	0	1	$B_3B_2B_1B_0$	(decimal 13)
<hr/>						
+	1	0	1	1	since $B_0 = 1$	
	0	0	0	0	Z	since $B_1 = 0$
<hr/>						
+	0	1	0	1	1	addition
	1	0	1	1	Z	Z since $B_2 = 1$
<hr/>						
+	1	1	0	1	1	1 addition
	1	0	1	1	Z	Z Z since $B_3 = 1$
<hr/>						
	1	0	0	0	1	1
	1	1	1	1	1	1 addition (decimal 143)

 
Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

	1	0	1	1	$A_3A_2A_1A_0$	(decimal 11)		
	\times	1	1	0	$B_3B_2B_1B_0$	(decimal 13)		
<hr/>								
+		1	0	1	1	since $B_0 = 1$		
		0	0	0	0	Z since $B_1 = 0$		
<hr/>								
+		0	1	0	1	addition		
		1	0	1	1	Z Z since $B_2 = 1$		
<hr/>								
+		1	1	0	1	addition		
		1	0	1	1	Z Z Z since $B_3 = 1$		
<hr/>								
	1	0	0	0	1	1	addition	(decimal 143)

 
Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

		1	0	1	1		$A_3A_2A_1A_0$	(decimal 11)
	\times	1	1	0	1		$B_3B_2B_1B_0$	(decimal 13)
<hr/>								
+		1	0	1	1		since $B_0 = 1$	
		0	0	0	0	Z	since $B_1 = 0$	
<hr/>								
+		0	1	0	1	1	addition	
	1	0	1	1	Z	Z	since $B_2 = 1$	
<hr/>								
+		1	1	0	1	1	addition	
	1	0	1	1	Z	Z	since $B_3 = 1$	
<hr/>								
	1	0	0	0	1	1	addition	(decimal 143)

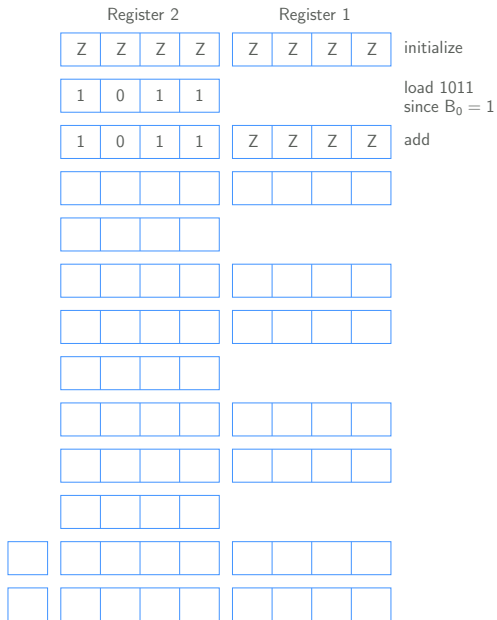
Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

		1	0	1	1		$A_3A_2A_1A_0$	(decimal 11)
	\times	1	1	0	1		$B_3B_2B_1B_0$	(decimal 13)
		<hr/>						
+		1	0	1	1		since $B_0 = 1$	
		0	0	0	0	Z	since $B_1 = 0$	
		<hr/>						
+		0	1	0	1	1	addition	
		1	0	1	1	Z	since $B_2 = 1$	
		<hr/>						
+		1	1	0	1	1	addition	
		1	0	1	1	Z	since $B_3 = 1$	
		<hr/>						
		1	0	0	0	1	addition	(decimal 143)

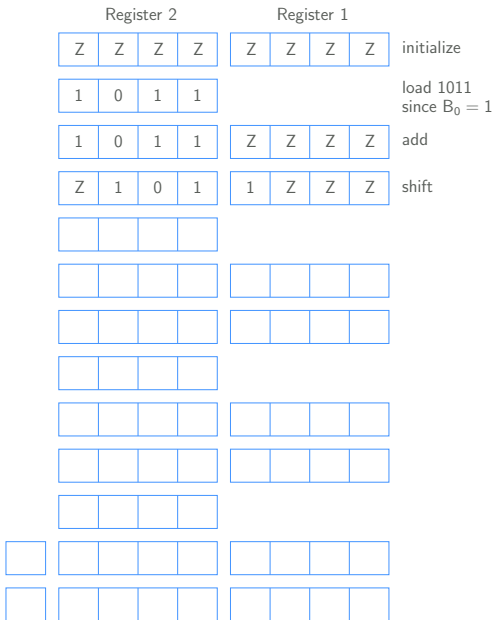Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

		1	0	1	1		$A_3A_2A_1A_0$	(decimal 11)
	\times	1	1	0	1		$B_3B_2B_1B_0$	(decimal 13)
<hr/>								
+		1	0	1	1		since $B_0 = 1$	
		0	0	0	0	Z	since $B_1 = 0$	
<hr/>								
+		0	1	0	1	1	addition	
		1	0	1	1	Z Z	since $B_2 = 1$	
<hr/>								
+		1	1	0	1	1	addition	
		1	0	1	1	Z Z Z	since $B_3 = 1$	
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								


Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.

[illegible]

Multiplication using shift and add

		1	0	1	1		$A_3A_2A_1A_0$	(decimal 11)
	\times	1	1	0	1		$B_3B_2B_1B_0$	(decimal 13)
<hr/>								
+		1	0	1	1		since $B_0 = 1$	
		0	0	0	0	Z	since $B_1 = 0$	
<hr/>								
+		0	1	0	1	1	addition	
		1	0	1	1	Z Z	since $B_2 = 1$	
<hr/>								
+		1	1	0	1	1	addition	
		1	0	1	1	Z Z Z	since $B_3 = 1$	
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								

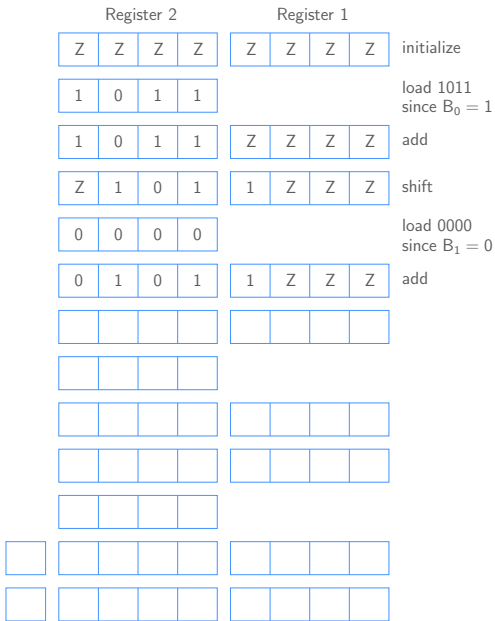
Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

		1	0	1	1		$A_3A_2A_1A_0$	(decimal 11)
	\times	1	1	0	1		$B_3B_2B_1B_0$	(decimal 13)
<hr/>								
+		1	0	1	1		since $B_0 = 1$	
		0	0	0	0	Z	since $B_1 = 0$	
<hr/>								
+		0	1	0	1	1	addition	
	1	0	1	1	Z	Z	since $B_2 = 1$	
<hr/>								
+		1	1	0	1	1	addition	
	1	0	1	1	Z	Z	since $B_3 = 1$	
<hr/>								
	1	0	0	0	1	1	addition	(decimal 143)

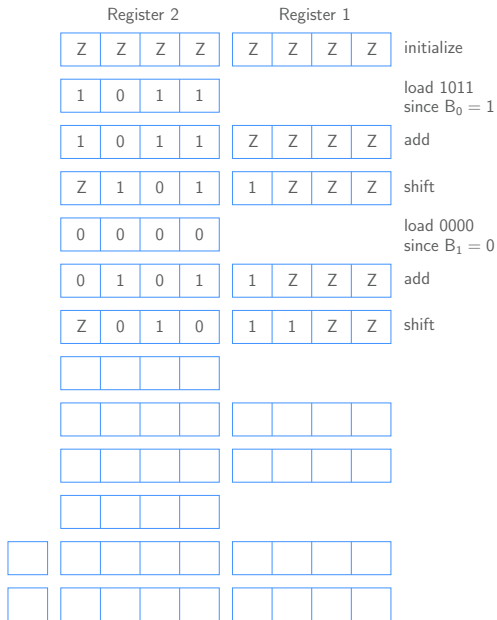Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

		1	0	1	1		$A_3A_2A_1A_0$	(decimal 11)
	\times	1	1	0	1		$B_3B_2B_1B_0$	(decimal 13)
<hr/>								
+		1	0	1	1		since $B_0 = 1$	
		0	0	0	0	Z	since $B_1 = 0$	
<hr/>								
+		0	1	0	1	1	addition	
	1	0	1	1	Z	Z	since $B_2 = 1$	
<hr/>								
+		1	1	0	1	1	addition	
	1	0	1	1	Z	Z	since $B_3 = 1$	
<hr/>								
	1	0	0	0	1	1	addition	(decimal 143)

Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.

Register 2				Register 1				
Z	Z	Z	Z	Z	Z	Z	Z	initialize
1	0	1	1					load 1011 since $B_0 = 1$
1	0	1	1	Z	Z	Z	Z	add
Z	1	0	1	1	Z	Z	Z	shift
0	0	0	0					load 0000 since $B_1 = 0$
0	1	0	1	1	Z	Z	Z	add
Z	0	1	0	1	1	Z	Z	shift
1	0	1	1					load 1011 since $B_2 = 1$

Multiplication using shift and add

		1	0	1	1		$A_3A_2A_1A_0$	(decimal 11)
	\times	1	1	0	1		$B_3B_2B_1B_0$	(decimal 13)
<hr/>								
+		1	0	1	1		since $B_0 = 1$	
		0	0	0	0	Z	since $B_1 = 0$	
<hr/>								
+		0	1	0	1	1	addition	
		1	0	1	1	Z Z	since $B_2 = 1$	
<hr/>								
+		1	1	0	1	1	addition	
		1	0	1	1	Z Z Z	since $B_3 = 1$	
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								
		1	0	0	0	1	1	1
		1	0	0	0	1	1	1
<hr/>								


Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.

Register 2				Register 1				
Z	Z	Z	Z	Z	Z	Z	Z	initialize
1	0	1	1					load 1011 since $B_0 = 1$
1	0	1	1	Z	Z	Z	Z	add
Z	1	0	1	1	Z	Z	Z	shift
0	0	0	0					load 0000 since $B_1 = 0$
0	1	0	1	1	Z	Z	Z	add
Z	0	1	0	1	1	Z	Z	shift
1	0	1	1					load 1011 since $B_2 = 1$
1	1	0	1	1	1	Z	Z	add

Multiplication using shift and add

	1	0	1	1	$A_3A_2A_1A_0$	(decimal 11)		
\times	1	1	0	1	$B_3B_2B_1B_0$	(decimal 13)		
<hr/>								
+		1	0	1	1	since $B_0 = 1$		
		0	0	0	Z	since $B_1 = 0$		
<hr/>								
+		0	1	0	1	1	addition	
	1	0	1	1	Z	Z	since $B_2 = 1$	
<hr/>								
+		1	1	0	1	1	1	addition
	1	0	1	1	Z	Z	Z	since $B_3 = 1$
<hr/>								
	1	0	0	0	1	1	1	addition (decimal 143)

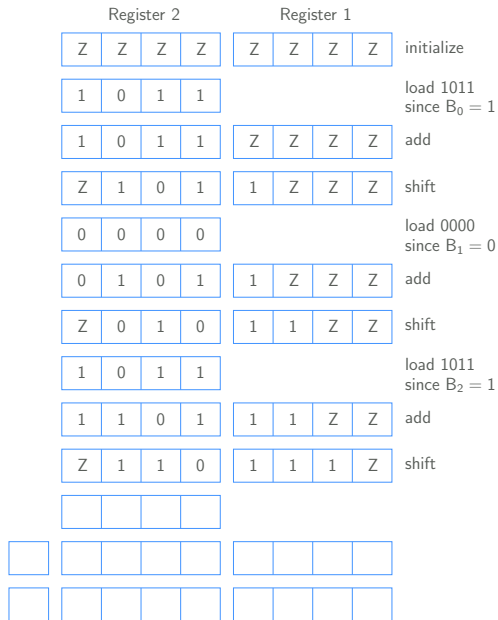
Note that Z = 0. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

	1	0	1	1	$A_3A_2A_1A_0$	(decimal 11)			
\times	1	1	0	1	$B_3B_2B_1B_0$	(decimal 13)			
<hr/>									
+		1	0	1	1	since $B_0 = 1$			
	0	0	0	0	Z	since $B_1 = 0$			
<hr/>									
+		0	1	0	1	1	addition		
	1	0	1	1	Z	Z	since $B_2 = 1$		
<hr/>									
+		1	1	0	1	1	1	addition	
	1	0	1	1	Z	Z	Z	since $B_3 = 1$	
<hr/>									
	1	0	0	0	1	1	1	1	addition (decimal 143)

 Note that Z = 0. We use Z to denote 0s which are independent of the numbers being multiplied.



Multiplication using shift and add

	1	0	1	1	$A_3A_2A_1A_0$	(decimal 11)			
\times	1	1	0	1	$B_3B_2B_1B_0$	(decimal 13)			
<hr/>									
+		1	0	1	1	since $B_0 = 1$			
	0	0	0	0	Z	since $B_1 = 0$			
<hr/>									
+		0	1	0	1	1	addition		
	1	0	1	1	Z	Z	since $B_2 = 1$		
<hr/>									
+		1	1	0	1	1	1	addition	
	1	0	1	1	Z	Z	Z	since $B_3 = 1$	
<hr/>									
	1	0	0	0	1	1	1	1	addition (decimal 143)

Note that Z = 0. We use Z to denote 0s which are independent of the numbers being multiplied.


Register 2				Register 1				
Z	Z	Z	Z	Z	Z	Z	Z	initialize
1	0	1	1					load 1011 since $B_0 = 1$
1	0	1	1	Z	Z	Z	Z	add
Z	1	0	1	1	Z	Z	Z	shift
0	0	0	0					load 0000 since $B_1 = 0$
0	1	0	1	1	Z	Z	Z	add
Z	0	1	0	1	1	Z	Z	shift
1	0	1	1					load 1011 since $B_2 = 1$
1	1	0	1	1	1	Z	Z	add
Z	1	1	0	1	1	1	Z	shift
1	0	1	1					load 1011 since $B_3 = 1$
1	0	0	0	1	1	1	Z	add


Multiplication using shift and add

		1	0	1	1	$A_3A_2A_1A_0$	(decimal 11)			
	\times	1	1	0	1	$B_3B_2B_1B_0$	(decimal 13)			
<hr/>										
+		1	0	1	1	since $B_0 = 1$				
		0	0	0	0	Z	since $B_1 = 0$			
<hr/>										
+		0	1	0	1	1	addition			
	1	0	1	1	Z	Z	since $B_2 = 1$			
<hr/>										
+		1	1	0	1	1	1	addition		
	1	0	1	1	Z	Z	Z	since $B_3 = 1$		
<hr/>										
	1	0	0	0	1	1	1	1	addition	(decimal 143)


Note that $Z = 0$. We use Z to denote 0s which are independent of the numbers being multiplied.

Register 2				Register 1				
Z	Z	Z	Z	Z	Z	Z	Z	initialize
1	0	1	1					load 1011 since $B_0 = 1$
1	0	1	1	Z	Z	Z	Z	add
Z	1	0	1	1	Z	Z	Z	shift
0	0	0	0					load 0000 since $B_1 = 0$
0	1	0	1	1	Z	Z	Z	add
Z	0	1	0	1	1	Z	Z	shift
1	0	1	1					load 1011 since $B_2 = 1$
1	1	0	1	1	1	Z	Z	add
Z	1	1	0	1	1	1	Z	shift
1	0	1	1					load 1011 since $B_3 = 1$
1	0	0	0	1	1	1	Z	add
Z	1	0	0	0	1	1	1	shift

 

 


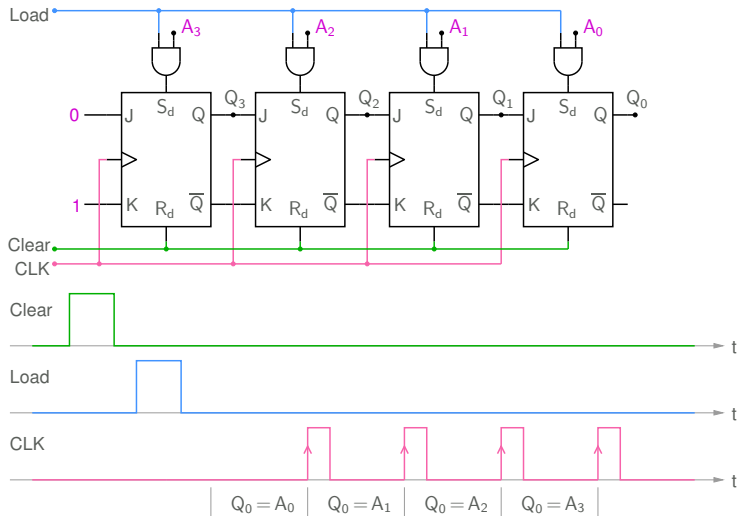* All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).




* All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).

 
* When $\text{Load} = 1$, $S_d = A_i$, $R_d = 0 \rightarrow A_i$ gets loaded into the i^{th} flip-flop.




 
- * All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).
- * When $\text{Load} = 1$, $S_d = A_i$, $R_d = 0 \rightarrow A_i$ gets loaded into the i^{th} flip-flop.
- * Subsequently, with every clock pulse, the data shifts right and appears *serially* at the output Q_0 .
 \rightarrow parallel in-serial out data movement



 
- * All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).
- * When $\text{Load} = 1$, $S_d = A_i$, $R_d = 0 \rightarrow A_i$ gets loaded into the i^{th} flip-flop.
- * Subsequently, with every clock pulse, the data shifts right and appears *serially* at the output Q_0 .
 \rightarrow parallel in-serial out data movement



 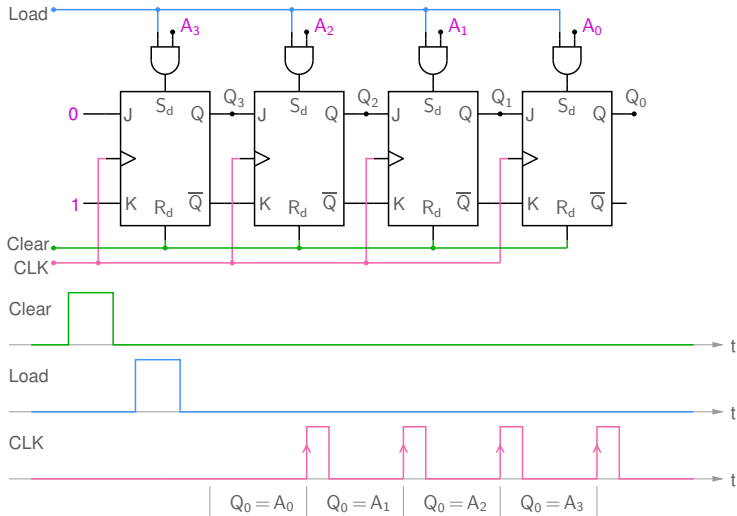
- * All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).
- * When $\text{Load} = 1$, $S_d = A_i$, $R_d = 0 \rightarrow A_i$ gets loaded into the i^{th} flip-flop.
- * Subsequently, with every clock pulse, the data shifts right and appears *serially* at the output Q_0 .
 \rightarrow parallel in-serial out data movement



 - * All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).
- * When $\text{Load} = 1$, $S_d = A_i$, $R_d = 0 \rightarrow A_i$ gets loaded into the i^{th} flip-flop.
- * Subsequently, with every clock pulse, the data shifts right and appears *serially* at the output Q_0 .
 \rightarrow parallel in-serial out data movement



 - * All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).
- * When $\text{Load} = 1$, $S_d = A_i$, $R_d = 0 \rightarrow A_i$ gets loaded into the i^{th} flip-flop.
- * Subsequently, with every clock pulse, the data shifts right and appears *serially* at the output Q_0 .
 \rightarrow parallel in-serial out data movement




0


0	0	0	0
---	---	---	---

●

 
- * All flip-flops are cleared in the beginning (with $R_d = \text{Clear} = 1$, $S_d = 0$).
- * When $\text{Load} = 1$, $S_d = A_i$, $R_d = 0 \rightarrow A_i$ gets loaded into the i^{th} flip-flop.
- * Subsequently, with every clock pulse, the data shifts right and appears *serially* at the output Q_0 .
 \rightarrow parallel in-serial out data movement




State transition diagram

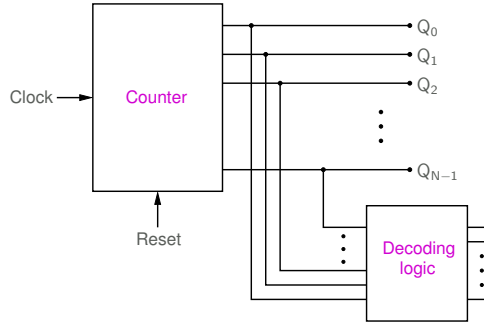

General configuration

 


State transition diagram

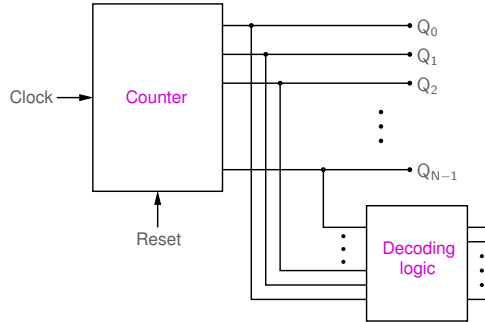


General configuration

 * A counter with k states is called a modulo- k (mod- k) counter.




State transition diagram

 


General configuration

 - * A counter with k states is called a modulo- k (mod- k) counter.
- * A counter can be made with flip-flops, each flip-flop serving as a memory element with two states (0 or 1).




State transition diagram

 


General configuration

- * A counter with k states is called a modulo- k (mod- k) counter.
- * A counter can be made with flip-flops, each flip-flop serving as a memory element with two states (0 or 1).
- * If there are N flip-flops in a counter, there are 2^N possible states (since each flip-flop can have $Q = 0$ or $Q = 1$). It is possible to exclude some of these states.
→ N flip-flops can be used to make a mod- k counter with $k \leq 2^N$.

 


State transition diagram

 


General configuration


- * A counter with k states is called a modulo- k (mod- k) counter.
- * A counter can be made with flip-flops, each flip-flop serving as a memory element with two states (0 or 1).
- * If there are N flip-flops in a counter, there are 2^N possible states (since each flip-flop can have $Q = 0$ or $Q = 1$). It is possible to exclude some of these states.
→ N flip-flops can be used to make a mod- k counter with $k \leq 2^N$.
- * Typically, a reset facility is also provided, which can be used to force a certain state to initialize the counter.

 


State transition diagram

 

state	Q ₀	Q ₁	Q ₂
1	0	0	0
2	1	1	0
3	1	1	1
4	0	1	1
5	1	0	1
1	0	0	0

 


X is 1 for state 3; else, it is 0.

 

X is 1 for state 3; else, it is 0.

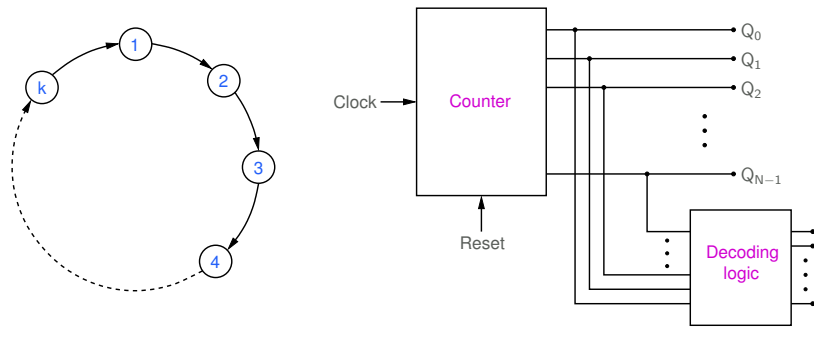
- * The counter outputs (i.e., the flip-flop outputs, Q_0, Q_1, \dots, Q_{N-1}) can be decoded using appropriate logic.




X is 1 for state 3; else, it is 0.

- * The counter outputs (i.e., the flip-flop outputs, Q_0, Q_1, \dots, Q_{N-1}) can be decoded using appropriate logic.
- * In particular, it is possible to have a decoder output (say, X) which is 1 only for state i , and 0 otherwise.
 → For k clock pulses, we get a single pulse at X, i.e., the clock frequency has been divided by k . For this reason, a mod- k counter is also called a divide-by- k counter.

A binary ripple counter

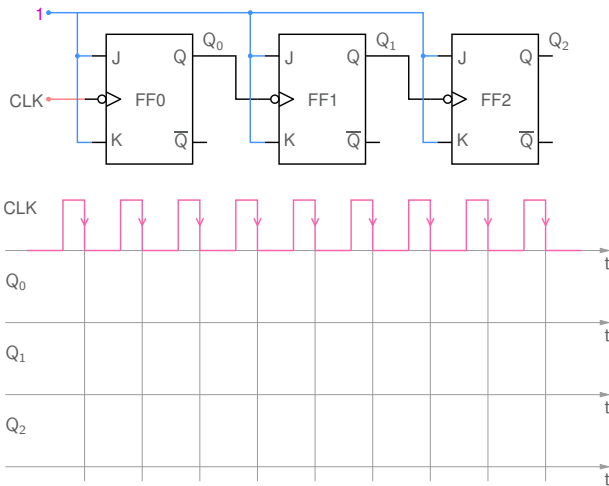


A binary ripple counter

 


- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.

A binary ripple counter

 


- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.
- * Since $J = K = 1$, each flip-flop will toggle when an active (in this case, negative) clock edge arrives.

A binary ripple counter

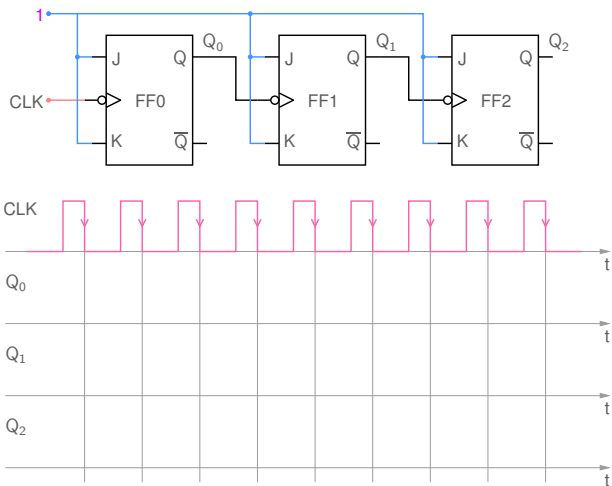


- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.
- * Since $J = K = 1$, each flip-flop will toggle when an active (in this case, negative) clock edge arrives.
- * For FF1 and FF2, Q_0 and Q_1 , respectively, provide the clock.

A binary ripple counter

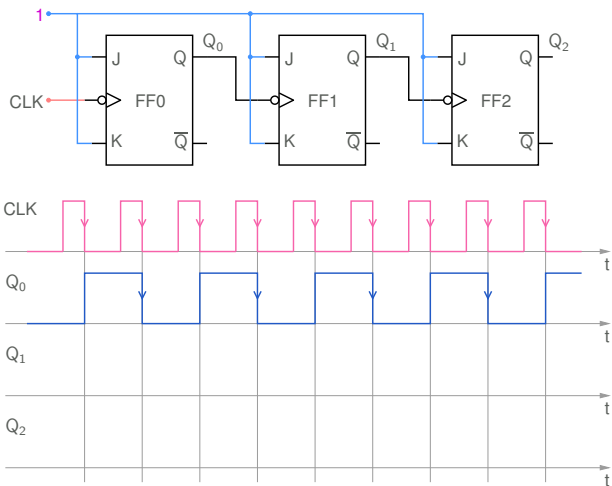


- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.
- * Since $J = K = 1$, each flip-flop will toggle when an active (in this case, negative) clock edge arrives.
- * For FF1 and FF2, Q_0 and Q_1 , respectively, provide the clock.

A binary ripple counter

 


- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.
- * Since $J = K = 1$, each flip-flop will toggle when an active (in this case, negative) clock edge arrives.
- * For FF1 and FF2, Q_0 and Q_1 , respectively, provide the clock.

A binary ripple counter

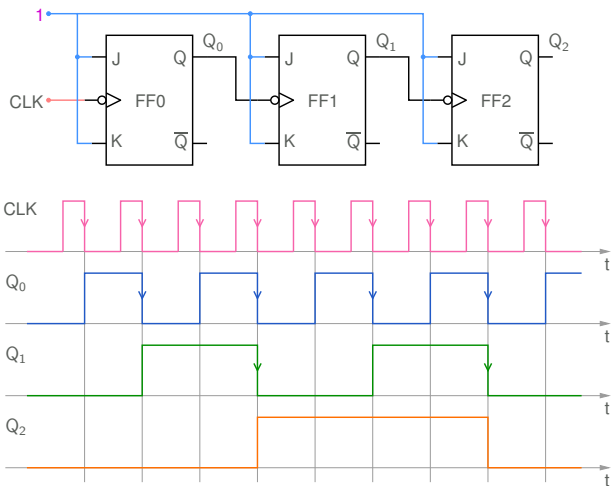

- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.
- * Since $J = K = 1$, each flip-flop will toggle when an active (in this case, negative) clock edge arrives.
- * For FF1 and FF2, Q_0 and Q_1 , respectively, provide the clock.

A binary ripple counter

 


Q ₂	Q ₁	Q ₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

↓ repeats

- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.
- * Since $J = K = 1$, each flip-flop will toggle when an active (in this case, negative) clock edge arrives.
- * For FF1 and FF2, Q_0 and Q_1 , respectively, provide the clock.

A binary ripple counter

 


Q ₂	Q ₁	Q ₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

↓ repeats

- * $J = K = 1$ for all flip-flops. Let $Q_0 = Q_1 = Q_2 = 0$ initially.
- * Since $J = K = 1$, each flip-flop will toggle when an active (in this case, negative) clock edge arrives.
- * For FF1 and FF2, Q_0 and Q_1 , respectively, provide the clock.
- * Note that the direct inputs S_d and R_d (not shown) are assumed to be $S_d = R_d = 0$ for all flip-flops, allowing normal flip-flop operation.


A binary ripple counter

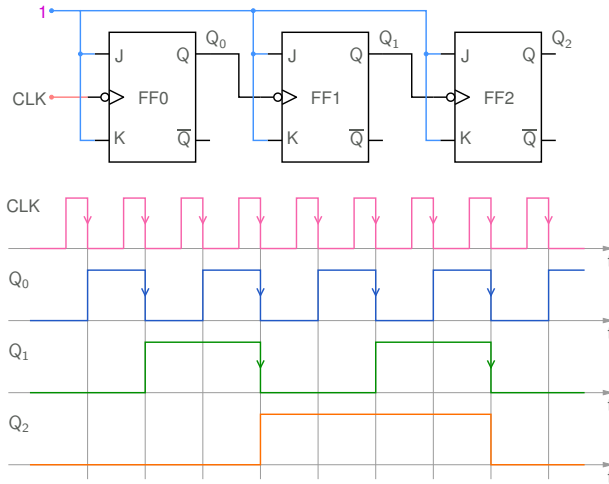

Q ₂	Q ₁	Q ₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

↓ repeats

A binary ripple counter

 


Q_2	Q_1	Q_0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

↓ repeats

- * The counter has 8 states, $Q_2 Q_1 Q_0 = 000, 001, 010, 011, 100, 101, 110, 111$.
→ it is a mod-8 counter. In particular, it is a *binary, mod-8, up* counter (since it counts *up* from 000 to 111).

A binary ripple counter

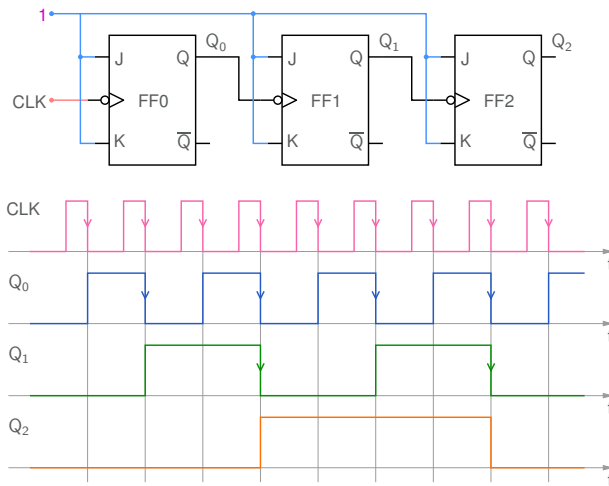


Q ₂	Q ₁	Q ₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

↓ repeats

- * The counter has 8 states, $Q_2 Q_1 Q_0 = 000, 001, 010, 011, 100, 101, 110, 111$.
→ it is a *mod-8* counter. In particular, it is a *binary, mod-8, up* counter (since it counts *up* from 000 to 111).
- * If the clock frequency is f_c , the frequency at the Q_0 , Q_1 , Q_2 outputs is $f_c/2$, $f_c/4$, $f_c/8$, respectively. For this counter, therefore, div-by-2, div-by-4, div-by-8 outputs are already available, without requiring decoding logic.

A binary ripple counter

 


Q ₂	Q ₁	Q ₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

↓ repeats

- * The counter has 8 states, $Q_2 Q_1 Q_0 = 000, 001, 010, 011, 100, 101, 110, 111$.
→ it is a mod-8 counter. In particular, it is a *binary, mod-8, up* counter (since it counts *up* from 000 to 111).
- * If the clock frequency is f_c , the frequency at the Q_0 , Q_1 , Q_2 outputs is $f_c/2$, $f_c/4$, $f_c/8$, respectively. For this counter, therefore, div-by-2, div-by-4, div-by-8 outputs are already available, without requiring decoding logic.
- * This type of counter is called a “ripple” counter since the clock transitions *ripple* through the flip-flops.


A binary ripple counter

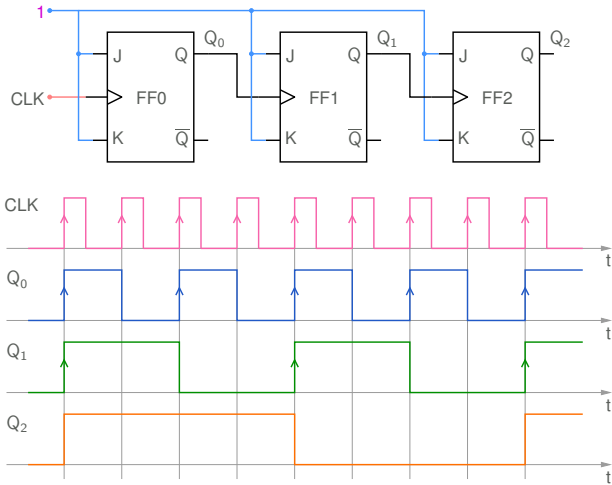

Q_2	Q_1	Q_0
0	0	0
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

↓ repeats



A binary ripple counter

 

Q_2	Q_1	Q_0
0	0	0
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0
↓ repeats		



* If positive edge-triggered flip-flops are used, we get a binary *down* counter (counting down from 111 to 000).

Binary ripple counters

 
 


* Home work: Sketch the waveforms (CLK, Q_0 , Q_1 , Q_2), and tabulate the counter states in each case.


Up-down binary ripple counters

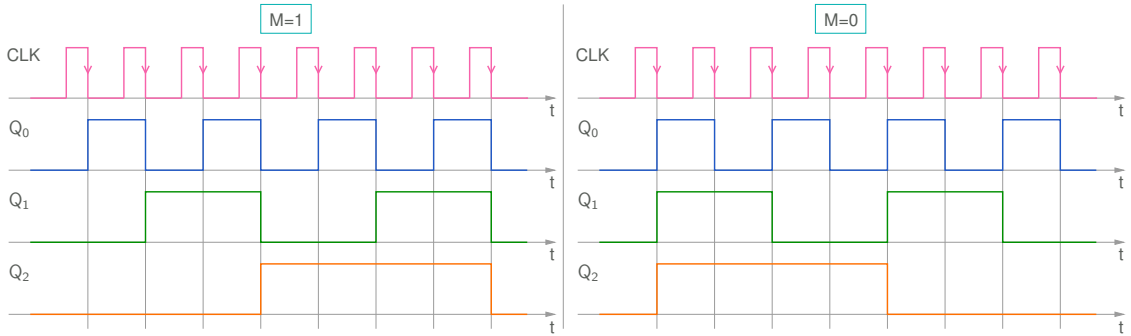 


Up-down binary ripple counters

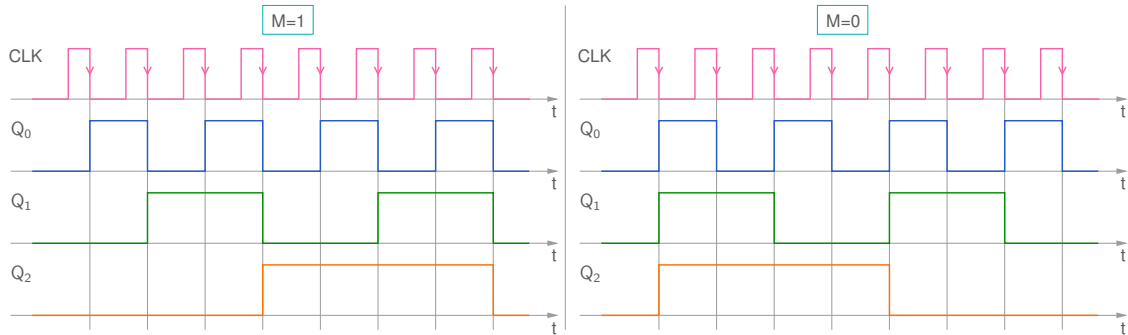 

 * When Mode (M) = 1, the counter counts up; else, it counts down. (SEQUEL file: ee101_counter_3.sqproj)




Decade counter using direct inputs

 

Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0


↓ repeats

SEQUEL file: ee101_counter_5.sqproj

 

Decade counter using direct inputs

 
- * When the counter reaches $Q_3 Q_2 Q_1 Q_0 = 1010$ (i.e., decimal 10), $Q_3 Q_1 = 1$, and the flip-flops are cleared to $Q_3 Q_2 Q_1 Q_0 = 0000$.



Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0


↓ repeats

SEQUENCE file: ee101_counter_5.sqproj

 

Decade counter using direct inputs

 - * When the counter reaches $Q_3 Q_2 Q_1 Q_0 = 1010$ (i.e., decimal 10), $Q_3 Q_1 = 1$, and the flip-flops are cleared to $Q_3 Q_2 Q_1 Q_0 = 0000$.
- * The counter counts from 0000 (decimal 0) to 1001 (decimal 9) → "decade counter."





Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0


↓ repeats

SEQUENCE file: ee101_counter_5.sqproj

A synchronous counter

  


A synchronous counter

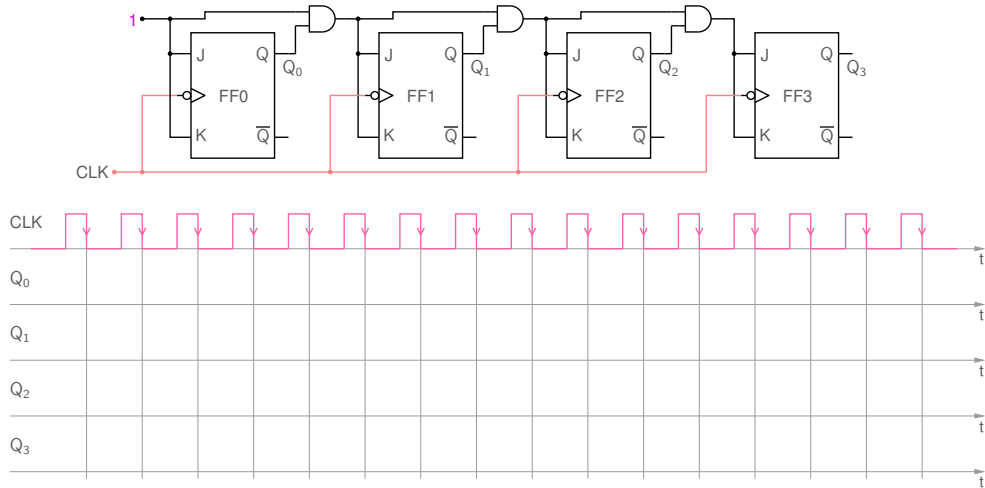


* Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.

A synchronous counter

 


- * Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- * $J_0 = K_0 = 1$, $J_1 = K_1 = Q_0$, $J_2 = K_2 = Q_1 Q_0$, $J_3 = K_3 = Q_2 Q_1 Q_0$.

A synchronous counter

 


- * Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- * $J_0 = K_0 = 1$, $J_1 = K_1 = Q_0$, $J_2 = K_2 = Q_1 Q_0$, $J_3 = K_3 = Q_2 Q_1 Q_0$.
- * FF0 toggles after every active edge.
FF1 toggles if $Q_0 = 1$ (just before the active clock edge); else, it retains its previous state. (Similarly, for FF2 and FF3)

A synchronous counter

 


- * Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- * $J_0 = K_0 = 1$, $J_1 = K_1 = Q_0$, $J_2 = K_2 = Q_1 Q_0$, $J_3 = K_3 = Q_2 Q_1 Q_0$.
- * FF0 toggles after every active edge.
FF1 toggles if $Q_0 = 1$ (just before the active clock edge); else, it retains its previous state. (Similarly, for FF2 and FF3)

A synchronous counter

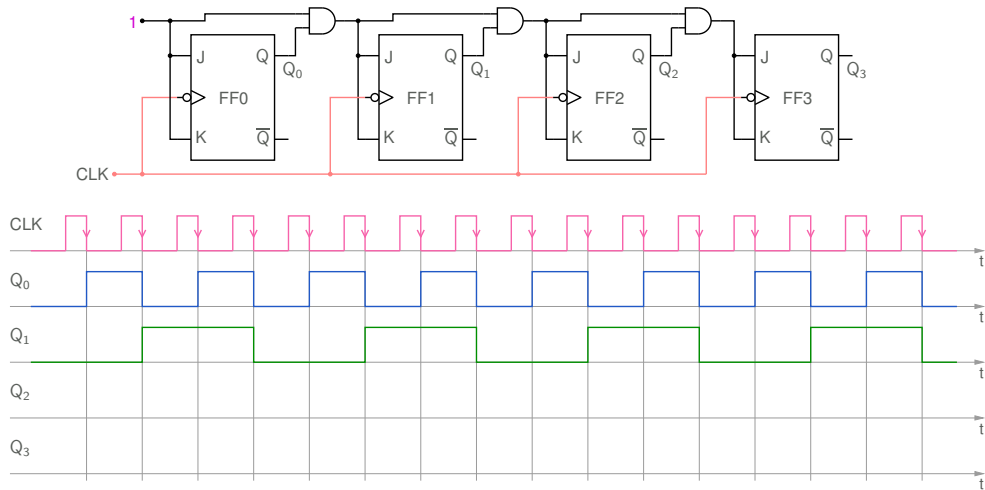


- * Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- * $J_0 = K_0 = 1$, $J_1 = K_1 = Q_0$, $J_2 = K_2 = Q_1 Q_0$, $J_3 = K_3 = Q_2 Q_1 Q_0$.
- * FF0 toggles after every active edge.
FF1 toggles if $Q_0 = 1$ (just before the active clock edge); else, it retains its previous state. (Similarly, for FF2 and FF3)

A synchronous counter

 


- * Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- * $J_0 = K_0 = 1$, $J_1 = K_1 = Q_0$, $J_2 = K_2 = Q_1 Q_0$, $J_3 = K_3 = Q_2 Q_1 Q_0$.
- * FF0 toggles after every active edge.
FF1 toggles if $Q_0 = 1$ (just before the active clock edge); else, it retains its previous state. (Similarly, for FF2 and FF3)

A synchronous counter

 


- * Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- * $J_0 = K_0 = 1$, $J_1 = K_1 = Q_0$, $J_2 = K_2 = Q_1 Q_0$, $J_3 = K_3 = Q_2 Q_1 Q_0$.
- * FF0 toggles after every active edge.
FF1 toggles if $Q_0 = 1$ (just before the active clock edge); else, it retains its previous state. (Similarly, for FF2 and FF3)


A synchronous counter

 

- * Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- * $J_0 = K_0 = 1$, $J_1 = K_1 = Q_0$, $J_2 = K_2 = Q_1 Q_0$, $J_3 = K_3 = Q_2 Q_1 Q_0$.
- * FF0 toggles after every active edge.
FF1 toggles if $Q_0 = 1$ (just before the active clock edge); else, it retains its previous state. (Similarly, for FF2 and FF3)
- * From the waveforms, we see that it is a binary up counter.

 


CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

 

CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1		

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0		

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1		

 
- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

 - * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
 $\rightarrow J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.



CLK	J	K	Q_{n+1}
↑	0	0	Q_n
↑	0	1	0
↑	1	0	1
↑	1	1	$\overline{Q_n}$


CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

- * Consider the *reverse* problem: We are given Q_n and the next desired state (Q_{n+1}). What should J and K be in order to make that happen?
- * $Q_n = 0, Q_{n+1} = 0$: We can either force $Q_{n+1} = 0$ with $J = 0, K = 1$, or let $Q_{n+1} = Q_n$ by making $J = 0, K = 0$.
→ $J = 0, K = X$ (i.e., K can be 0 or 1).
- * Similarly, work out the other entries in the table.
- * The table for a negative edge-triggered flip-flop would be identical except for the active edge.

Design of synchronous counters

state	Q_2	Q_1	Q_0
1	0	0	0
2	0	0	1
3	0	1	0
4	0	1	1
5	1	0	0
1	0	0	0

↓ repeats

 

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design a synchronous mod-5 counter with the given state transition table.

Design of synchronous counters

state	Q_2	Q_1	Q_0
-------	-------	-------	-------

1	0	0	0
---	---	---	---

2	0	0	1
---	---	---	---


3	0	1	0
---	---	---	---

4	0	1	1
---	---	---	---

5	1	0	0
---	---	---	---

1	0	0	0
---	---	---	---

↓ repeats

 

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0


Design a synchronous mod-5 counter with the given state transition table.

Outline of method:

Design of synchronous counters

state	Q_2	Q_1	Q_0
1	0	0	0
2	0	0	1
3	0	1	0
4	0	1	1
5	1	0	0
1	0	0	0

↓ repeats

 

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design a synchronous mod-5 counter with the given state transition table.

Outline of method:

* State 1 \rightarrow State 2 means


$Q_2: 0 \rightarrow 0,$

$Q_1: 0 \rightarrow 0,$

$Q_0: 0 \rightarrow 1.$

state	Q_2	Q_1	Q_0
1	0	0	0
2	0	0	1
3	0	1	0
4	0	1	1
5	1	0	0
1	0	0	0

↓ repeats

 

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design a synchronous mod-5 counter with the given state transition table.

Outline of method:

- * State 1 \rightarrow State 2 means

$Q_2: 0 \rightarrow 0,$

$Q_1: 0 \rightarrow 0,$

$Q_0: 0 \rightarrow 1.$

- * Refer to the right table. For $Q_2: 0 \rightarrow 0$, we must have $J_2 = 0$, $K_2 = X$, and so on.

Design of synchronous counters

state	Q_2	Q_1	Q_0
-------	-------	-------	-------

1 0 0 0

2 0 0 1


3 0 1 0

4 0 1 1

5 1 0 0

1 0 0 0

↓ repeats

 

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design a synchronous mod-5 counter with the given state transition table.

Outline of method:

- * State 1 \rightarrow State 2 means
 $Q_2: 0 \rightarrow 0$,
 $Q_1: 0 \rightarrow 0$,
 $Q_0: 0 \rightarrow 1$.
- * Refer to the right table. For $Q_2: 0 \rightarrow 0$, we must have $J_2 = 0$, $K_2 = X$, and so on.
- * When we cover all transitions in the left table, we have the truth tables for J_0 , K_0 , J_1 , K_1 , J_2 , K_2 in terms of Q_0 , Q_1 , Q_2 .

Design of synchronous counters

state	Q_2	Q_1	Q_0
-------	-------	-------	-------

1 0 0 0

2 0 0 1


3 0 1 0

4 0 1 1

5 1 0 0

1 0 0 0

↓ repeats

 

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design a synchronous mod-5 counter with the given state transition table.

Outline of method:

- * State 1 \rightarrow State 2 means
 $Q_2: 0 \rightarrow 0$,
 $Q_1: 0 \rightarrow 0$,
 $Q_0: 0 \rightarrow 1$.
- * Refer to the right table. For $Q_2: 0 \rightarrow 0$, we must have $J_2 = 0$, $K_2 = X$, and so on.
- * When we cover all transitions in the left table, we have the truth tables for J_0 , K_0 , J_1 , K_1 , J_2 , K_2 in terms of Q_0 , Q_1 , Q_2 .
- * The last step is to come up with suitable functions for J_0 , K_0 , J_1 , K_1 , J_2 , K_2 in terms of Q_0 , Q_1 , Q_2 . This can be done with K-maps. (If the number of flip-flops is more than 4, other techniques can be employed.)

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0						
2	0	0	1						
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0						
2	0	0	1						
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X				
2	0	0	1						
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X		
2	0	0	1						
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1						
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1						
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X				
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X		
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0						
4	0	1	1						
5	1	0	0						
1	0	0	0						



CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X				
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0		
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1						
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1						
5	1	0	0						
1	0	0	0						



CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X				
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1		
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0						
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0						
1	0	0	0						



CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1				
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X		
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design of synchronous counters

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

- * We now have the truth tables for J_0 , K_0 , J_1 , K_1 , J_2 , K_2 in terms of Q_0 , Q_1 , Q_2 . The next step is to find logical functions for each of them.

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

CLK	Q_n	Q_{n+1}	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

- * We now have the truth tables for J_0 , K_0 , J_1 , K_1 , J_2 , K_2 in terms of Q_0 , Q_1 , Q_2 . The next step is to find logical functions for each of them.
- * Note that we have not tabulated the J and K values for those combinations of Q_0 , Q_1 , Q_2 which do not occur in the state transition table (such as $Q_2 Q_1 Q_0 = 110$). We treat these as don't care conditions.

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

J_2

$Q_2 Q_1$	00	01	11	10
Q_0				
0	0	0	X	X
1	0	1	X	X

K_2

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	X	X	1
1	X	X	X	X

J_1

$Q_2 Q_1$	00	01	11	10
Q_0				
0	0	X	X	0
1	1	X	X	X

K_1

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	0	X	X
1	X	1	X	X

J_0

$Q_2 Q_1$	00	01	11	10
Q_0				
0	1	1	X	0
1	X	X	X	X

K_0

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	X	X	X
1	1	1	X	X

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

J_2

$Q_2 Q_1$	00	01	11	10
Q_0				
0	0	0	X	X
1	0	1	X	X

K_2

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	X	X	1
1	X	X	X	X

J_1

$Q_2 Q_1$	00	01	11	10
Q_0				
0	0	X	X	0
1	1	X	X	X

K_1

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	0	X	X
1	X	1	X	X

J_0

$Q_2 Q_1$	00	01	11	10
Q_0				
0	1	1	X	0
1	X	X	X	X

K_0

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	X	X	X
1	1	1	X	X

* We treat the unused states ($Q_2 Q_1 Q_0 = 101, 110, 111$) as (additional) don't care conditions. Since these are different from the don't care conditions arising from the state transition table, we mark them with a different colour.

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

J_2

$Q_2 Q_1$	00	01	11	10
Q_0				
0	0	0	X	X
1	0	1	X	X

K_2

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	X	X	1
1	X	X	X	X

J_1

$Q_2 Q_1$	00	01	11	10
Q_0				
0	0	X	X	0
1	1	X	X	X

K_1

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	0	X	X
1	X	1	X	X

J_0

$Q_2 Q_1$	00	01	11	10
Q_0				
0	1	1	X	0
1	X	X	X	X

K_0

$Q_2 Q_1$	00	01	11	10
Q_0				
0	X	X	X	X
1	1	1	X	X

- * We treat the unused states ($Q_2 Q_1 Q_0 = 101, 110, 111$) as (additional) don't care conditions. Since these are different from the don't care conditions arising from the state transition table, we mark them with a different colour.
- * We will assume that a suitable initialization facility is provided to ensure that the counter starts up in one of the five allowed states (say, $Q_2 Q_1 Q_0 = 000$).

state	Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

J_2

	$Q_2 Q_1$	00	01	11	10
Q_0	0	0	0	X	X
	1	0	1	X	X

K_2

	$Q_2 Q_1$	00	01	11	10
Q_0	0	X	X	X	1
	1	X	X	X	X

J_1

	$Q_2 Q_1$	00	01	11	10
Q_0	0	0	X	X	0
	1	1	X	X	X

K_1

	$Q_2 Q_1$	00	01	11	10
Q_0	0	X	0	X	X
	1	X	1	X	X



J_0

	$Q_2 Q_1$	00	01	11	10
Q_0	0	1	1	X	0
	1	X	X	X	X

K_0


	$Q_2 Q_1$	00	01	11	10
Q_0	0	X	X	X	X
	1	1	1	X	X

- * We treat the unused states ($Q_2 Q_1 Q_0 = 101, 110, 111$) as (additional) don't care conditions. Since these are different from the don't care conditions arising from the state transition table, we mark them with a different colour.
- * We will assume that a suitable initialization facility is provided to ensure that the counter starts up in one of the five allowed states (say, $Q_2 Q_1 Q_0 = 000$).
- * From the K-maps, $J_2 = Q_1 Q_0$, $K_2 = 1$, $J_1 = Q_0$, $K_1 = Q_0$, $J_0 = \overline{Q_2}$, $K_0 = 1$.

  


SEQUEL file: ee101_counter_6.sqproj

 Design of synchronous counters: verification



 
$$\begin{aligned} * \quad & J_2 = Q_1 Q_0, \\ & K_2 = 1, \\ & J_1 = Q_0, \\ & K_1 = Q_0, \\ & J_0 = \overline{Q_2}, \\ & K_0 = 1. \end{aligned}$$




SEQUEL file: ee101_counter_6.sqproj

 Design of synchronous counters: verification




- * $J_2 = Q_1 Q_0$,
 $K_2 = 1$,
 $J_1 = Q_0$,
 $K_1 = Q_0$,
 $J_0 = \overline{Q_2}$,
 $K_0 = 1$.

 - * Note that the design is independent of whether positive or negative edge-triggered flip-flops are used.






SEQUENCE file: ee101_counter_6.sqproj





Combination of counters: Approach 1

 





Combination of counters: Approach 1

   





Combination of counters: Approach 1

    





Combination of counters: Approach 1

    

Combination of counters: Approach 1

   
 


Combination of counters: Approach 1

    


→ the combined counter is a mod- $k_1 k_2$ counter.

Combination of counters: example

  



mod-2 counter

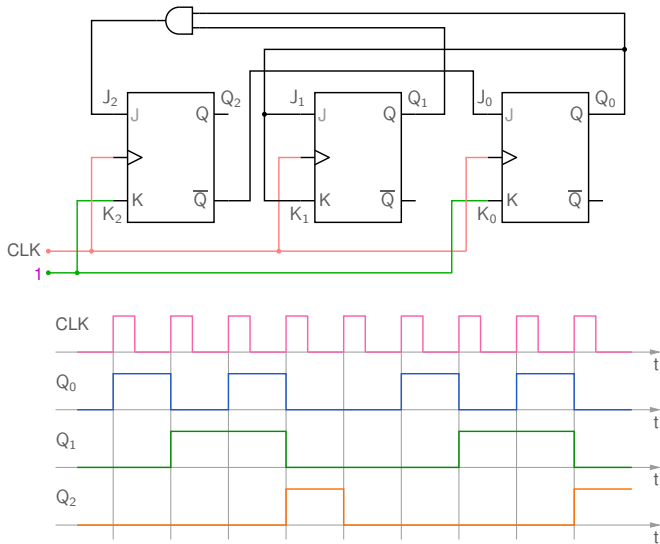


mod-5 counter

Combination of counters: example



SEQUEL file: ee101_counter_7.sqproj

 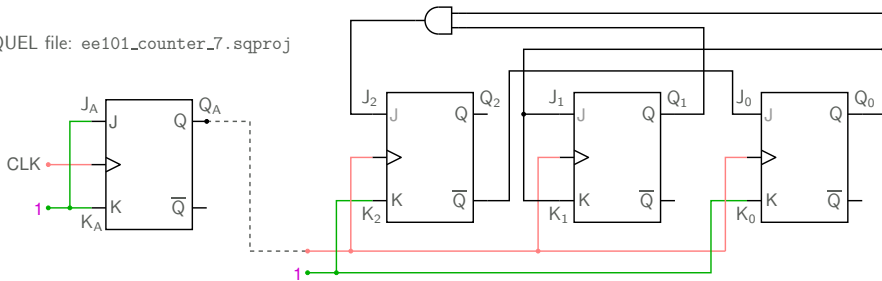



Combination of counters: Approach 2

 



Combination of counters: Approach 2

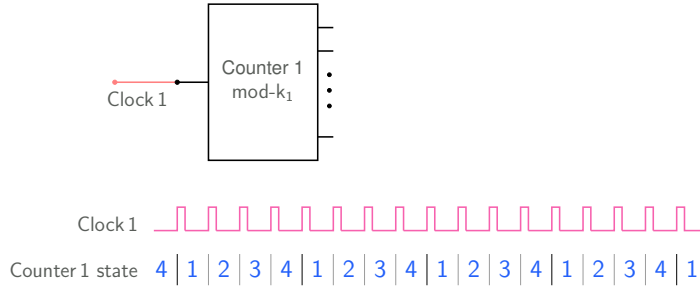 



Combination of counters: Approach 2

  



Combination of counters: Approach 2

  



Combination of counters: Approach 2

  

Combination of counters: Approach 2

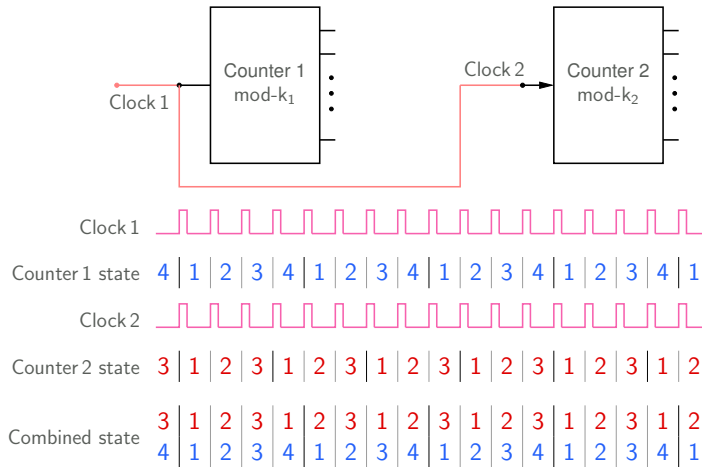
 


Combination of counters: Approach 2

 
 


→ the combined counter is a mod- k_1k_2 counter.

  Combination of counters: example (same as before)





mod-2 counter

  

mod-5 counter

Combination of counters: example


SEQUEL file: ee101_counter_8.sqproj

 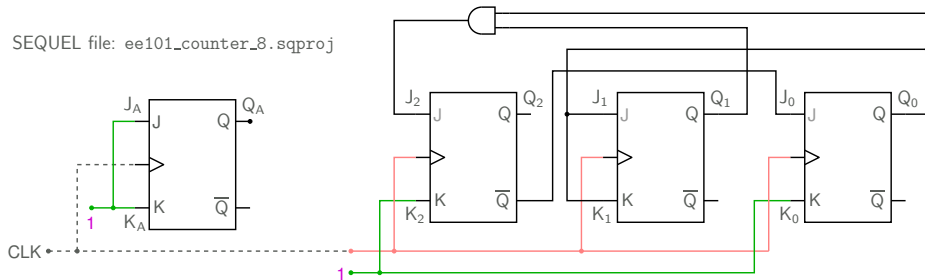

The 555 timer is useful in timer, pulse generation, and oscillator applications. We will look at two common applications.


The 555 timer is useful in timer, pulse generation, and oscillator applications. We will look at two common applications.

- * Monostable multivibrator

 



The 555 timer is useful in timer, pulse generation, and oscillator applications. We will look at two common applications.

- * Monostable multivibrator


 


- * Astable multivibrator


 


 

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
0	0	previous	

  


R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
0	0	previous	

  



R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
0	0	previous	





555 monostable multivibrator

 



555 monostable multivibrator

 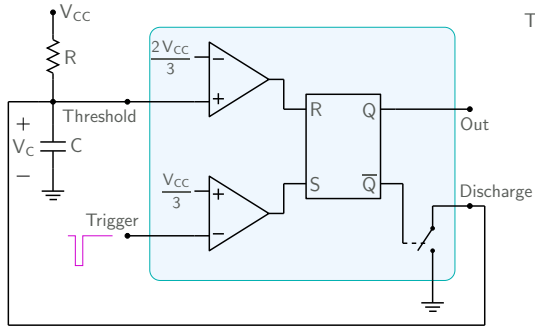


555 monostable multivibrator

  


555 monostable multivibrator

 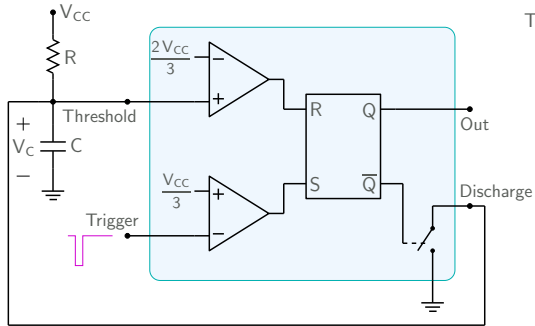


555 monostable multivibrator

 

$$V_C(t) = V_{CC} (1 - e^{-t/\tau})$$

 


555 monostable multivibrator

 


$$V_C(t) = V_{CC} (1 - e^{-t/\tau})$$
 
$$\rightarrow \frac{2V_{CC}}{3} = V_{CC} (1 - e^{-T/\tau})$$




555 monostable multivibrator

 


$$V_C(t) = V_{CC} (1 - e^{-t/\tau})$$

$$\rightarrow \frac{2V_{CC}}{3} = V_{CC} (1 - e^{-T/\tau})$$
 
$$\rightarrow e^{-T/\tau} = \frac{1}{3} \rightarrow \boxed{T = \tau \log 3 \approx 1.1 \tau}$$



555 monostable multivibrator

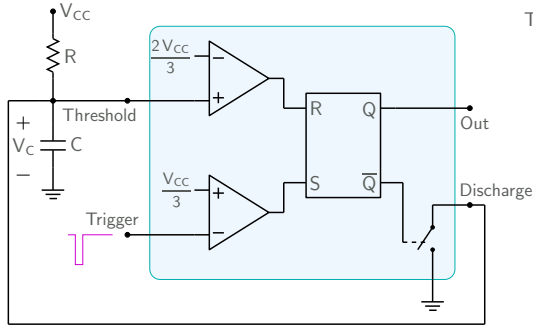


$$V_C(t) = V_{CC} (1 - e^{-t/\tau})$$


$$\rightarrow \frac{2V_{CC}}{3} = V_{CC} (1 - e^{-T/\tau})$$

$$\rightarrow e^{-T/\tau} = \frac{1}{3} \rightarrow \boxed{T = \tau \log 3 \approx 1.1 \tau}$$



SEQUEL file: ic555_mono_1.sqproj

 


555 astable multivibrator

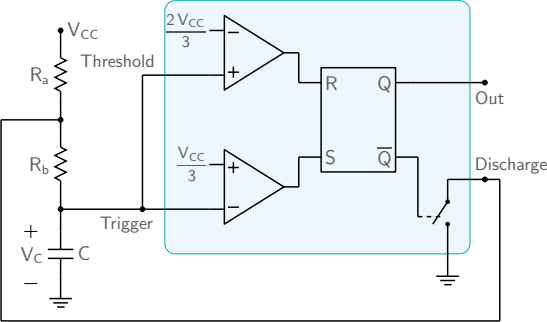

555 astable multivibrator

  


555 astable multivibrator

 


Charging:
 
$$V_C(0) = \frac{V_{CC}}{3}, \quad V_C(\infty) = V_{CC}.$$



555 astable multivibrator

 


Charging:


$$V_C(0) = \frac{V_{CC}}{3}, \quad V_C(\infty) = V_{CC}.$$

$$\text{Let } V_C(t) = A e^{-t/\tau_1} + B$$
 
$$\rightarrow B = V_{CC}, \quad A = -\frac{2V_{CC}}{3}$$



555 astable multivibrator

 


Charging:

$$V_C(0) = \frac{V_{CC}}{3}, \quad V_C(\infty) = V_{CC}.$$


$$\text{Let } V_C(t) = A e^{-t/\tau_1} + B$$

$$\rightarrow B = V_{CC}, \quad A = -\frac{2V_{CC}}{3}$$
 
$$\frac{2V_{CC}}{3} = -\frac{2V_{CC}}{3} e^{-T_H/\tau_1} + V_{CC}$$



555 astable multivibrator

 

Charging:


$$V_C(0) = \frac{V_{CC}}{3}, \quad V_C(\infty) = V_{CC}.$$

$$\text{Let } V_C(t) = A e^{-t/\tau_1} + B$$


$$\rightarrow B = V_{CC}, \quad A = -\frac{2V_{CC}}{3}$$

$$\frac{2V_{CC}}{3} = -\frac{2V_{CC}}{3} e^{-T_H/\tau_1} + V_{CC}$$


 
$$\rightarrow T_H = \tau_1 \log 2, \text{ with } \tau_1 = (R_a + R_b) C.$$




555 astable multivibrator

 

555 astable multivibrator

  


555 astable multivibrator

 


Discharging: $V_C(0) = \frac{2V_{CC}}{3}$, $V_C(\infty) = 0$.
 
$$\rightarrow V_C(t) = \frac{2V_{CC}}{3} e^{-t/\tau_2}$$




555 astable multivibrator

 


Discharging: $V_C(0) = \frac{2V_{CC}}{3}$, $V_C(\infty) = 0$.

$$\rightarrow V_C(t) = \frac{2V_{CC}}{3} e^{-t/\tau_2}$$
 
$$\frac{V_{CC}}{3} = \frac{2V_{CC}}{3} e^{-T_L/\tau_2}$$



555 astable multivibrator

 


Discharging: $V_C(0) = \frac{2V_{CC}}{3}$, $V_C(\infty) = 0$.


$$\rightarrow V_C(t) = \frac{2V_{CC}}{3} e^{-t/\tau_2}$$

$$\frac{V_{CC}}{3} = \frac{2V_{CC}}{3} e^{-T_L/\tau_2}$$
 
$$\rightarrow T_L = \tau_2 \log 2, \text{ with } \tau_2 = R_b C.$$



555 astable multivibrator

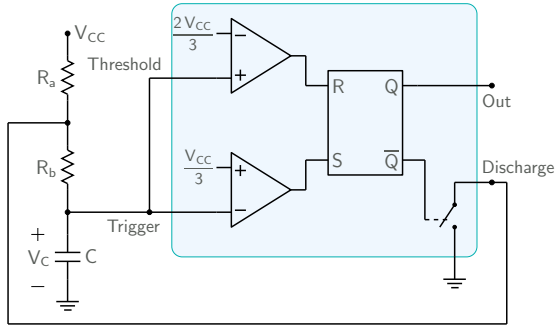

Discharging: $V_C(0) = \frac{2V_{CC}}{3}$, $V_C(\infty) = 0$.

$$\rightarrow V_C(t) = \frac{2V_{CC}}{3} e^{-t/\tau_2}$$

$$\frac{V_{CC}}{3} = \frac{2V_{CC}}{3} e^{-T_L/\tau_2}$$

$$\rightarrow T_L = \tau_2 \log 2, \text{ with } \tau_2 = R_b C.$$

SEQUEL file: ic555_astable_1.sqproj

