
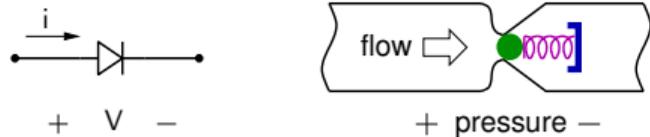


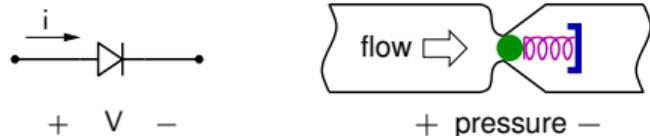


- * A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).



- * A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).
- * A check valve presents a small resistance if the pressure $p > 0$, but blocks the flow (i.e., presents a large resistance) if $p < 0$.





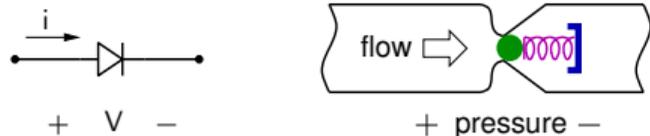- * A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).
- * A check valve presents a small resistance if the pressure $p > 0$, but blocks the flow (i.e., presents a large resistance) if $p < 0$.
- * Similarly, a diode presents a small resistance in the forward direction and a large resistance in the reverse direction.



- * A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).
- * A check valve presents a small resistance if the pressure $p > 0$, but blocks the flow (i.e., presents a large resistance) if $p < 0$.
- * Similarly, a diode presents a small resistance in the forward direction and a large resistance in the reverse direction.
- * Note: In a practical diode, the resistance $R_D = V/i$ is a nonlinear function of the applied voltage V . However, it is often a good approximation to treat it as a constant resistance which is small if V is positive and large if V is negative.

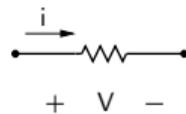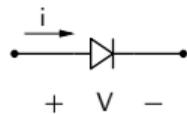
Simple models: $R_{\text{on}}/R_{\text{off}}$ model



$$R = R_{\text{on}} \text{ if } V > 0$$


$$R = R_{\text{off}} \text{ if } V < 0$$

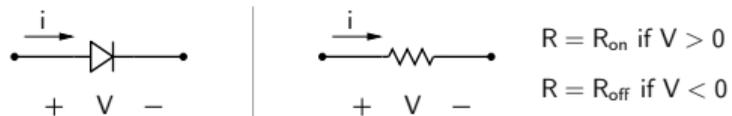Simple models: $R_{\text{on}}/R_{\text{off}}$ model





- * Since the resistance is different in the forward and reverse directions, the $i - V$ relationship is not a straight line.

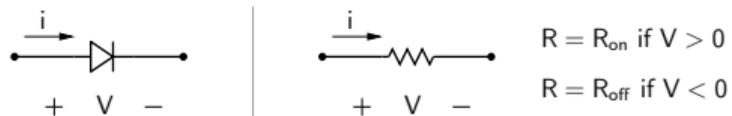Simple models: $R_{\text{on}}/R_{\text{off}}$ model



- * Since the resistance is different in the forward and reverse directions, the $i - V$ relationship is not a straight line.
- * Examples:

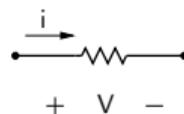
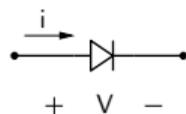
Simple models: $R_{\text{on}}/R_{\text{off}}$ model




$$R = R_{\text{on}} \text{ if } V > 0$$


$$R = R_{\text{off}} \text{ if } V < 0$$

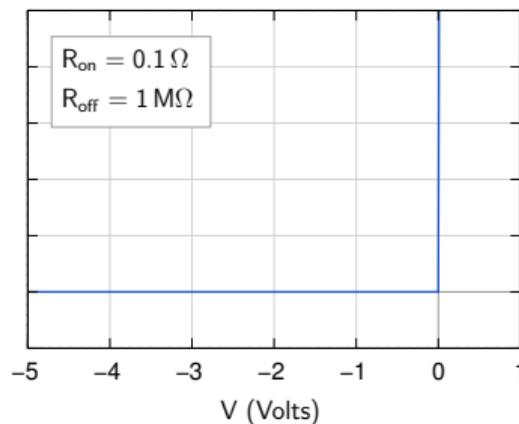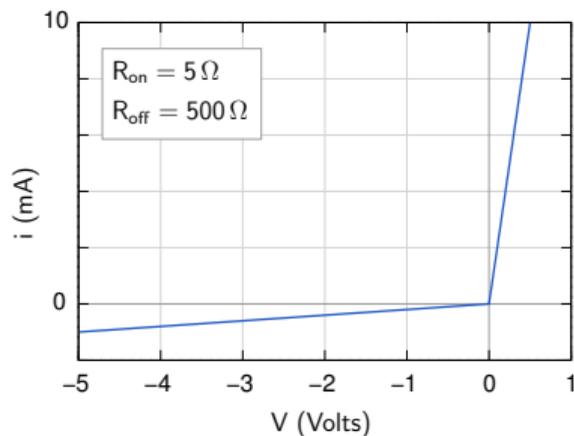- * Since the resistance is different in the forward and reverse directions, the $i - V$ relationship is not a straight line.
- * Examples:




Simple models: ideal switch

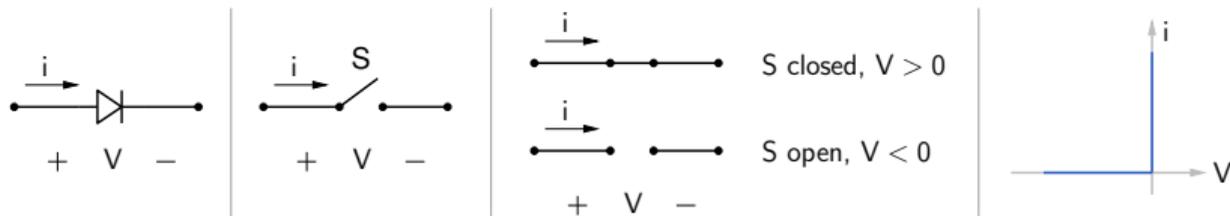


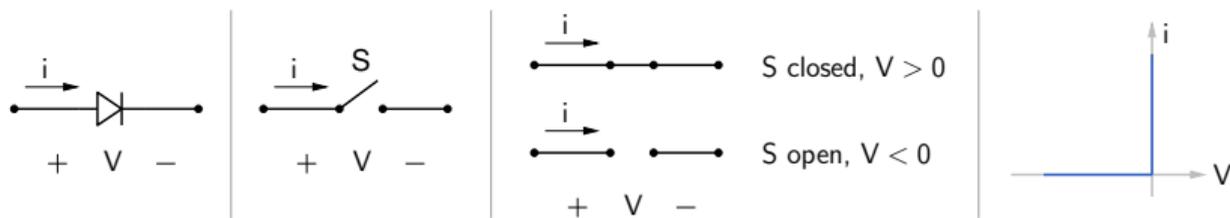

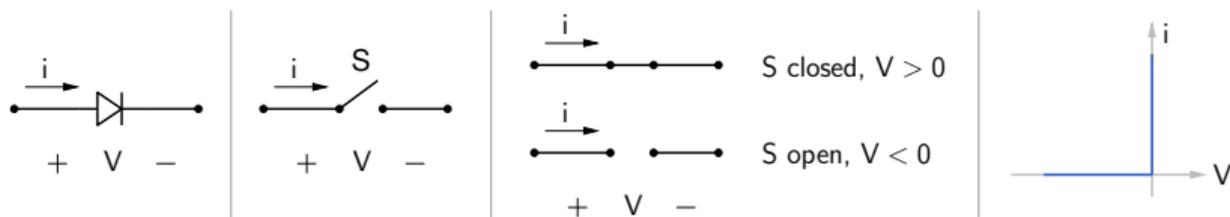* Forward bias: $i > 0$ A, $V = 0$ V, \rightarrow S is closed (a perfect contact).




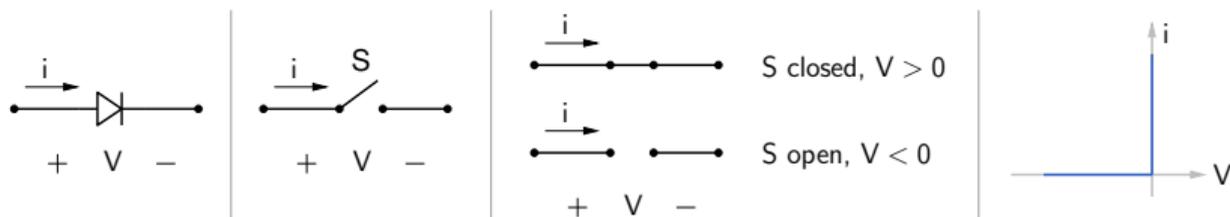- * Forward bias: $i > 0\text{ A}$, $V = 0\text{ V}$, $\rightarrow S$ is closed (a perfect contact).
- * Reverse bias: $V < 0\text{ V}$, $i = 0\text{ A}$ $\rightarrow S$ is open (a perfect open circuit). The diode is said to “block” the reverse applied voltage.




- * Forward bias: $i > 0\text{ A}$, $V = 0\text{ V}$, $\rightarrow S$ is closed (a perfect contact).
- * Reverse bias: $V < 0\text{ V}$, $i = 0\text{ A}$ $\rightarrow S$ is open (a perfect open circuit). The diode is said to “block” the reverse applied voltage.
- * The actual values of V and i for a diode in a circuit get determined by the i - V relationship of the diode *and* the constraints on V and i imposed by the circuit.

Shockley diode equation

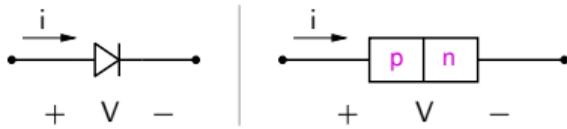

Shockley diode equation

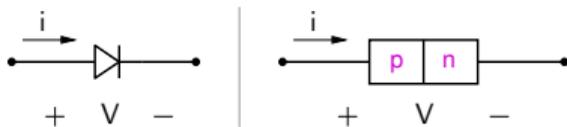

$$i = I_s \left[\exp \left(\frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$


k_B = Boltzmann's constant = $1.38 \times 10^{-23} \text{ J/K}$.

q = electron charge = $1.602 \times 10^{-19} \text{ Coul}$.

T = temperature in $^{\circ}\text{K}$.

$V_T \approx 25 \text{ mV}$ at room temperature (27°C).

Shockley diode equation

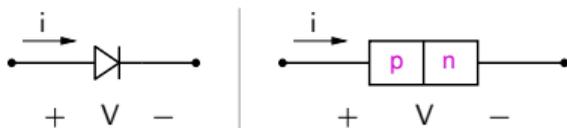

$$i = I_s \left[\exp \left(\frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

k_B = Boltzmann's constant = $1.38 \times 10^{-23} \text{ J/K}$.


q = electron charge = $1.602 \times 10^{-19} \text{ Coul}$.

T = temperature in $^{\circ}\text{K}$.

$V_T \approx 25 \text{ mV}$ at room temperature (27°C).

* I_s is called the "reverse saturation current."

Shockley diode equation

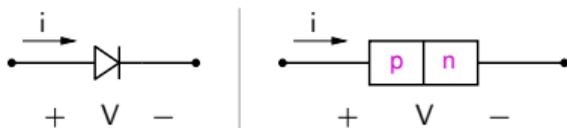

$$i = I_s \left[\exp \left(\frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

k_B = Boltzmann's constant = $1.38 \times 10^{-23} \text{ J/K}$.


q = electron charge = $1.602 \times 10^{-19} \text{ Coul}$.

T = temperature in $^{\circ}\text{K}$.

$V_T \approx 25 \text{ mV}$ at room temperature (27°C).

- * I_s is called the “reverse saturation current.”
- * For a typical low-power silicon diode, I_s is of the order of 10^{-13} A (i.e., 0.1 pA).

Shockley diode equation

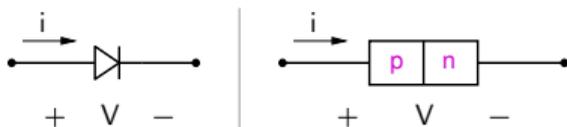

$$i = I_s \left[\exp \left(\frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

k_B = Boltzmann's constant = $1.38 \times 10^{-23} \text{ J/K}$.


q = electron charge = $1.602 \times 10^{-19} \text{ Coul}$.

T = temperature in $^\circ\text{K}$.

$V_T \approx 25 \text{ mV}$ at room temperature (27°C).

- * I_s is called the “reverse saturation current.”
- * For a typical low-power silicon diode, I_s is of the order of 10^{-13} A (i.e., 0.1 pA).
- * Although I_s is very small, it gets multiplied by a large exponential factor, giving a diode current of several mA for $V \approx 0.7 \text{ V}$ in a silicon diode.

Shockley diode equation

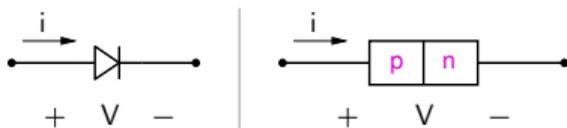

$$i = I_s \left[\exp \left(\frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

$k_B =$ Boltzmann's constant $= 1.38 \times 10^{-23} \text{ J/K}$.


$q =$ electron charge $= 1.602 \times 10^{-19} \text{ Coul}$.

$T =$ temperature in $^{\circ}\text{K}$.

$V_T \approx 25 \text{ mV}$ at room temperature (27°C).

- * I_s is called the “reverse saturation current.”
- * For a typical low-power silicon diode, I_s is of the order of 10^{-13} A (i.e., 0.1 pA).
- * Although I_s is very small, it gets multiplied by a large exponential factor, giving a diode current of several mA for $V \approx 0.7 \text{ V}$ in a silicon diode.
- * The “turn-on” voltage (V_{on}) of a diode depends on the value of I_s . V_{on} may be defined as the voltage at which the diode starts carrying a substantial forward current (say, a few mA).
For a silicon diode, $V_{\text{on}} \approx 0.7 \text{ V}$.
For LEDs, V_{on} varies from about 1.8 V (red) to 3.3 V (blue).


Shockley diode equation

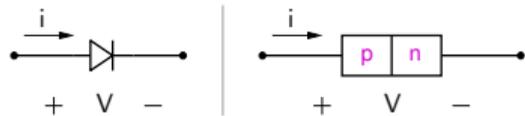

$$i = I_s \left[\exp \left(\frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

Example: $I_s = 1 \times 10^{-13}$ A, $V_T = 25$ mV.

Shockley diode equation

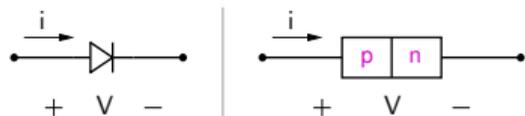

$$i = I_s \left[\exp \left(\frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

Example: $I_s = 1 \times 10^{-13}$ A, $V_T = 25$ mV.

V	$x = V/V_T$	e^x	i (Amp)
0.1	3.87	0.479×10^2	0.469×10^{-11}
0.2	7.74	0.229×10^4	0.229×10^{-9}
0.3	11.6	0.110×10^6	0.110×10^{-7}
0.4	15.5	0.525×10^7	0.525×10^{-6}
0.5	19.3	0.251×10^9	0.251×10^{-4}
0.6	23.2	0.120×10^{11}	0.120×10^{-2}
0.62	24.0	0.260×10^{11}	0.260×10^{-2}
0.64	24.8	0.565×10^{11}	0.565×10^{-2}
0.66	25.5	0.122×10^{12}	0.122×10^{-1}
0.68	26.3	0.265×10^{12}	0.265×10^{-1}
0.70	27.1	0.575×10^{12}	0.575×10^{-1}
0.72	27.8	0.125×10^{13}	0.125


Shockley diode equation





$$i = I_s \left[\exp\left(\frac{V}{V_T}\right) - 1 \right], \text{ where } V_T = k_B T / q.$$

Example: $I_s = 1 \times 10^{-13}$ A, $V_T = 25$ mV.

V	$x = V/V_T$	e^x	i (Amp)
0.1	3.87	0.479×10^2	0.469×10^{-11}
0.2	7.74	0.229×10^4	0.229×10^{-9}
0.3	11.6	0.110×10^6	0.110×10^{-7}
0.4	15.5	0.525×10^7	0.525×10^{-6}
0.5	19.3	0.251×10^9	0.251×10^{-4}
0.6	23.2	0.120×10^{11}	0.120×10^{-2}
0.62	24.0	0.260×10^{11}	0.260×10^{-2}
0.64	24.8	0.565×10^{11}	0.565×10^{-2}
0.66	25.5	0.122×10^{12}	0.122×10^{-1}
0.68	26.3	0.265×10^{12}	0.265×10^{-1}
0.70	27.1	0.575×10^{12}	0.575×10^{-1}
0.72	27.8	0.125×10^{13}	0.125


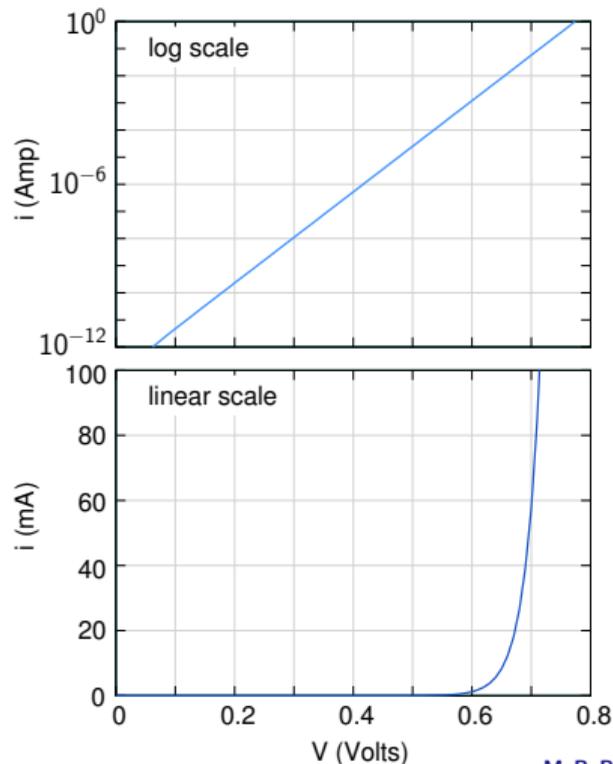


Diode circuit model

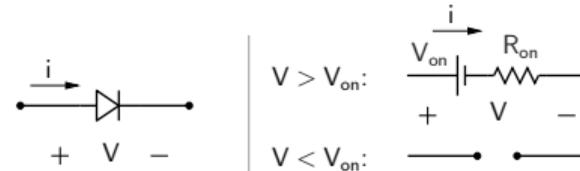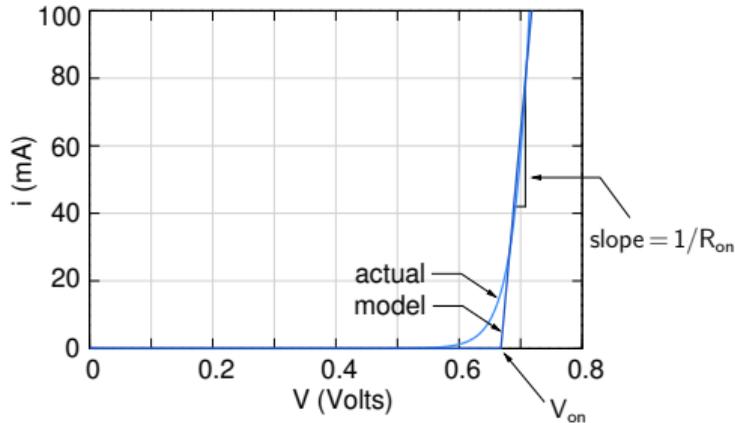

- * In many circuits, R_{on} can be neglected (assumed to be 0Ω) since it is much smaller than the other resistances in the circuit. In that case, the diode in forward conduction can be replaced with simply a battery.

Diode circuit model

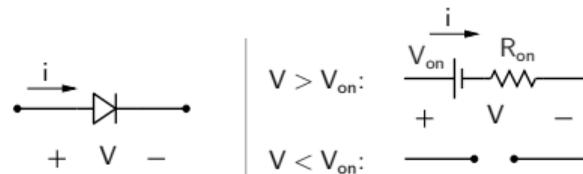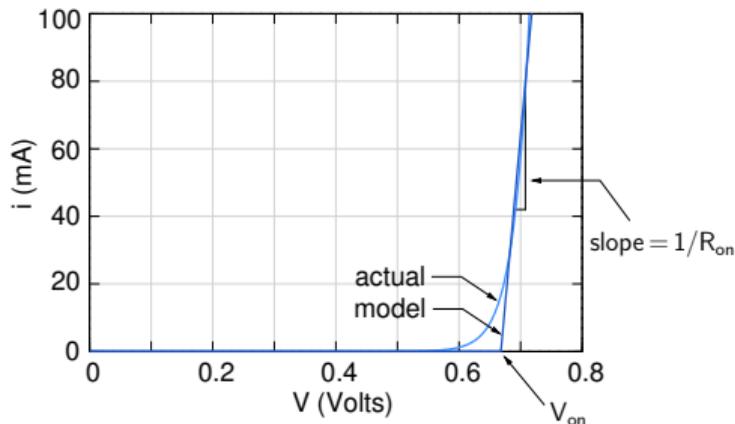



- * In many circuits, R_{on} can be neglected (assumed to be $0\ \Omega$) since it is much smaller than the other resistances in the circuit. In that case, the diode in forward conduction can be replaced with simply a battery.
- * Note that the “battery” shown in the above model is not a “source” of power! It can only absorb power (see the direction of the current), causing heat dissipation.

- * In DC situations, for each diode in the circuit, we need to establish whether it is on or off, replace it with the corresponding equivalent circuit, and then obtain the quantities of interest.



- * In DC situations, for each diode in the circuit, we need to establish whether it is on or off, replace it with the corresponding equivalent circuit, and then obtain the quantities of interest.
- * In transient analysis, we need to find the time points at which a diode turns on or off, and analyse the circuit in intervals between these time points.

- * In DC situations, for each diode in the circuit, we need to establish whether it is on or off, replace it with the corresponding equivalent circuit, and then obtain the quantities of interest.
- * In transient analysis, we need to find the time points at which a diode turns on or off, and analyse the circuit in intervals between these time points.
- * In some diode circuits, the exponential nature of the diode I-V relationship (the Shockley model) is made use of. For these circuits, computation is usually difficult, and computer simulation may be required to solve the resulting non-linear equations.


Diode circuit example

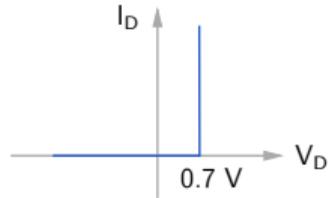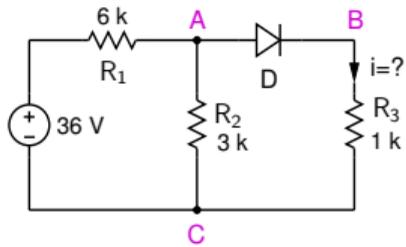


Diode circuit example

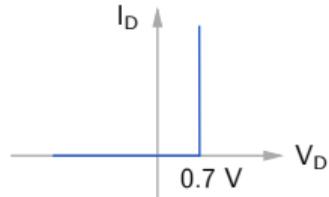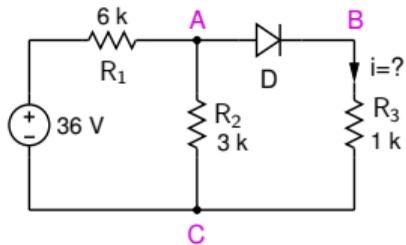


Case 1: D is off.

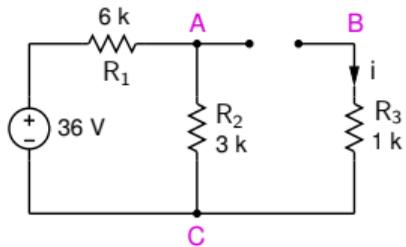

Diode circuit example

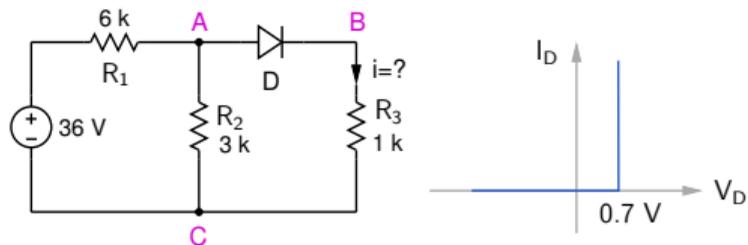


Case 1: D is off.

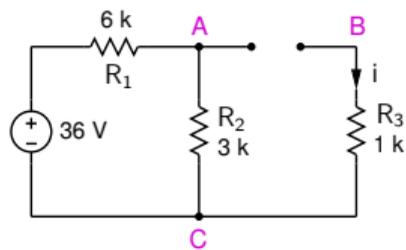


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$

which is not consistent with our assumption of D being off.

Diode circuit example

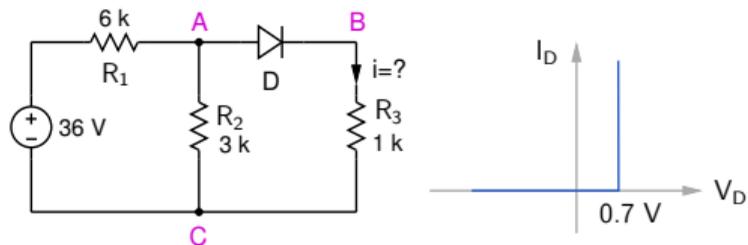

Case 1: D is off.


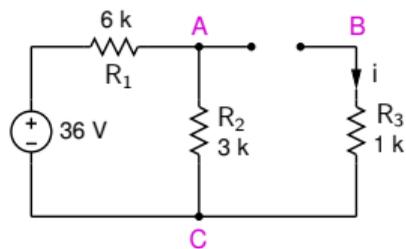


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$


which is not consistent with our assumption of D being off.

→ D must be on.

Diode circuit example

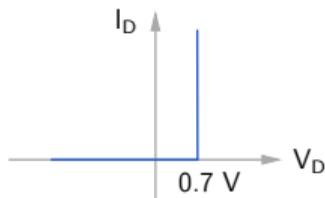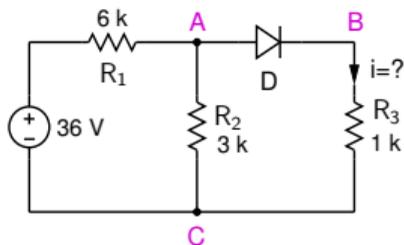

Case 1: D is off.

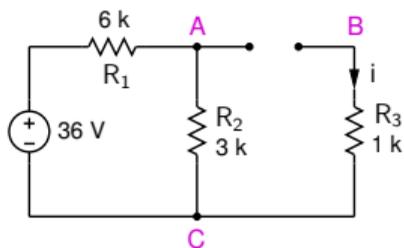


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$



which is not consistent with our assumption of D being off.

→ D must be on.


Case 2: D is on.

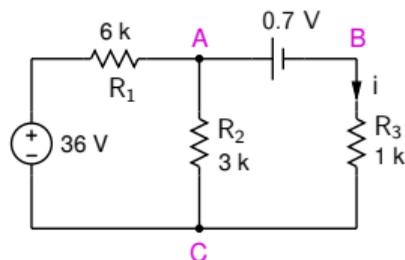

Diode circuit example

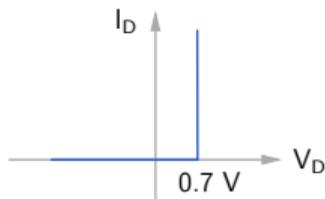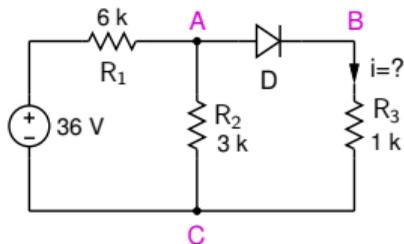

Case 1: D is off.

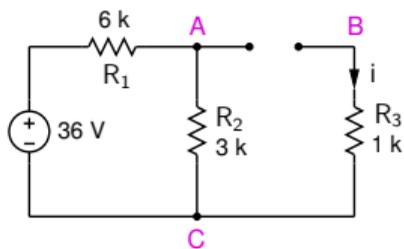


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$

which is not consistent with our assumption of D being off.

→ D must be on.

Case 2: D is on.


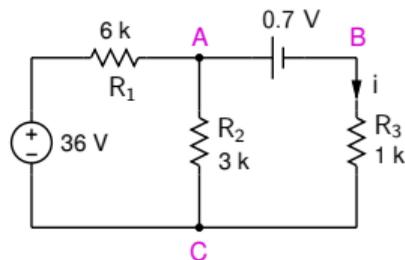


Taking $V_C = 0 \text{ V}$,


$$\frac{V_A - 36}{6 \text{ k}} + \frac{V_A}{3 \text{ k}} + \frac{V_A - 0.7}{1 \text{ k}} = 0,$$

→ $V_A = 4.47 \text{ V}$, $i = 3.77 \text{ mA}$.

Diode circuit example

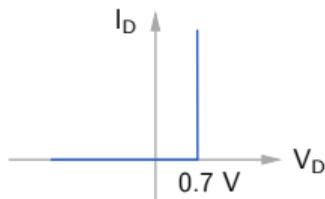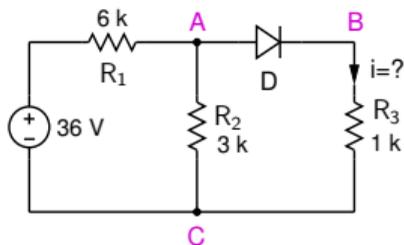

Case 1: D is off.

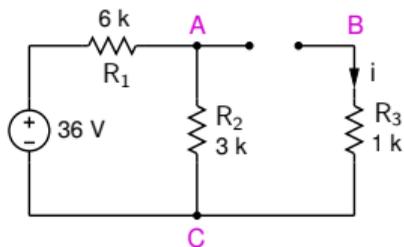


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$

which is not consistent with our assumption of D being off.

→ D must be on.

Case 2: D is on.

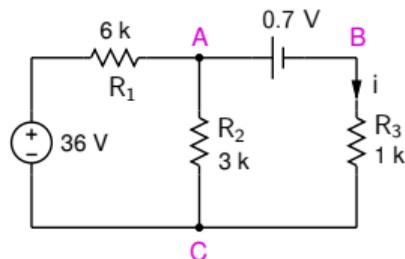



Taking $V_C = 0 \text{ V}$,

$$\frac{V_A - 36}{6 \text{ k}} + \frac{V_A}{3 \text{ k}} + \frac{V_A - 0.7}{1 \text{ k}} = 0,$$

→ $V_A = 4.47 \text{ V}$, $i = 3.77 \text{ mA}$.



Remark: Often, we can figure out by inspection if a diode is on or off.

Diode circuit example

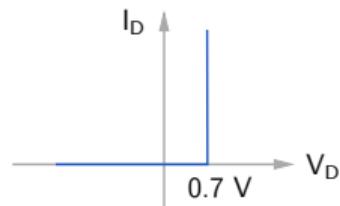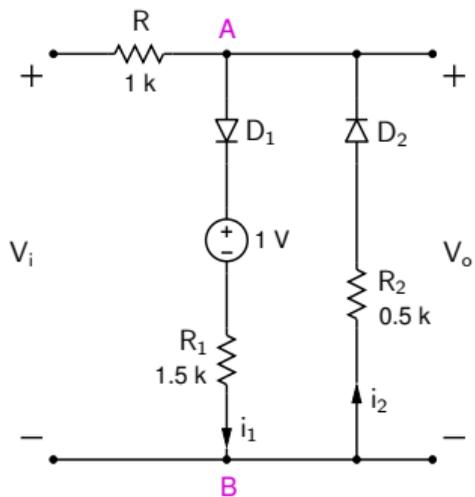

- (a) Plot V_o versus V_i for $-5 \text{ V} < V_i < 5 \text{ V}$.
- (b) Plot $V_o(t)$ for a triangular input:
 -5 V to $+5 \text{ V}$, 500 Hz .



Diode circuit example

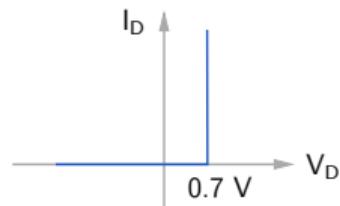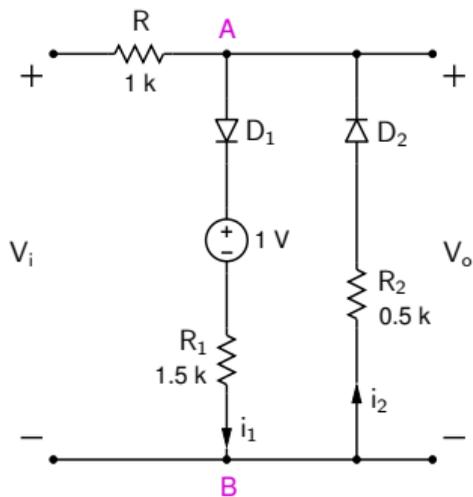

- Plot V_o versus V_i for $-5\text{ V} < V_i < 5\text{ V}$.
- Plot $V_o(t)$ for a triangular input: -5 V to $+5\text{ V}$, 500 Hz .

First, let us show that D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.

Diode circuit example

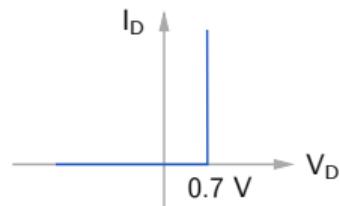
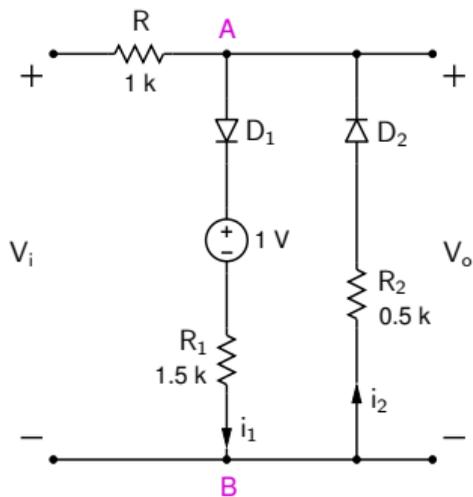


- Plot V_o versus V_i for $-5\text{ V} < V_i < 5\text{ V}$.
- Plot $V_o(t)$ for a triangular input: -5 V to $+5\text{ V}$, 500 Hz .

First, let us show that D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.

Consider D_1 to be on $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$.

Diode circuit example

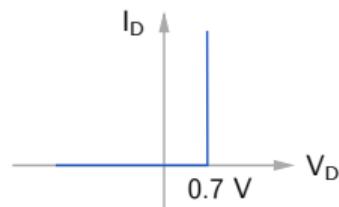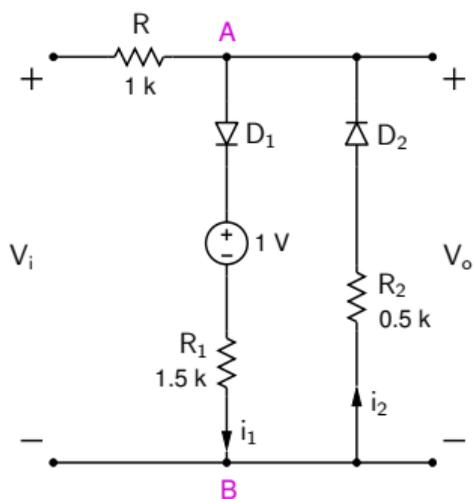

- (a) Plot V_o versus V_i for $-5 \text{ V} < V_i < 5 \text{ V}$.
- (b) Plot $V_o(t)$ for a triangular input:
 -5 V to $+5 \text{ V}$, 500 Hz .



First, let us show that D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.

Consider D_1 to be on $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$.

Note that $i_1 > 0$, since D_1 can only conduct in the forward direction.

$\Rightarrow V_{AB} > 1.7 \text{ V} \Rightarrow D_2$ cannot conduct.

Diode circuit example

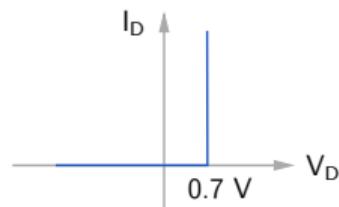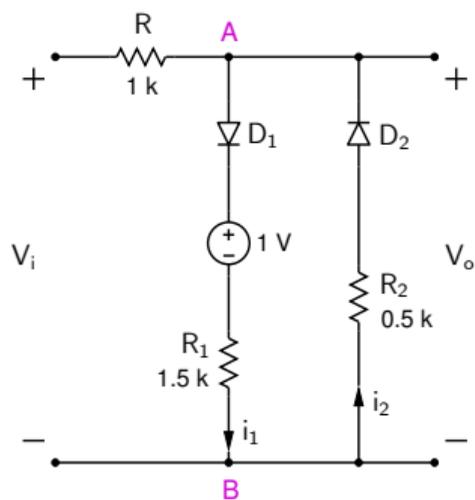

- (a) Plot V_o versus V_i for $-5 \text{ V} < V_i < 5 \text{ V}$.
- (b) Plot $V_o(t)$ for a triangular input:
 -5 V to $+5 \text{ V}$, 500 Hz .

First, let us show that D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.



Consider D_1 to be on $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$.

Note that $i_1 > 0$, since D_1 can only conduct in the forward direction.

$\Rightarrow V_{AB} > 1.7 \text{ V} \Rightarrow D_2$ cannot conduct.

Similarly, if D_2 is on, $V_{BA} > 0.7 \text{ V}$, i.e., $V_{AB} < -0.7 \text{ V} \Rightarrow D_1$ cannot conduct.

Diode circuit example

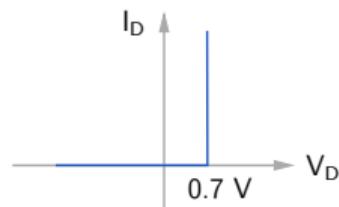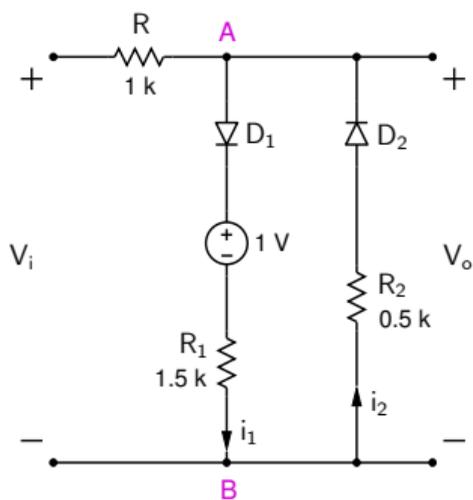

- (a) Plot V_o versus V_i for $-5 \text{ V} < V_i < 5 \text{ V}$.
- (b) Plot $V_o(t)$ for a triangular input:
 -5 V to $+5 \text{ V}$, 500 Hz .

First, let us show that D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.

Consider D_1 to be on $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$.


Note that $i_1 > 0$, since D_1 can only conduct in the forward direction.

$\Rightarrow V_{AB} > 1.7 \text{ V} \Rightarrow D_2$ cannot conduct.


Similarly, if D_2 is on, $V_{BA} > 0.7 \text{ V}$, i.e., $V_{AB} < -0.7 \text{ V} \Rightarrow D_1$ cannot conduct.

Clearly, D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.

Diode circuit example

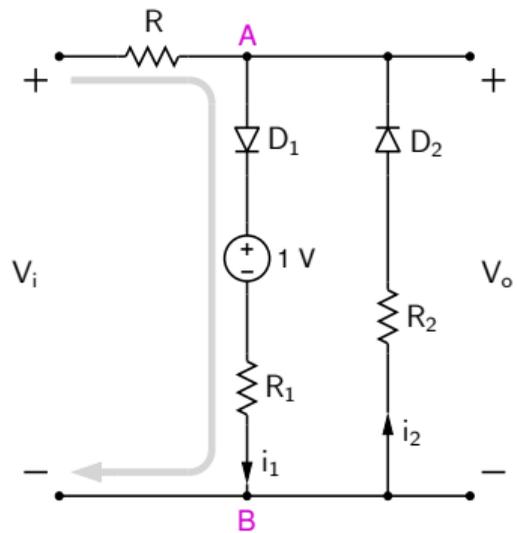


Diode circuit example

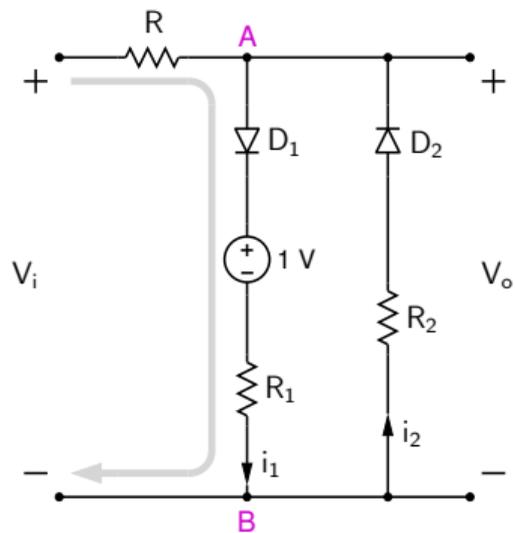

D_1 on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Diode circuit example

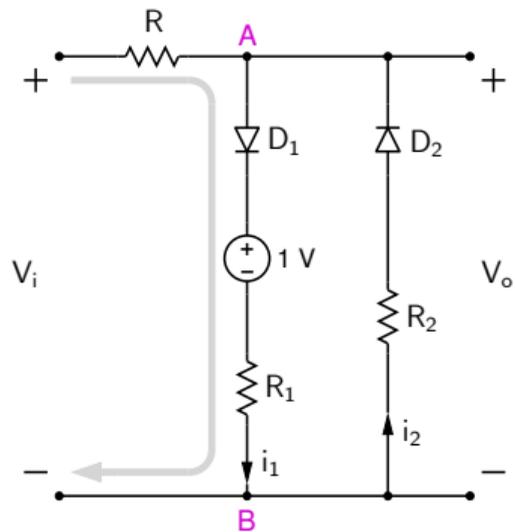


D_1 on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since $i_1 > 0$, $V_i > 1.7\text{V}$


Diode circuit example

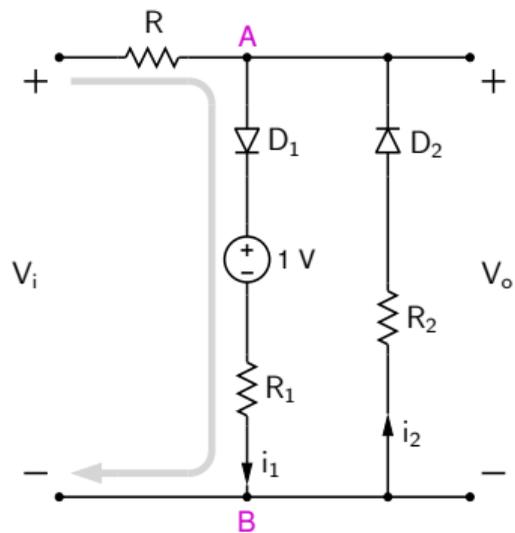


D_1 on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since $i_1 > 0$, $V_i > 1.7V$

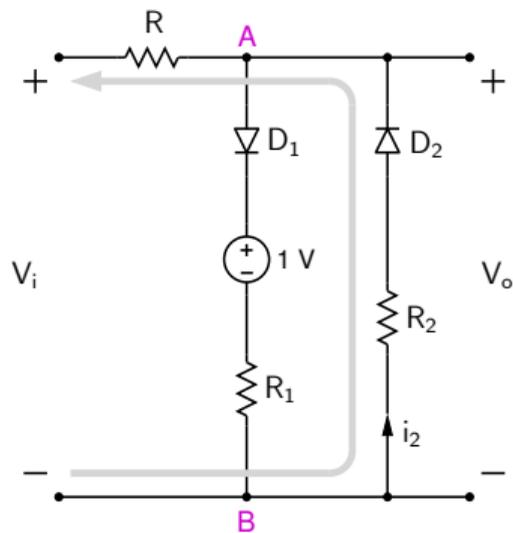


Diode circuit example

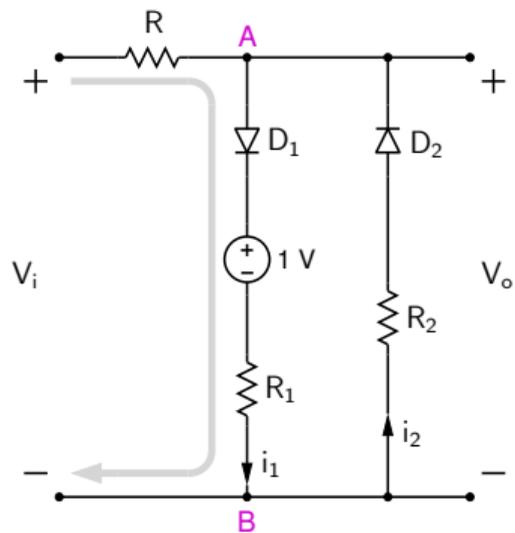

D_1 on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$


Since $i_1 > 0$, $V_i > 1.7V$

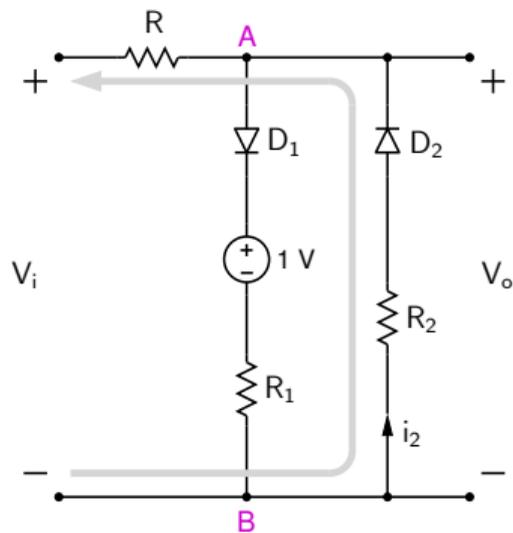

D_2 on:

$$i_2(R + R_2) + 0.7 + V_i = 0$$


Diode circuit example

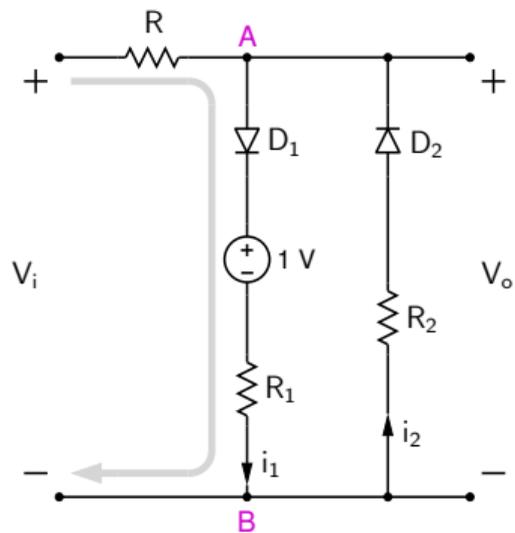

D_1 on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since $i_1 > 0$, $V_i > 1.7V$

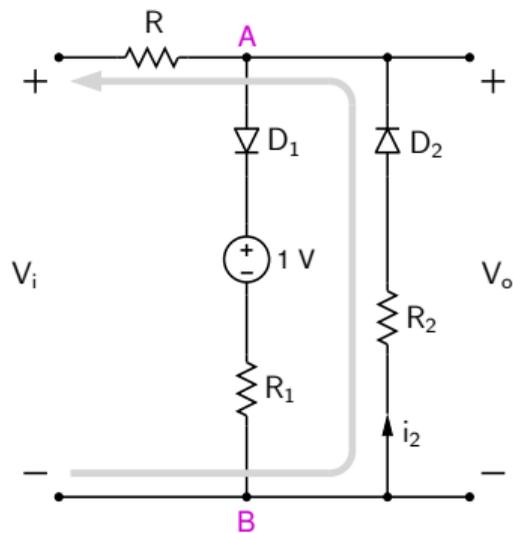


D_2 on:

$$i_2(R + R_2) + 0.7 + V_i = 0$$

$$V_i = -[0.7 + i_2(R + R_2)]$$


Diode circuit example

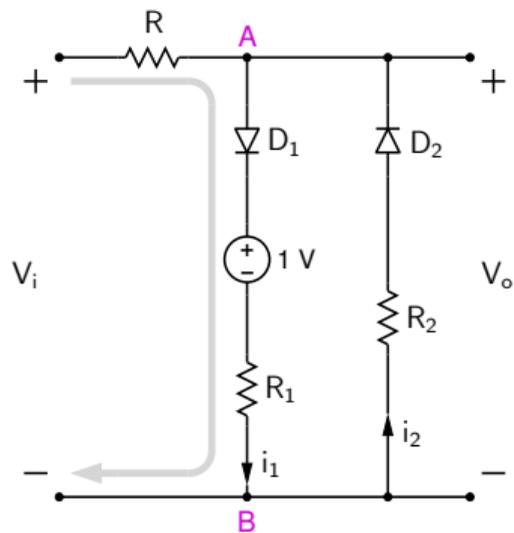

D_1 on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since $i_1 > 0$, $V_i > 1.7V$

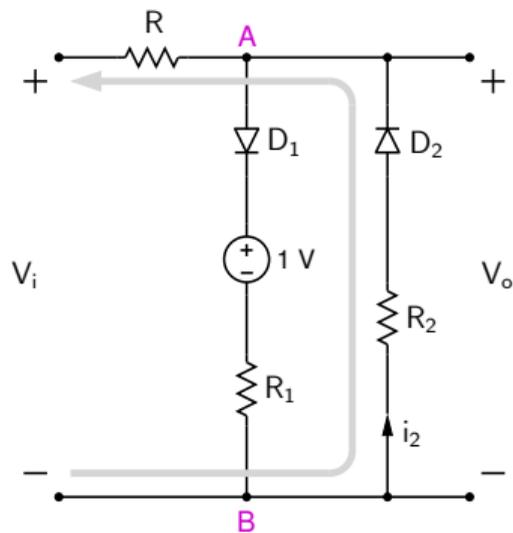


D_2 on:

$$i_2(R + R_2) + 0.7 + V_i = 0$$

$$V_i = -[0.7 + i_2(R + R_2)]$$

Since $i_2 > 0$, $V_i < -0.7V$


Diode circuit example

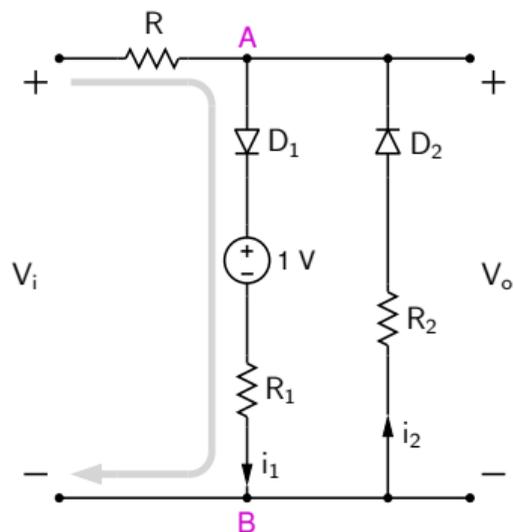

D_1 on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since $i_1 > 0$, $V_i > 1.7V$

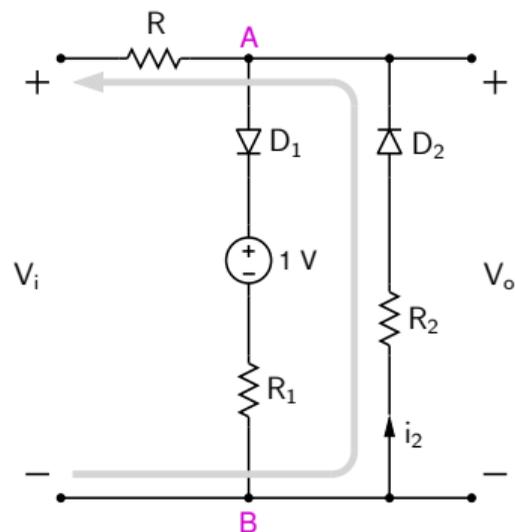

D_2 on:


$$i_2(R + R_2) + 0.7 + V_i = 0$$

$$V_i = -[0.7 + i_2(R + R_2)]$$



Since $i_2 > 0$, $V_i < -0.7V$

For $-0.7V < V_i < 1.7V$, neither D_1 nor D_2 can conduct.

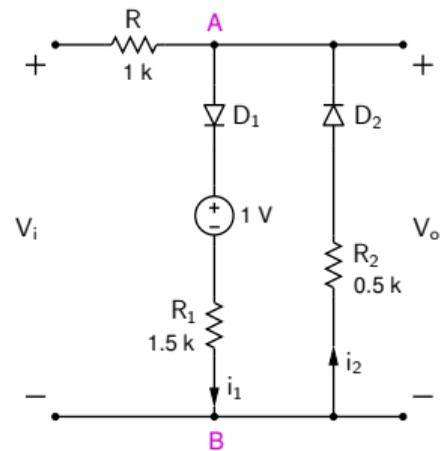- * For $-0.7\text{ V} < V_i < 1.7\text{ V}$, both D_1 and D_2 are off.
→ no drop across R , and $V_o = V_i$. (1)



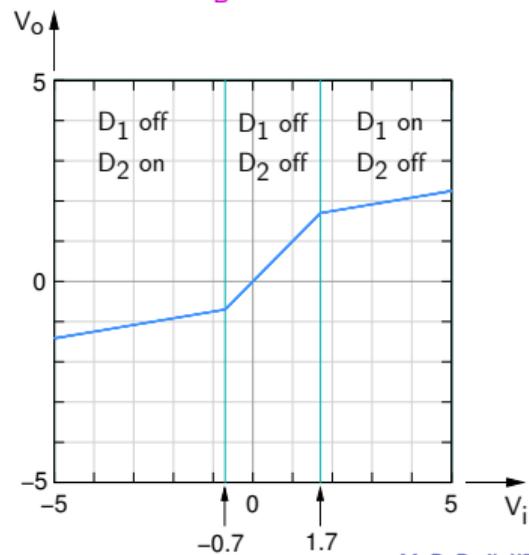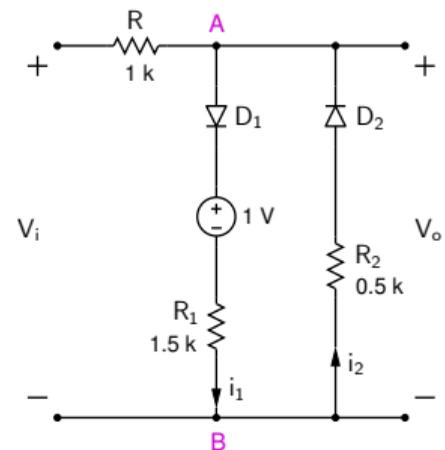- * For $-0.7\text{ V} < V_i < 1.7\text{ V}$, both D_1 and D_2 are off.
 \rightarrow no drop across R , and $V_o = V_i$. (1)





* For $-0.7 \text{ V} < V_i < 1.7 \text{ V}$, both D_1 and D_2 are off.
 \rightarrow no drop across R , and $V_o = V_i$. (1)

* For $V_i < -0.7 \text{ V}$, D_2 conducts. $\rightarrow V_o = -0.7 - i_2 R_2$.
 Use KVL to get i_2 : $V_i + i_2 R_2 + 0.7 + R i_2 = 0$.

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$

$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}. \quad (2)$$
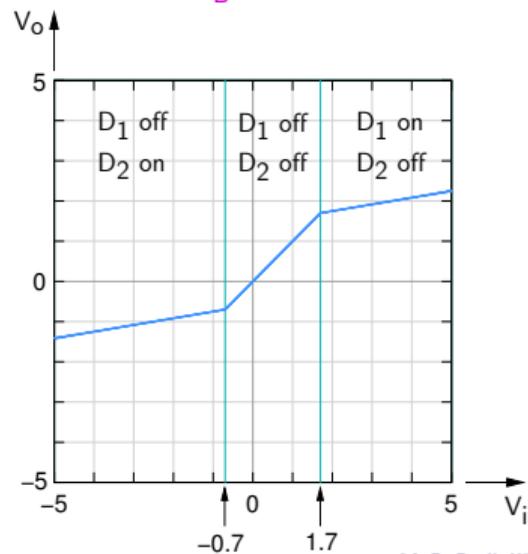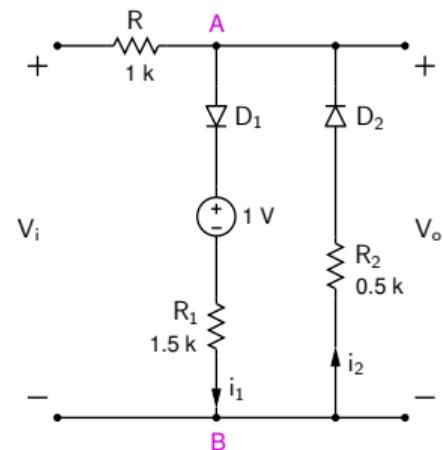
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_2}{R + R_2} = \frac{0.5 \text{ k}}{1 \text{ k} + 0.5 \text{ k}} = \frac{1}{3}.$$



* For $-0.7 \text{ V} < V_i < 1.7 \text{ V}$, both D_1 and D_2 are off.
 \rightarrow no drop across R , and $V_o = V_i$. (1)

* For $V_i < -0.7 \text{ V}$, D_2 conducts. $\rightarrow V_o = -0.7 - i_2 R_2$.
 Use KVL to get i_2 : $V_i + i_2 R_2 + 0.7 + R i_2 = 0$.

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$

$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}. \quad (2)$$



$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_2}{R + R_2} = \frac{0.5 \text{ k}}{1 \text{ k} + 0.5 \text{ k}} = \frac{1}{3}.$$

* For $V_i > 1.7 \text{ V}$, D_1 conducts. $\rightarrow V_o = 0.7 + 1 + i_1 R_1$.
 Use KVL to get i_1 : $-V_i + i_1 R + 0.7 + 1 + i_1 R_1 = 0$.

$$\rightarrow i_1 = \frac{V_i - 1.7}{R + R_1}, \text{ and}$$

$$V_o = 1.7 + R_1 i_1 = \frac{R_1}{R + R_1} V_i + 1.7 \frac{R}{R + R_1}. \quad (3)$$
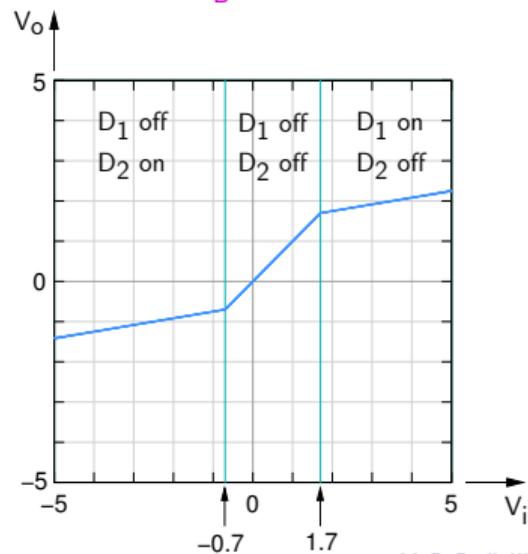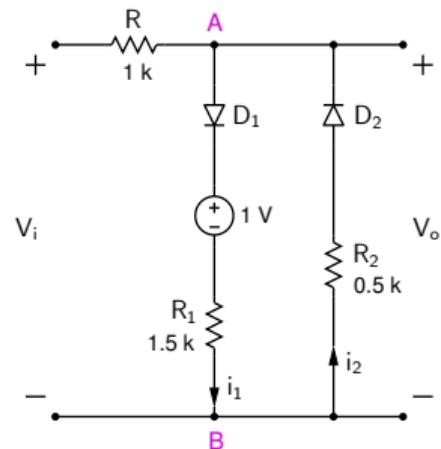
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1.5 \text{ k}}{1 \text{ k} + 1.5 \text{ k}} = \frac{3}{5}.$$



- * For $-0.7 \text{ V} < V_i < 1.7 \text{ V}$, both D_1 and D_2 are off.
 \rightarrow no drop across R , and $V_o = V_i$. (1)

- * For $V_i < -0.7 \text{ V}$, D_2 conducts. $\rightarrow V_o = -0.7 - i_2 R_2$.
 Use KVL to get i_2 : $V_i + i_2 R_2 + 0.7 + R i_2 = 0$.

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$

$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}. \quad (2)$$

$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_2}{R + R_2} = \frac{0.5 \text{ k}}{1 \text{ k} + 0.5 \text{ k}} = \frac{1}{3}.$$



- * For $V_i > 1.7 \text{ V}$, D_1 conducts. $\rightarrow V_o = 0.7 + 1 + i_1 R_1$.
 Use KVL to get i_1 : $-V_i + i_1 R + 0.7 + 1 + i_1 R_1 = 0$.



$$\rightarrow i_1 = \frac{V_i - 1.7}{R + R_1}, \text{ and}$$

$$V_o = 1.7 + R_1 i_1 = \frac{R_1}{R + R_1} V_i + 1.7 \frac{R}{R + R_1}. \quad (3)$$

$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1.5 \text{ k}}{1 \text{ k} + 1.5 \text{ k}} = \frac{3}{5}.$$

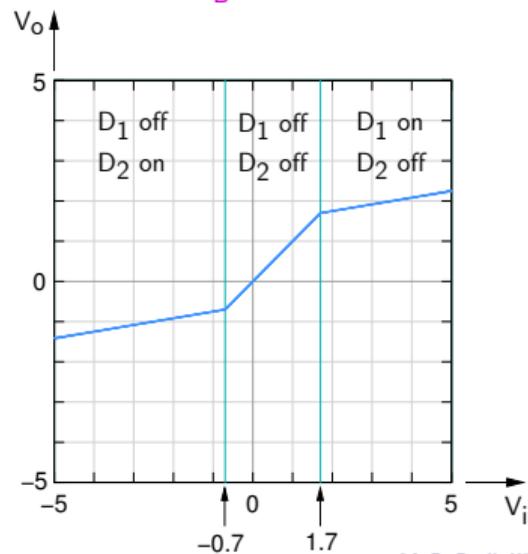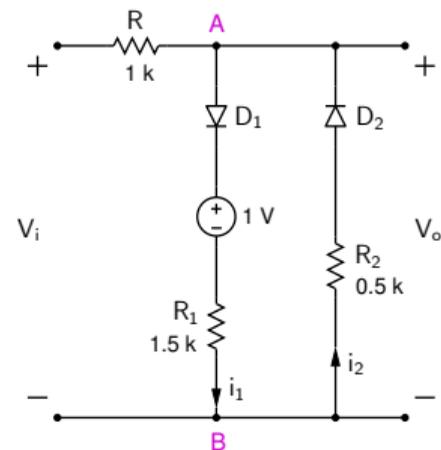- * Using Eqs. (1)-(3), we plot V_o versus V_i .
 (SEQUEL file: ee101_diode_circuit_1.sqproj)




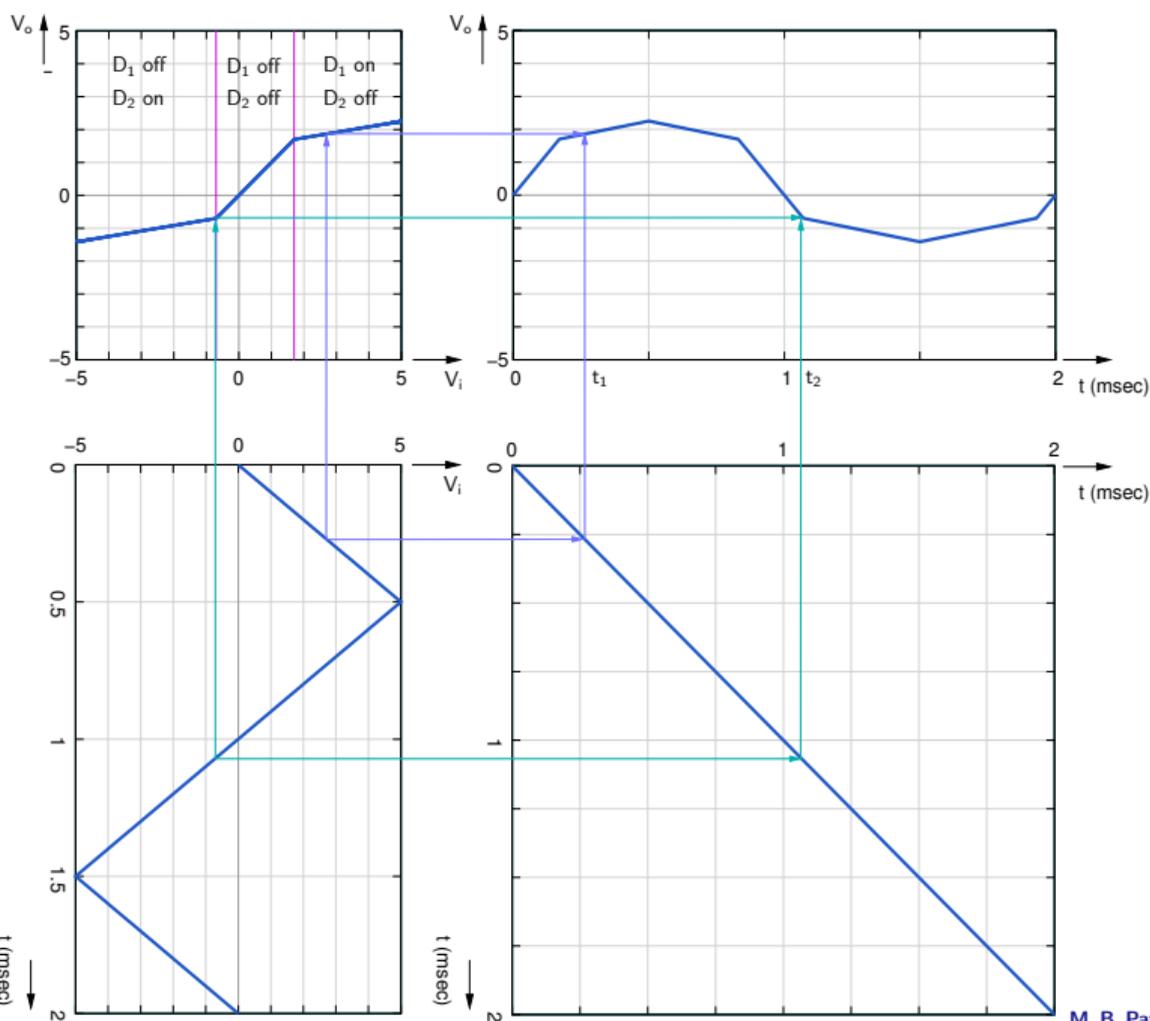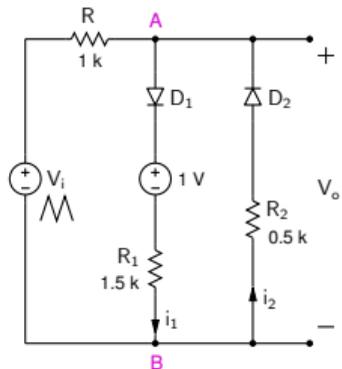

Point-by-point construction of V_o versus t :


Two time points, t_1 and t_2 , are shown as examples.

Diode circuit example

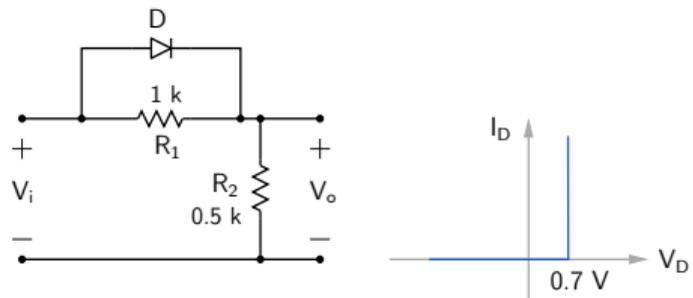


Plot V_o versus V_i for $-5 \text{ V} < V_i < 5 \text{ V}$.

Diode circuit example


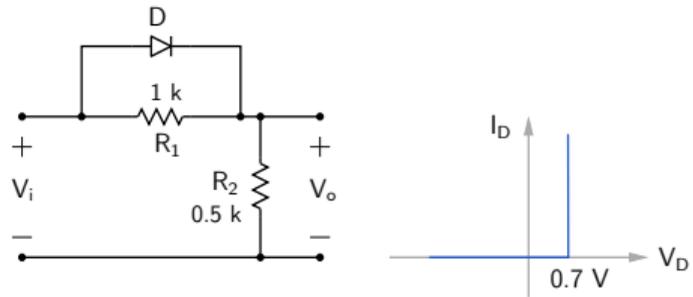


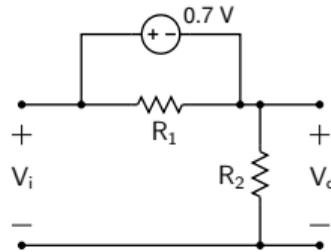Plot V_o versus V_i for $-5 \text{ V} < V_i < 5 \text{ V}$.




D on
 $V_o = V_i - 0.7$


Diode circuit example

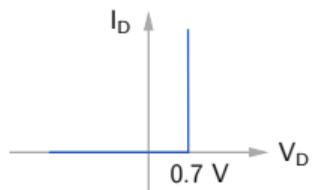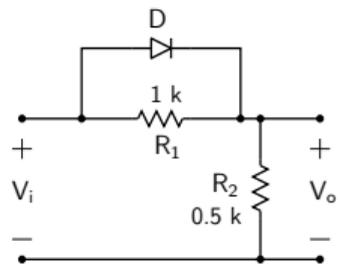

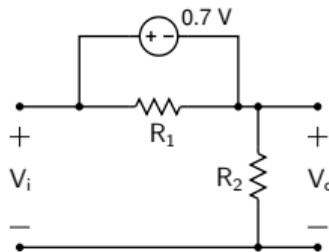Plot V_o versus V_i for $-5\text{ V} < V_i < 5\text{ V}$.





D on
 $V_o = V_i - 0.7$

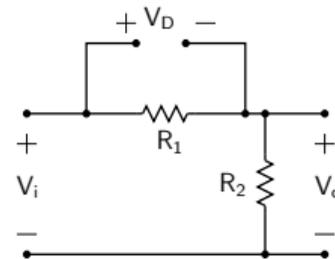


D off
 $V_o = \frac{R_2}{R_1 + R_2} V_i$


Diode circuit example

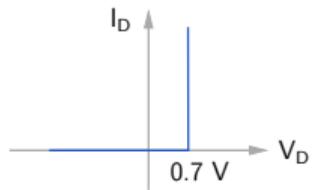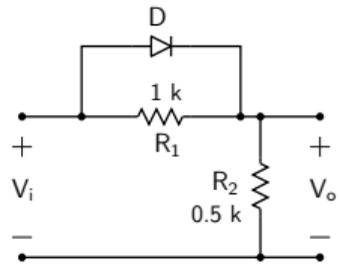

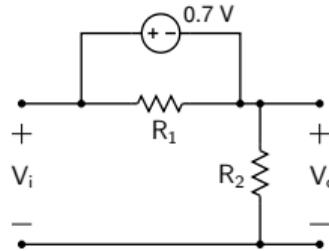Plot V_o versus V_i for $-5\text{ V} < V_i < 5\text{ V}$.




D on
 $V_o = V_i - 0.7$

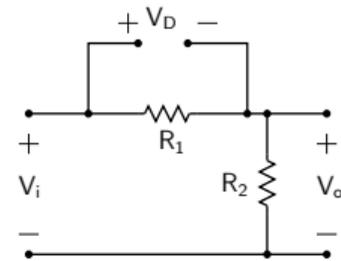


D off
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of V_i will the diode turn on?


Diode circuit example

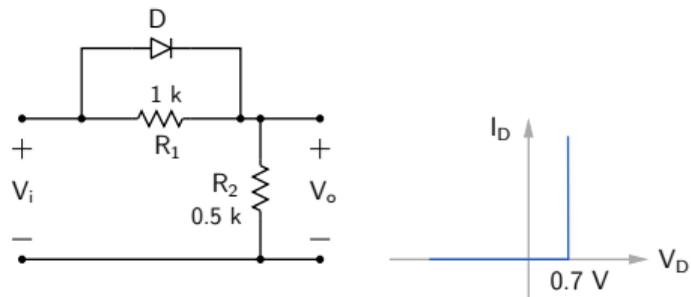

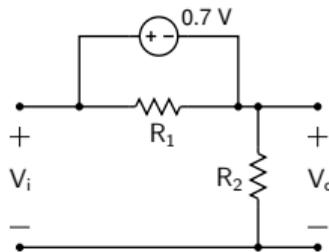Plot V_o versus V_i for $-5\text{ V} < V_i < 5\text{ V}$.



D on
 $V_o = V_i - 0.7$

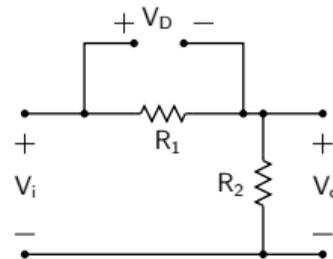


D off
 $V_o = \frac{R_2}{R_1 + R_2} V_i$


At what value of V_i will the diode turn on?

In the off state, $V_D = \frac{R_1}{R_1 + R_2} V_i$.


Diode circuit example

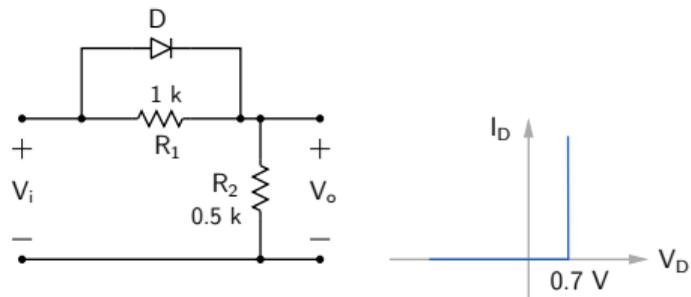

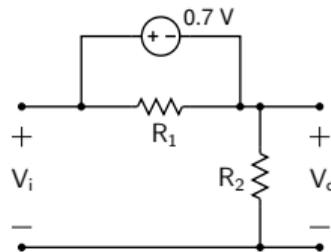Plot V_o versus V_i for $-5\text{ V} < V_i < 5\text{ V}$.



D on
 $V_o = V_i - 0.7$

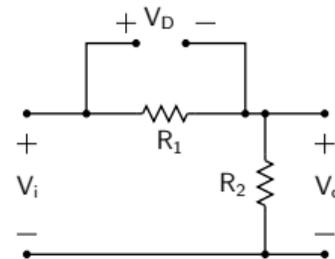

D off
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of V_i will the diode turn on?


In the off state, $V_D = \frac{R_1}{R_1 + R_2} V_i$.

As V_i increases, V_D increases.


For D to turn on, we need $V_D = 0.7\text{ V}$.

i.e., $V_i = \frac{R_1 + R_2}{R_1} \times 0.7 = 1.05\text{ V}$.


Diode circuit example

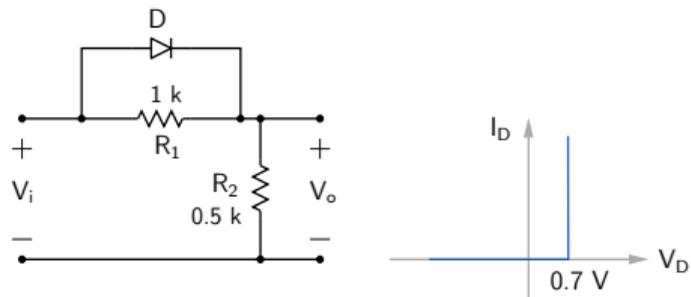

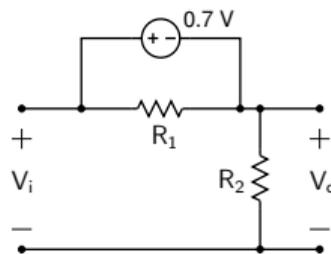Plot V_o versus V_i for $-5\text{ V} < V_i < 5\text{ V}$.



D on
 $V_o = V_i - 0.7$

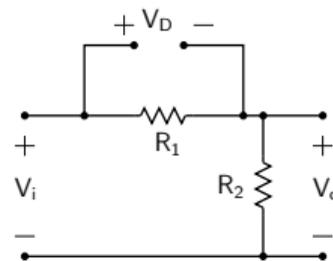

D off
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of V_i will the diode turn on?

In the off state, $V_D = \frac{R_1}{R_1 + R_2} V_i$.


As V_i increases, V_D increases.

For D to turn on, we need $V_D = 0.7\text{ V}$.


i.e., $V_i = \frac{R_1 + R_2}{R_1} \times 0.7 = 1.05\text{ V}$.

(SEQUEL file: ee101_diode_circuit_2.sqproj)


Diode circuit example

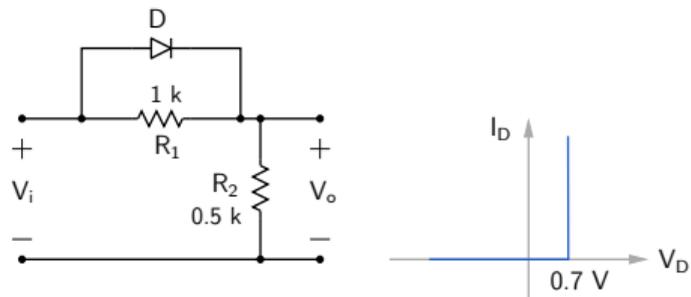

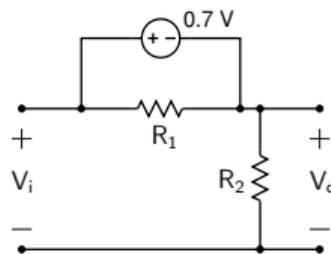Plot V_o versus V_i for $-5 \text{ V} < V_i < 5 \text{ V}$.



D on
 $V_o = V_i - 0.7$

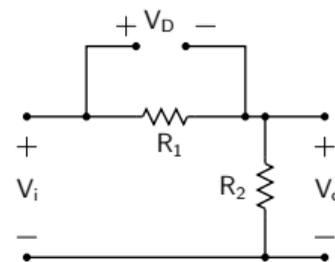

D off
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of V_i will the diode turn on?


In the off state, $V_D = \frac{R_1}{R_1 + R_2} V_i$.

As V_i increases, V_D increases.


For D to turn on, we need $V_D = 0.7 \text{ V}$.

i.e., $V_i = \frac{R_1 + R_2}{R_1} \times 0.7 = 1.05 \text{ V}$.

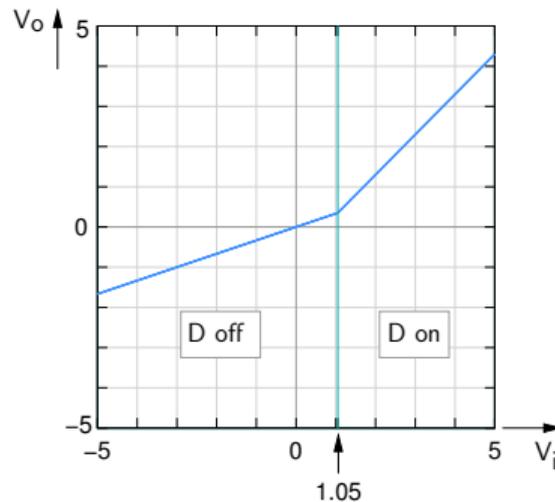
(SEQUEL file: ee101_diode_circuit_2.sqproj)




Diode circuit example

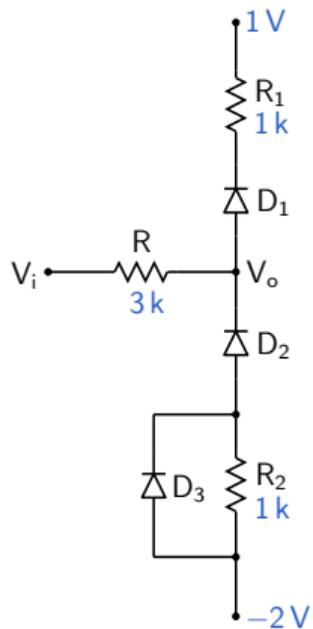


Plot V_o versus V_i (Ref: Sedra/Smith).

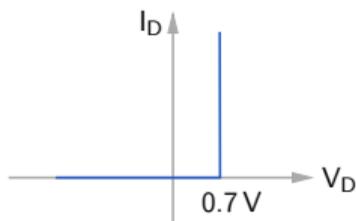

Diode circuit example

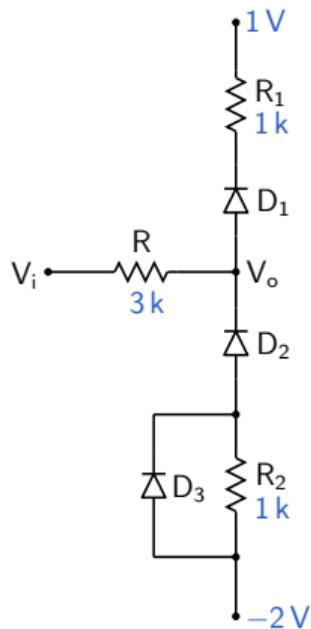


Plot V_o versus V_i (Ref: Sedra/Smith).

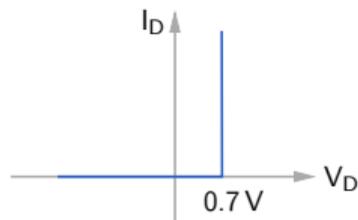


It is easier to find the status (on/off) of each diode w. r. t. V_o .


Diode circuit example

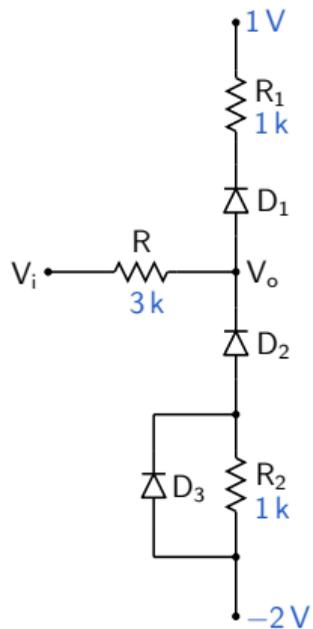


Plot V_o versus V_i (Ref: Sedra/Smith).

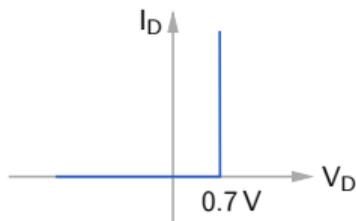

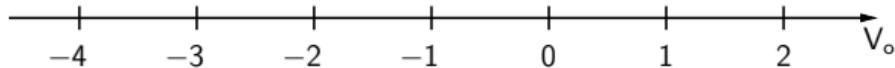
It is easier to find the status (on/off) of each diode w. r. t. V_o .




Diode circuit example

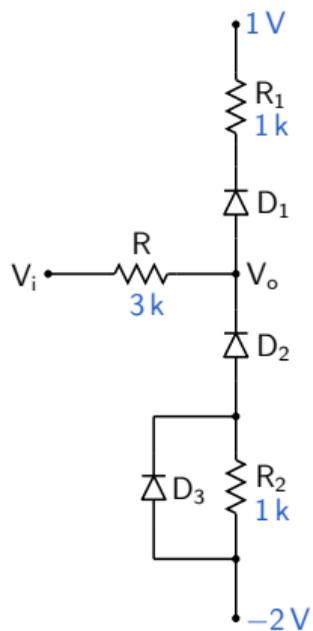


Plot V_o versus V_i (Ref: Sedra/Smith).

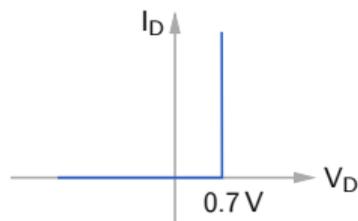

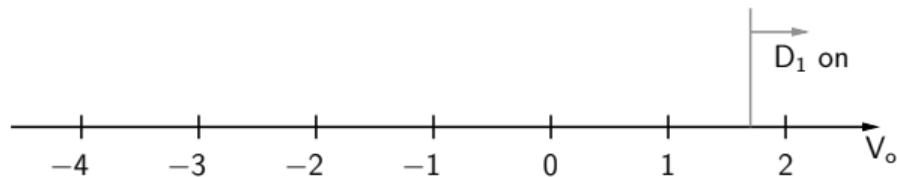
It is easier to find the status (on/off) of each diode w. r. t. V_o .




Diode circuit example

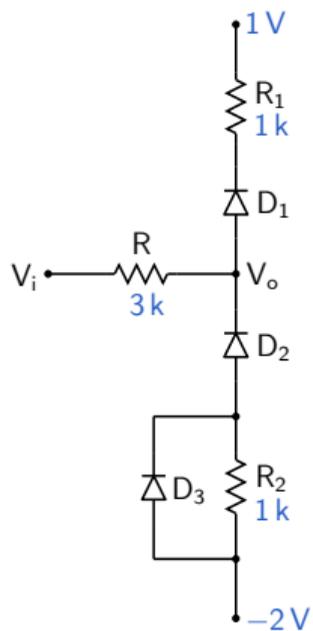


Plot V_o versus V_i (Ref: Sedra/Smith).

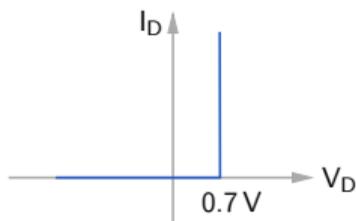

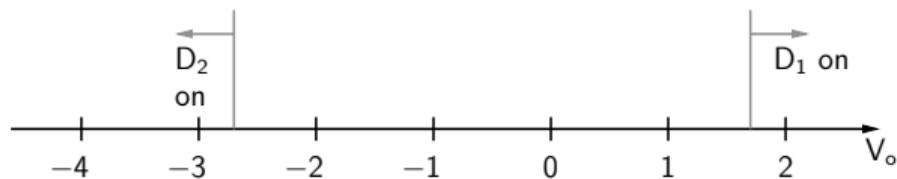
It is easier to find the status (on/off) of each diode w. r. t. V_o .




Diode circuit example


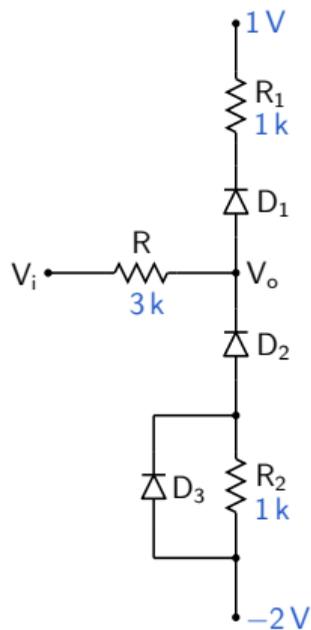




Plot V_o versus V_i (Ref: Sedra/Smith).

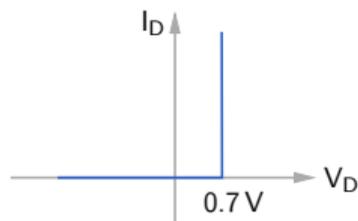

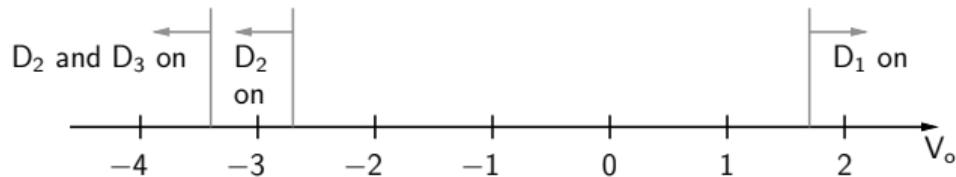It is easier to find the status (on/off) of each diode w. r. t. V_o .





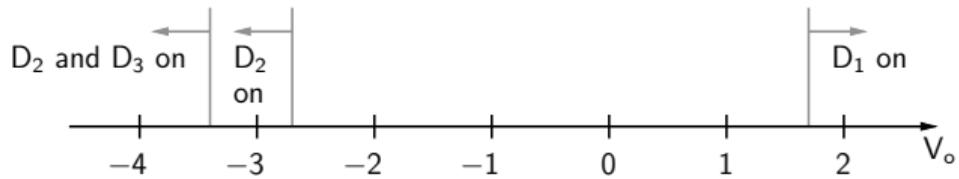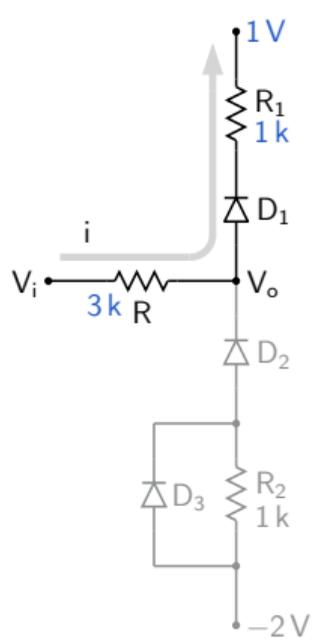

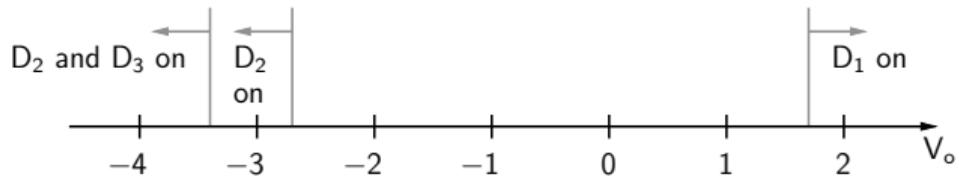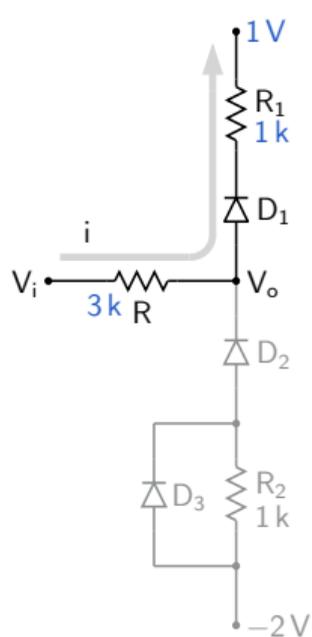

When D_1 just starts conducting,

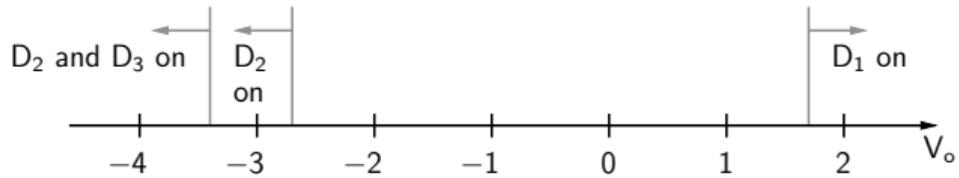
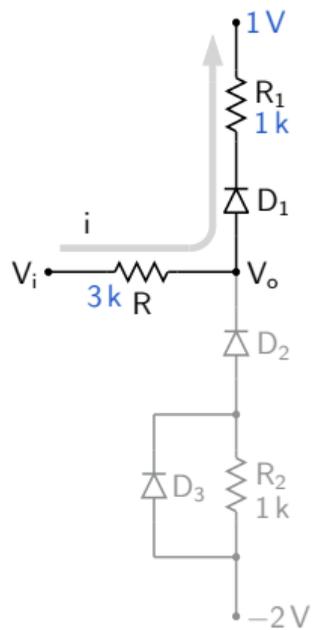
$$V_o = 1.7V, i \approx 0 \rightarrow V_i = 1.7V$$



When D_1 just starts conducting,

$$V_o = 1.7\text{V}, i \approx 0 \rightarrow V_i = 1.7\text{V}$$
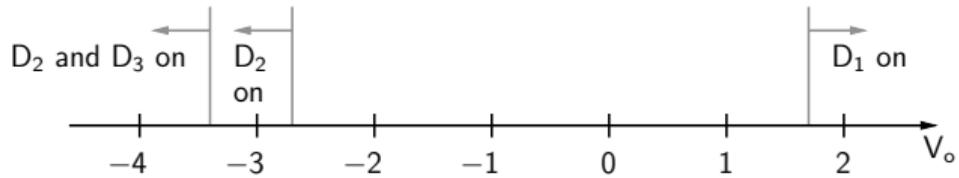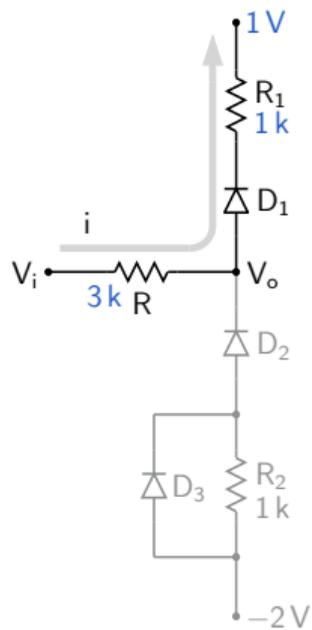
$$\text{For } V_i > 1.7\text{V}, V_o = 1.7 + \left(\frac{V_i - 1.7}{R + R_1} \right) R_1$$





When D_1 just starts conducting,

$$V_o = 1.7\text{V}, i \approx 0 \rightarrow V_i = 1.7\text{V}$$

$$\text{For } V_i > 1.7\text{V}, V_o = 1.7 + \left(\frac{V_i - 1.7}{R + R_1} \right) R_1$$
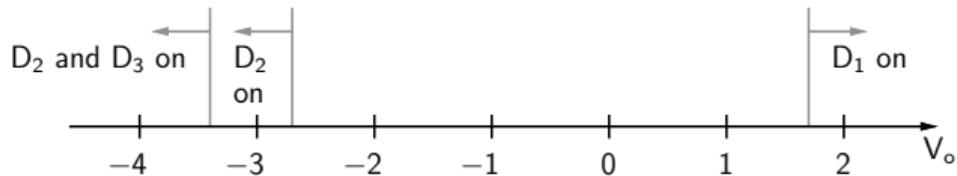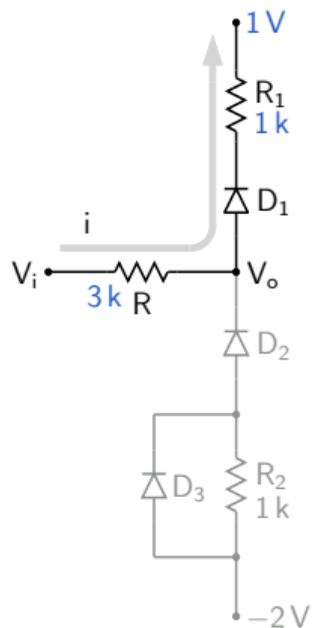
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1}{4}$$





When D_1 just starts conducting,



$$V_o = 1.7\text{V}, i \approx 0 \rightarrow V_i = 1.7\text{V}$$

$$\text{For } V_i > 1.7\text{V}, V_o = 1.7 + \left(\frac{V_i - 1.7}{R + R_1}\right) R_1$$
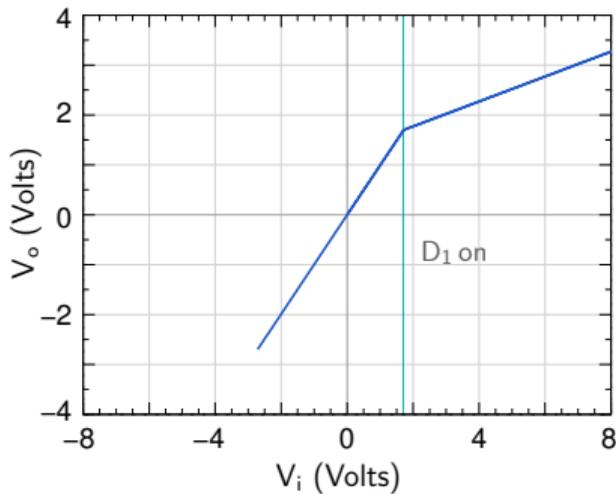
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1}{4}$$





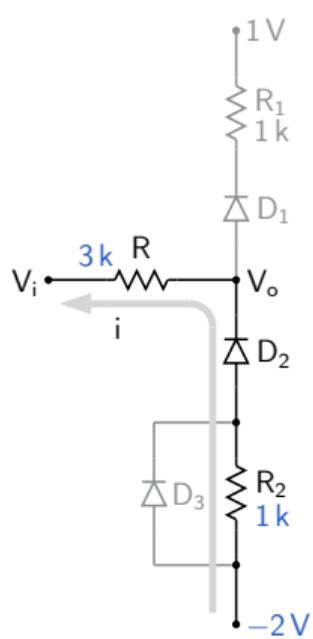

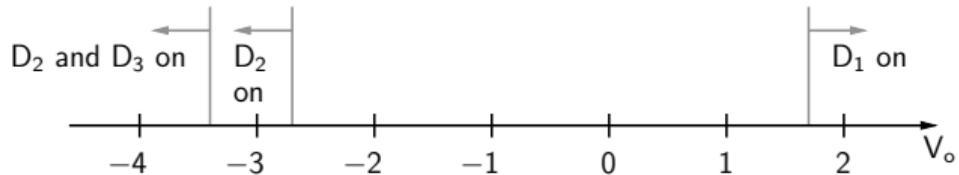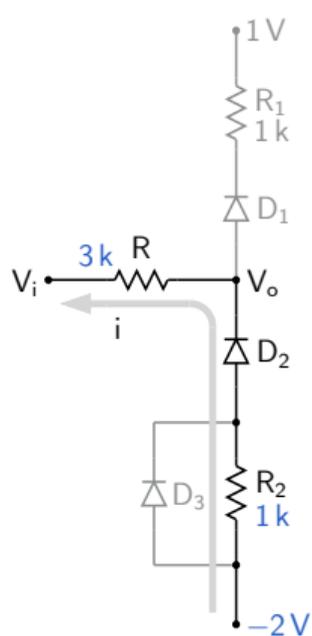

When D_2 just starts conducting,

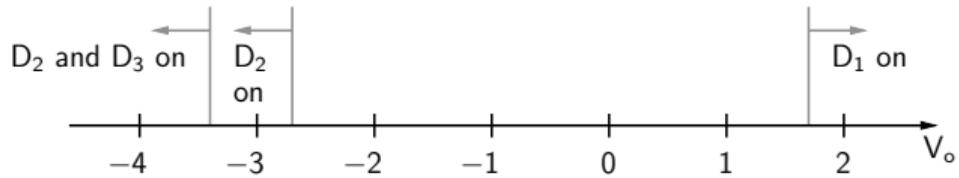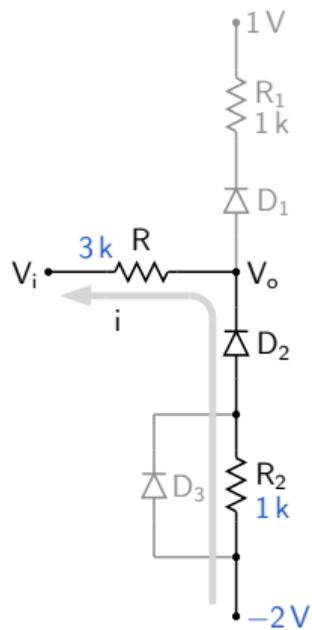
$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$



When D_2 just starts conducting,

$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$
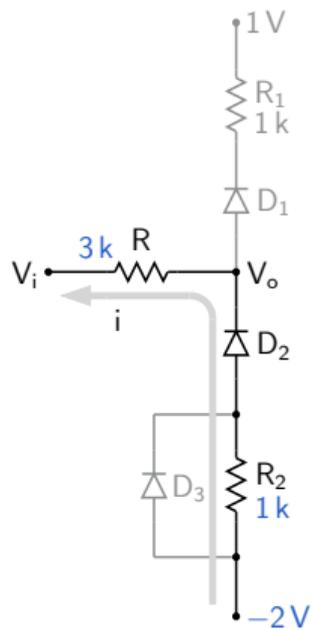
$$\text{For } V_i < -2.7V, V_o = V_i + \left(\frac{-2.7 - V_i}{R + R_2} \right) R$$





When D_2 just starts conducting,

$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$

$$\text{For } V_i < -2.7V, V_o = V_i + \left(\frac{-2.7 - V_i}{R + R_2} \right) R$$
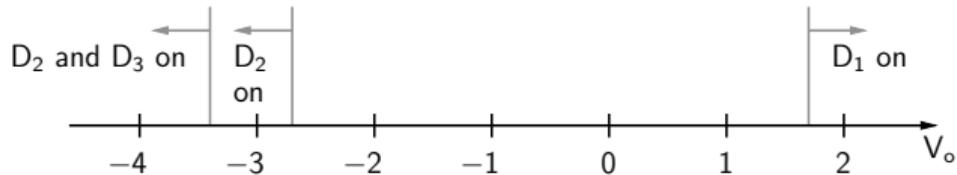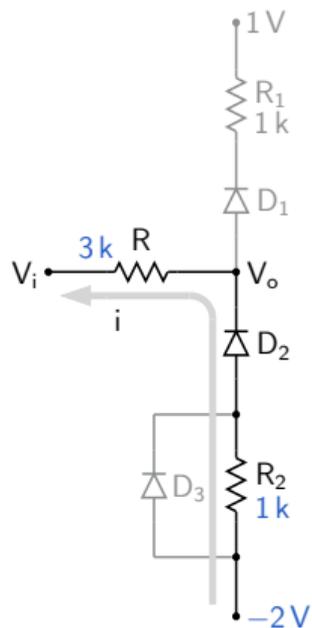
$$\text{Slope } \frac{dV_o}{dV_i} = 1 - \frac{R}{R + R_2} = \frac{R_2}{R + R_2} = \frac{1}{4}$$






When D_2 just starts conducting,


$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$

$$\text{For } V_i < -2.7V, V_o = V_i + \left(\frac{-2.7 - V_i}{R + R_2} \right) R$$
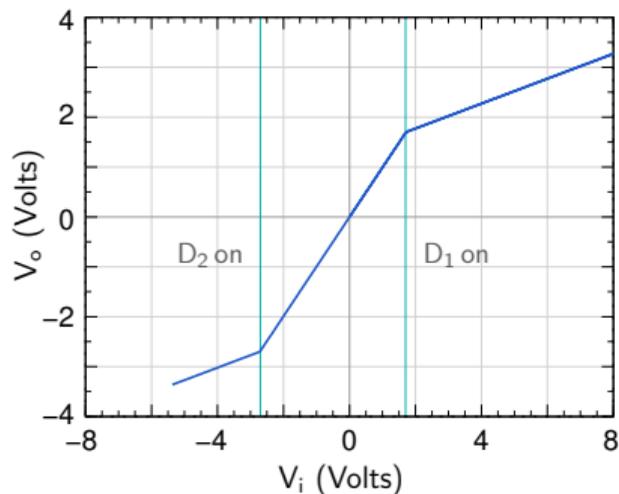
$$\text{Slope } \frac{dV_o}{dV_i} = 1 - \frac{R}{R + R_2} = \frac{R_2}{R + R_2} = \frac{1}{4}$$





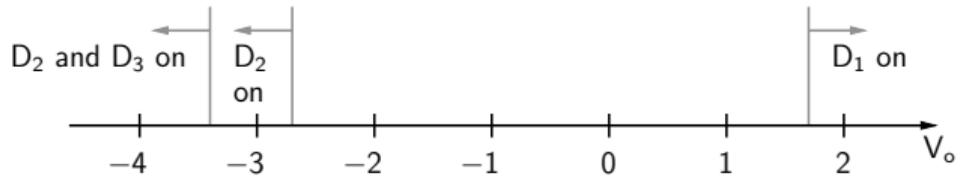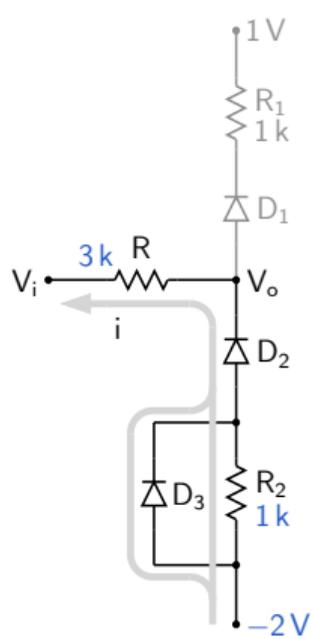

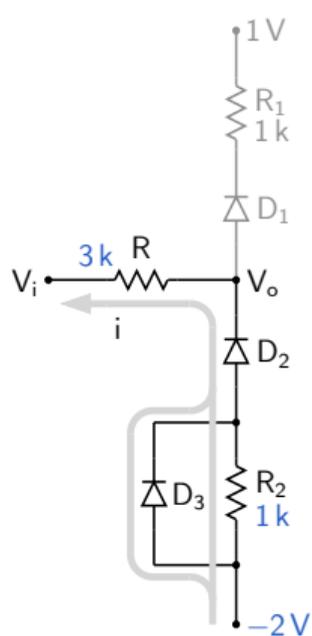

When D_3 just starts conducting,

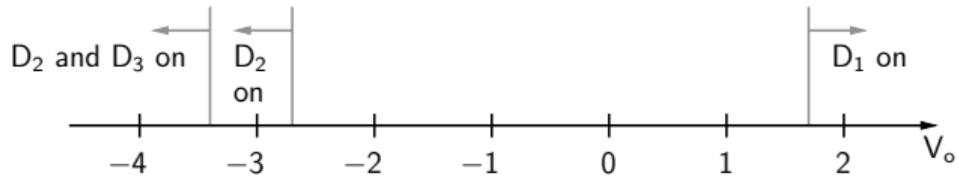
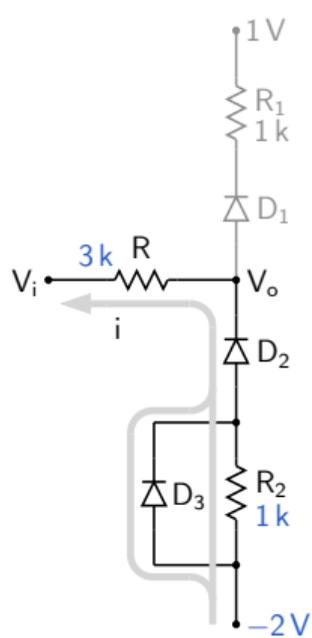
$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7V \rightarrow V_i = -5.5V$$



When D_3 just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7 \text{ V} \rightarrow V_i = -5.5 \text{ V}$$
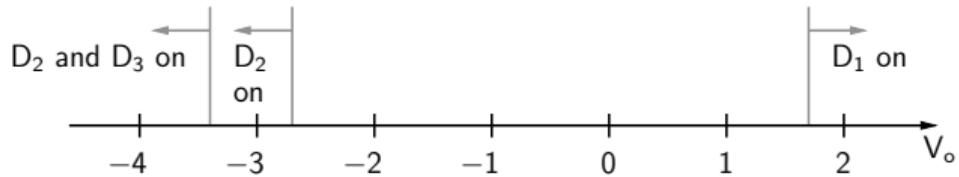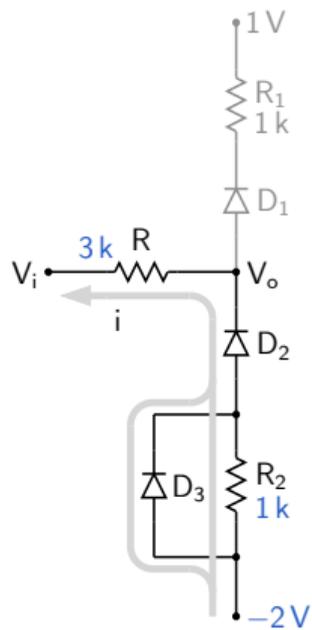
$$V_o = -2 - 0.7 - 0.7 = -3.4 \text{ V}$$




When D_3 just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7V \rightarrow V_i = -5.5V$$

$$V_o = -2 - 0.7 - 0.7 = -3.4V$$

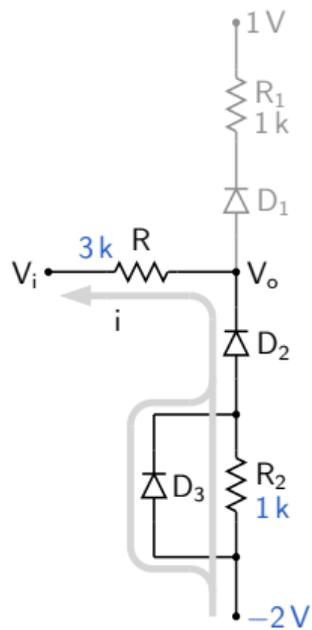For $V_i < -5.5V$, $V_o = -3.4V$ (constant)






When D_3 just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7\text{V} \rightarrow V_i = -5.5\text{V}$$

$$V_o = -2 - 0.7 - 0.7 = -3.4\text{V}$$

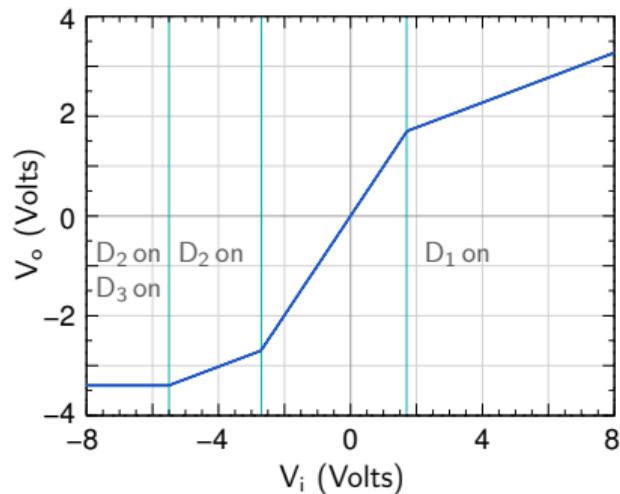For $V_i < -5.5\text{V}$, $V_o = -3.4\text{V}$ (constant)



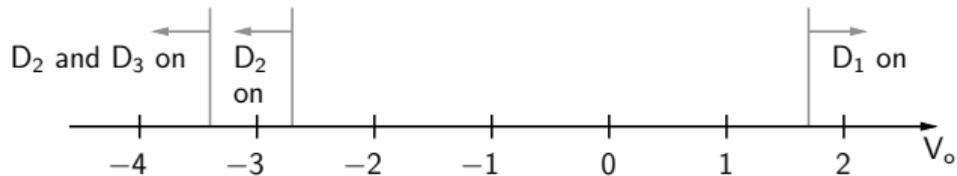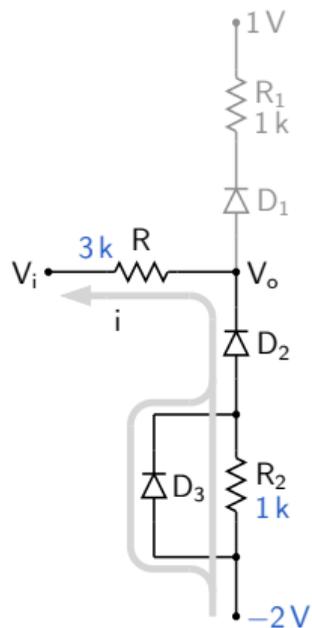


When D_3 just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7 \text{ V} \rightarrow V_i = -5.5 \text{ V}$$

$$V_o = -2 - 0.7 - 0.7 = -3.4 \text{ V}$$

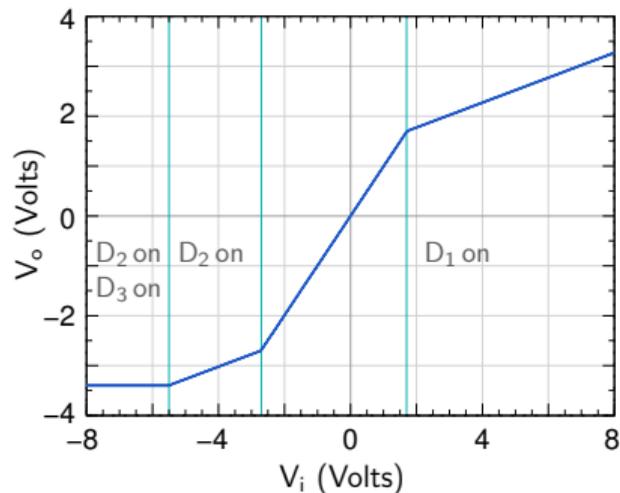
For $V_i < -5.5 \text{ V}$, $V_o = -3.4 \text{ V}$ (constant)




SEQUEL file:


ee101_diode_circuit.12.sqproj

Reverse breakdown

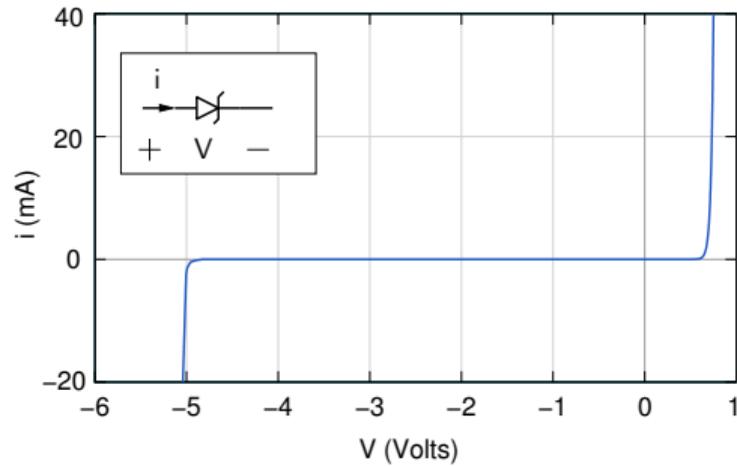


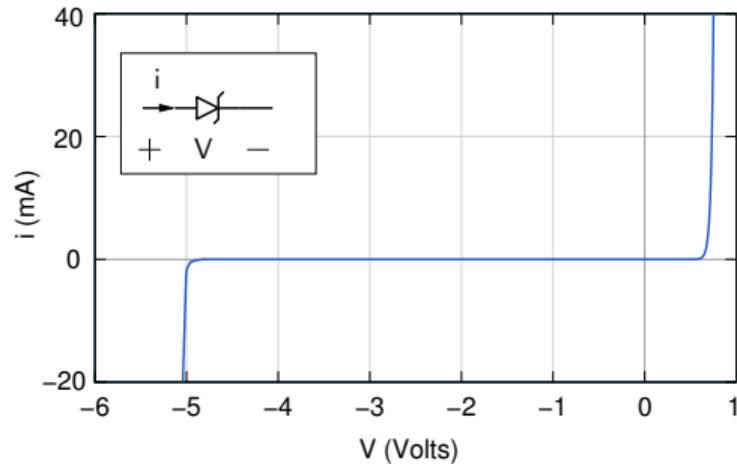

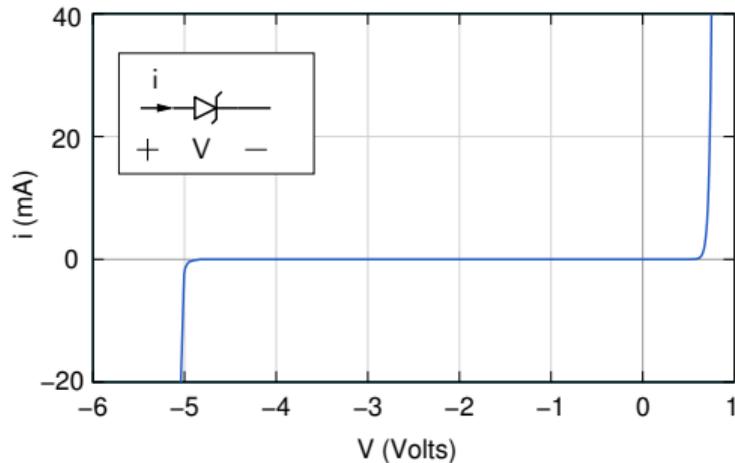* In the reverse direction, an ideal diode presents a large resistance for *any* applied voltage.





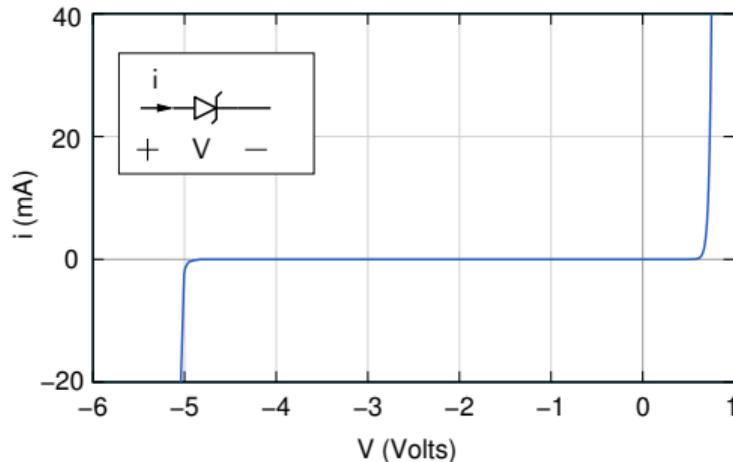- * In the reverse direction, an ideal diode presents a large resistance for *any* applied voltage.
- * A real diode cannot withstand indefinitely large reverse voltages and “breaks down” at a certain voltage called the “breakdown voltage” (V_{BR}).





- * In the reverse direction, an ideal diode presents a large resistance for *any* applied voltage.
- * A real diode cannot withstand indefinitely large reverse voltages and “breaks down” at a certain voltage called the “breakdown voltage” (V_{BR}).
- * When the reverse bias $V_R > V_{BR}$ (i.e., $V < -V_{BR}$), the diode allows a large amount of current. If the current is not constrained by the external circuit, the diode would get damaged.

Reverse breakdown

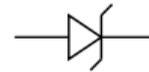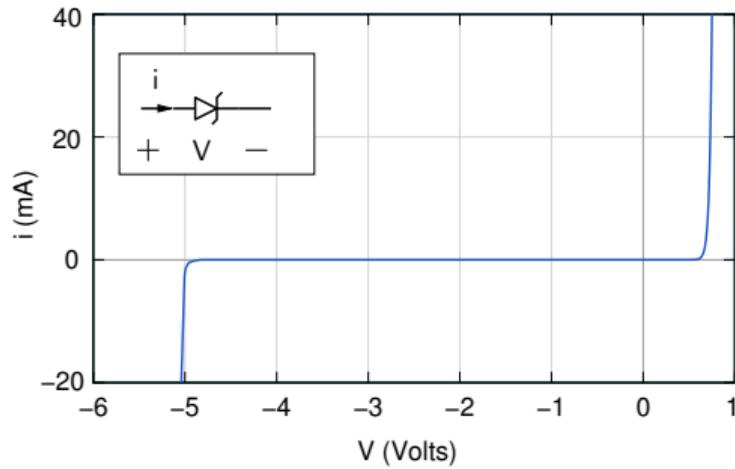



Symbol for a Zener diode

Reverse breakdown

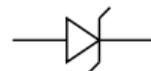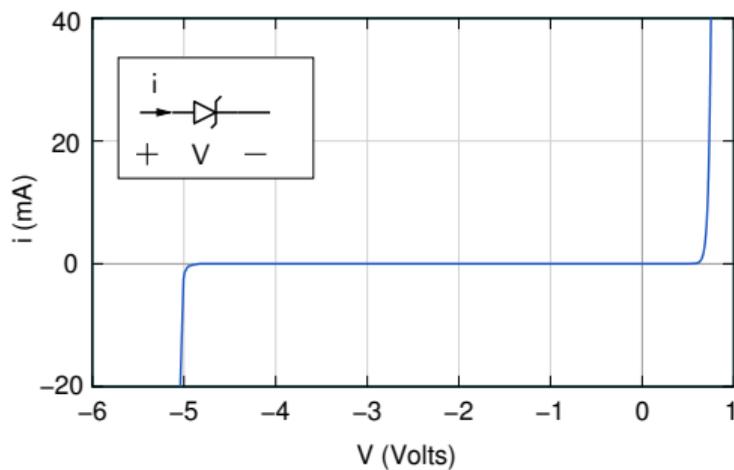



Symbol for a Zener diode

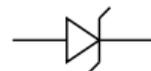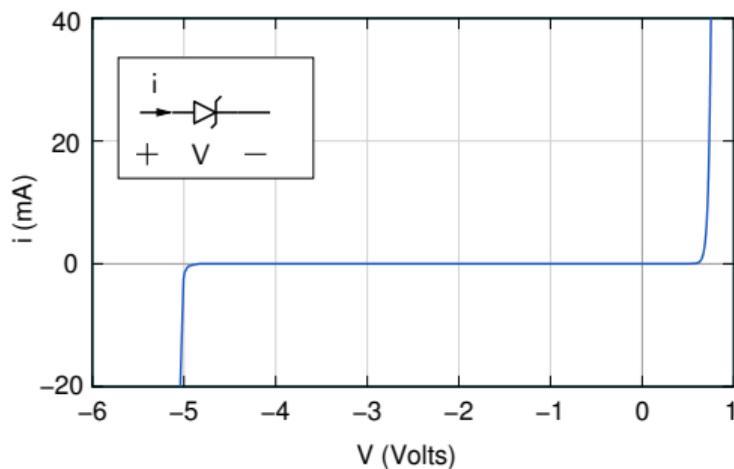- * A wide variety of diodes is available, with V_{BR} ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.





Symbol for a Zener diode

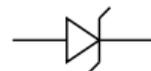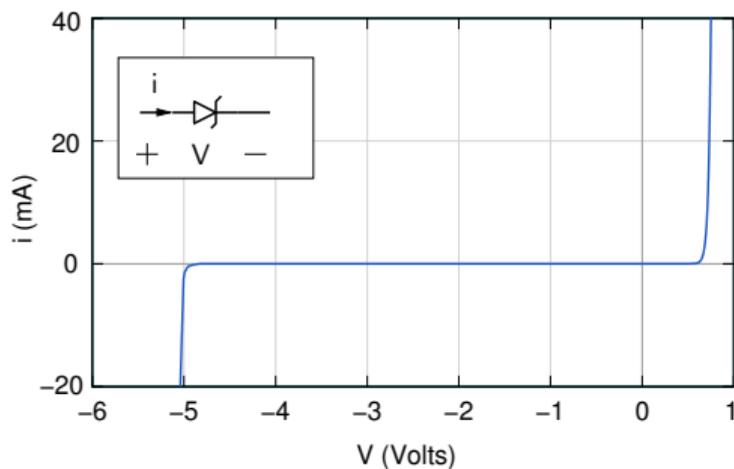- * A wide variety of diodes is available, with V_{BR} ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.
- * Diodes with high V_{BR} are generally used in power electronics applications and are therefore also designed to carry a large forward current (tens or hundreds of Amps).



Symbol for a Zener diode


- * A wide variety of diodes is available, with V_{BR} ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.
- * Diodes with high V_{BR} are generally used in power electronics applications and are therefore also designed to carry a large forward current (tens or hundreds of Amps).
- * Typically, circuits are designed so that the reverse bias across any diode is less than the V_{BR} rating for that diode.

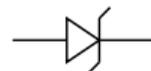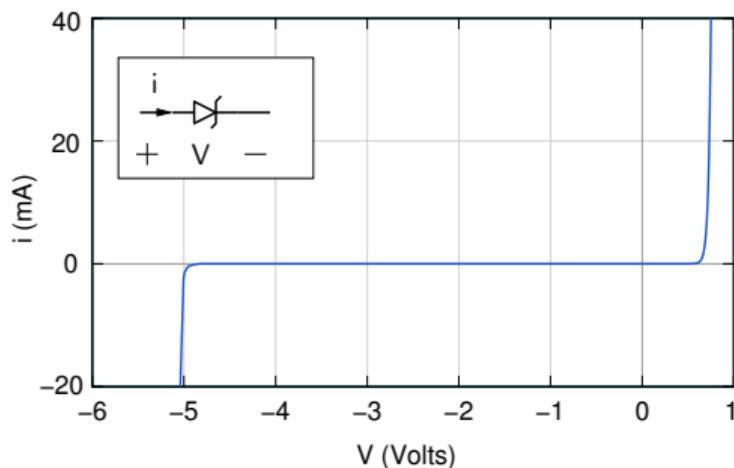


Symbol for a Zener diode

- * A wide variety of diodes is available, with V_{BR} ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.
- * Diodes with high V_{BR} are generally used in power electronics applications and are therefore also designed to carry a large forward current (tens or hundreds of Amps).
- * Typically, circuits are designed so that the reverse bias across any diode is less than the V_{BR} rating for that diode.
- * “Zener” diodes typically have V_{BR} of a few Volts, which is denoted by V_Z . They are often used to limit the voltage swing in electronic circuits.

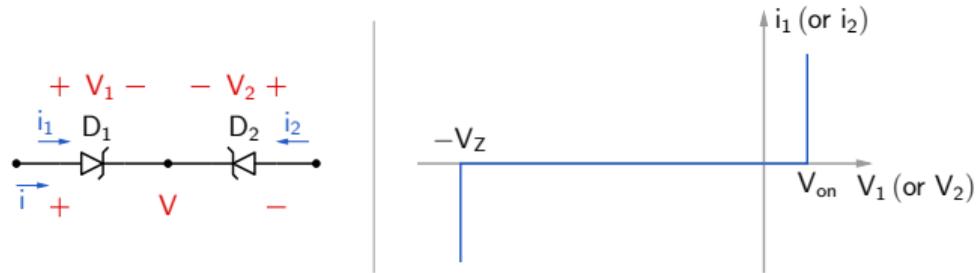Two Zener diodes connected "back-to-back"




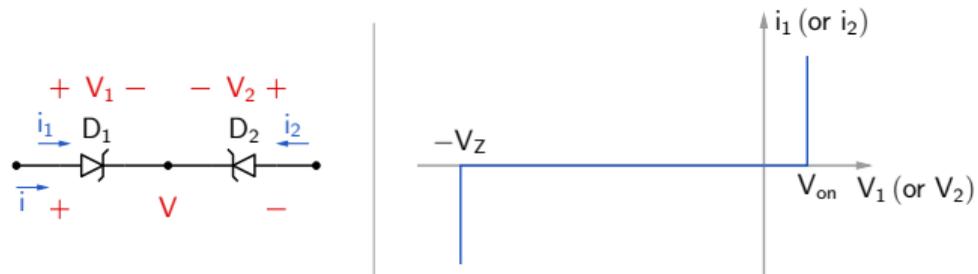Two Zener diodes connected "back-to-back"




* $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction

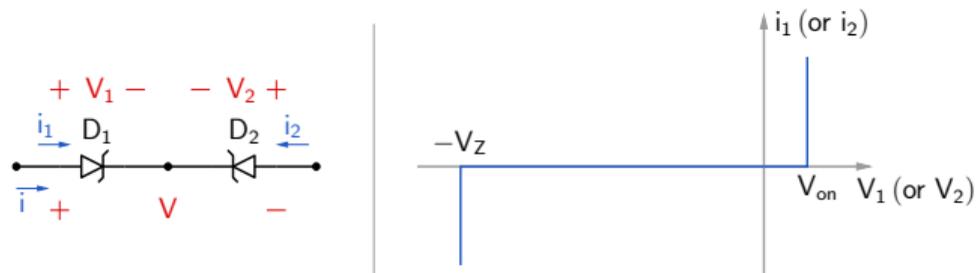Two Zener diodes connected "back-to-back"




- * $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$.

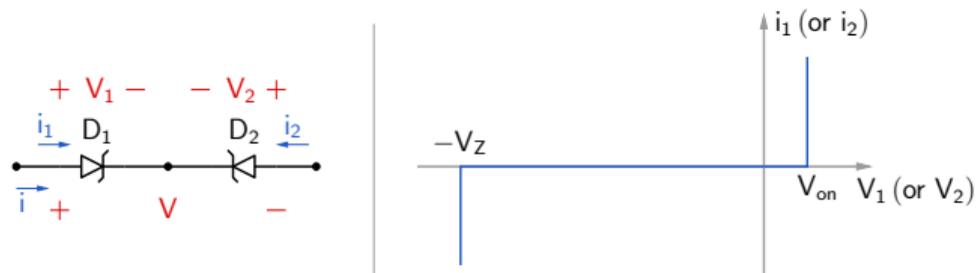Two Zener diodes connected "back-to-back"



- * $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$.
Total voltage drop $V = V_1 - V_2 = V_{on} + V_Z$.

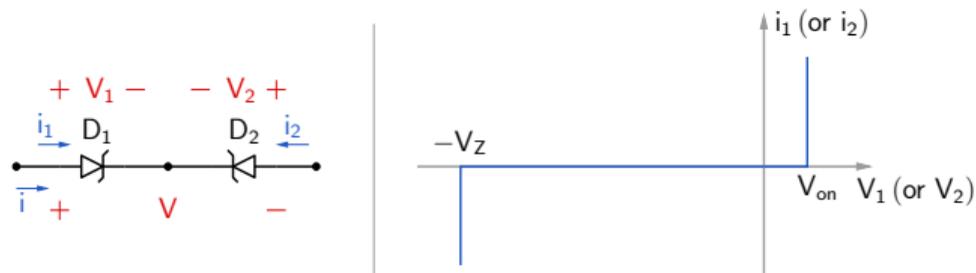Two Zener diodes connected "back-to-back"




* $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction

$\rightarrow V_1 = V_{on}, V_2 = -V_Z.$

Total voltage drop $V = V_1 - V_2 = V_{on} + V_Z.$

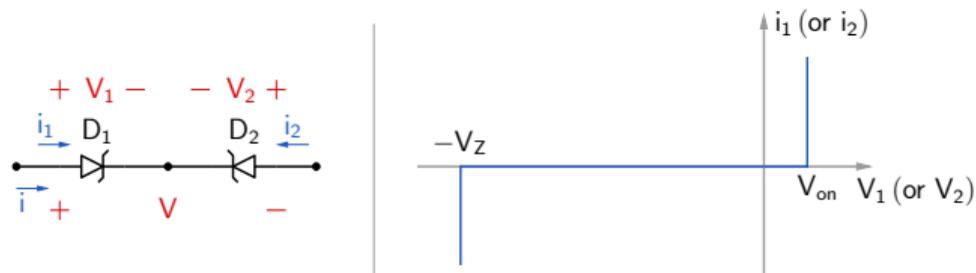
Example: $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}.$

Two Zener diodes connected “back-to-back”




- * $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$.
Total voltage drop $V = V_1 - V_2 = V_{on} + V_Z$.
Example: $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$.
- * $i < 0 \rightarrow D_1$ in reverse conduction, D_2 in forward conduction

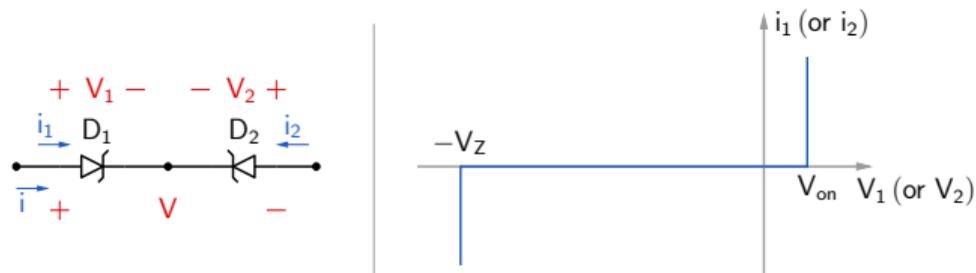Two Zener diodes connected “back-to-back”




- * $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$.
Total voltage drop $V = V_1 - V_2 = V_{on} + V_Z$.
Example: $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$.
- * $i < 0 \rightarrow D_1$ in reverse conduction, D_2 in forward conduction
 $\rightarrow V_1 = -V_Z, V_2 = V_{on}$.

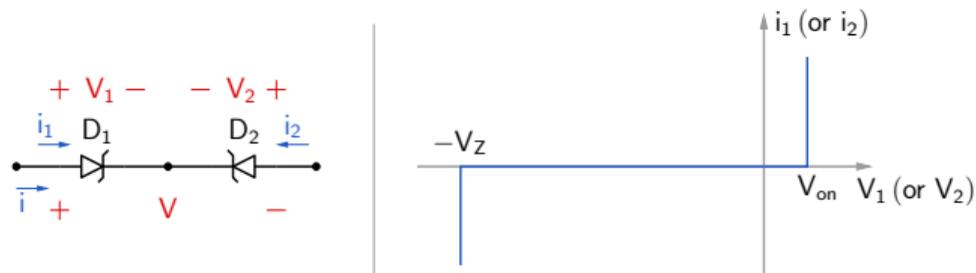Two Zener diodes connected "back-to-back"




- * $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$.
Total voltage drop $V = V_1 - V_2 = V_{on} + V_Z$.
Example: $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$.
- * $i < 0 \rightarrow D_1$ in reverse conduction, D_2 in forward conduction
 $\rightarrow V_1 = -V_Z, V_2 = V_{on}$.
Total voltage drop $V = V_1 - V_2 = -V_Z - V_{on} = -(V_Z + V_{on}) = -5.7\text{ V}$.

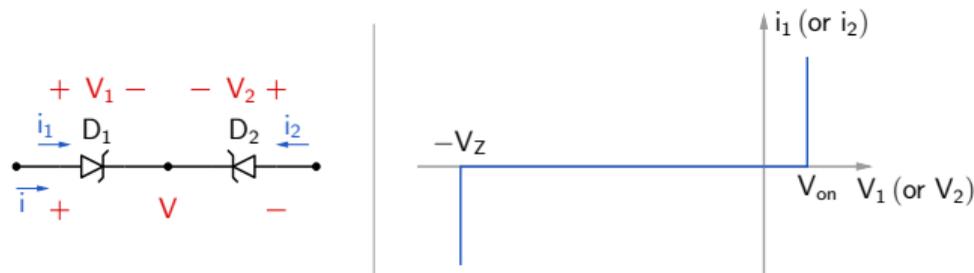Two Zener diodes connected "back-to-back"




- * $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$.
Total voltage drop $V = V_1 - V_2 = V_{on} + V_Z$.
Example: $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$.
- * $i < 0 \rightarrow D_1$ in reverse conduction, D_2 in forward conduction
 $\rightarrow V_1 = -V_Z, V_2 = V_{on}$.
Total voltage drop $V = V_1 - V_2 = -V_Z - V_{on} = -(V_Z + V_{on}) = -5.7\text{ V}$.
- * For $-(V_Z + V_{on}) < V < (V_Z + V_{on})$, conduction is not possible $\rightarrow i = 0$.

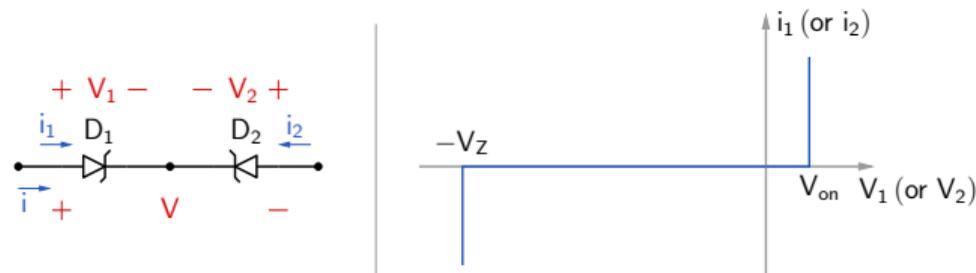
Two Zener diodes connected "back-to-back"



- * $i > 0 \rightarrow D_1$ in forward conduction, D_2 in reverse conduction
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$.
 Total voltage drop $V = V_1 - V_2 = V_{on} + V_Z$.
 Example: $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$.
- * $i < 0 \rightarrow D_1$ in reverse conduction, D_2 in forward conduction
 $\rightarrow V_1 = -V_Z, V_2 = V_{on}$.
 Total voltage drop $V = V_1 - V_2 = -V_Z - V_{on} = -(V_Z + V_{on}) = -5.7\text{ V}$.
- * For $-(V_Z + V_{on}) < V < (V_Z + V_{on})$, conduction is not possible $\rightarrow i = 0$.

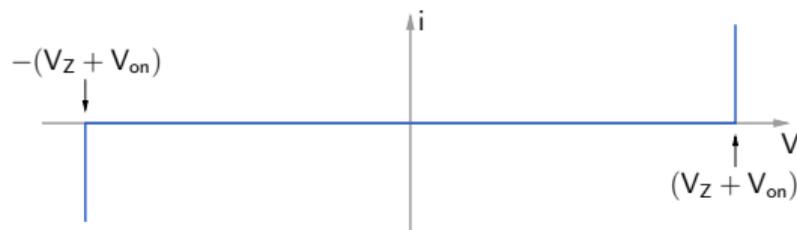



Diode circuit example (voltage limiter)

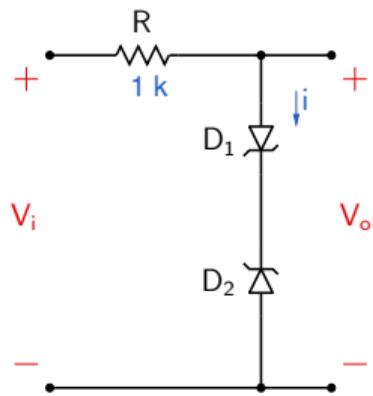

$$V_{\text{on}} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot V_o versus V_i .


Diode circuit example (voltage limiter)

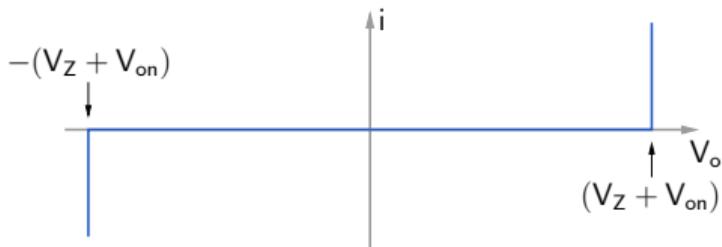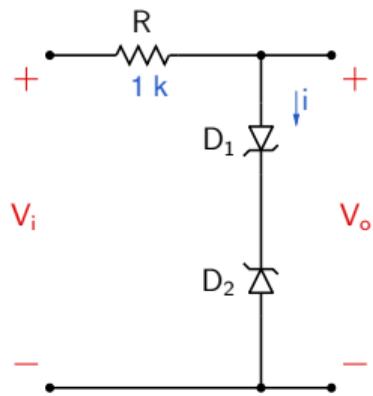

$$V_{on} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot V_o versus V_i .

Diode circuit example (voltage limiter)

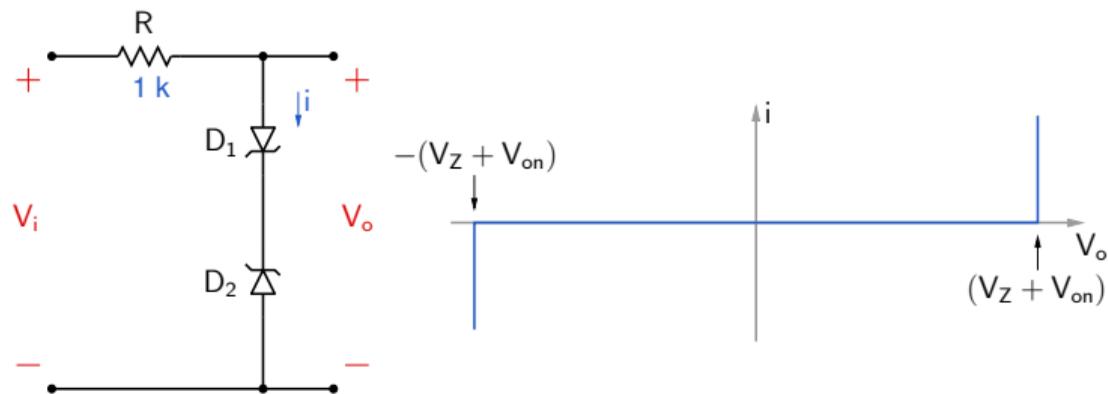


$$V_{on} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot V_o versus V_i .



* For $-5.7\text{ V} < V_i < 5.7\text{ V}$, no conduction is possible $\rightarrow V_o = V_i$.

Diode circuit example (voltage limiter)

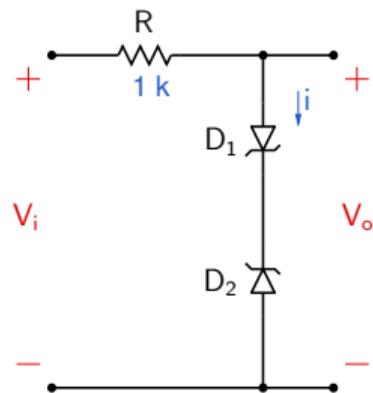


$$V_{\text{on}} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot V_o versus V_i .

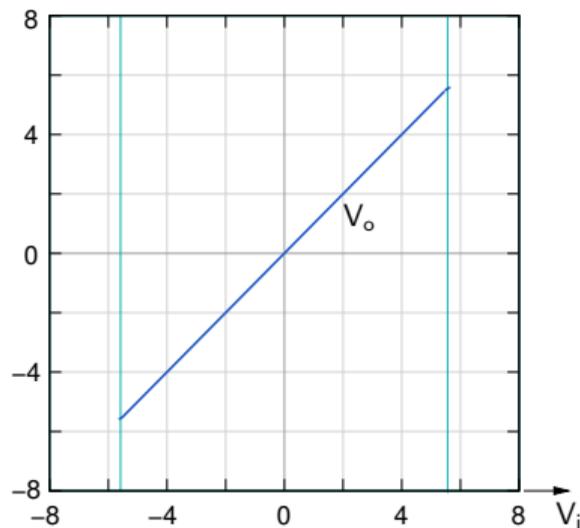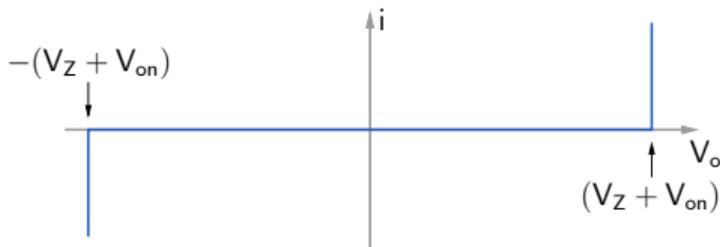



* For $-5.7\text{ V} < V_i < 5.7\text{ V}$, no conduction is possible $\rightarrow V_o = V_i$.

Diode circuit example (voltage limiter)

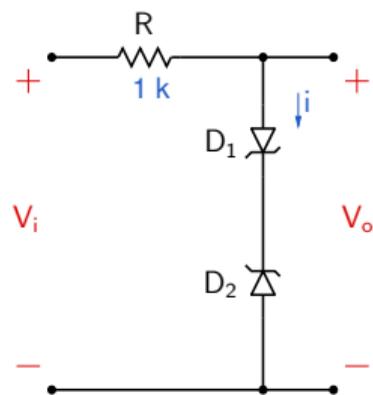


$$V_{\text{on}} = 0.7 \text{ V}, V_Z = 5 \text{ V}.$$

Plot V_o versus V_i .

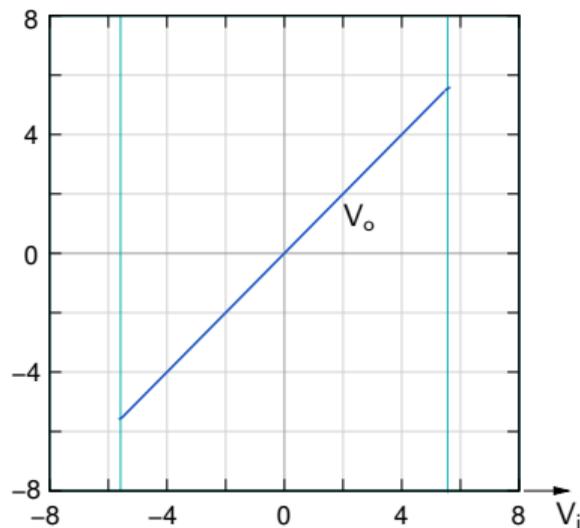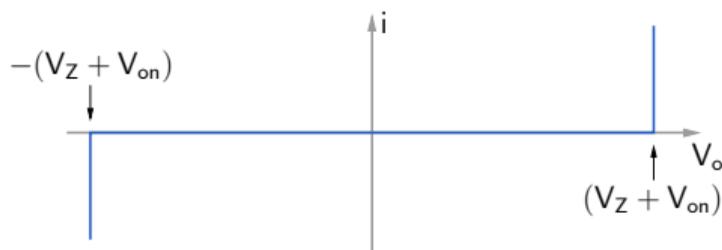



- * For $-5.7 \text{ V} < V_i < 5.7 \text{ V}$, no conduction is possible $\rightarrow V_o = V_i$.
- * For $V_i > 5.7 \text{ V}$, D_1 is forward-biased, D_2 is reverse-biased, and $V_o = (V_{\text{on}} + V_Z)$. The excess voltage $(V_i - (V_{\text{on}} + V_Z))$ drops across R .

Diode circuit example (voltage limiter)

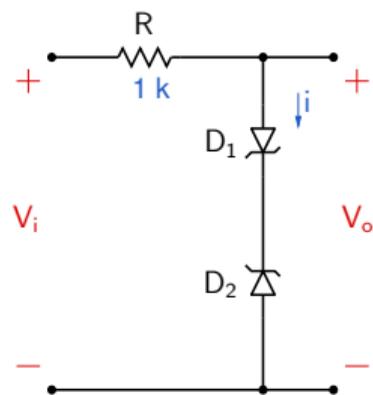


$$V_{\text{on}} = 0.7 \text{ V}, V_Z = 5 \text{ V}.$$

Plot V_o versus V_i .

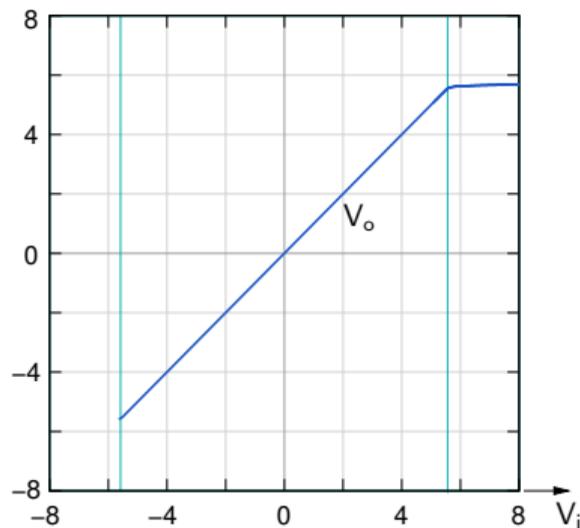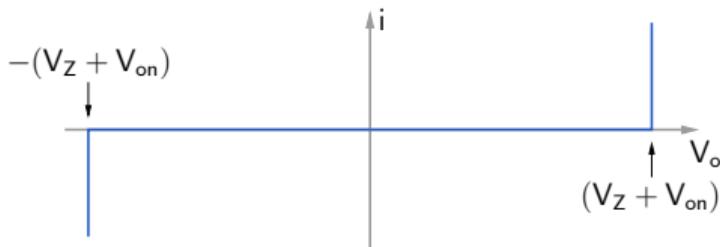


- * For $-5.7\text{V} < V_i < 5.7\text{V}$, no conduction is possible $\rightarrow V_o = V_i$.
- * For $V_i > 5.7\text{V}$, D_1 is forward-biased, D_2 is reverse-biased, and $V_o = (V_{\text{on}} + V_Z)$. The excess voltage $(V_i - (V_{\text{on}} + V_Z))$ drops across R .

Diode circuit example (voltage limiter)

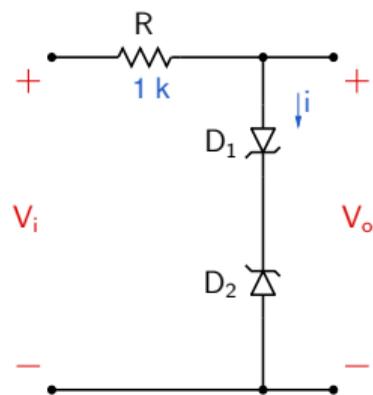


$$V_{\text{on}} = 0.7 \text{ V}, V_Z = 5 \text{ V}.$$

Plot V_o versus V_i .

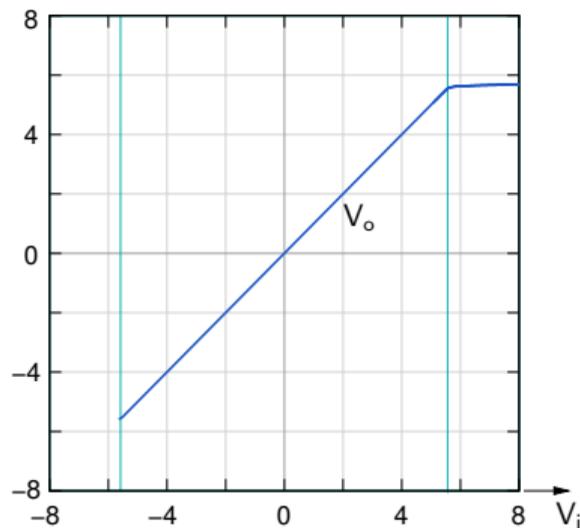



- * For $-5.7\text{V} < V_i < 5.7\text{V}$, no conduction is possible $\rightarrow V_o = V_i$.
- * For $V_i > 5.7\text{V}$, D_1 is forward-biased, D_2 is reverse-biased, and $V_o = (V_{\text{on}} + V_Z)$. The excess voltage $(V_i - (V_{\text{on}} + V_Z))$ drops across R .
- * For $V_i < -5.7\text{V}$, D_2 is forward-biased, D_1 is reverse-biased, and $V_o = -(V_{\text{on}} + V_Z)$. The excess voltage $(-V_i - (V_{\text{on}} + V_Z))$ drops across R .

Diode circuit example (voltage limiter)

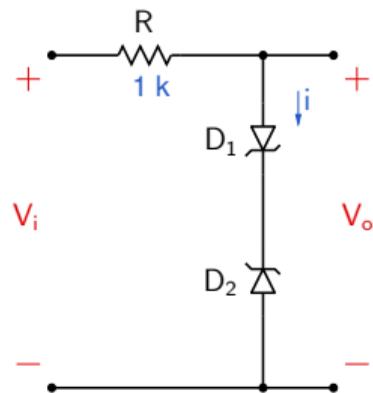



$$V_{on} = 0.7 \text{ V}, V_Z = 5 \text{ V}.$$

Plot V_o versus V_i .

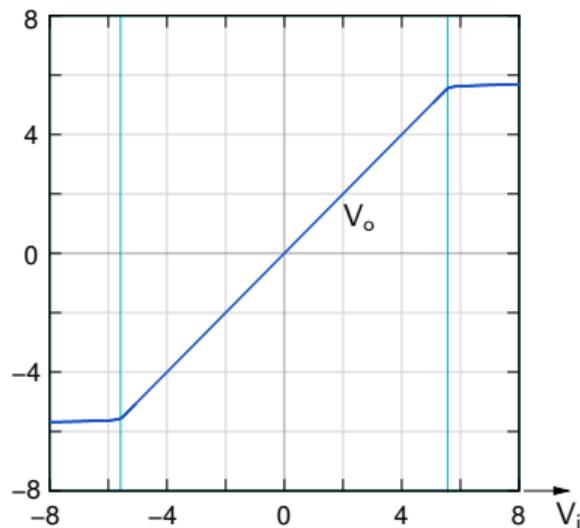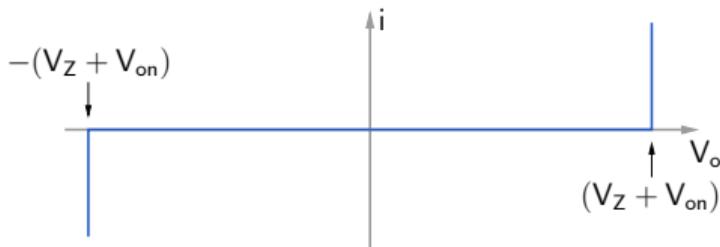

- * For $-5.7 \text{ V} < V_i < 5.7 \text{ V}$, no conduction is possible $\rightarrow V_o = V_i$.
- * For $V_i > 5.7 \text{ V}$, D_1 is forward-biased, D_2 is reverse-biased, and $V_o = (V_{on} + V_Z)$. The excess voltage $(V_i - (V_{on} + V_Z))$ drops across R .
- * For $V_i < -5.7 \text{ V}$, D_2 is forward-biased, D_1 is reverse-biased, and $V_o = -(V_{on} + V_Z)$. The excess voltage $(-V_i - (V_{on} + V_Z))$ drops across R .

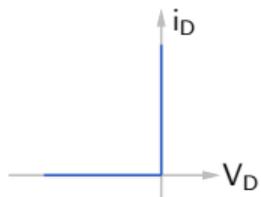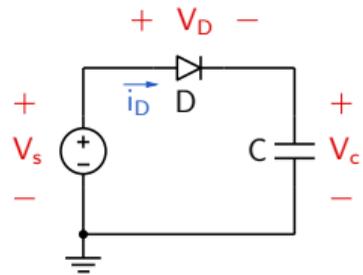Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$



$$V_{on} = 0\text{ V}$$

$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

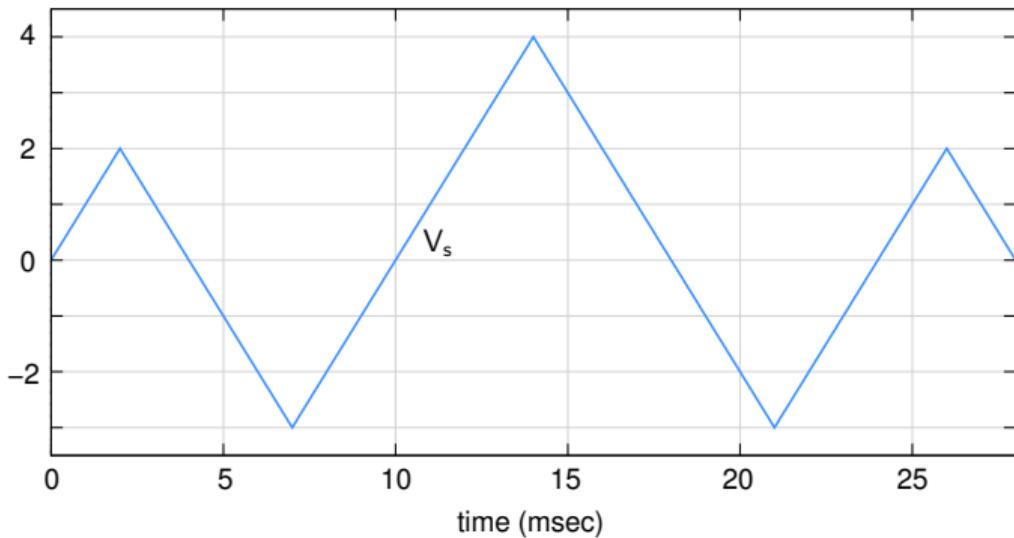

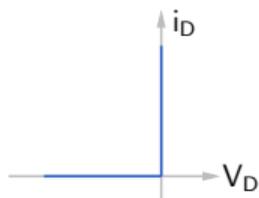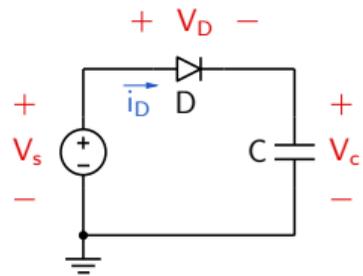Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

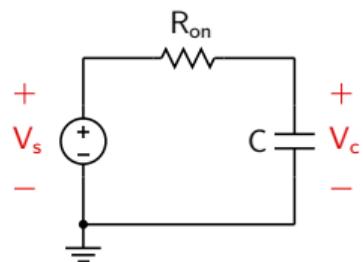


$$V_s > V_c$$

$$\tau = R_{on}C$$


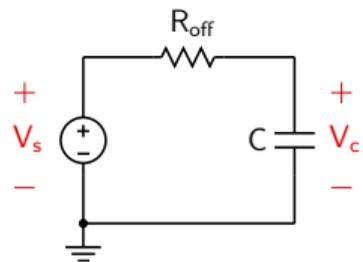


$$V_s < V_c$$

$$\tau = R_{off}C$$

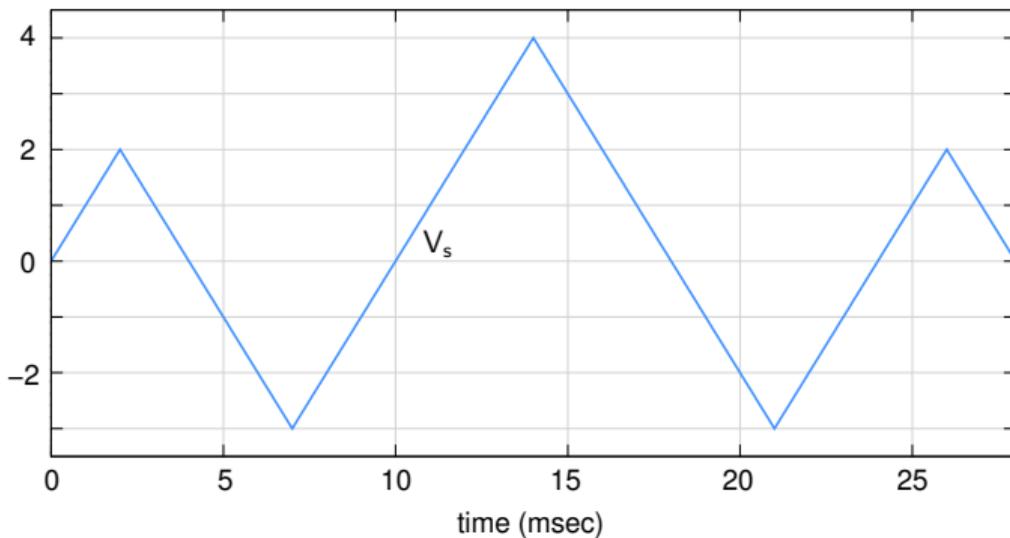

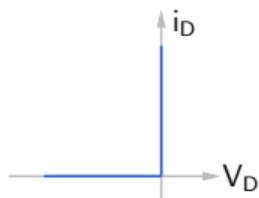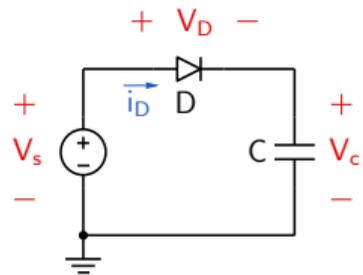Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

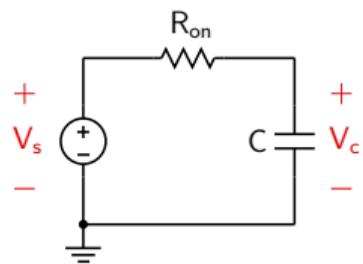


$$V_s > V_c$$

$$\tau = R_{on}C$$



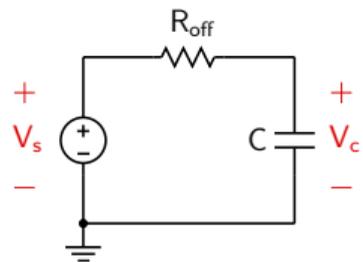


$$V_s < V_c$$


$$\tau = R_{off}C$$

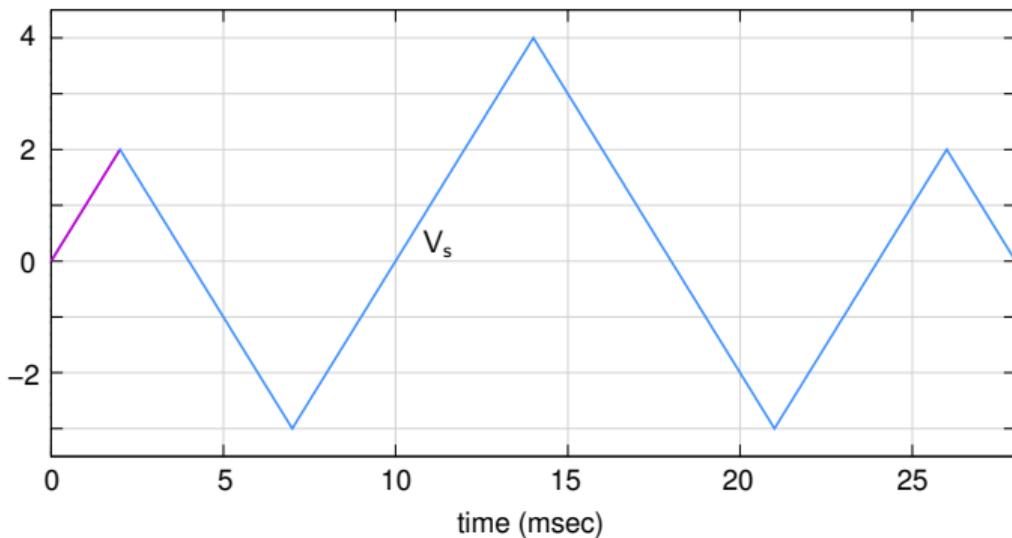

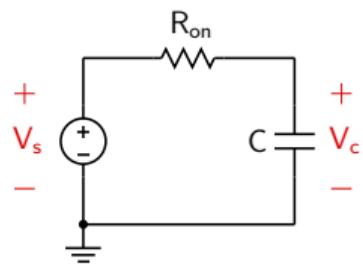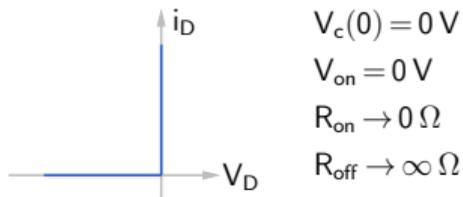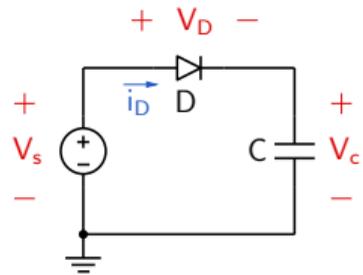
Peak detector (with $V_{on} = 0\text{ V}$)






$V_s > V_c$
 $\tau = R_{on}C$

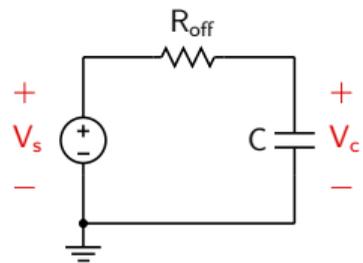


$V_s < V_c$
 $\tau = R_{off}C$

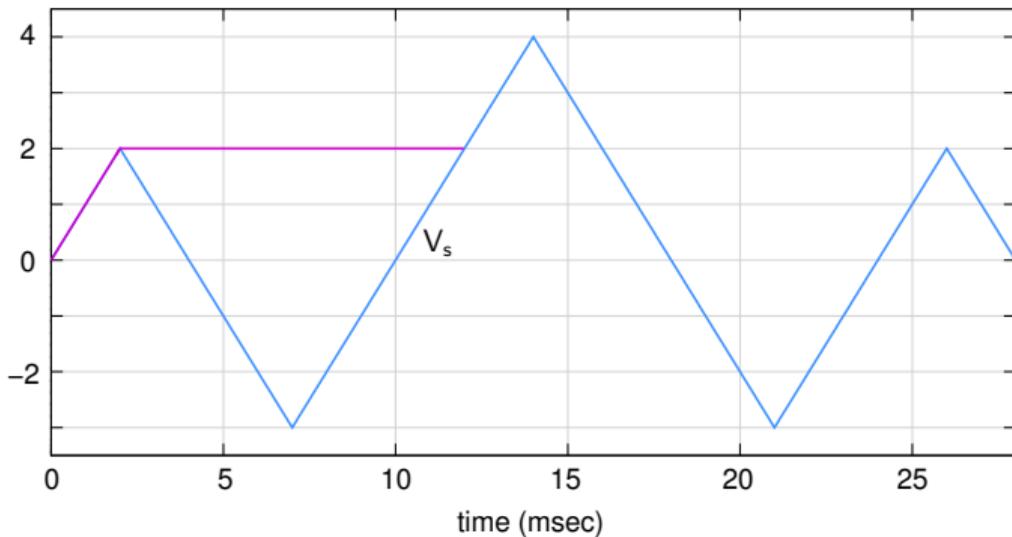

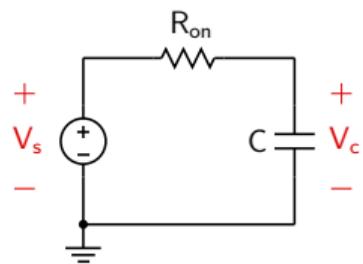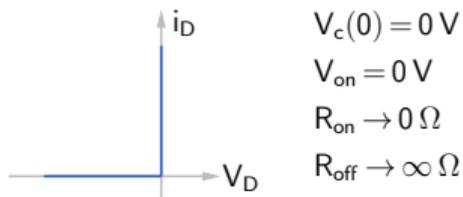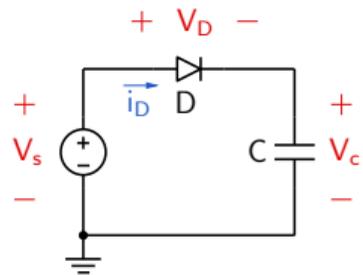
Peak detector (with $V_{on} = 0\text{ V}$)





$V_s > V_c$
 $\tau = R_{on}C$

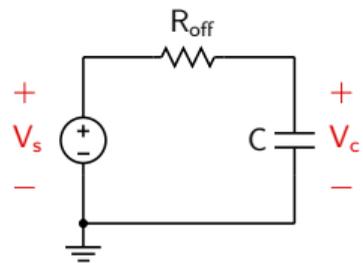

$V_s < V_c$
 $\tau = R_{off}C$

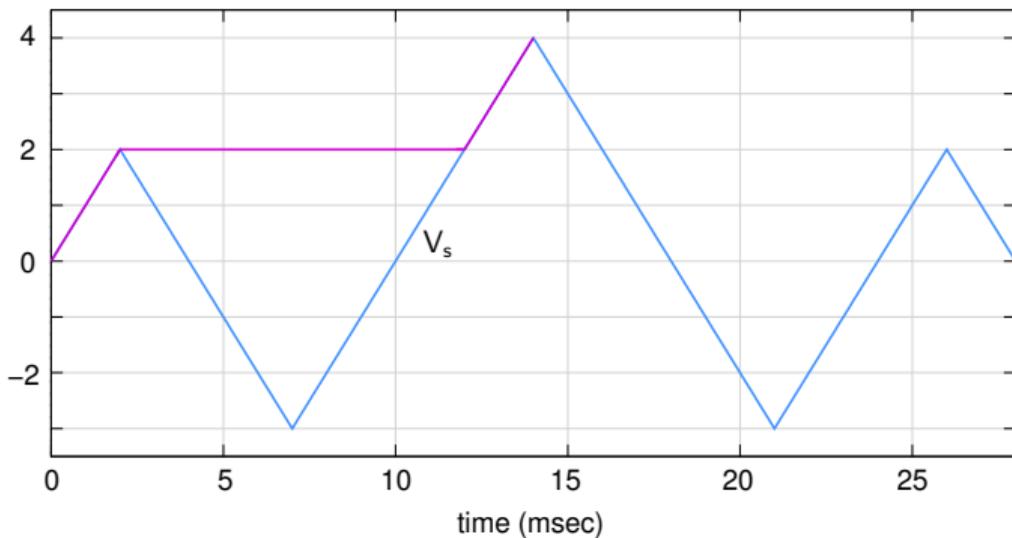

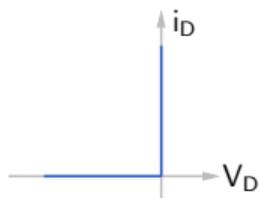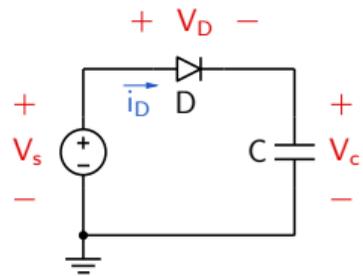Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

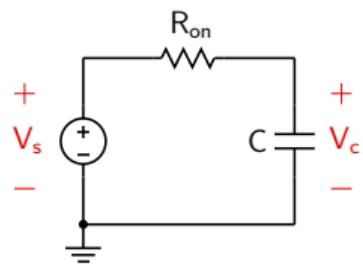


$$V_s > V_c$$

$$\tau = R_{on}C$$


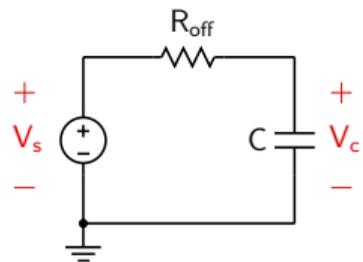


$$V_s < V_c$$

$$\tau = R_{off}C$$

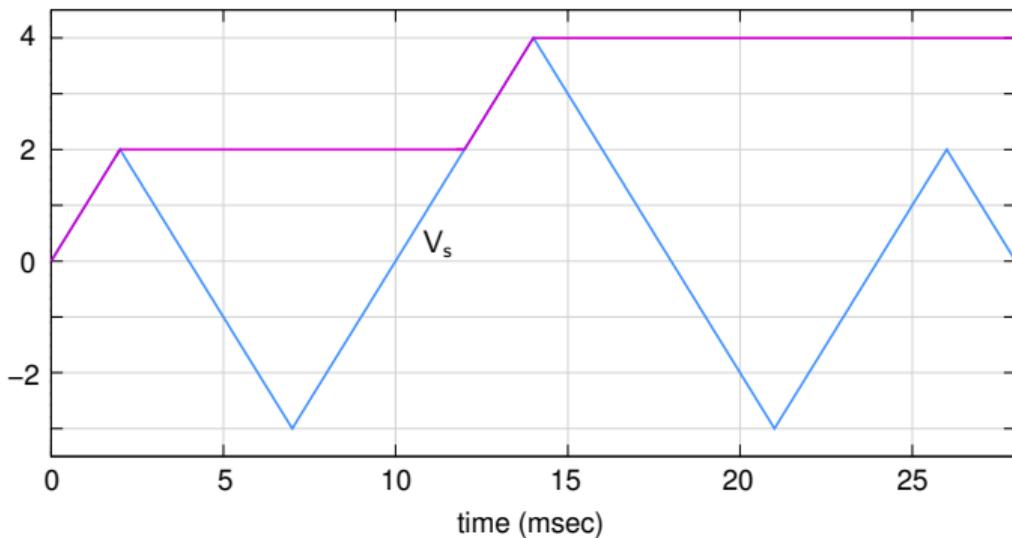

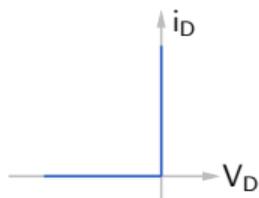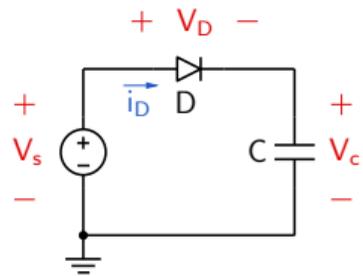Peak detector (with $V_{on} = 0\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

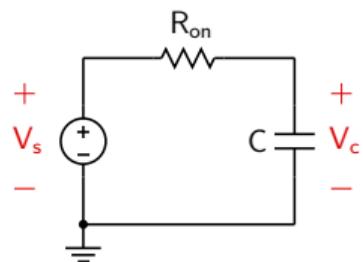


$$V_s > V_c$$

$$\tau = R_{on}C$$


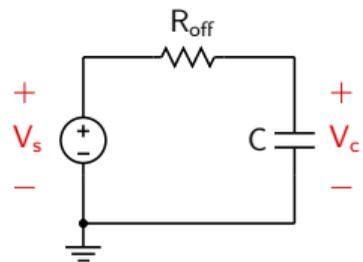


$$V_s < V_c$$

$$\tau = R_{off}C$$

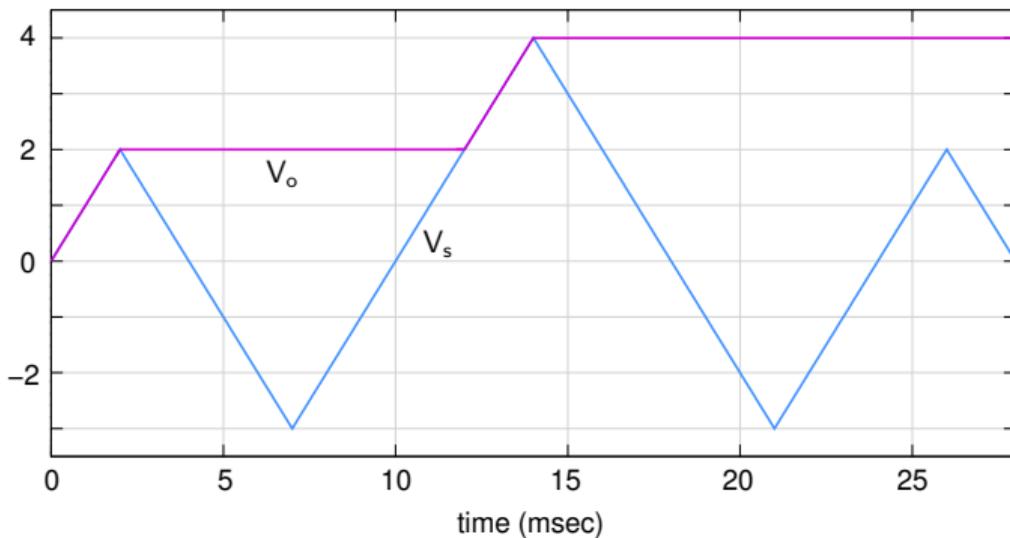

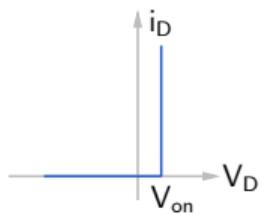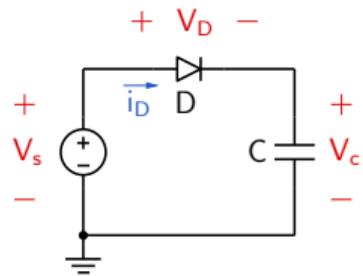Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$



$$V_{on} = 0.7\text{ V}$$

$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

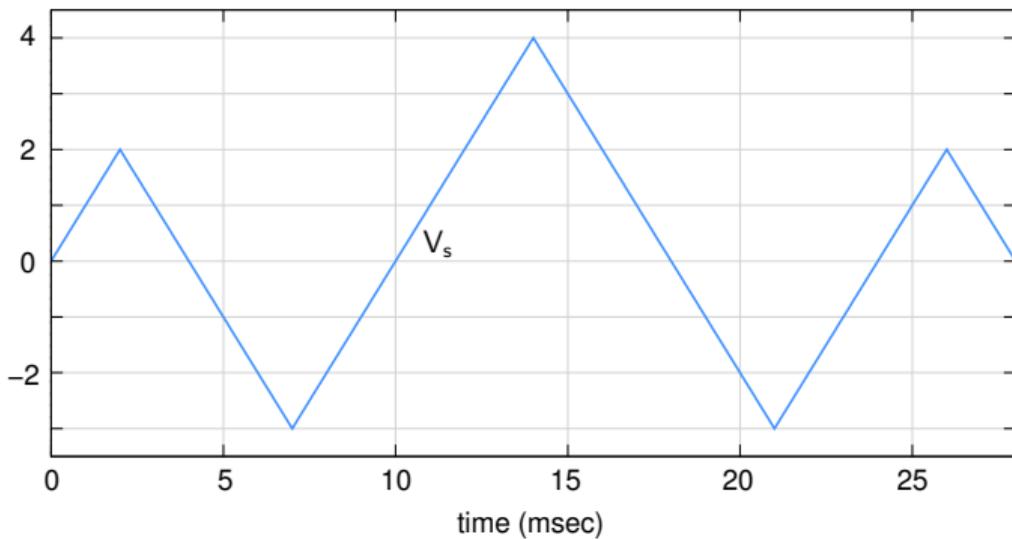

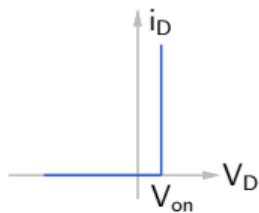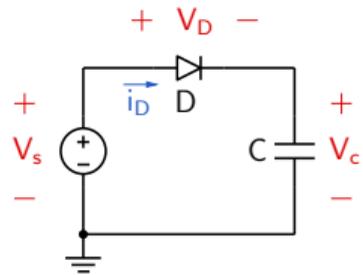Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

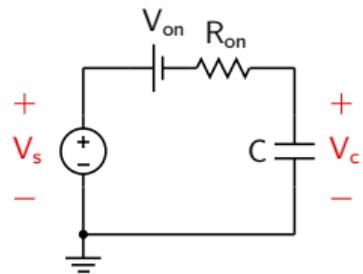


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


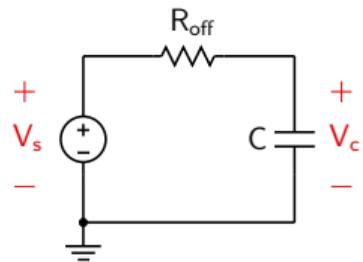


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

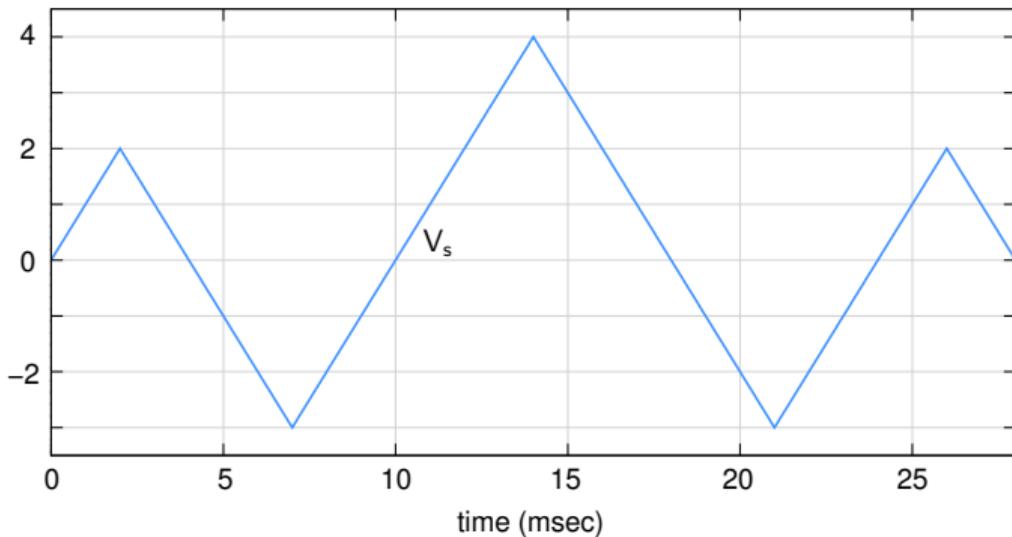

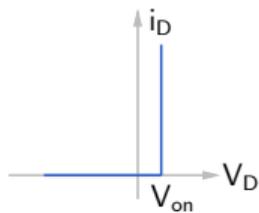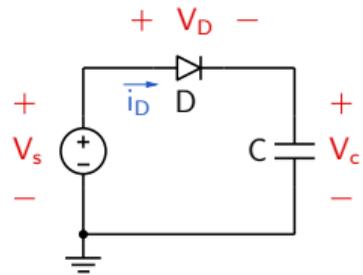Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

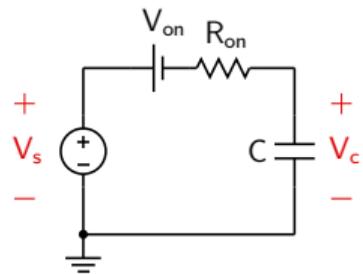


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


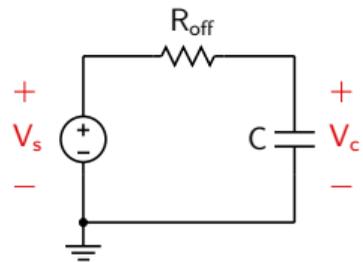


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

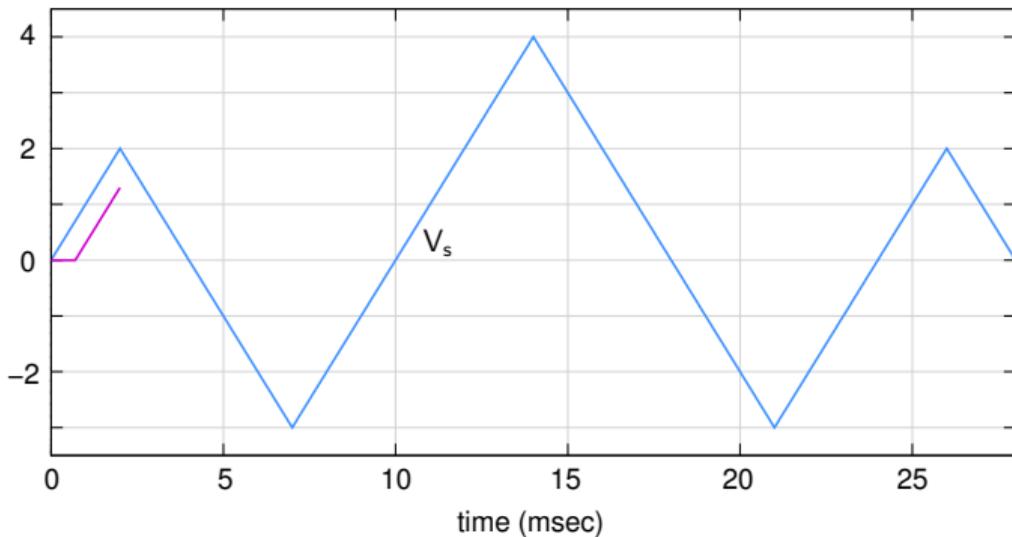

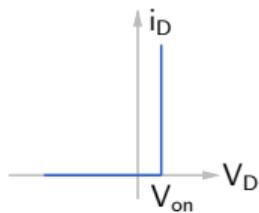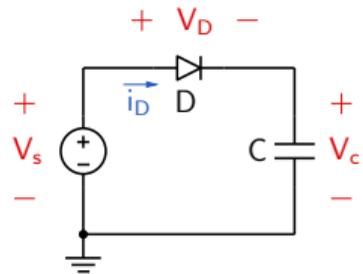Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

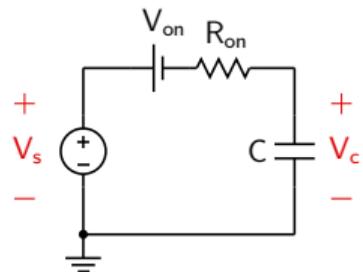


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


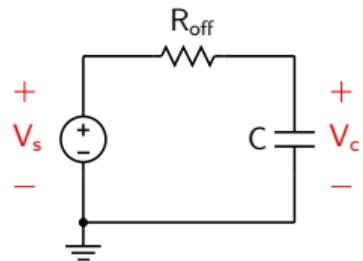


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

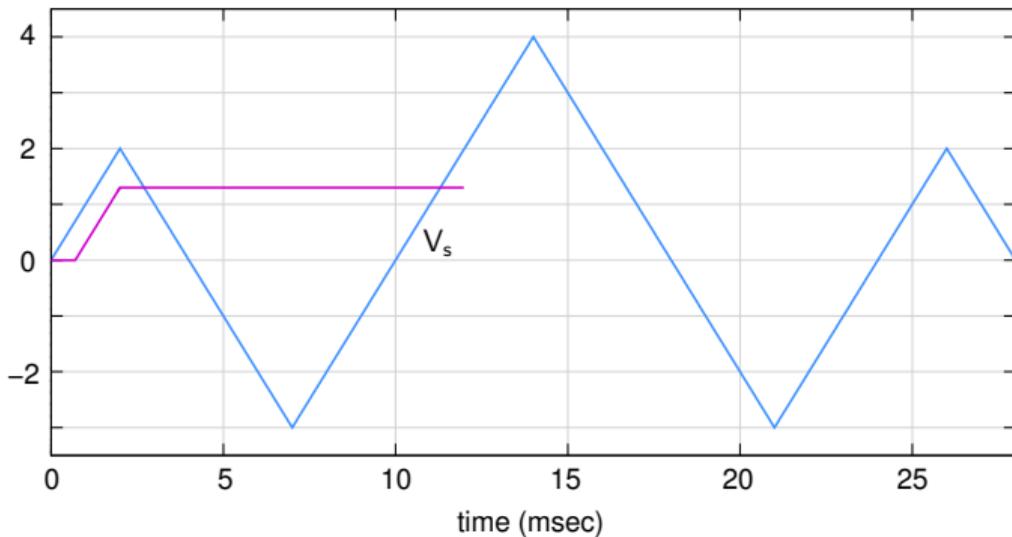

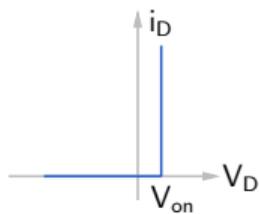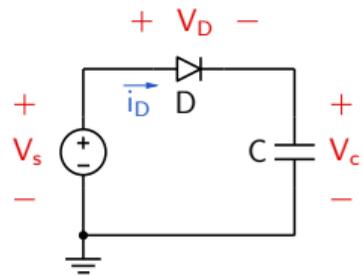Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

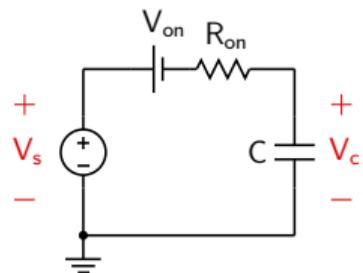


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


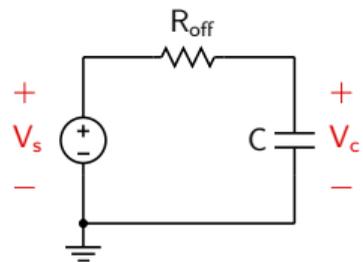


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

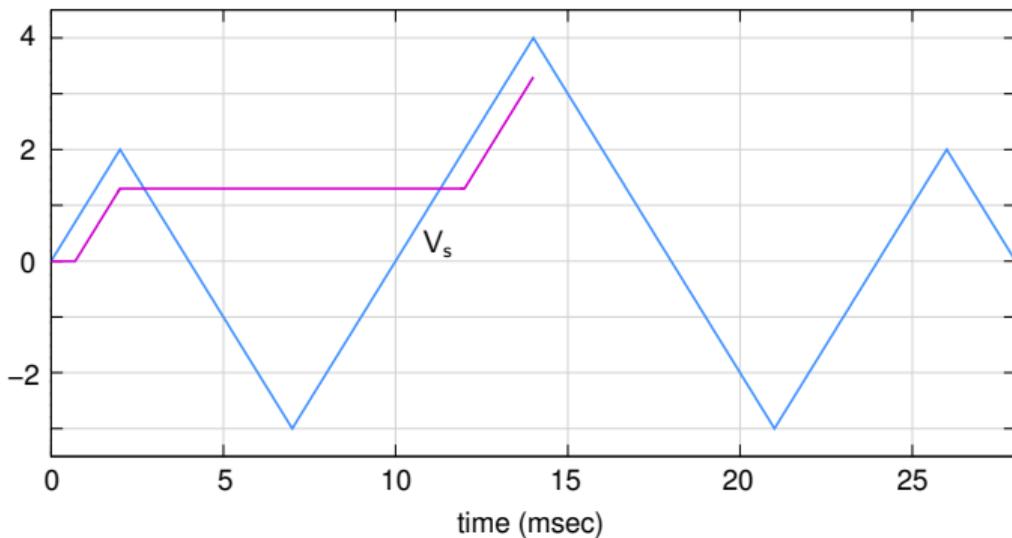

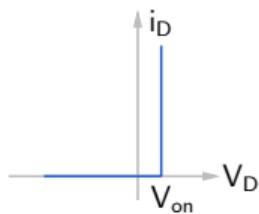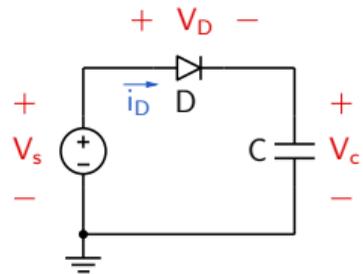Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

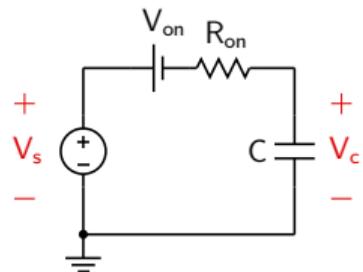


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$


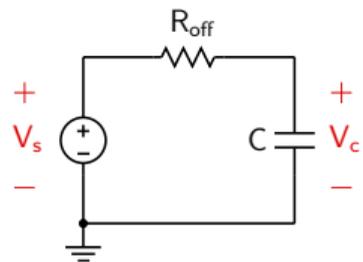


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

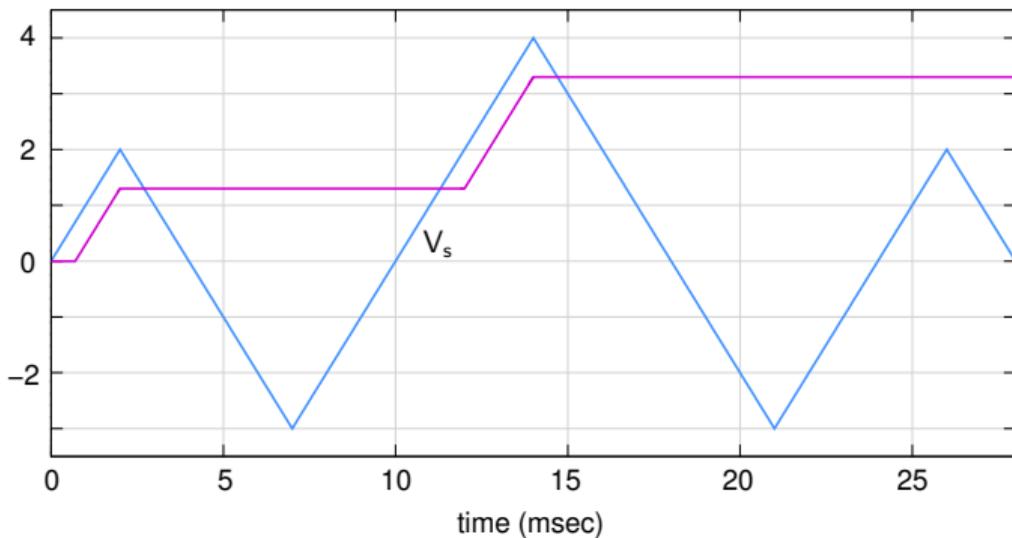

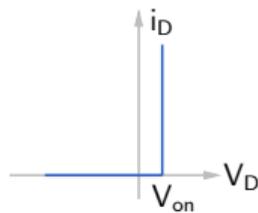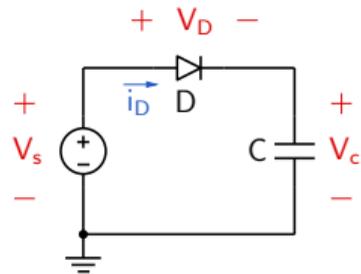Peak detector (with $V_{on} = 0.7\text{ V}$)




$$V_c(0) = 0\text{ V}$$

$$V_{on} = 0.7\text{ V}$$


$$R_{on} \rightarrow 0\ \Omega$$

$$R_{off} \rightarrow \infty\ \Omega$$

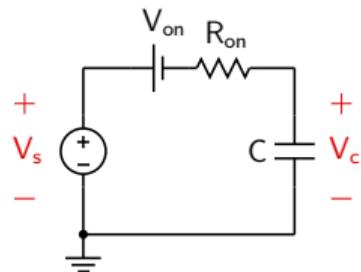


$$V_s > V_c + V_{on}$$

$$\tau = R_{on}C$$

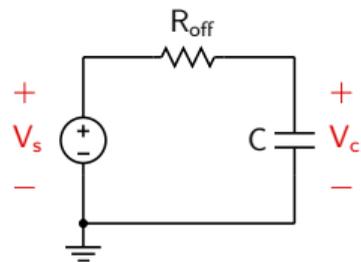


$$V_s < V_c + V_{on}$$

$$\tau = R_{off}C$$

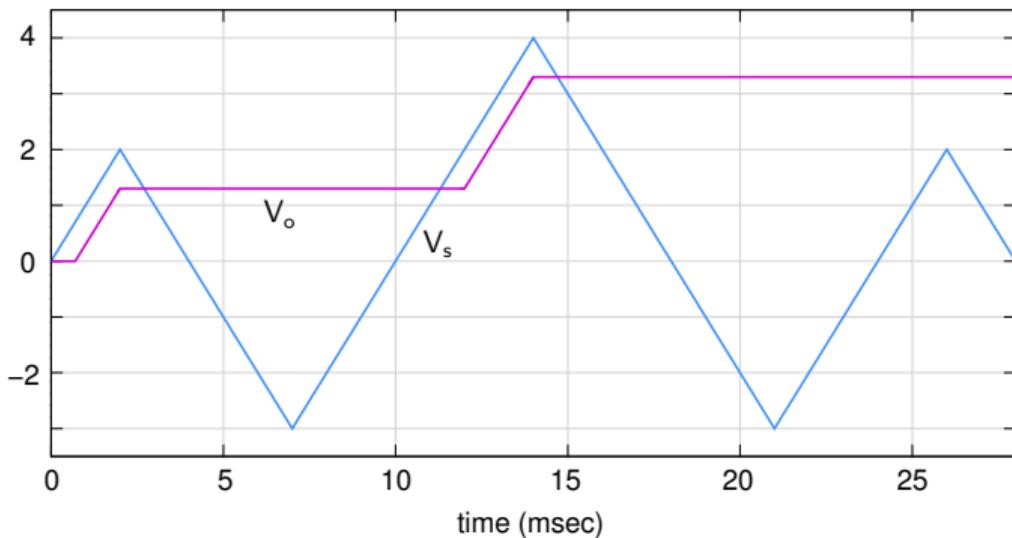


Clamper circuits

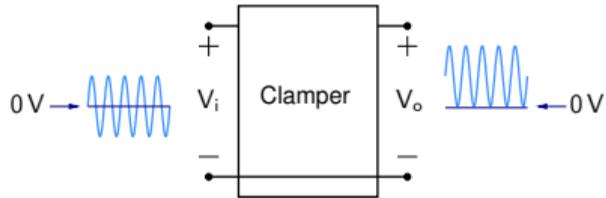


- * A clamper circuit provides a “level shift.” (The shape of the input signal is not altered.)

Clamper circuits

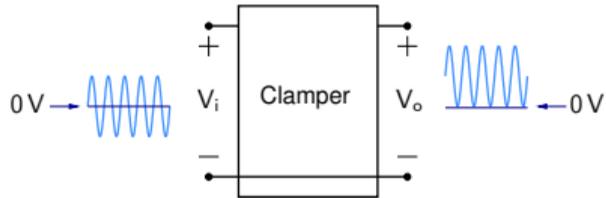



- * A clamper circuit provides a “level shift.” (The shape of the input signal is not altered.)
- * The shift could be positive or negative.

Clamper circuits

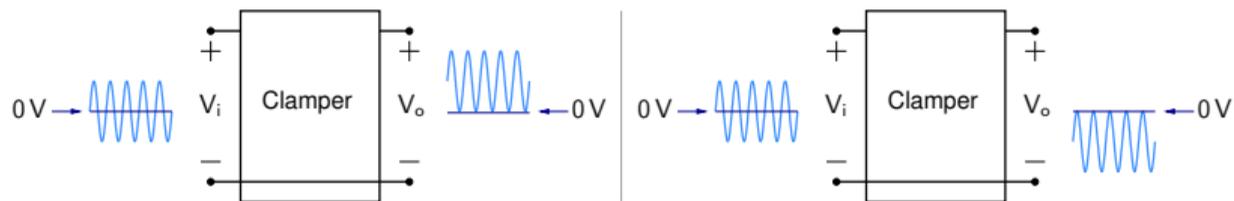

- * A clamper circuit provides a “level shift.” (The shape of the input signal is not altered.)
- * The shift could be positive or negative.

Clamper circuits

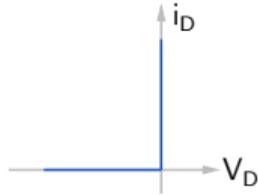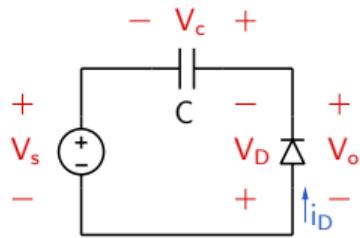


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

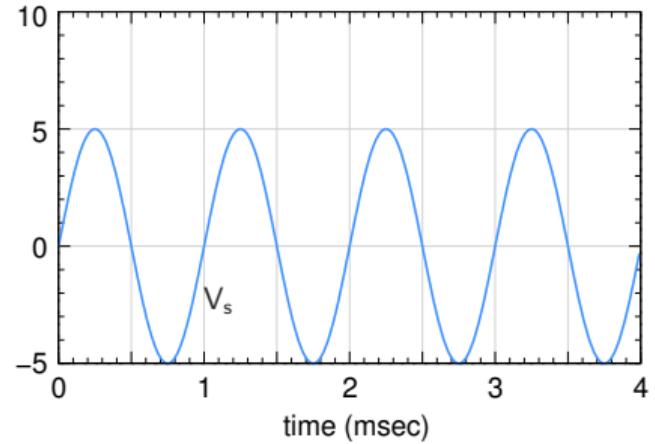

Clamper circuits

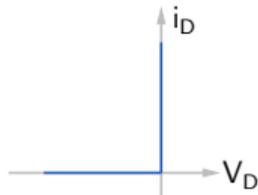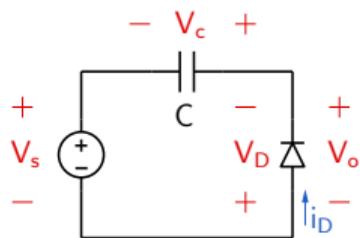


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

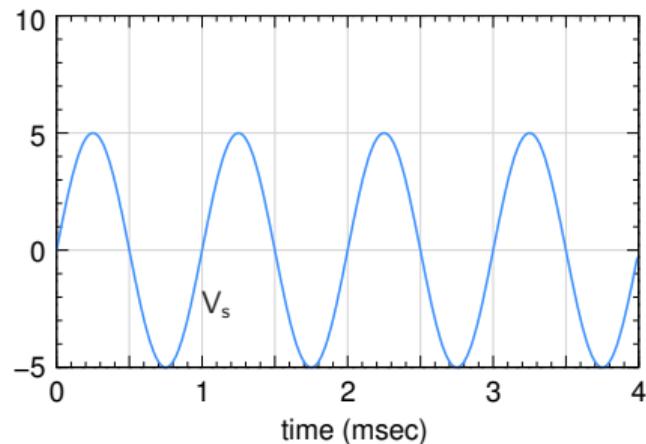

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.

Clamper circuits

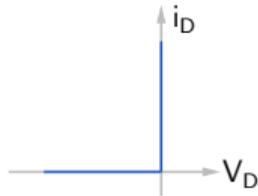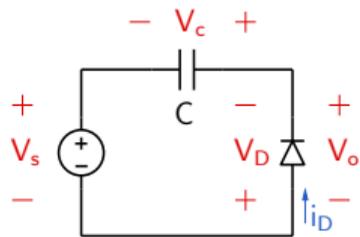


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

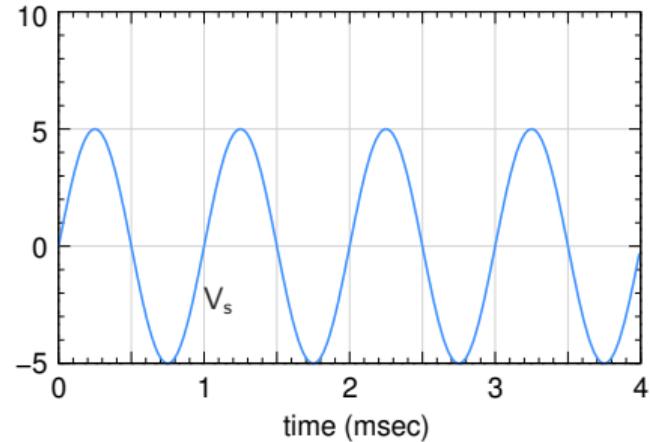

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

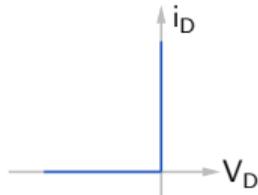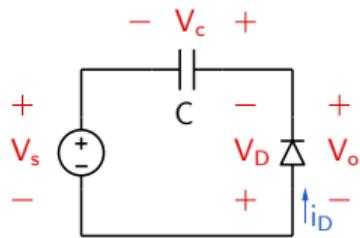


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

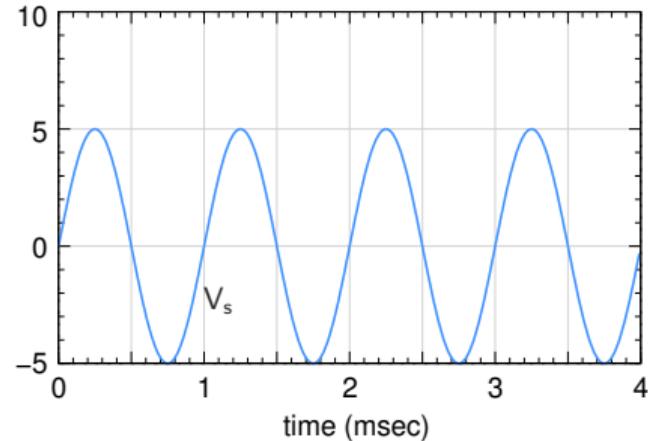

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

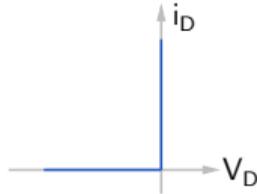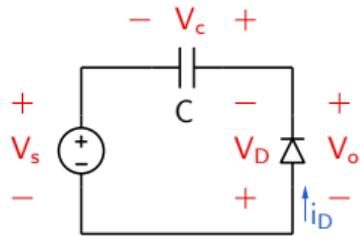


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

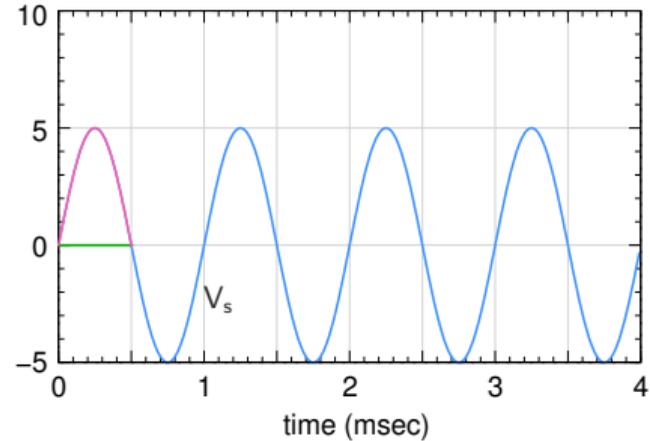

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

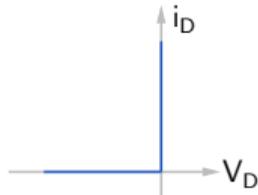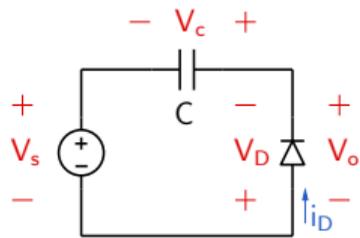


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

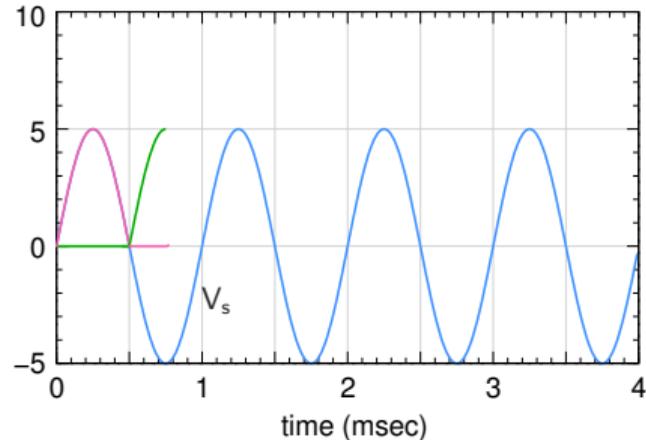

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

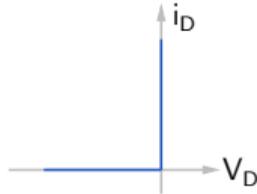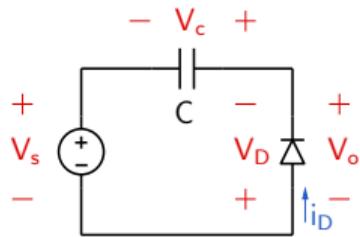


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

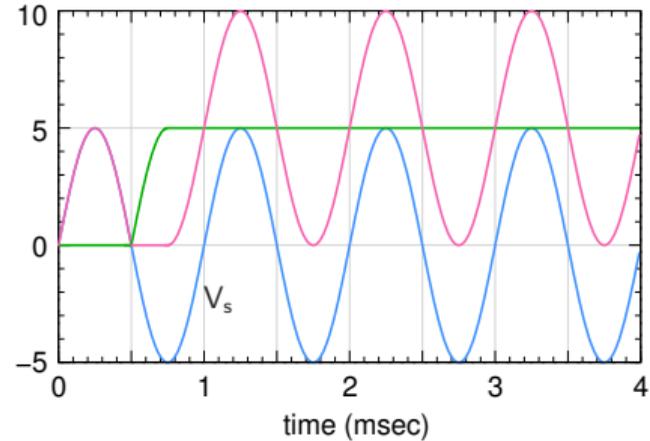

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

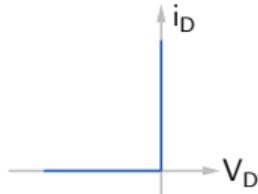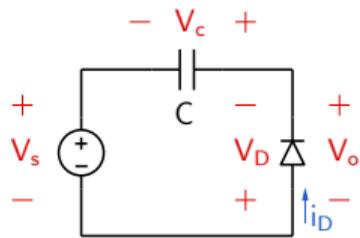


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

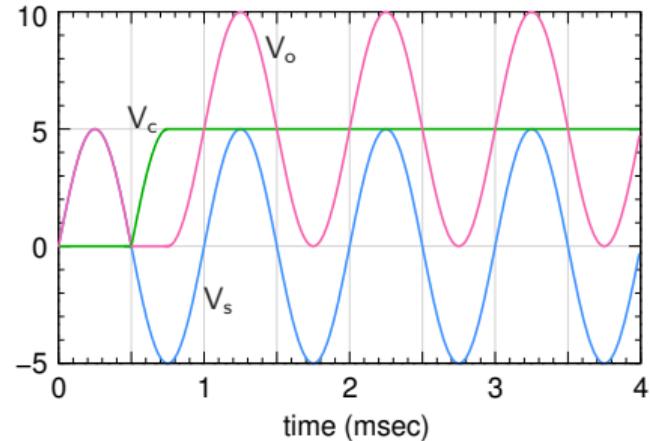

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.

Clamper circuits

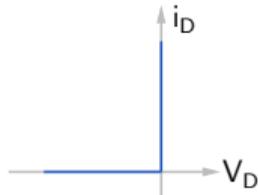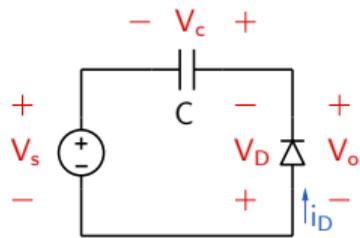


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

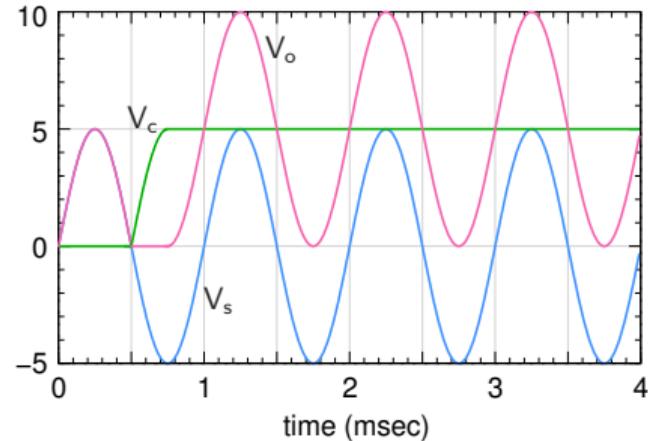

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$, i.e., a positive level shift.
- * Note that we are generally interested only in the steady-state behaviour and not in the transient at the beginning.

Clamper circuits

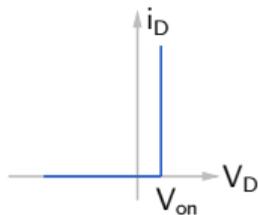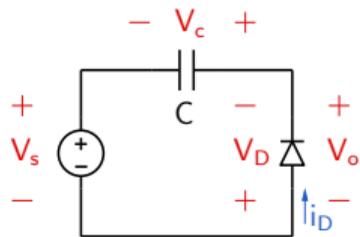


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

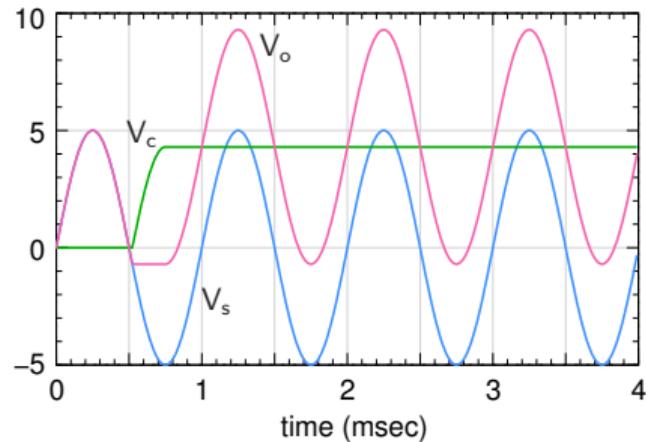

Clamper circuits

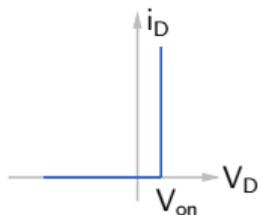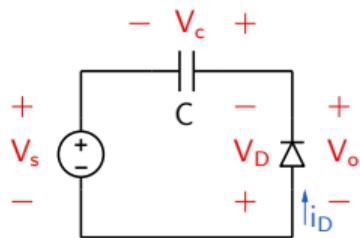


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

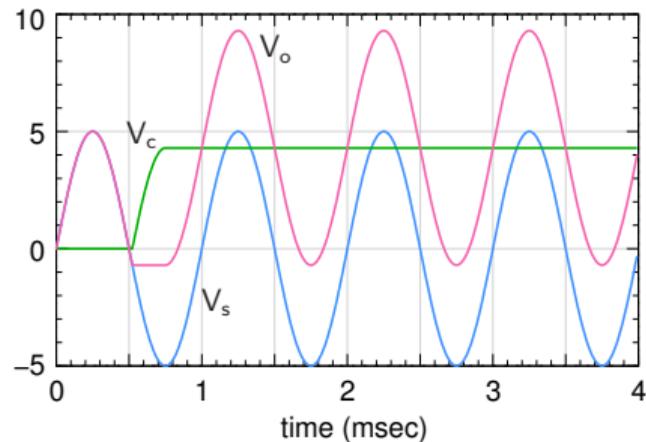

- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit). In this phase,
 $V_c + V_s + V_{on} = 0 \rightarrow V_c = -V_s - V_{on}$.

Clamper circuits

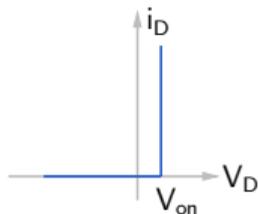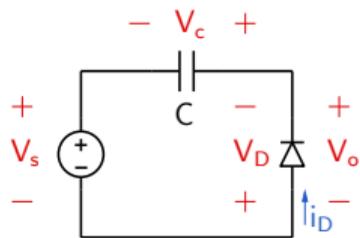


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

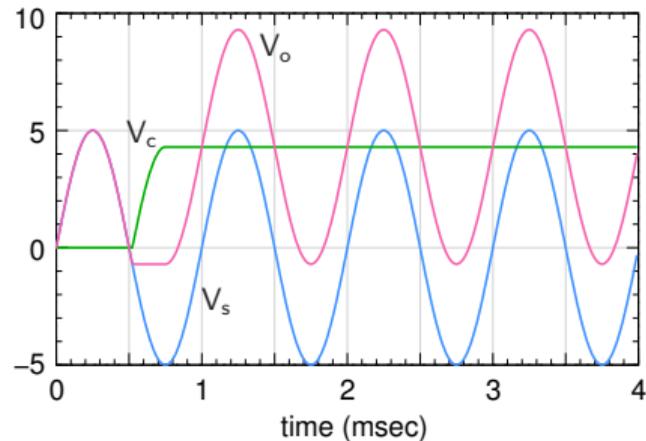



- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit).

In this phase,

$$V_c + V_s + V_{on} = 0 \rightarrow V_c = -V_s - V_{on}.$$

- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

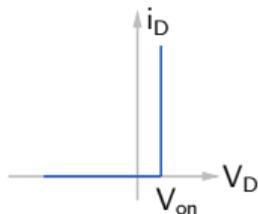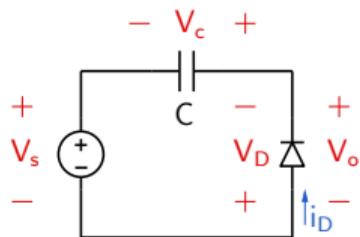


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

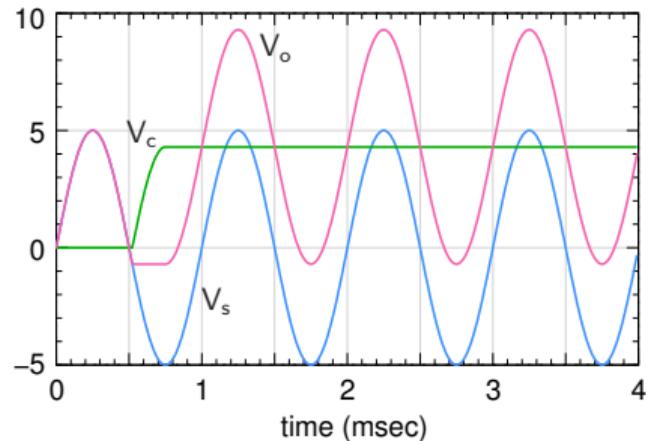

- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit). In this phase,
 $V_c + V_s + V_{on} = 0 \rightarrow V_c = -V_s - V_{on}$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value ($V_m - V_{on}$), it cannot change any more. We then have
 $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m - V_{on}$. In this case, V_o gets clamped at -0.7 V .

Clamper circuits

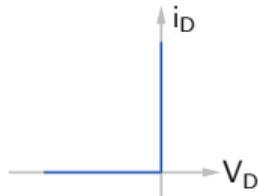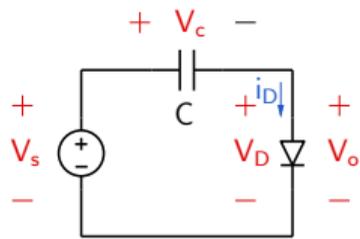


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

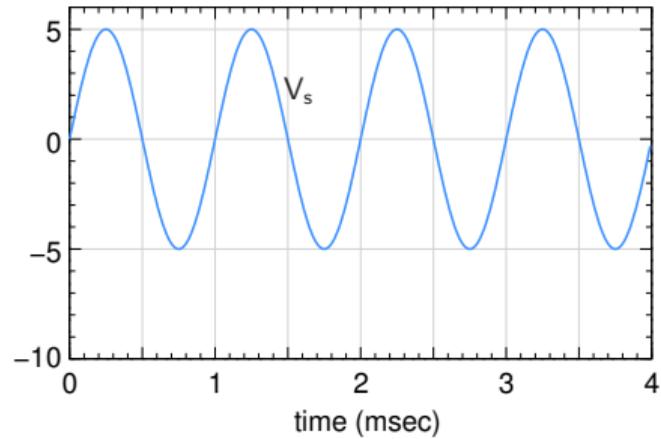

Clamper circuits

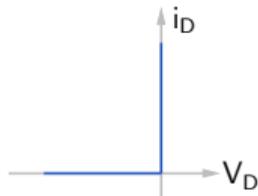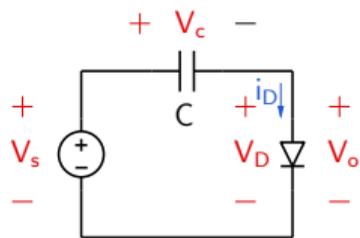


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

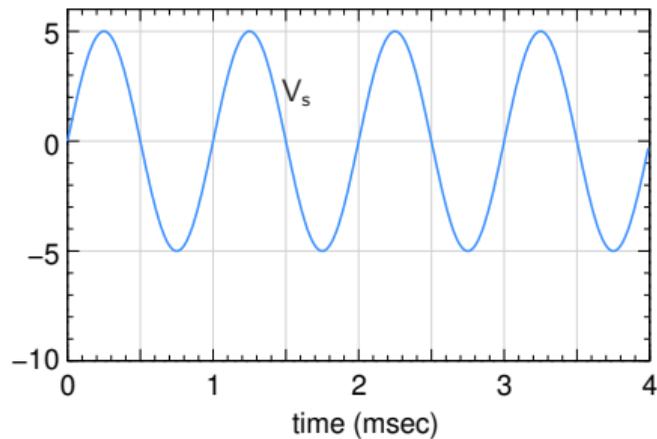

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.

Clamper circuits

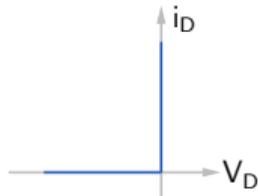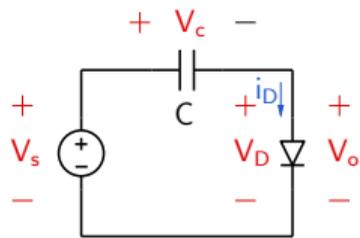


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

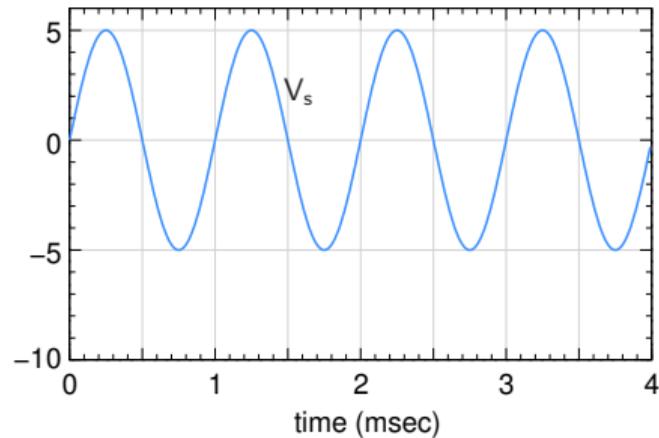

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

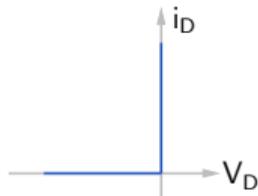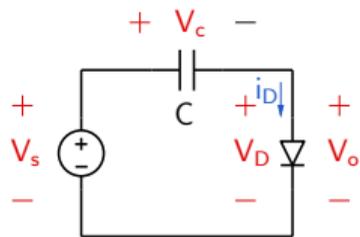


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

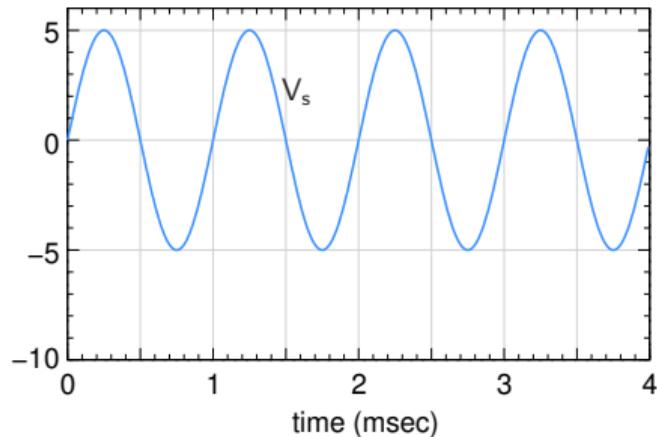

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

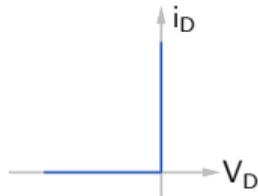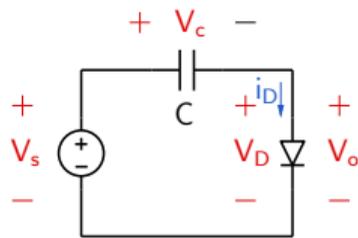


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

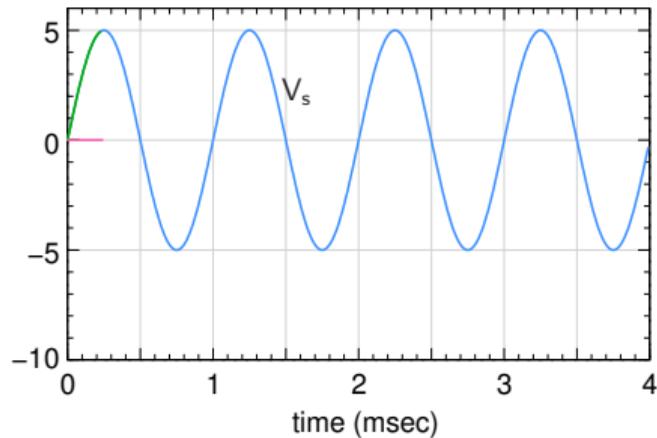

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

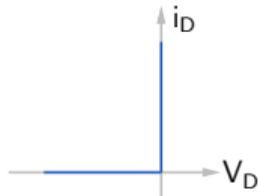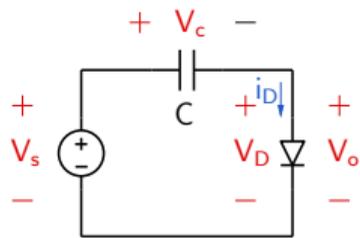


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

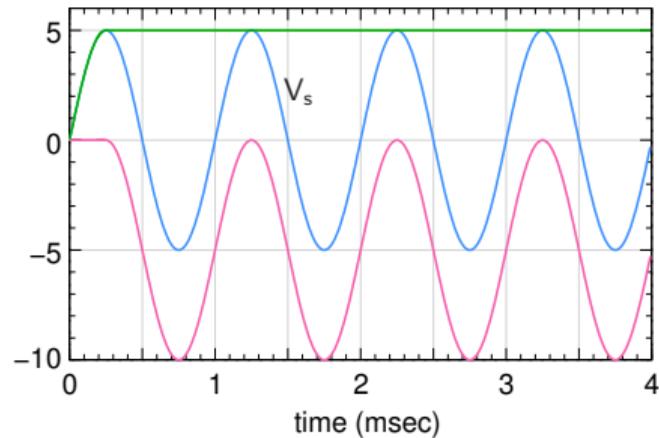

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

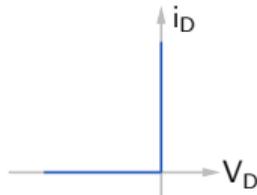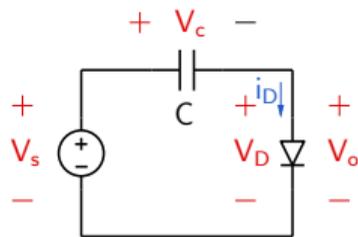


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

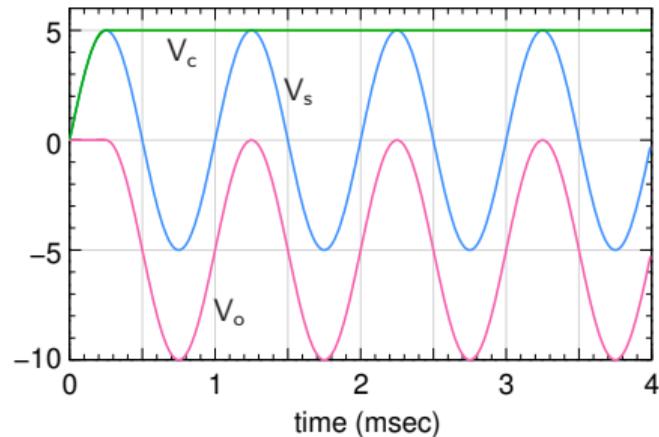

- * When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_D = 0 \rightarrow V_c - V_s = 0 \rightarrow V_c = V_s$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m$, i.e., a negative level shift.

Clamper circuits

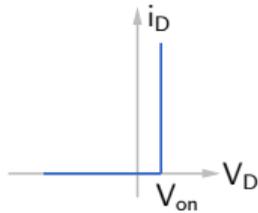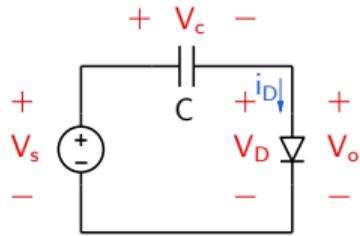


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$



$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

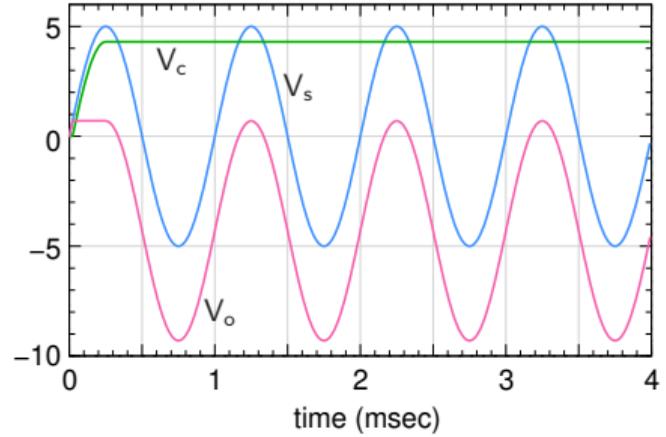

Clamper circuits

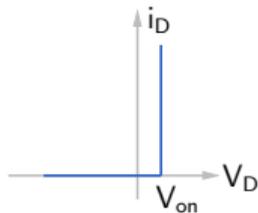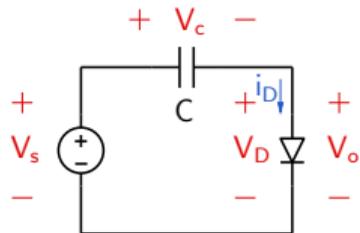


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$

$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$


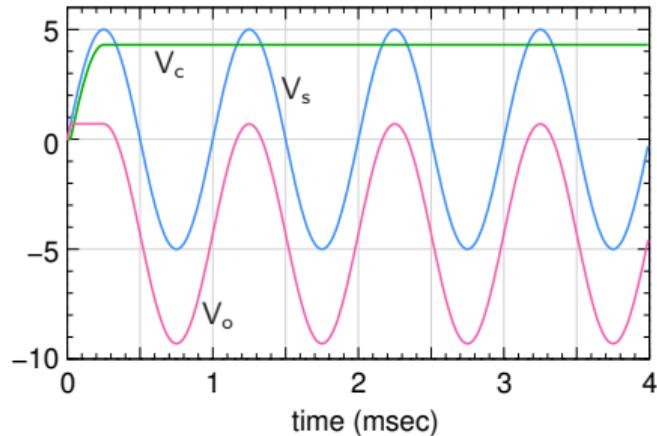


* When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit).

In this phase,

$$V_c + V_{on} - V_s = 0 \rightarrow V_c = V_s - V_{on}.$$

Clamper circuits

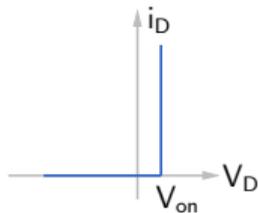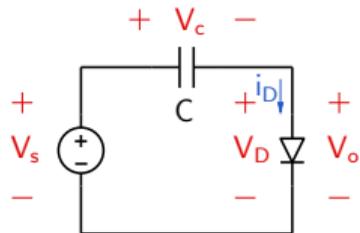


$$V_s(t) = V_m \sin \omega t$$

$$V_c(0) = 0 \text{ V}$$

$$V_{on} = 0.7 \text{ V}$$



$$R_{on} \rightarrow 0 \Omega$$

$$R_{off} \rightarrow \infty \Omega$$

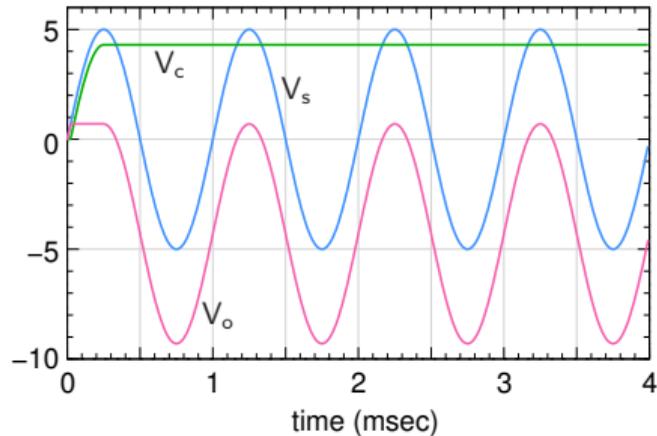


- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit).
In this phase,
 $V_c + V_{on} - V_s = 0 \rightarrow V_c = V_s - V_{on}$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.

Clamper circuits

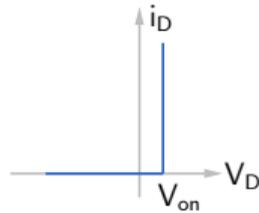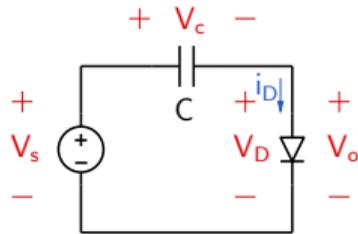

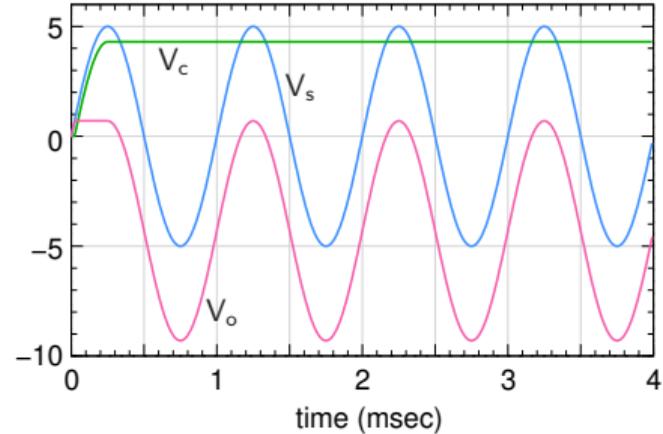
$$\begin{aligned}V_s(t) &= V_m \sin \omega t \\V_c(0) &= 0 \text{ V} \\V_{on} &= 0.7 \text{ V} \\R_{on} &\rightarrow 0 \Omega \\R_{off} &\rightarrow \infty \Omega\end{aligned}$$




- * When D conducts, the capacitor charges instantaneously since R_{on} is small (as in the last circuit). In this phase,
 $V_c + V_{on} - V_s = 0 \rightarrow V_c = V_s - V_{on}$.
- * V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse direction.
- * After V_c reaches its maximum value ($V_m - V_{on}$), it cannot change any more. We then have
 $V_o(t) = V_s(t) - V_c(t) = V_s(t) - V_m + V_{on}$. In this case, V_o gets clamped at 0.7V.

Voltage doubler (peak-to-peak detector)

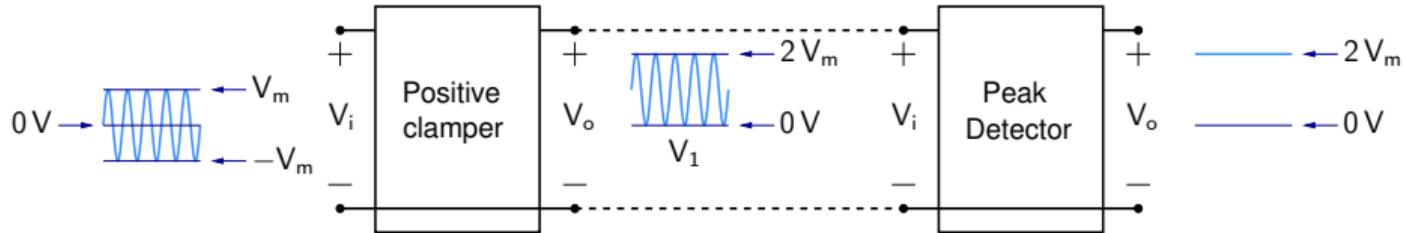


Voltage doubler (peak-to-peak detector)

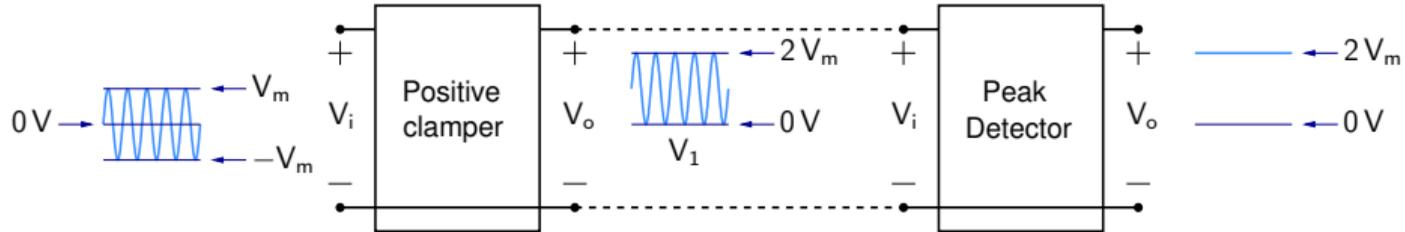


* Input voltage: $-V_m$ to V_m

Voltage doubler (peak-to-peak detector)

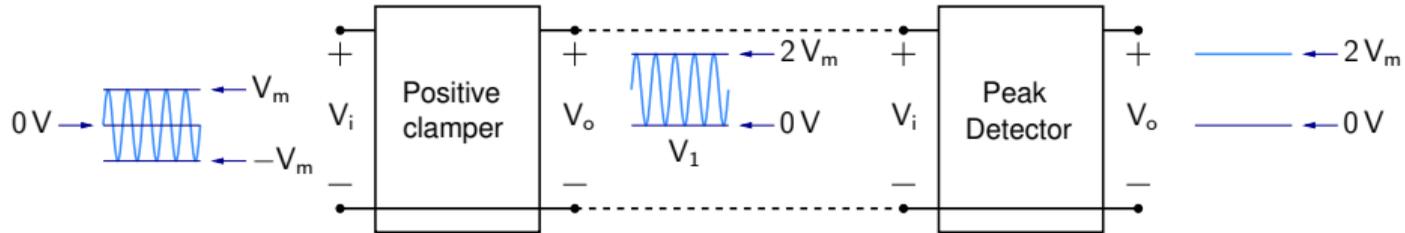



- * Input voltage: $-V_m$ to V_m
- * Output of positive clamper (V_1): 0 to $2V_m$

Voltage doubler (peak-to-peak detector)



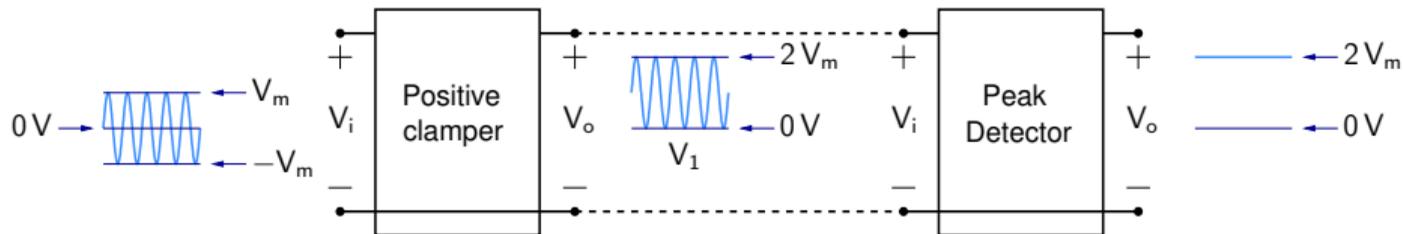


- * Input voltage: $-V_m$ to V_m
- * Output of positive clamper (V_1): 0 to $2V_m$
- * The peak detector detects the peak of $V_1(t)$, i.e., $2V_m$ (dc).





Voltage doubler (peak-to-peak detector)

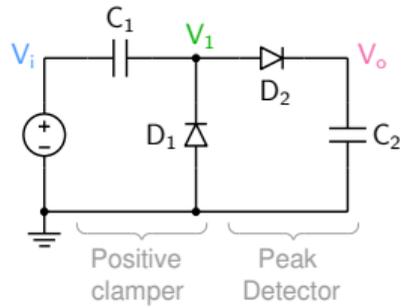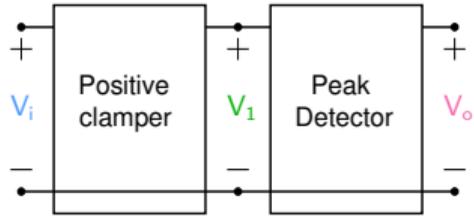



Voltage doubler (peak-to-peak detector)

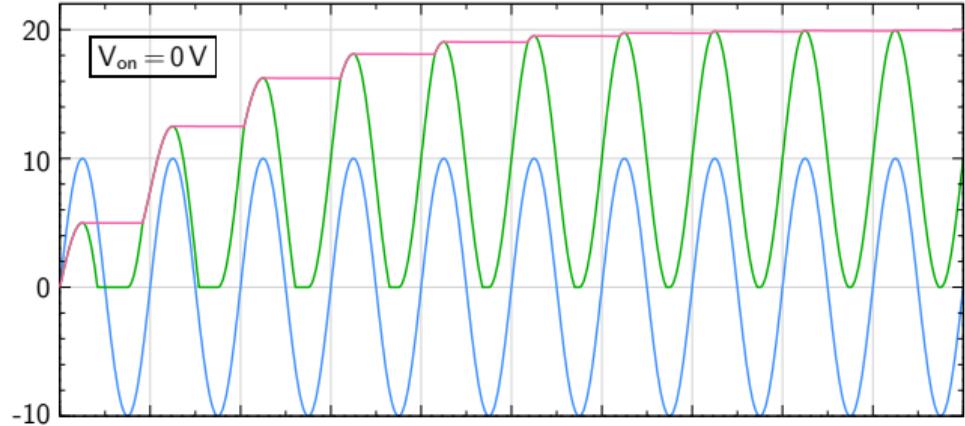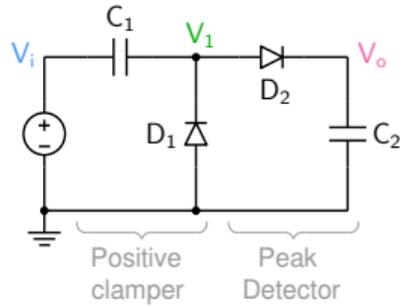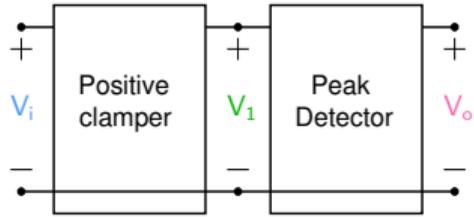


Voltage doubler (peak-to-peak detector)

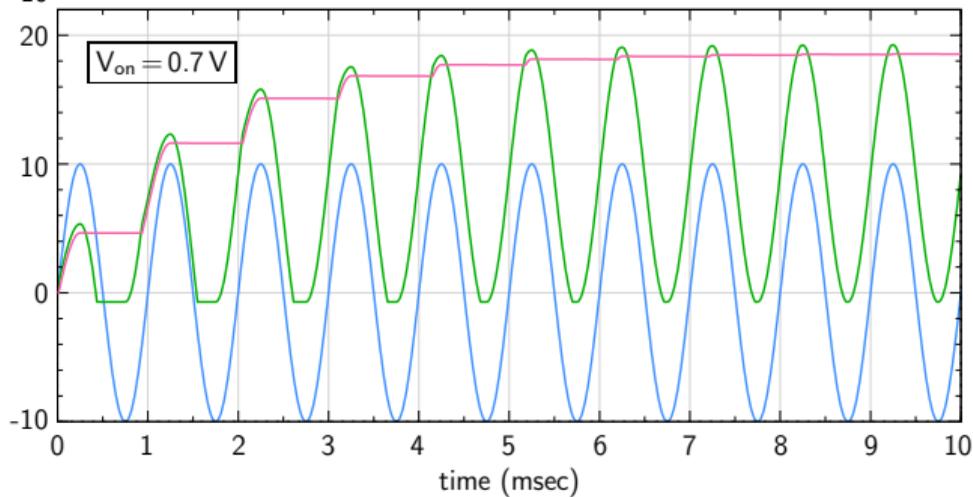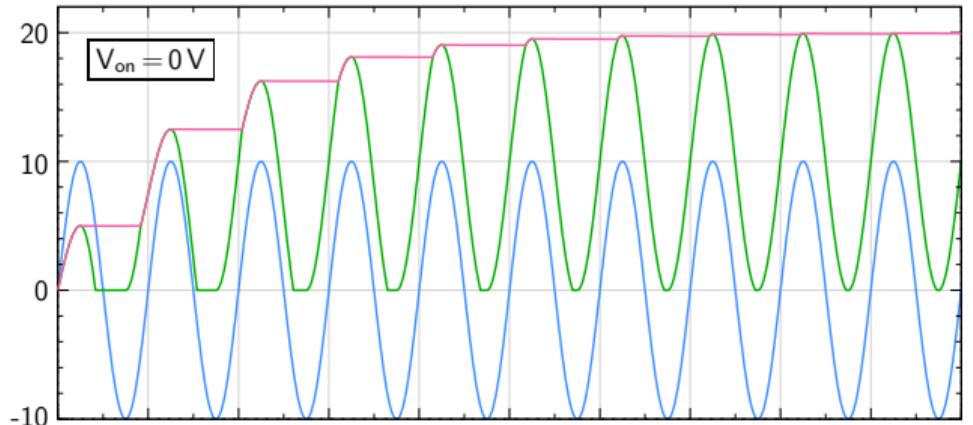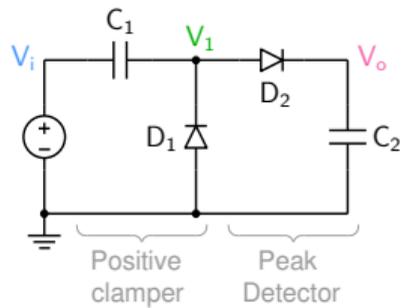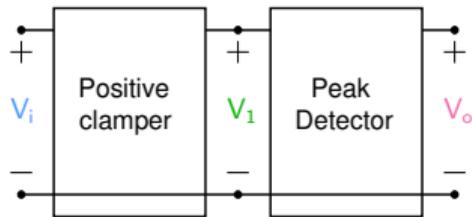


Voltage doubler (peak-to-peak detector)

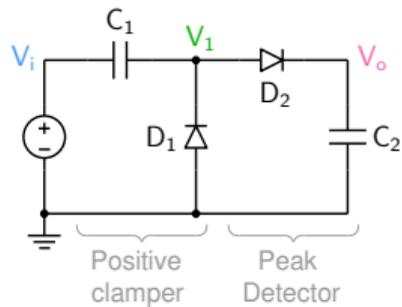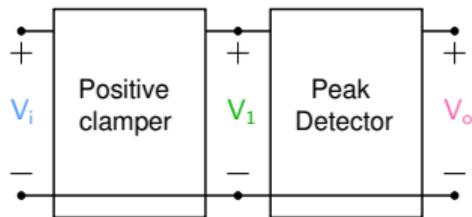


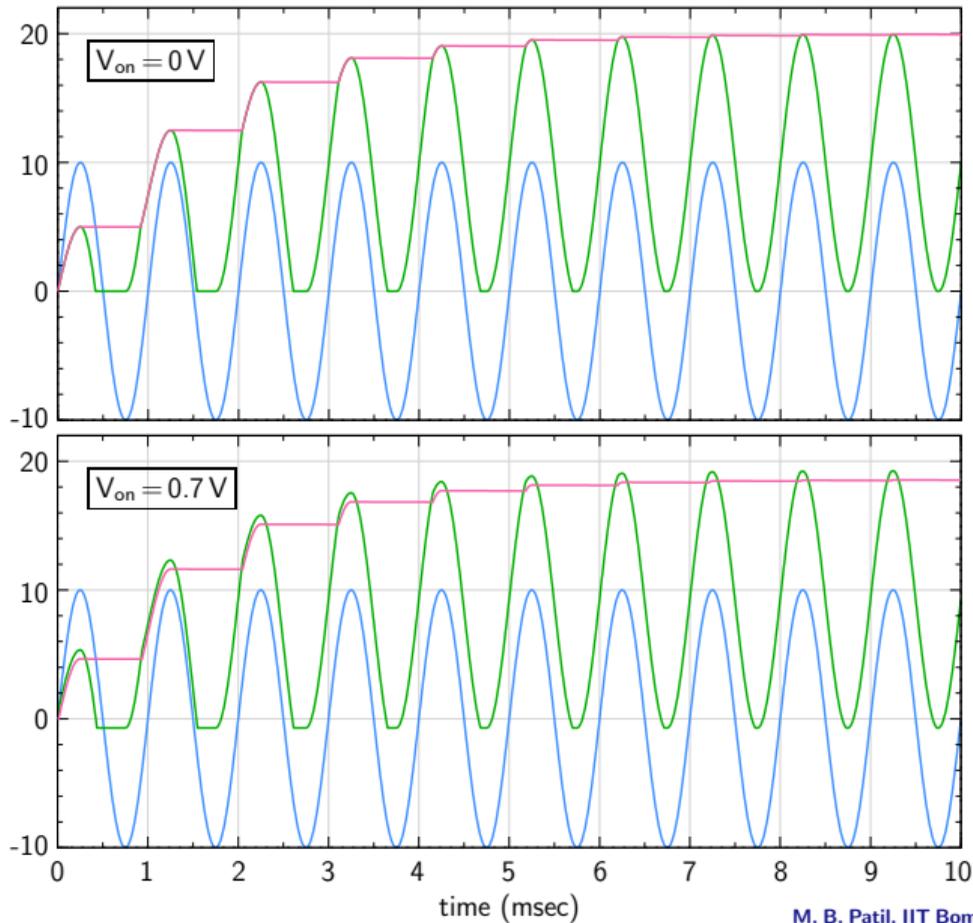
SEQUEL file: ee101_voltage_doubler.sqproj




Diode circuit example

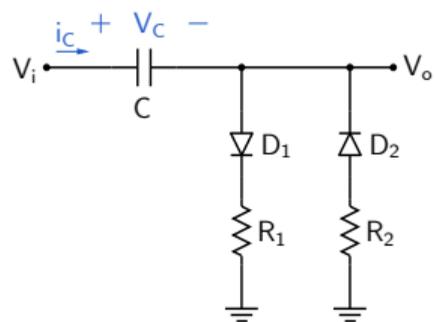

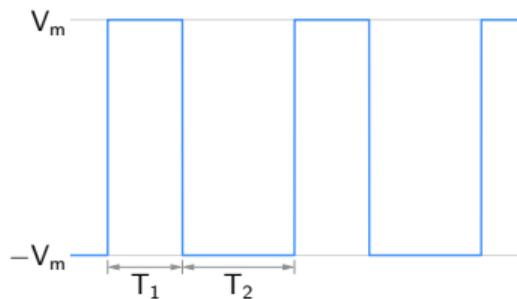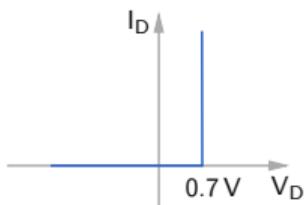Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.




Diode circuit example

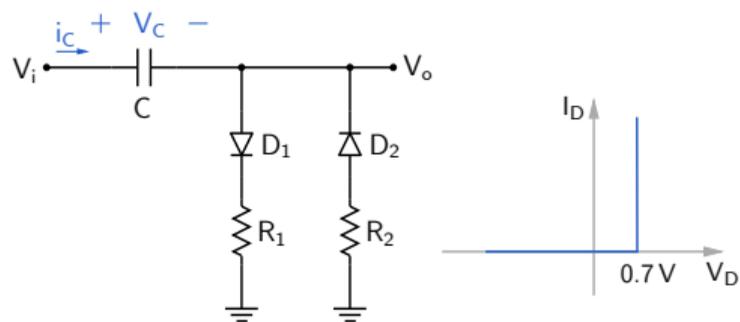


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

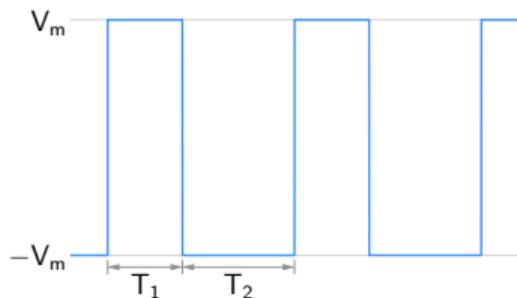* Charging time constant $\tau_1 = R_1 C$.




Diode circuit example

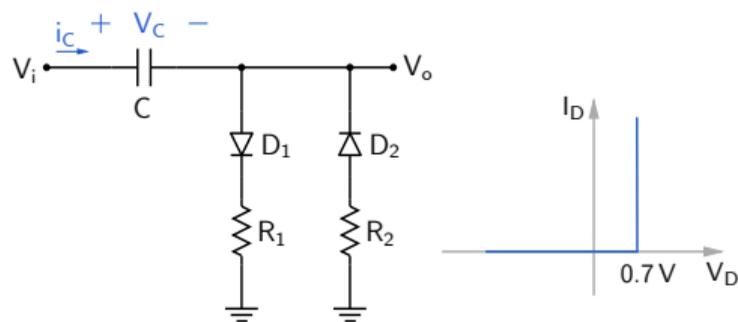


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

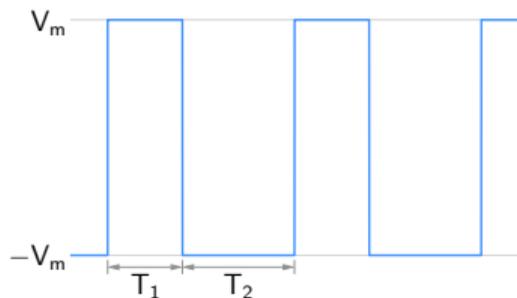- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.




Diode circuit example

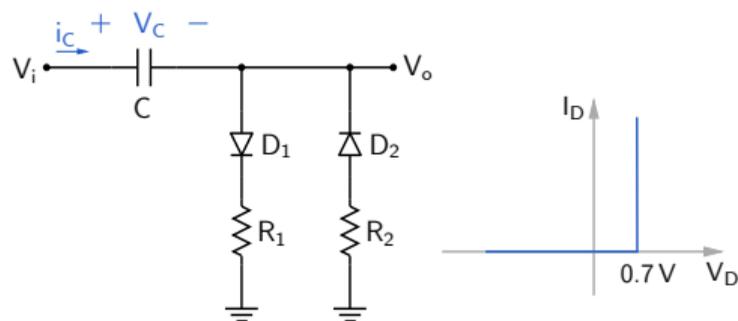


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

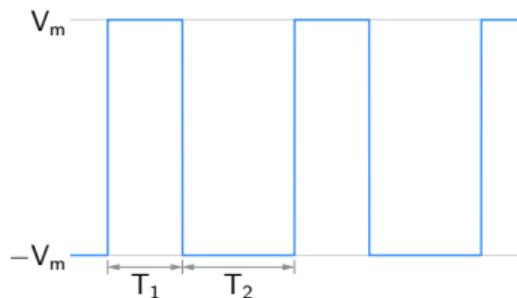- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.
- * Since $\tau_1 \gg T$ and $\tau_2 \gg T$, we expect V_C to be nearly constant in steady state, i.e., $V_C(t) \approx \text{constant} \equiv V_C^0$.




Diode circuit example

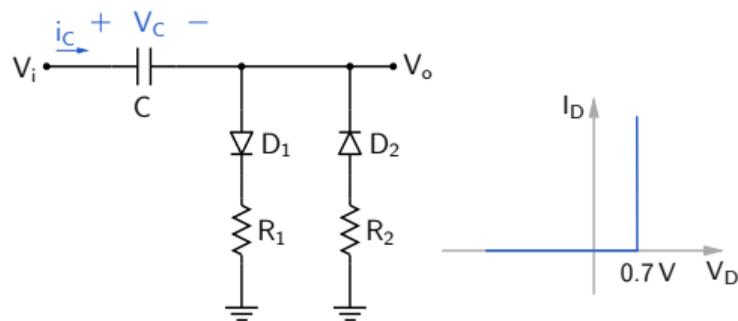


Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.

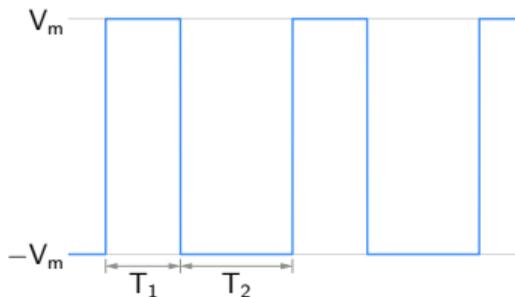- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.
- * Since $\tau_1 \gg T$ and $\tau_2 \gg T$, we expect V_C to be nearly constant in steady state, i.e., $V_C(t) \approx \text{constant} \equiv V_C^0$.
- * $V_o(t) = V_i(t) - V_C(t) \approx V_i(t) - V_C^0$.




Diode circuit example




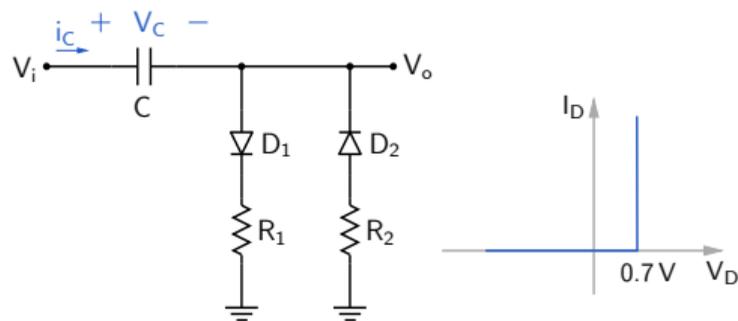







Assuming $R_1 C$ and $R_2 C$ to be large compared to T , find $V_o(t)$ in steady state.




- * Charging time constant $\tau_1 = R_1 C$.
- * Discharging time constant $\tau_2 = R_2 C$.
- * Since $\tau_1 \gg T$ and $\tau_2 \gg T$, we expect V_C to be nearly constant in steady state, i.e., $V_C(t) \approx \text{constant} \equiv V_C^0$.
- * $V_o(t) = V_i(t) - V_C(t) \approx V_i(t) - V_C^0$.

Let us look at an example.

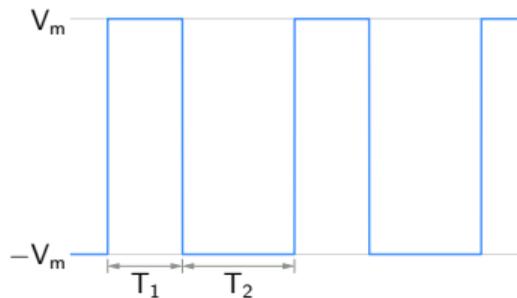


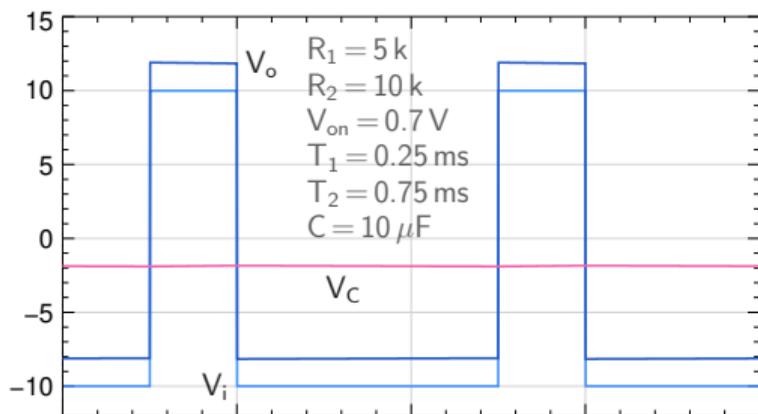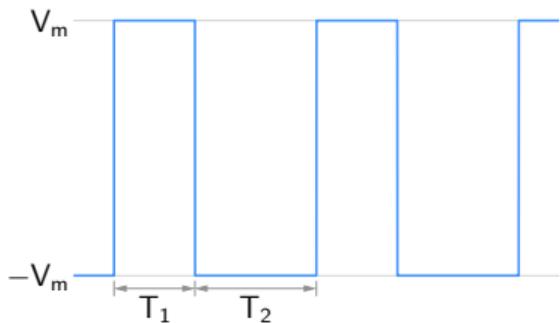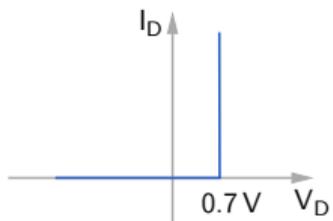
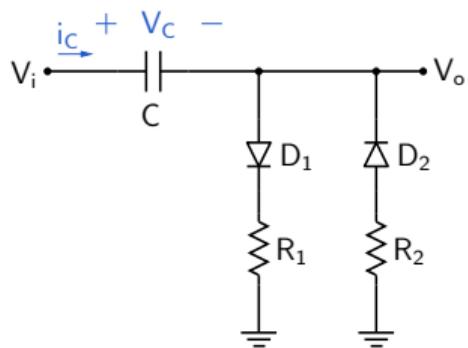


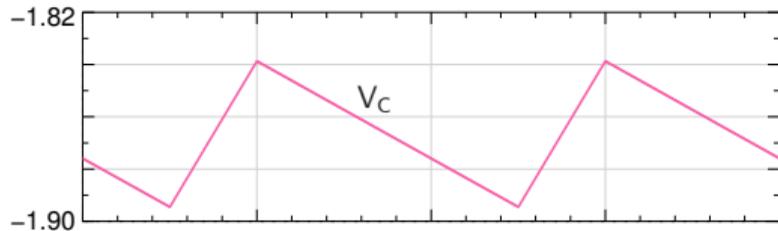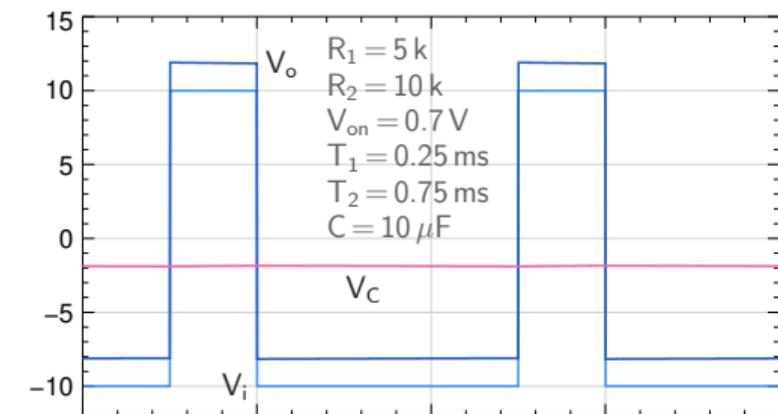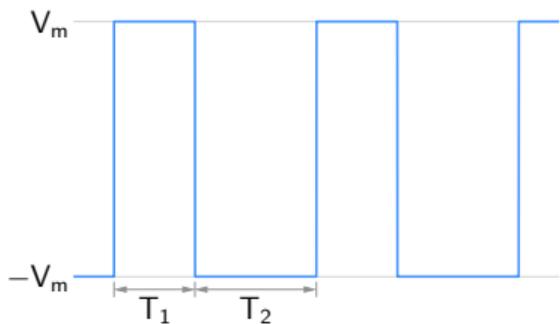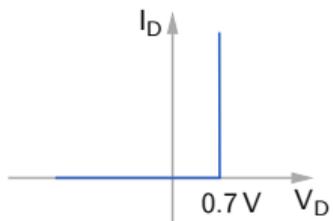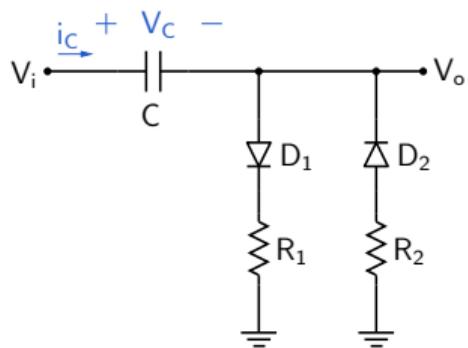

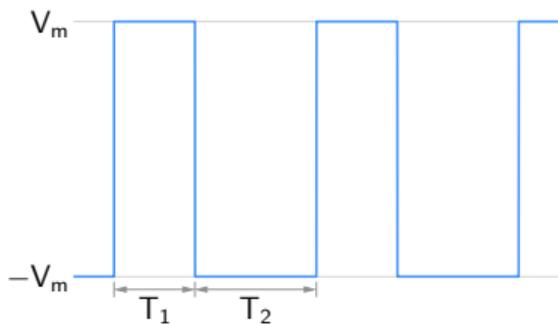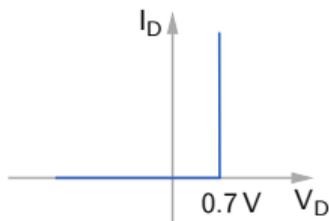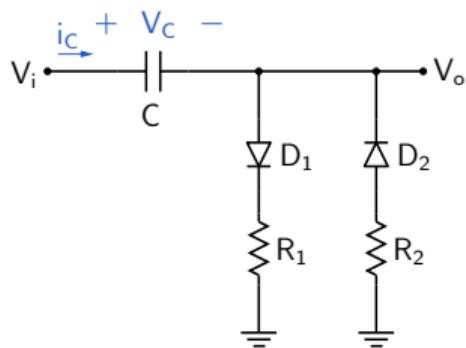



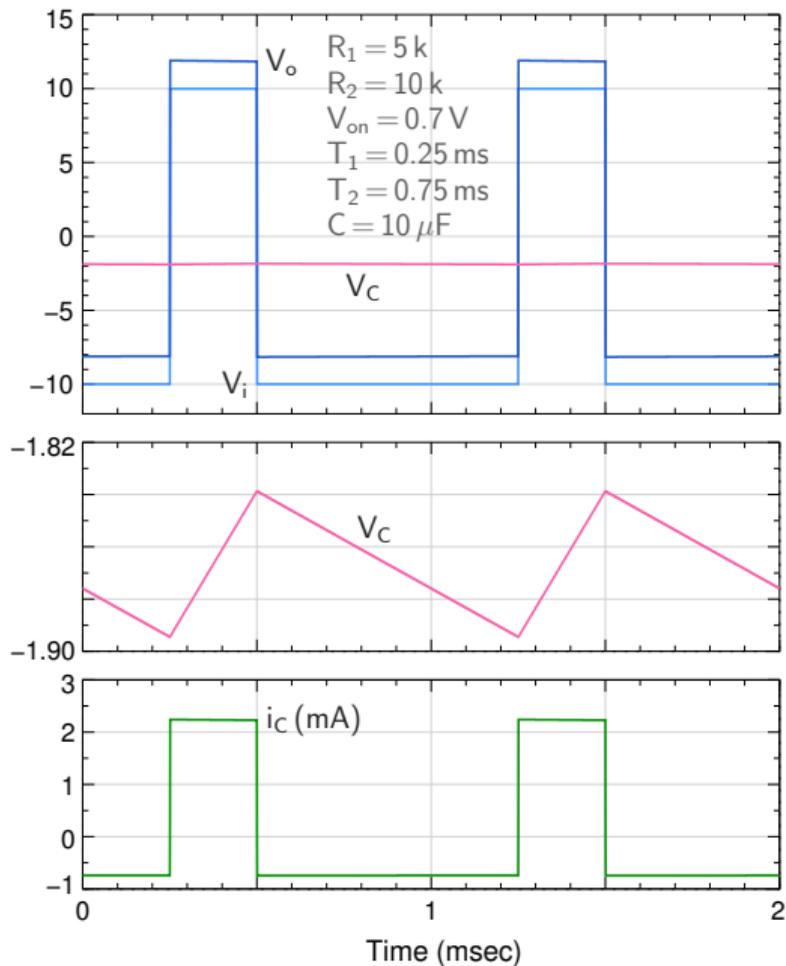
SEQUEL file:
ee101_diode_circuit_13.sqproj



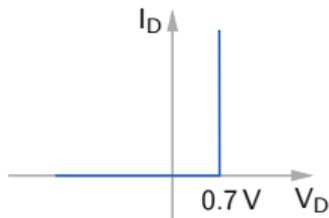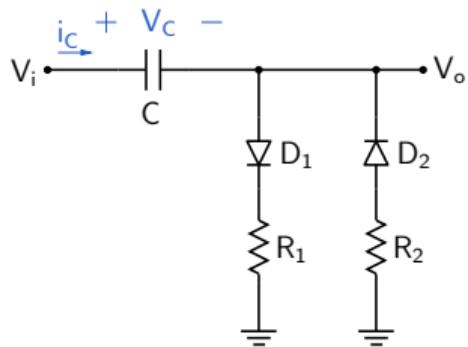


Charge conservation:


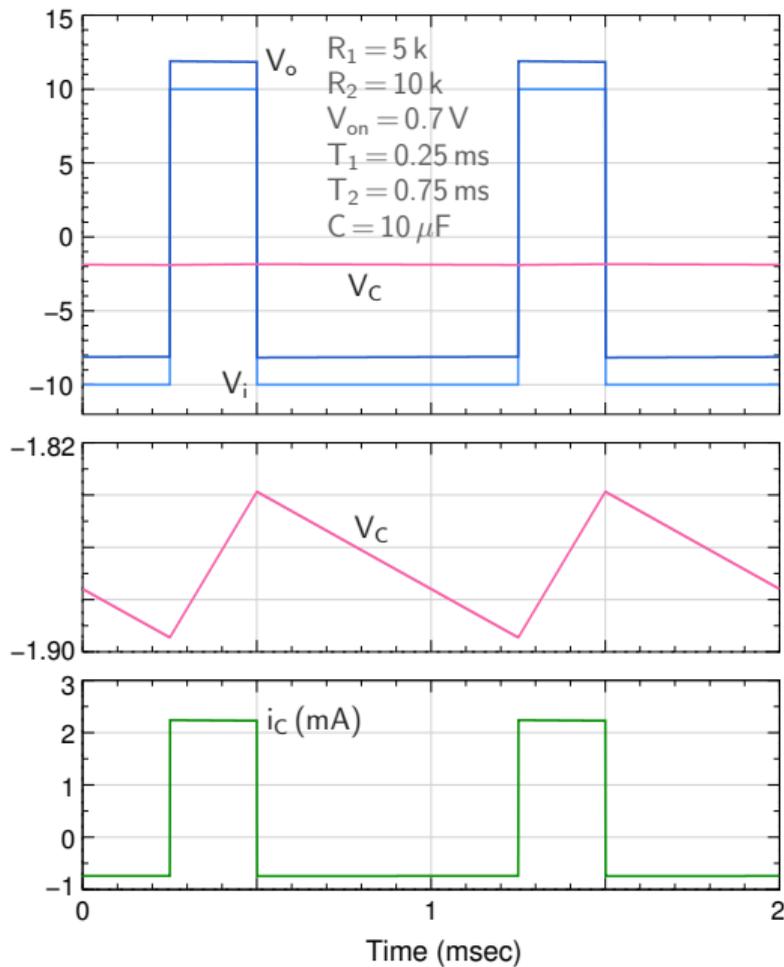


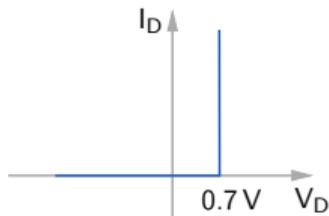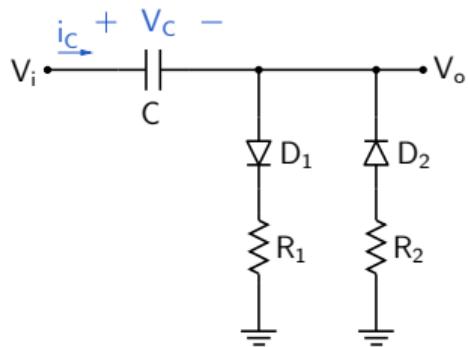

Charge conservation:
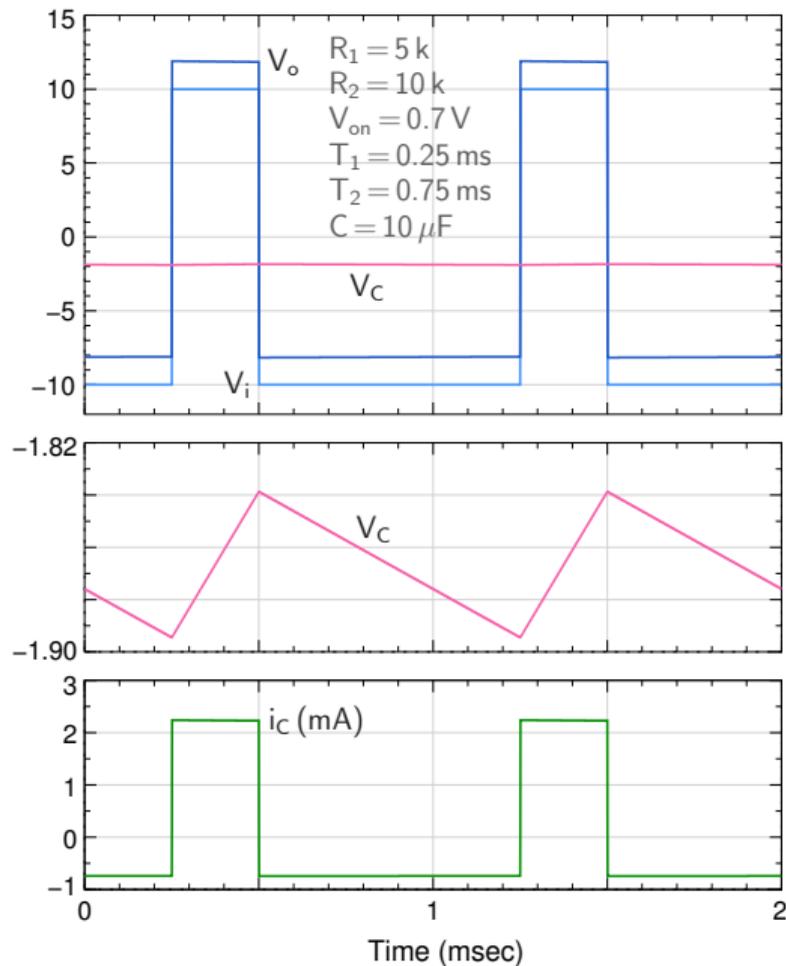
$$\Delta Q = \int_0^T i_c dt = \int_0^{T_1} i_c dt + \int_{T_1}^{T_1+T_2} i_c dt = 0.$$




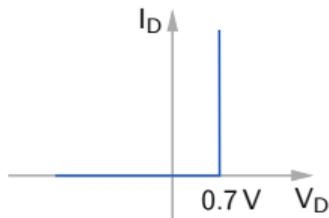
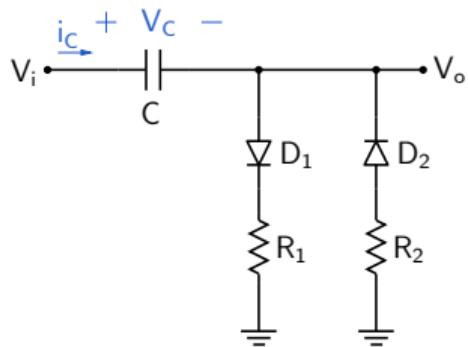


Charge conservation:

$$\Delta Q = \int_0^T i_C dt = \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0.$$
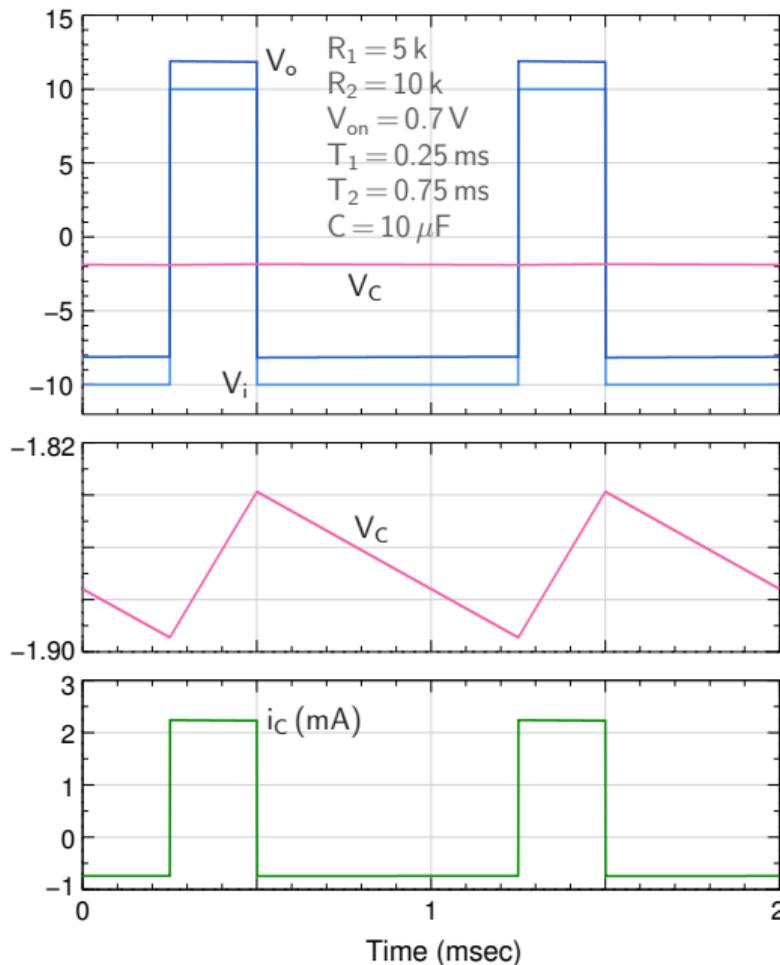
$$T_1 \left(\frac{V_m - V_C - V_{on}}{R_1} \right) - T_2 \left(\frac{0 - (-V_m - V_C) - V_{on}}{R_2} \right) = 0.$$



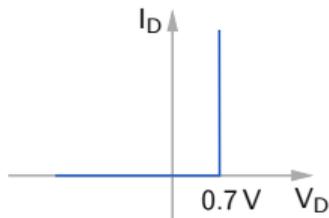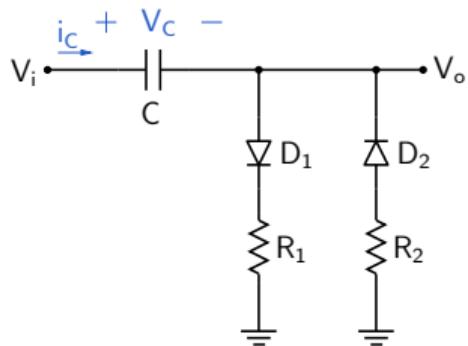





Charge conservation:

$$\Delta Q = \int_0^T i_C dt = \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0.$$

$$T_1 \left(\frac{V_m - V_C - V_{on}}{R_1} \right) - T_2 \left(\frac{0 - (-V_m - V_C) - V_{on}}{R_2} \right) = 0.$$
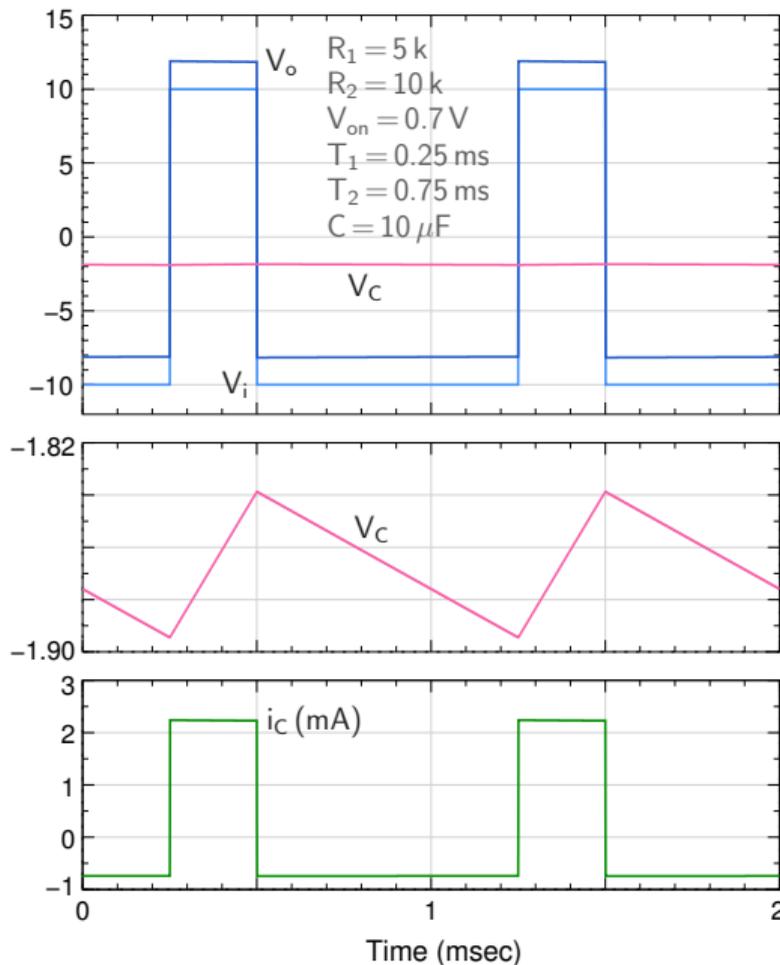
$$\left(\frac{T_1}{R_1} - \frac{T_2}{R_2} \right) (V_m - V_{on}) = V_C \left(\frac{T_1}{R_1} + \frac{T_2}{R_2} \right).$$



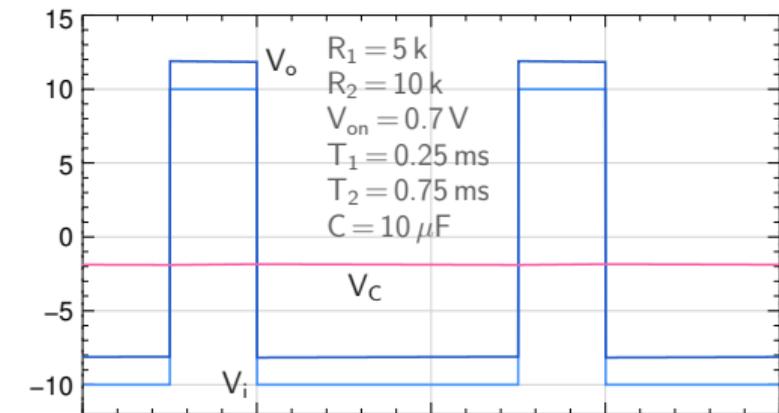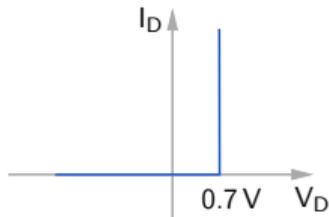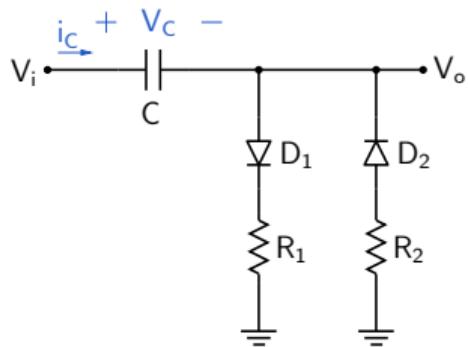



Charge conservation:

$$\Delta Q = \int_0^T i_C dt = \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0.$$

$$T_1 \left(\frac{V_m - V_C - V_{on}}{R_1} \right) - T_2 \left(\frac{0 - (-V_m - V_C) - V_{on}}{R_2} \right) = 0.$$

$$\left(\frac{T_1}{R_1} - \frac{T_2}{R_2} \right) (V_m - V_{on}) = V_C \left(\frac{T_1}{R_1} + \frac{T_2}{R_2} \right).$$

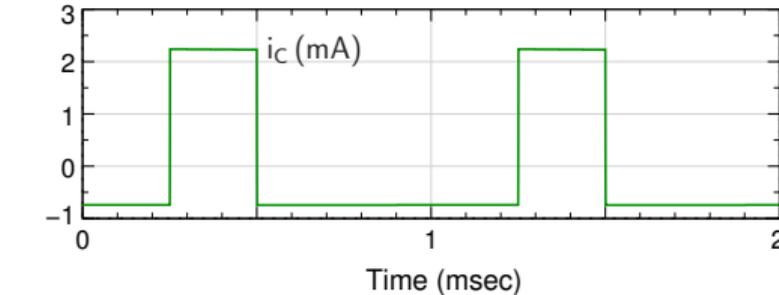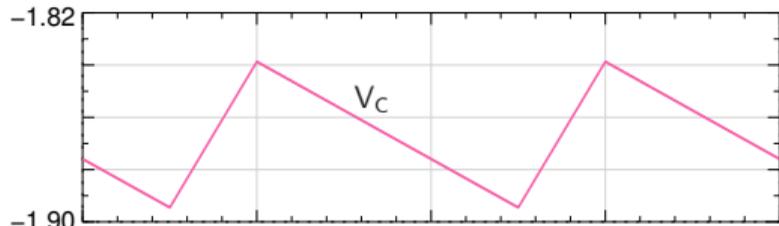
$$\rightarrow V_C = \frac{\left(\frac{T_1}{R_1} - \frac{T_2}{R_2} \right)}{\left(\frac{T_1}{R_1} + \frac{T_2}{R_2} \right)} (V_m - V_{on}) = -1.86 \text{ V}.$$



- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

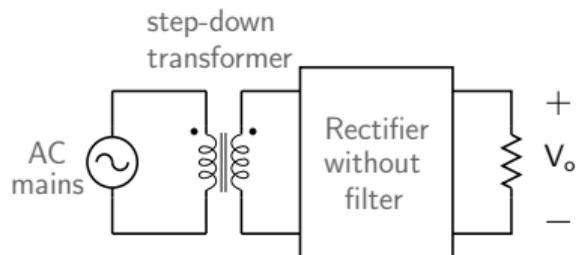


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

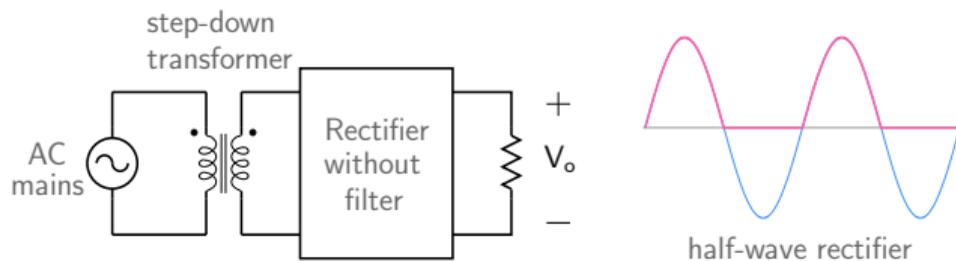



- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

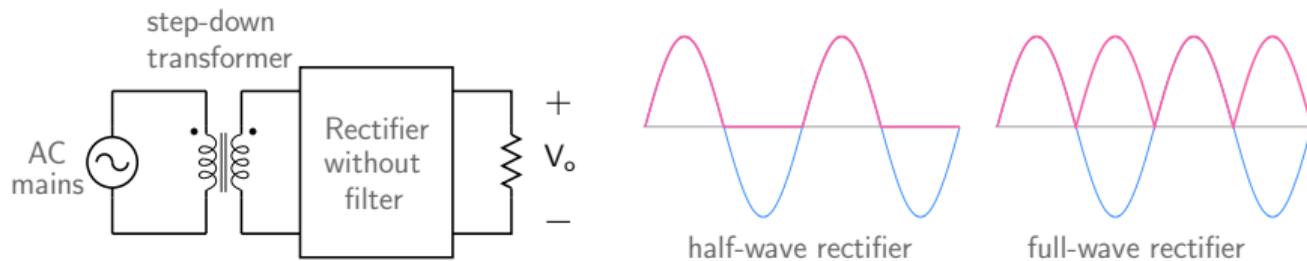



- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

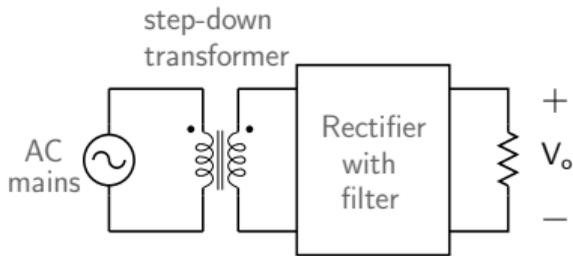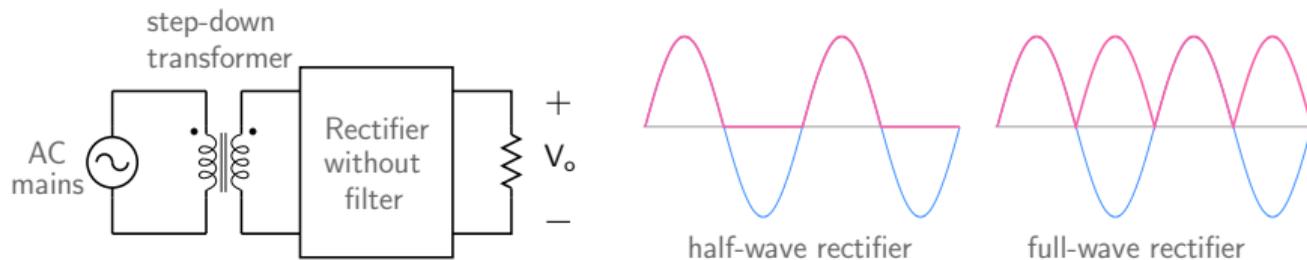


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

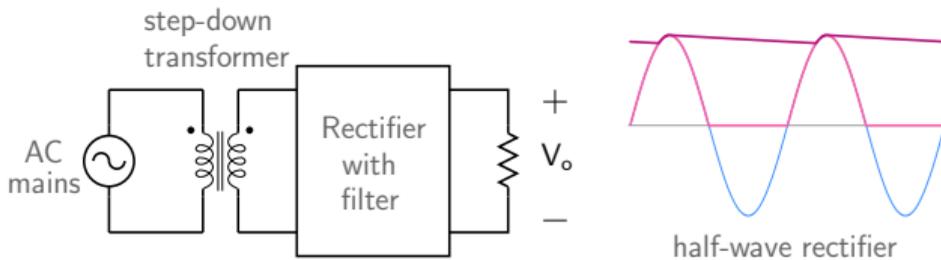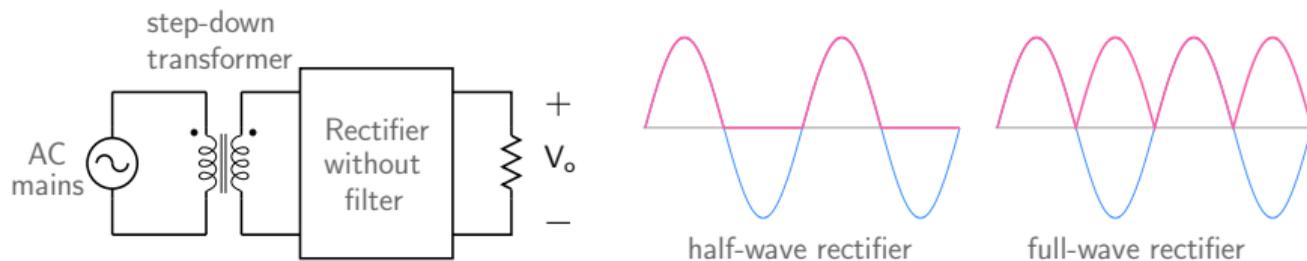


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20 V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers

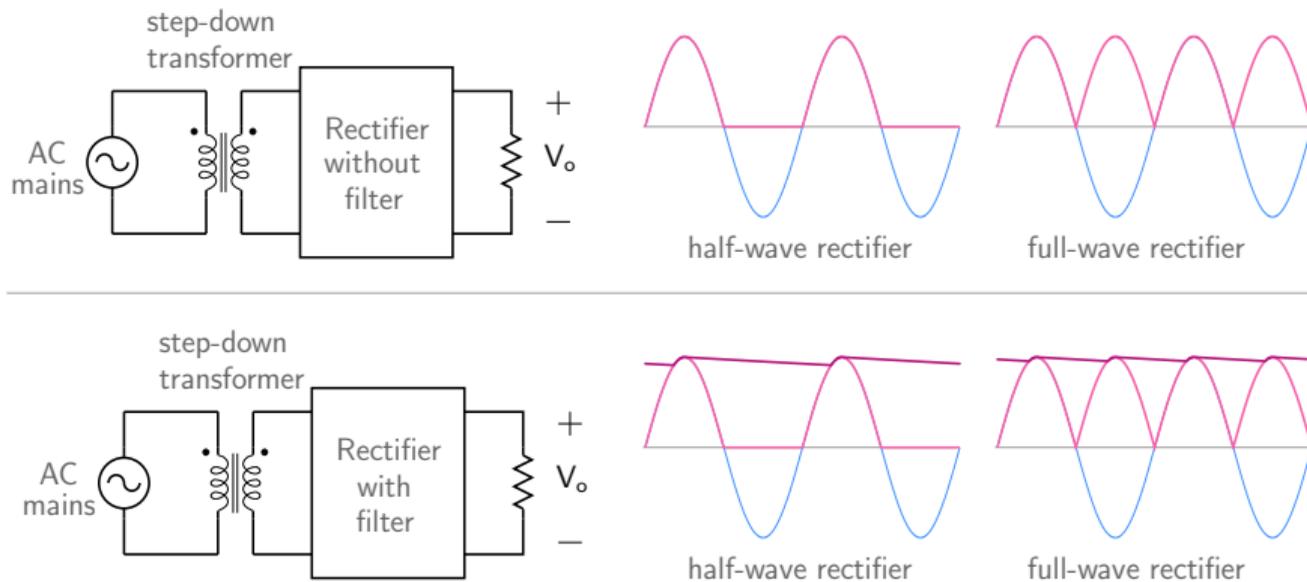




- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage

Rectifiers



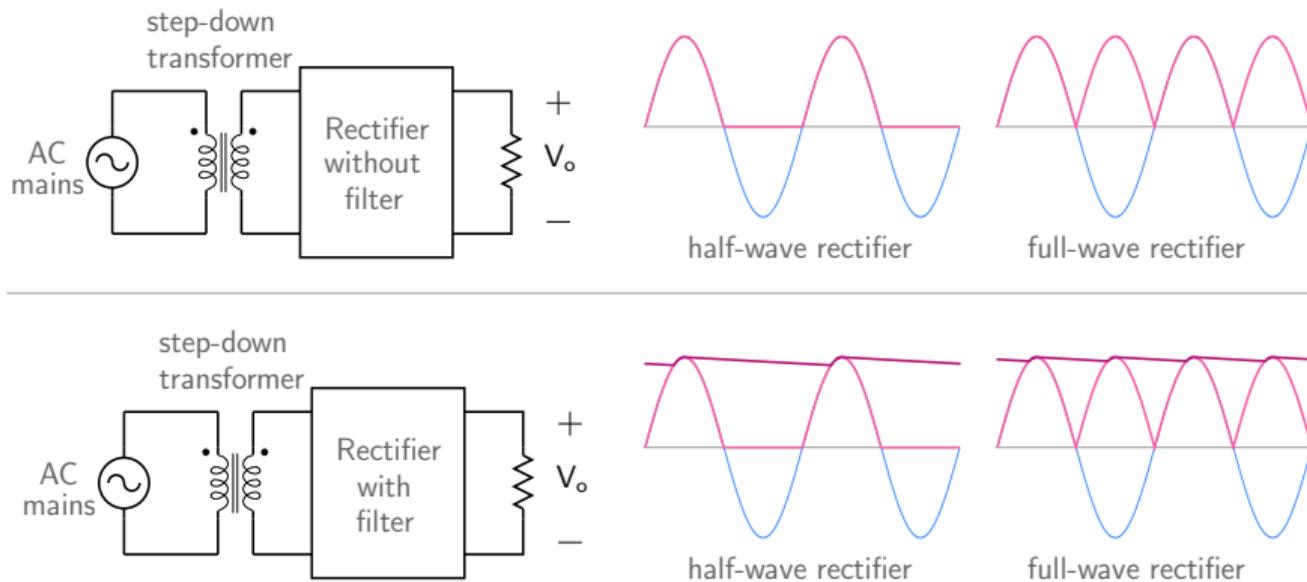


- * A rectifier is used to convert an AC voltage to a DC voltage (typically 5 to 20V), e.g., a mobile phone charger.
- * AC mains \rightarrow step-down transformer \rightarrow DC voltage OR
AC mains \rightarrow DC voltage \rightarrow lower DC voltage
- * A voltage regulator would be typically used to remove the ripple riding on the DC output.

Half-wave rectifier without filter

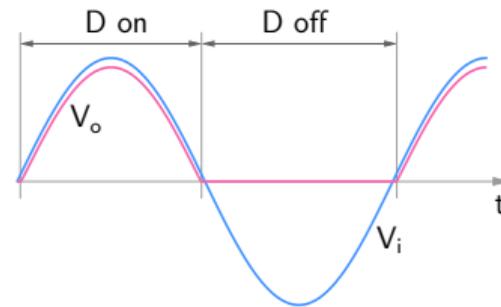
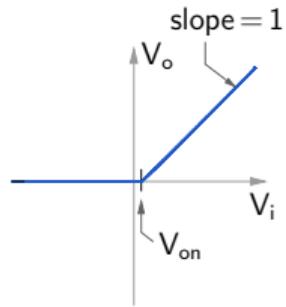
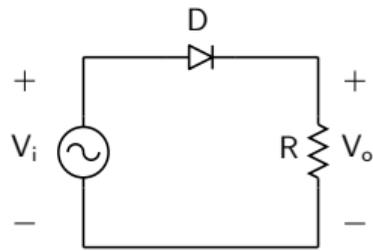


Half-wave rectifier without filter

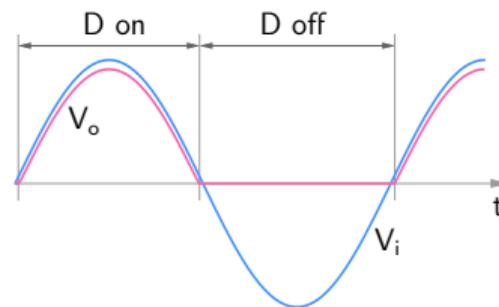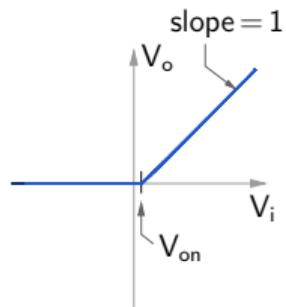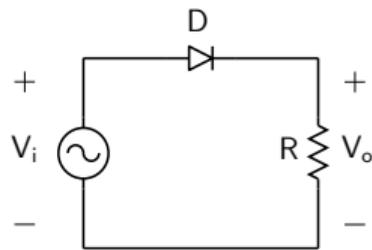


* D conducts only if $V_i > V_{on}$, and in that case $V_o = V_i - V_{on}$, a straight line with slope = 1.

Half-wave rectifier without filter

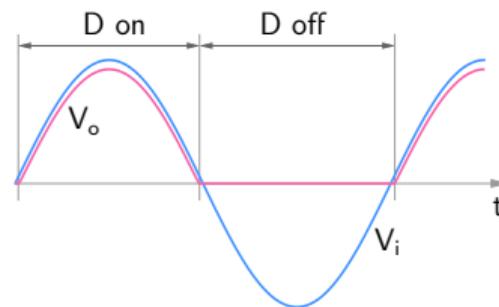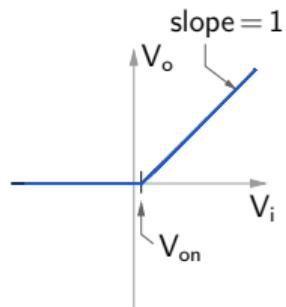
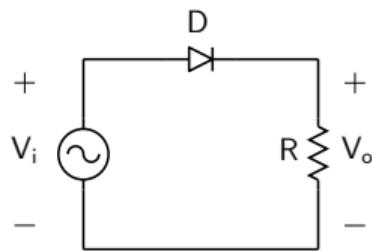


- * D conducts only if $V_i > V_{on}$, and in that case $V_o = V_i - V_{on}$, a straight line with slope = 1.
- * If $V_i < V_{on}$, D does not conduct $\rightarrow V_o = 0$.


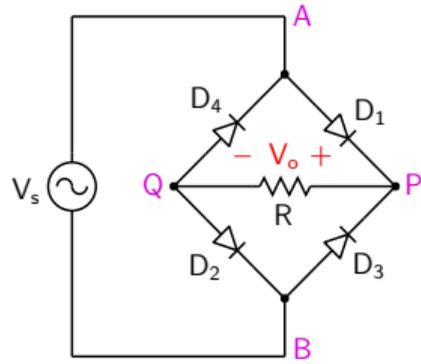
Full-wave (bridge) rectifier without filter




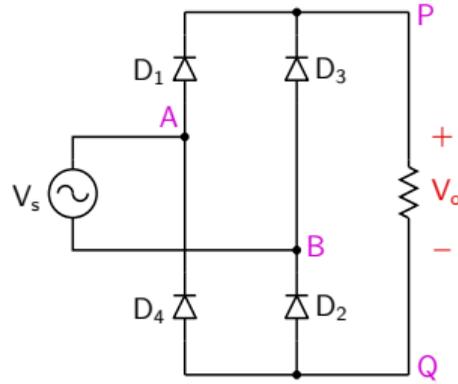
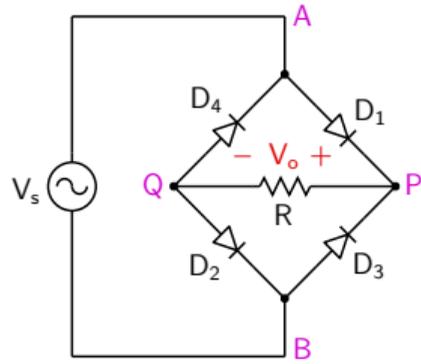
Full-wave (bridge) rectifier without filter





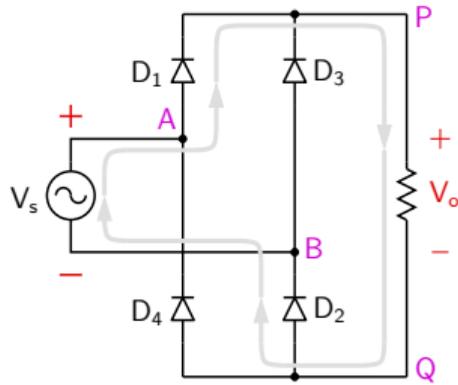
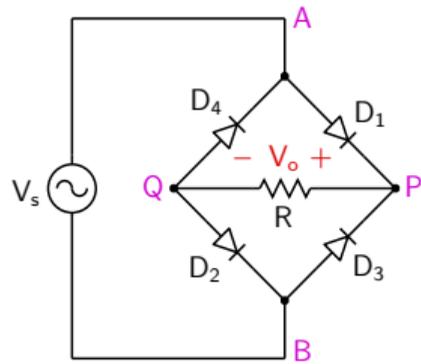
Full-wave (bridge) rectifier without filter



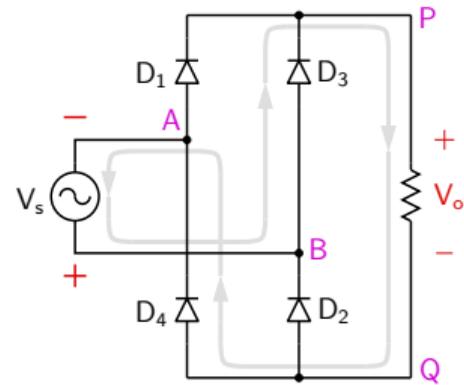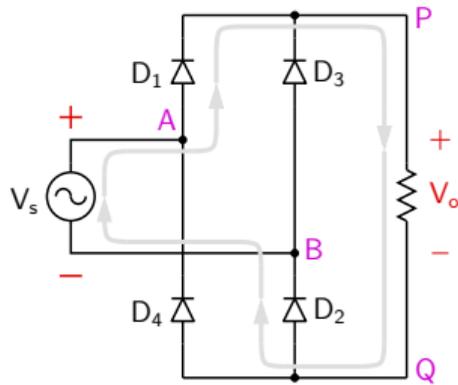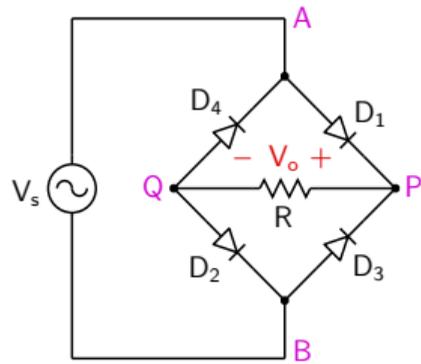
Full-wave (bridge) rectifier without filter



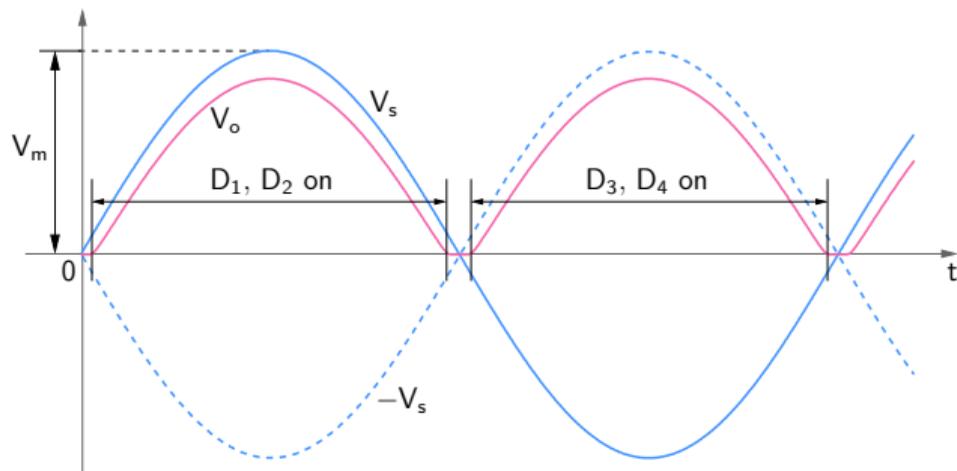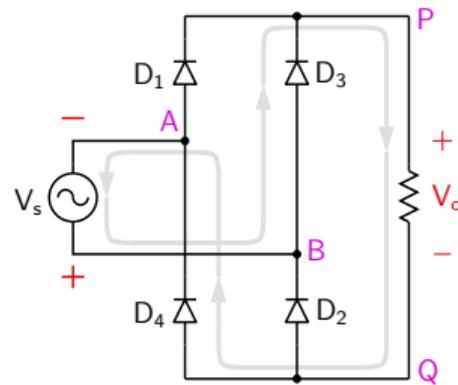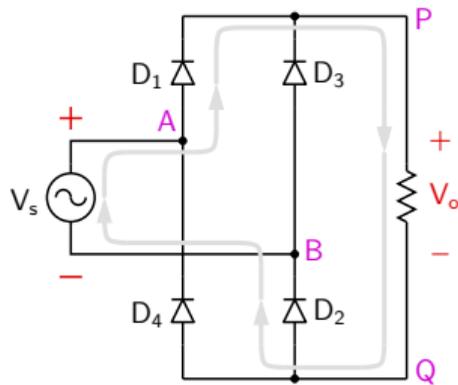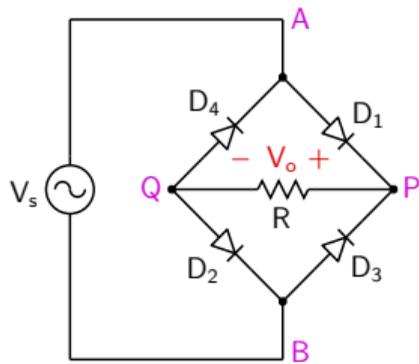
Full-wave (bridge) rectifier without filter



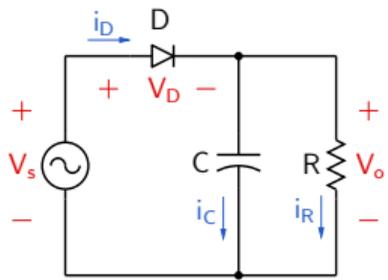Half-wave rectifier with capacitor filter




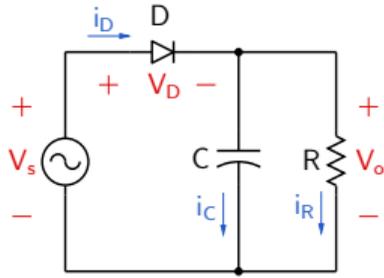Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.

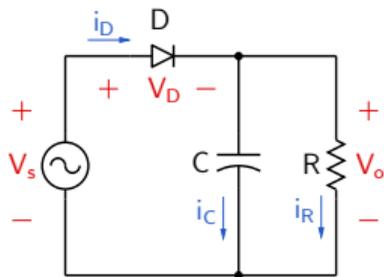
Half-wave rectifier with capacitor filter



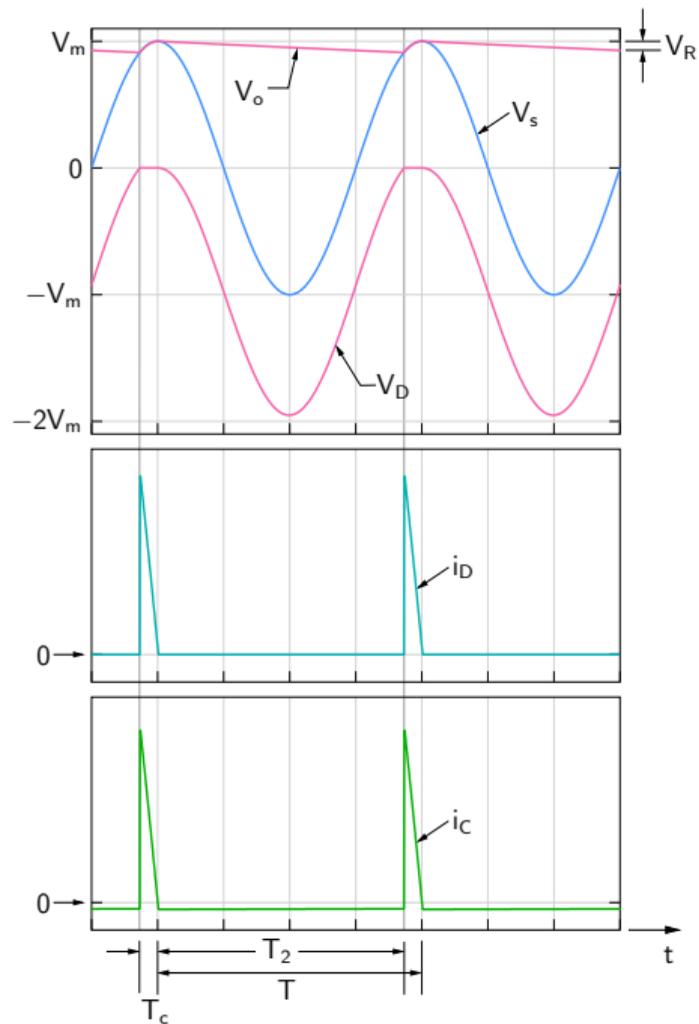
- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.



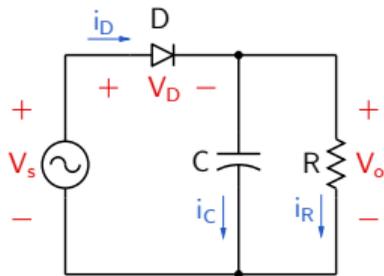
Half-wave rectifier with capacitor filter



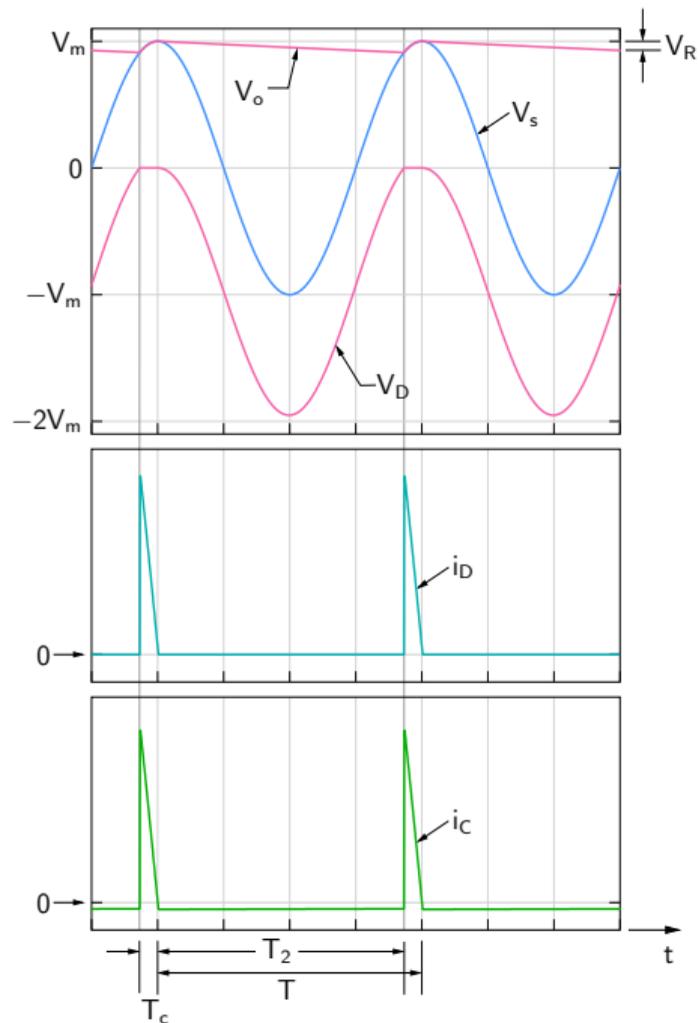
- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"



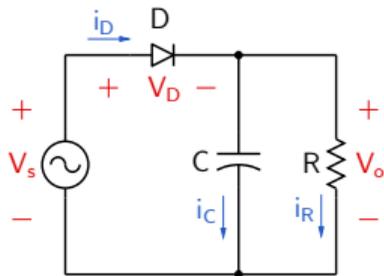
Half-wave rectifier with capacitor filter



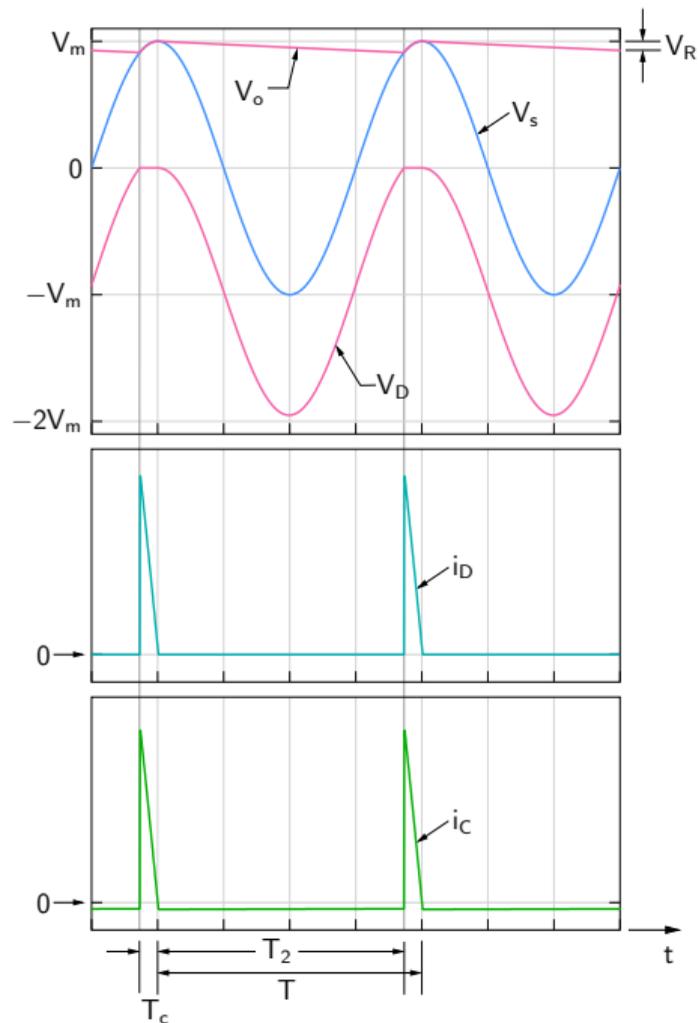
- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.



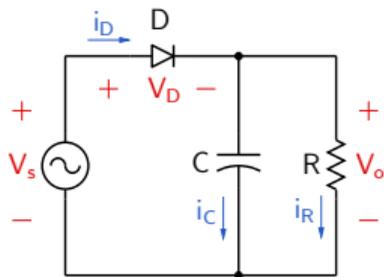
Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.
- * $V_D(t) = V_s(t) - V_o(t) \approx V_s(t) - V_m$
 \rightarrow The maximum reverse bias ("Peak Inverse Voltage" or PIV) across the diode is $2V_m$.

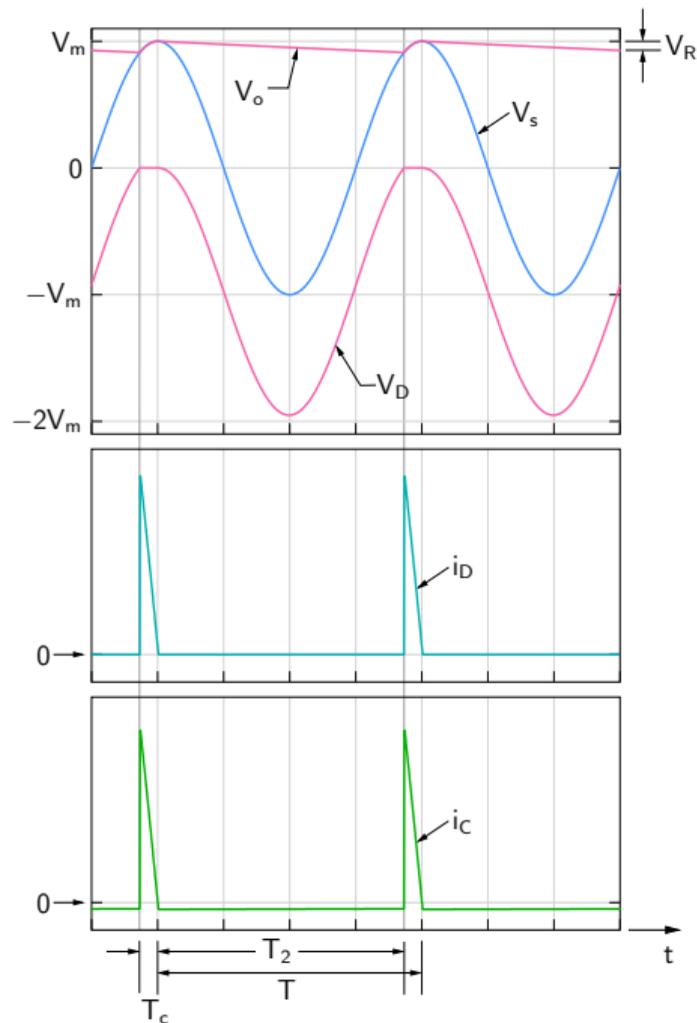

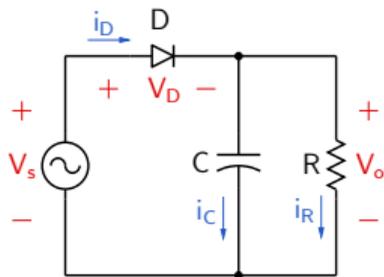
Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.
- * $V_D(t) = V_s(t) - V_o(t) \approx V_s(t) - V_m$
 \rightarrow The maximum reverse bias ("Peak Inverse Voltage" or PIV) across the diode is $2V_m$.
- * With $V_{on} = 0.7V$, the plots are slightly different.

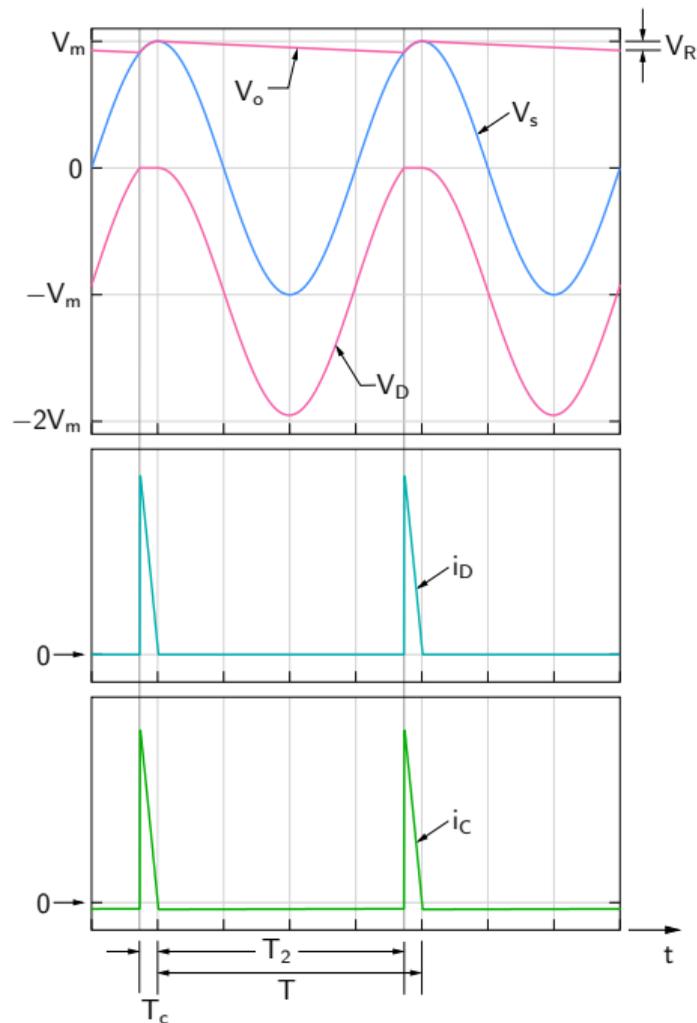

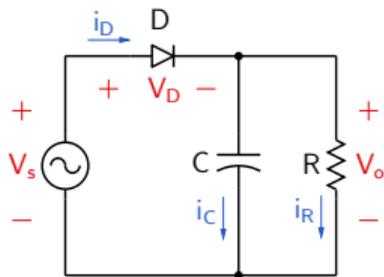
Half-wave rectifier with capacitor filter




- * Similar to the peak detector except that the load resistance provides a discharge path for the capacitor in this case.
- * Because of the load current i_R , there is a drop in the output voltage \rightarrow "ripple"
- * The peak diode current is much larger than the average load current.
- * $V_D(t) = V_s(t) - V_o(t) \approx V_s(t) - V_m$
 \rightarrow The maximum reverse bias ("Peak Inverse Voltage" or PIV) across the diode is $2V_m$.
- * With $V_{on} = 0.7V$, the plots are slightly different.

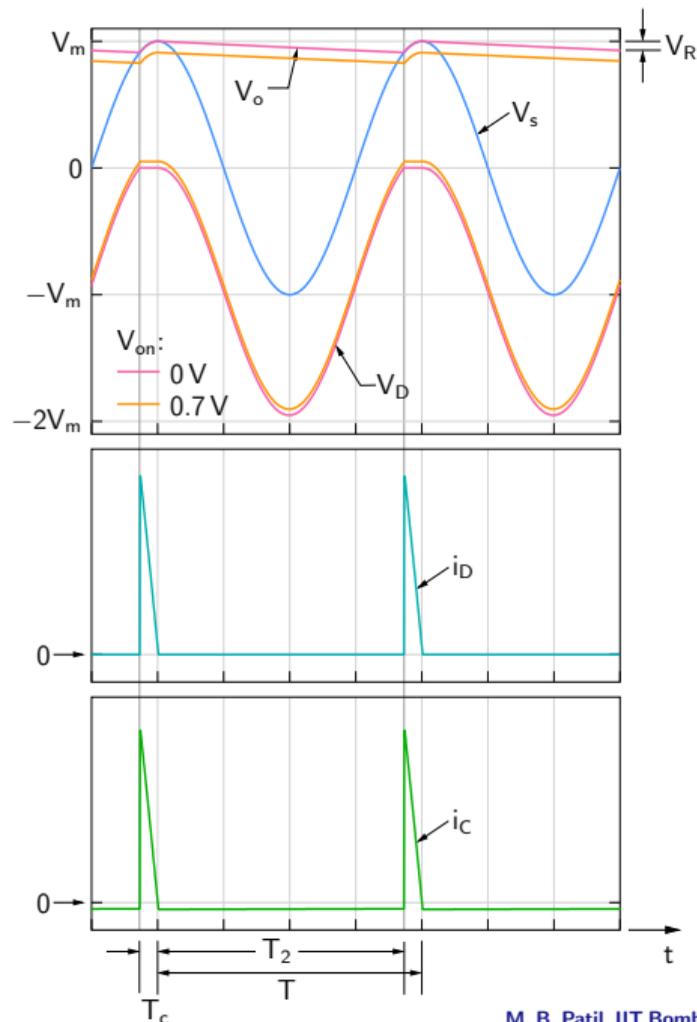

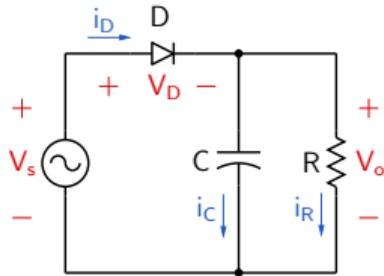
Half-wave rectifier with capacitor filter



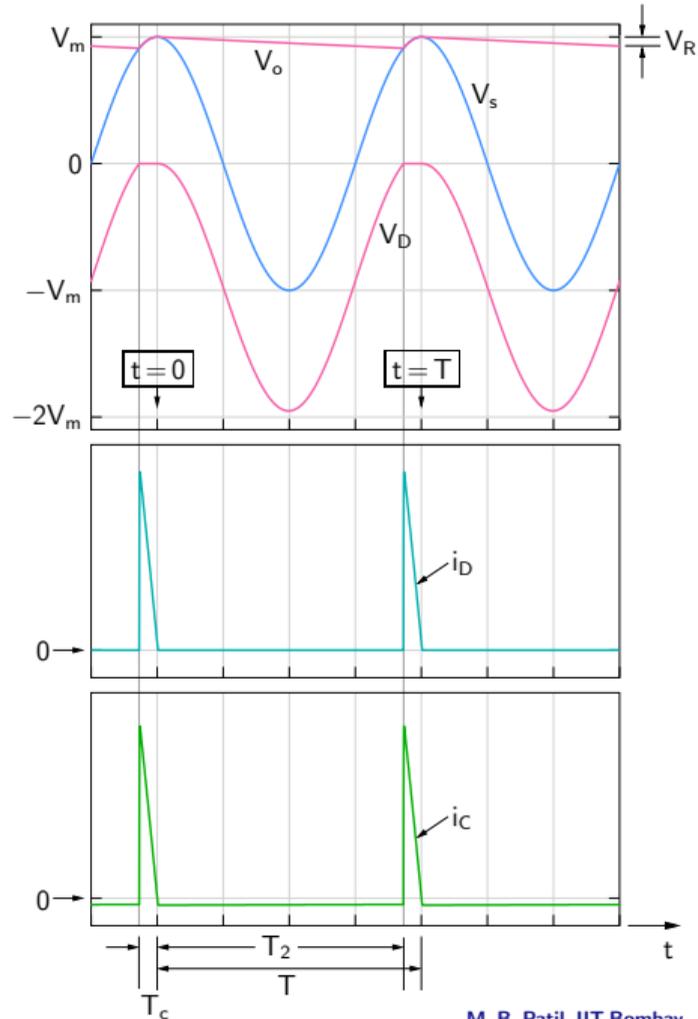$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)



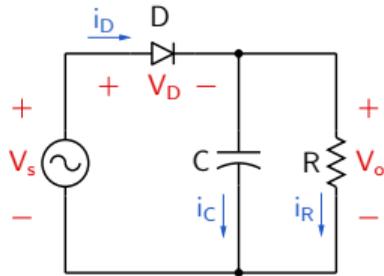Half-wave rectifier with capacitor filter




$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)


(a) filter capacitance

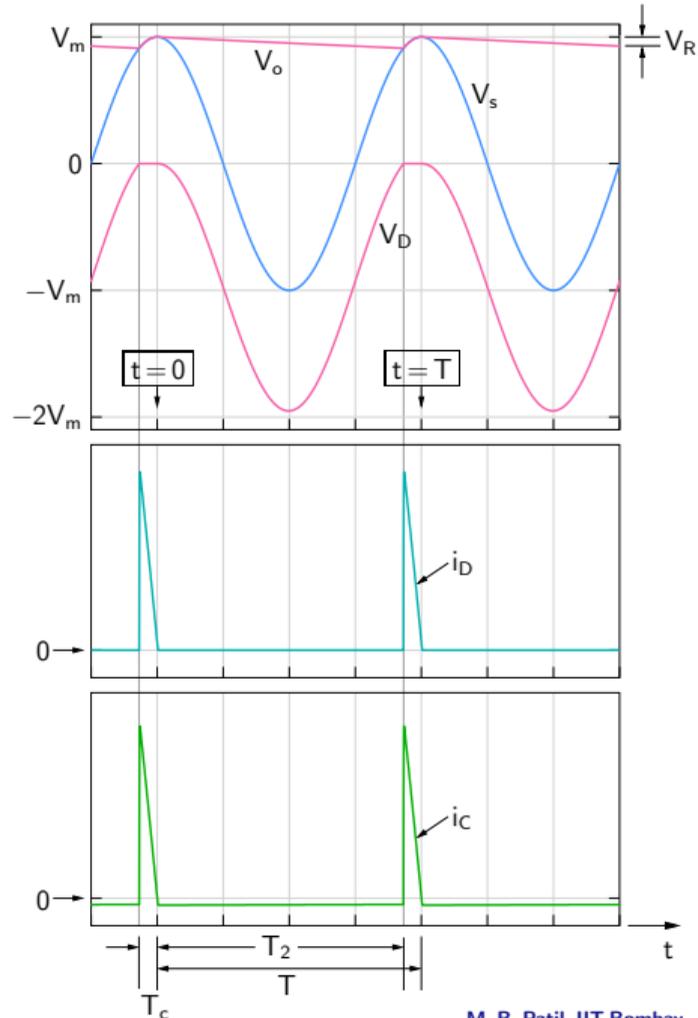1. In the discharge phase,

$$V_o(t) = V_m e^{-t/\tau} \approx V_m \left(1 - \frac{t}{\tau}\right).$$



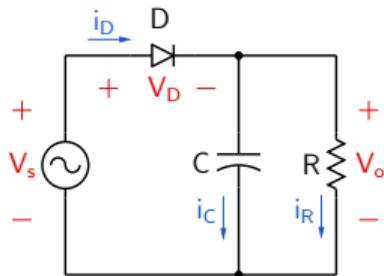Half-wave rectifier with capacitor filter



$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

(a) filter capacitance


1. In the discharge phase,

$$V_o(t) = V_m e^{-t/\tau} \approx V_m \left(1 - \frac{t}{\tau}\right).$$



The drop in $V_o(t)$ is given by the second term.

Using $T_2 \approx T$,

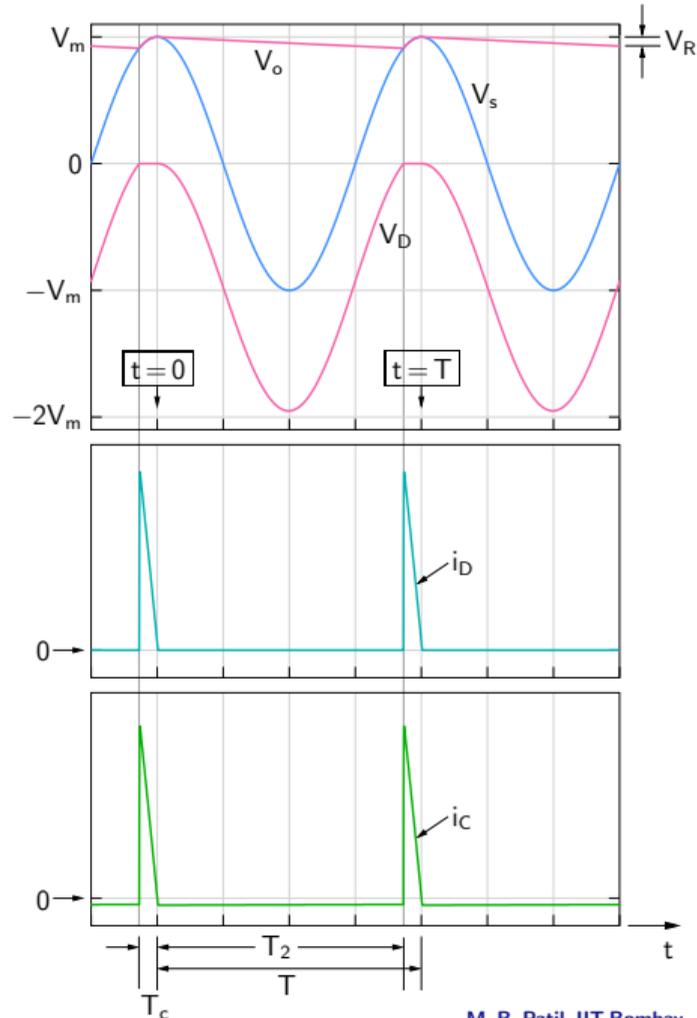
$$V_R = V_m \frac{T}{\tau} = V_m \frac{T}{RC}.$$



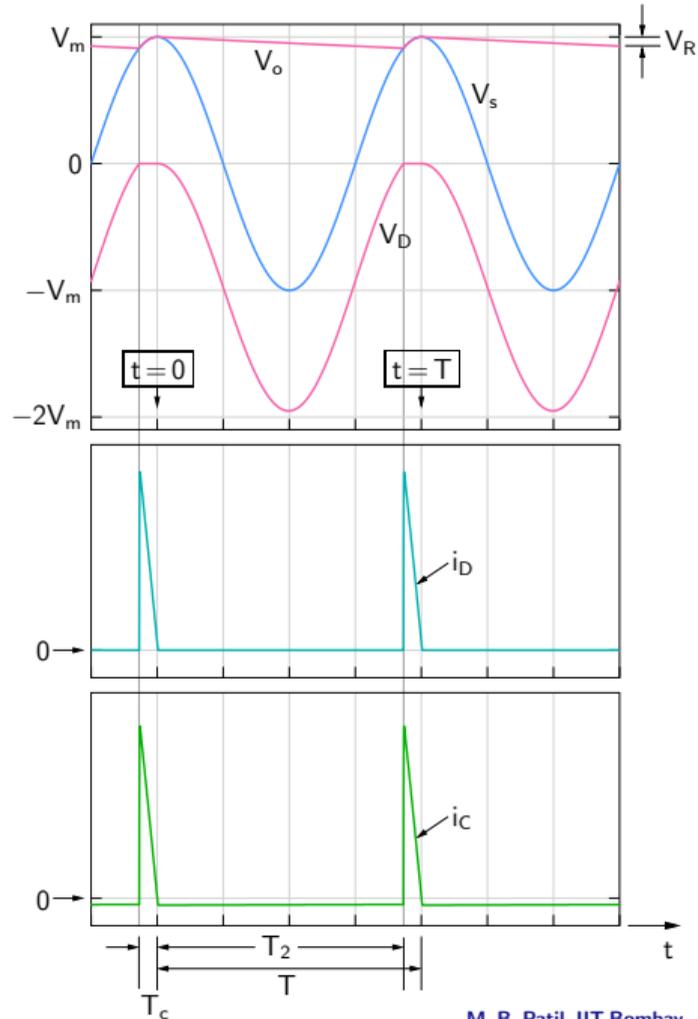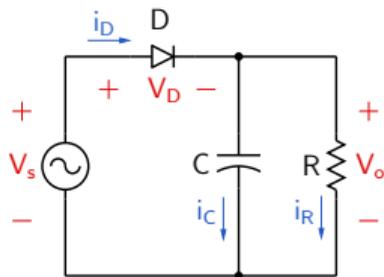Half-wave rectifier with capacitor filter



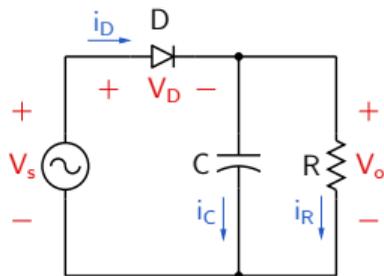
Half-wave rectifier with capacitor filter




(a) Ripple voltage V_R

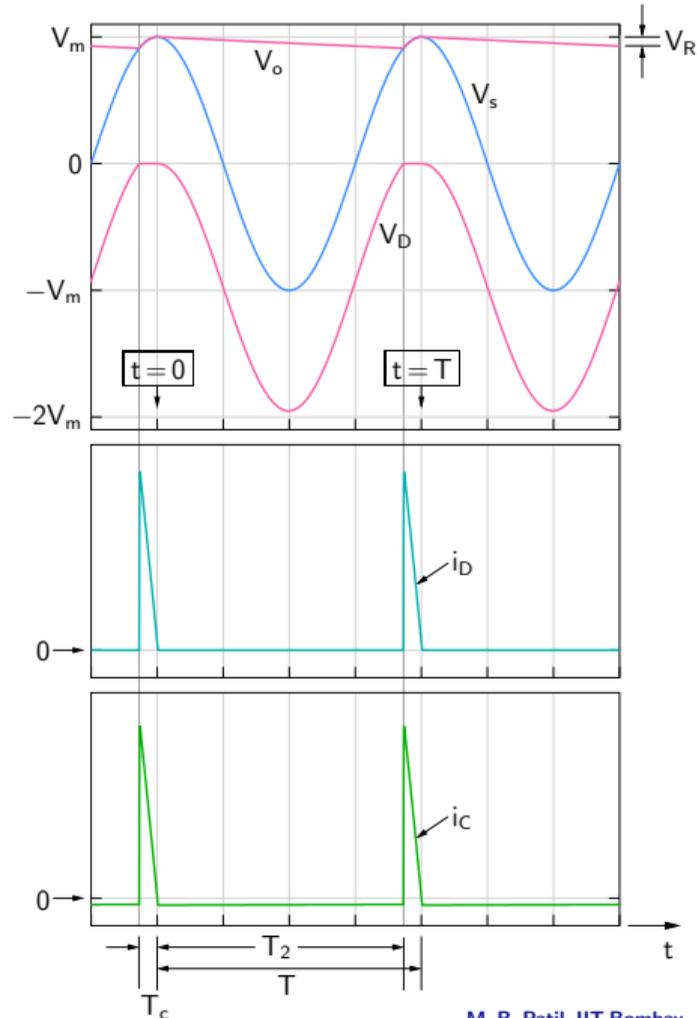2. Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T} \rightarrow V_R = V_m \frac{T}{RC}$$



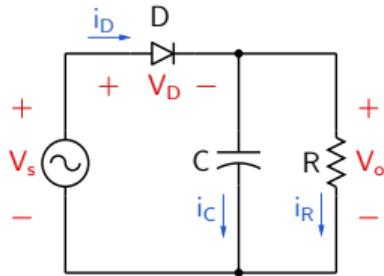Half-wave rectifier with capacitor filter




(a) Ripple voltage V_R

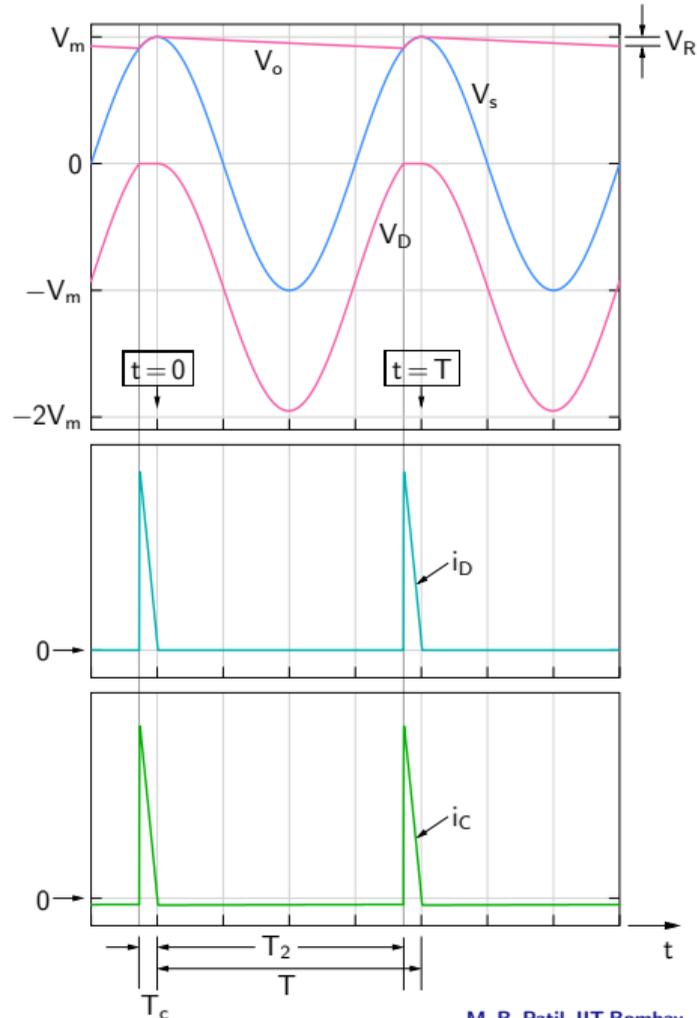
2. Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T} \rightarrow V_R = V_m \frac{T}{RC}.$$


$$\rightarrow C = \frac{V_m}{V_R} \frac{T}{R} = \frac{16\text{ V}}{2\text{ V}} \frac{20\text{ ms}}{100\ \Omega} = 1600\ \mu\text{F}.$$



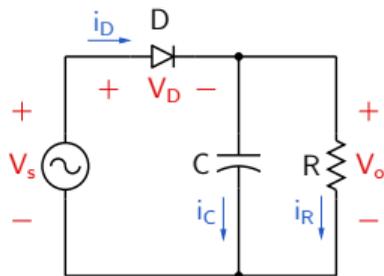
Half-wave rectifier with capacitor filter



(b) Average diode current

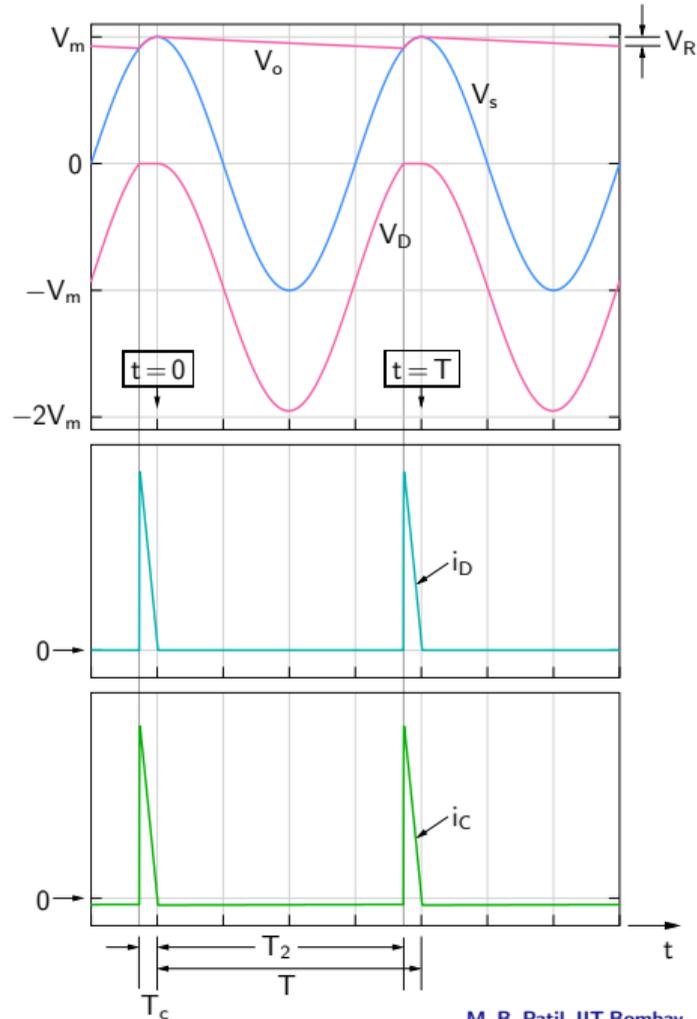

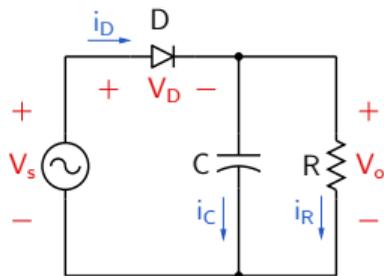
Half-wave rectifier with capacitor filter



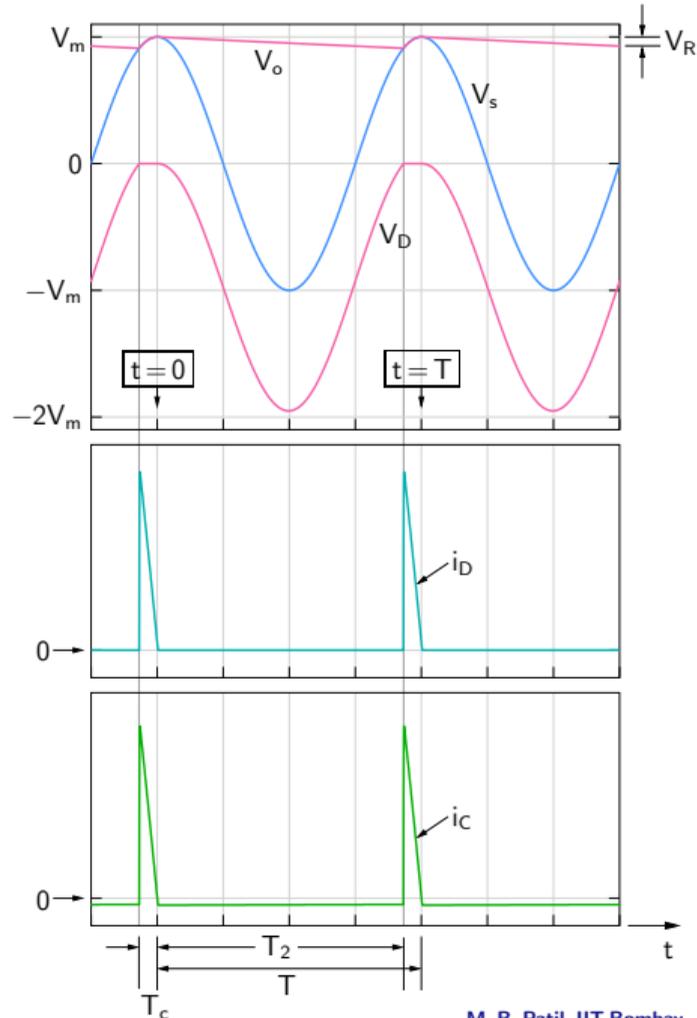
(b) Average diode current

Using charge balance,

$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$



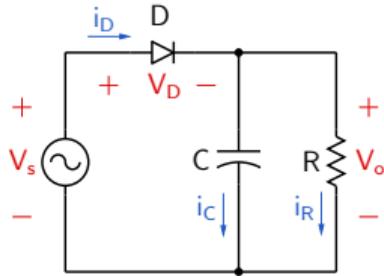Half-wave rectifier with capacitor filter




(b) Average diode current


Using charge balance,

$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$
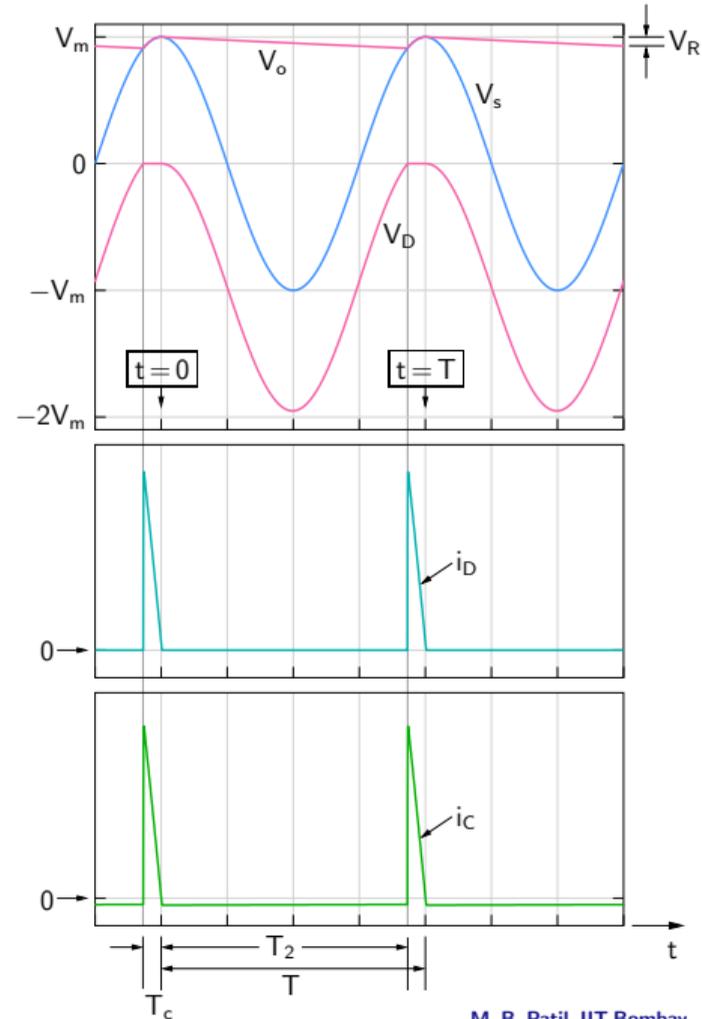
$$\rightarrow \int_{T-T_c}^T i_D dt = \int_0^T i_R dt.$$



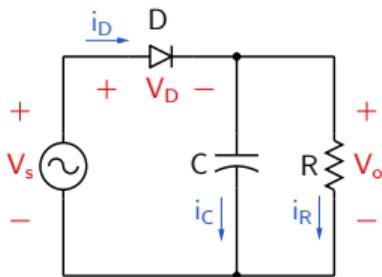Half-wave rectifier with capacitor filter



(b) Average diode current


Using charge balance,

$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$


$$\rightarrow \int_{T-T_c}^T i_D dt = \int_0^{T-T_c} i_R dt.$$

$$i_D^{av} = \frac{1}{T} \int_0^T i_D dt = \frac{1}{T} \int_{T-T_c}^T i_D dt$$
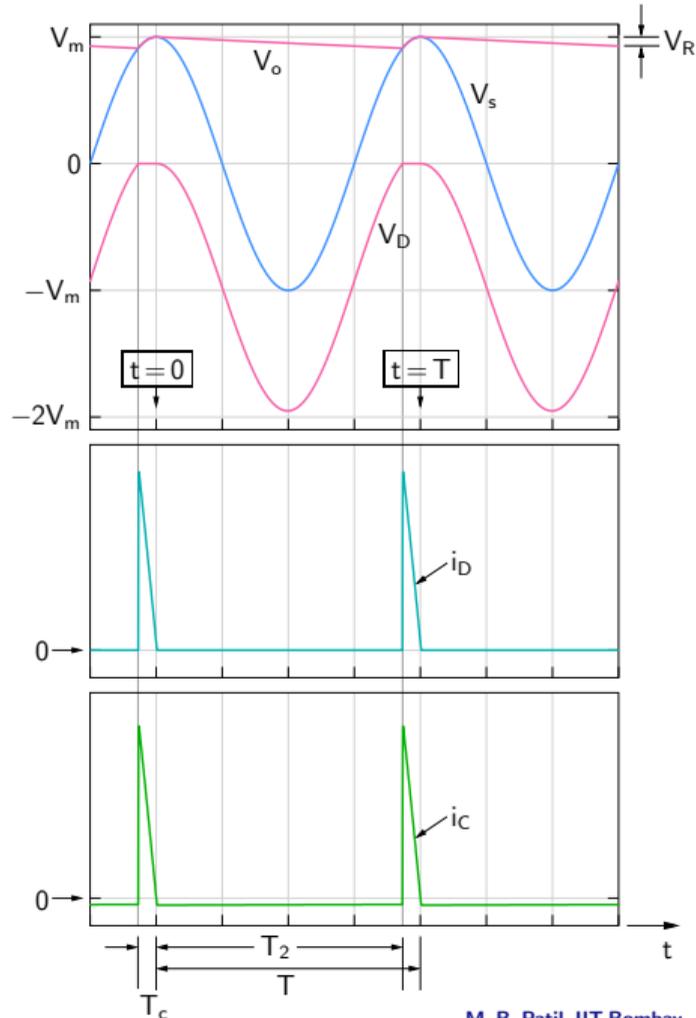
$$= \frac{1}{T} \int_0^{T-T_c} i_R dt \approx \frac{V_m}{R}.$$



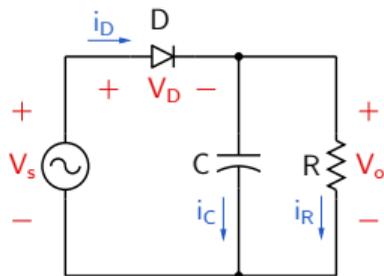Half-wave rectifier with capacitor filter



(b) Average diode current

Using charge balance,


$$\int_{T-T_c}^T (i_D - i_R) dt = \int_0^{T-T_c} i_R dt$$


$$\rightarrow \int_{T-T_c}^T i_D dt = \int_0^{T-T_c} i_R dt.$$

$$i_D^{av} = \frac{1}{T} \int_0^T i_D dt = \frac{1}{T} \int_{T-T_c}^T i_D dt$$


$$= \frac{1}{T} \int_0^{T-T_c} i_R dt \approx \frac{V_m}{R}.$$

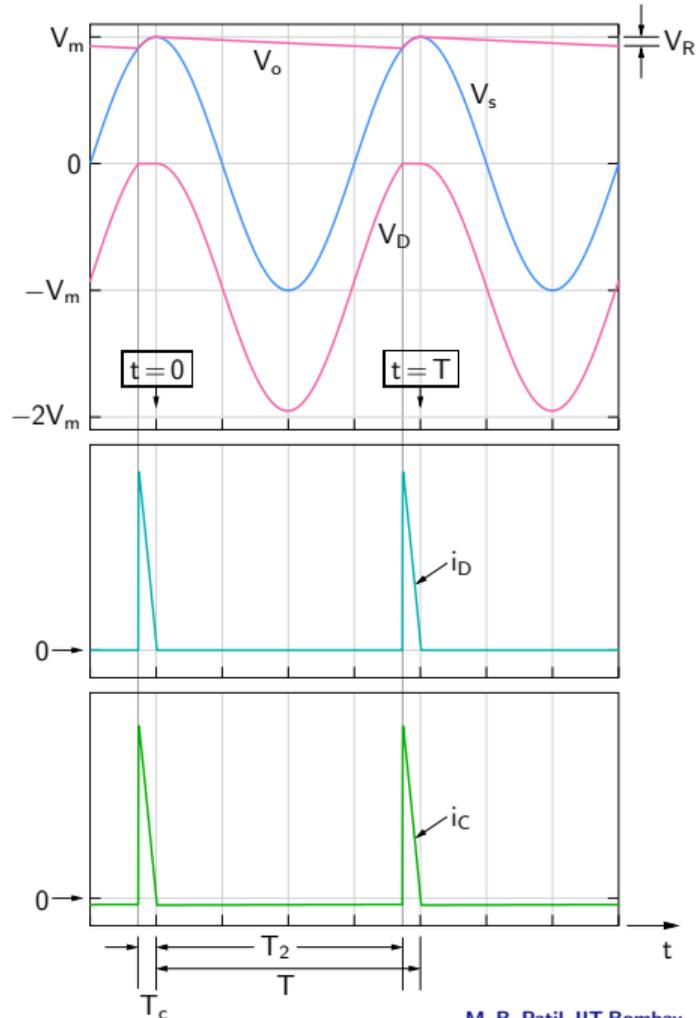
$$i_D^{av} \approx \frac{16 \text{ V}}{100 \Omega} = 160 \text{ mA}.$$



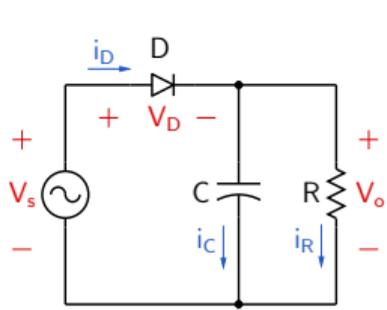


(b) Peak diode current

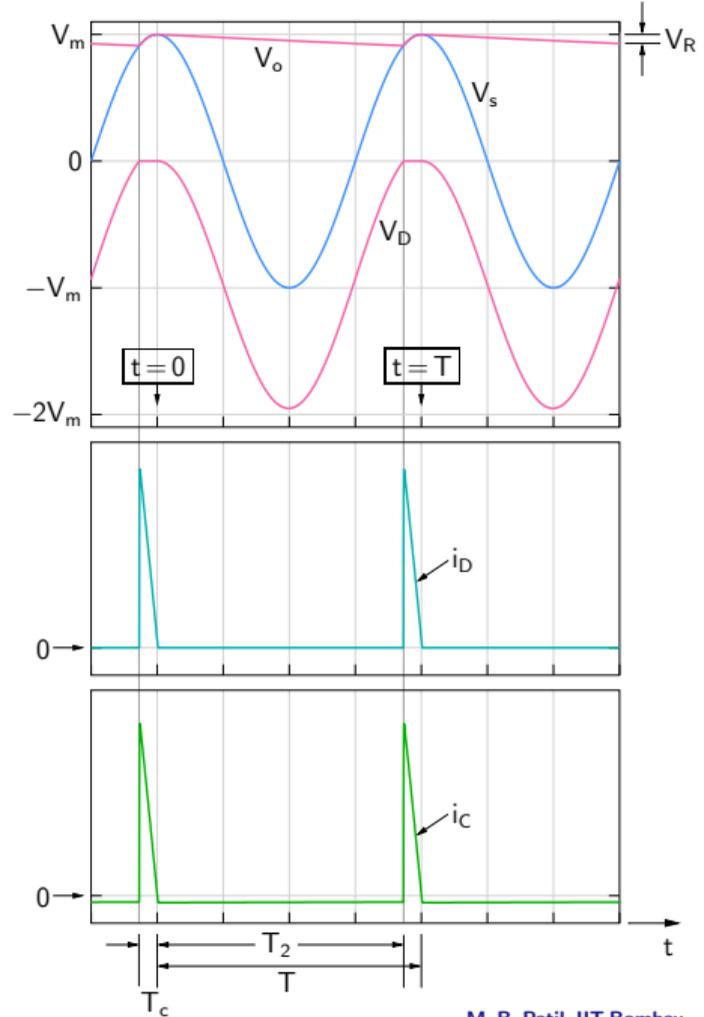


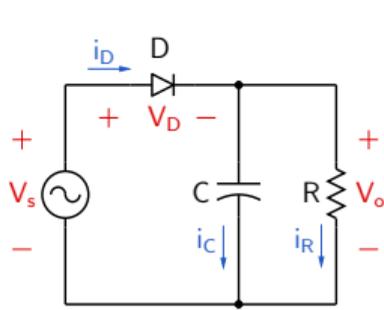

(b) Peak diode current


$$i_D^{\text{peak}} = C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R}$$

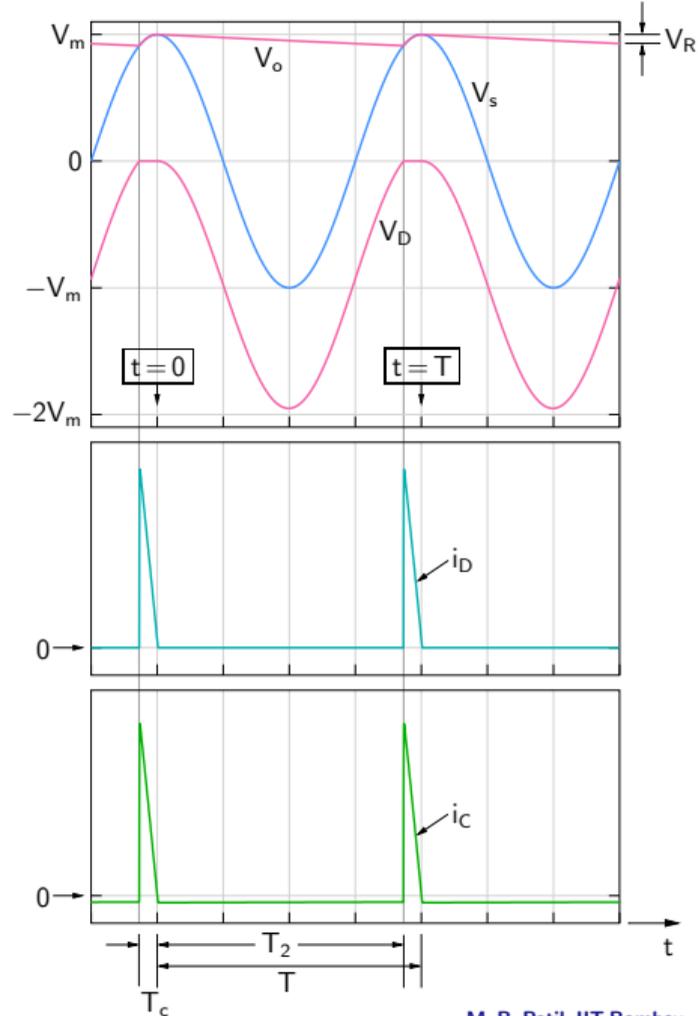


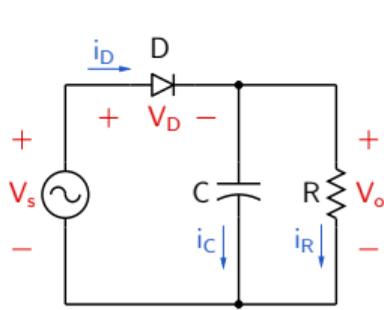

(b) Peak diode current

$$\begin{aligned}
 i_D^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_c) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_c + 0.16
 \end{aligned}$$

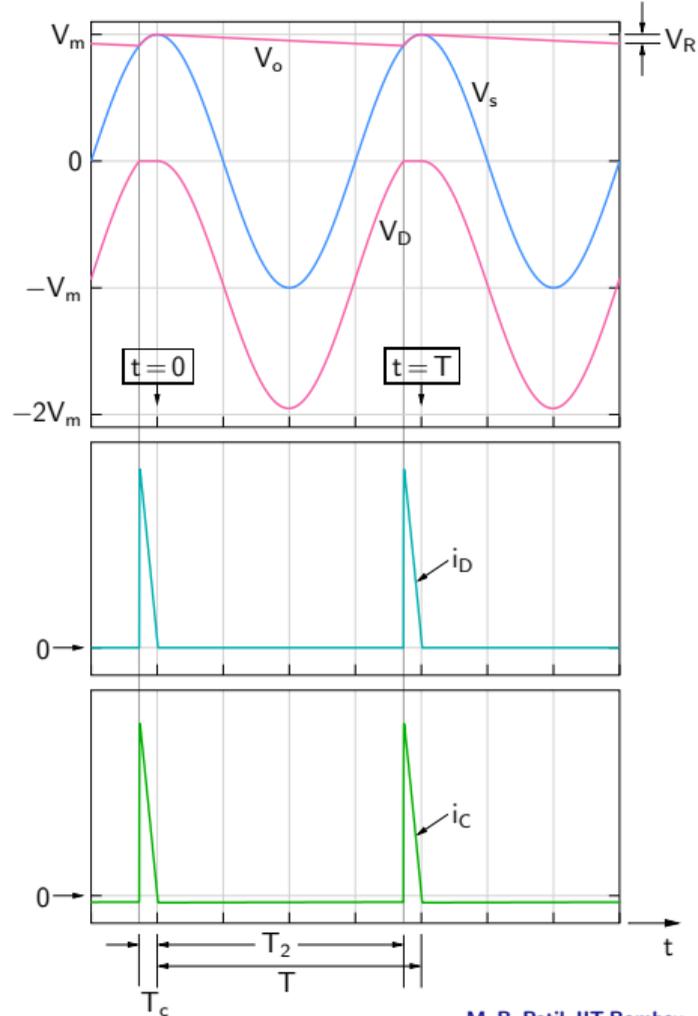

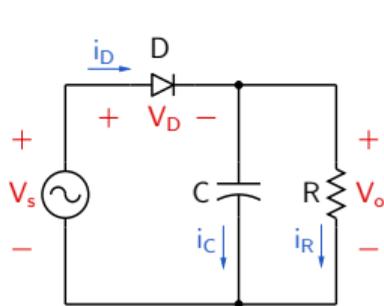



(b) Peak diode current

$$\begin{aligned}
 i_D^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_c) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_c + 0.16
 \end{aligned}$$

$$V_m \cos(-\omega T_c) = V_m - V_R, \text{ giving}$$
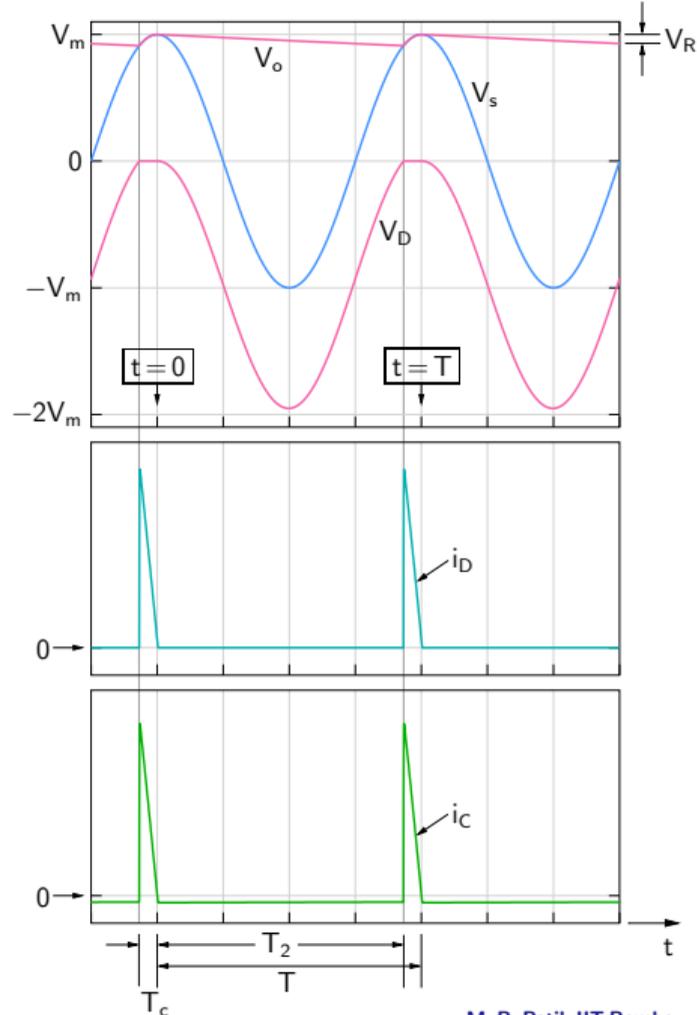
$$\omega T_c = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.$$



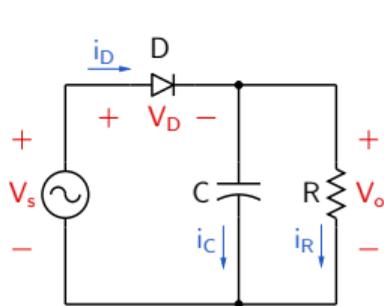


(b) Peak diode current


$$\begin{aligned}
 i_D^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_c) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_c + 0.16
 \end{aligned}$$

$$V_m \cos(-\omega T_c) = V_m - V_R, \text{ giving}$$


$$\omega T_c = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.$$

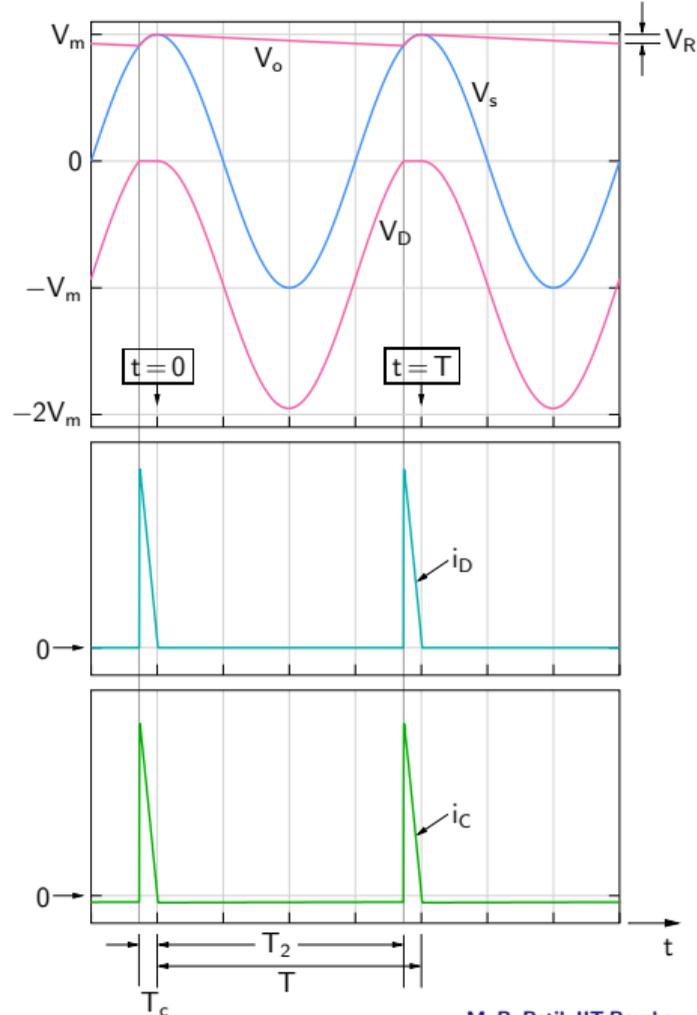
$$\begin{aligned}
 i_D^{\text{peak}} &= 2\pi \times 50 \times 1600 \times 10^{-6} \times 16 \times \sin 29^\circ + 0.16 \\
 &= 3.89 + 0.16 = 4.05 \text{ A.}
 \end{aligned}$$



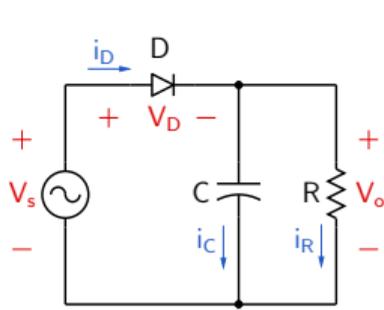

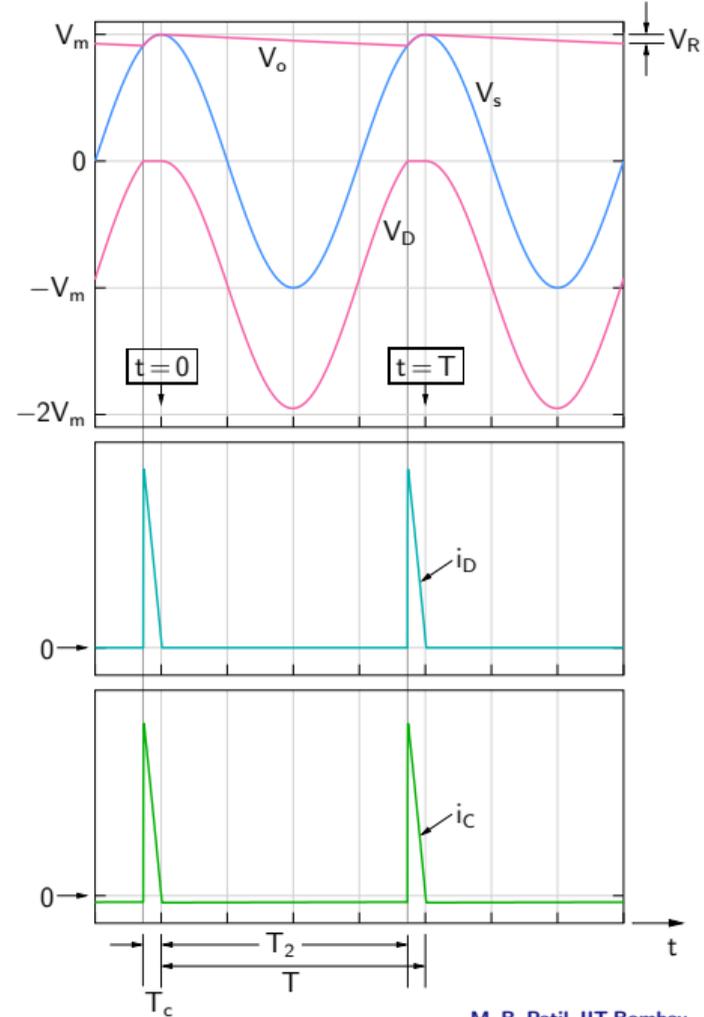
(b) Peak diode current: analytic expression




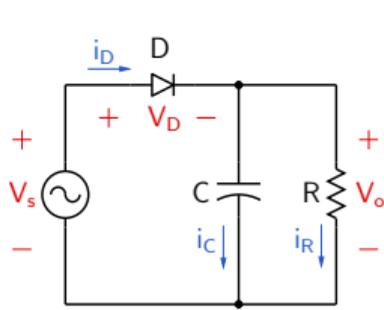

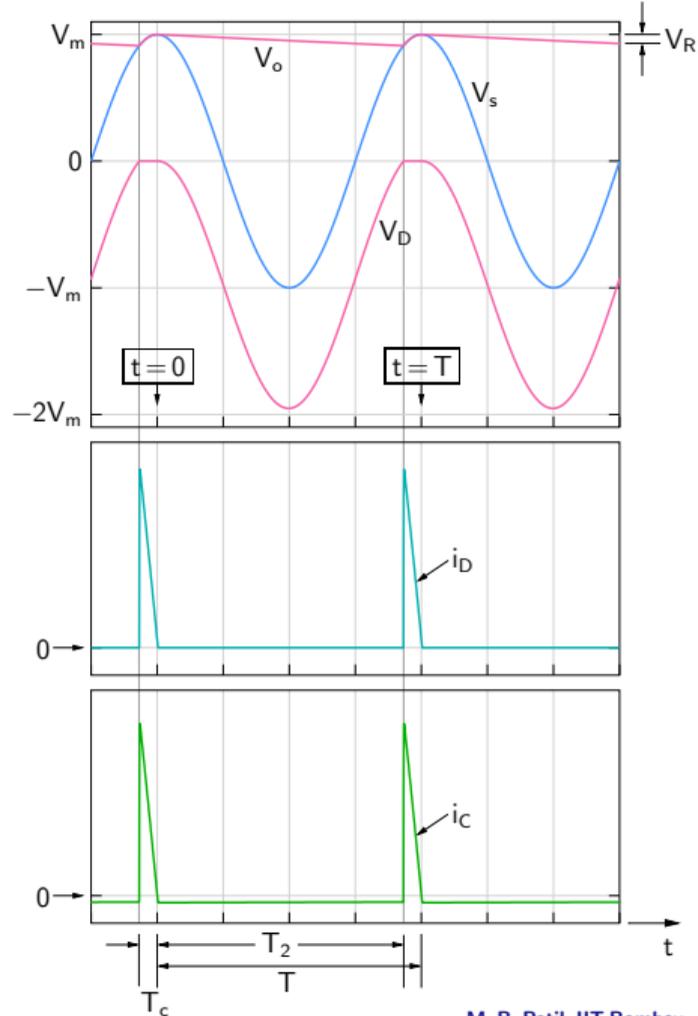(b) Peak diode current: analytic expression

$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$




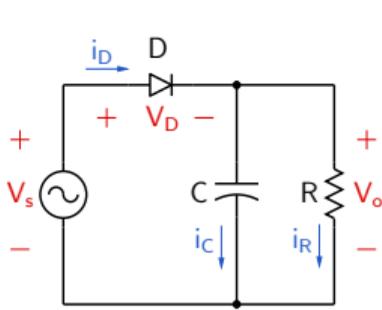


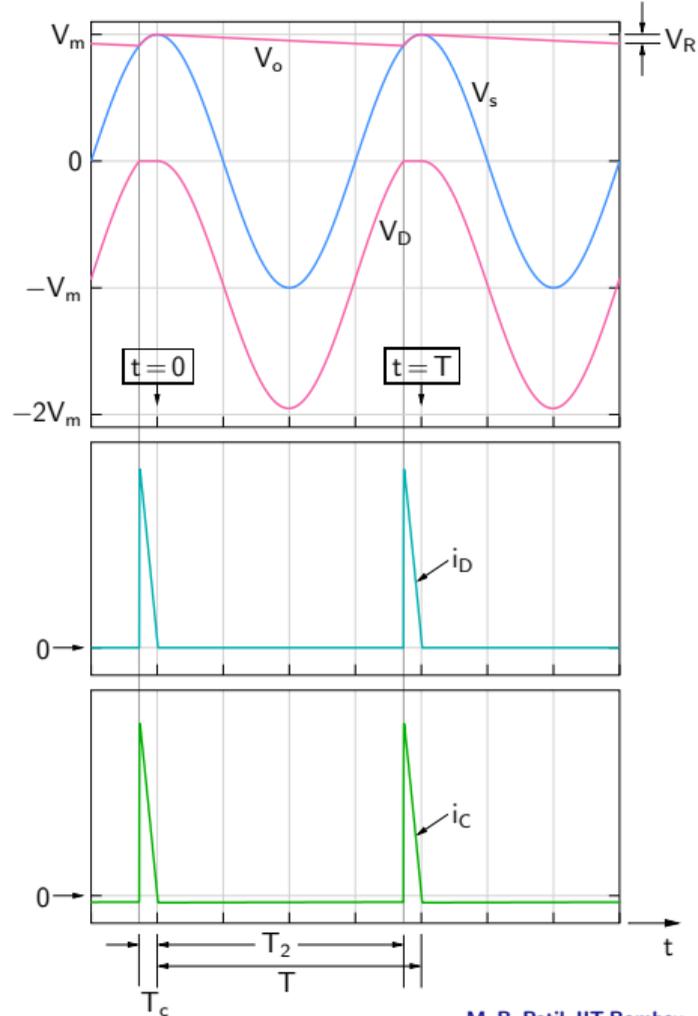(b) Peak diode current: analytic expression

$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$



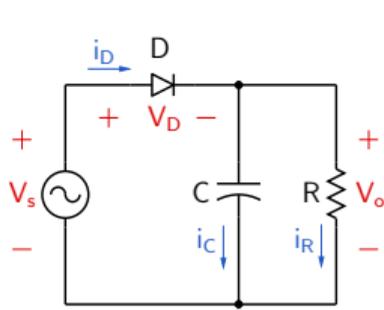



(b) Peak diode current: analytic expression

$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

$$\begin{aligned} i_D^{\text{peak}} &= i_R + C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} \\ &= i_R + \omega C V_m \sin \omega T_c \\ &= i_R + \omega C V_m \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

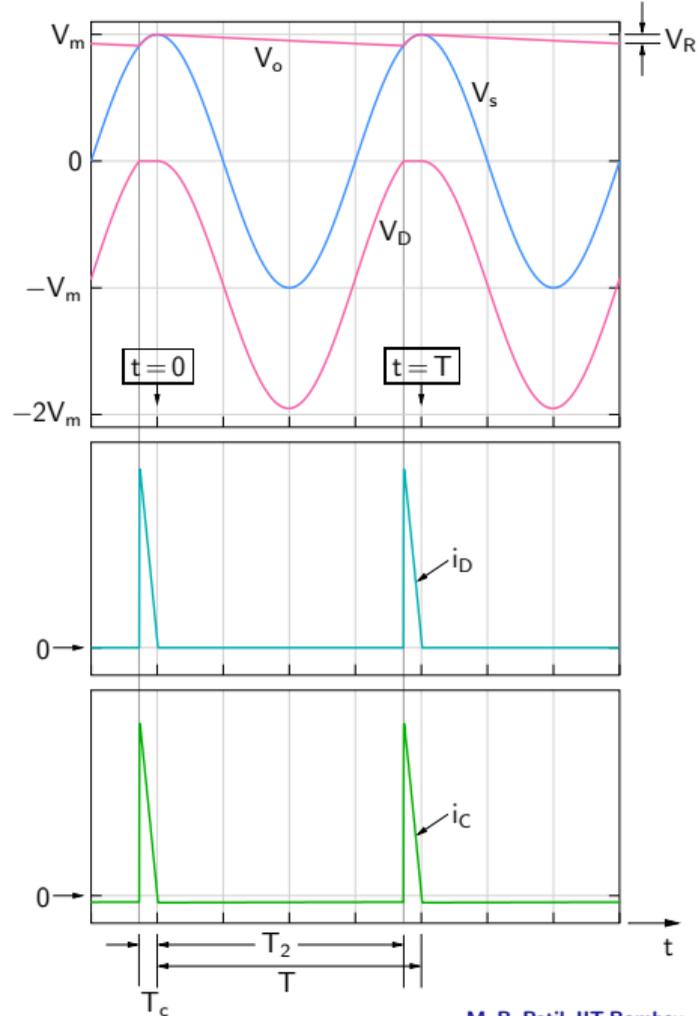

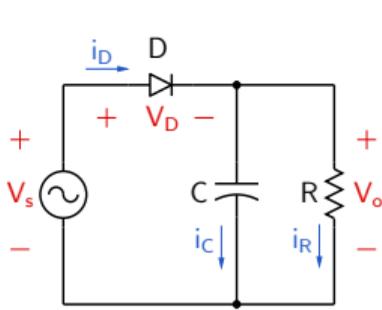


(b) Peak diode current: analytic expression


$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

$$\begin{aligned} i_D^{\text{peak}} &= i_R + C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} \\ &= i_R + \omega C V_m \sin \omega T_c \\ &= i_R + \omega C V_m \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

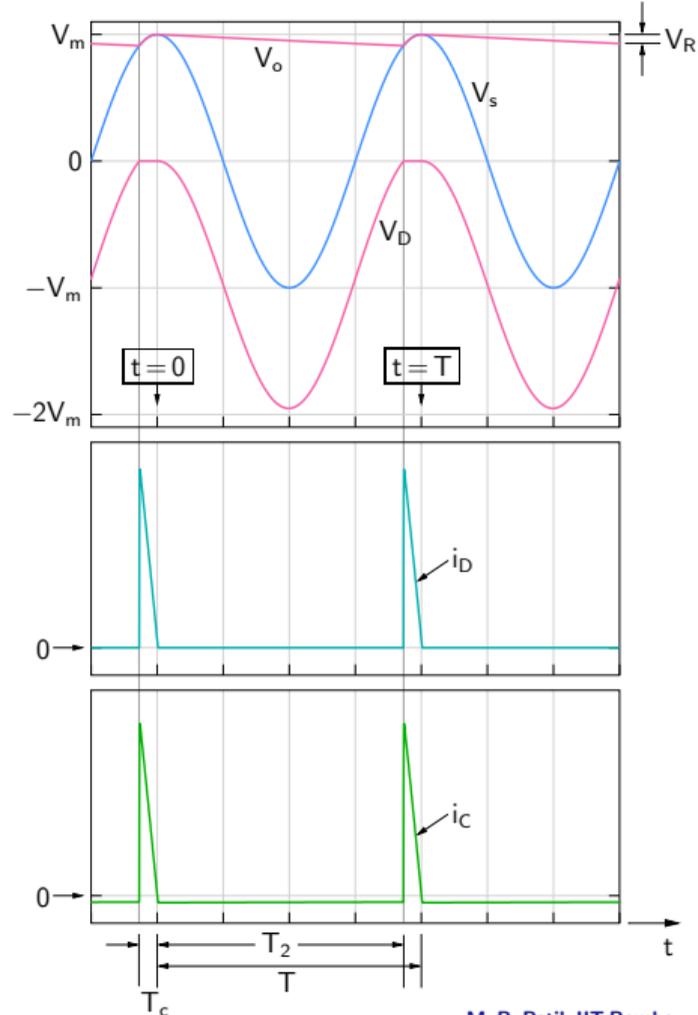(c) Maximum reverse bias $\approx 2 V_m = 32 \text{ V}$.



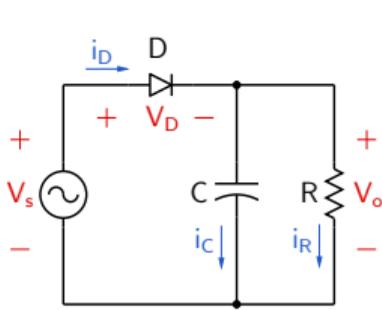

(b) Peak diode current: analytic expression


$$V_m \cos(-\omega T_c) = V_m - V_R \rightarrow \cos \omega T_c = 1 - \frac{V_R}{V_m} \equiv 1 - x$$

$$\begin{aligned} \sin \omega T_c &= \sqrt{1 - \cos^2 \omega T_c} = \sqrt{1 - (1 - x)^2} \\ &= \sqrt{1 - (1 - 2x + x^2)} \approx \sqrt{2x} = \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$




$$\begin{aligned} i_D^{\text{peak}} &= i_R + C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} \\ &= i_R + \omega C V_m \sin \omega T_c \\ &= i_R + \omega C V_m \sqrt{\frac{2V_R}{V_m}} \end{aligned}$$

(c) Maximum reverse bias $\approx 2 V_m = 32 \text{ V}$.


SEQUEL file: ee101_half_rectifier.sqproj

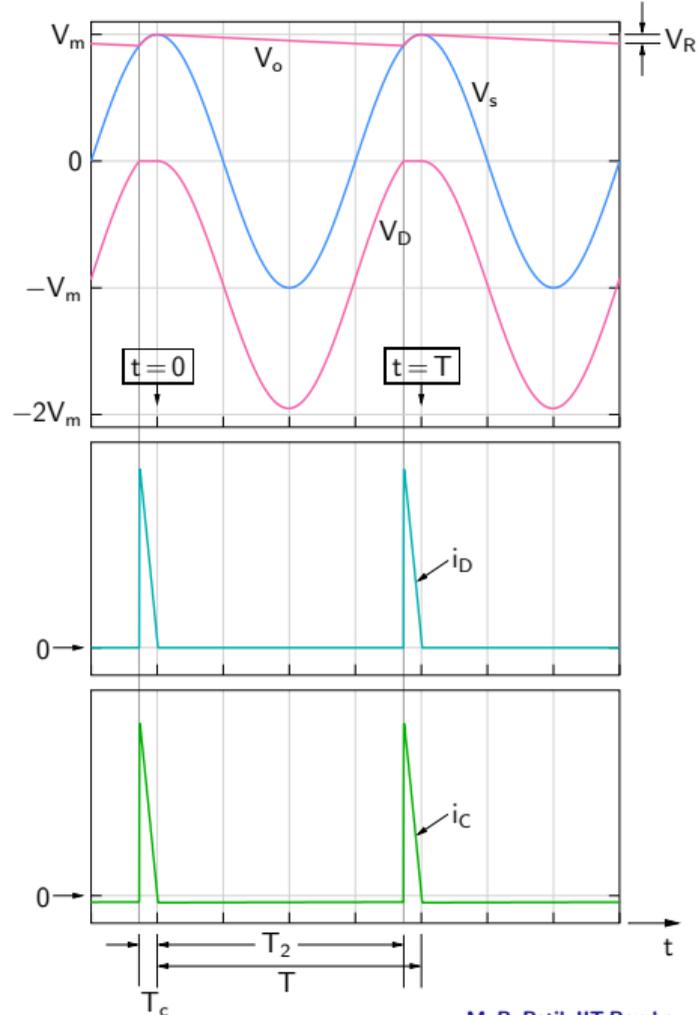

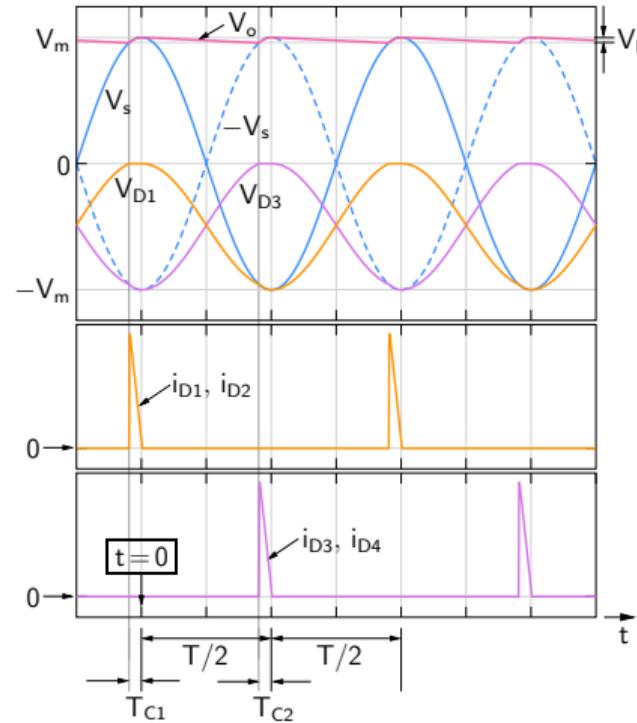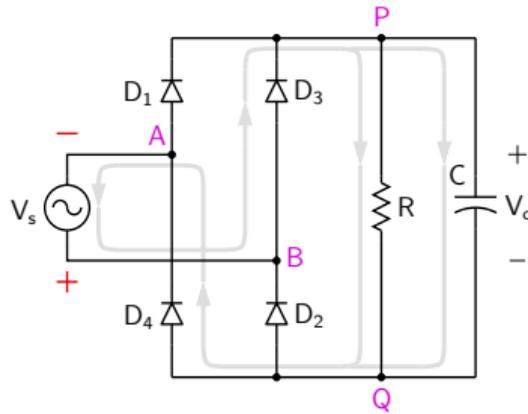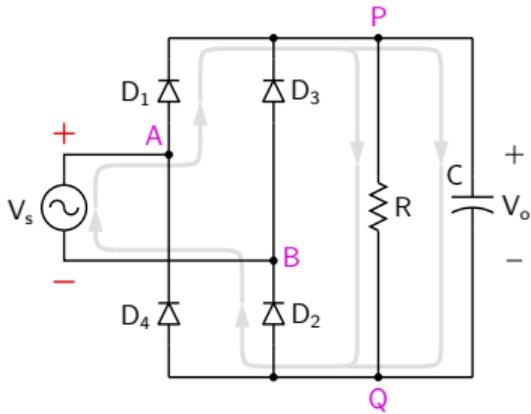
Full-wave (bridge) rectifier with capacitor filter



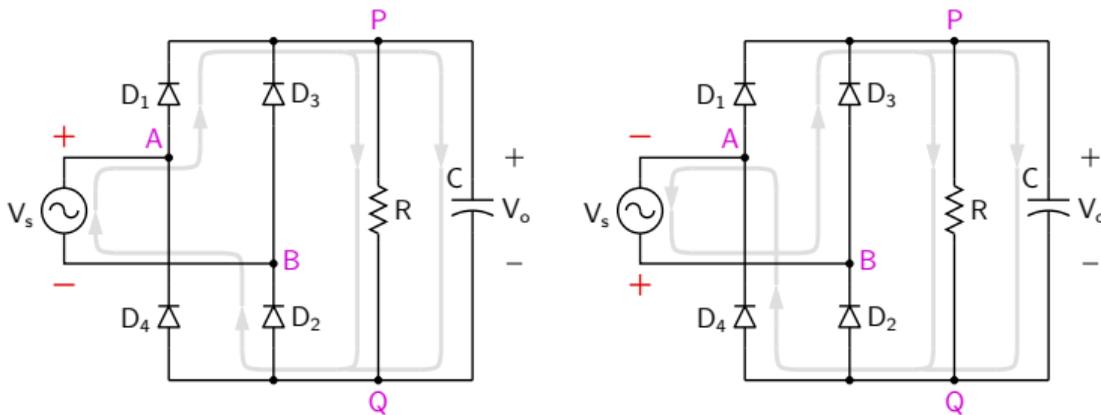
Full-wave (bridge) rectifier with capacitor filter



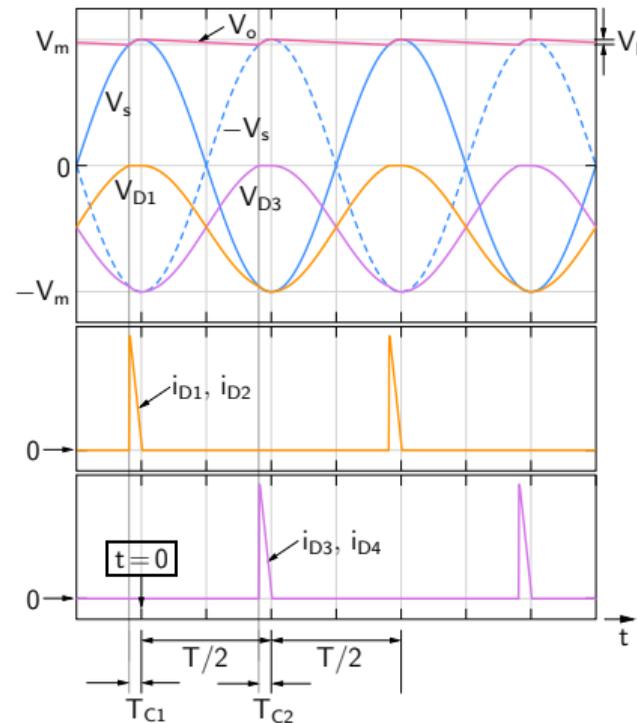
* As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.



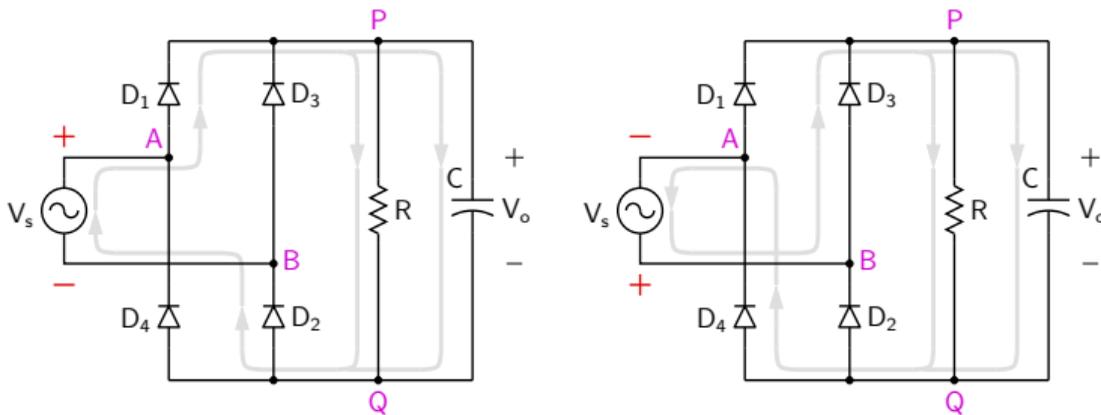
Full-wave (bridge) rectifier with capacitor filter



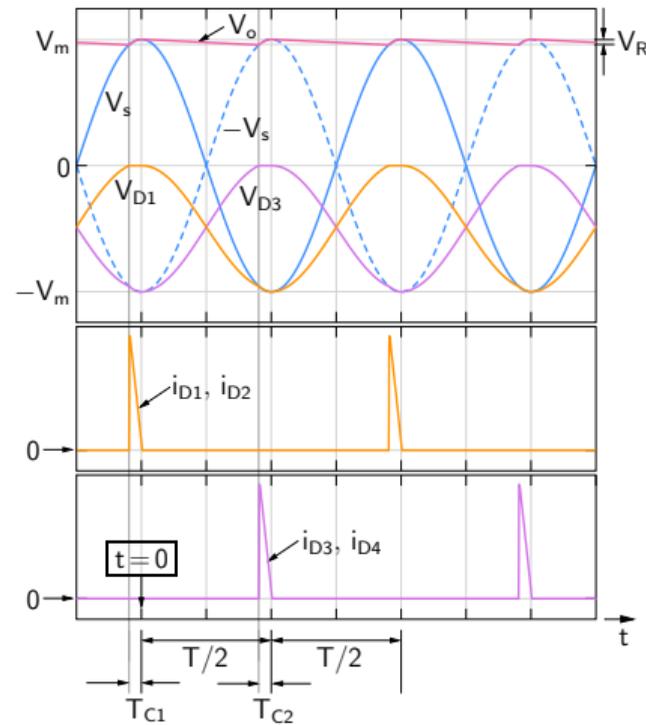
- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.



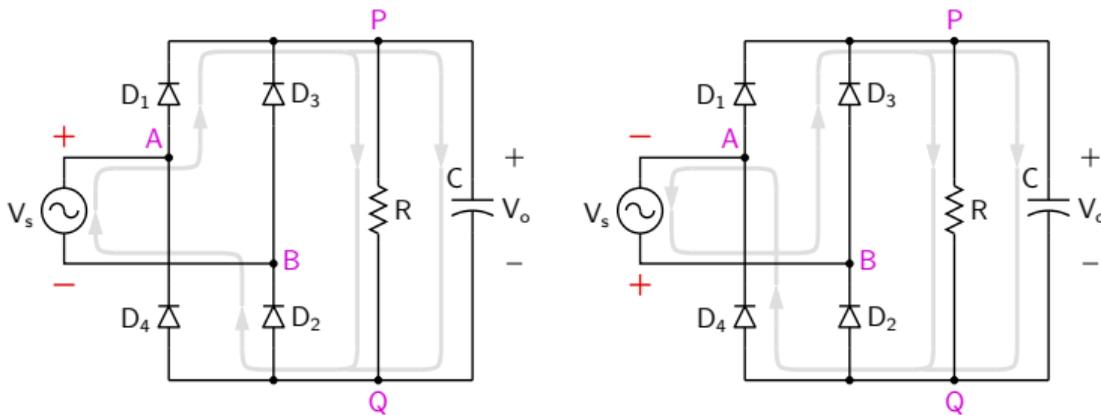
Full-wave (bridge) rectifier with capacitor filter



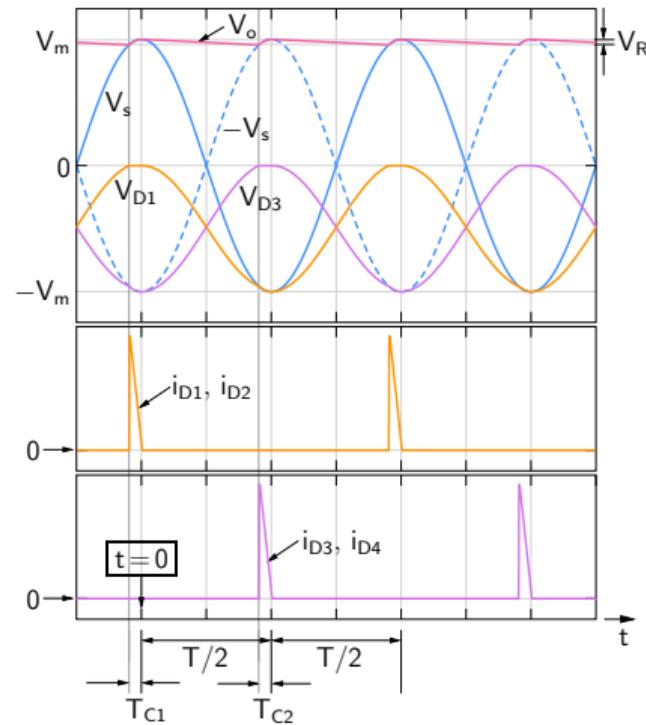
- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.
- * Charging through D_3, D_4 takes place when $V_o(t)$ falls below $-V_s(t)$.



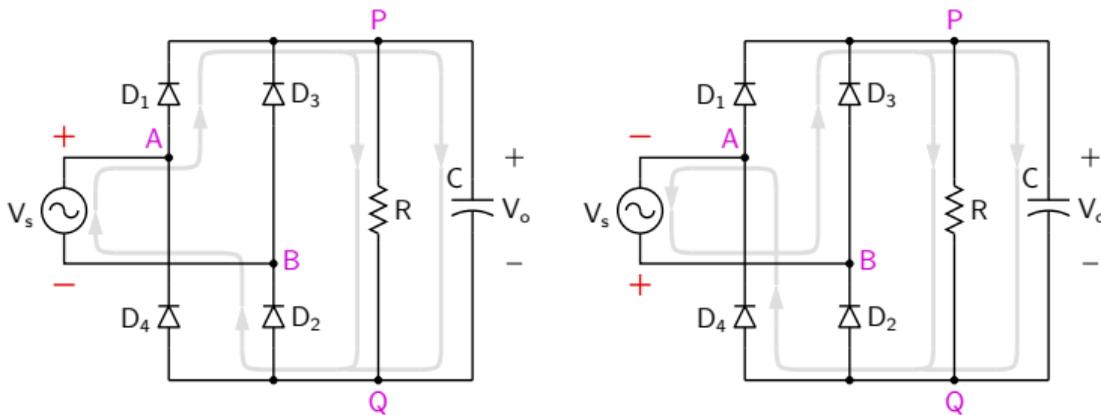
Full-wave (bridge) rectifier with capacitor filter



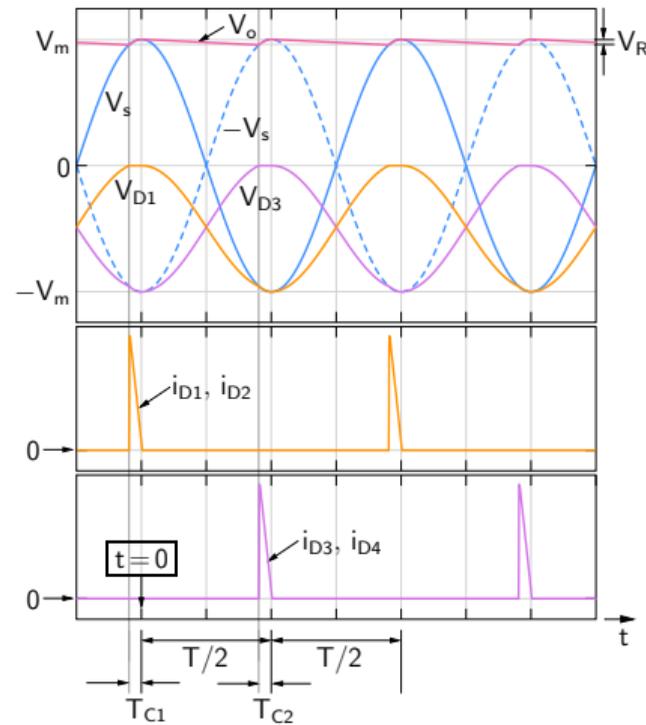
- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.
- * Charging through D_3, D_4 takes place when $V_o(t)$ falls below $-V_s(t)$.
- * The discharging interval is typically much longer than the charging intervals (T_{C1} and T_{C2}).



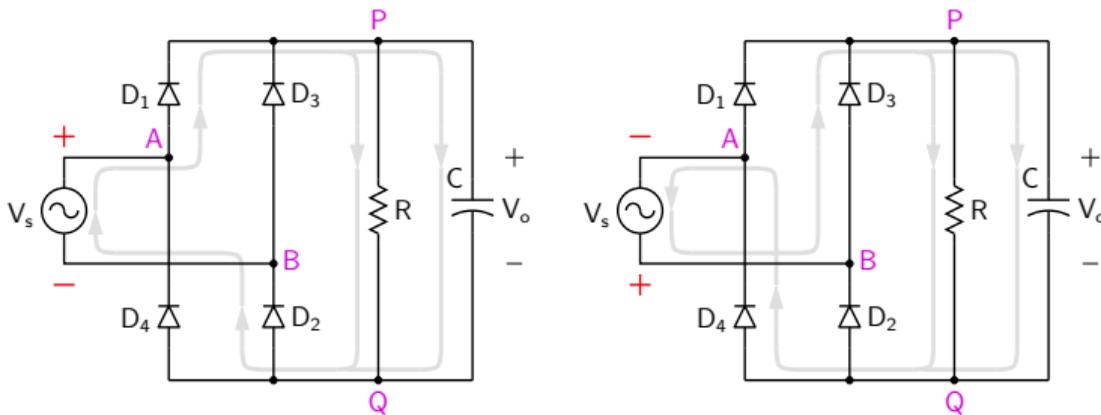
Full-wave (bridge) rectifier with capacitor filter




- * As in the half-wave rectifier case, we have charging and discharging intervals, and $V_o \approx V_m$ is maintained.
- * Charging through D_1, D_2 takes place when $V_o(t)$ falls below $V_s(t)$.
- * Charging through D_3, D_4 takes place when $V_o(t)$ falls below $-V_s(t)$.
- * The discharging interval is typically much longer than the charging intervals (T_{C1} and T_{C2}).
- * The maximum reverse bias across any of the diodes is V_m .

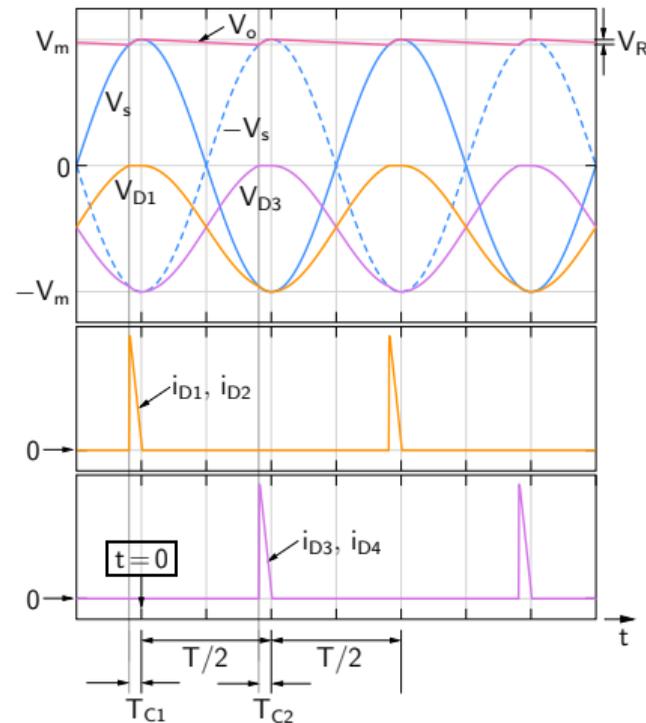

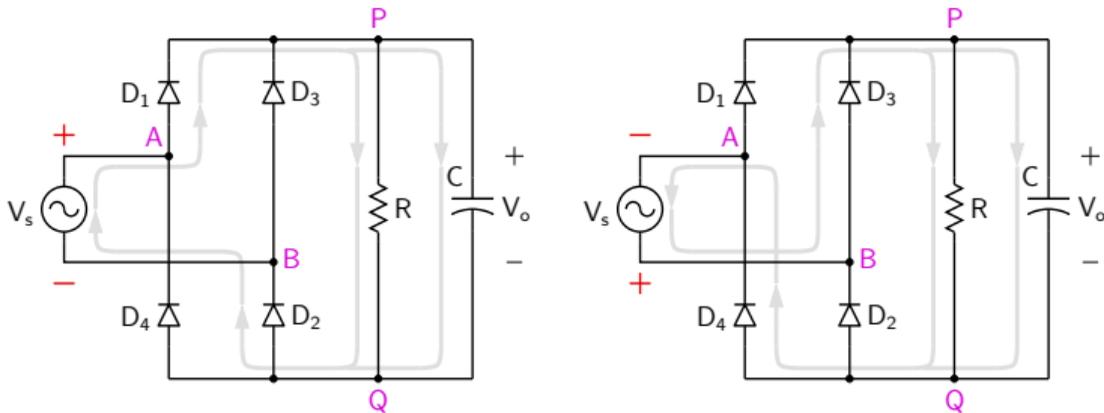
Full-wave rectifier with capacitor filter



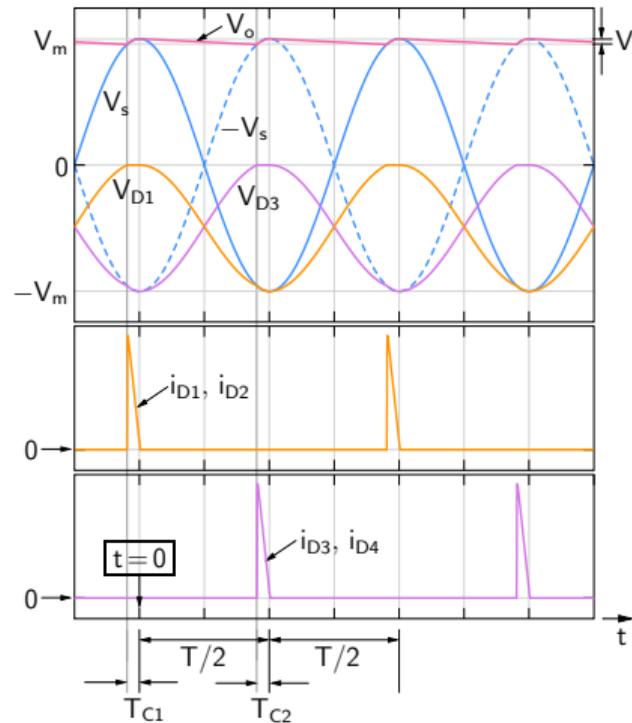$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)




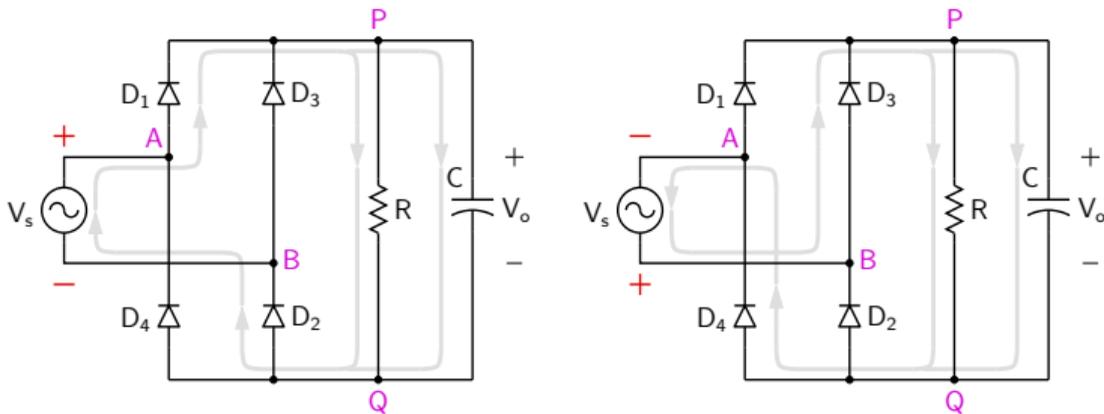Full-wave rectifier with capacitor filter




$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

(a) filter capacitance:

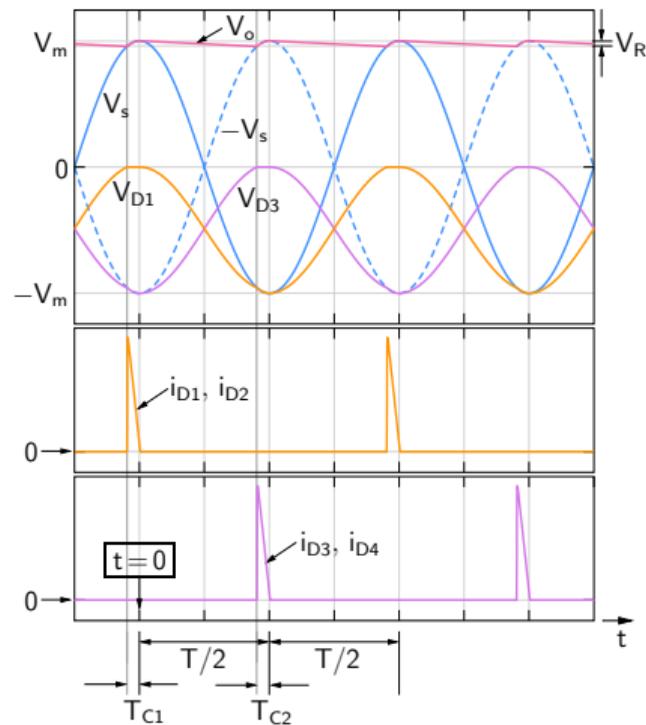

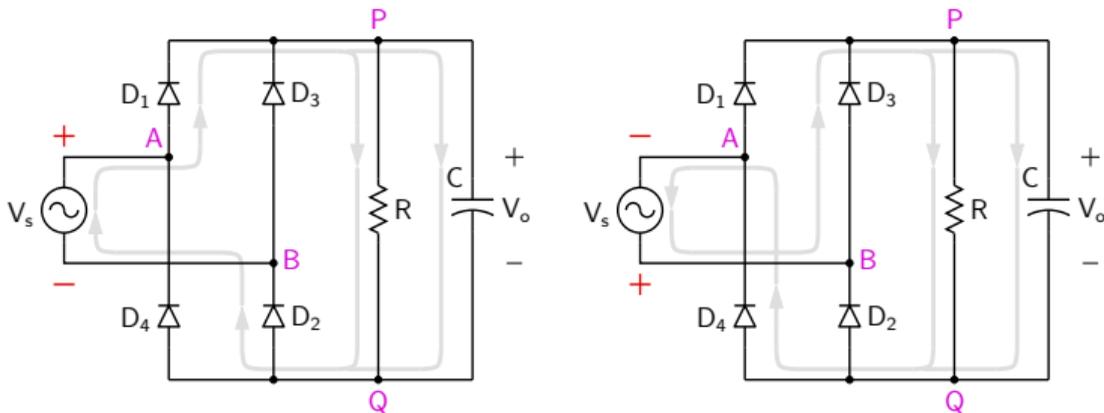Full-wave rectifier with capacitor filter




$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

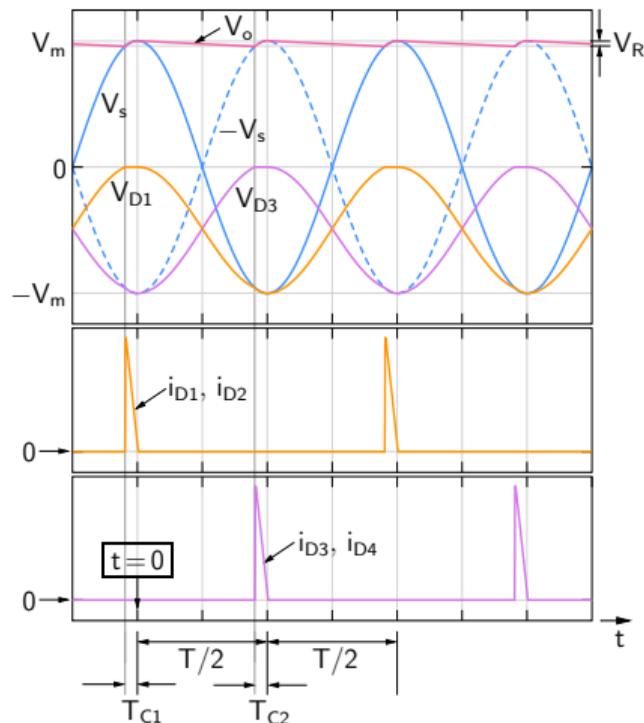
(a) filter capacitance:

Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T/2} \rightarrow V_R = V_m \frac{T}{2RC}.$$



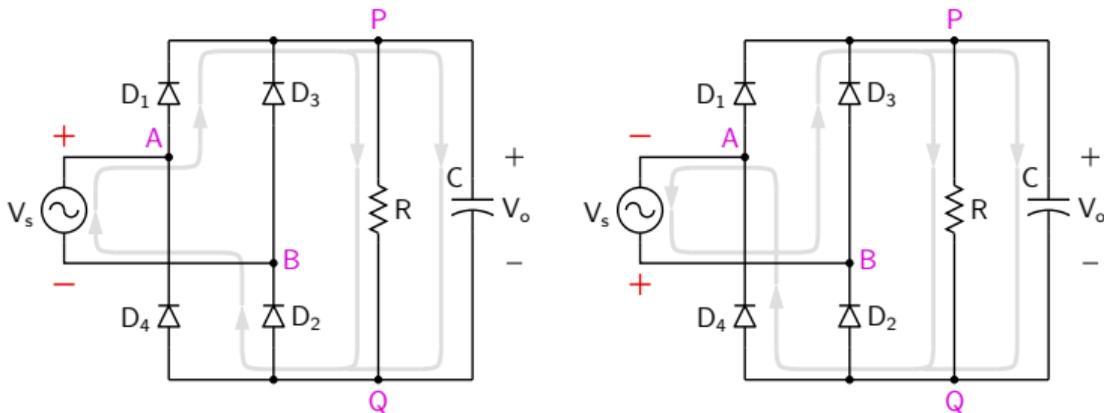Full-wave rectifier with capacitor filter




$V_m = 16\text{ V}$, $f = 50\text{ Hz}$, $R = 100\ \Omega$. For a ripple voltage $V_R = 2\text{ V}$, find (a) the filter capacitance C , (b) average and peak diode currents, (c) maximum reverse voltage across the diode. (Let $V_{on} = 0\text{ V}$.)

(a) filter capacitance:



Assuming $i_C = i_R = \frac{V_o}{R} \approx \frac{V_m}{R}$ in the discharge phase, we get

$$i_C = \frac{V_m}{R} = C \frac{\Delta V_o}{\Delta t} \approx C \frac{V_R}{T/2} \rightarrow V_R = V_m \frac{T}{2RC}.$$

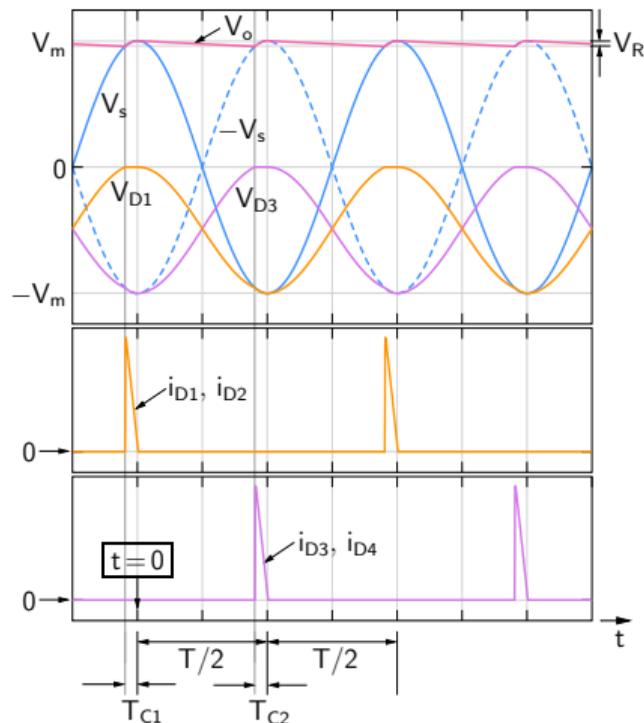
$$\rightarrow C = \frac{1}{2} \frac{V_m}{V_R} \frac{T}{R} = \frac{1}{2} \frac{16\text{ V}}{2\text{ V}} \frac{20\text{ ms}}{100\ \Omega} = 800\ \mu\text{F}.$$



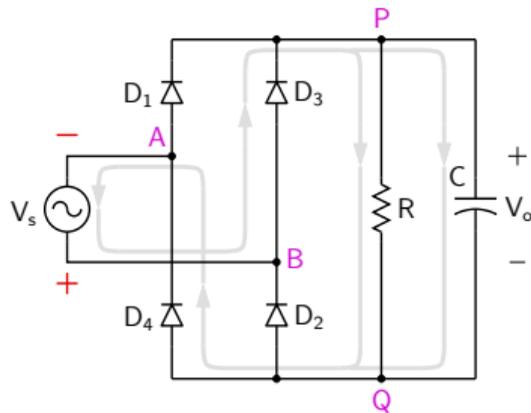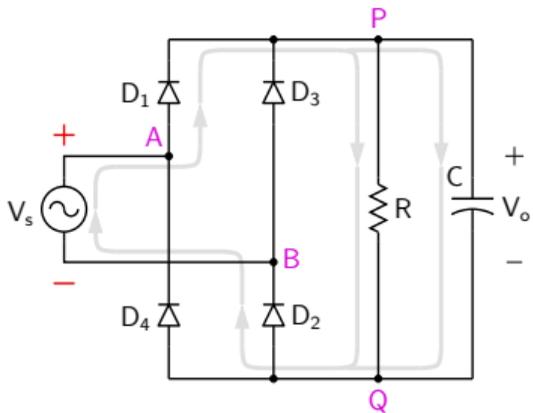
Full-wave rectifier with capacitor filter



(b) Average diode current

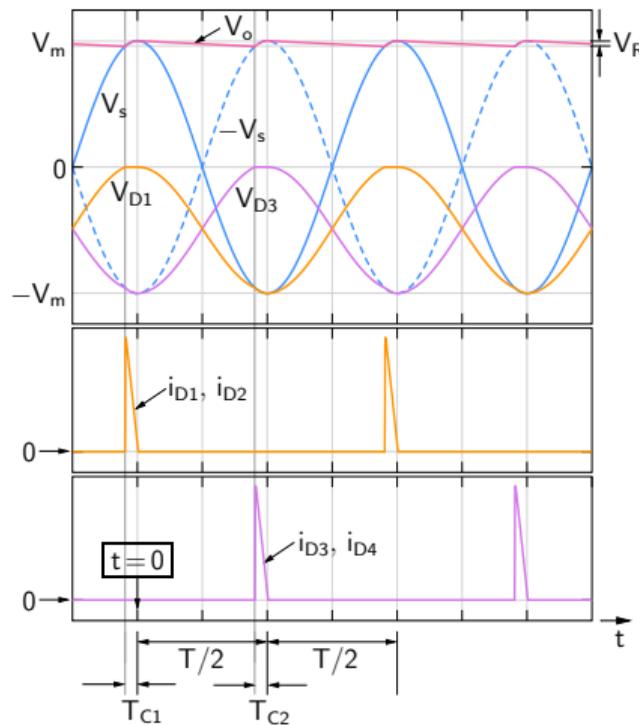


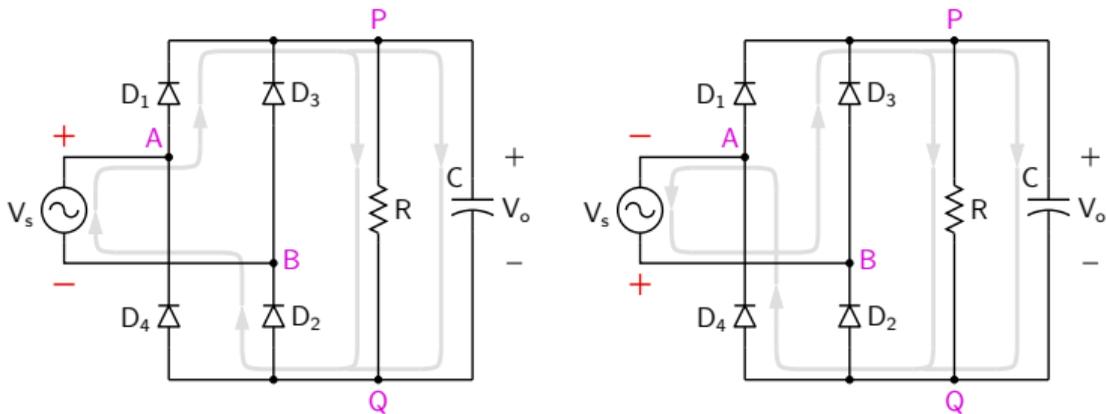Full-wave rectifier with capacitor filter




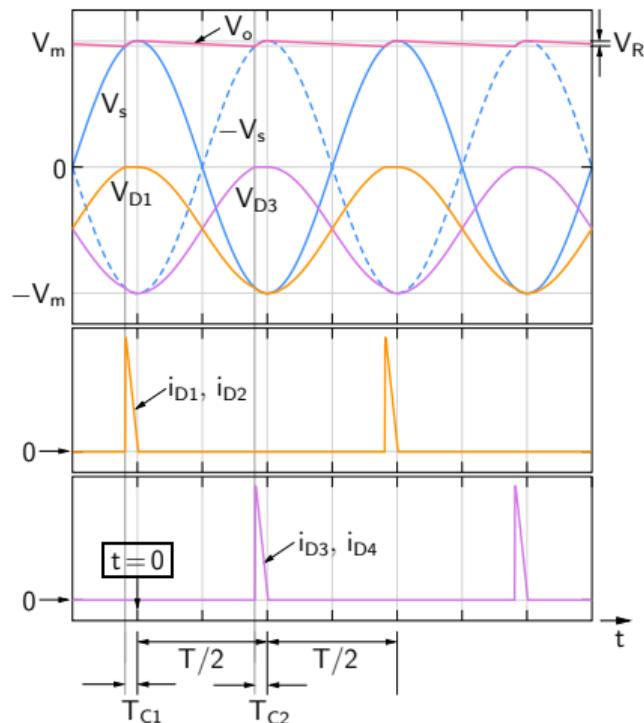(b) Average diode current

Half of the charge lost by the capacitor is supplied by $i_{D1} (= i_{D2})$, and the other half by $i_{D3} (= i_{D4})$.



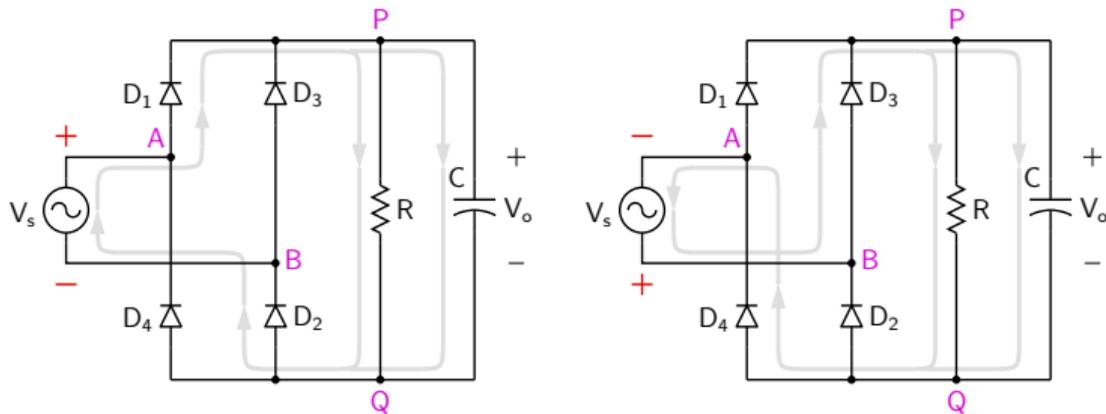
Full-wave rectifier with capacitor filter



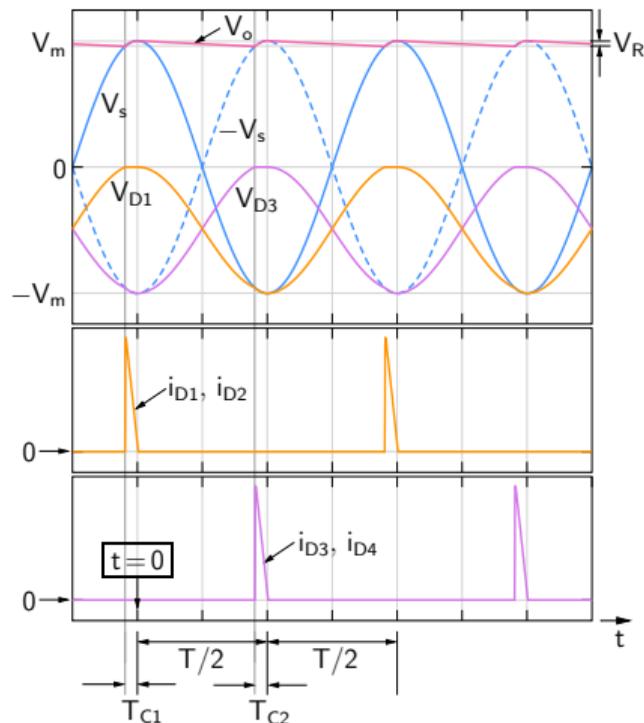
(b) Average diode current

Half of the charge lost by the capacitor is supplied by i_{D1} ($= i_{D2}$), and the other half by i_{D3} ($= i_{D4}$).

$$i_D^{av} = \frac{1}{T} \times \frac{1}{2} \times (\text{Charge lost in one cycle})$$



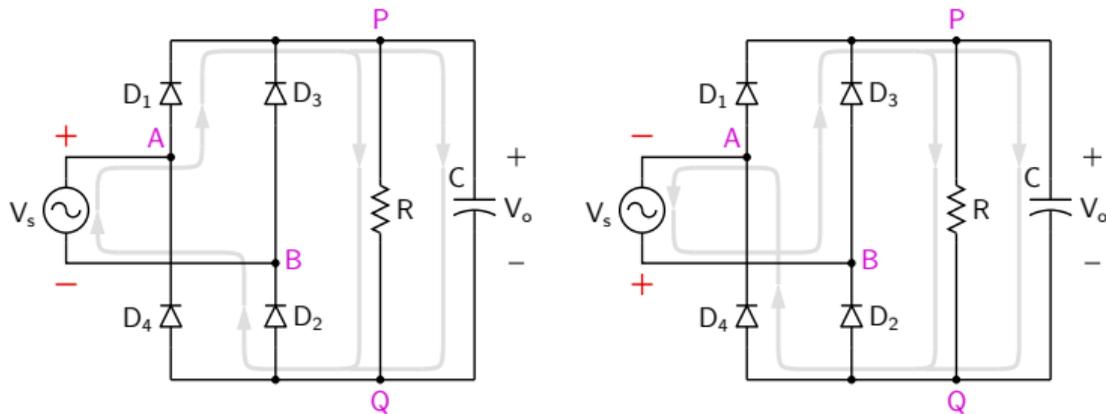Full-wave rectifier with capacitor filter




(b) Average diode current



Half of the charge lost by the capacitor is supplied by i_{D1} ($= i_{D2}$), and the other half by i_{D3} ($= i_{D4}$).

$$i_D^{av} = \frac{1}{T} \times \frac{1}{2} \times (\text{Charge lost in one cycle})$$

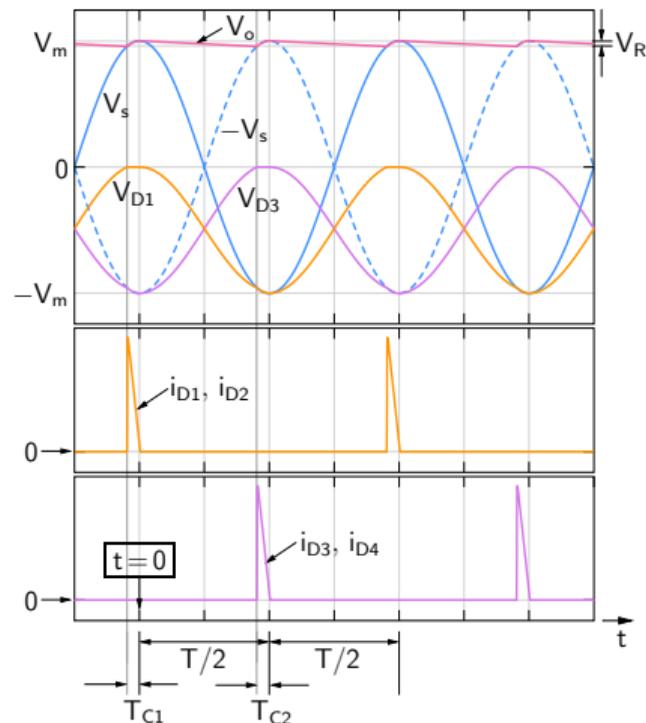
$$\approx \frac{1}{T} \times \frac{1}{2} \times \left(\frac{V_m}{R} \times T \right) = \frac{V_m}{2R} = \frac{16\text{ V}}{2 \times 100\ \Omega} = 80\text{ mA}.$$



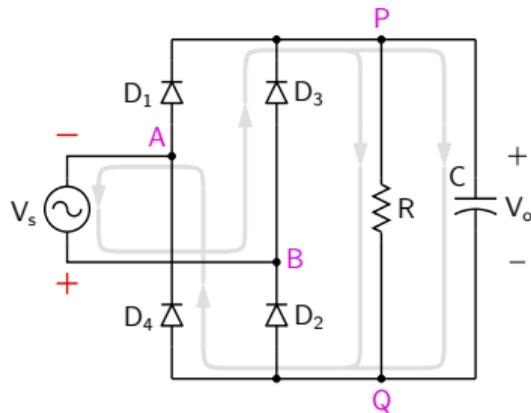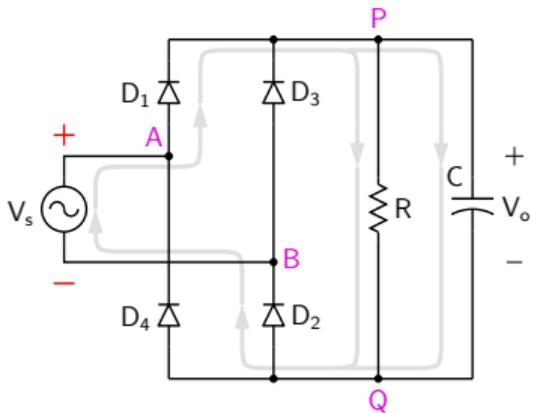
Full-wave rectifier with capacitor filter



(b) Peak diode current

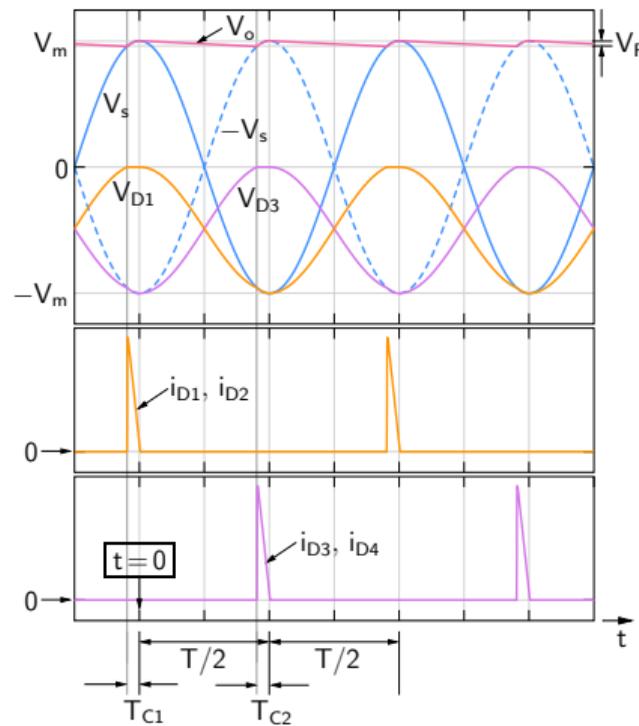


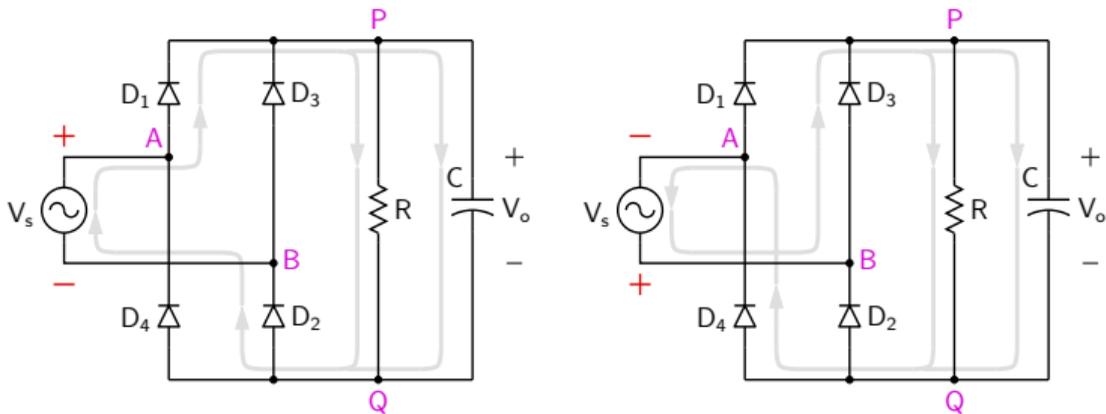Full-wave rectifier with capacitor filter




(b) Peak diode current

$$\begin{aligned}
 i_{D1}^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_{C1}} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_{C1}) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_{C1} + 0.16
 \end{aligned}$$

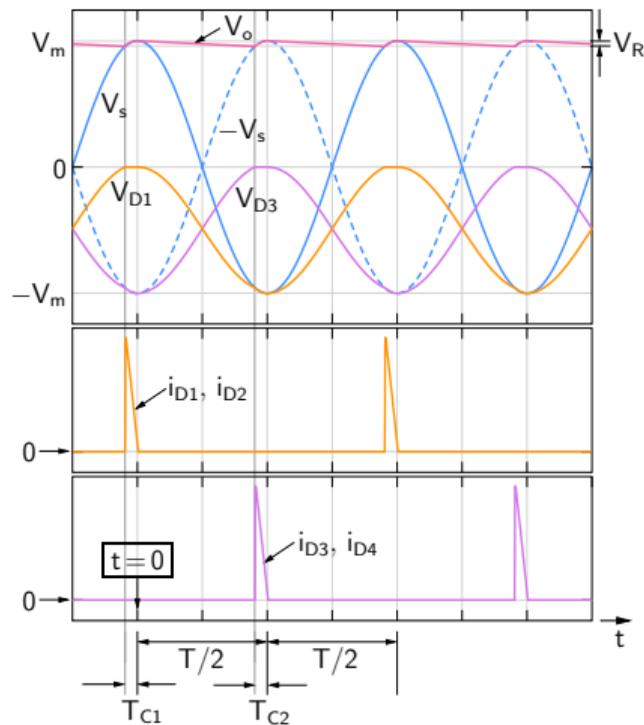

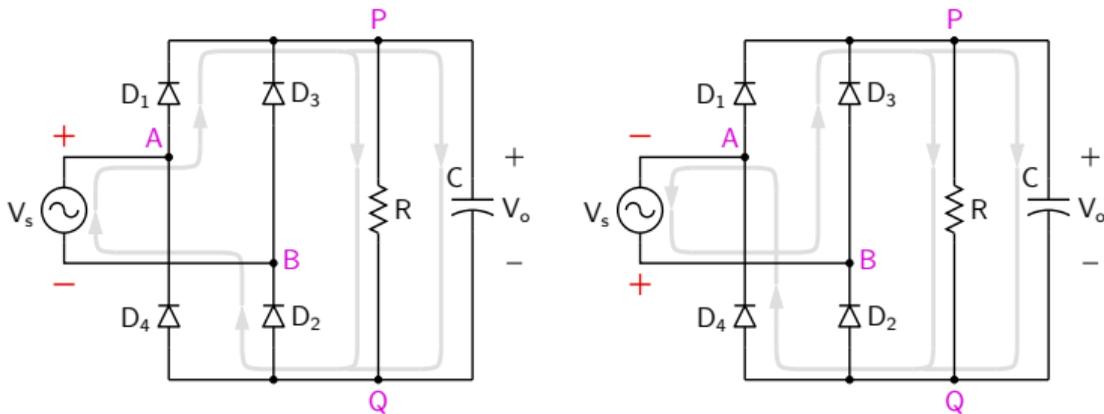
Full-wave rectifier with capacitor filter




(b) Peak diode current

$$\begin{aligned}
 i_{D1}^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_{C1}} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_{C1}) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_{C1} + 0.16
 \end{aligned}$$
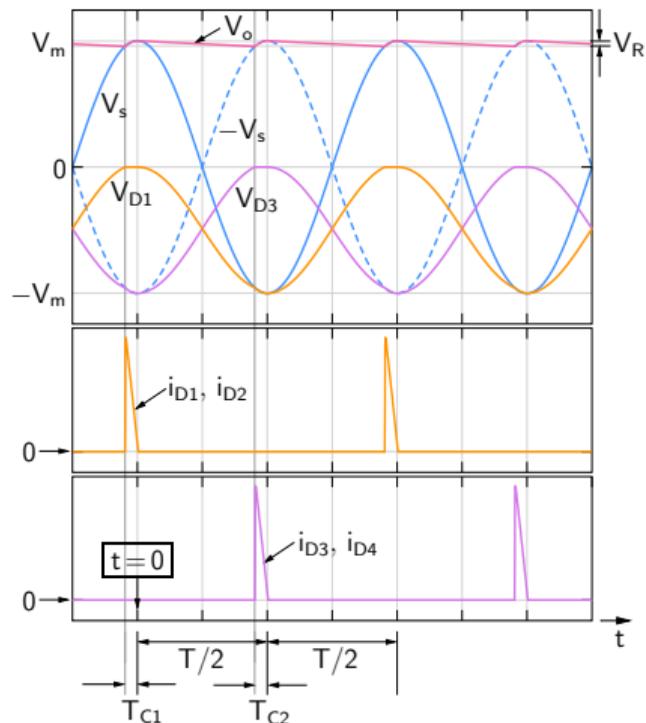
$$\omega T_{C1} = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.$$



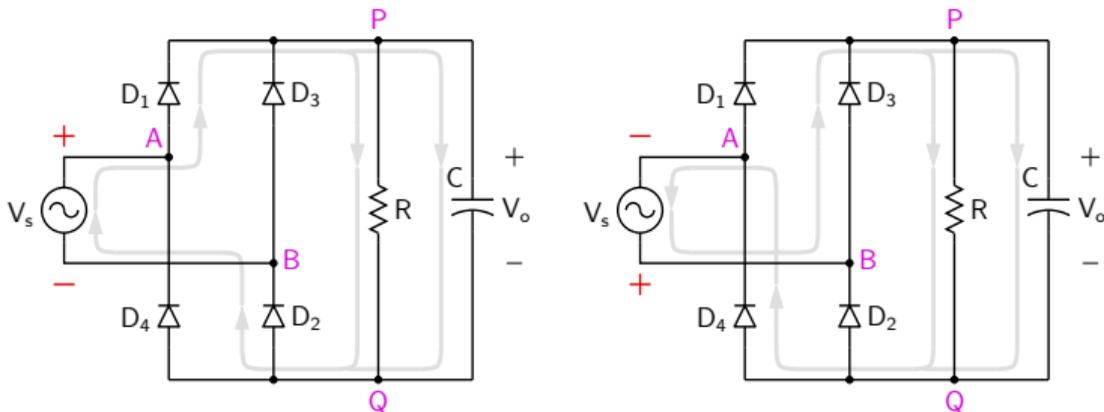Full-wave rectifier with capacitor filter




(b) Peak diode current


$$\begin{aligned}
 i_{D1}^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_{C1}} + \frac{V_m}{R} \\
 &= -\omega C V_m \sin(-\omega T_{C1}) + \frac{16 \text{ V}}{100 \Omega} \\
 &= \omega C V_m \sin \omega T_{C1} + 0.16
 \end{aligned}$$

$$\omega T_{C1} = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{2}{16} \right) = 29^\circ.$$

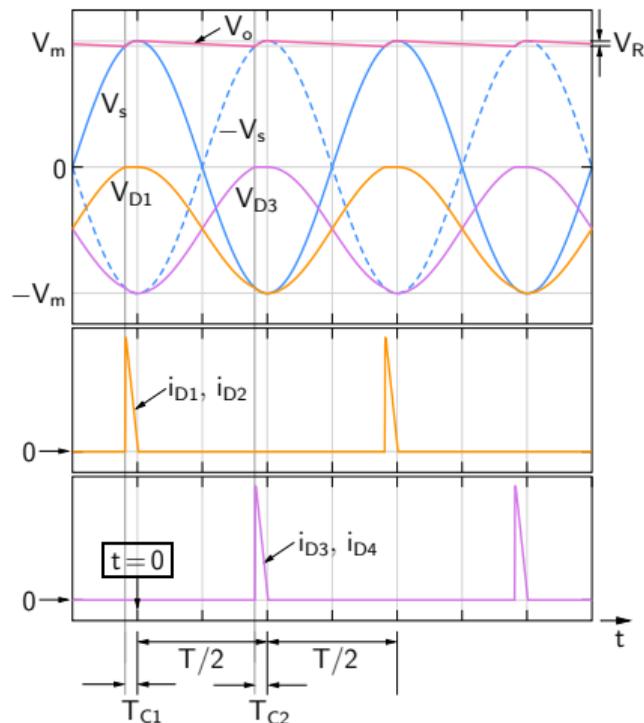
$$\begin{aligned}
 i_{D1}^{\text{peak}} &= 2\pi \times 50 \times 800 \times 10^{-6} \times 16 \times \sin 29^\circ + 0.16 \\
 &= 1.95 + 0.16 = 2.1 \text{ A}.
 \end{aligned}$$



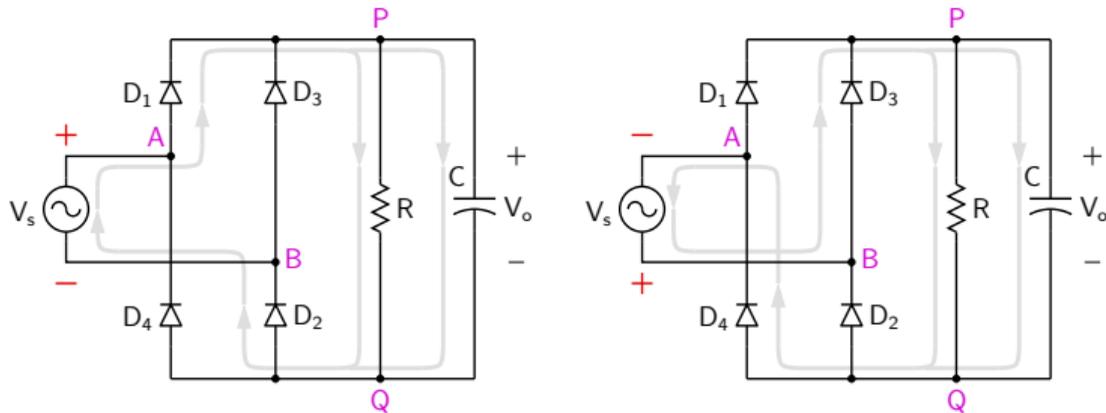
Full-wave rectifier with capacitor filter



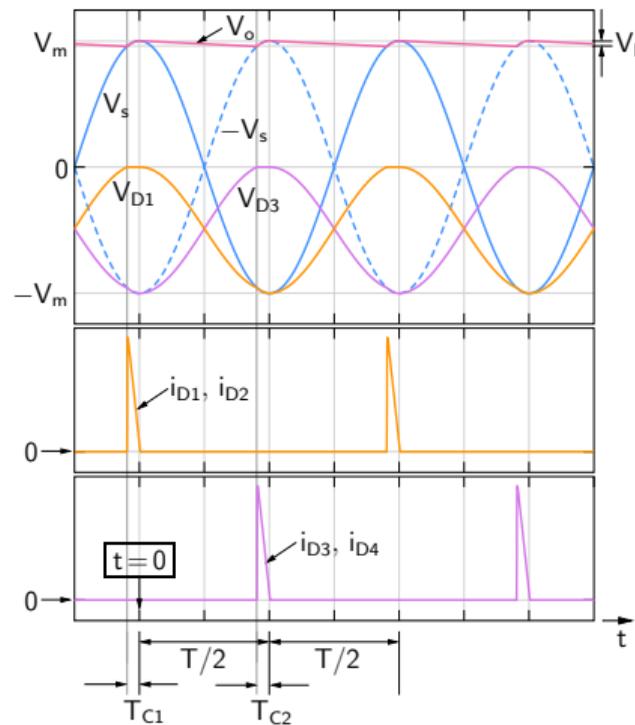(c) Maximum reverse bias = $V_m = 16\text{ V}$.




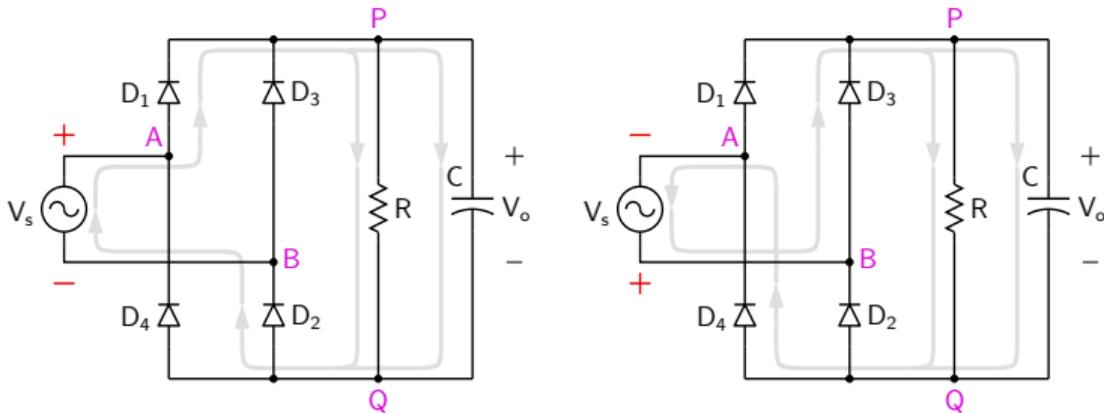Full-wave rectifier with capacitor filter



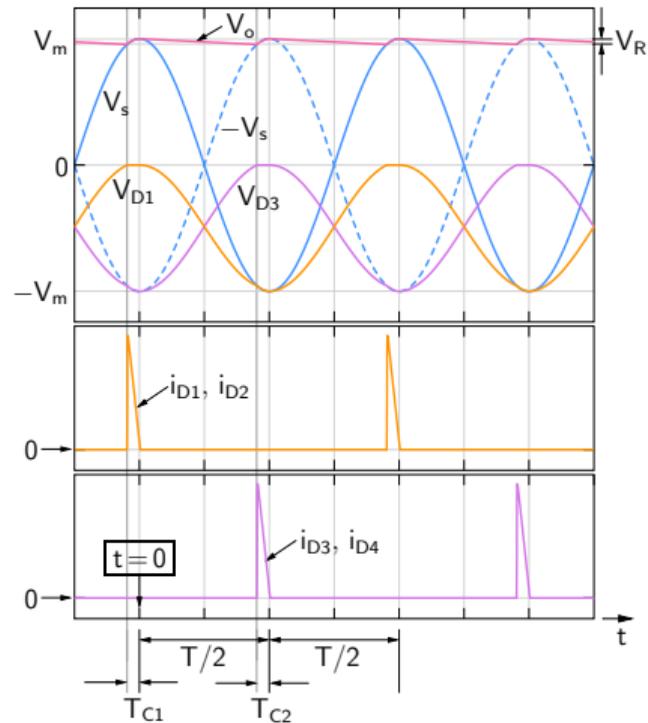(c) Maximum reverse bias = $V_m = 16\text{ V}$.

SEQUEL file: [diode_rectifier_4.sqproj](#)



Comparison of half-wave and full-wave (bridge) rectifiers with capacitive filter

For the same source voltage ($V_m \sin \omega t$), load (R), and ripple voltage (V_R), compare the half-wave and full-wave rectifiers.

Comparison of half-wave and full-wave (bridge) rectifiers with capacitive filter

For the same source voltage ($V_m \sin \omega t$), load (R), and ripple voltage (V_R), compare the half-wave and full-wave rectifiers.

Parameter	Half-wave	Full-wave
Number of diodes	1	4
Filter capacitance	C	$C/2$
Average diode current	i_D^{av}	$i_D^{\text{av}}/2$
Peak diode current	i_D^{peak}	$i_D^{\text{peak}}/2$
Maximum reverse voltage	$2 V_m$	V_m