
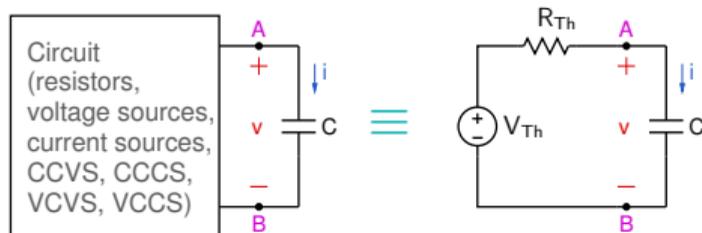


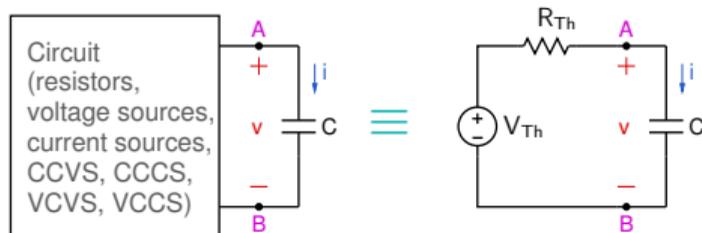\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$ .




\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$ .

\* Homogeneous solution:
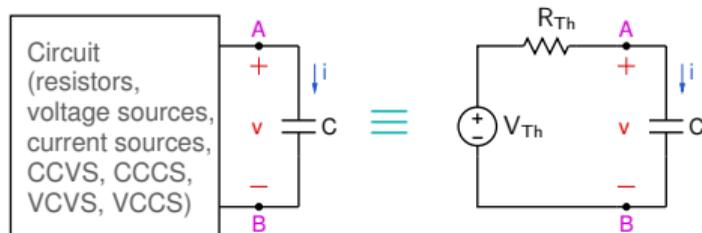
$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left( \frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$




\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$ .

\* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left( \frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$
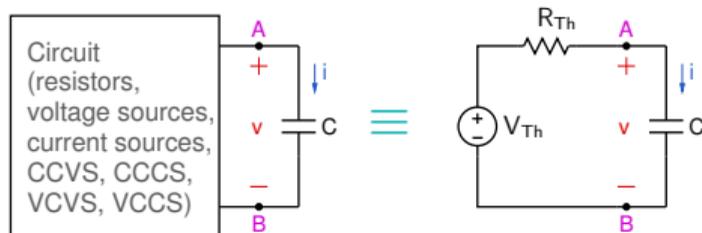
$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .


\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$ .

\* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left( \frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$

$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$

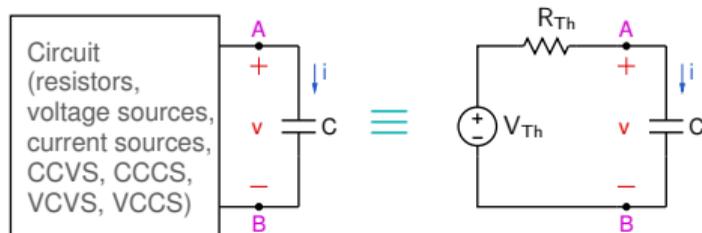\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $i = 0$ , and we get  $v^{(p)} = V_{Th}$  as a particular solution (which happens to be simply a constant).



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$ .


\* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left( \frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$

$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$

\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $i = 0$ , and we get  $v^{(p)} = V_{Th}$  as a particular solution (which happens to be simply a constant).

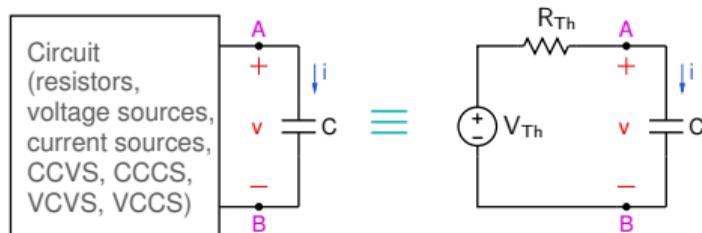\*  $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$ .



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v \rightarrow \frac{dv}{dt} + \frac{v}{R_{Th} C} = \frac{V_{Th}}{R_{Th} C}$ .

\* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant." } \left( \frac{\text{V}}{\text{Coul/sec}} \times \frac{\text{Coul}}{\text{V}} \right)$$


$$\rightarrow \frac{dv}{v} = -\frac{dt}{\tau} \rightarrow \log v = -\frac{t}{\tau} + K_0 \rightarrow v^{(h)} = \exp[(-t/\tau) + K_0] = K \exp(-t/\tau).$$

\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $i = 0$ , and we get  $v^{(p)} = V_{Th}$  as a particular solution (which happens to be simply a constant).

\*  $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$ .


\* In general,  $v(t) = A \exp(-t/\tau) + B$ , where  $A$  and  $B$  can be obtained from known conditions on  $v$ .
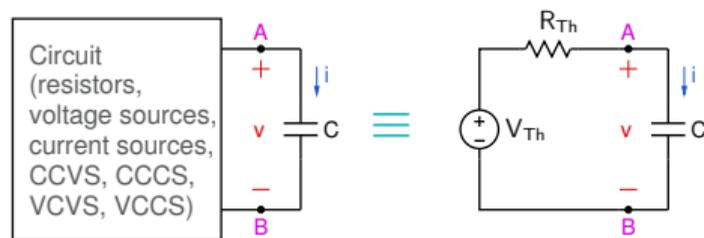
## RC circuits with DC sources (continued)




- \* If all sources are DC (constant), we have  $v(t) = A \exp(-t/\tau) + B$ ,  $\tau = R_{Th}C$ .

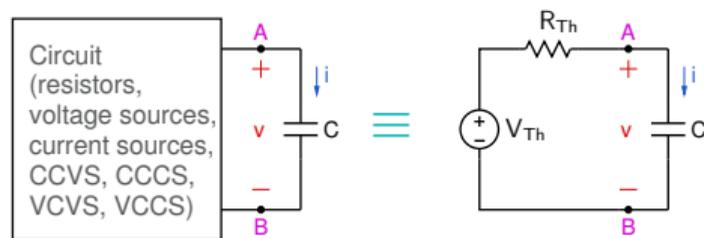
## RC circuits with DC sources (continued)



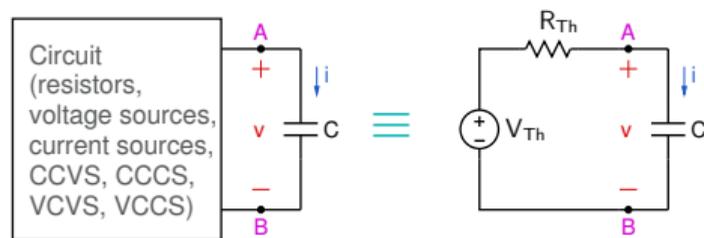- \* If all sources are DC (constant), we have  $v(t) = A \exp(-t/\tau) + B$ ,  $\tau = R_{Th}C$ .
- \*  $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .



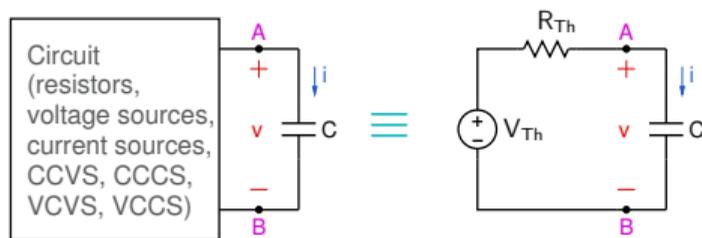- \* If all sources are DC (constant), we have  $v(t) = A \exp(-t/\tau) + B$ ,  $\tau = R_{Th}C$ .
- \*  $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $i \rightarrow 0$ , i.e., the capacitor behaves like an open circuit since all derivatives vanish.



- \* If all sources are DC (constant), we have  $v(t) = A \exp(-t/\tau) + B$ ,  $\tau = R_{Th}C$ .
- \*  $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $i \rightarrow 0$ , i.e., the capacitor behaves like an open circuit since all derivatives vanish.
- \* Since the circuit in the black box is linear, *any* variable (current or voltage) in the circuit can be expressed as  $x(t) = K_1 \exp(-t/\tau) + K_2$ , where  $K_1$  and  $K_2$  can be obtained from suitable conditions on  $x(t)$ .

$t/\tau$	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

$t/\tau$	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

\* For  $t/\tau = 5$ ,  $e^{-t/\tau} \simeq 0$ ,  $1 - e^{-t/\tau} \simeq 1$ .


$t/\tau$	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

\* For  $t/\tau = 5$ ,  $e^{-t/\tau} \simeq 0$ ,  $1 - e^{-t/\tau} \simeq 1$ .

\* We can say that the transient lasts for about 5 time constants.

# Plot of $f(t) = e^{-t/\tau}$

$t/\tau$	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

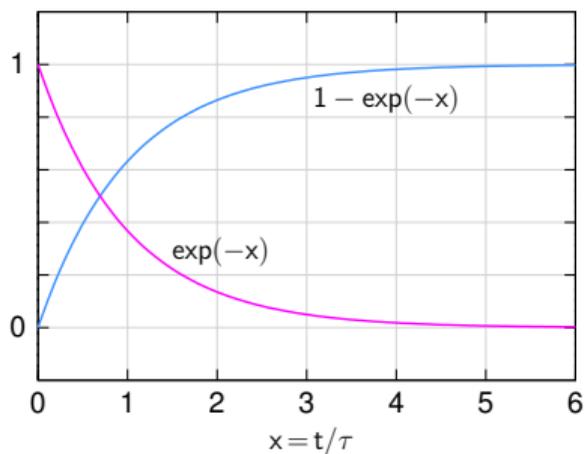

\* For  $t/\tau = 5$ ,  $e^{-t/\tau} \simeq 0$ ,  $1 - e^{-t/\tau} \simeq 1$ .

\* We can say that the transient lasts for about 5 time constants.

Plot of  $f(t) = A e^{-t/\tau} + B$

Plot of  $f(t) = A e^{-t/\tau} + B$

\* At  $t=0$ ,  $f = A + B$ .

Plot of  $f(t) = A e^{-t/\tau} + B$

\* At  $t=0$ ,  $f = A + B$ .

\* As  $t \rightarrow \infty$ ,  $f \rightarrow B$ .

## Plot of $f(t) = A e^{-t/\tau} + B$

- \* At  $t=0$ ,  $f = A + B$ .
- \* As  $t \rightarrow \infty$ ,  $f \rightarrow B$ .
- \* The graph of  $f(t)$  lies between  $(A + B)$  and  $B$ .

Note: If  $A > 0$ ,  $A + B > B$ . If  $A < 0$ ,  $A + B < B$ .

## Plot of $f(t) = A e^{-t/\tau} + B$

\* At  $t=0$ ,  $f = A + B$ .

\* As  $t \rightarrow \infty$ ,  $f \rightarrow B$ .

\* The graph of  $f(t)$  lies between  $(A + B)$  and  $B$ .

Note: If  $A > 0$ ,  $A + B > B$ . If  $A < 0$ ,  $A + B < B$ .

\* At  $t=0$ ,  $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$ .

If  $A > 0$ , the derivative (slope) at  $t=0$  is negative; else, it is positive.

## Plot of $f(t) = A e^{-t/\tau} + B$

\* At  $t=0$ ,  $f = A + B$ .

\* As  $t \rightarrow \infty$ ,  $f \rightarrow B$ .

\* The graph of  $f(t)$  lies between  $(A + B)$  and  $B$ .

Note: If  $A > 0$ ,  $A + B > B$ . If  $A < 0$ ,  $A + B < B$ .

\* At  $t=0$ ,  $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$ .

If  $A > 0$ , the derivative (slope) at  $t=0$  is negative; else, it is positive.

\* As  $t \rightarrow \infty$ ,  $\frac{df}{dt} \rightarrow 0$ , i.e.,  $f$  becomes constant (equal to  $B$ ).

## Plot of $f(t) = A e^{-t/\tau} + B$

\* At  $t=0$ ,  $f = A + B$ .

\* As  $t \rightarrow \infty$ ,  $f \rightarrow B$ .


\* The graph of  $f(t)$  lies between  $(A + B)$  and  $B$ .

Note: If  $A > 0$ ,  $A + B > B$ . If  $A < 0$ ,  $A + B < B$ .

\* At  $t=0$ ,  $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$ .

If  $A > 0$ , the derivative (slope) at  $t=0$  is negative; else, it is positive.

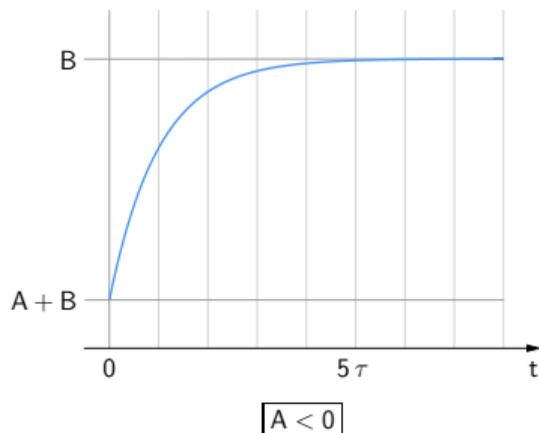\* As  $t \rightarrow \infty$ ,  $\frac{df}{dt} \rightarrow 0$ , i.e.,  $f$  becomes constant (equal to  $B$ ).



## Plot of $f(t) = A e^{-t/\tau} + B$


- \* At  $t=0$ ,  $f = A + B$ .
- \* As  $t \rightarrow \infty$ ,  $f \rightarrow B$ .
- \* The graph of  $f(t)$  lies between  $(A + B)$  and  $B$ .

Note: If  $A > 0$ ,  $A + B > B$ . If  $A < 0$ ,  $A + B < B$ .


- \* At  $t=0$ ,  $\frac{df}{dt} = A e^{-t/\tau} \left(-\frac{1}{\tau}\right) = -\frac{A}{\tau}$ .

If  $A > 0$ , the derivative (slope) at  $t=0$  is negative; else, it is positive.

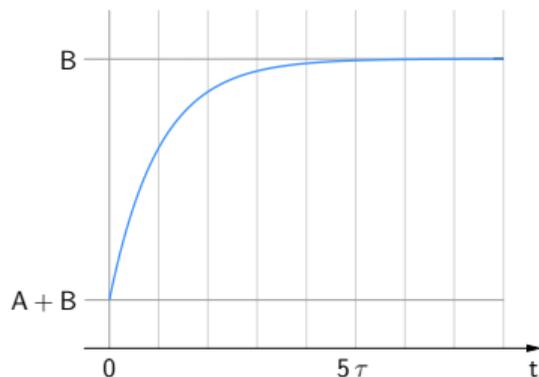
- \* As  $t \rightarrow \infty$ ,  $\frac{df}{dt} \rightarrow 0$ , i.e.,  $f$  becomes constant (equal to  $B$ ).





$A < 0$

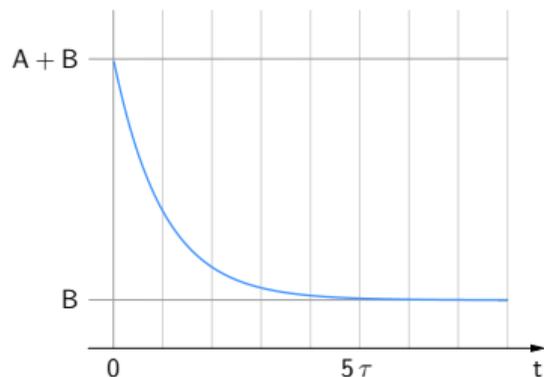


$A > 0$

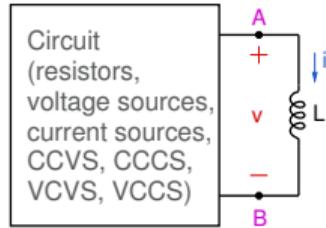

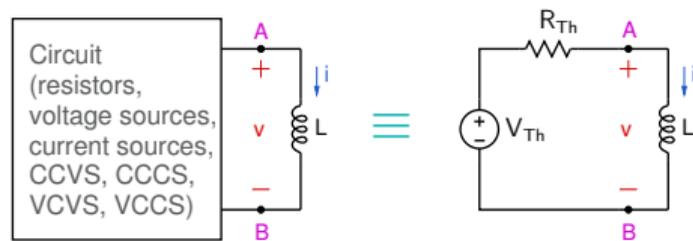

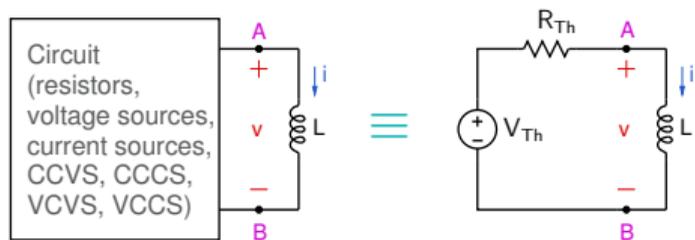


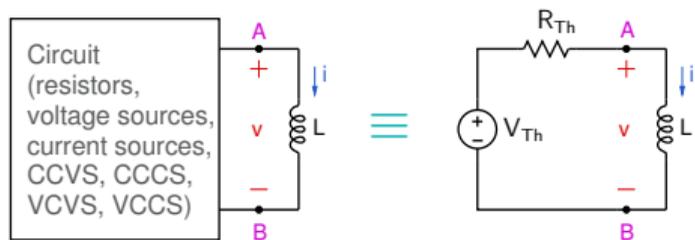\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

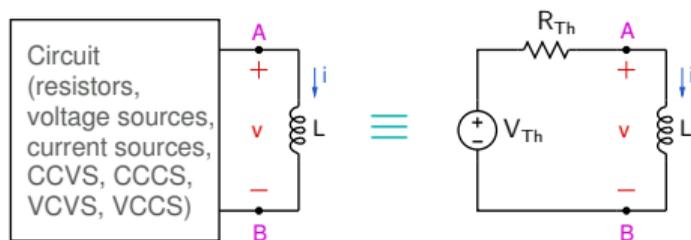\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .




\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .

\* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$
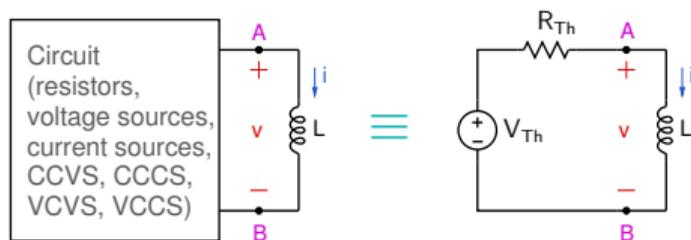
$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .


\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .

\* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

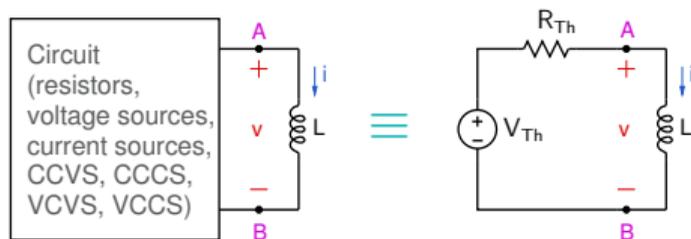\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $v = 0$ , and we get  $i^{(p)} = V_{Th}/R_{Th}$  as a particular solution (which happens to be simply a constant).



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .


\* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $v = 0$ , and we get  $i^{(p)} = V_{Th}/R_{Th}$  as a particular solution (which happens to be simply a constant).

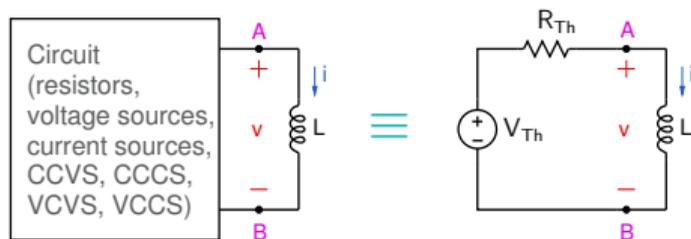\*  $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$ .



\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .

\* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$


$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $v = 0$ , and we get  $i^{(p)} = V_{Th}/R_{Th}$  as a particular solution (which happens to be simply a constant).


\*  $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$ .

\* In general,  $i(t) = A \exp(-t/\tau) + B$ , where  $A$  and  $B$  can be obtained from known conditions on  $i$ .
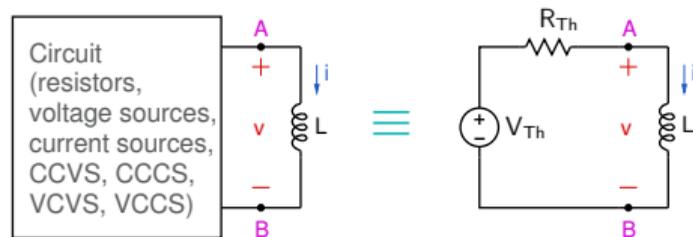
## RL circuits with DC sources (continued)



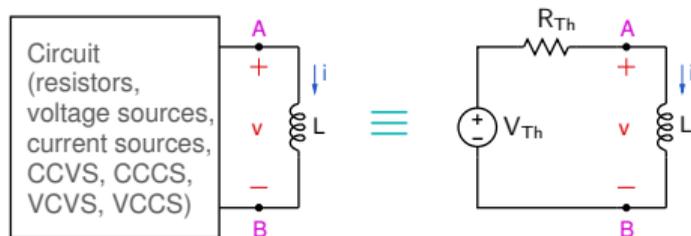- \* If all sources are DC (constant), we have  $i(t) = A \exp(-t/\tau) + B$ ,  $\tau = L/R_{Th}$ .




- \* If all sources are DC (constant), we have


$$i(t) = A \exp(-t/\tau) + B, \quad \tau = L/R_{Th}.$$

- \*  $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau).$
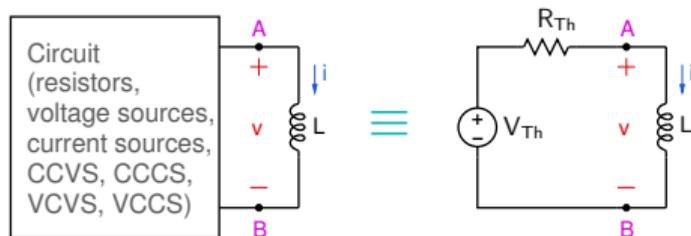
## RL circuits with DC sources (continued)





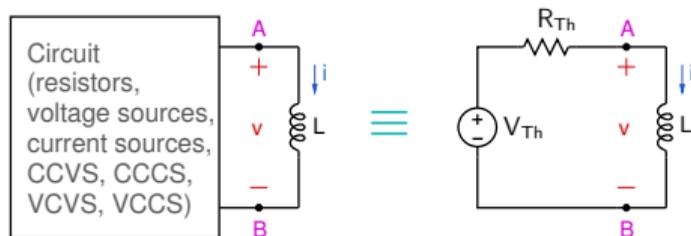- \* If all sources are DC (constant), we have  $i(t) = A \exp(-t/\tau) + B$ ,  $\tau = L/R_{Th}$ .
- \*  $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $v \rightarrow 0$ , i.e., the inductor behaves like a short circuit since all derivatives vanish.




- \* If all sources are DC (constant), we have  $i(t) = A \exp(-t/\tau) + B$ ,  $\tau = L/R_{Th}$ .
- \*  $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $v \rightarrow 0$ , i.e., the inductor behaves like a short circuit since all derivatives vanish.
- \* Since the circuit in the black box is linear, *any* variable (current or voltage) in the circuit can be expressed as  $x(t) = K_1 \exp(-t/\tau) + K_2$ , where  $K_1$  and  $K_2$  can be obtained from suitable conditions on  $x(t)$ .
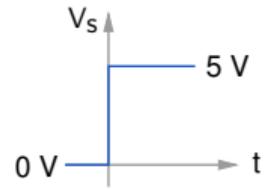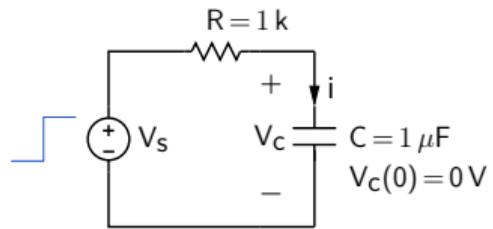
## RC circuits: Can $V_C$ change “suddenly?”



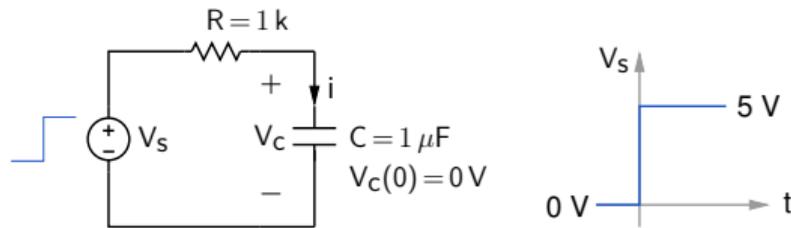
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
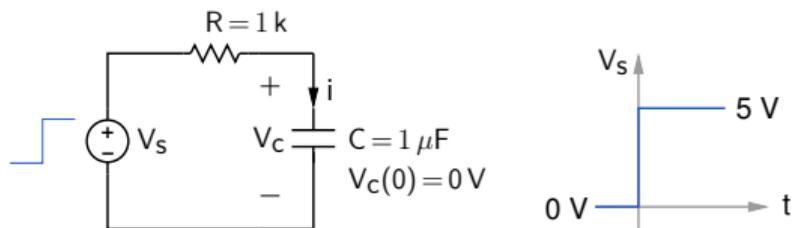
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\text{ }\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
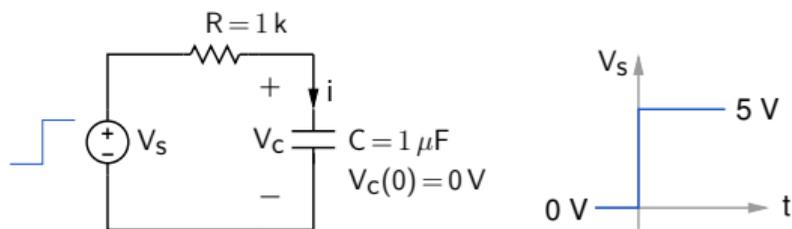
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\text{ }\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$ .
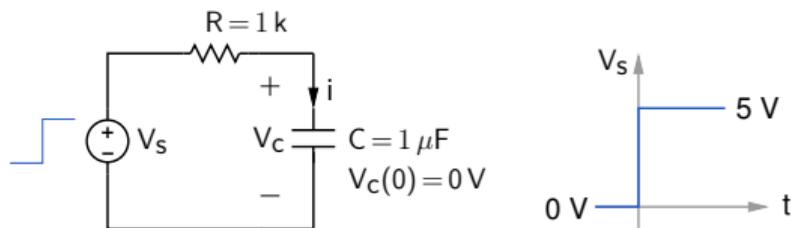
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\text{ }\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$ .
- \* With  $i = 1\text{ A}$ , the voltage drop across  $R$  would be 1000 V! Not allowed by KVL.
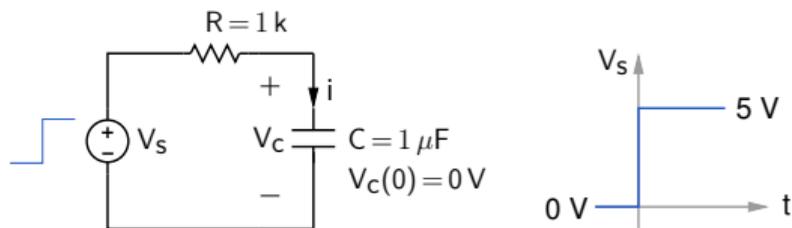
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\ \mu\text{s}$  at a constant rate of  $1\text{ V}/1\ \mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\ \mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$ .
- \* With  $i = 1\text{ A}$ , the voltage drop across  $R$  would be 1000 V! Not allowed by KVL.
- \* We conclude that  $V_C(0^+) = V_C(0^-) \Rightarrow$  A capacitor does not allow abrupt changes in  $V_C$  if there is a finite resistance in the circuit.
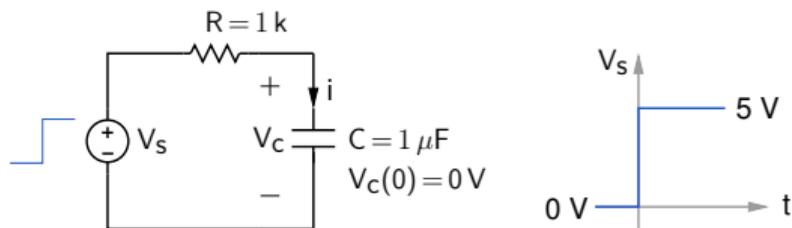
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from  $0\text{ V}$  (at  $t = 0^-$ ), to  $5\text{ V}$  (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by  $1\text{ V}$  in  $1\ \mu\text{s}$  at a constant rate of  $1\text{ V}/1\ \mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\ \mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$ .
- \* With  $i = 1\text{ A}$ , the voltage drop across  $R$  would be  $1000\text{ V}$ ! Not allowed by KVL.
- \* We conclude that  $V_C(0^+) = V_C(0^-) \Rightarrow$  A capacitor does not allow abrupt changes in  $V_C$  if there is a finite resistance in the circuit.
- \* Similarly, an inductor does not allow abrupt changes in  $i_L$ .
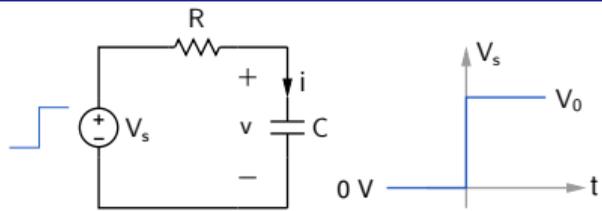
## RC circuits: charging and discharging transients



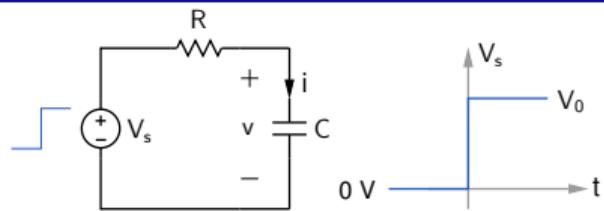
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$
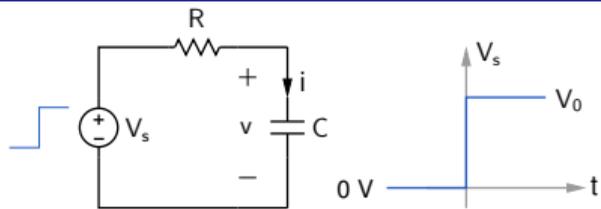
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$


$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$
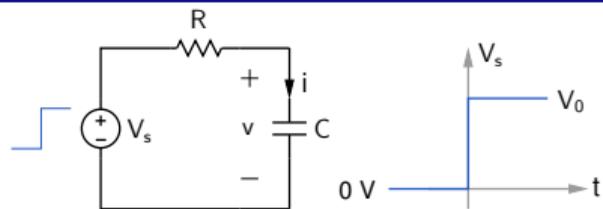
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$
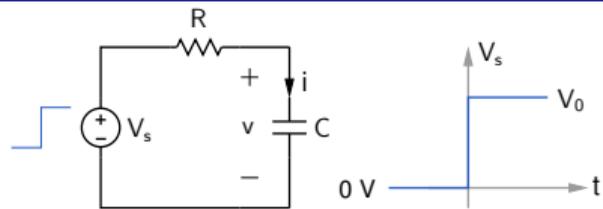
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$

Imposing (1) and (2) on Eq. (A), we get


$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$
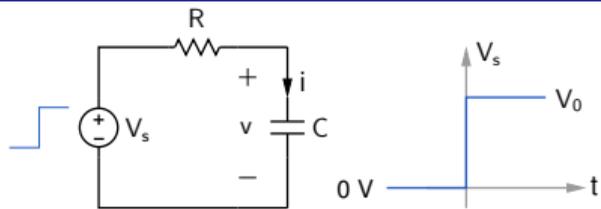
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$


$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

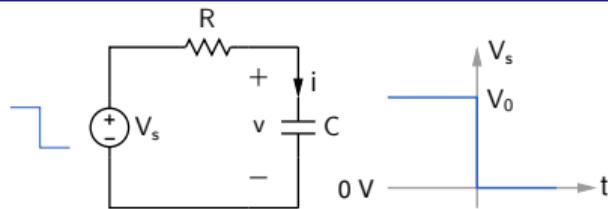
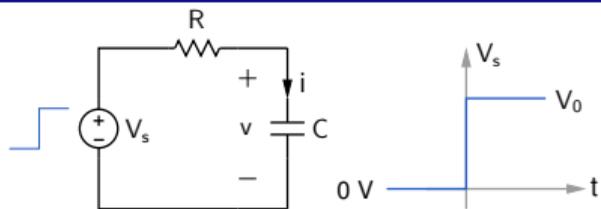
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$


$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

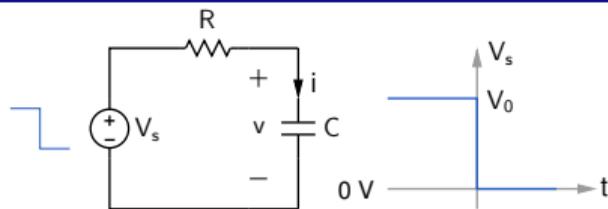

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$
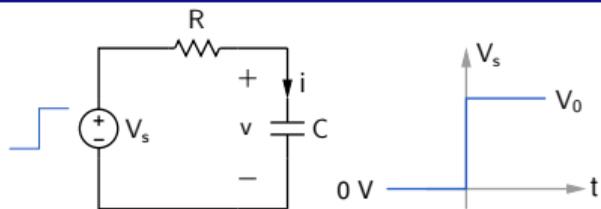
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

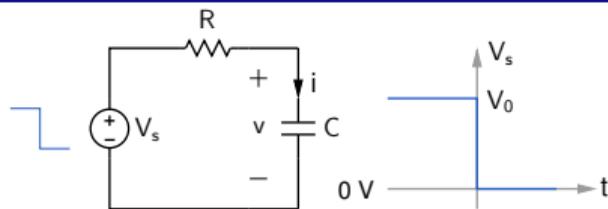

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) v(0^-) = V_S(0^-) = V_0$$


$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$
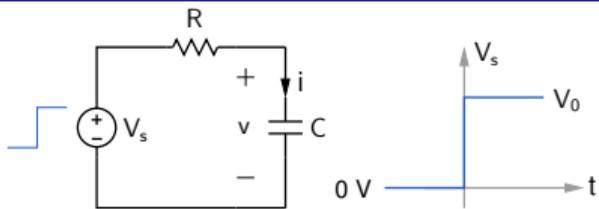
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

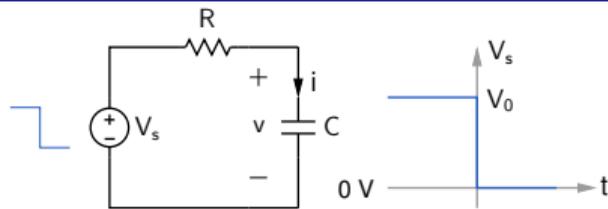

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_S(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: V_0 = A + B,$$

$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$
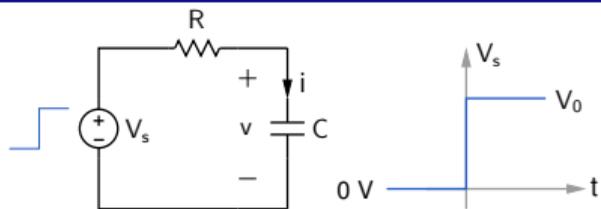
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) v(0^-) = V_S(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } B = V_0, A = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

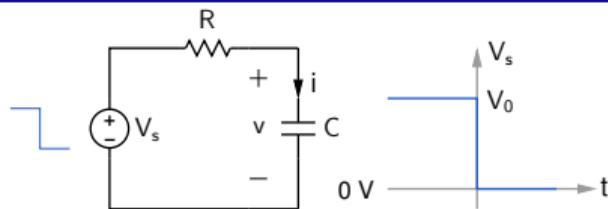

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) v(0^-) = V_S(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \text{ As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_S(\infty) = 0 \text{ V}$$

Imposing (1) and (2) on Eq. (A), we get


$$t = 0^+: V_0 = A + B,$$

$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$


$$v(t) = V_0 \exp(-t/\tau)$$
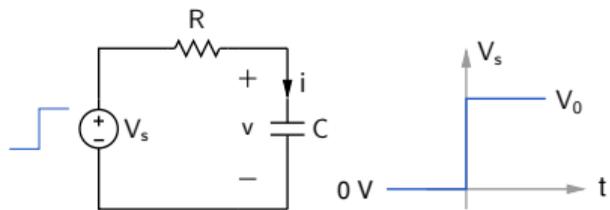
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

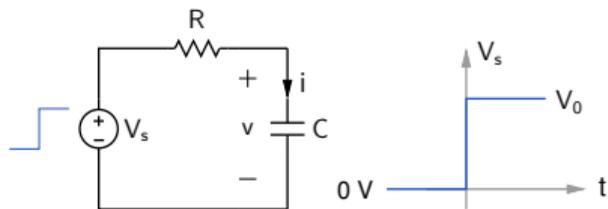
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A) } i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$
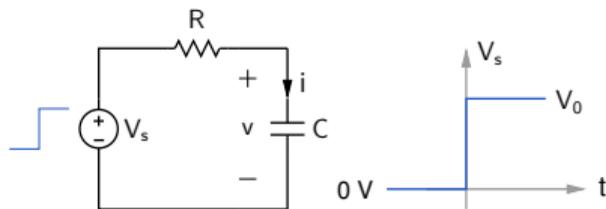
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
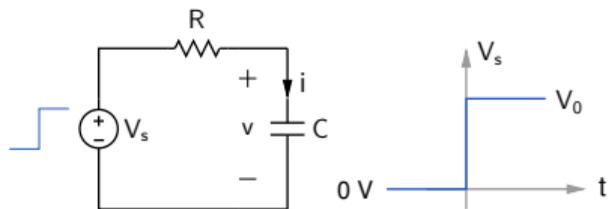
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$


$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
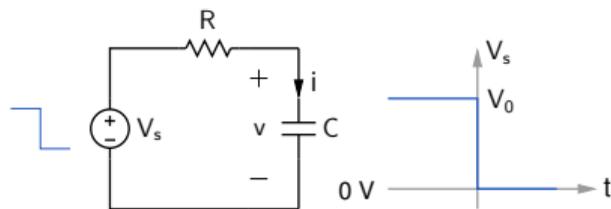
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute  $i(t)$ ,  $t > 0$ .

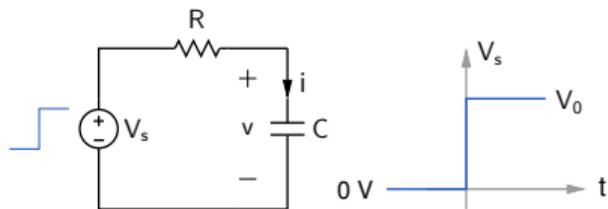

Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$


Using these conditions, we obtain
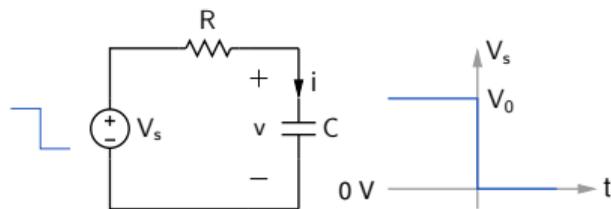
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute  $i(t)$ ,  $t > 0$ .
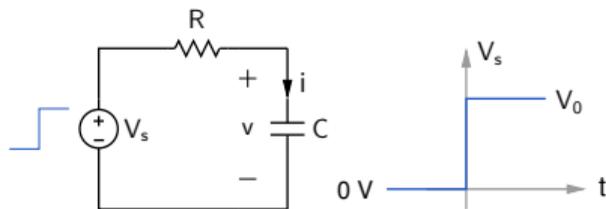
$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
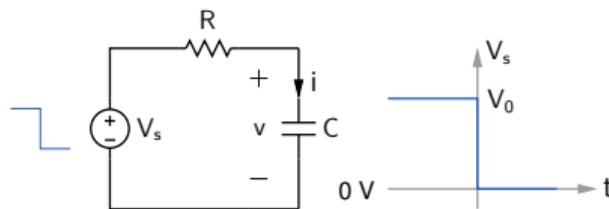
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .


$$t = 0^+: v = V_0, V_s = 0 \Rightarrow i(0^+) = -V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

$$A' = -\frac{V_0}{R}, B' = 0 \Rightarrow i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

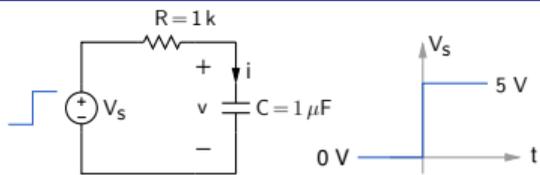
## RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$
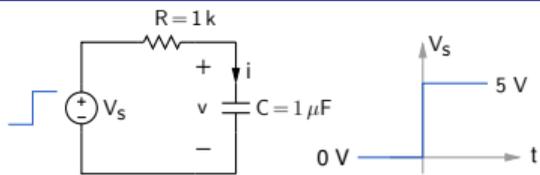
## RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$


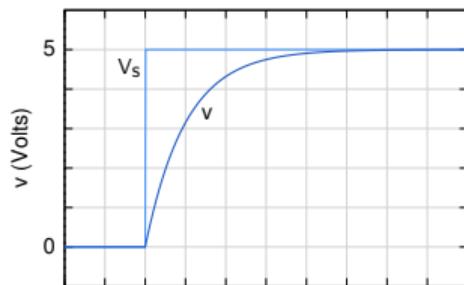

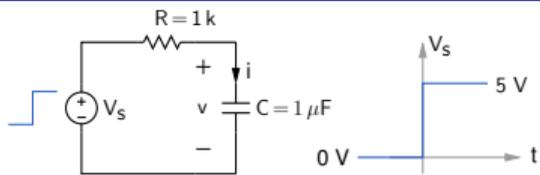
## RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$


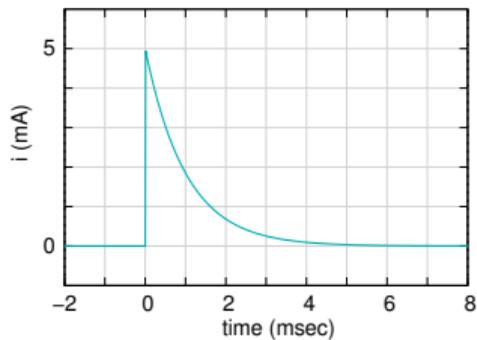
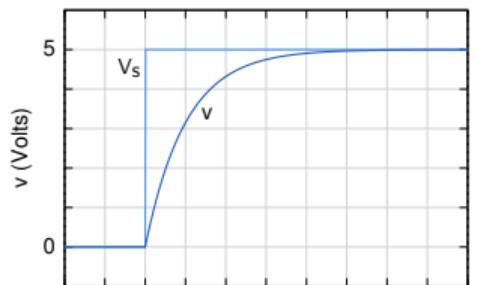

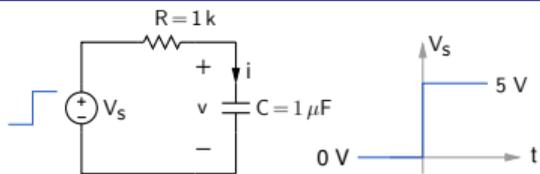
# RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

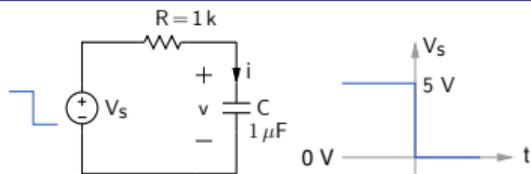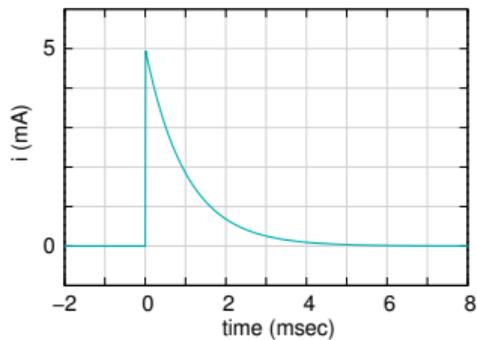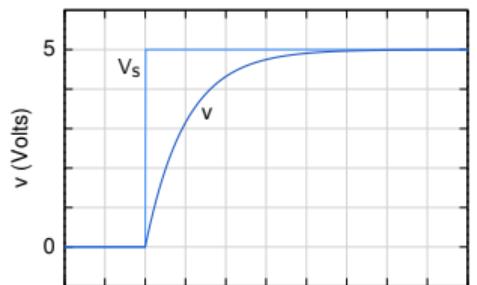

$$v(t) = V_0 \exp(-t/\tau)$$




$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$
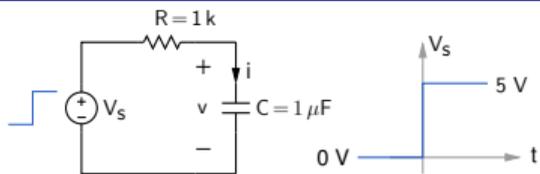
# RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

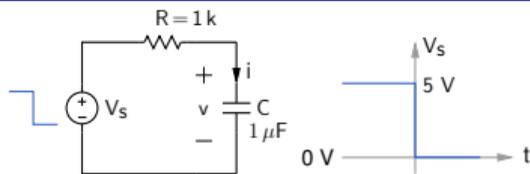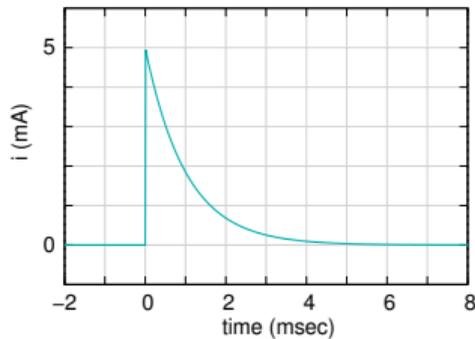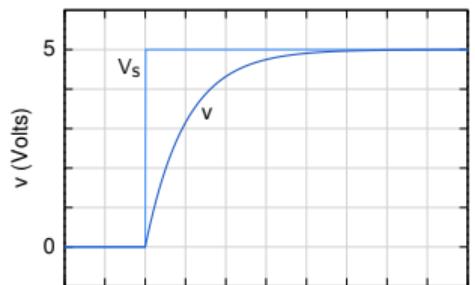


$$v(t) = V_0 \exp(-t/\tau)$$

$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$



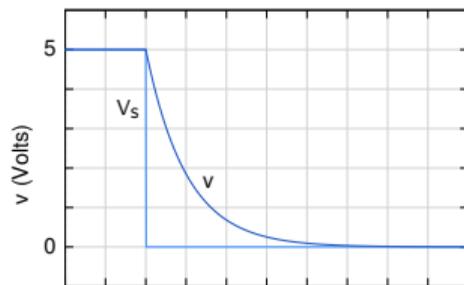

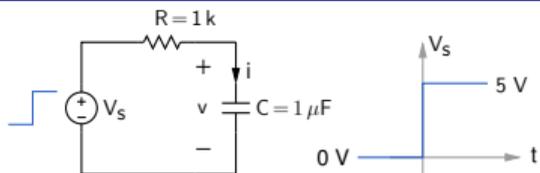
# RC circuits: charging and discharging transients





$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

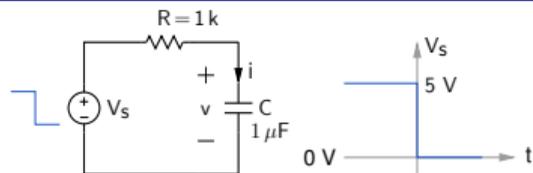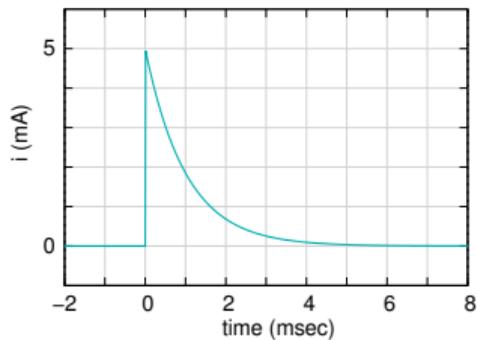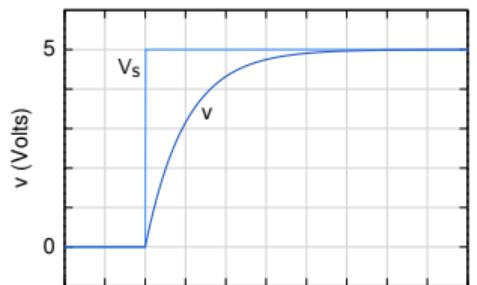


$$v(t) = V_0 \exp(-t/\tau)$$



$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

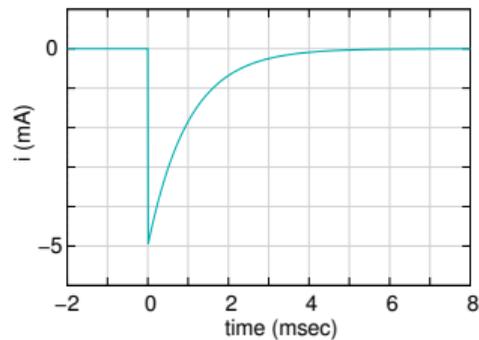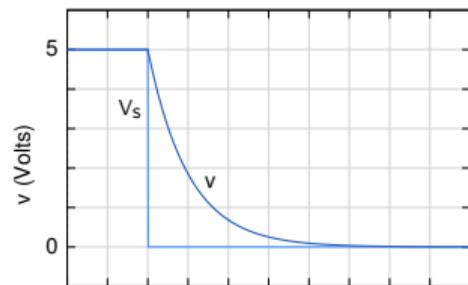

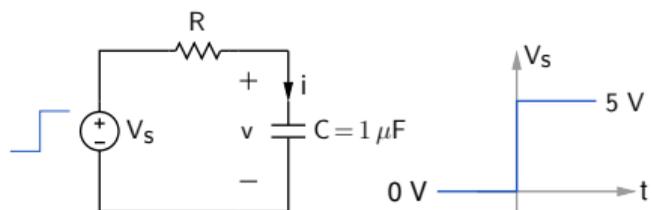
# RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

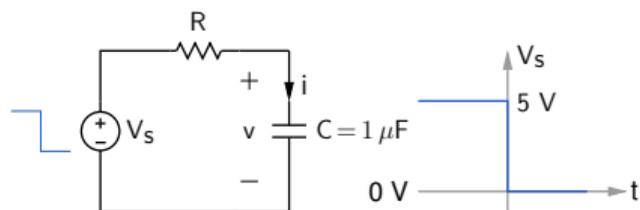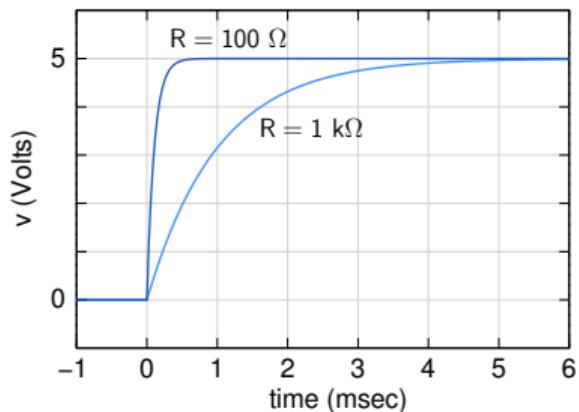


$$v(t) = V_0 \exp(-t/\tau)$$

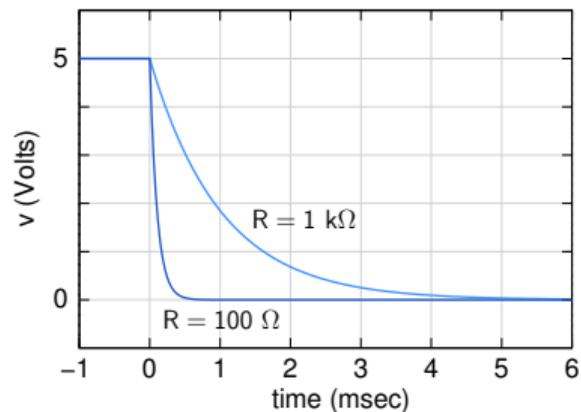

\* Identify intervals in which the source voltages/currents are constant.

For example,

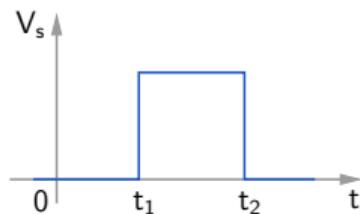


(1)  $t < t_1$

(2)  $t_1 < t < t_2$

(3)  $t > t_2$

- \* Identify intervals in which the source voltages/currents are constant.

For example,

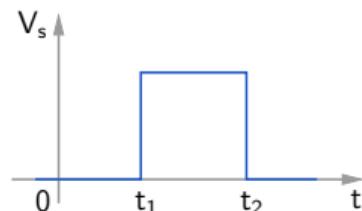

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- \* For *any* current or voltage  $x(t)$ , write general expressions such as,


$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- \* Identify intervals in which the source voltages/currents are constant.

For example,

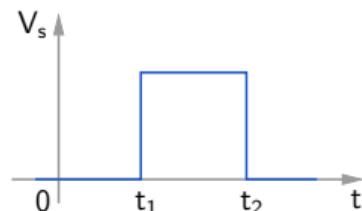

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- \* For any current or voltage  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$


$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- \* Work out suitable conditions on  $x(t)$  at specific time points using

- \* Identify intervals in which the source voltages/currents are constant.

For example,

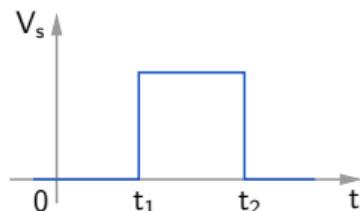

- (1)  $t < t_1$
- (2)  $t_1 < t < t_2$
- (3)  $t > t_2$

- \* For any current or voltage  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$


- \* Work out suitable conditions on  $x(t)$  at specific time points using

- (a) If the source voltage/current has not changed for a "long" time (long compared to  $\tau$ ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$

- \* Identify intervals in which the source voltages/currents are constant.

For example,

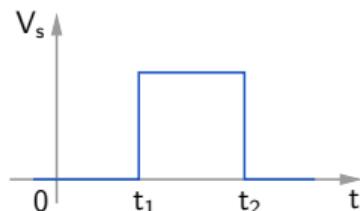

- (1)  $t < t_1$
- (2)  $t_1 < t < t_2$
- (3)  $t > t_2$

- \* For any current or voltage  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- \* Work out suitable conditions on  $x(t)$  at specific time points using

- If the source voltage/current has not changed for a “long” time (long compared to  $\tau$ ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$


- When a source voltage (or current) changes, say, at  $t = t_0$ ,

$V_C(t)$  or  $i_L(t)$  cannot change abruptly, i.e.,

$$V_C(t_0^+) = V_C(t_0^-), \text{ and } i_L(t_0^+) = i_L(t_0^-).$$

- \* Identify intervals in which the source voltages/currents are constant.

For example,

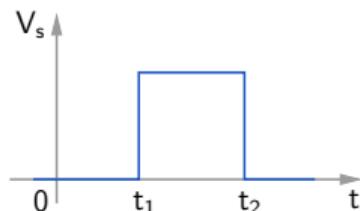

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- \* For any current or voltage  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- \* Work out suitable conditions on  $x(t)$  at specific time points using

- If the source voltage/current has not changed for a “long” time (long compared to  $\tau$ ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$


- When a source voltage (or current) changes, say, at  $t = t_0$ ,

$V_C(t)$  or  $i_L(t)$  cannot change abruptly, i.e.,


$$V_C(t_0^+) = V_C(t_0^-), \text{ and } i_L(t_0^+) = i_L(t_0^-).$$

- \* Compute  $A_1, B_1, \dots$  using the conditions on  $x(t)$ .

## RL circuit: example

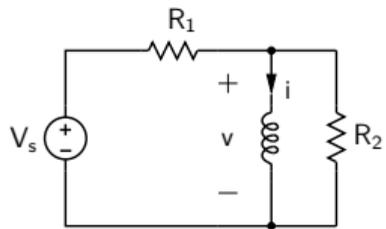

Find  $i(t)$ .

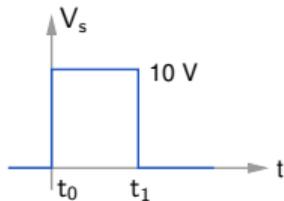

$$R_1 = 10 \Omega$$



$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

## RL circuit: example

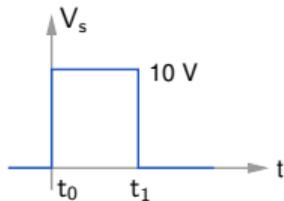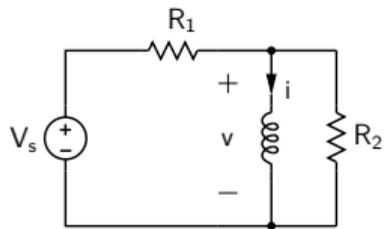

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find  $i(t)$ .



There are three intervals of constant  $V_s$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

(3)  $t > t_1$

## RL circuit: example

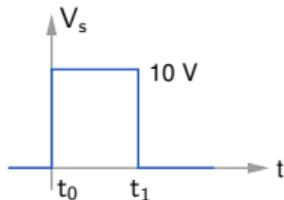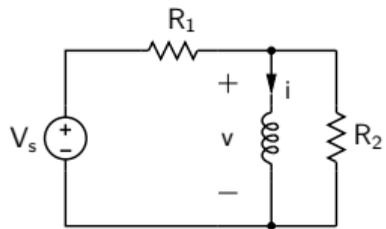

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find  $i(t)$ .


There are three intervals of constant  $V_s$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

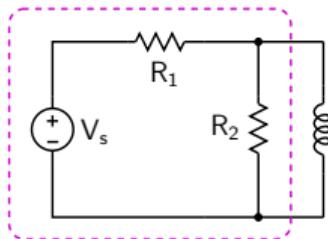(3)  $t > t_1$



$R_{Th}$  seen by  $L$  is the same in all intervals:



$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

## RL circuit: example

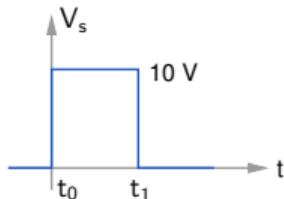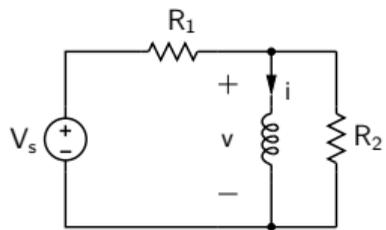

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find  $i(t)$ .


There are three intervals of constant  $V_s$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

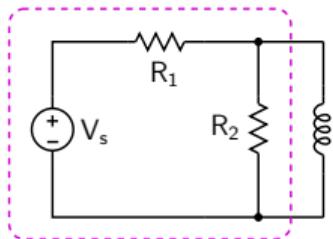(3)  $t > t_1$

$R_{Th}$  seen by L is the same in all intervals:





$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At  $t = t_0^-$ ,  $v = 0 \text{ V}$ ,  $V_s = 0 \text{ V}$ .

$\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$ .

## RL circuit: example

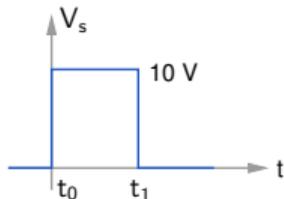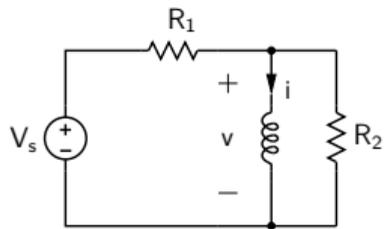

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find  $i(t)$ .


There are three intervals of constant  $V_s$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

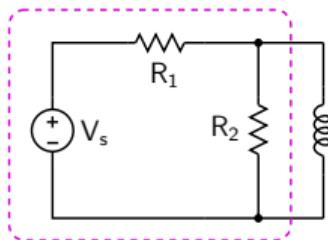(3)  $t > t_1$

$R_{Th}$  seen by L is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$



At  $t = t_0^-$ ,  $v = 0 \text{ V}$ ,  $V_s = 0 \text{ V}$ .  
 $\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$ .

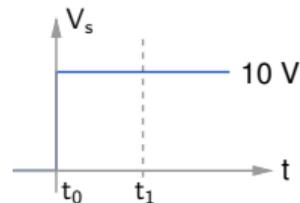If  $V_s$  did not change at  $t = t_1$ ,  
we would have



$v(\infty) = 0 \text{ V}$ ,  $i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}$ .

## RL circuit: example

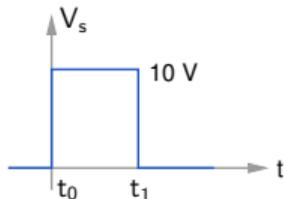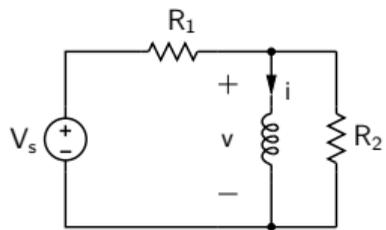

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

Find  $i(t)$ .


There are three intervals of constant  $V_s$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

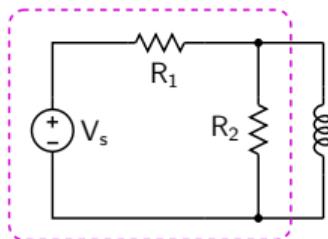(3)  $t > t_1$

$R_{Th}$  seen by  $L$  is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At  $t = t_0^-$ ,  $v = 0 \text{ V}$ ,  $V_s = 0 \text{ V}$ .  
 $\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$ .


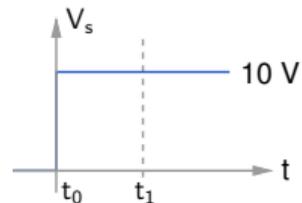
If  $V_s$  did not change at  $t = t_1$ ,  
we would have



$v(\infty) = 0 \text{ V}$ ,  $i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}$ .

Using  $i(t_0^+)$  and  $i(\infty)$ , we can obtain  
 $i(t)$ ,  $t > 0$  (See next slide).

# RL circuit: example

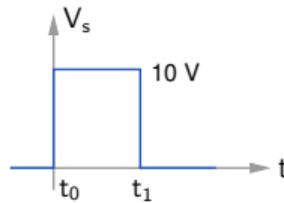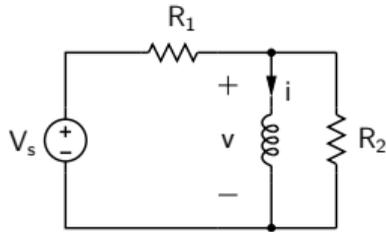


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$


$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$


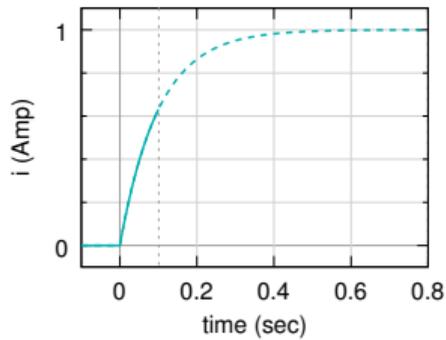


## RL circuit: example

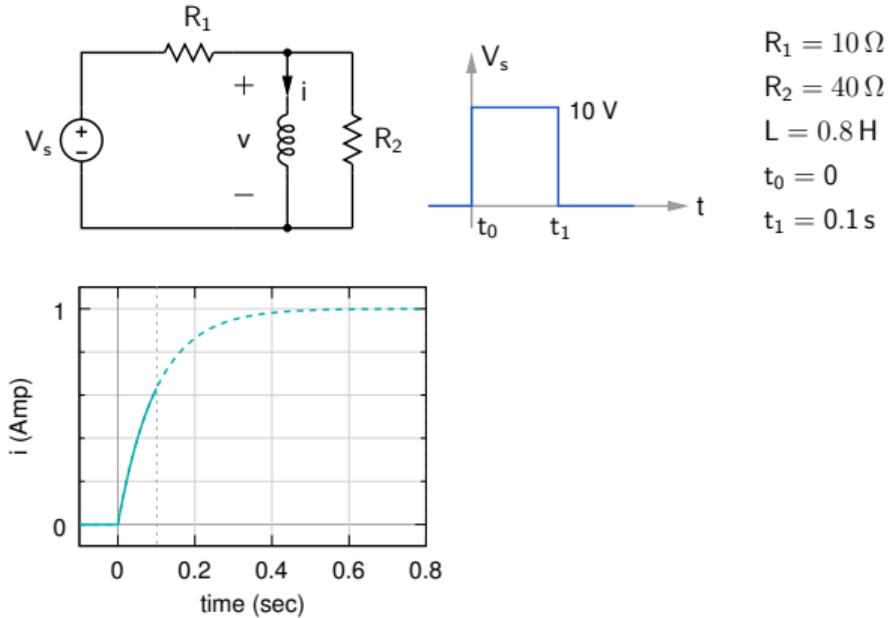

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

## RL circuit: example

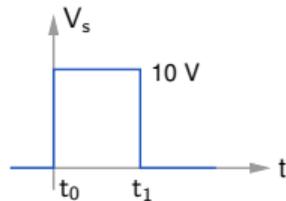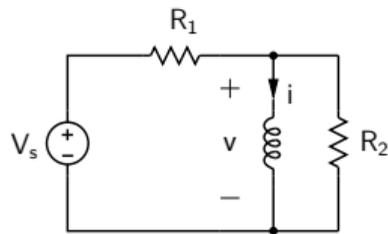


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$


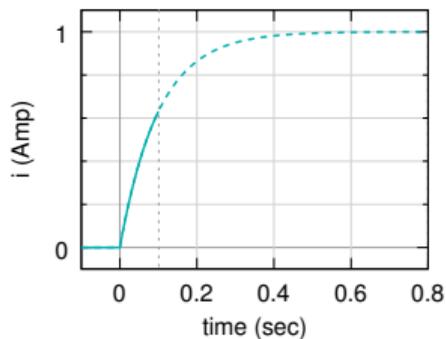


For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.

Consider  $t > t_1$ .

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

## RL circuit: example

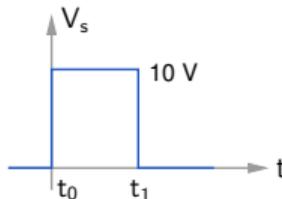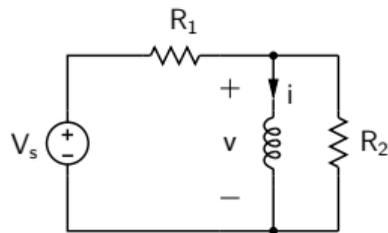


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

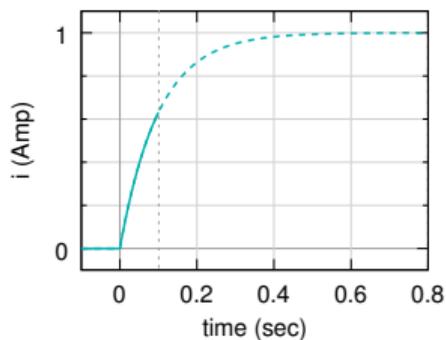

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.



For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.

Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

## RL circuit: example

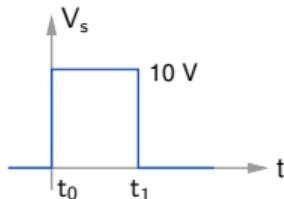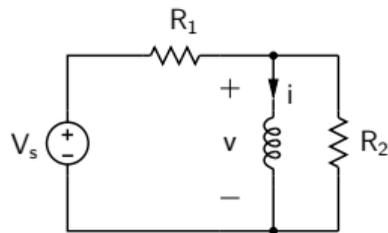


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

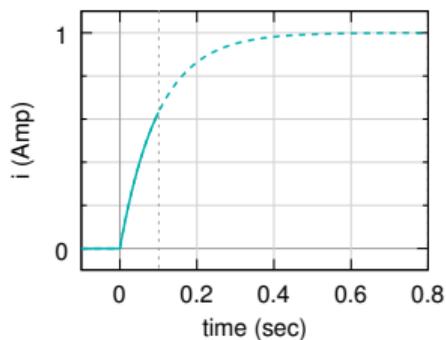

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.



Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

## RL circuit: example

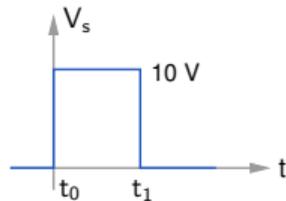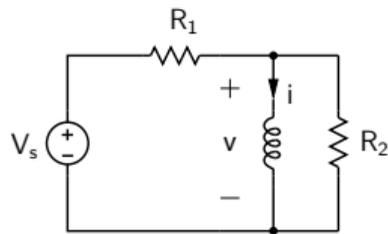


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

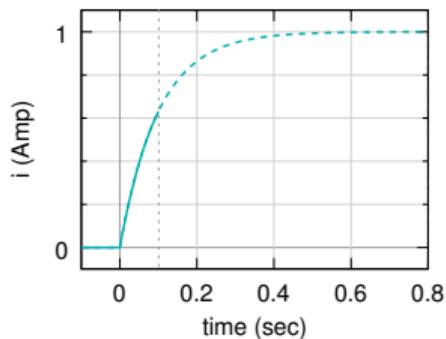

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.

Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$



$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

It is convenient to rewrite  $i(t)$  as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

## RL circuit: example

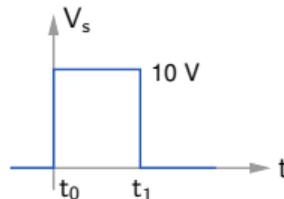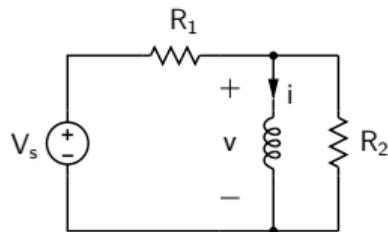


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

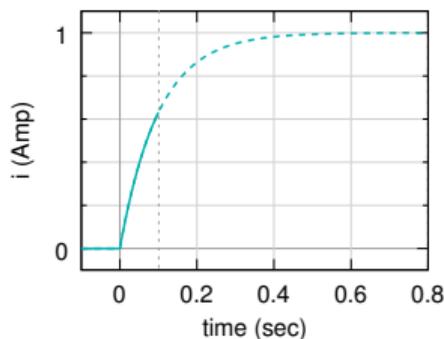

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.

Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$


It is convenient to rewrite  $i(t)$  as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

Using  $i(t_1^+)$  and  $i(\infty)$ , we get

$$i(t) = 0.632 \exp[-(t - t_1)/\tau] \text{ A.}$$

## RL circuit: example

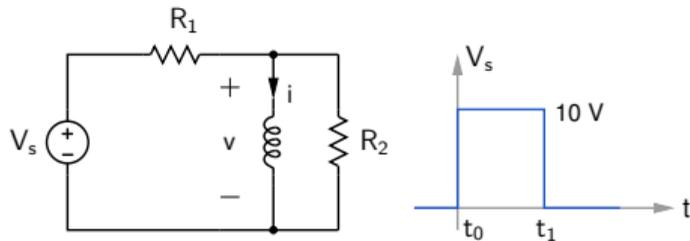

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$



$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
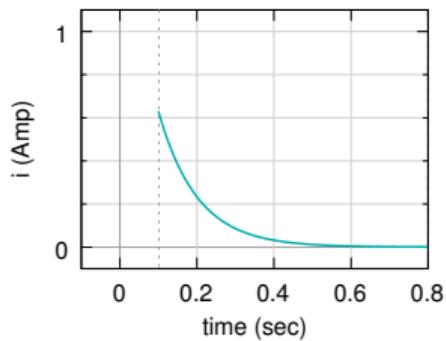
$$i(t) = 0.632 \exp[-(t - t_1)/\tau] \text{ A.}$$



## RL circuit: example

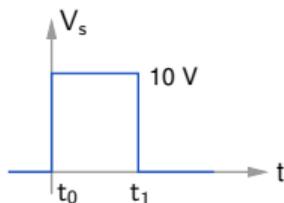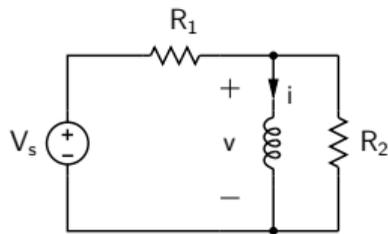

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$


$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
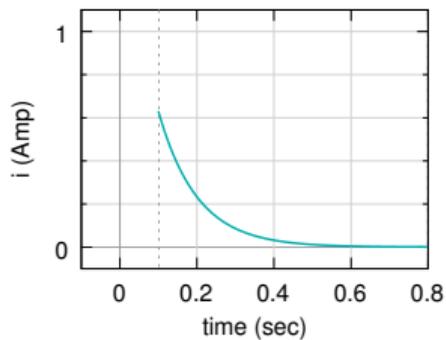
$$i(t) = 0.632 \exp[-(t - t_1)/\tau] \text{ A.}$$




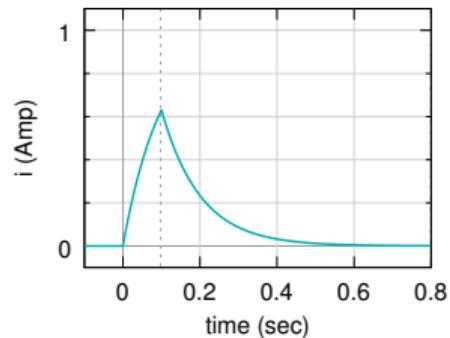Combining the solutions for  $t_0 < t < t_1$  and  $t > t_1$ , we get




(SEQUEL file: ee101\_rl1.sqproj)

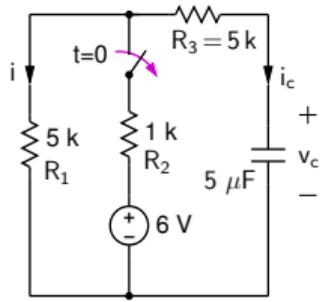
RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .



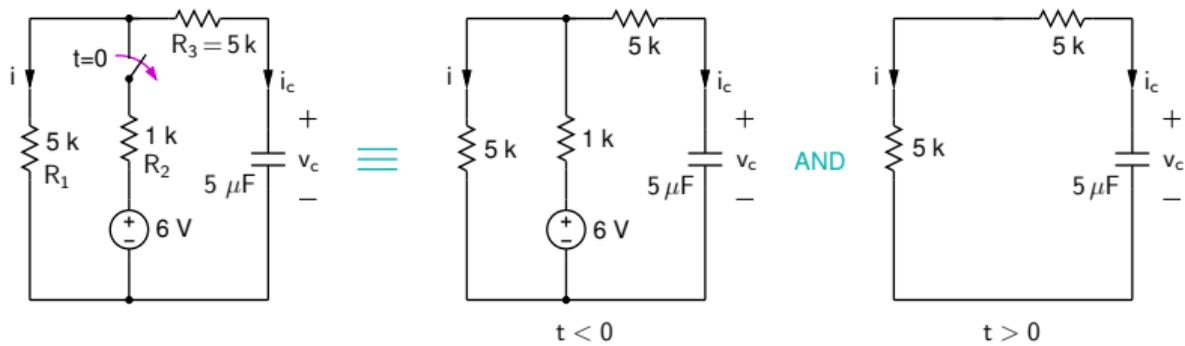RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .




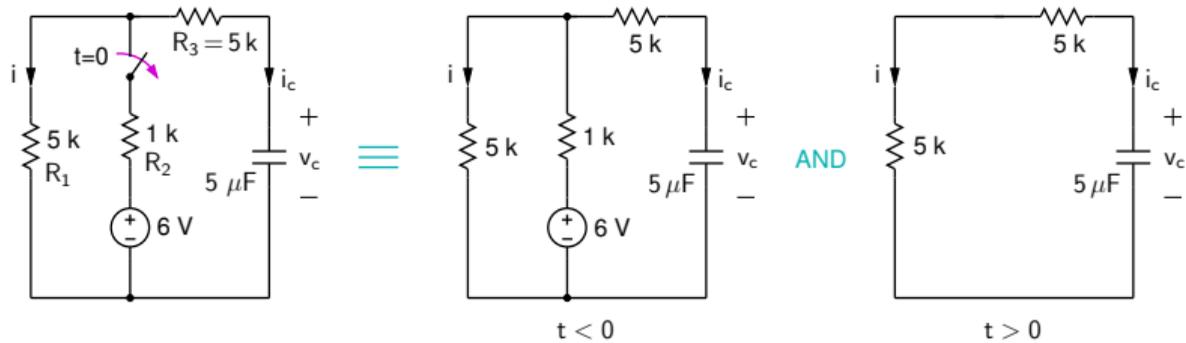RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .



$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

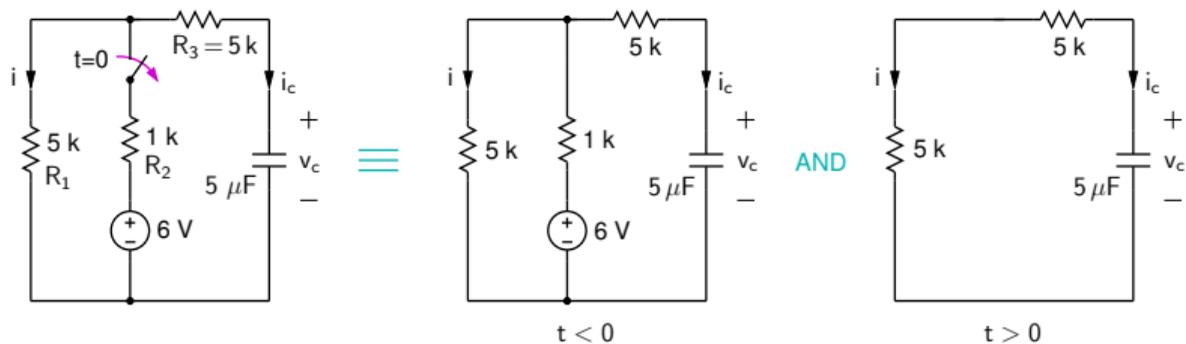
RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .



$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

$v_c(0^-) = i(0^-) R_1 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$

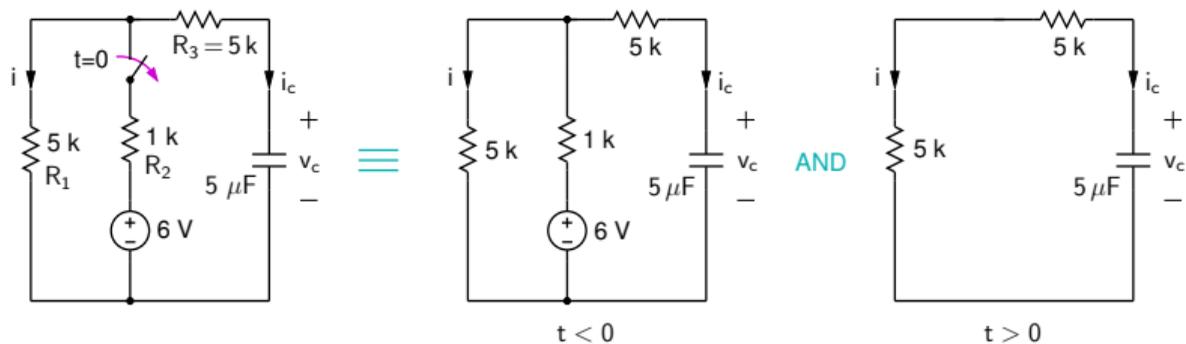RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .




$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

$v_c(0^-) = i(0^-) R_1 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .

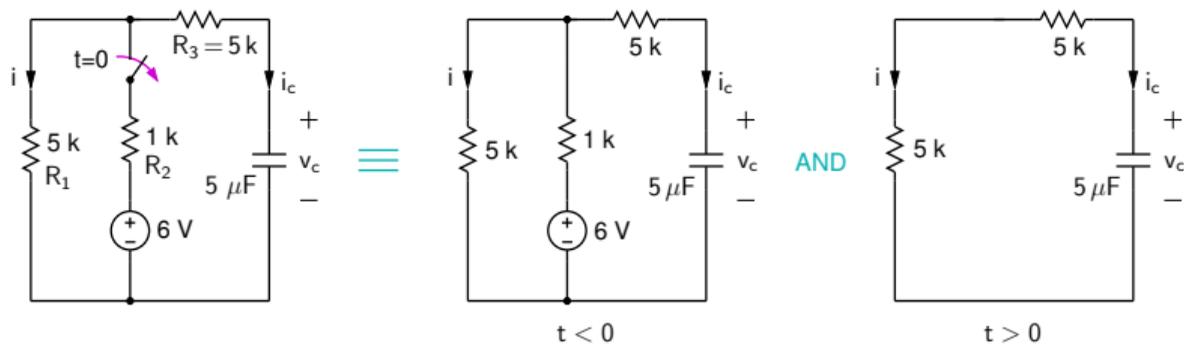RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .




$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

$v_c(0^-) = i(0^-) R_1 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .

Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$ .

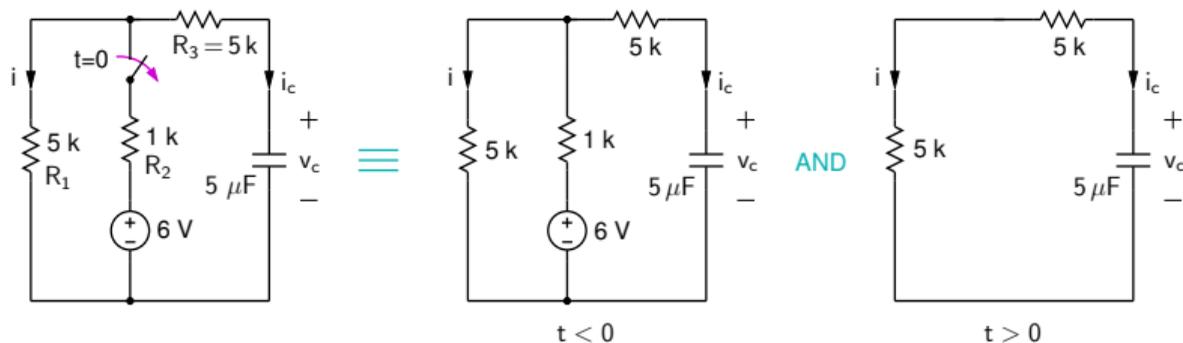RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .



$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

$v_c(0^-) = i(0^-) R_1 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$


$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .

Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$ .

Using  $i(0^+)$  and  $i(\infty) = 0 \text{ A}$ , we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$ .

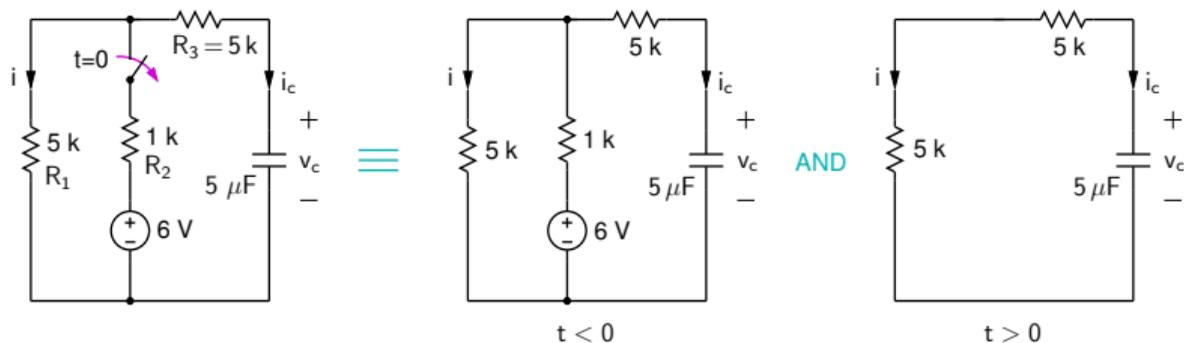RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .



$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .


$v_c(0^-) = i(0^-) R_1 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .


Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$ .

Using  $i(0^+)$  and  $i(\infty) = 0 \text{ A}$ , we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$ .

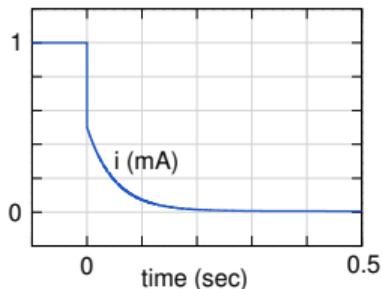

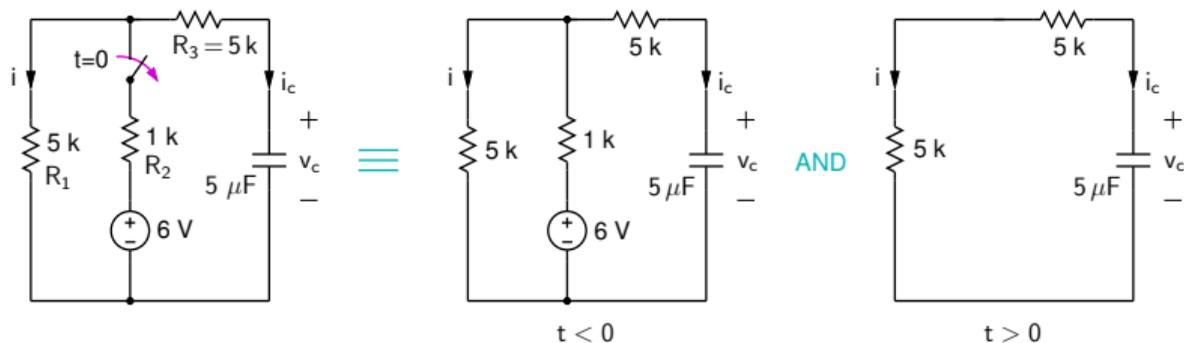RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .



$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6\text{ V}/(5\text{ k} + 1\text{ k}) = 1\text{ mA}$ .


$v_c(0^-) = i(0^-) R_1 = 5\text{ V} \Rightarrow v_c(0^+) = 5\text{ V}$

$\Rightarrow i(0^+) = 5\text{ V}/(5\text{ k} + 5\text{ k}) = 0.5\text{ mA}$ .


Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10\text{ k} \times 5\text{ }\mu\text{F} = 50\text{ ms}$ .

Using  $i(0^+)$  and  $i(\infty) = 0\text{ A}$ , we get

$i(t) = 0.5 \exp(-t/\tau)\text{ mA}$ .

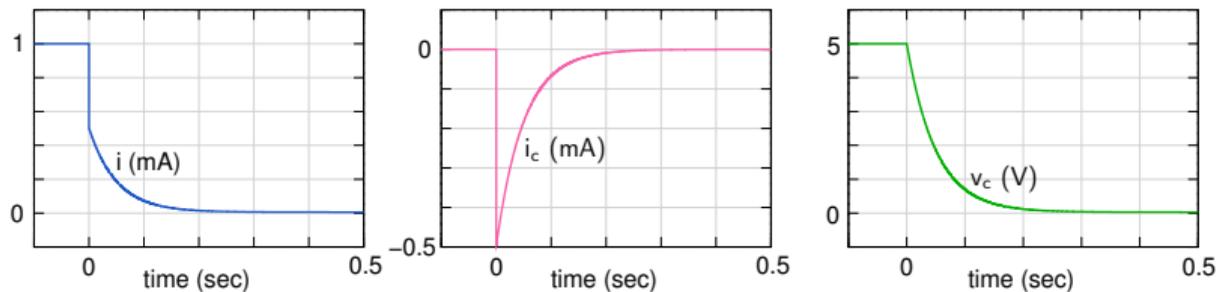

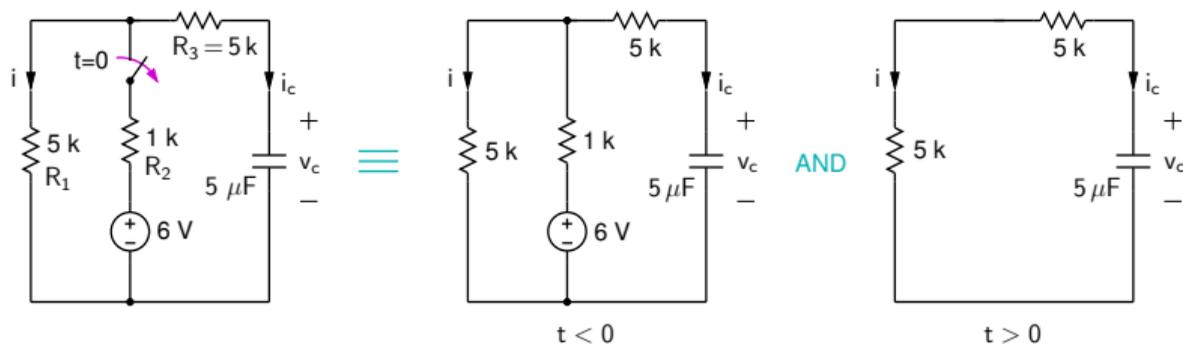RC circuit: The switch has been closed for a long time and opens at  $t = 0$ .



$t = 0^-$ : capacitor is an open circuit  $\Rightarrow i(0^-) = 6\ \text{V} / (5\ \text{k} + 1\ \text{k}) = 1\ \text{mA}$ .

$v_c(0^-) = i(0^-) R_1 = 5\ \text{V} \Rightarrow v_c(0^+) = 5\ \text{V}$




$\Rightarrow i(0^+) = 5\ \text{V} / (5\ \text{k} + 5\ \text{k}) = 0.5\ \text{mA}$ .

Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10\ \text{k} \times 5\ \mu\text{F} = 50\ \text{ms}$ .



Using  $i(0^+)$  and  $i(\infty) = 0\ \text{A}$ , we get

$i(t) = 0.5 \exp(-t/\tau)\ \text{mA}$ .


(SEQUEL file: ee101\_rc2.sqproj)

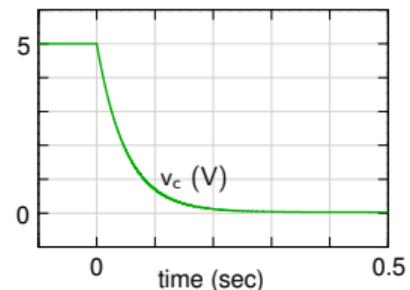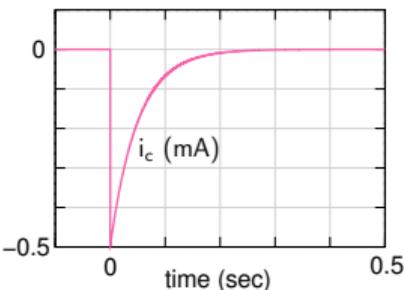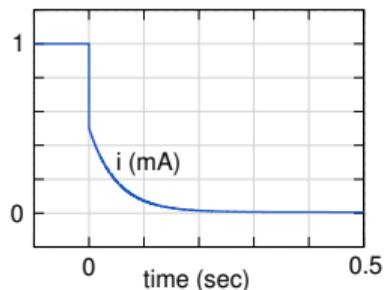



## RC circuit: example

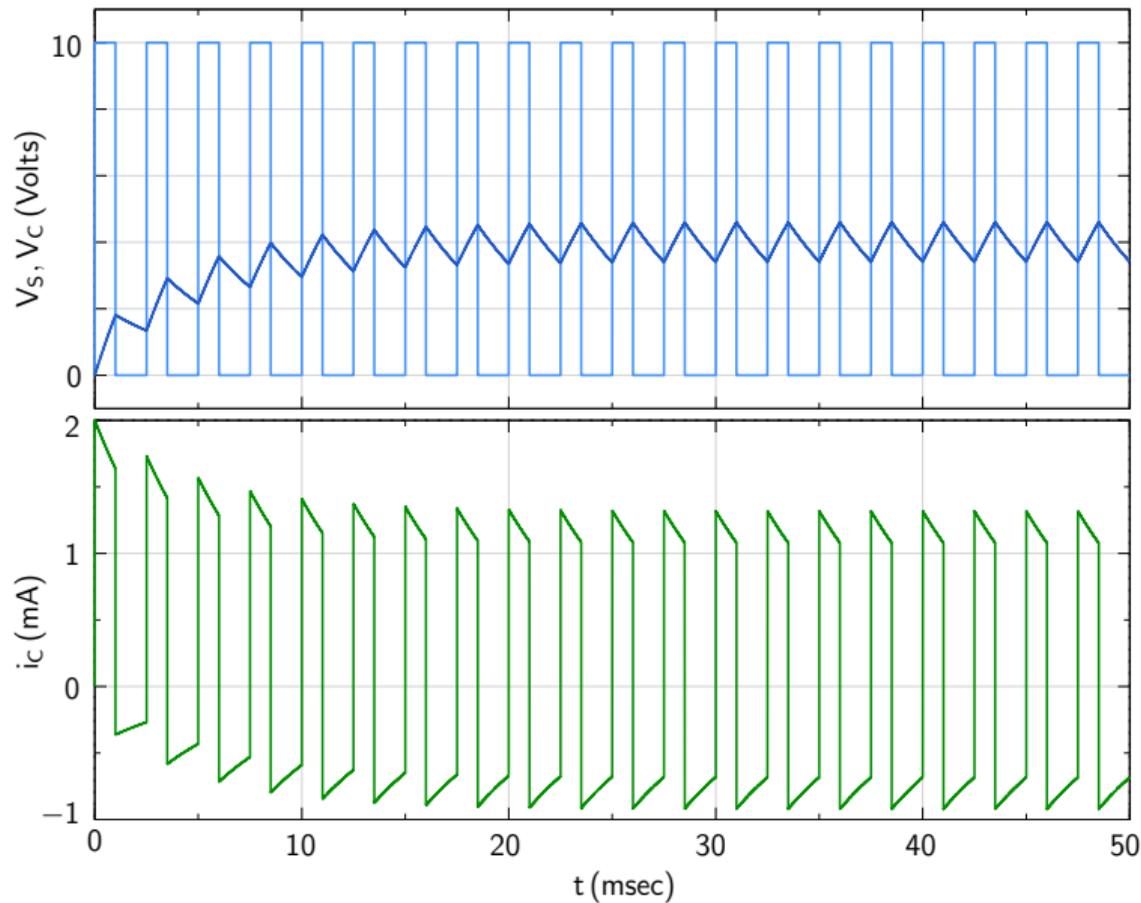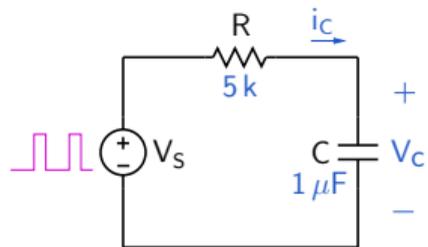




## RC circuit: example

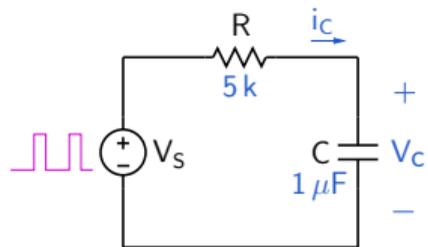


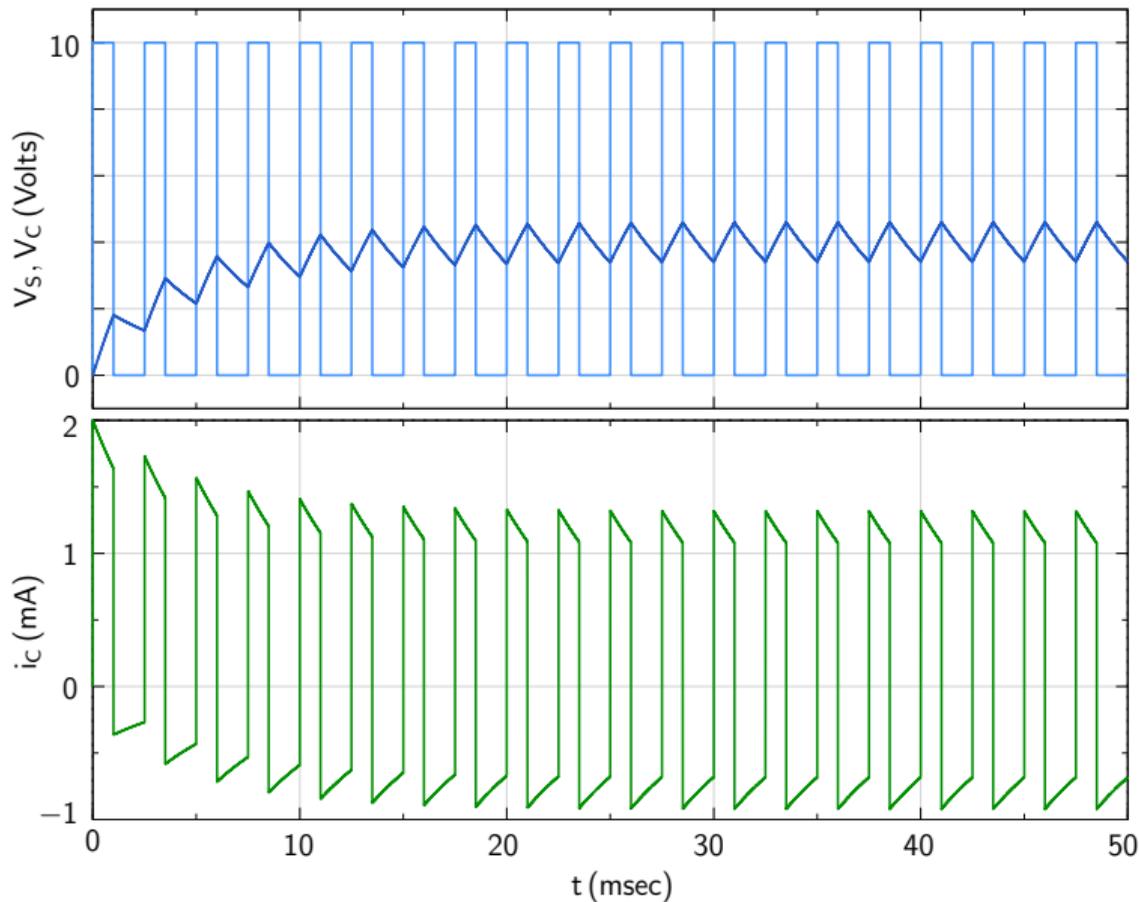
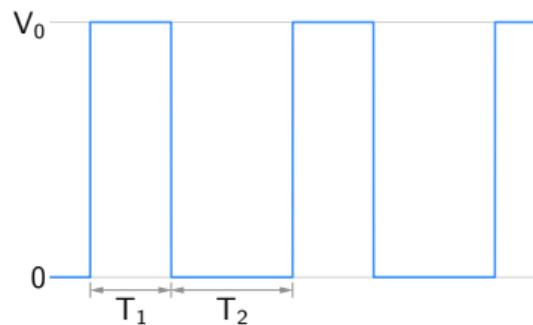
Find expressions for  $V_C(t)$  and  $i_C(t)$  in steady state (in terms of  $R$ ,  $C$ ,  $V_0$ ,  $T_1$ ,  $T_2$ ).



## RC circuit: example

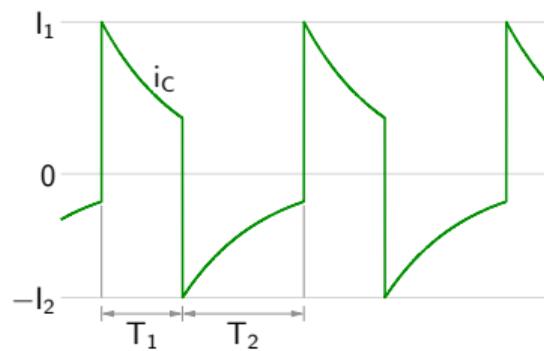
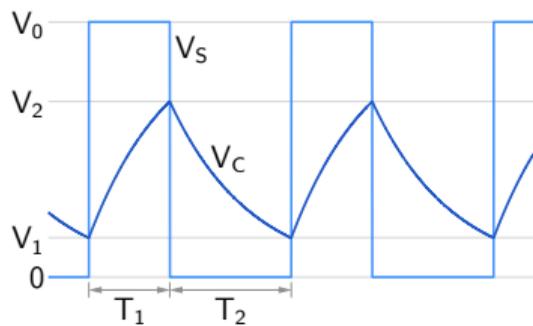
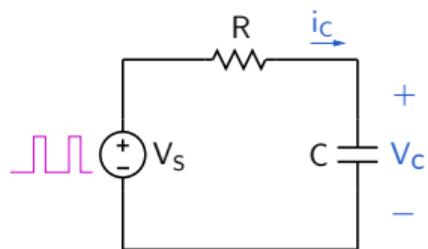


# RC circuit: example

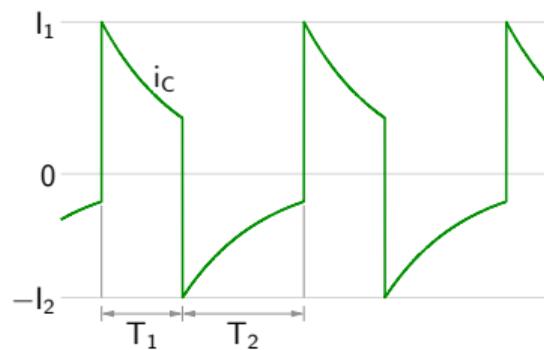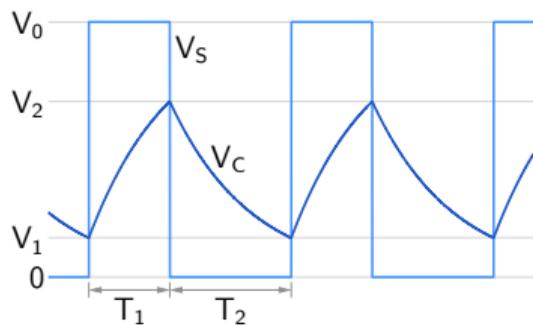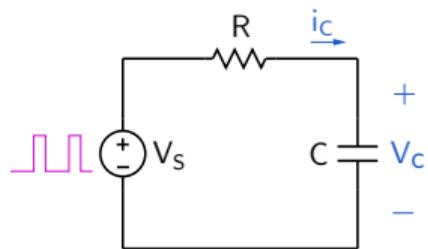

$0 < t < T_1$  Let  $V_C^{(1)}(t) = A e^{-t/\tau} + B$




## RC circuit: example

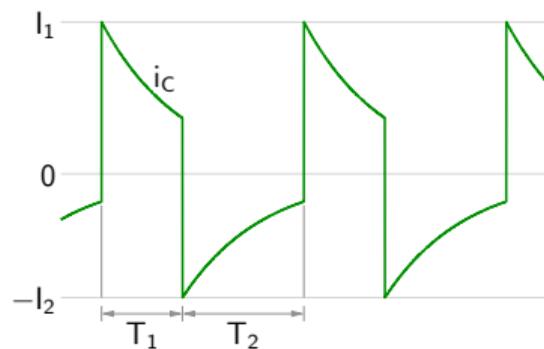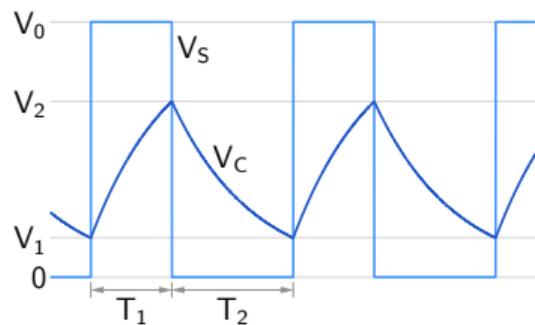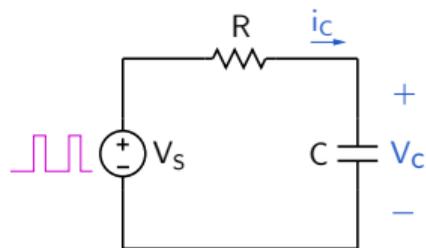

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

## RC circuit: example

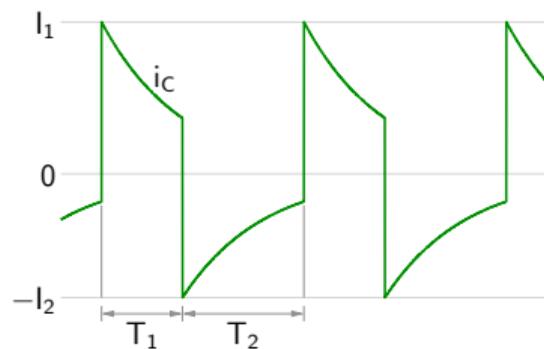
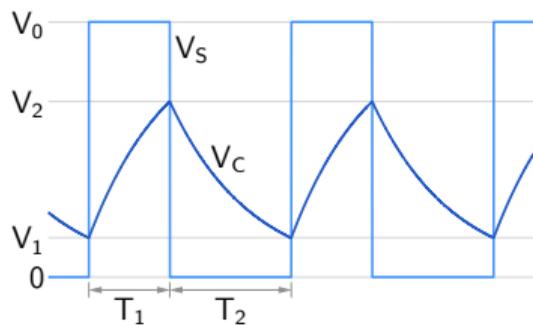
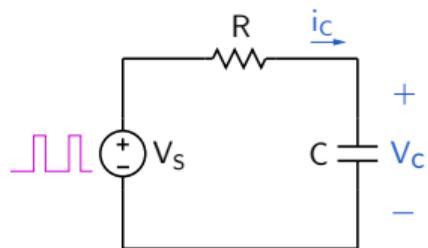


$0 < t < T_1$  Let  $V_C^{(1)}(t) = A e^{-t/\tau} + B$

$V_C^{(1)}(0) = V_1, V_C^{(1)}(\infty) = V_0$

$\rightarrow B = V_0, A = V_1 - V_0.$

# RC circuit: example

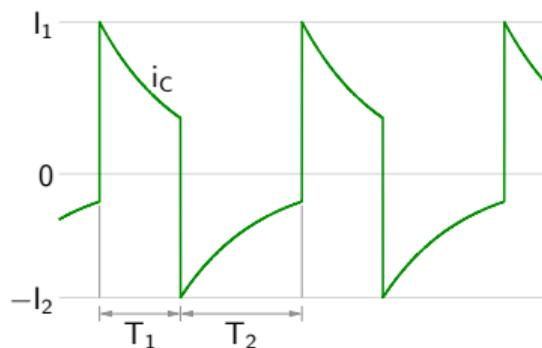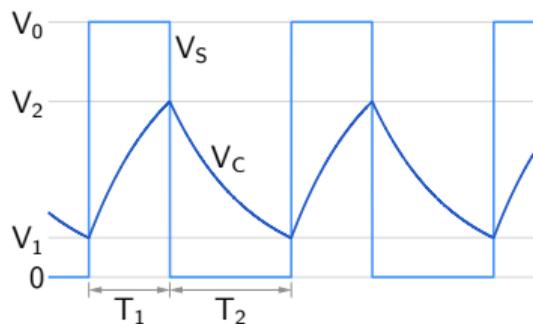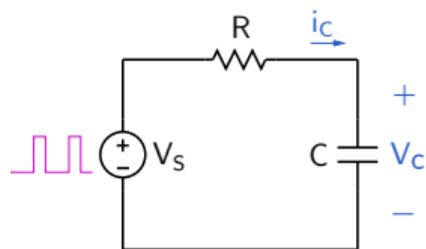




$0 < t < T_1$  Let  $V_C^{(1)}(t) = A e^{-t/\tau} + B$

$V_C^{(1)}(0) = V_1, V_C^{(1)}(\infty) = V_0$

$\rightarrow B = V_0, A = V_1 - V_0.$

$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$

# RC circuit: example

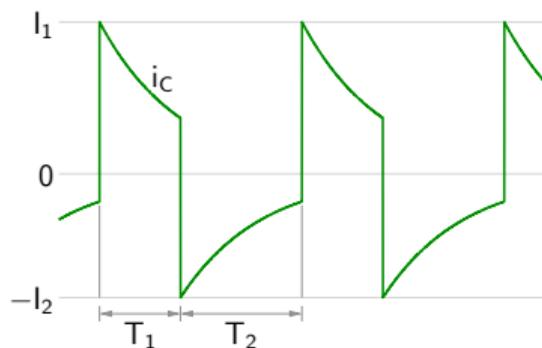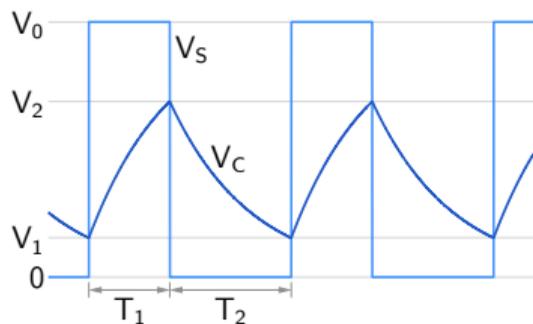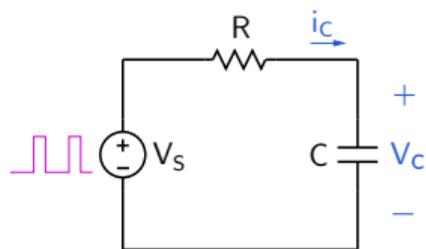

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$




$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

# RC circuit: example

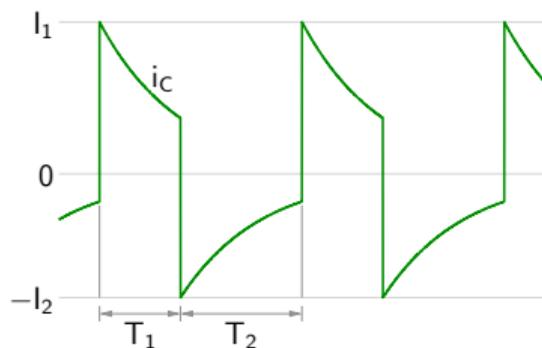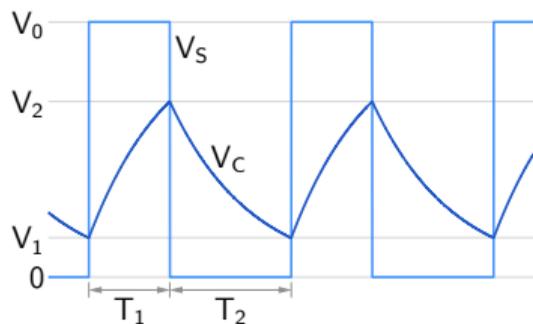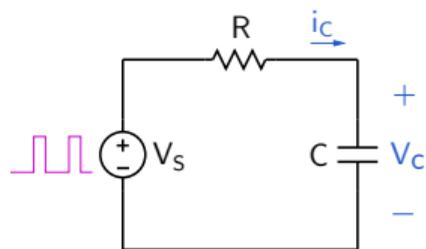

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$




$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

# RC circuit: example

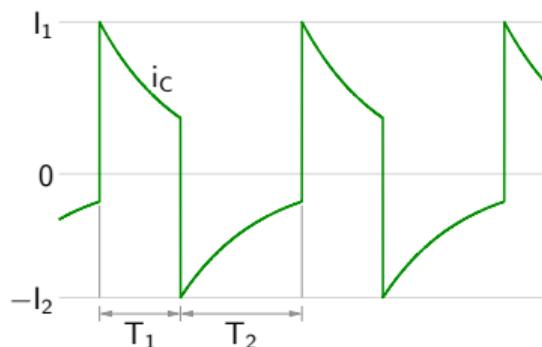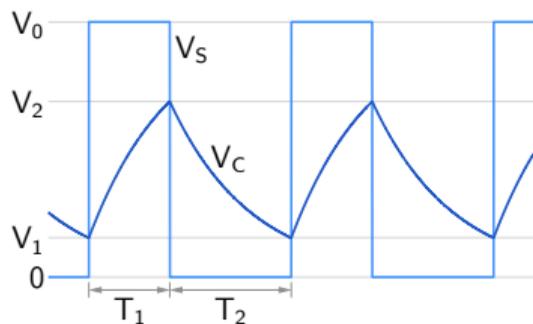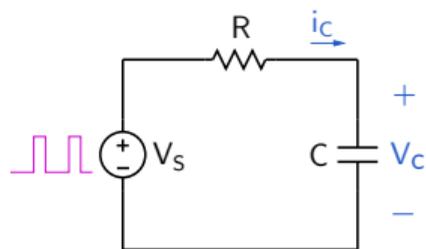

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$




$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

# RC circuit: example

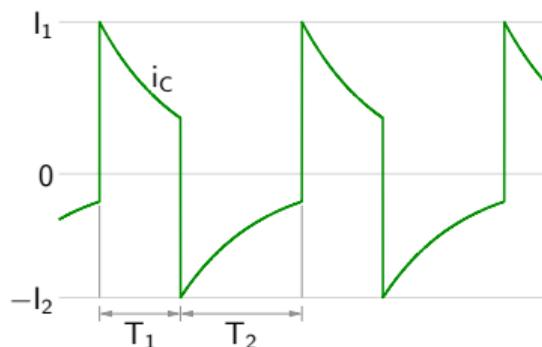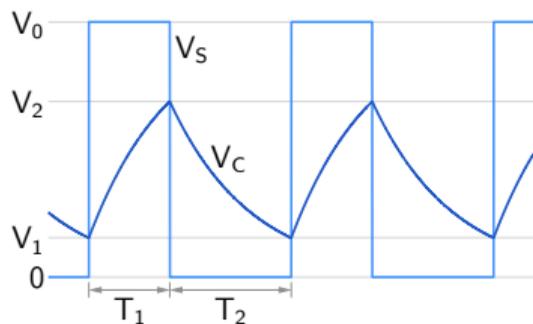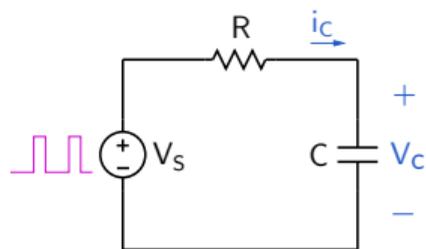

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$




$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

## RC circuit: example

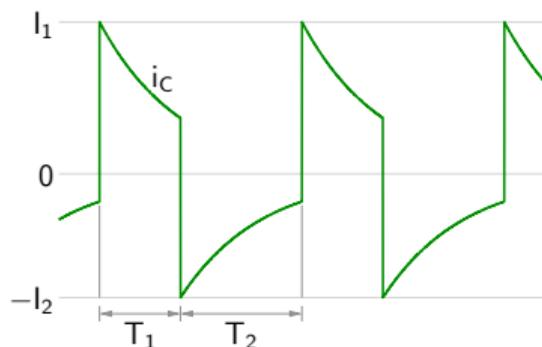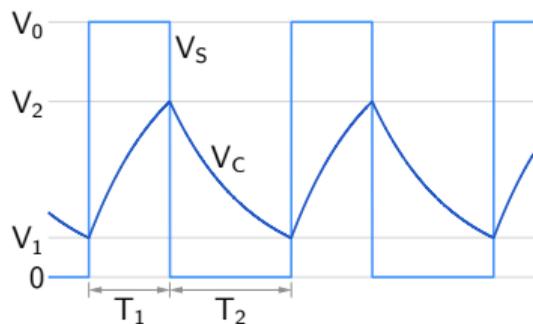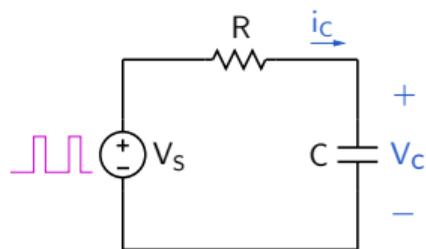

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$




$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

# RC circuit: example

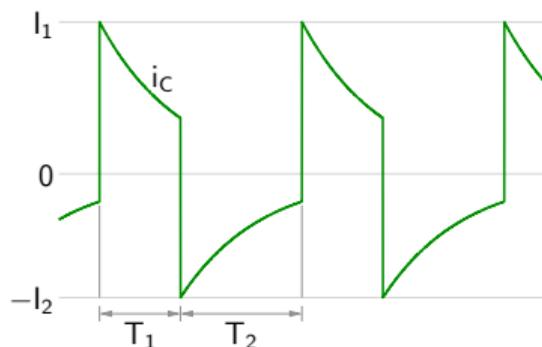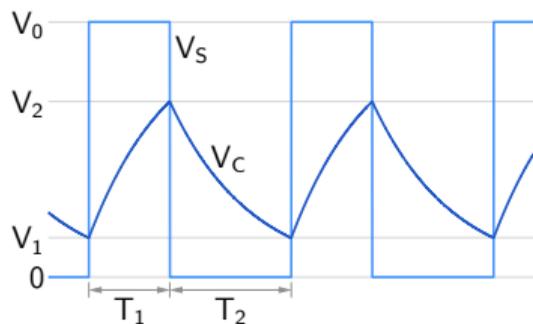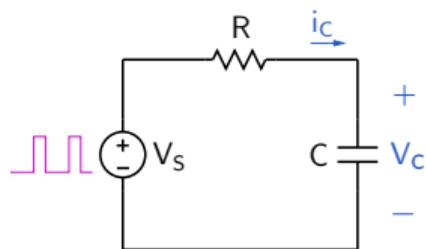

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$




$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

# RC circuit: example

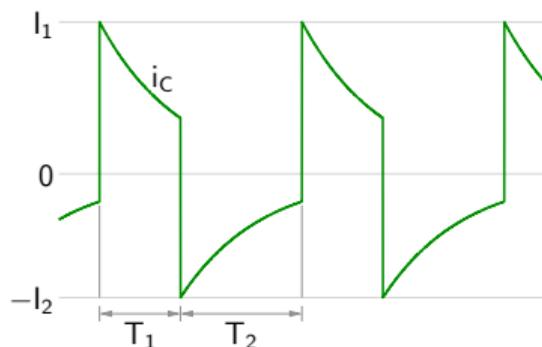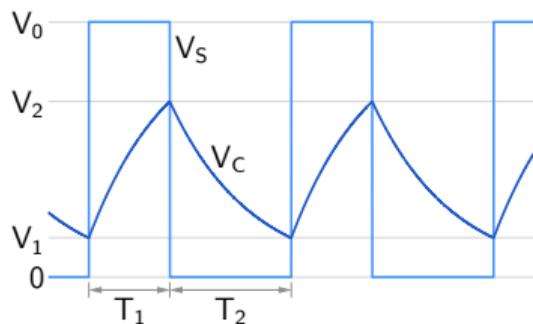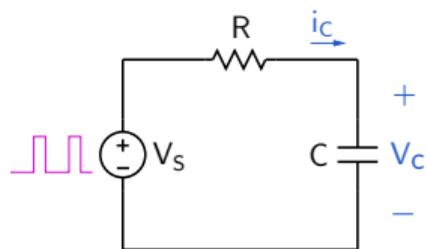

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$




Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

# RC circuit: example

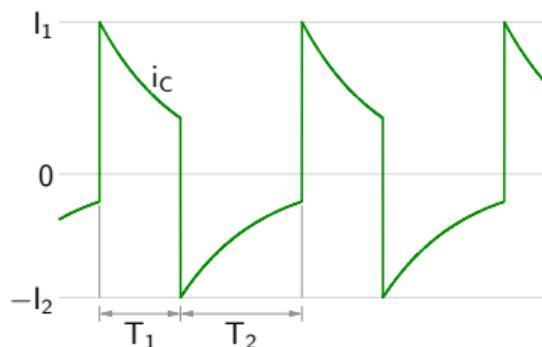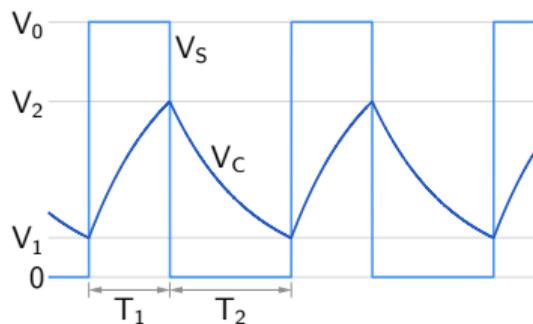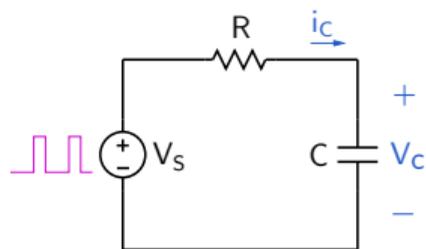

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:




$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with  $a \equiv e^{-T_1/\tau}$ ,  $b \equiv e^{-T_2/\tau}$ .

# RC circuit: example

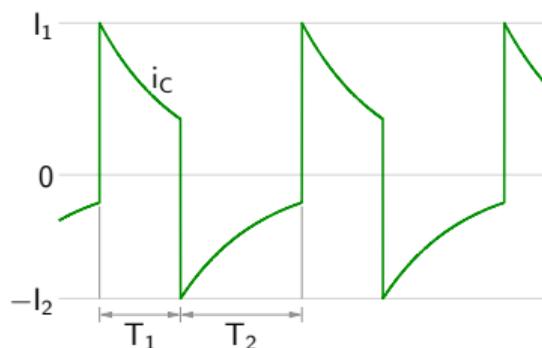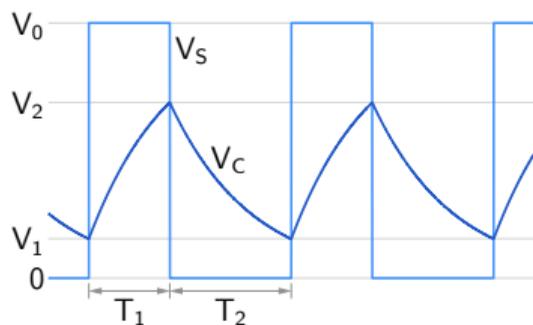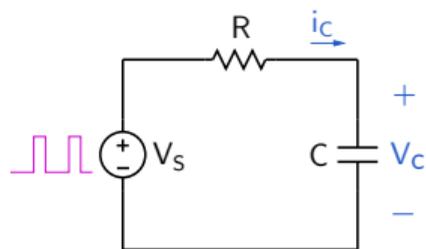

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$




$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with  $a \equiv e^{-T_1/\tau}$ ,  $b \equiv e^{-T_2/\tau}$ .

$$V_2 = -(V_0 - V_1)a + V_0 \quad (5)$$

# RC circuit: example

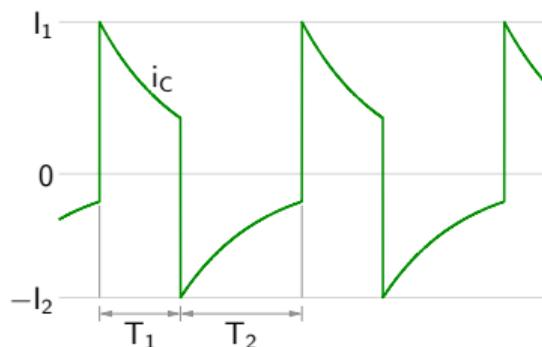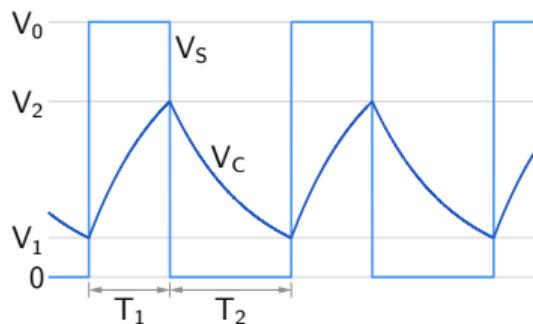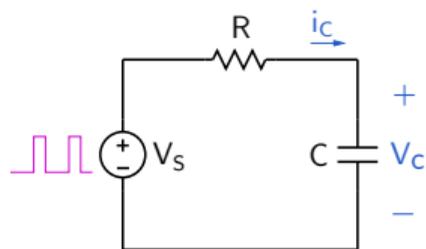

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$




$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with  $a \equiv e^{-T_1/\tau}$ ,  $b \equiv e^{-T_2/\tau}$ .

$$V_2 = -(V_0 - V_1)a + V_0 \quad (5)$$

$$V_1 = b V_2 \quad (6)$$

# RC circuit: example

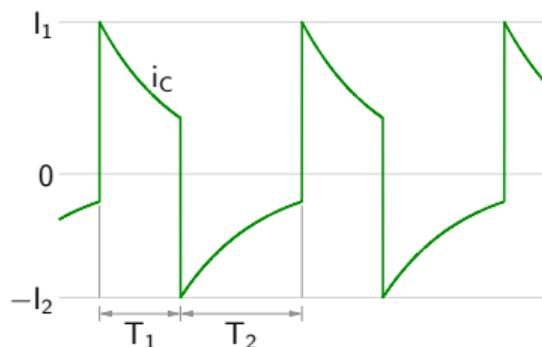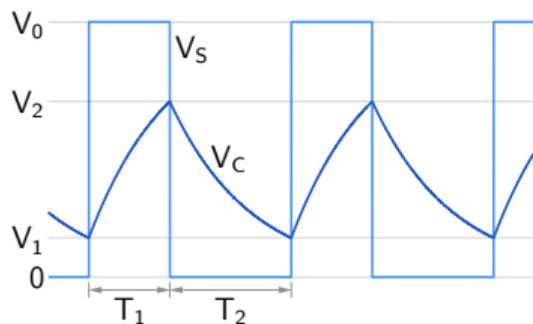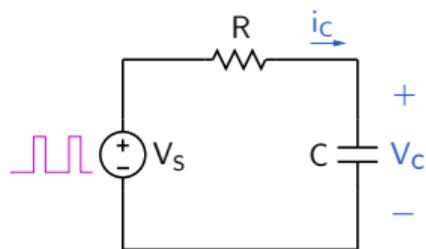

$$0 < t < T_1 \quad \text{Let } V_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$V_C^{(1)}(0) = V_1, \quad V_C^{(1)}(\infty) = V_0$$

$$\rightarrow B = V_0, \quad A = V_1 - V_0.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0 \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } V_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$V_C^{(2)}(T_1) = V_2, \quad V_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = V_2 e^{T_1/\tau}.$$

$$V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$V_C^{(1)}(T_1) = V_2, \quad V_C^{(2)}(T_1 + T_2) = V_1.$$

$$V_2 = -(V_0 - V_1)e^{-T_1/\tau} + V_0 \quad (3)$$

$$V_1 = V_2 e^{-(T_1+T_2-T_1)/\tau} = V_2 e^{-T_2/\tau} \quad (4)$$

Rewrite with  $a \equiv e^{-T_1/\tau}$ ,  $b \equiv e^{-T_2/\tau}$ .




$$V_2 = -(V_0 - V_1)a + V_0 \quad (5)$$

$$V_1 = b V_2 \quad (6)$$

Solve to get




$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}$$

# RC circuit: example

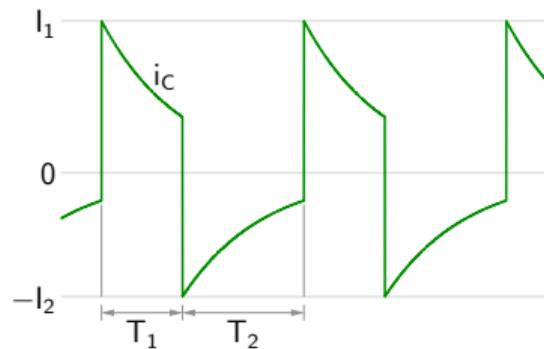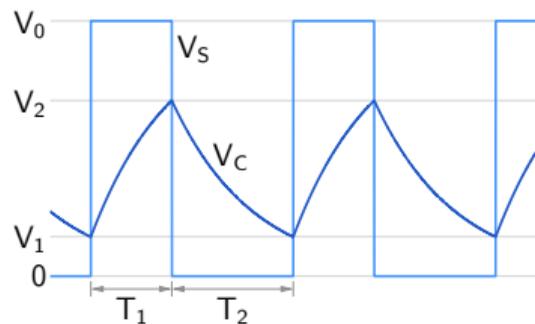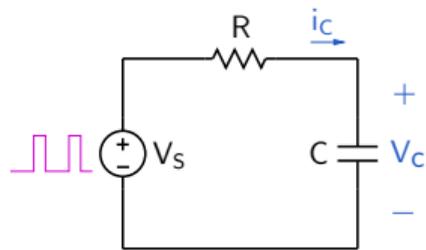

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$




## RC circuit: example

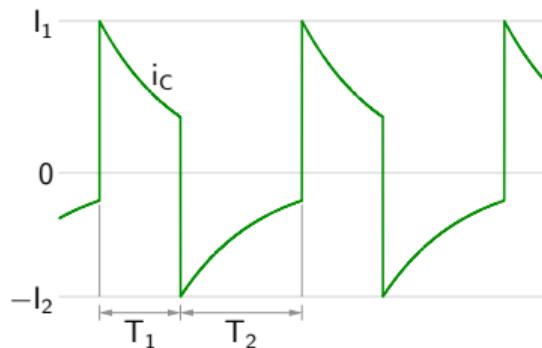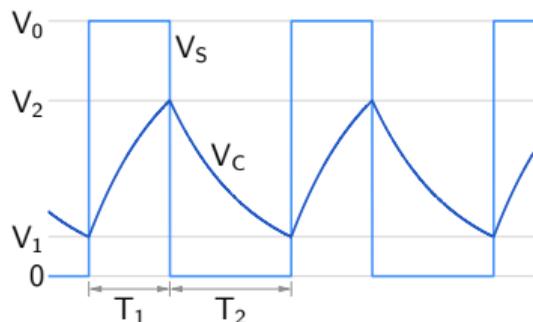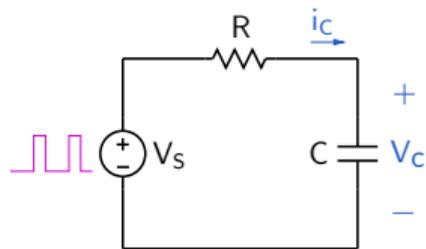

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

## RC circuit: example

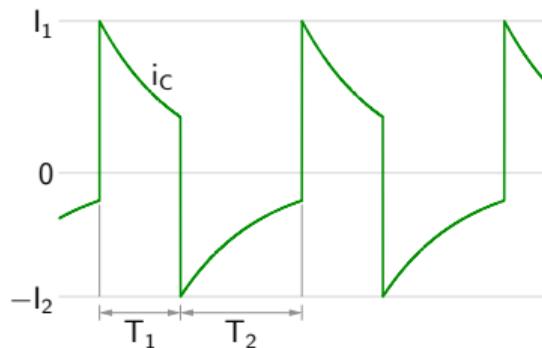
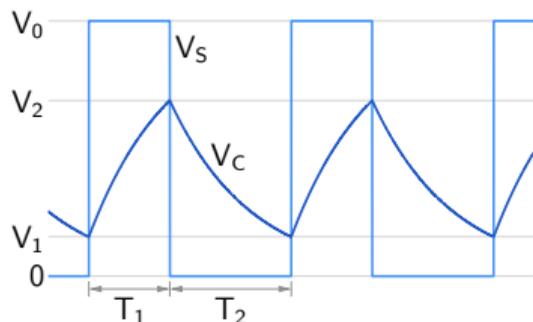
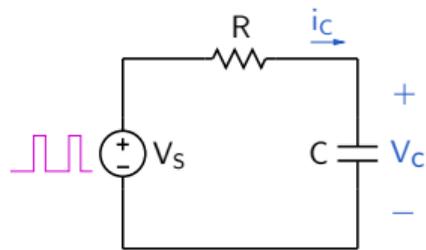


$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:

## RC circuit: example

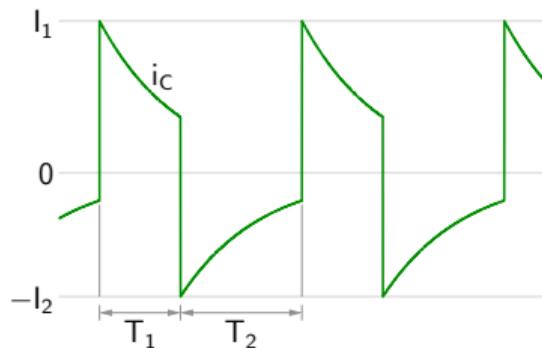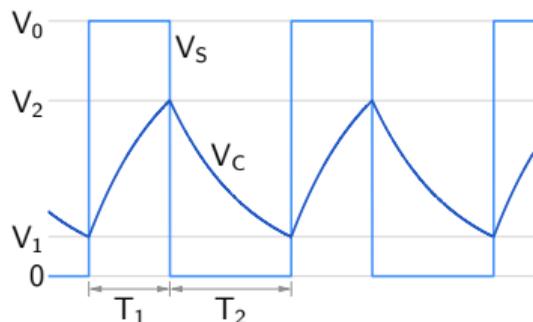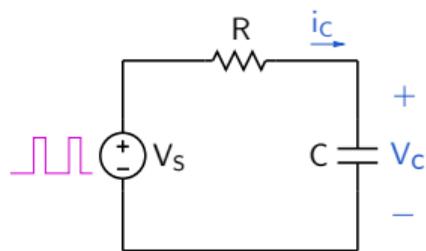

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$




$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:

Method 1:

$$i_c(t) = C \frac{dV_C}{dt} \quad (\text{home work})$$

## RC circuit: example

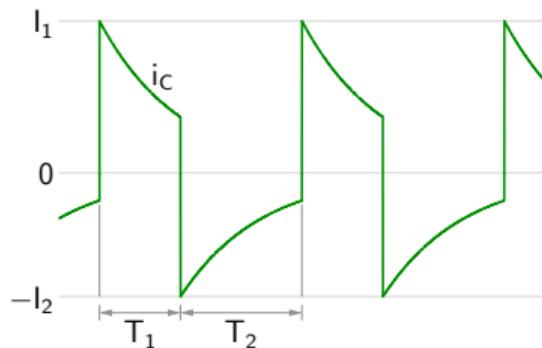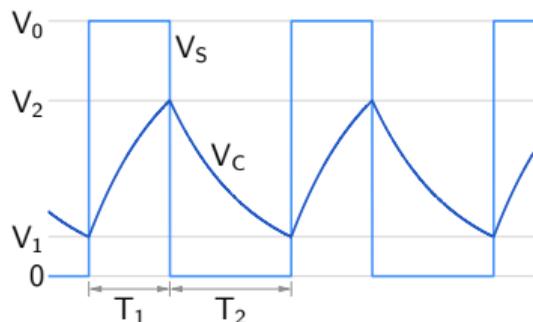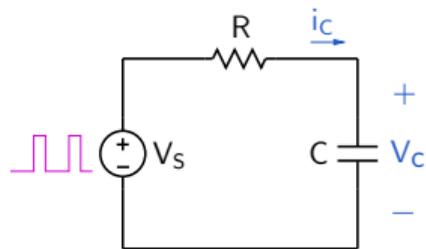

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:




Method 1:

$$i_c(t) = C \frac{dV_C}{dt} \text{ (home work)}$$

Method 2:

Start from scratch!

## RC circuit: example

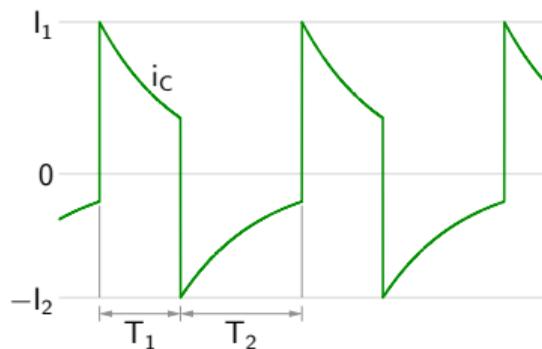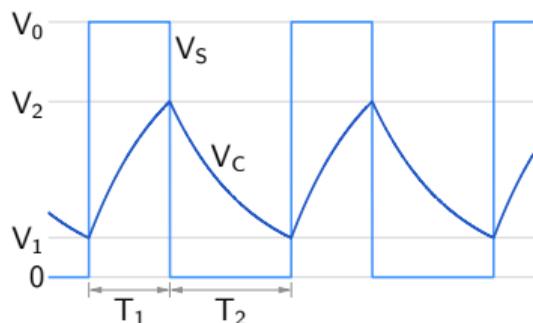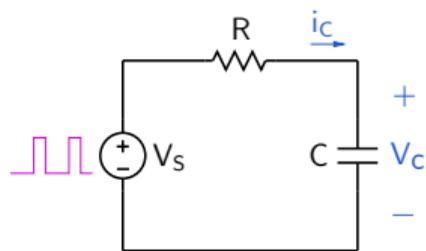

$$V_1 = b V_0 \frac{1-a}{1-ab}, \quad V_2 = V_0 \frac{1-a}{1-ab}, \quad \text{with } a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau}.$$

$$V_C^{(1)}(t) = -(V_0 - V_1)e^{-t/\tau} + V_0, \quad V_C^{(2)}(t) = V_2 e^{-(t-T_1)/\tau}.$$

Current calculation:

Method 1:




$$i_c(t) = C \frac{dV_C}{dt} \text{ (home work)}$$

Method 2:




Start from scratch!



## RC circuit: example

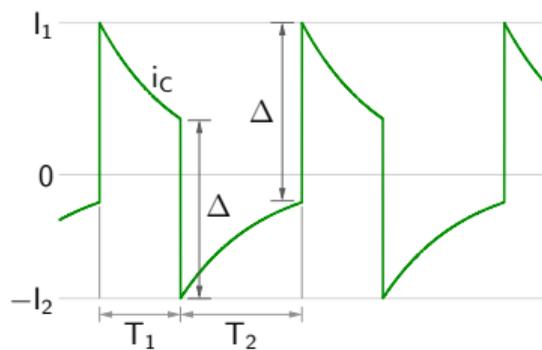
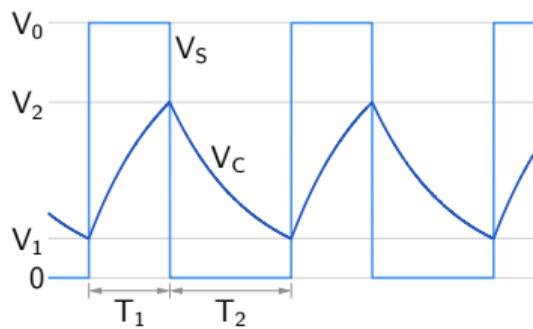
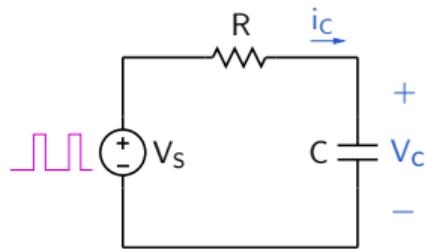


## RC circuit: example

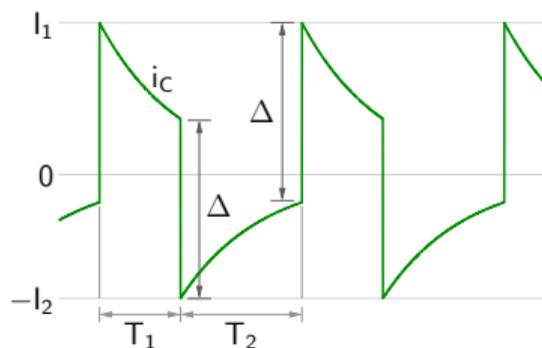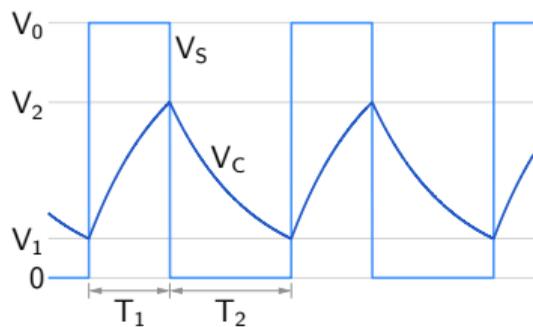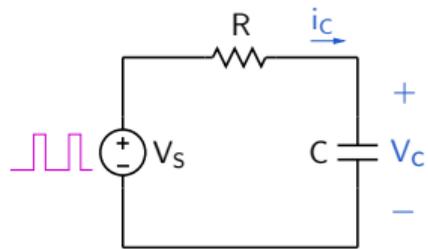

$0 < t < T_1$  Let  $i_C^{(1)}(t) = Ae^{-t/\tau} + B$




# RC circuit: example

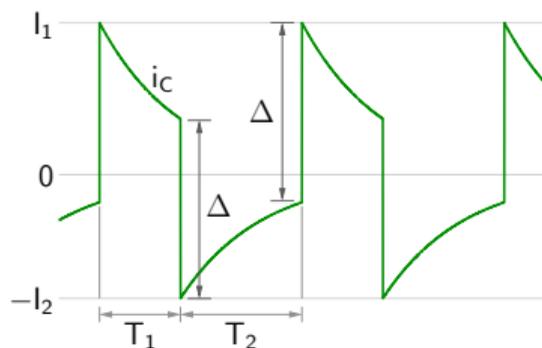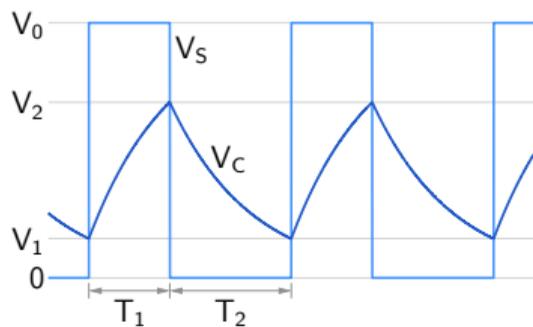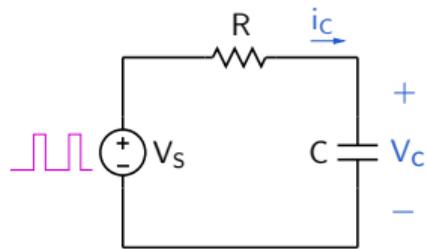

$0 < t < T_1$  Let  $i_C^{(1)}(t) = Ae^{-t/\tau} + B$

$i_C^{(1)}(0) = I_1, i_C^{(1)}(\infty) = 0$

## RC circuit: example

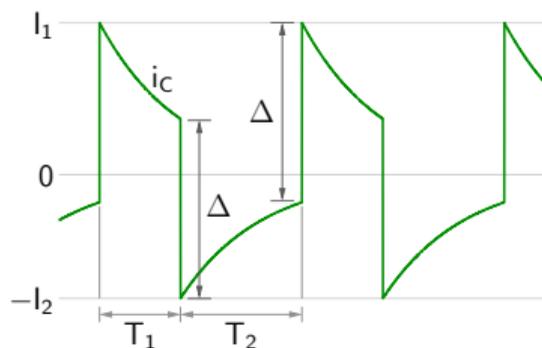
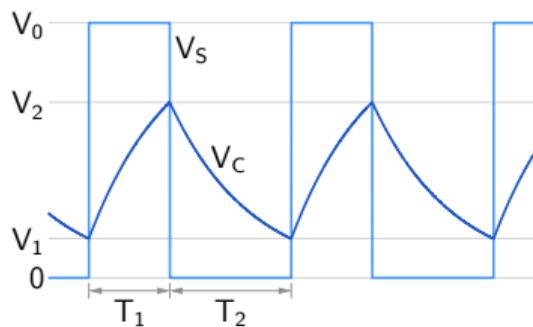
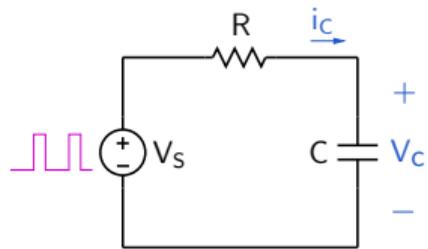


$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = Ae^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

## RC circuit: example

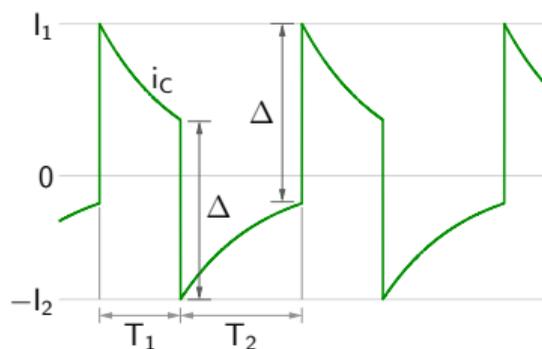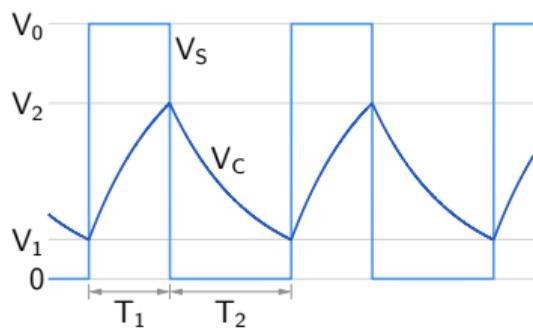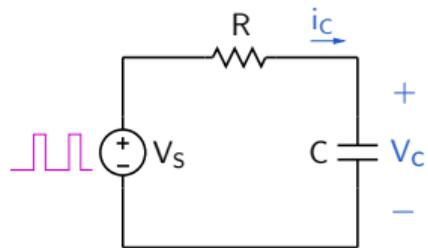




$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

# RC circuit: example

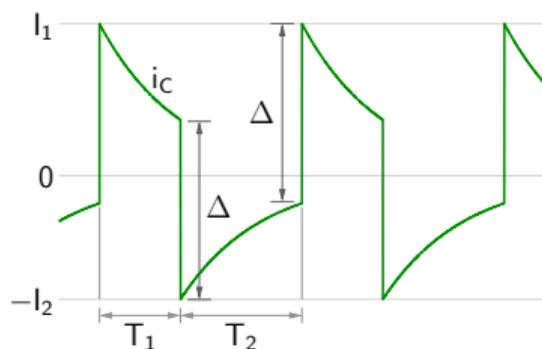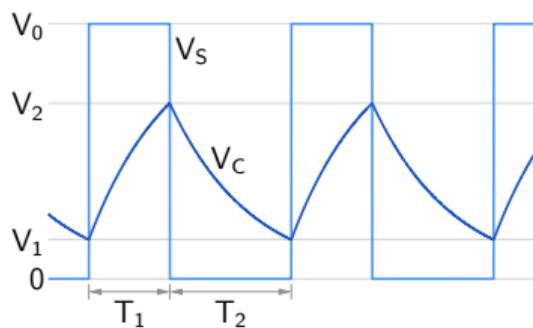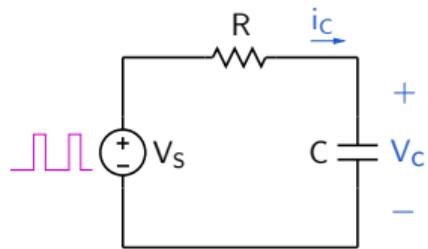

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$




$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

# RC circuit: example

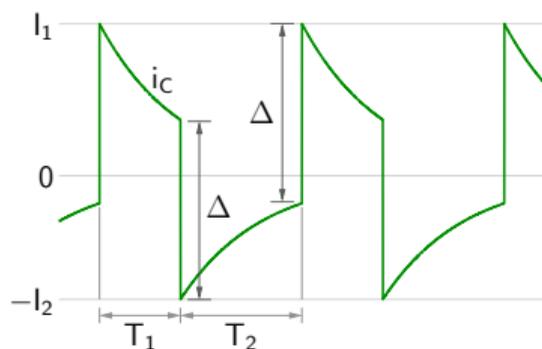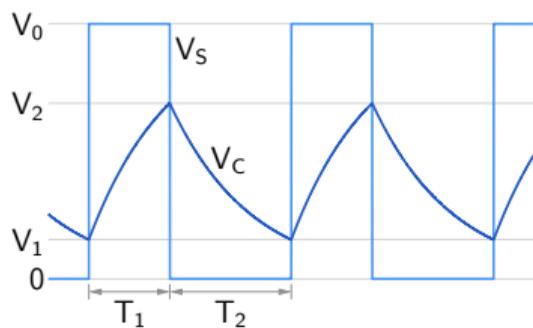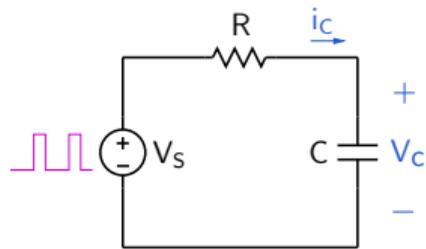

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$




$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -I_2, \quad i_C^{(2)}(\infty) = 0$$

## RC circuit: example

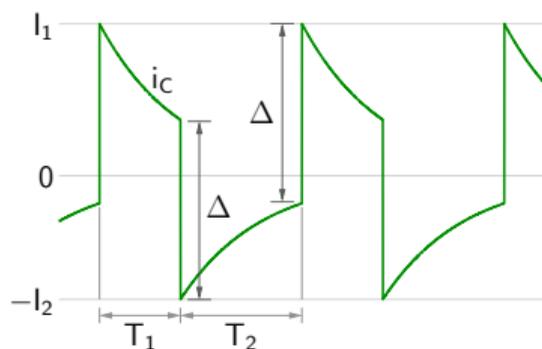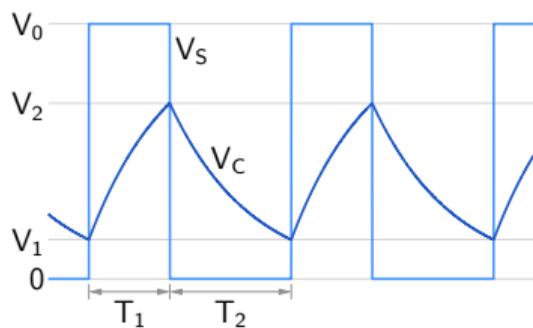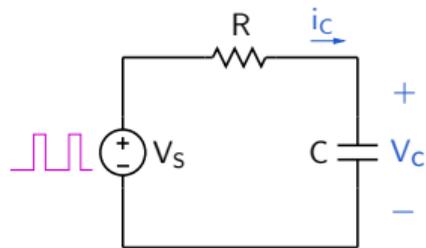

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$




$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -I_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -I_2 e^{T_1/\tau}.$$

# RC circuit: example

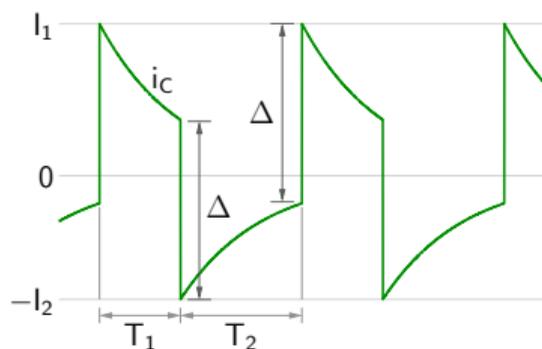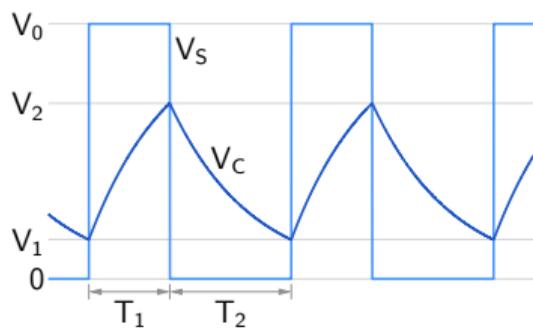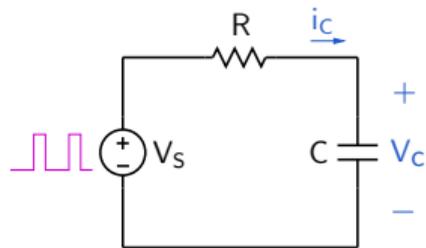

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$




$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -I_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -I_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -I_2 e^{-(t-T_1)/\tau} \quad (2)$$

## RC circuit: example

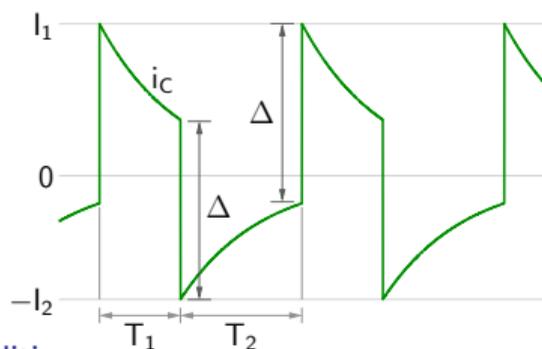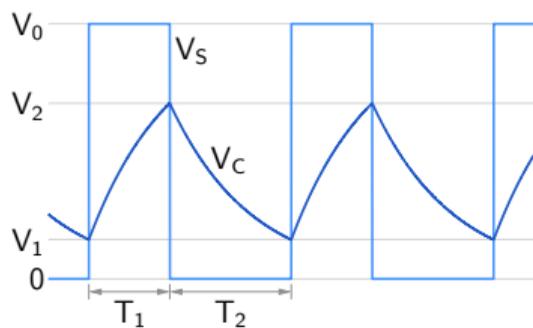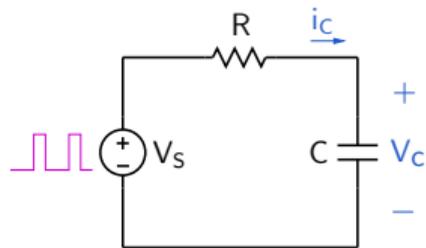

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -I_2, \quad i_C^{(2)}(\infty) = 0$$




$$\rightarrow B' = 0, \quad A' = -I_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -I_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

# RC circuit: example

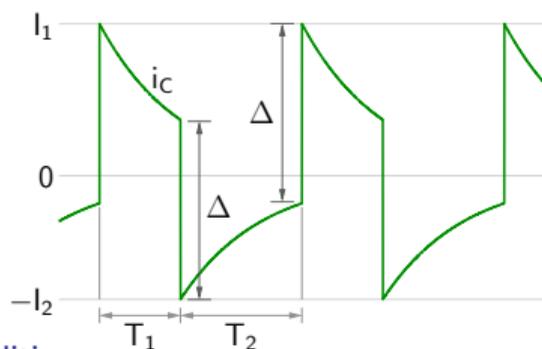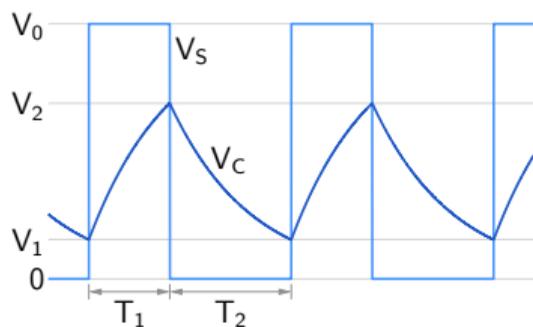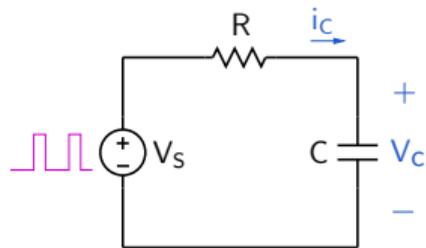

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = I_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = I_1.$$

$$i_C^{(1)}(t) = I_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -I_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -I_2 e^{T_1/\tau}.$$




$$i_C^{(2)}(t) = -I_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

# RC circuit: example

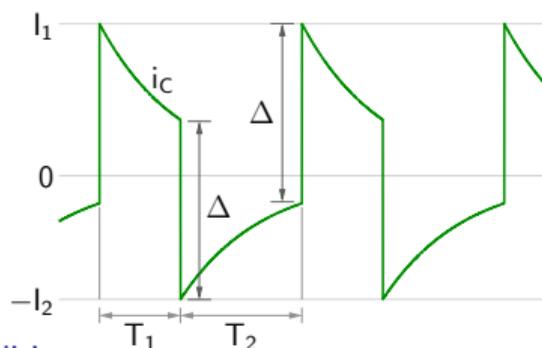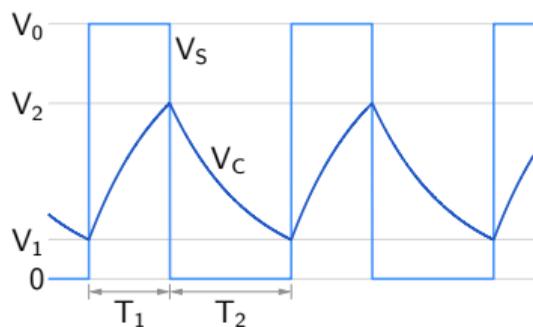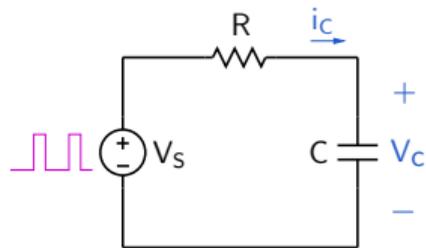

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$




Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

# RC circuit: example

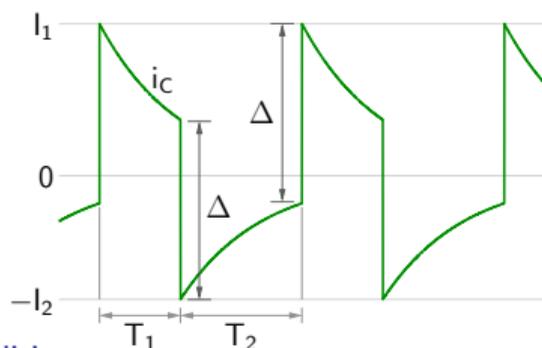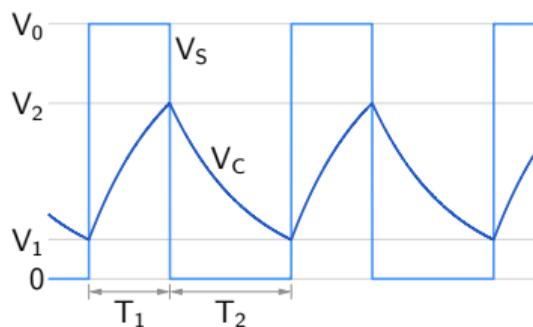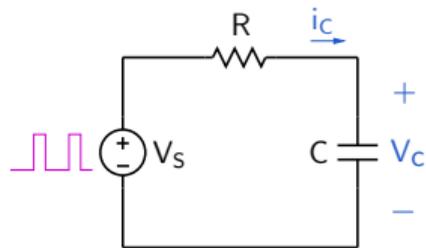

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:




$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$h_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

# RC circuit: example

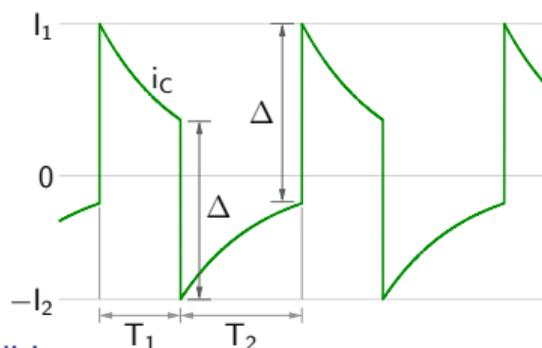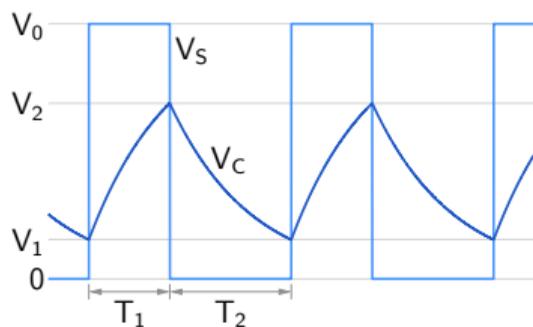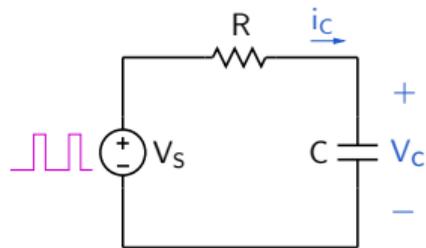

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$




$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$h_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

$$a h_1 + l_2 = \Delta \quad (5)$$

# RC circuit: example

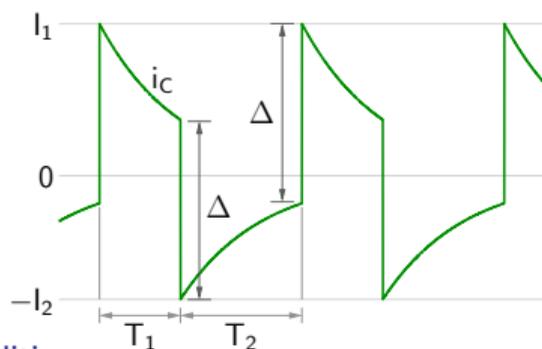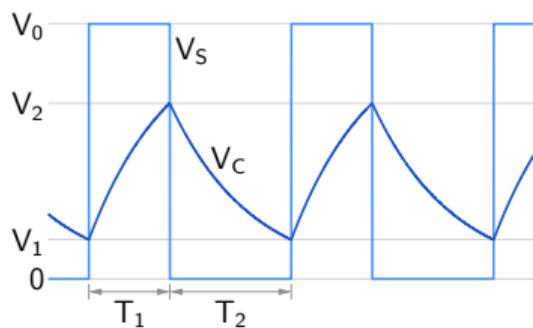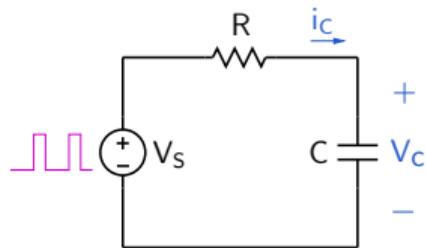

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = l_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = l_1.$$

$$i_C^{(1)}(t) = l_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$




$$l_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$l_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

$$a l_1 + l_2 = \Delta \quad (5)$$

$$l_1 + b l_2 = \Delta \quad (6)$$

# RC circuit: example

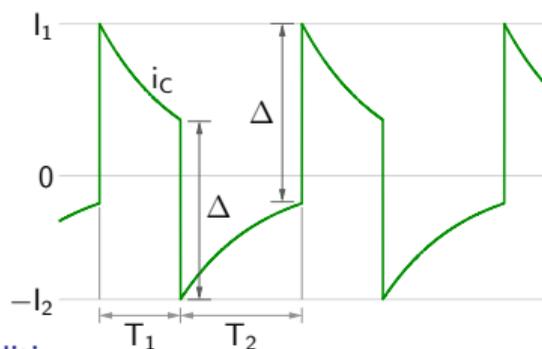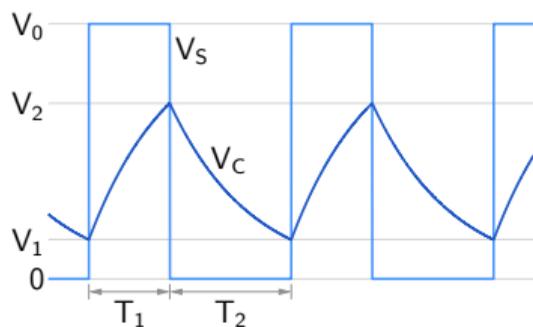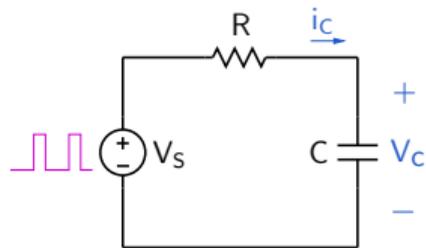

$$0 < t < T_1 \quad \text{Let } i_C^{(1)}(t) = A e^{-t/\tau} + B$$

$$i_C^{(1)}(0) = h_1, \quad i_C^{(1)}(\infty) = 0$$

$$\rightarrow B = 0, \quad A = h_1.$$

$$i_C^{(1)}(t) = h_1 e^{-t/\tau} \quad (1)$$

$$T_1 < t < T_2 \quad \text{Let } i_C^{(2)}(t) = A' e^{-t/\tau} + B'$$

$$i_C^{(2)}(T_1) = -l_2, \quad i_C^{(2)}(\infty) = 0$$

$$\rightarrow B' = 0, \quad A' = -l_2 e^{T_1/\tau}.$$

$$i_C^{(2)}(t) = -l_2 e^{-(t-T_1)/\tau} \quad (2)$$

Now use the conditions:

$$i_C^{(1)}(T_1) - i_C^{(2)}(T_1) = \Delta = V_0/R,$$

$$i_C^{(1)}(0) - i_C^{(2)}(T_1 + T_2) = \Delta = V_0/R.$$

$$h_1 e^{-T_1/\tau} - (-l_2) = \Delta \quad (3)$$

$$h_1 - (-l_2 e^{-(T_1+T_2-T_1)/\tau}) = \Delta \quad (4)$$

$$a h_1 + l_2 = \Delta \quad (5)$$


$$h_1 + b l_2 = \Delta \quad (6)$$

Solve to get




$$h_1 = \Delta \frac{1-b}{1-ab}, \quad l_2 = \Delta \frac{1-a}{1-ab}$$

$$(a = e^{-T_1/\tau}, \quad b = e^{-T_2/\tau})$$

# RC circuit: example

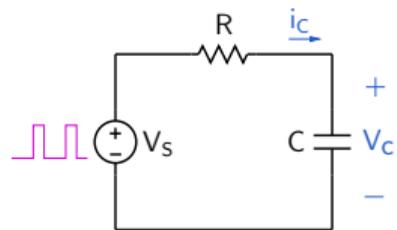


Charge conservation:

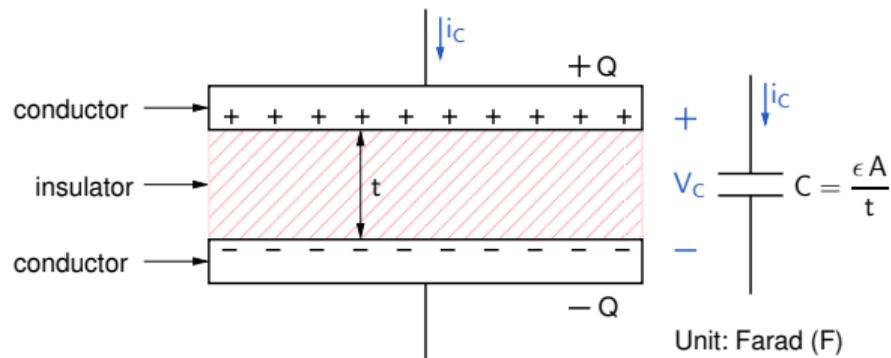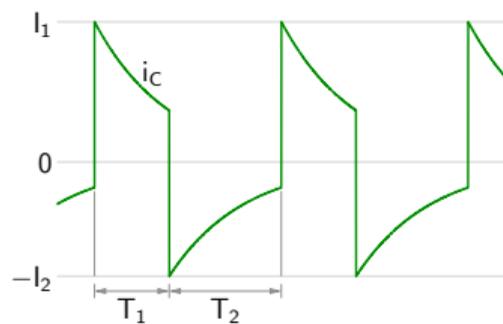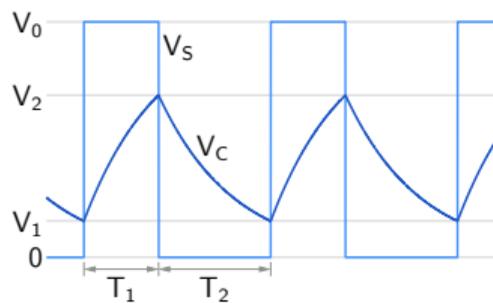




$$i_c = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$

# RC circuit: example

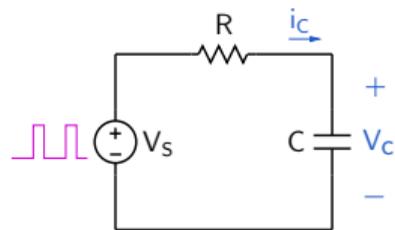




Charge conservation:

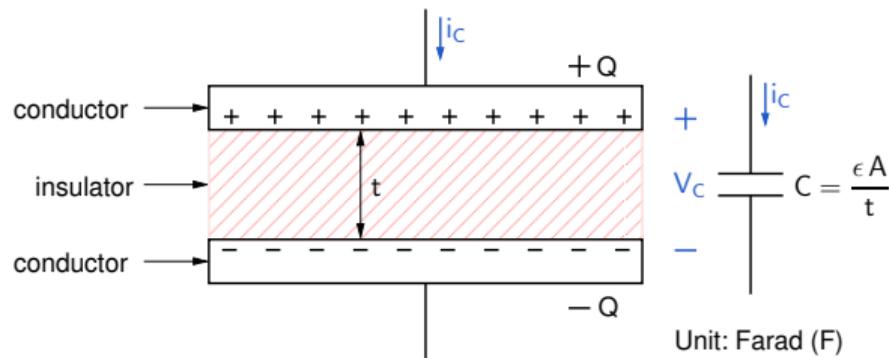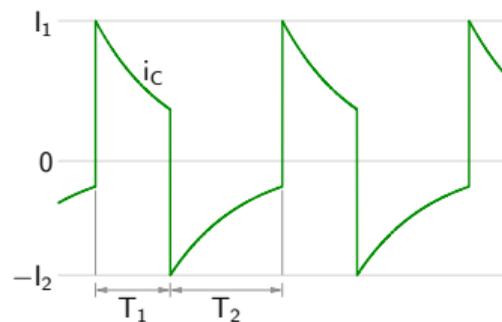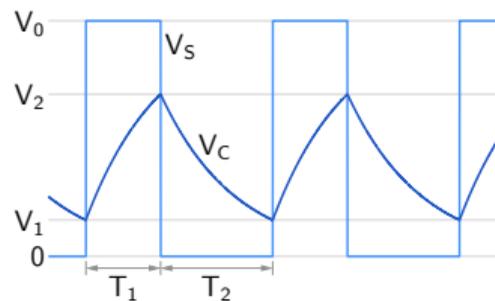Periodic steady state: All quantities are periodic, i.e.,  
 $x(t_0 + T) = x(t_0)$



$$i_c = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$


# RC circuit: example

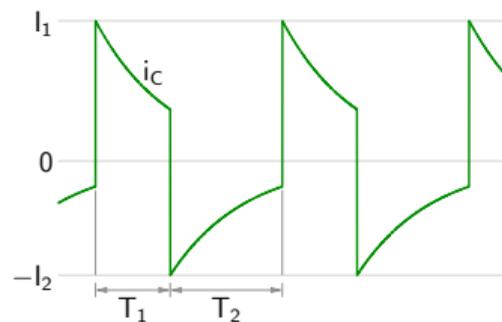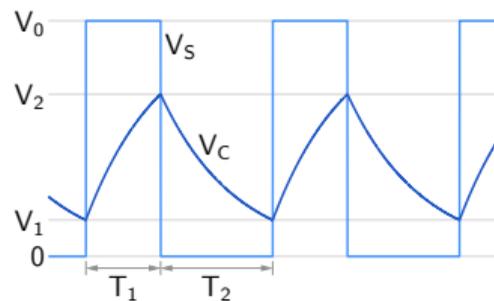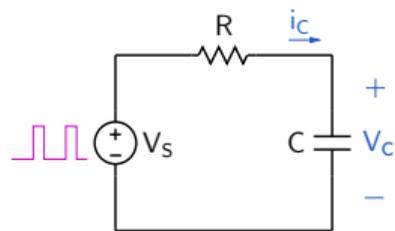

Charge conservation:




Periodic steady state: All quantities are periodic, i.e.,  
 $x(t_0 + T) = x(t_0)$

Capacitor charge:  $Q(t_0 + T) = Q(t_0)$

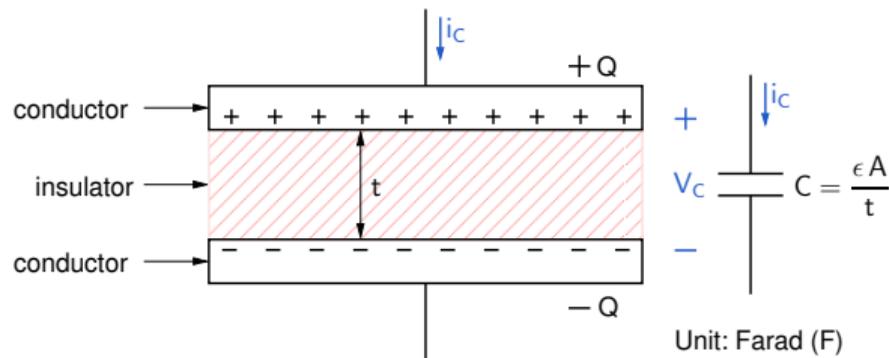

$$i_c = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$

# RC circuit: example

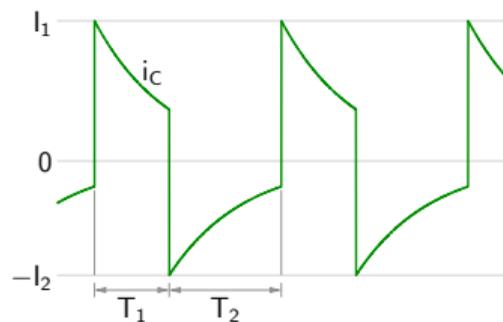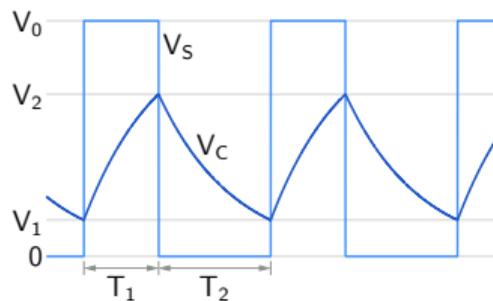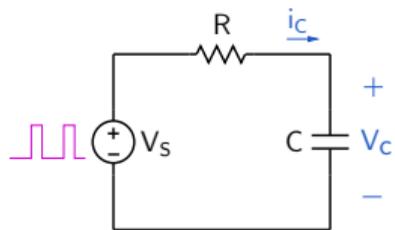


Charge conservation:

Periodic steady state: All quantities are periodic, i.e.,  
 $x(t_0 + T) = x(t_0)$




Capacitor charge:  $Q(t_0 + T) = Q(t_0)$
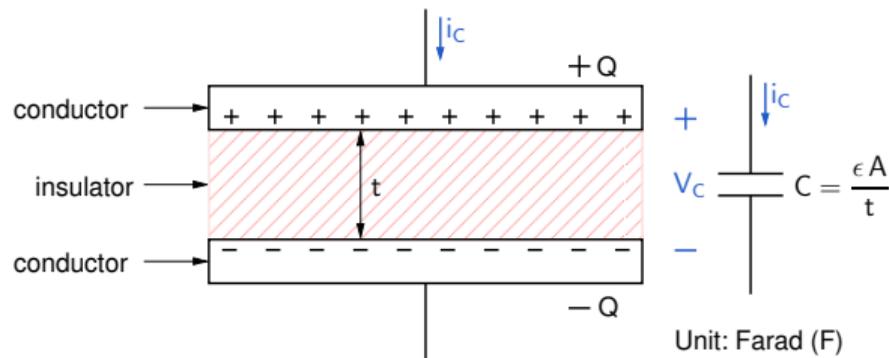
$$i_C = \frac{dQ}{dt} \rightarrow Q = \int i_C dt.$$



$$i_c = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

# RC circuit: example

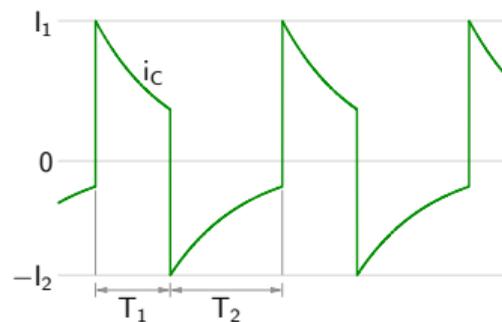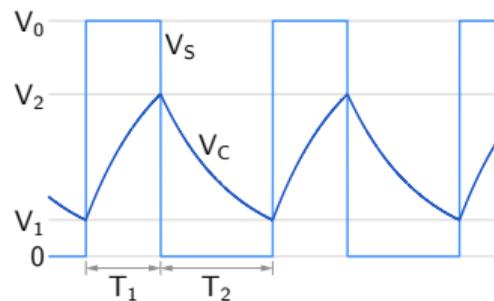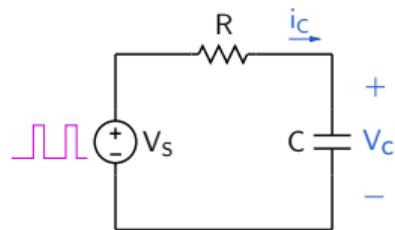

Charge conservation:


Periodic steady state: All quantities are periodic, i.e.,  
 $x(t_0 + T) = x(t_0)$

Capacitor charge:  $Q(t_0 + T) = Q(t_0)$

$$i_C = \frac{dQ}{dt} \rightarrow Q = \int i_C dt.$$




$$Q(t_0 + T) = Q(t_0) \rightarrow Q(t_0 + T) - Q(t_0) = 0$$
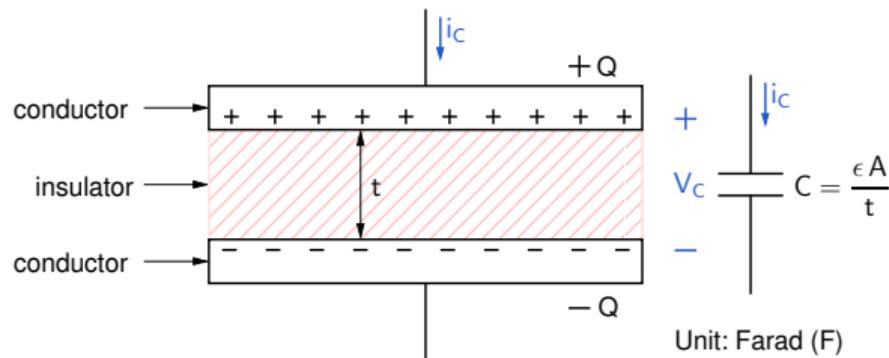
$$\rightarrow \int_{t_0}^{t_0+T} i_C dt = 0.$$



$$i_C = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

# RC circuit: example

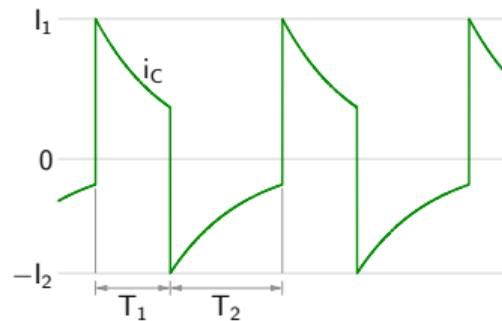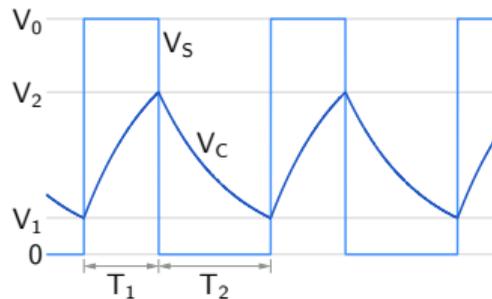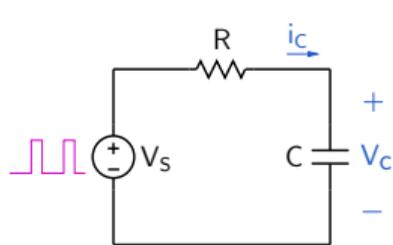

Charge conservation:

Periodic steady state: All quantities are periodic, i.e.,  
 $x(t_0 + T) = x(t_0)$

Capacitor charge:  $Q(t_0 + T) = Q(t_0)$


$$i_C = \frac{dQ}{dt} \rightarrow Q = \int i_C dt.$$

$$Q(t_0 + T) = Q(t_0) \rightarrow Q(t_0 + T) - Q(t_0) = 0$$

$$\rightarrow \int_{t_0}^{t_0+T} i_C dt = 0.$$

$$\int_0^T i_C dt = 0 \rightarrow \int_0^{T_1} i_C dt + \int_{T_1}^{T_1+T_2} i_C dt = 0$$
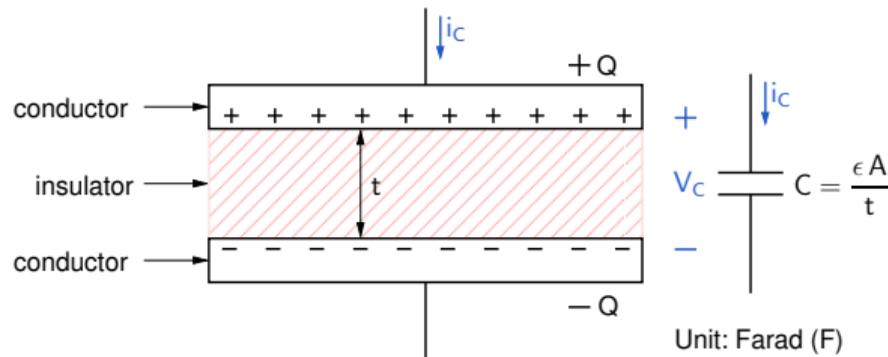
$$\rightarrow \int_{T_1}^{T_1+T_2} i_C dt = - \int_0^{T_1} i_C dt.$$







$$i_C = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

$T_1 = 1.5 \text{ msec}, T_2 = 1.5 \text{ msec}.$

$V_1 = 1.8 \text{ V}, V_2 = 8.2 \text{ V}.$

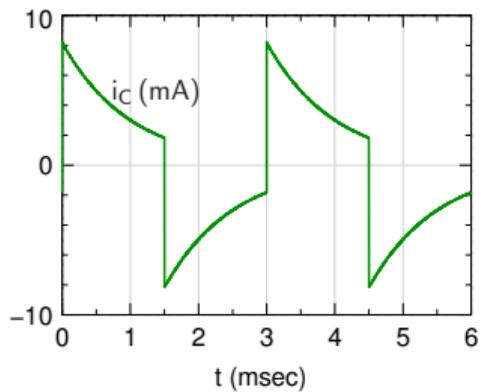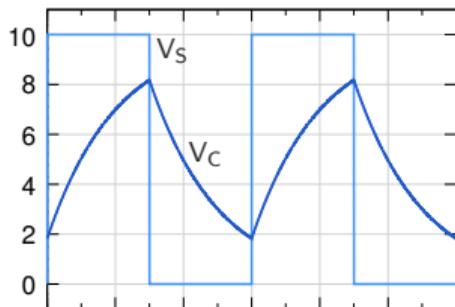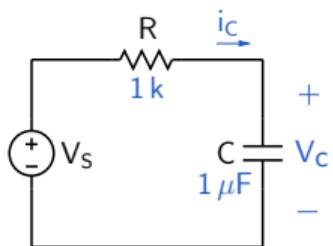$I_1 = 8.2 \text{ mA}, I_2 = 8.2 \text{ mA}.$




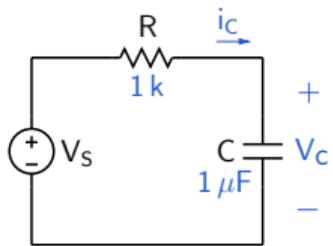

$$T_1 = 1.5 \text{ msec}, T_2 = 1.5 \text{ msec.}$$

$$V_1 = 1.8 \text{ V}, V_2 = 8.2 \text{ V.}$$



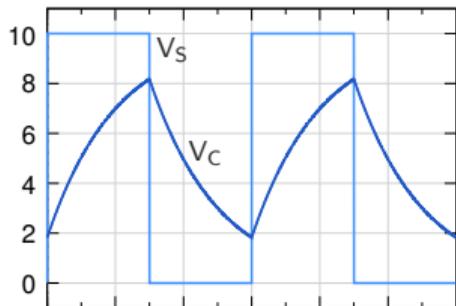
$$I_1 = 8.2 \text{ mA}, I_2 = 8.2 \text{ mA.}$$




$$T_1 = 1 \text{ msec}, T_2 = 2 \text{ msec.}$$

$$V_1 = 0.9 \text{ V}, V_2 = 6.7 \text{ V.}$$
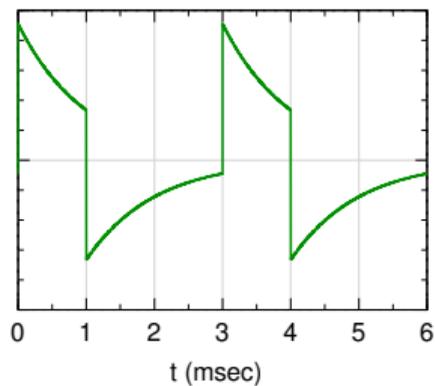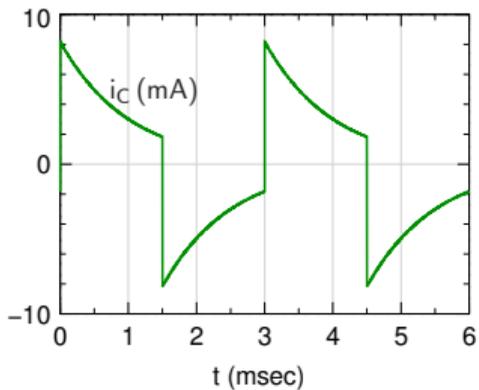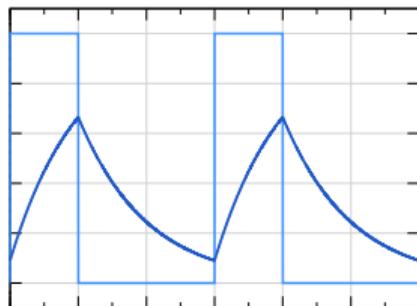
$$I_1 = 9.1 \text{ mA}, I_2 = 6.7 \text{ mA.}$$





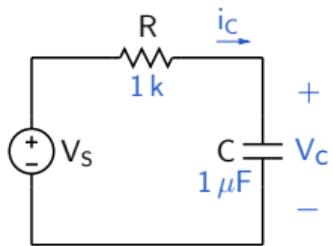

$$T_1 = 1.5 \text{ msec}, T_2 = 1.5 \text{ msec.}$$

$$V_1 = 1.8 \text{ V}, V_2 = 8.2 \text{ V.}$$

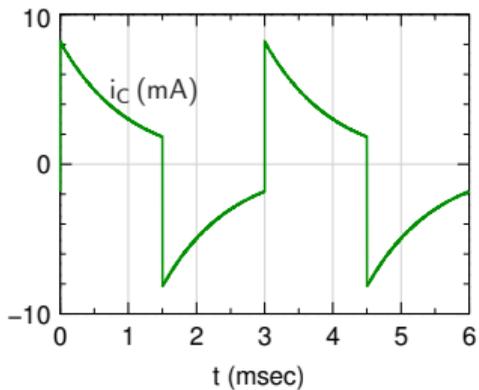
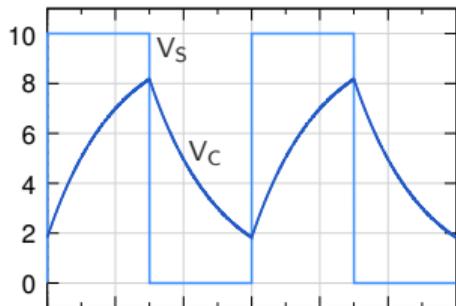
$$I_1 = 8.2 \text{ mA}, I_2 = 8.2 \text{ mA.}$$



$$T_1 = 1 \text{ msec}, T_2 = 2 \text{ msec.}$$

$$V_1 = 0.9 \text{ V}, V_2 = 6.7 \text{ V.}$$

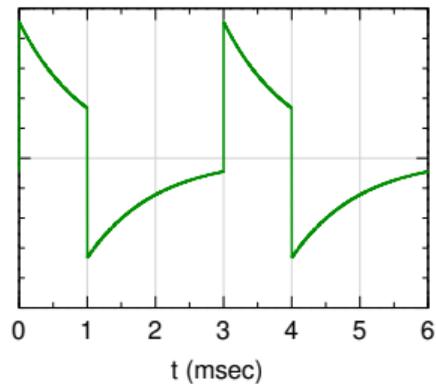
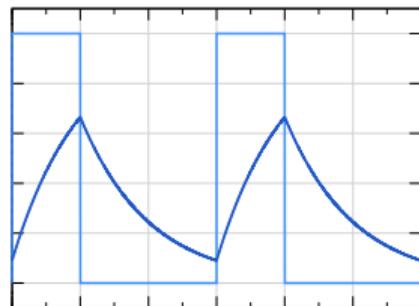
$$I_1 = 9.1 \text{ mA}, I_2 = 6.7 \text{ mA.}$$




$$T_1 = 2 \text{ msec}, T_2 = 1 \text{ msec.}$$

$$V_1 = 3.4 \text{ V}, V_2 = 9.1 \text{ V.}$$
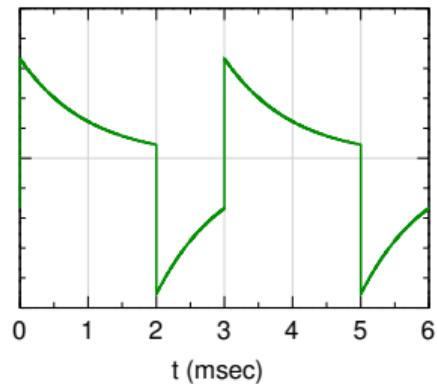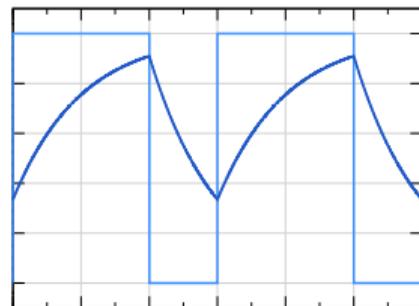
$$I_1 = 6.7 \text{ mA}, I_2 = 9.1 \text{ mA.}$$





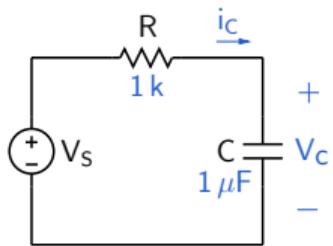

$$T_1 = 1.5 \text{ msec}, T_2 = 1.5 \text{ msec.}$$

$$V_1 = 1.8 \text{ V}, V_2 = 8.2 \text{ V.}$$

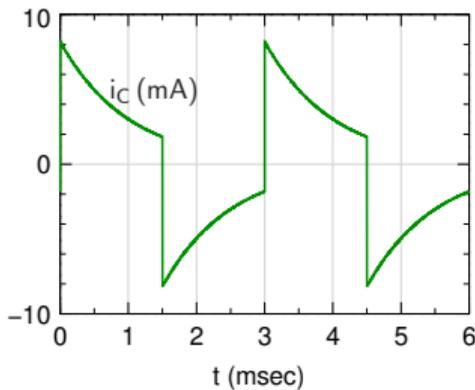
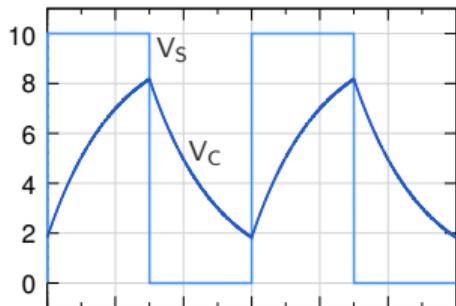
$$I_1 = 8.2 \text{ mA}, I_2 = 8.2 \text{ mA.}$$



$$T_1 = 1 \text{ msec}, T_2 = 2 \text{ msec.}$$

$$V_1 = 0.9 \text{ V}, V_2 = 6.7 \text{ V.}$$

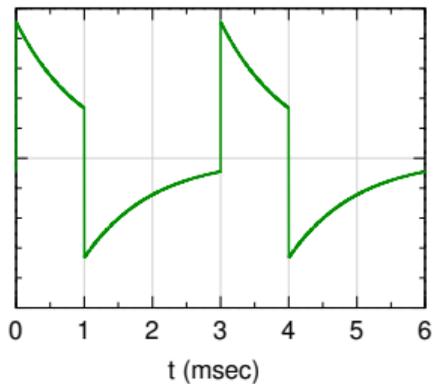
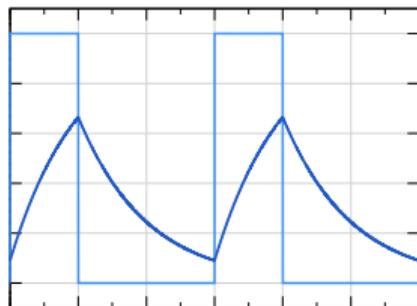
$$I_1 = 9.1 \text{ mA}, I_2 = 6.7 \text{ mA.}$$



$$T_1 = 2 \text{ msec}, T_2 = 1 \text{ msec.}$$

$$V_1 = 3.4 \text{ V}, V_2 = 9.1 \text{ V.}$$
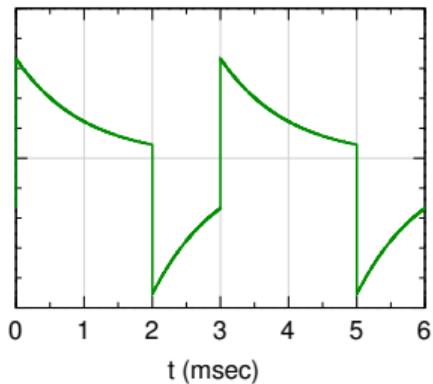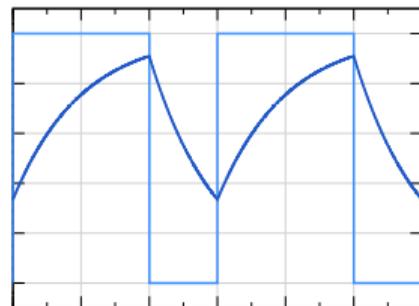
$$I_1 = 6.7 \text{ mA}, I_2 = 9.1 \text{ mA.}$$



SEQUEL file: ee101\_rc1b.sqproj

$T_1 = 1 \text{ msec}, T_2 = 2 \text{ msec}.$

$V_1 \approx 0 \text{ V}, V_2 = 10 \text{ V}.$

$I_1 = 100 \text{ mA}, I_2 = 100 \text{ mA}.$

