


- \* The Operational Amplifier (Op-Amp) is a versatile building block that can be used for realizing several electronic circuits.

- \* The Operational Amplifier (Op-Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The characteristics of an op-amp are nearly ideal  $\rightarrow$  op-amp circuits can be expected to perform as per theoretical design in most cases.


- \* The Operational Amplifier (Op-Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The characteristics of an op-amp are nearly ideal → op-amp circuits can be expected to perform as per theoretical design in most cases.
- \* Amplifiers built with op-amps work with DC input voltages as well → useful in sensor applications (e.g., temperature, pressure)

- \* The Operational Amplifier (Op-Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The characteristics of an op-amp are nearly ideal → op-amp circuits can be expected to perform as per theoretical design in most cases.
- \* Amplifiers built with op-amps work with DC input voltages as well → useful in sensor applications (e.g., temperature, pressure)
- \* The user can generally carry out circuit design without a thorough knowledge of the intricate details of an op-amp. This makes the design process simple.


# Op-Amp 741

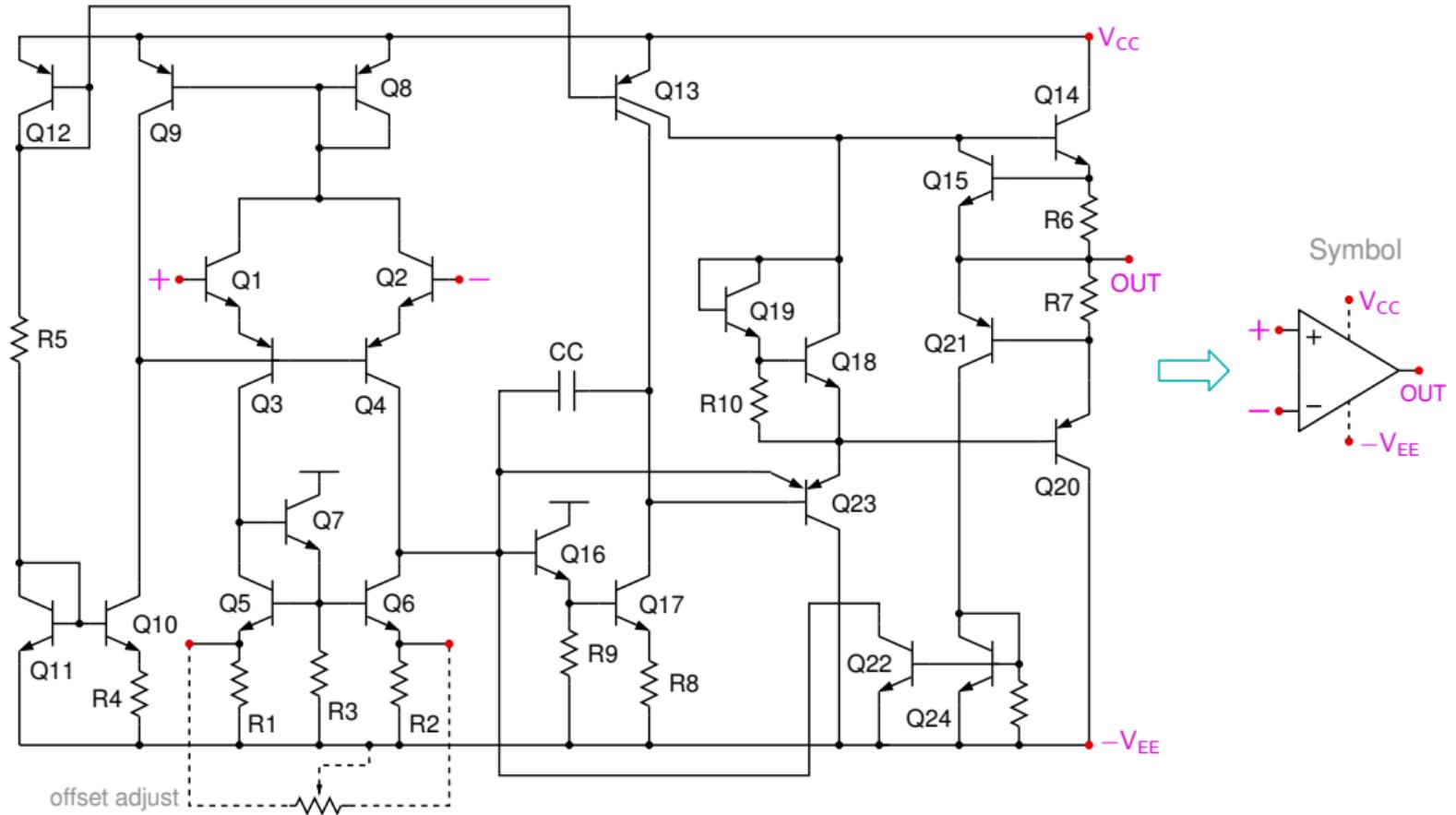

# Op-amp: equivalent circuit

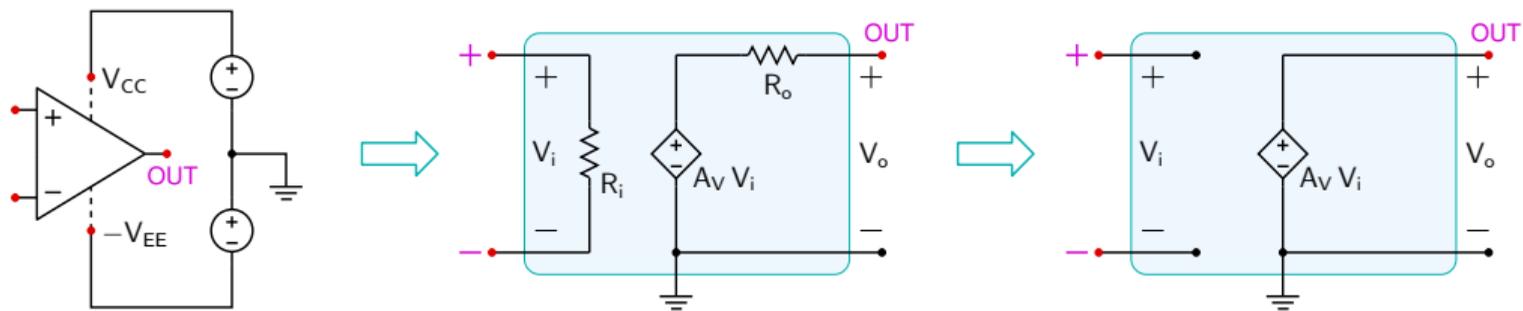


## Op-amp: equivalent circuit

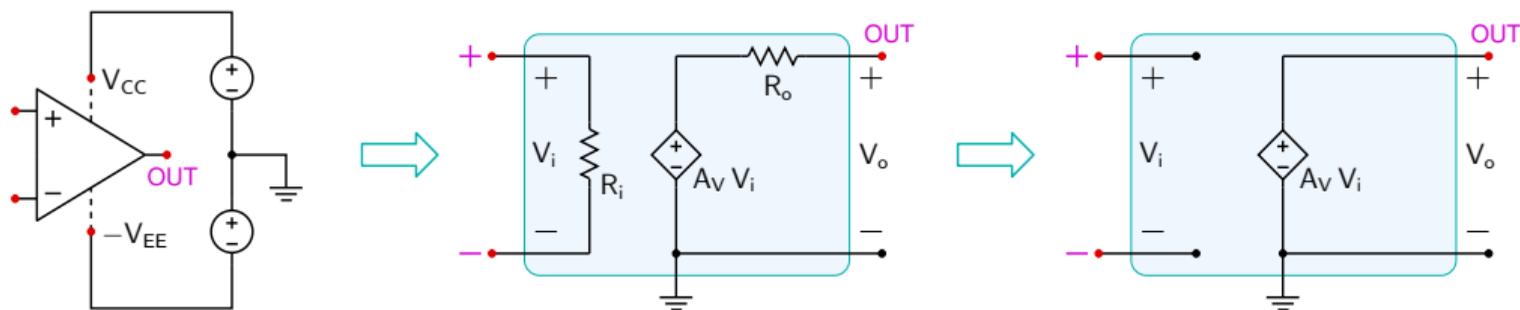


- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.

## Op-amp: equivalent circuit

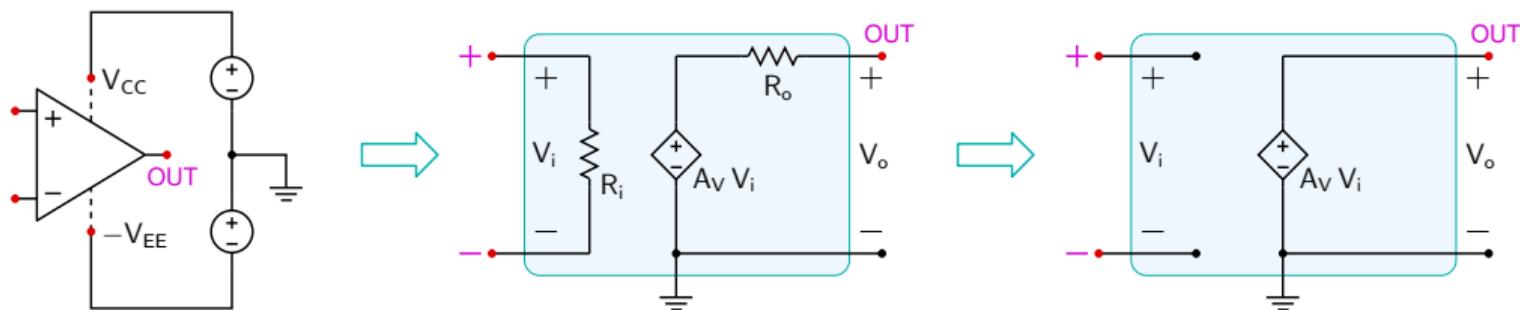


- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.
- \*  $V_{CC}$  and  $-V_{EE}$  ( $\sim \pm 5 V$  to  $\pm 15 V$ ) must be supplied; an op-amp will not work without them!

## Op-amp: equivalent circuit

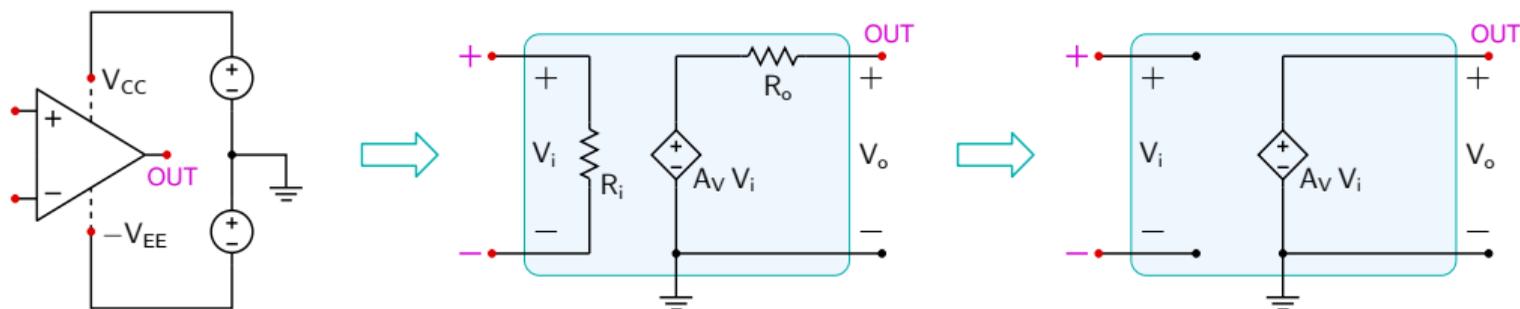

- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.
- \*  $V_{CC}$  and  $-V_{EE}$  ( $\sim \pm 5 V$  to  $\pm 15 V$ ) must be supplied; an op-amp will not work without them!  
In op-amp circuits, the supply voltages are often not shown explicitly.




## Op-amp: equivalent circuit

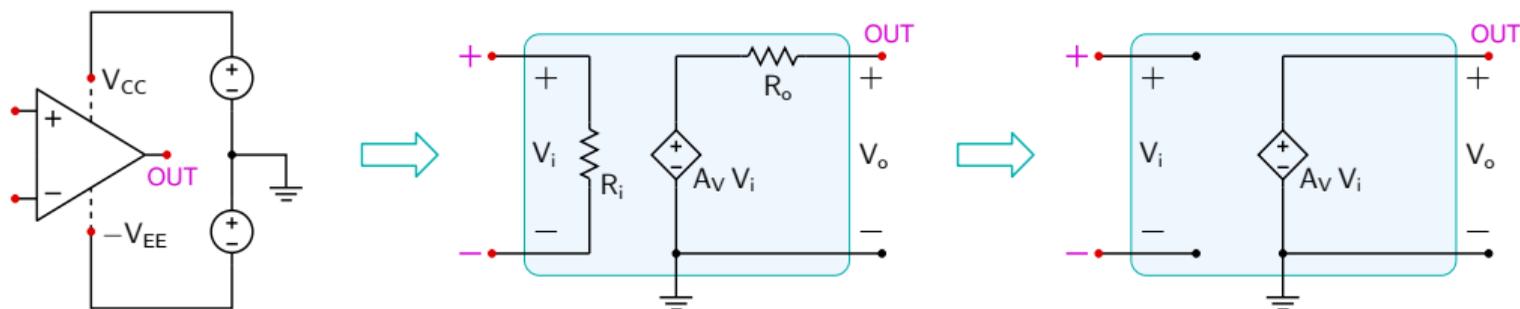




- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.
- \*  $V_{CC}$  and  $-V_{EE}$  ( $\sim \pm 5 V$  to  $\pm 15 V$ ) must be supplied; an op-amp will not work without them!  
In op-amp circuits, the supply voltages are often not shown explicitly.

Parameter	Ideal Op-Amp	741
* $A_V$	$\infty$	$10^5$ (100 dB)
$R_i$	$\infty$	2 M $\Omega$
$R_o$	0	75 $\Omega$

# Op-Amp: equivalent circuit

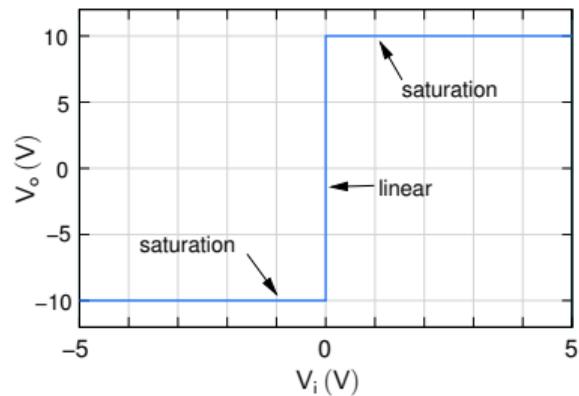
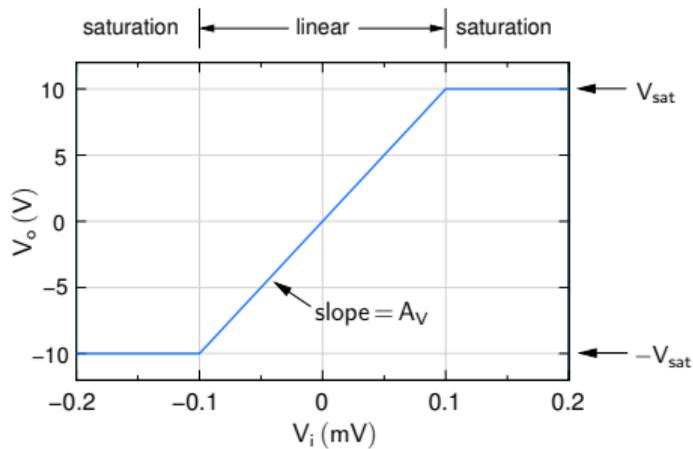
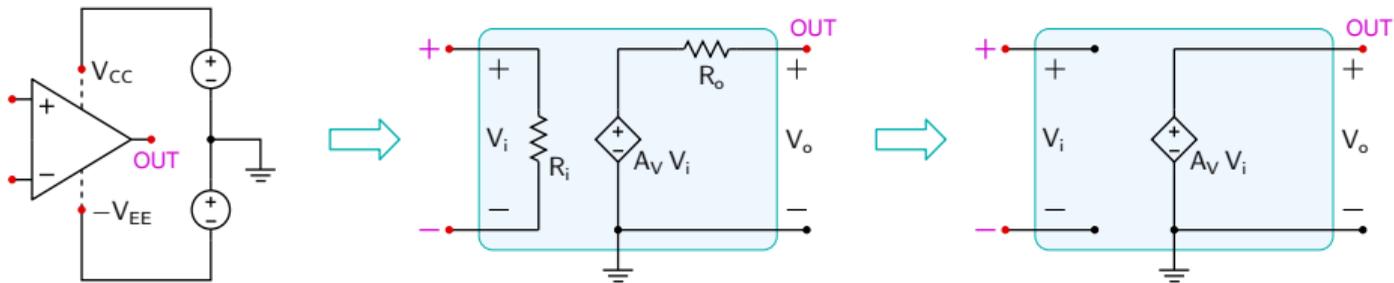


# Op-Amp: equivalent circuit

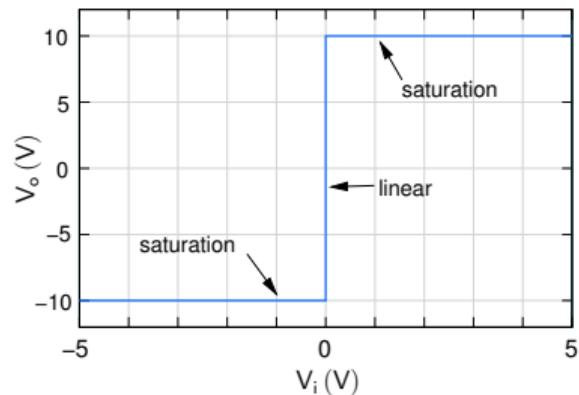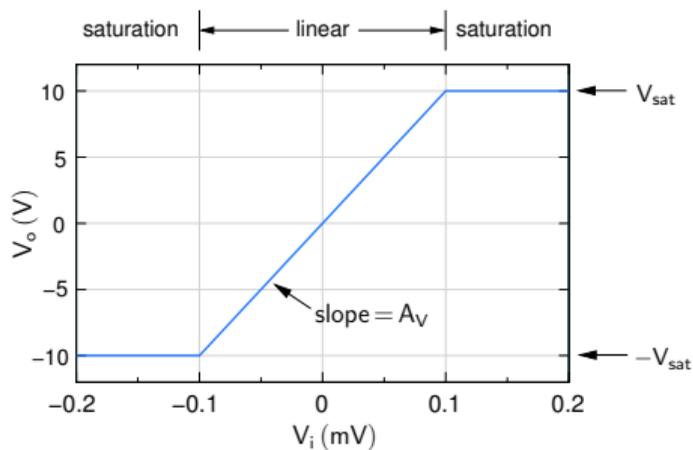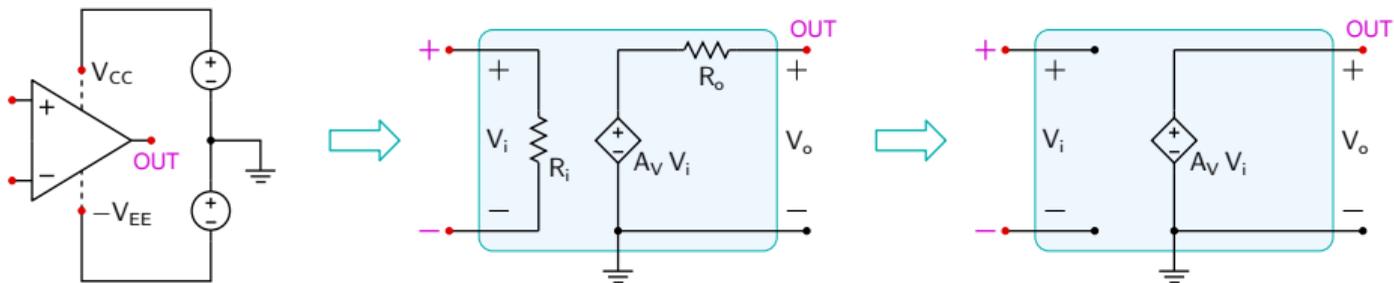



\* The output voltage  $V_o$  is limited to  $\pm V_{sat}$ , where  $V_{sat} \sim 1.5$  V less than  $V_{CC}$ .

# Op-Amp: equivalent circuit

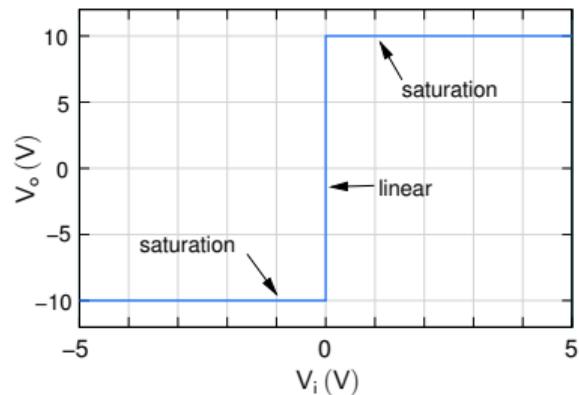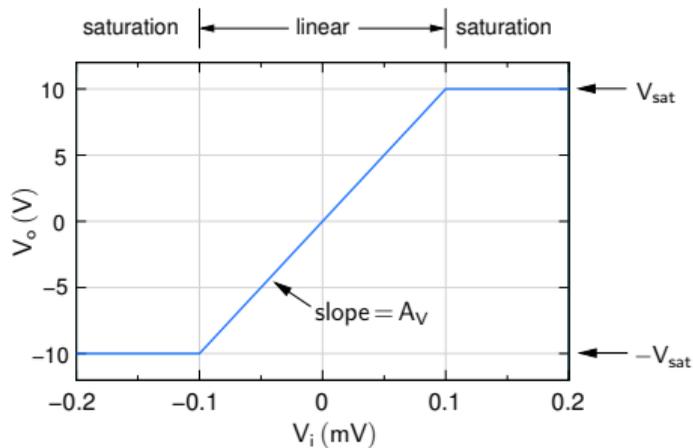
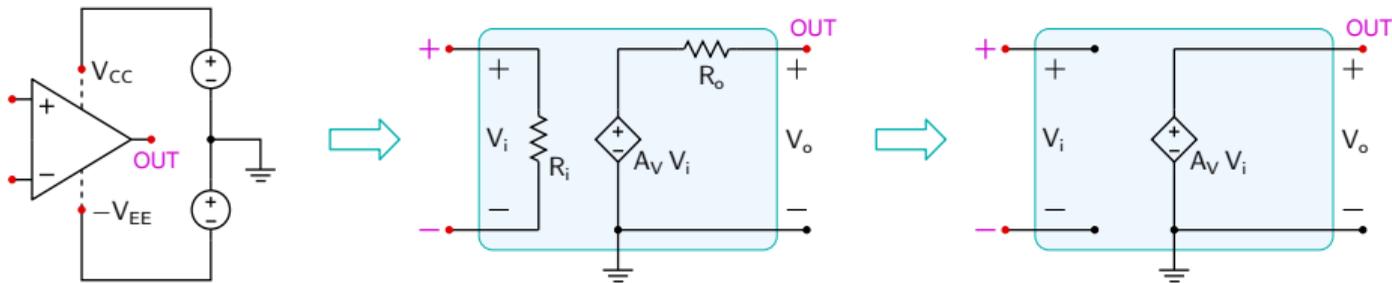


- \* The output voltage  $V_o$  is limited to  $\pm V_{sat}$ , where  $V_{sat} \sim 1.5$  V less than  $V_{CC}$ .
- \* For  $-V_{sat} < V_o < V_{sat}$ ,  $V_i = V_+ - V_- = V_o/A_V$ , which is very small  $\rightarrow V_+$  and  $V_-$  are *virtually* the same.

# Op-amp circuits

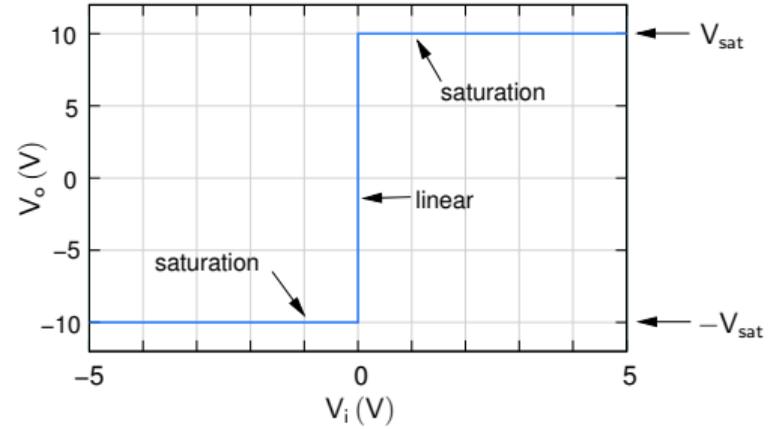
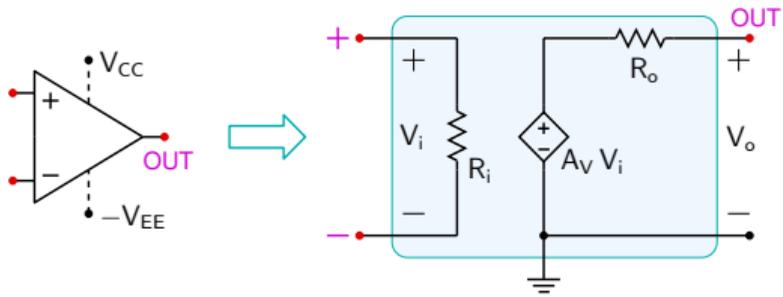


# Op-amp circuits

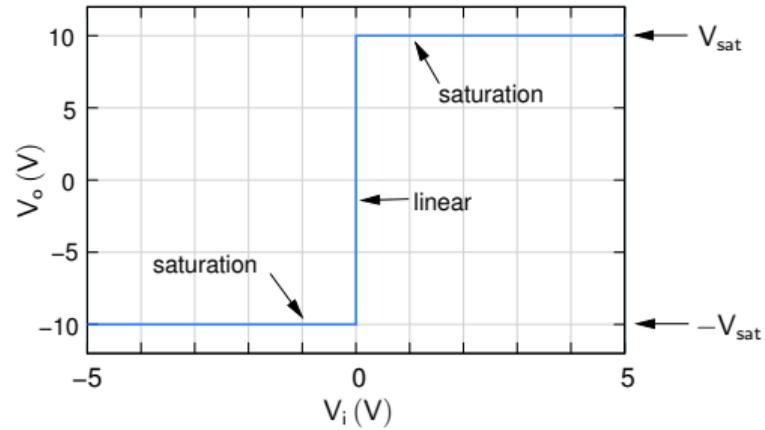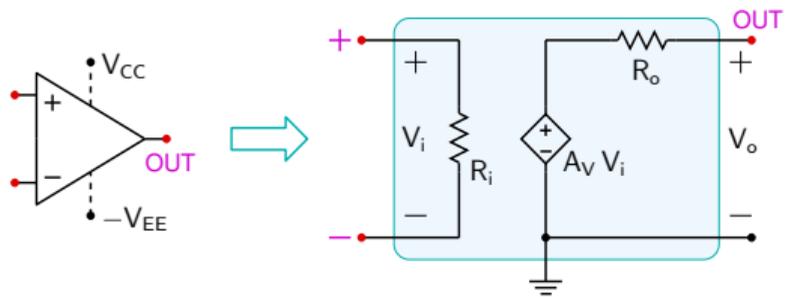



\* Broadly, op-amp circuits can be divided into two categories:

# Op-amp circuits

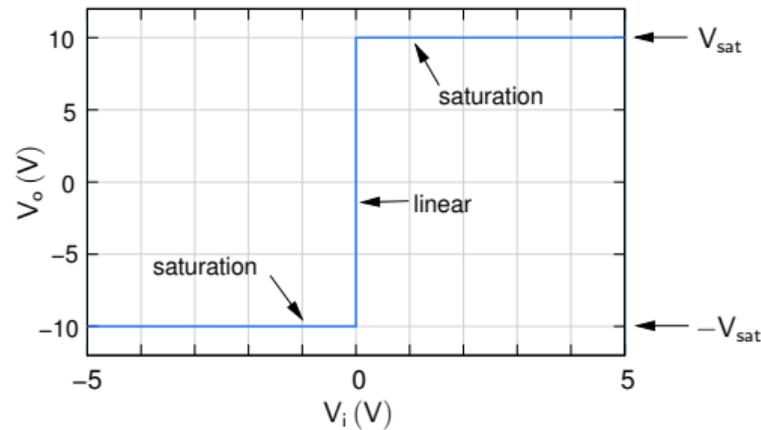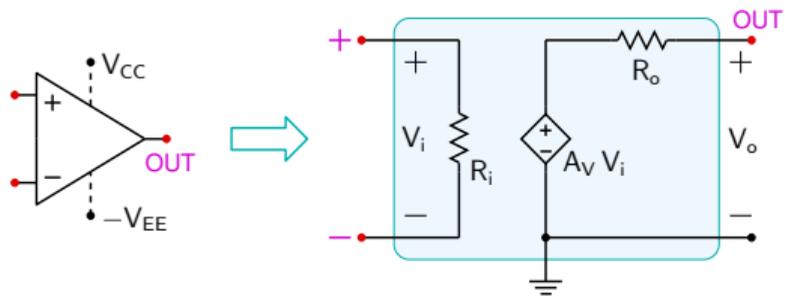

- \* Broadly, op-amp circuits can be divided into two categories:
  - op-amp operating in the linear region



# Op-amp circuits

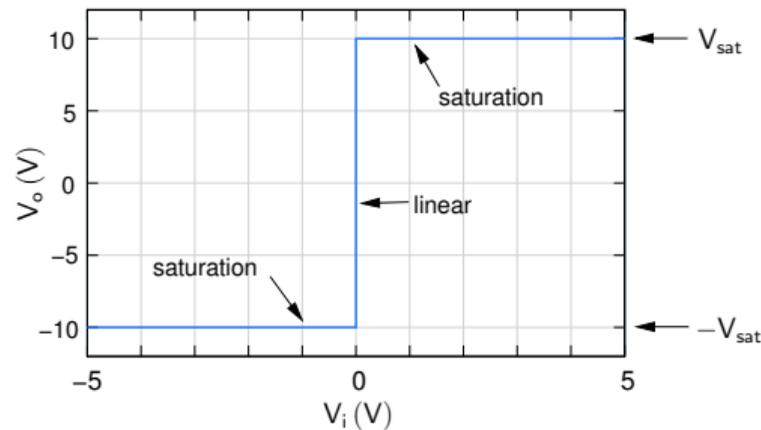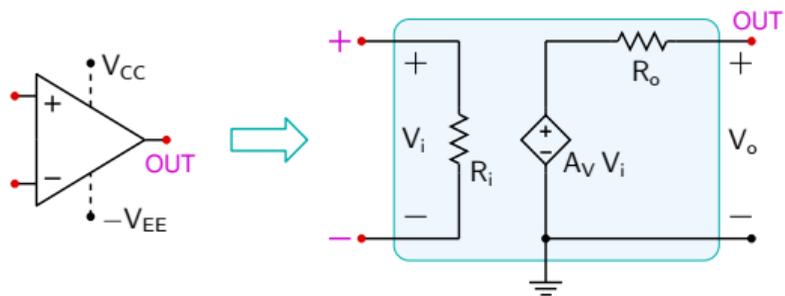

\* Broadly, op-amp circuits can be divided into two categories:

- op-amp operating in the linear region
- op-amp operating in the saturation region

# Op-amp circuits

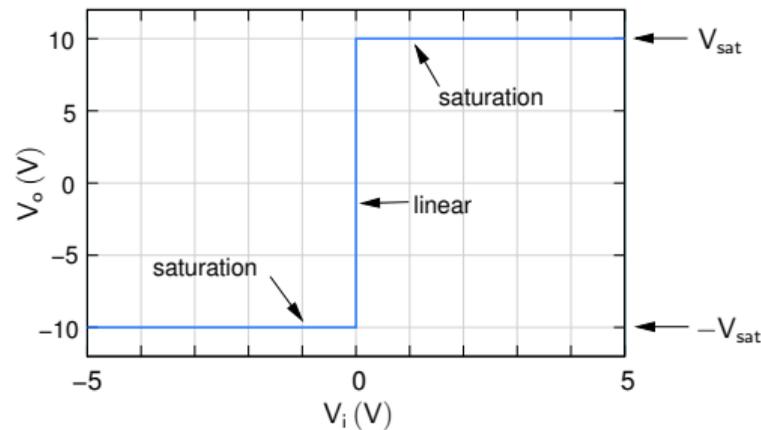
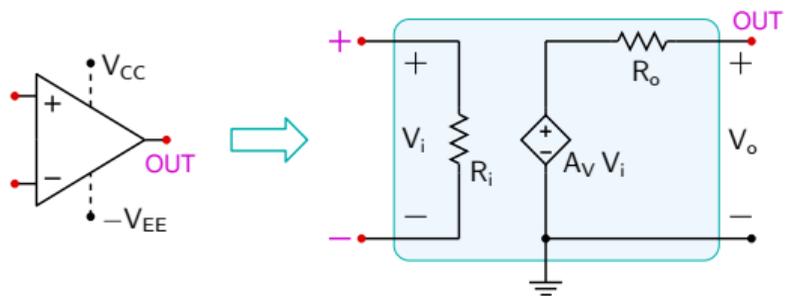


\* Broadly, op-amp circuits can be divided into two categories:

- op-amp operating in the linear region
- op-amp operating in the saturation region

\* Whether an op-amp in a given circuit will operate in linear or saturation region depends on

# Op-amp circuits

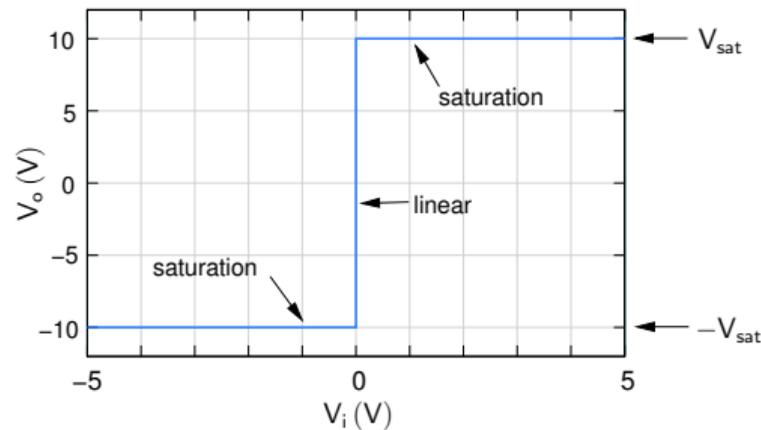
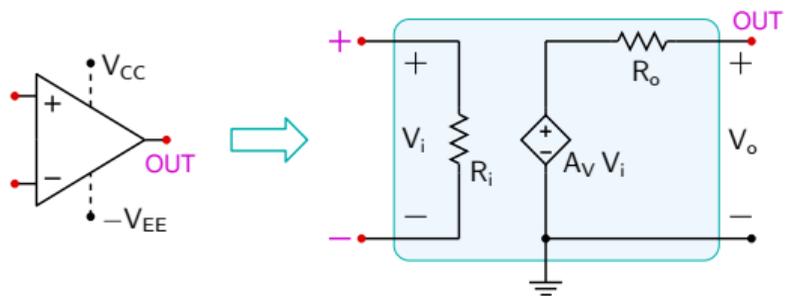


\* Broadly, op-amp circuits can be divided into two categories:

- op-amp operating in the linear region
- op-amp operating in the saturation region

\* Whether an op-amp in a given circuit will operate in linear or saturation region depends on

- input voltage magnitude

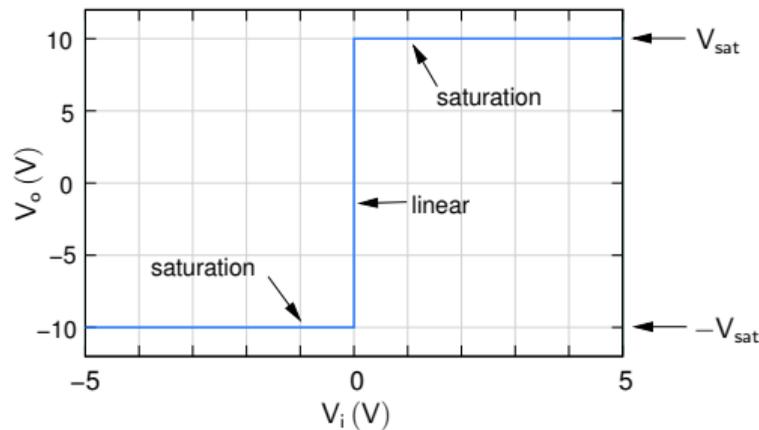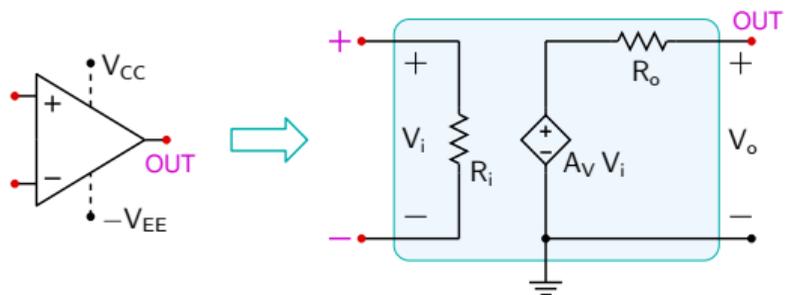



\* Broadly, op-amp circuits can be divided into two categories:

- op-amp operating in the linear region
- op-amp operating in the saturation region



\* Whether an op-amp in a given circuit will operate in linear or saturation region depends on

- input voltage magnitude
- type of feedback (negative or positive)  
(We will take a qualitative look at feedback later.)

# Op-amp circuits (linear region)

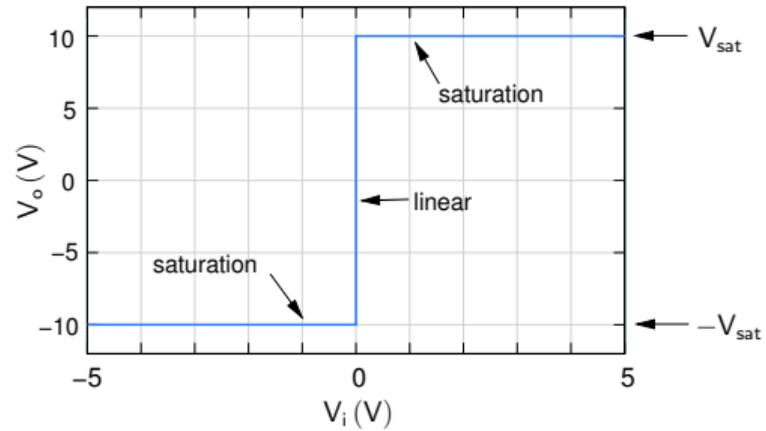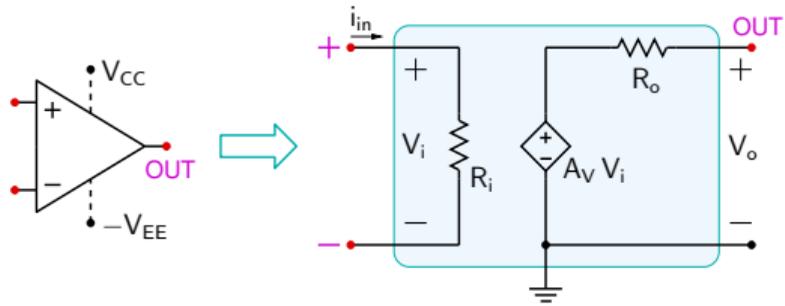

# Op-amp circuits (linear region)

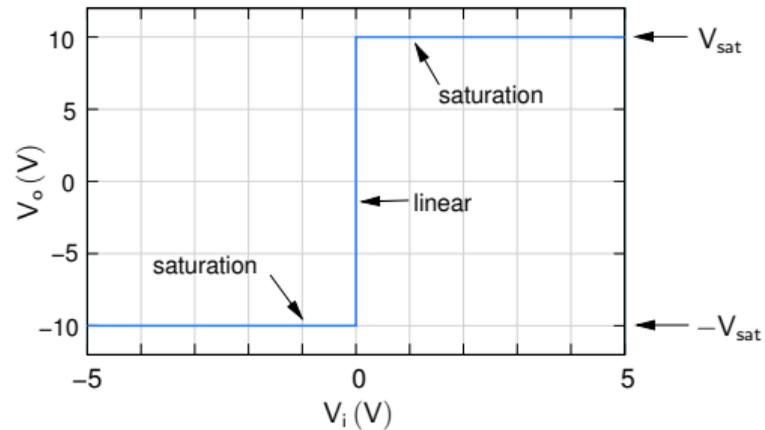
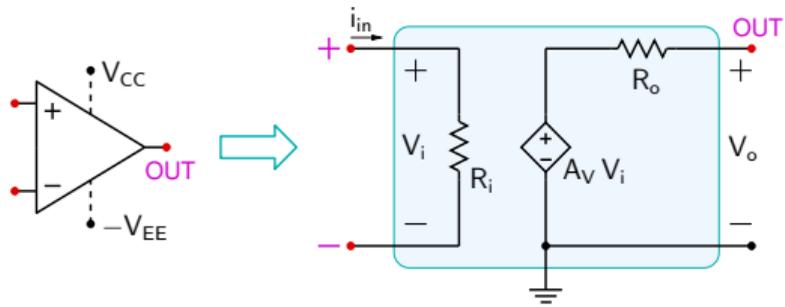


In the linear region,

\*  $V_o = A_V (V_+ - V_-)$ , i.e.,  $V_+ - V_- = V_o/A_V$ , which is very small

$$\rightarrow \boxed{V_+ \approx V_-}$$

# Op-amp circuits (linear region)

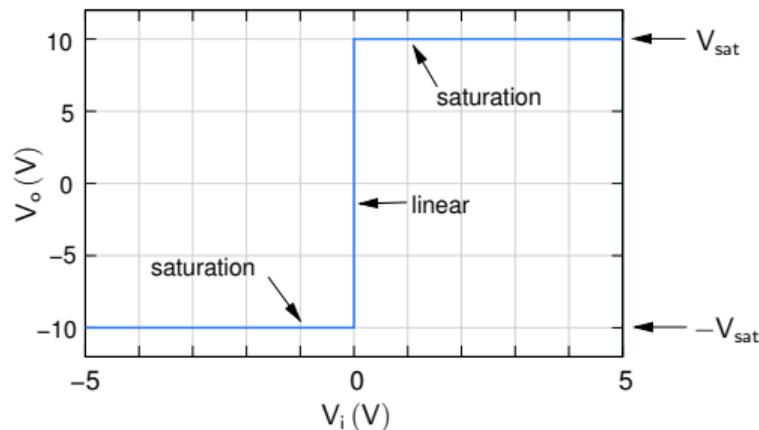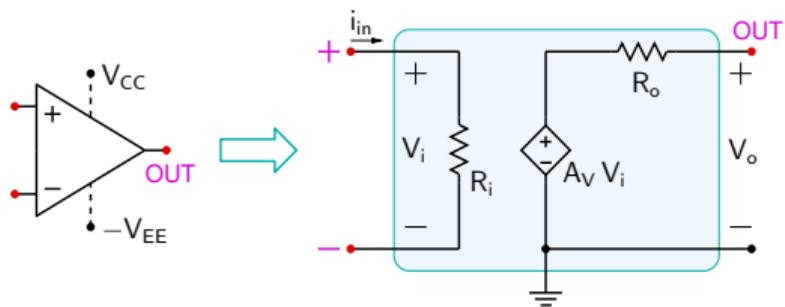

In the linear region,



\*  $V_o = A_V (V_+ - V_-)$ , i.e.,  $V_+ - V_- = V_o/A_V$ , which is very small

$$\rightarrow V_+ \approx V_-$$

\* Since  $R_i$  is typically much larger than other resistances in the circuit, we can assume  $R_i \rightarrow \infty$ .

$$\rightarrow i_{in} \approx 0$$

# Op-amp circuits (linear region)

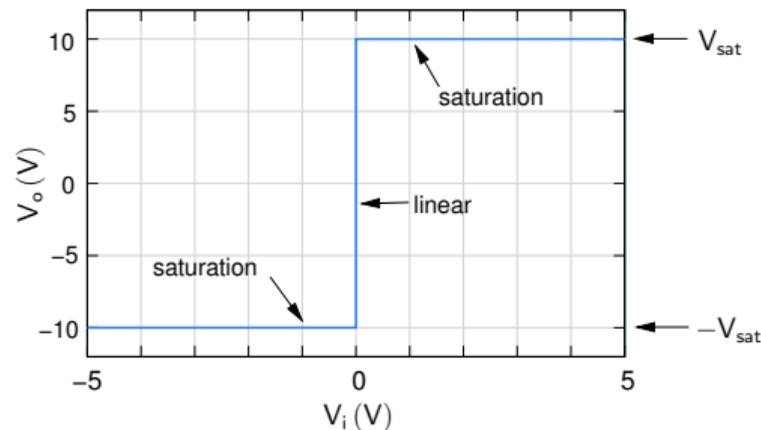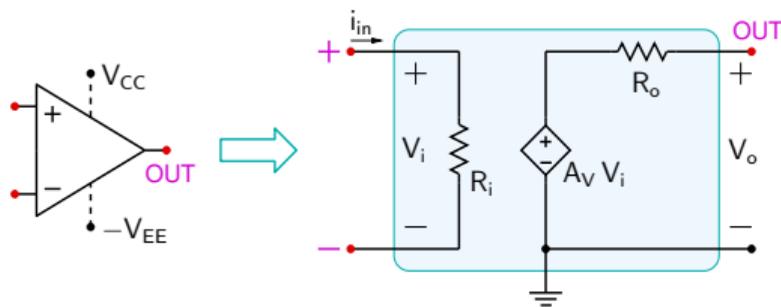

In the linear region,

\*  $V_o = A_V (V_+ - V_-)$ , i.e.,  $V_+ - V_- = V_o/A_V$ , which is very small


$$\rightarrow V_+ \approx V_-$$

\* Since  $R_i$  is typically much larger than other resistances in the circuit, we can assume  $R_i \rightarrow \infty$ .


$$\rightarrow i_{in} \approx 0$$

These two "golden rules" enable us to understand several op-amp circuits.

## Op-amp circuits (linear region)

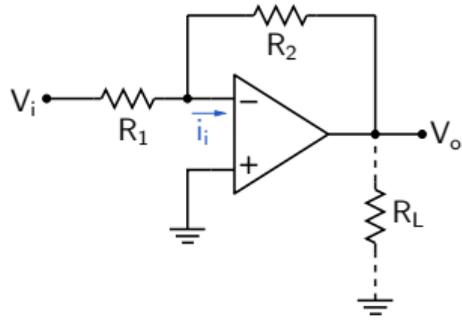


## Op-amp circuits (linear region)

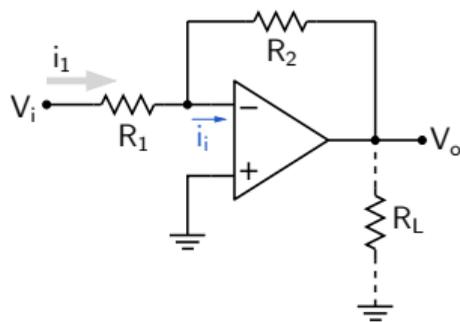

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

## Op-amp circuits (linear region)

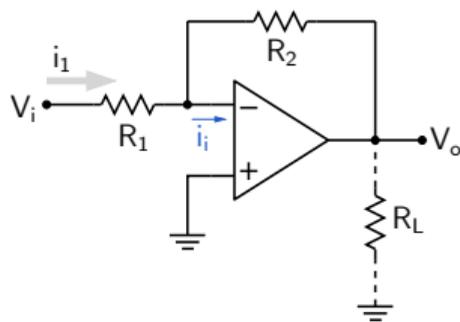


Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the op-amp) is zero,  $i_1$  goes through  $R_2$ .

## Op-amp circuits (linear region)

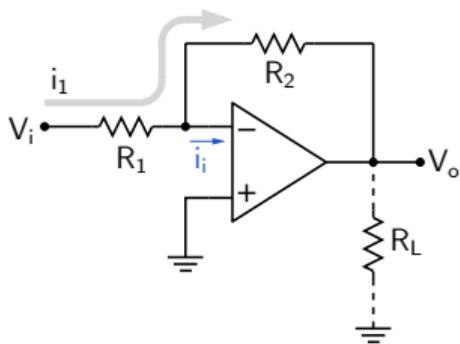


Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the op-amp) is zero,  $i_1$  goes through  $R_2$ .

## Op-amp circuits (linear region)

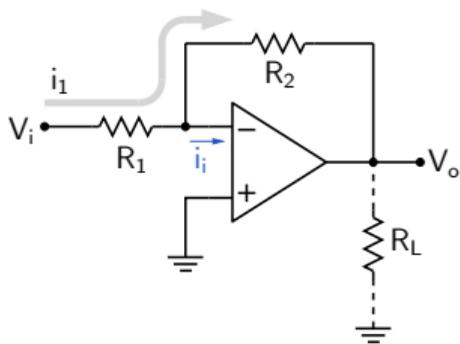


Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the op-amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

## Op-amp circuits (linear region)

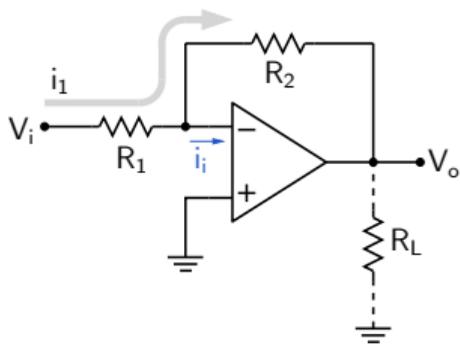

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .


(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the op-amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

The circuit is called an “inverting amplifier.”

## Op-amp circuits (linear region)

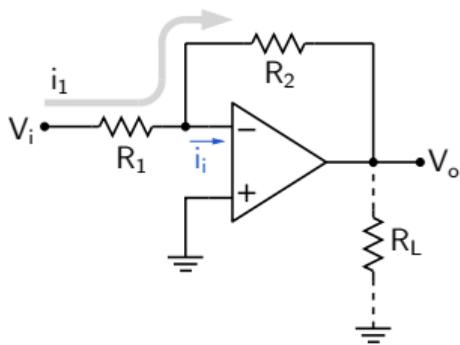

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)


Since  $i_i$  (current entering the op-amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

The circuit is called an “inverting amplifier.”

Where does the current go?

## Op-amp circuits (linear region)

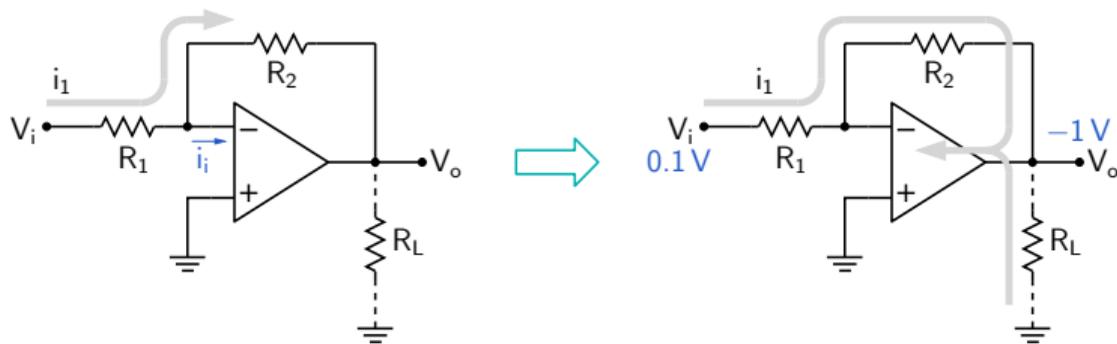

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)


Since  $i_i$  (current entering the op-amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

The circuit is called an “inverting amplifier.”

Where does the current go?

## Op-amp circuits (linear region)

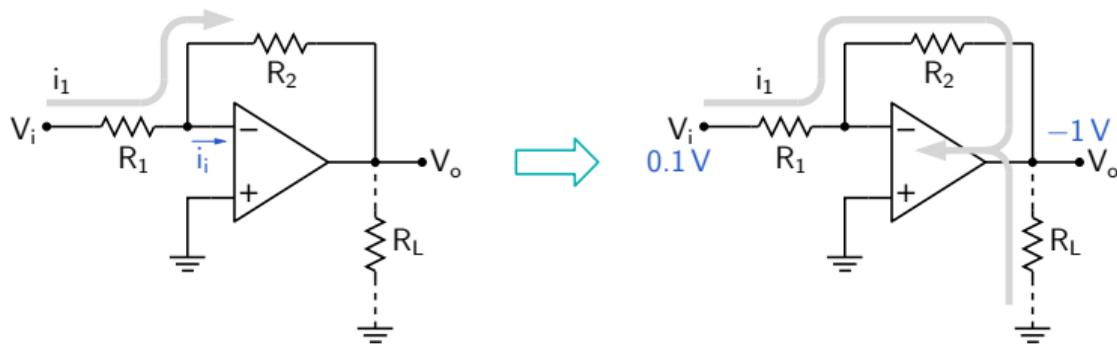

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R_1 = V_i/R_1$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the op-amp) is zero,  $i_1$  goes through  $R_2$ .



$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left(\frac{V_i}{R_1}\right) R_2 = -\left(\frac{R_2}{R_1}\right) V_i.$$

The circuit is called an “inverting amplifier.”



Where does the current go?

(Op-amp 741 can source or sink about 25 mA.)

## Op-amp circuits: inverting amplifier

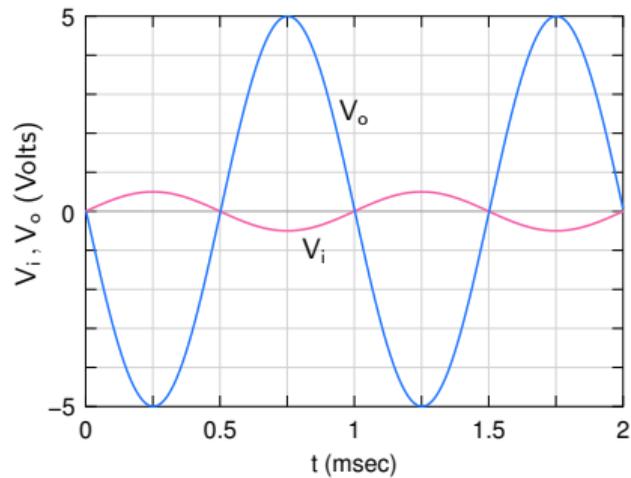
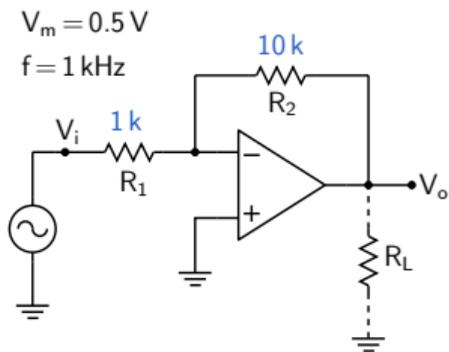


## Op-amp circuits: inverting amplifier

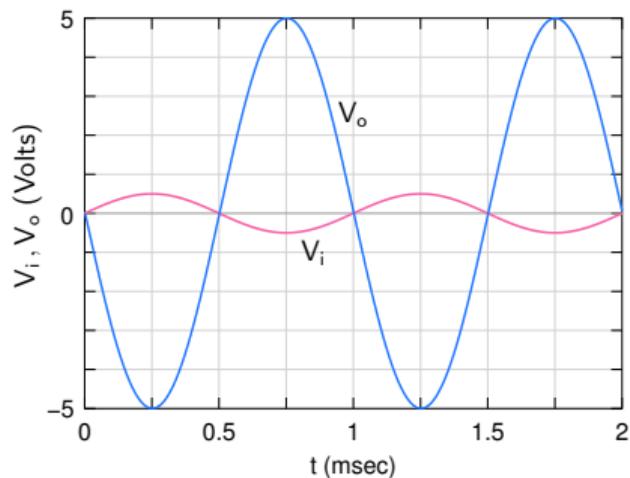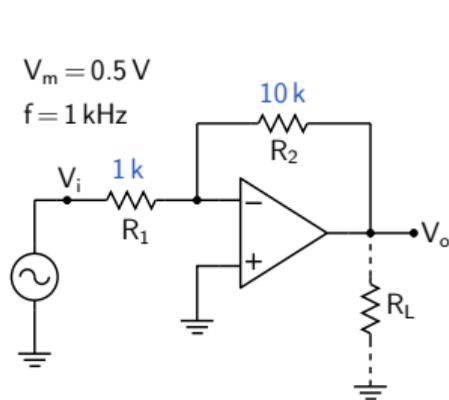



- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the op-amp which is  $\sim 10^5$ ).

## Op-amp circuits: inverting amplifier

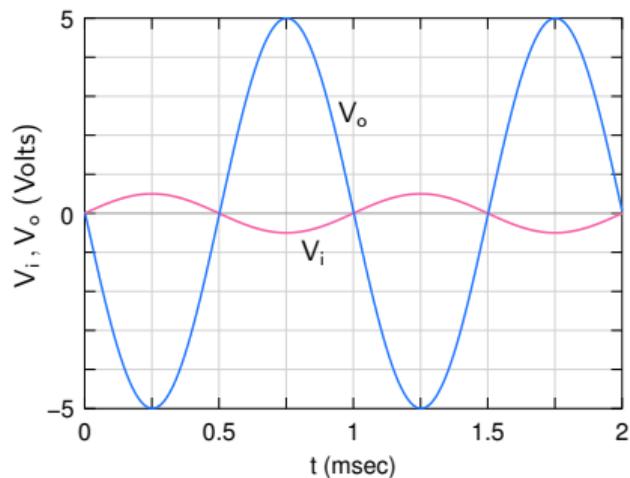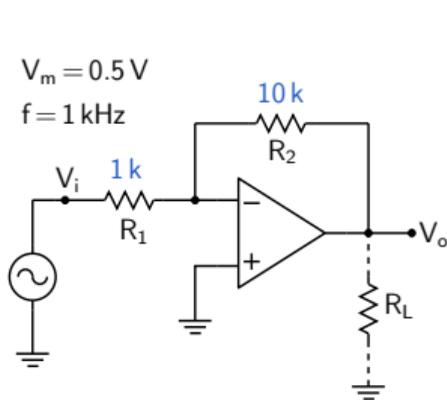



- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the op-amp which is  $\sim 10^5$ ).
- \* The gain can be adjusted simply by changing  $R_1$  or  $R_2$  !

## Op-amp circuits: inverting amplifier

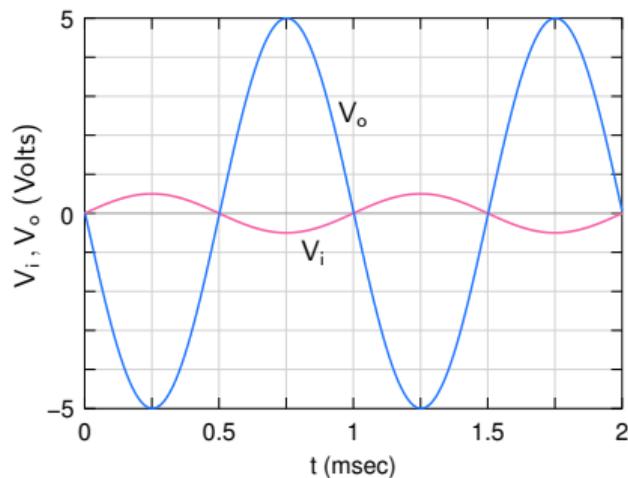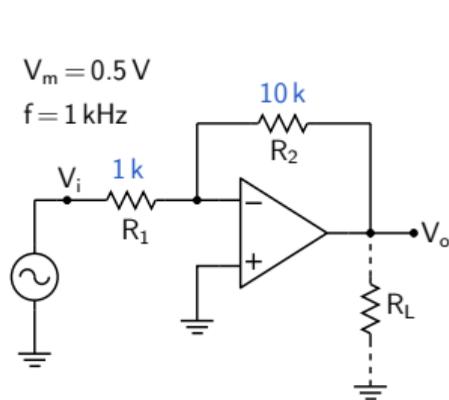

- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the op-amp which is  $\sim 10^5$ ).
- \* The gain can be adjusted simply by changing  $R_1$  or  $R_2$  !
- \* For the common-emitter amplifier, on the other hand, the gain  $-g_m (R_C \parallel R_L)$  depends on how the BJT is biased (since  $g_m$  depends on  $I_C$ ).



## Op-amp circuits: inverting amplifier

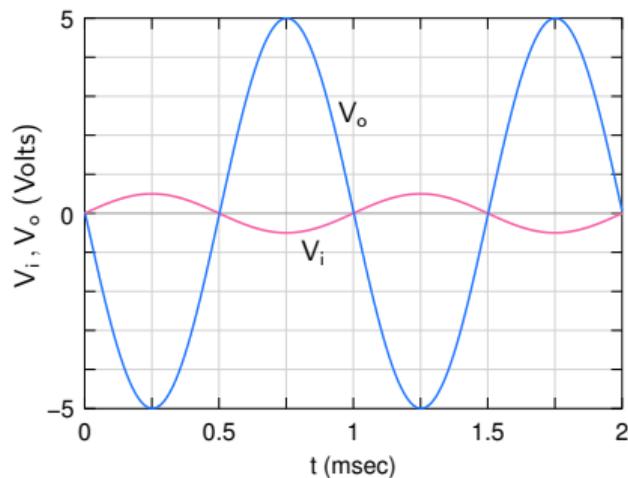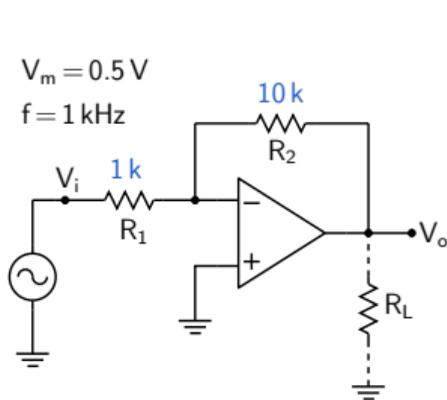



- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the op-amp which is  $\sim 10^5$ ).
- \* The gain can be adjusted simply by changing  $R_1$  or  $R_2$  !
- \* For the common-emitter amplifier, on the other hand, the gain  $-g_m (R_C \parallel R_L)$  depends on how the BJT is biased (since  $g_m$  depends on  $I_C$ ).

(SEQUEL file: ee101\_inv\_amp.1.sqproj)

## Op-amp circuits: inverting amplifier

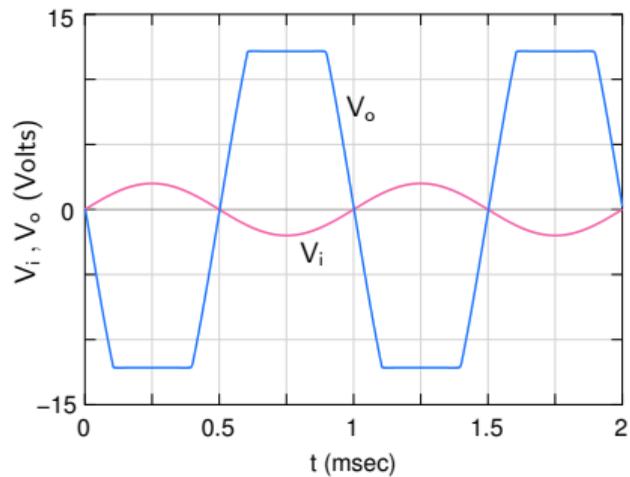
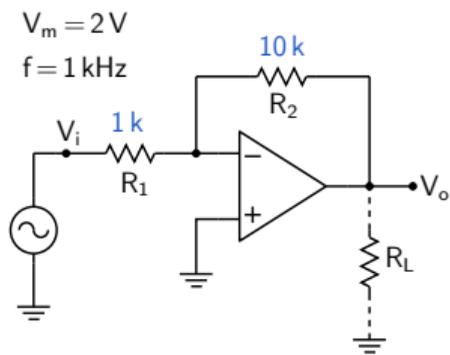


## Op-amp circuits: inverting amplifier

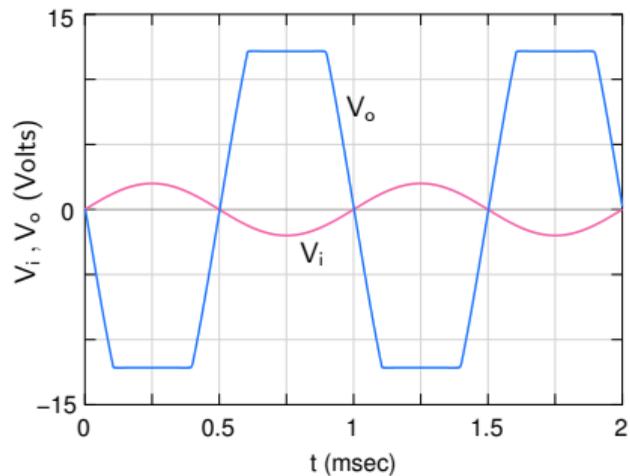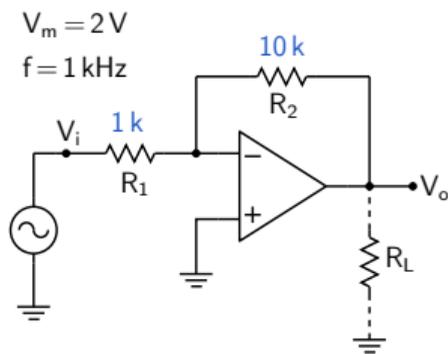



\* The output voltage is limited to  $\pm V_{\text{sat}}$ .

## Op-amp circuits: inverting amplifier

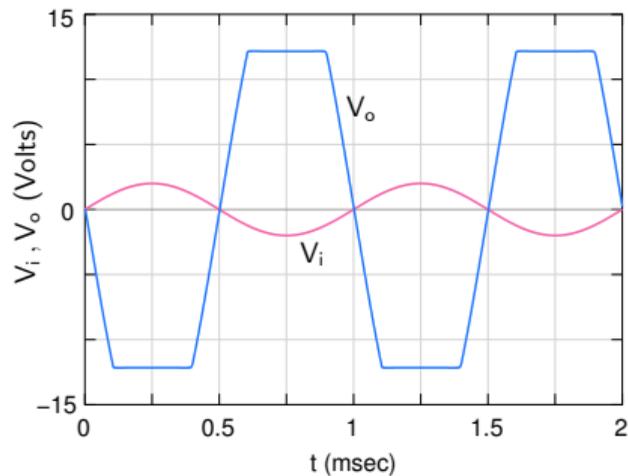
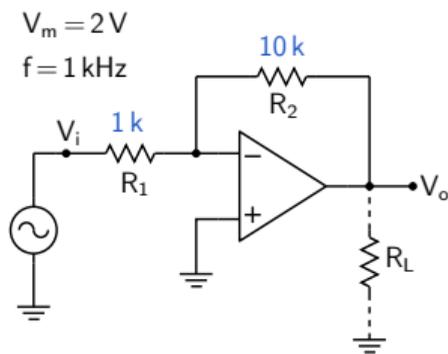


- \* The output voltage is limited to  $\pm V_{sat}$ .
- \*  $V_{sat}$  is  $\sim 1.5V$  less than the supply voltage  $V_{CC}$ .

## Op-amp circuits: inverting amplifier

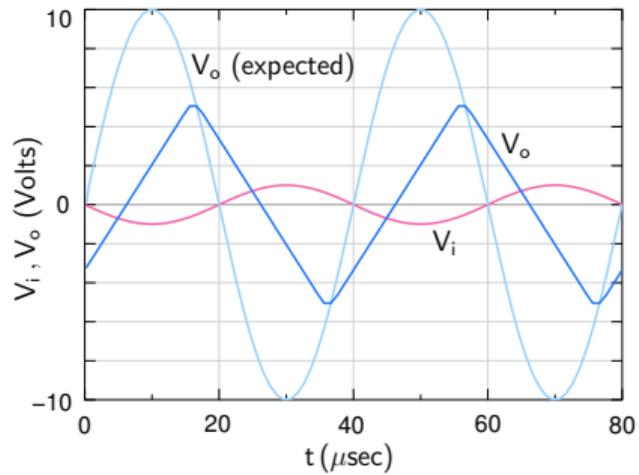
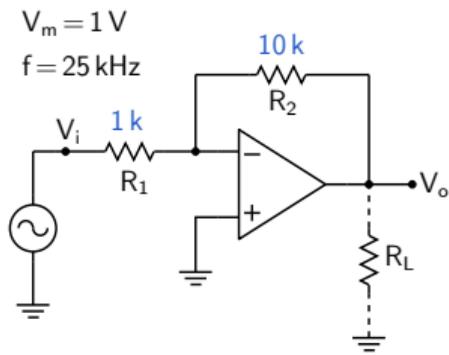


## Op-amp circuits: inverting amplifier

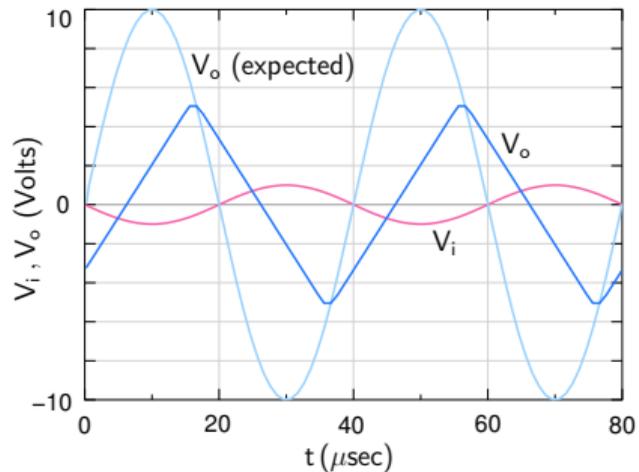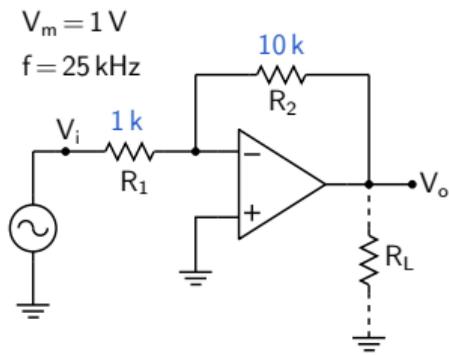



- \* If the signal frequency is too high, a practical op-amp cannot keep up with the input due to its “slew rate” limitation.

## Op-amp circuits: inverting amplifier

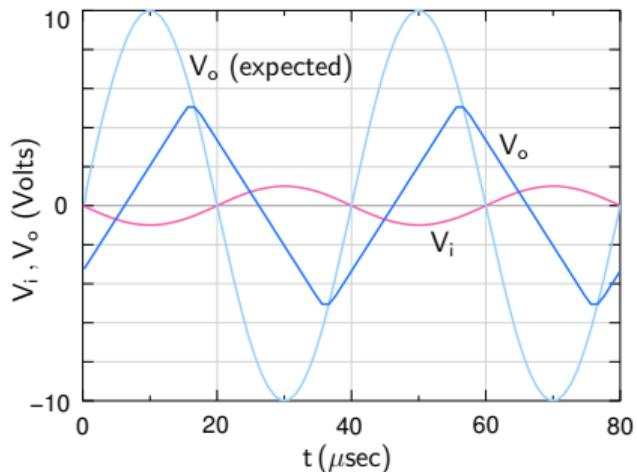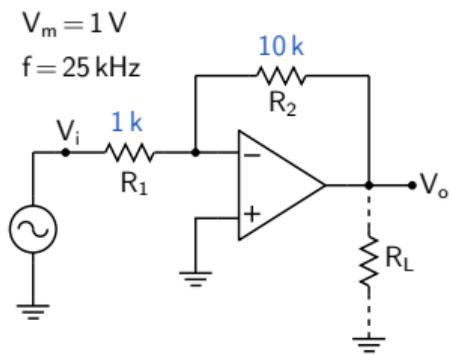



- \* If the signal frequency is too high, a practical op-amp cannot keep up with the input due to its “slew rate” limitation.
- \* The slew rate of an op-amp is the maximum rate at which the op-amp output can rise (or fall).

## Op-amp circuits: inverting amplifier

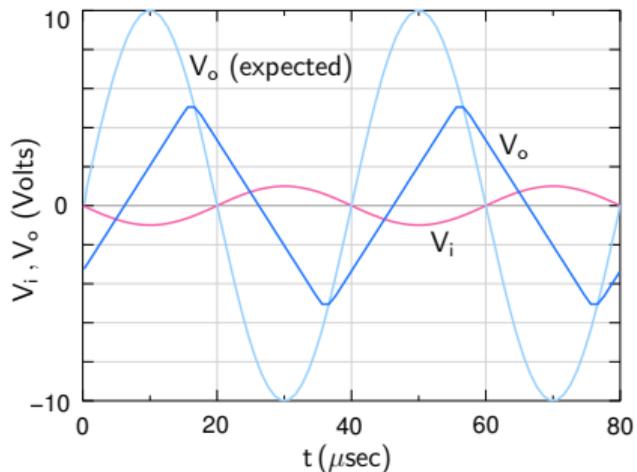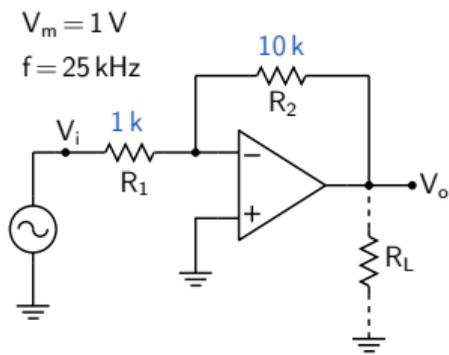

- \* If the signal frequency is too high, a practical op-amp cannot keep up with the input due to its “slew rate” limitation.
- \* The slew rate of an op-amp is the maximum rate at which the op-amp output can rise (or fall).
- \* For the 741, the slew rate is  $0.5\text{ V}/\mu\text{sec}$ .



## Op-amp circuits: inverting amplifier

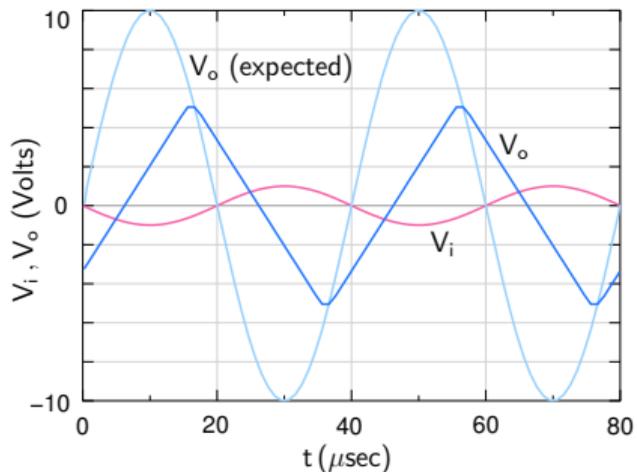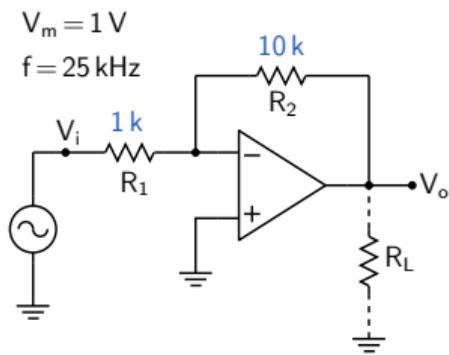

- \* If the signal frequency is too high, a practical op-amp cannot keep up with the input due to its “slew rate” limitation.
- \* The slew rate of an op-amp is the maximum rate at which the op-amp output can rise (or fall).
- \* For the 741, the slew rate is  $0.5\text{ V}/\mu\text{sec}$ .



(SEQUEL file: ee101\_inv\_amp.2.sqproj)

## Op-amp circuits: inverting amplifier

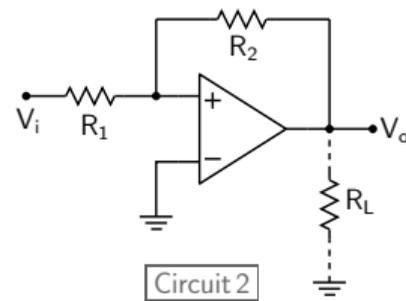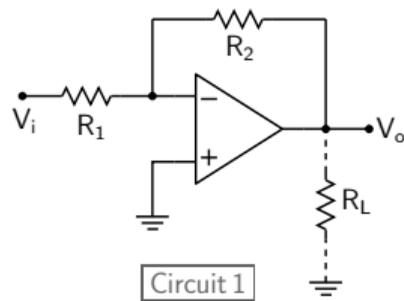

What if the + (non-inverting) and - (inverting) inputs of the op-amp are interchanged?



## Op-amp circuits: inverting amplifier

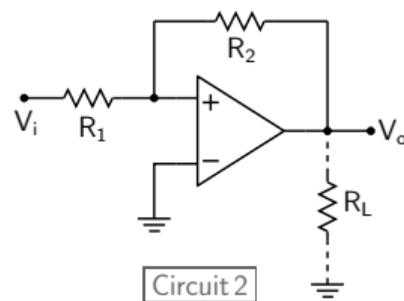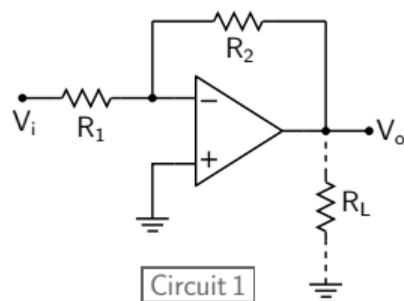

What if the + (non-inverting) and - (inverting) inputs of the op-amp are interchanged?

Our previous analysis would once again give us  $V_o = -\frac{R_2}{R_1} V_i$ .

## Op-amp circuits: inverting amplifier

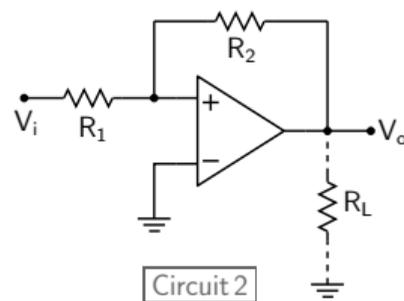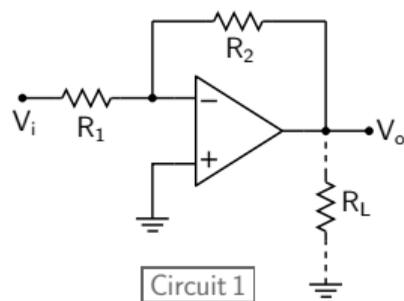

What if the + (non-inverting) and - (inverting) inputs of the op-amp are interchanged?



Our previous analysis would once again give us  $V_o = -\frac{R_2}{R_1} V_i$ .

However, from Circuit 1 to Circuit 2, the nature of the feedback changes from negative to positive.

→ Our assumption that the op-amp is working in the linear region does not hold for Circuit 2, and

$V_o = -\frac{R_2}{R_1} V_i$  does not apply any more.

## Op-amp circuits: inverting amplifier

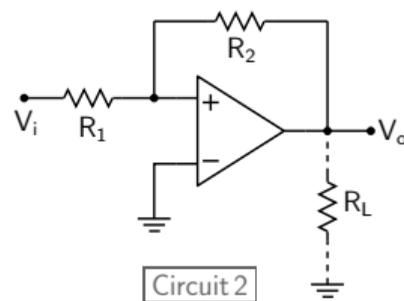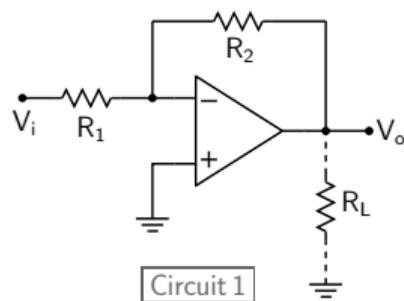

What if the + (non-inverting) and - (inverting) inputs of the op-amp are interchanged?

Our previous analysis would once again give us  $V_o = -\frac{R_2}{R_1} V_i$ .


However, from Circuit 1 to Circuit 2, the nature of the feedback changes from negative to positive.

→ Our assumption that the op-amp is working in the linear region does not hold for Circuit 2, and

$V_o = -\frac{R_2}{R_1} V_i$  does not apply any more.


(Circuit 2 is also useful, and we will discuss it later.)

## Op-amp circuits (linear region)

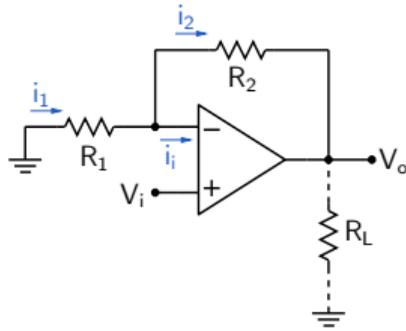

\*  $V_+ \approx V_- = V_i$


## Op-amp circuits (linear region)

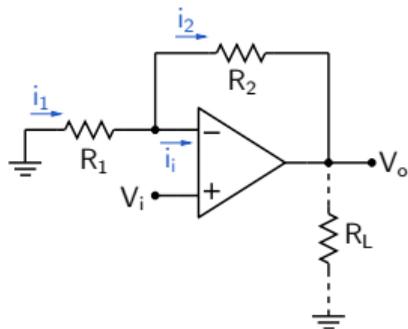

\*  $V_+ \approx V_- = V_i$

$\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1.$

## Op-amp circuits (linear region)

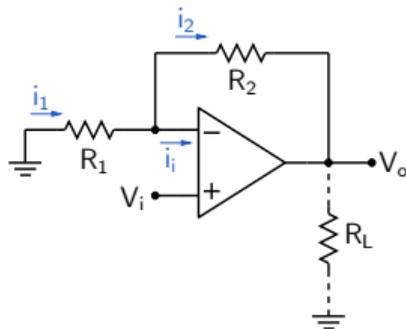


\*  $V_+ \approx V_- = V_i$

→  $i_1 = (0 - V_i)/R_1 = -V_i/R_1$ .


\* Since  $i_i = 0$ ,  $i_2 = i_1 \rightarrow V_o = V_- - i_2 R_2 = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right)$ .

## Op-amp circuits (linear region)

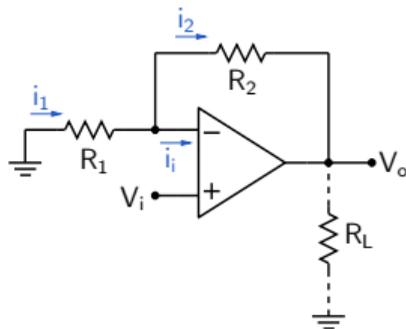

- \*  $V_+ \approx V_- = V_i$   
 $\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1$ .
- \* Since  $i_i = 0$ ,  $i_2 = i_1 \rightarrow V_o = V_- - i_2 R_2 = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right)$ .
- \* This circuit is known as the “non-inverting amplifier.”

## Op-amp circuits (linear region)

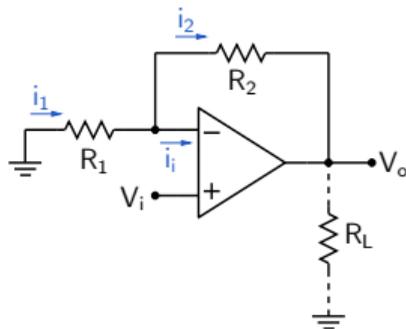

- \*  $V_+ \approx V_- = V_i$


- $\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1.$

- \* Since  $i_i = 0$ ,  $i_2 = i_1 \rightarrow V_o = V_- - i_2 R_2 = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right).$


- \* This circuit is known as the “non-inverting amplifier.”

- \* Again, interchanging + and - changes the nature of the feedback from negative to positive, and the circuit operation becomes completely different.

## Inverting or non-inverting?

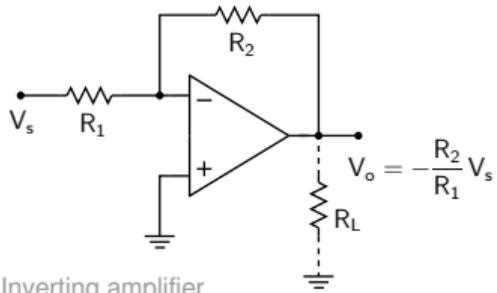


Inverting amplifier

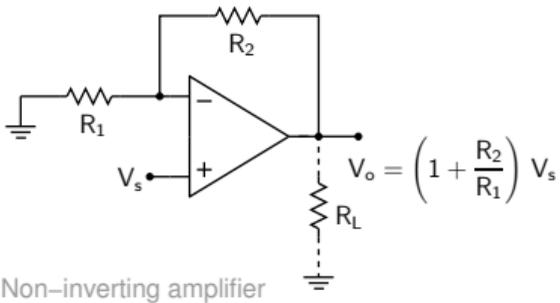


Non-inverting amplifier

- \* If the sign of the output voltage is not a concern, which configuration should be preferred?


## Inverting or non-inverting?

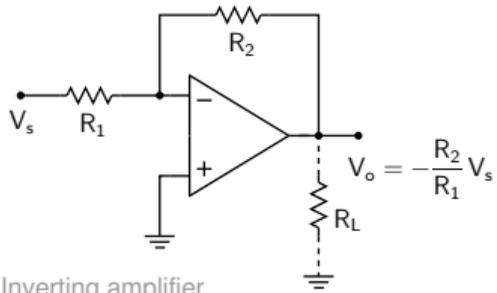

Inverting amplifier



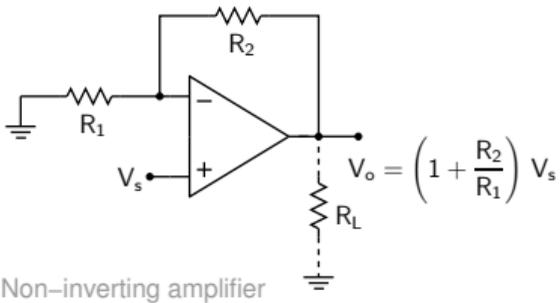


Non-inverting amplifier

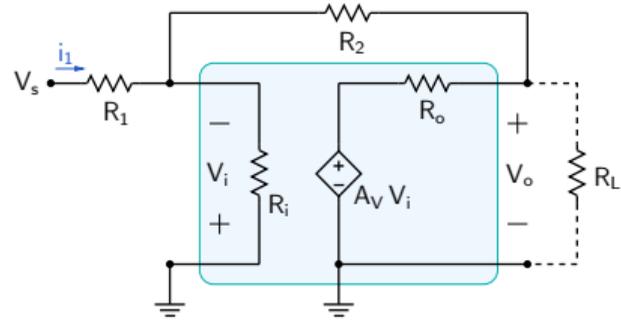


- \* If the sign of the output voltage is not a concern, which configuration should be preferred?

## Inverting or non-inverting?

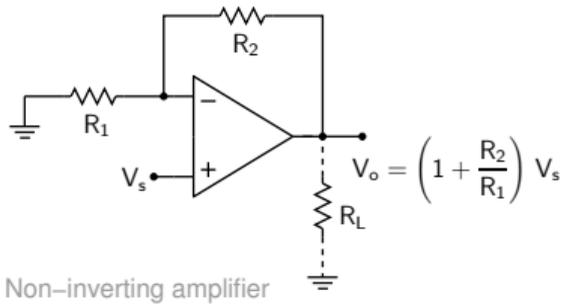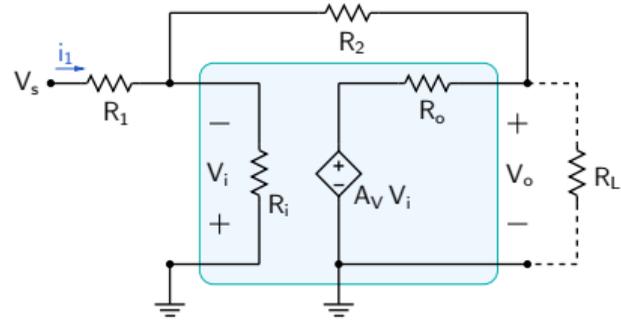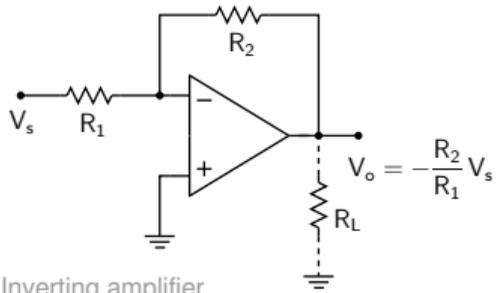


- \* If the sign of the output voltage is not a concern, which configuration should be preferred?
- \* For the inverting amplifier, since  $V_- \approx 0\text{ V}$ ,  $i_1 = V_s/R_1 \rightarrow R_{\text{in}} = V_s/i_1 = R_1$ .



## Inverting or non-inverting?

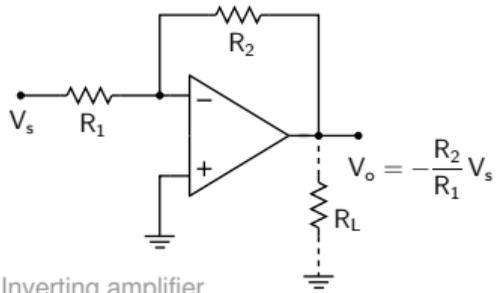

Inverting amplifier

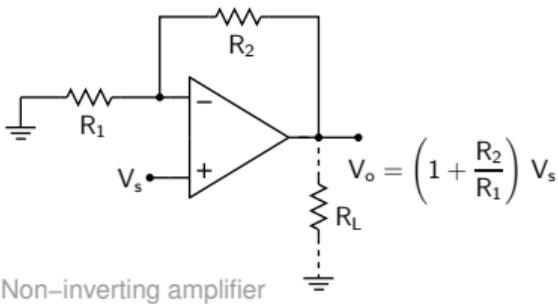


Non-inverting amplifier

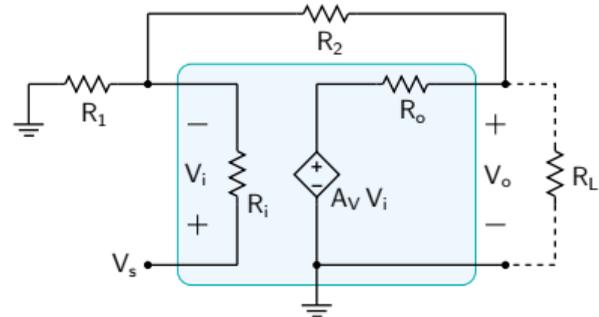
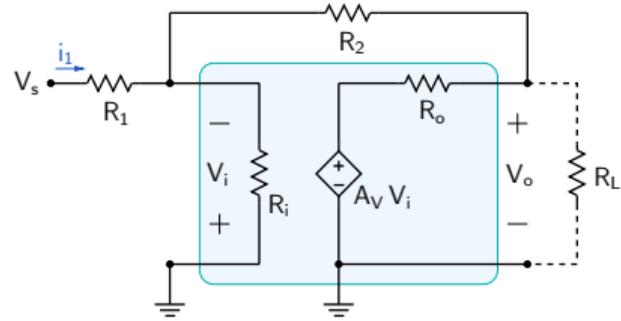


- \* If the sign of the output voltage is not a concern, which configuration should be preferred?
- \* For the inverting amplifier, since  $V_- \approx 0 V$ ,  $i_1 = V_s/R_1 \rightarrow R_{in} = V_s/i_1 = R_1$ .


# Inverting or non-inverting?

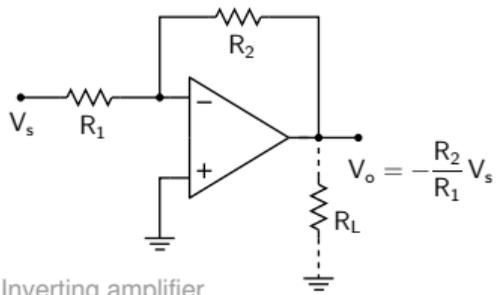

Inverting amplifier

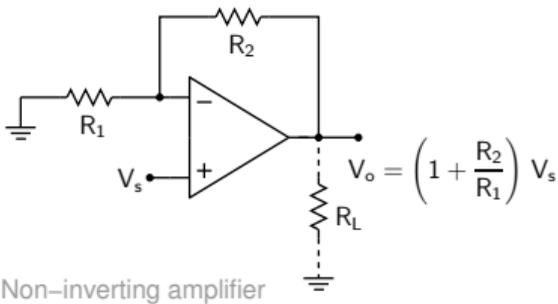
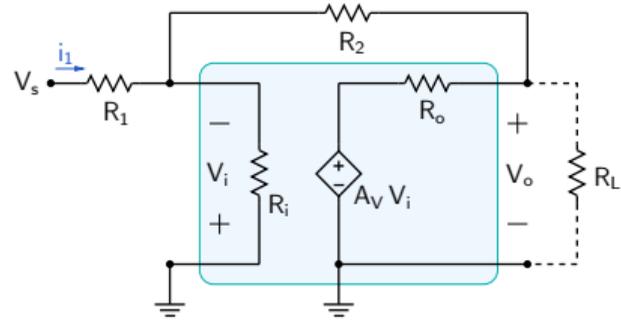


Non-inverting amplifier

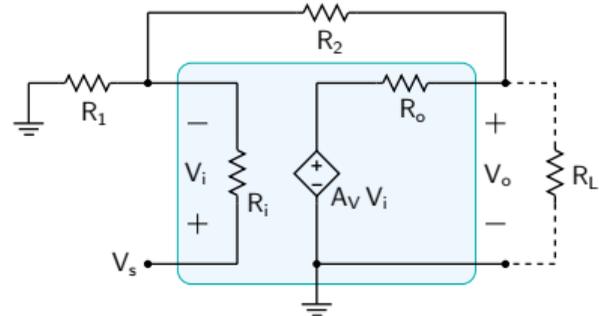


- \* If the sign of the output voltage is not a concern, which configuration should be preferred?
- \* For the inverting amplifier, since  $V_- \approx 0 V$ ,  $i_1 = V_s/R_1 \rightarrow R_{in} = V_s/i_1 = R_1$ .
- \* For the non-inverting amplifier,  $R_{in} \sim R_i A_V \frac{R_1}{R_1 + R_2}$ . Huge!

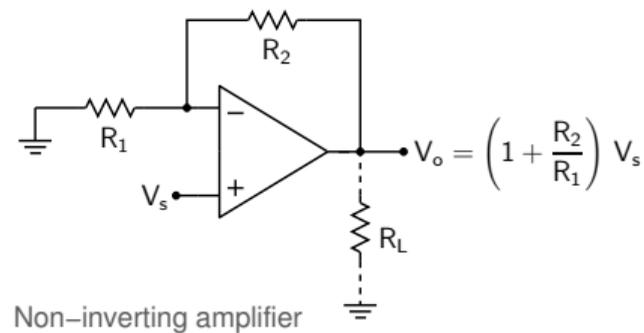
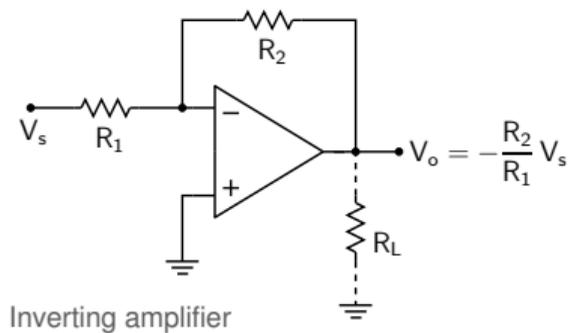
## Inverting and non-inverting amplifiers: summary






# Non-inverting amplifier

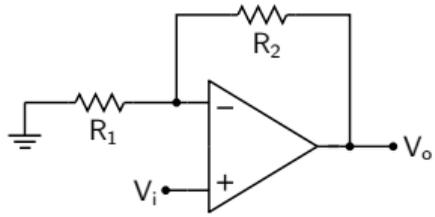





# Non-inverting amplifier

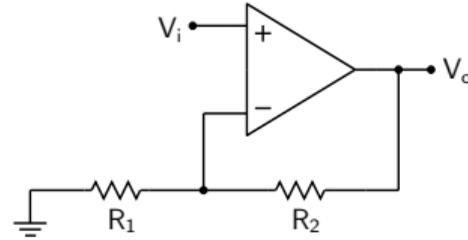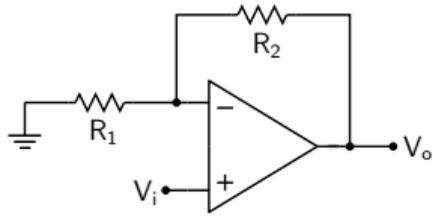


# Non-inverting amplifier

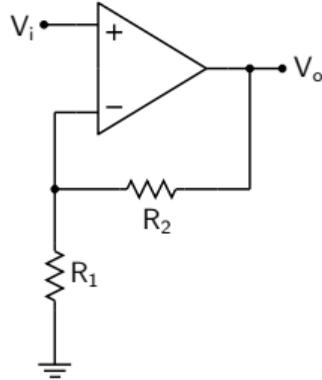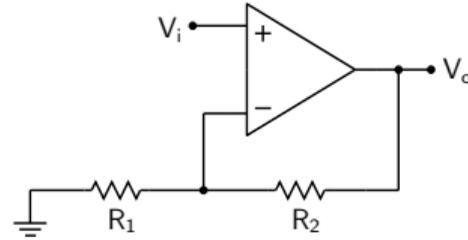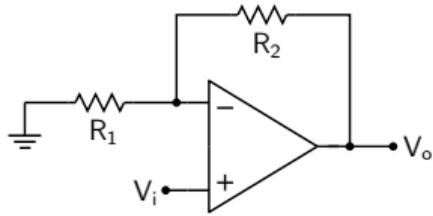

# Non-inverting amplifier

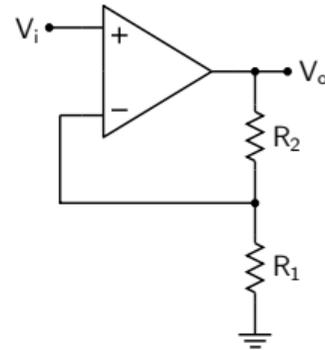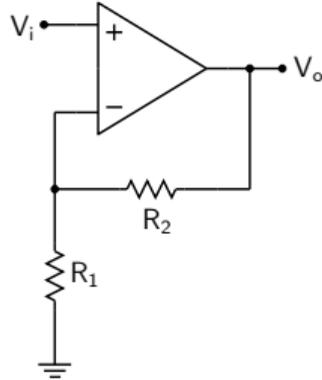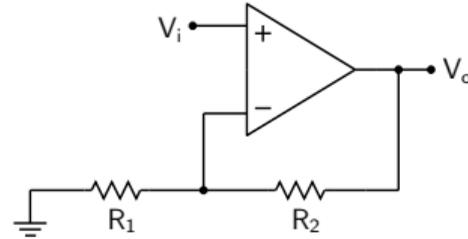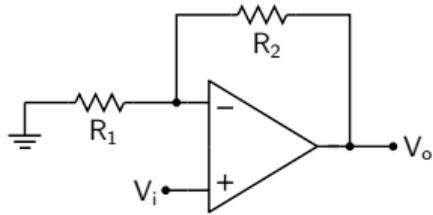


# Non-inverting amplifier

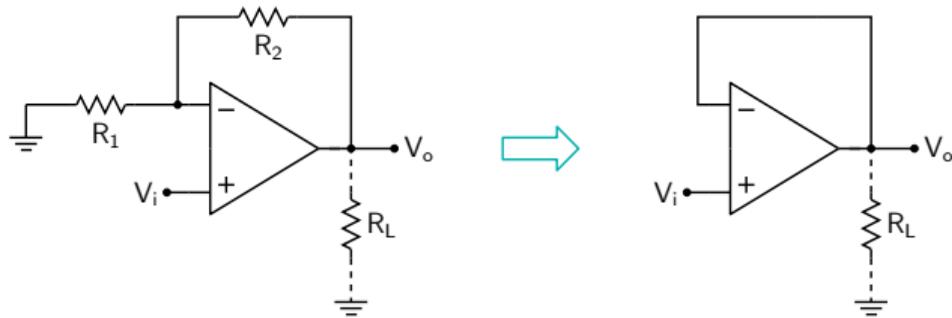

Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .


## Non-inverting amplifier

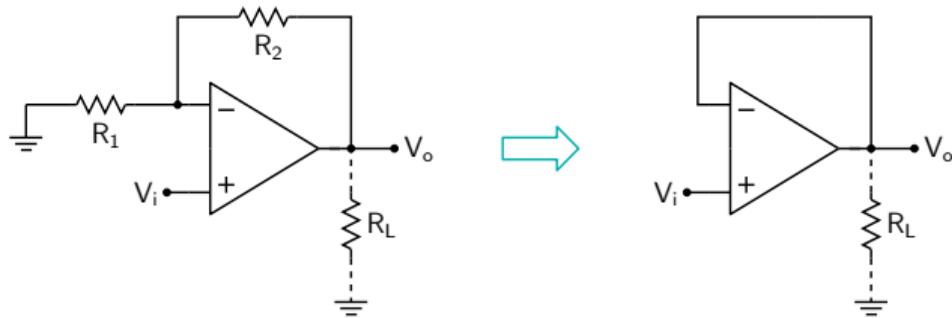

Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .

$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

## Non-inverting amplifier

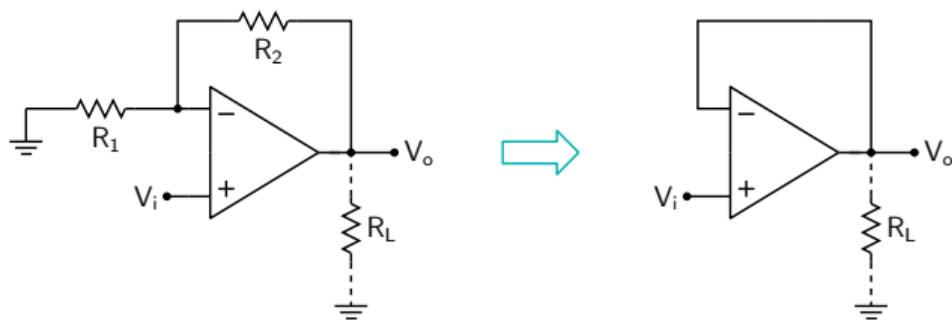


Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .

$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

This circuit is known as unity-gain amplifier/voltage follower/buffer.

## Non-inverting amplifier

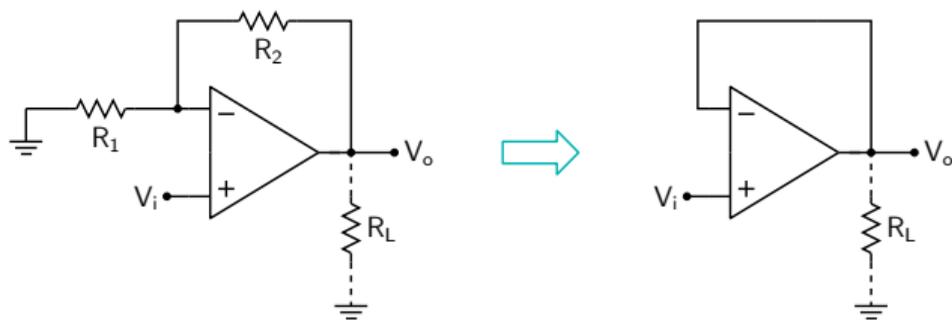


Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .


$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

This circuit is known as unity-gain amplifier/voltage follower/buffer.

What has been achieved?

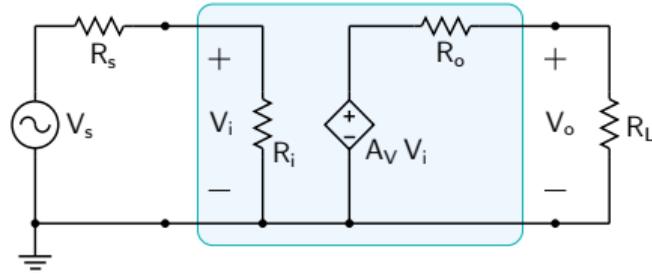

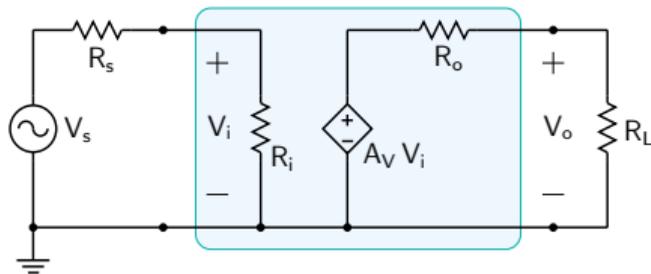
Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .



Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .

However, the actual output voltage is,
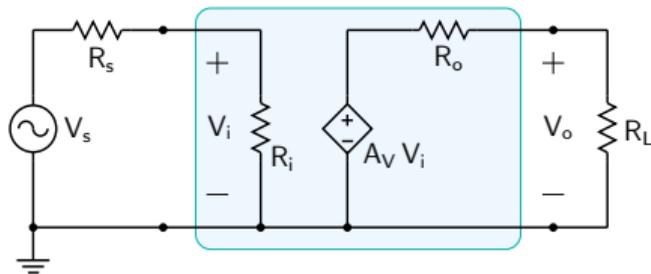
$$V_o = \frac{R_L}{R_o + R_L} A_V V_i = A_V \frac{R_L}{R_o + R_L} \frac{R_i}{R_i + R_s} V_s.$$




Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .

However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} A_V V_i = A_V \frac{R_L}{R_o + R_L} \frac{R_i}{R_i + R_s} V_s.$$

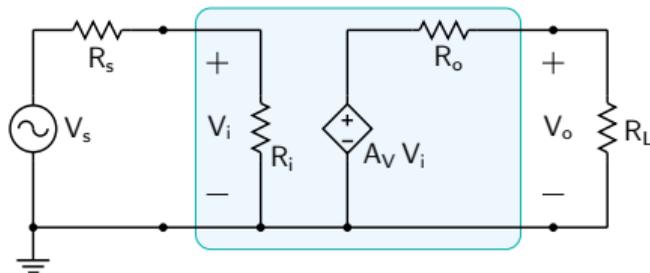To obtain the desired  $V_o$ , we need  $R_i \rightarrow \infty$  and  $R_o \rightarrow 0$ .



Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .



However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} A_V V_i = A_V \frac{R_L}{R_o + R_L} \frac{R_i}{R_i + R_s} V_s.$$



To obtain the desired  $V_o$ , we need  $R_i \rightarrow \infty$  and  $R_o \rightarrow 0$ .

The buffer (voltage follower) provides these features.

# Op-amp buffer: input resistance

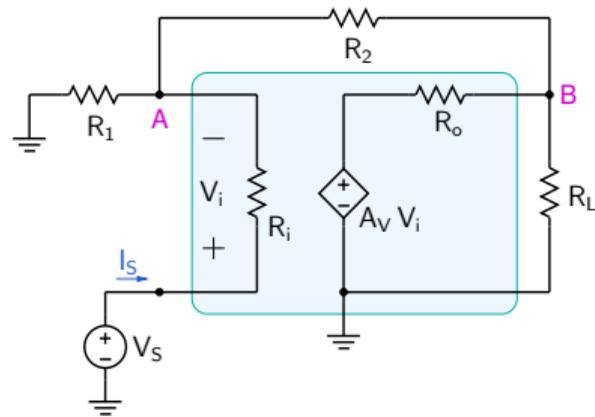
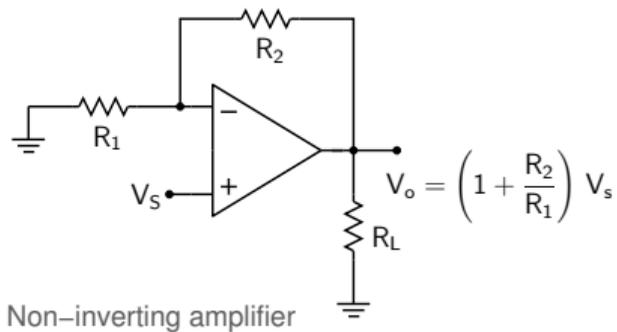


## Op-amp buffer: input resistance

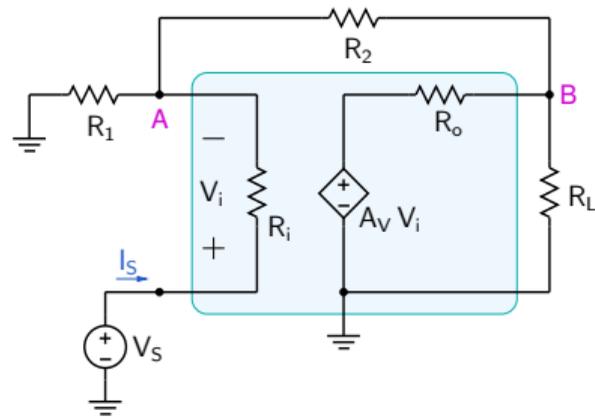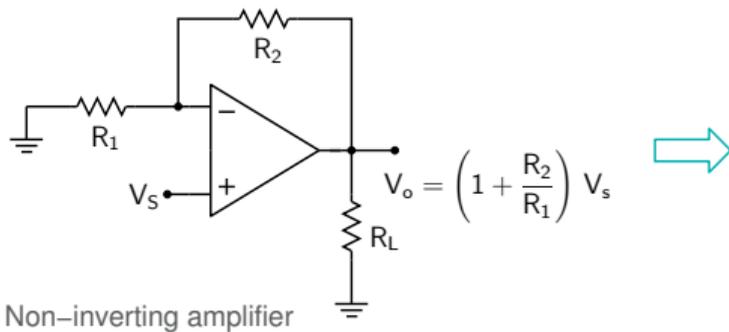

KCL at B:  $\frac{V_B}{R_L} + \frac{V_B - A_V V_i}{R_o} + \frac{V_B - V_A}{R_2} = 0.$



## Op-amp buffer: input resistance

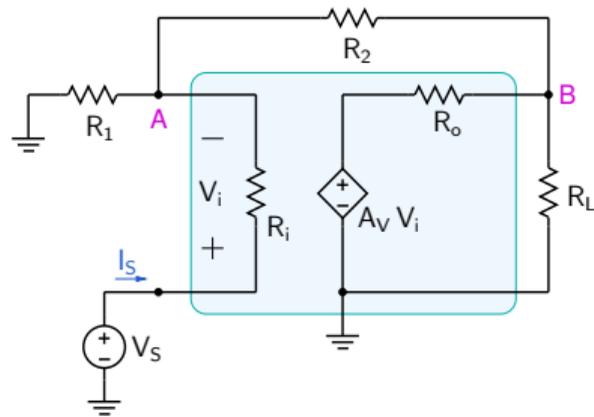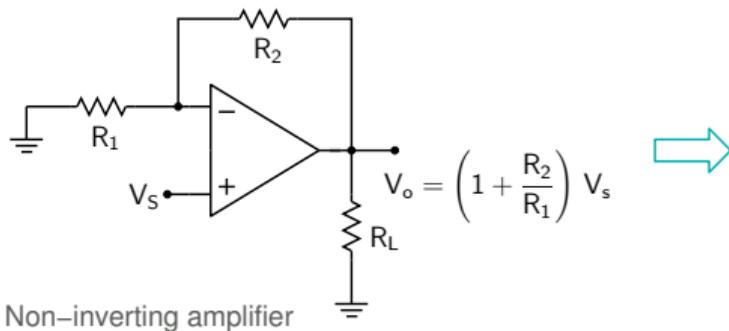

KCL at B: 
$$\frac{V_B}{R_L} + \frac{V_B - A_V V_i}{R_o} + \frac{V_B - V_A}{R_2} = 0.$$

Source current: 
$$I_s = \frac{V_A}{R_1} + \frac{V_A - V_B}{R_2}.$$

# Op-amp buffer: input resistance

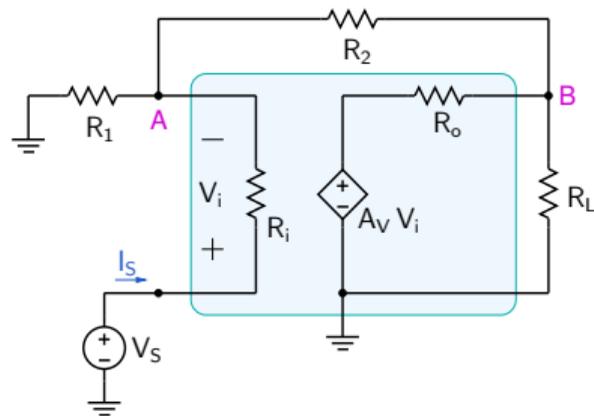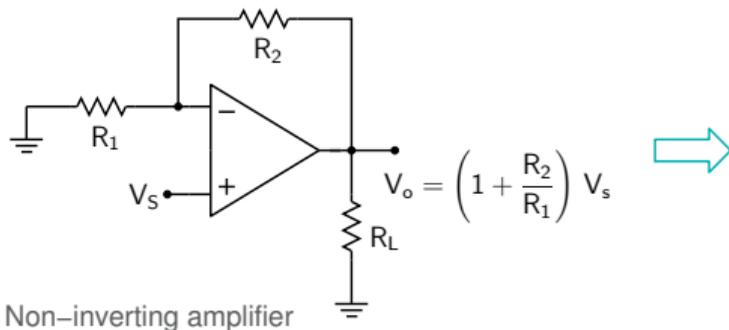



KCL at B: 
$$\frac{V_B}{R_L} + \frac{V_B - A_V V_i}{R_o} + \frac{V_B - V_A}{R_2} = 0.$$

Source current: 
$$I_s = \frac{V_A}{R_1} + \frac{V_A - V_B}{R_2}.$$

Using  $V_i = I_s R_i$ ,  $V_A = V_s - V_i$ , and after some algebra, we get

$$R_{in} = \frac{V_s}{I_s} = \frac{\left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) + R_i \left[\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2} + \frac{A_V}{R_2}\right]}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2}}$$

# Op-amp buffer: input resistance

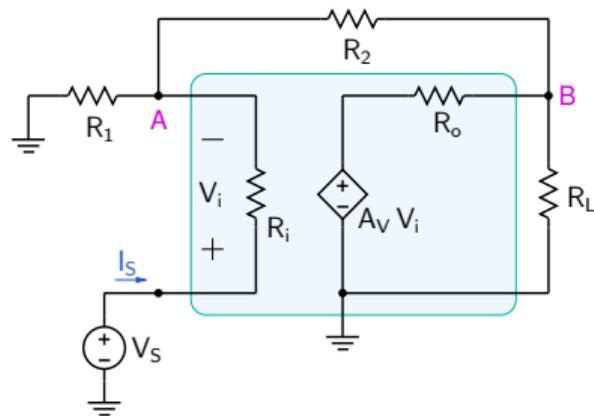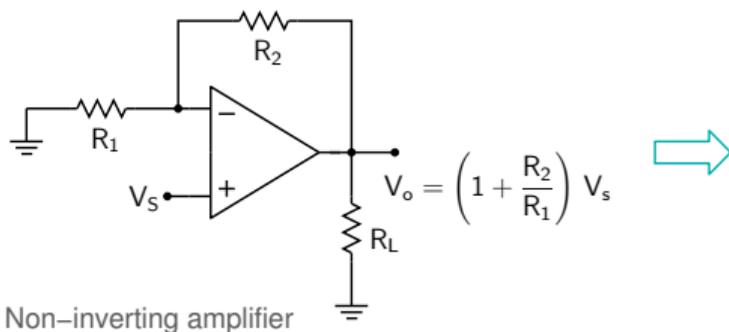

KCL at B:  $\frac{V_B}{R_L} + \frac{V_B - A_V V_i}{R_o} + \frac{V_B - V_A}{R_2} = 0.$



Source current:  $I_S = \frac{V_A}{R_1} + \frac{V_A - V_B}{R_2}.$

Using  $V_i = I_S R_i$ ,  $V_A = V_S - V_i$ , and after some algebra, we get

$$R_{in} = \frac{V_S}{I_S} = \frac{\left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) + R_i \left[\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2} + \frac{A_V}{R_2}\right]}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2}}$$




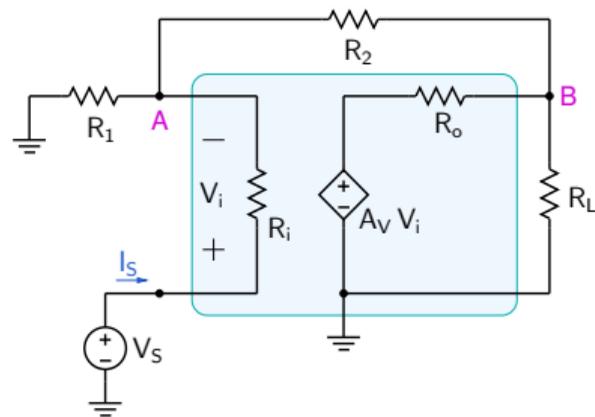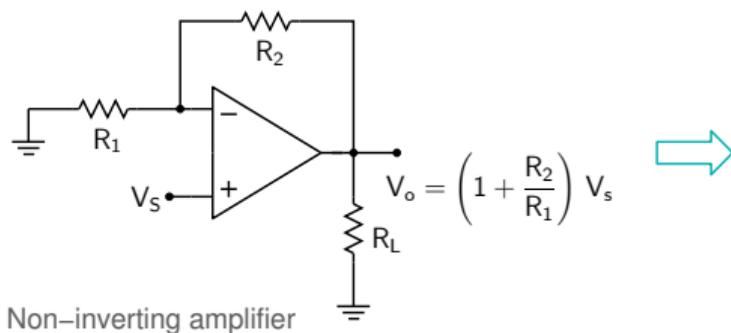
# Non-inverting amplifier: input resistance (continued)



$$R_{in} = \frac{V_s}{I_s} = \frac{\left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) + R_i \left[ \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2} + \frac{A_V}{R_2} \right]}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2}}$$
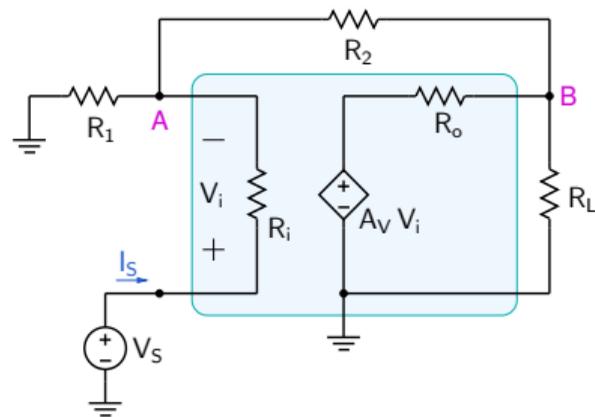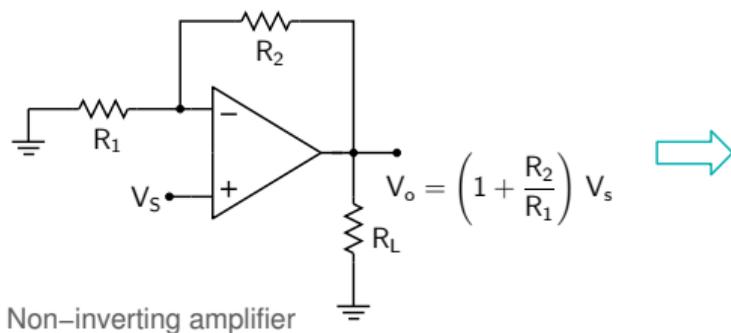
# Non-inverting amplifier: input resistance (continued)




$$R_{in} = \frac{V_S}{I_S} = \frac{\left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) + R_i \left[ \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2} + \frac{A_V}{R_2} \right]}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}\right) - \frac{R_o}{R_2^2}}$$


Since  $R_o$  is much smaller than  $R_1$ ,  $R_2$ ,  $R_L$ , or  $R_i$ ,

$$R_{in} \approx \frac{1 + R_i \left[ \left(\frac{1}{R_1} + \frac{1}{R_2}\right) + \frac{A_V}{R_2} \right]}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)} \approx \frac{R_i \left[ \frac{R_1 + R_2}{R_1 R_2} + \frac{A_V}{R_2} \right]}{\frac{R_1 + R_2}{R_1 R_2}} \approx A_V R_i \frac{R_1}{R_1 + R_2}$$

## Op-amp buffer: input resistance

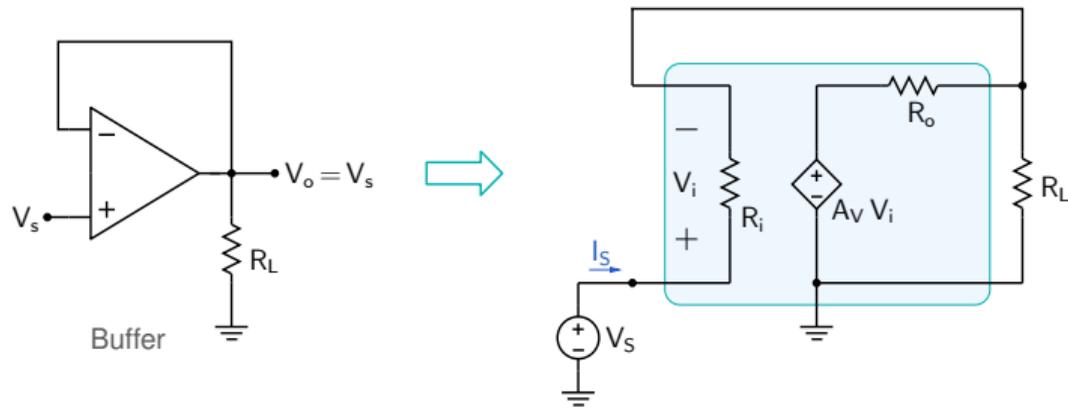


## Op-amp buffer: input resistance

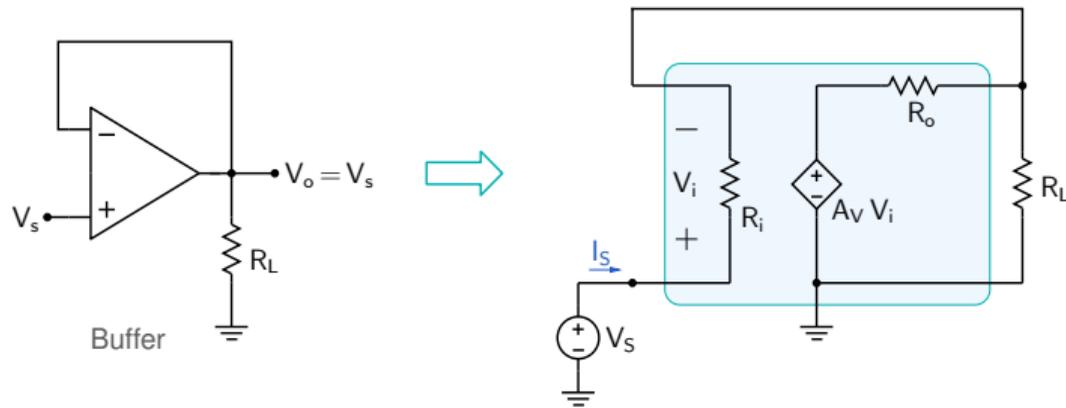

Let  $R_o \rightarrow 0$ .


## Op-amp buffer: input resistance

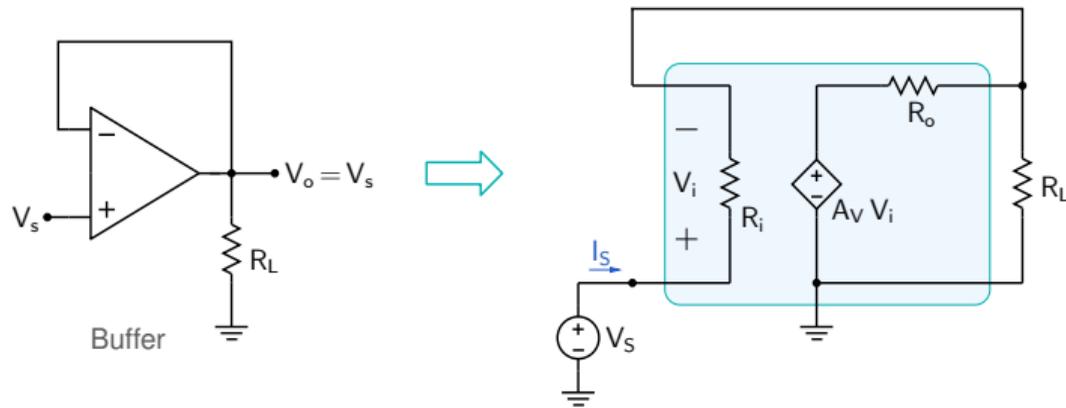

Let  $R_o \rightarrow 0$ .

$$V_S = V_i + A_V V_i = V_i(1 + A_V).$$

## Op-amp buffer: input resistance

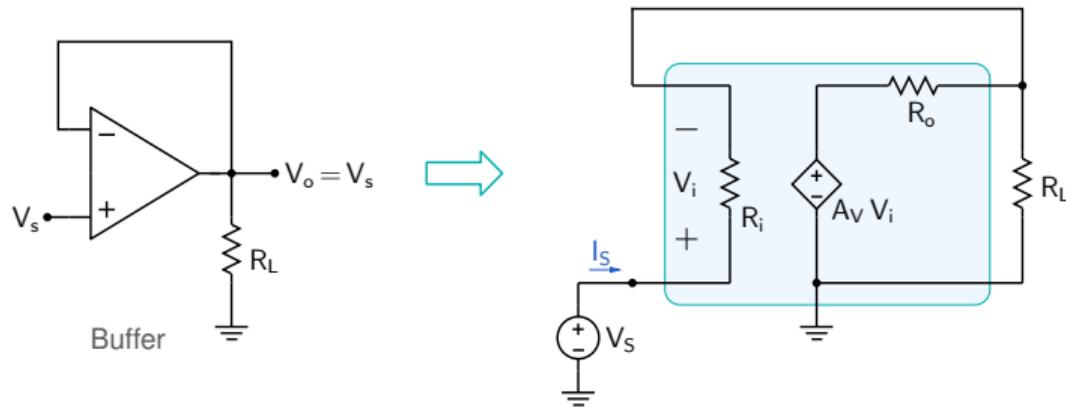


Let  $R_o \rightarrow 0$ .

$$V_S = V_i + A_V V_i = V_i(1 + A_V).$$

$$I_S = \frac{V_i}{R_i}.$$

## Op-amp buffer: input resistance

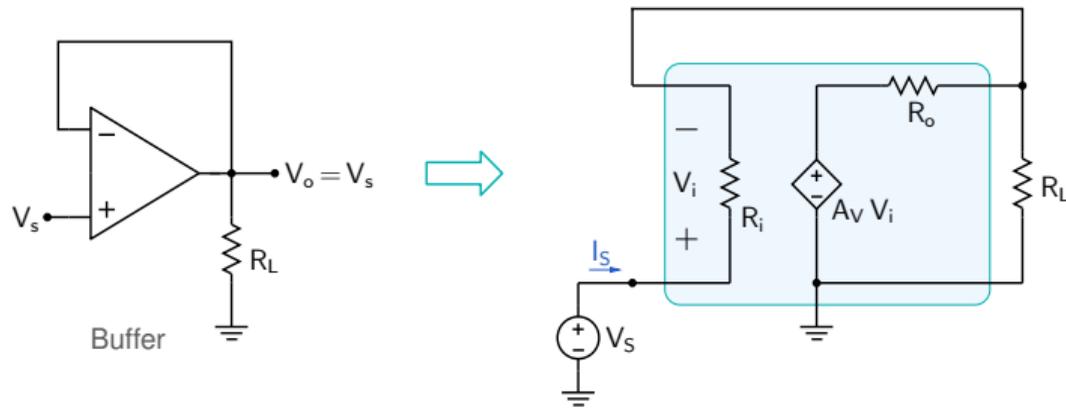



Let  $R_o \rightarrow 0$ .

$$V_S = V_i + A_V V_i = V_i(1 + A_V).$$

$$I_S = \frac{V_i}{R_i}.$$

$$\rightarrow R_{in} = \frac{V_S}{I_S} = R_i(A_V + 1)$$



## Op-amp buffer: output resistance

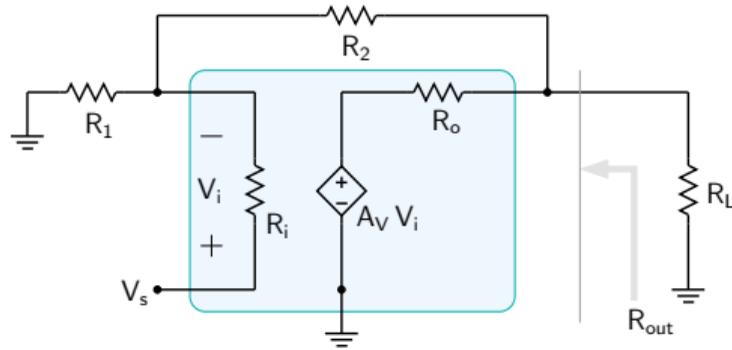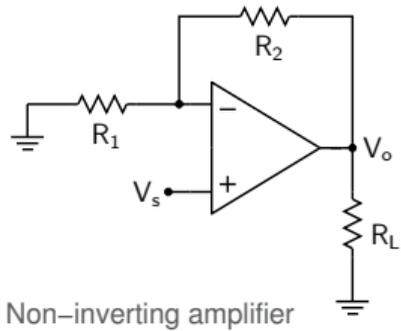

To find  $R_{out}$ ,

- \* Deactivate the input source.



## Op-amp buffer: output resistance

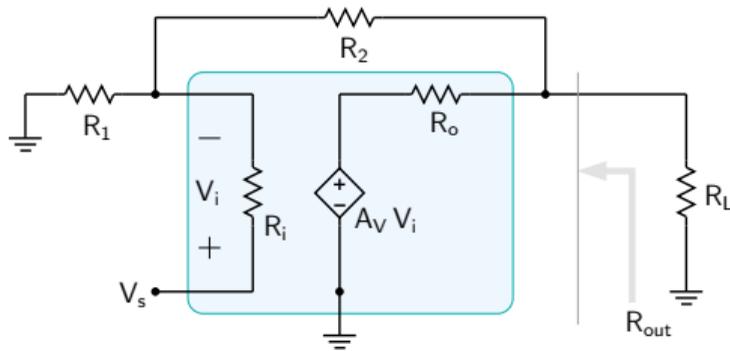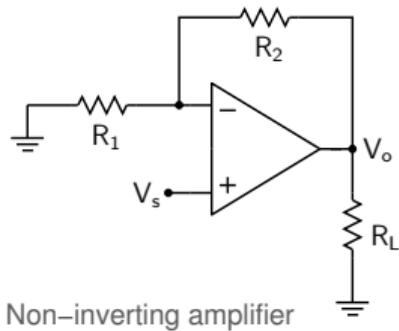

To find  $R_{out}$ ,

- \* Deactivate the input source.
- \* Replace  $R_L$  with a test source  $V'$ .



## Op-amp buffer: output resistance

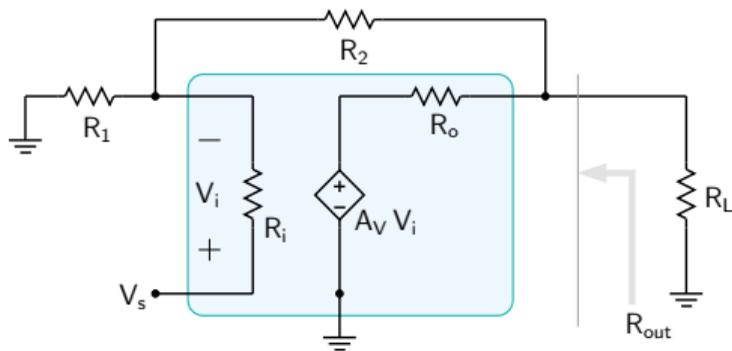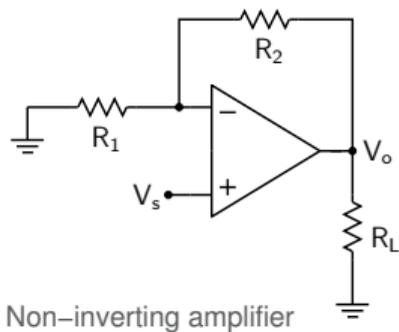

To find  $R_{out}$ ,

- \* Deactivate the input source.
- \* Replace  $R_L$  with a test source  $V'$ .
- \* Find the current ( $I'$ ) through  $V'$ .

# Op-amp buffer: output resistance

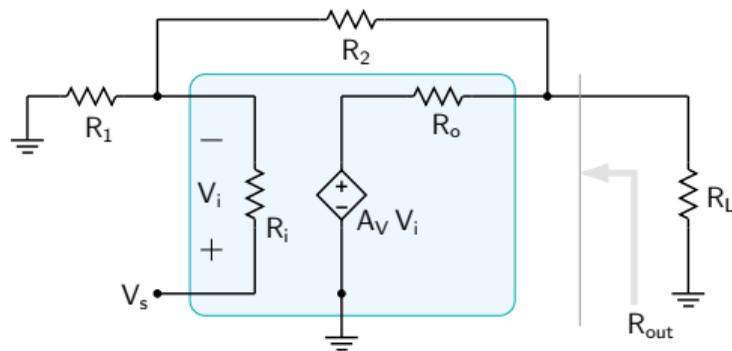
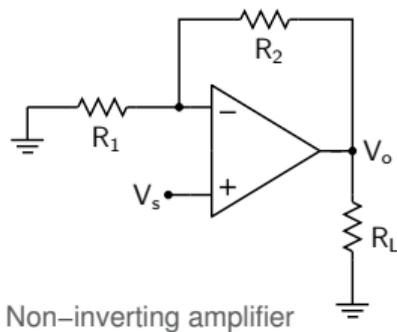


To find  $R_{out}$ ,



- \* Deactivate the input source.
- \* Replace  $R_L$  with a test source  $V'$ .
- \* Find the current ( $I'$ ) through  $V'$ .

- \*  $R_{out} = \frac{V'}{I'}$ .
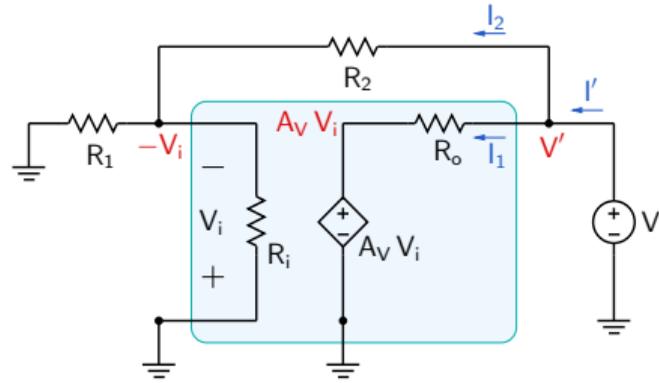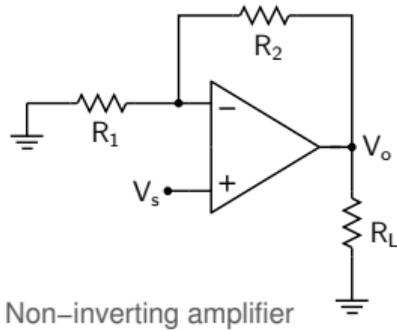
# Op-amp buffer: output resistance (continued)




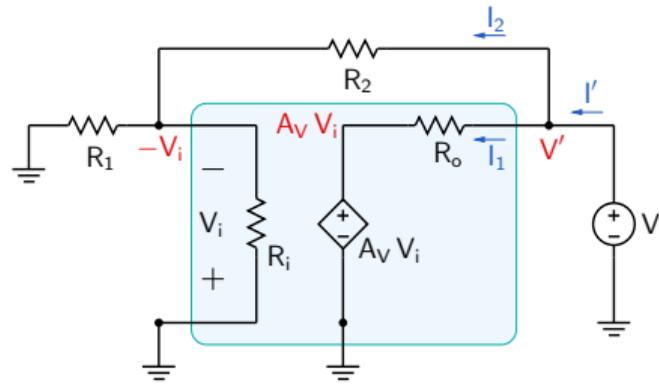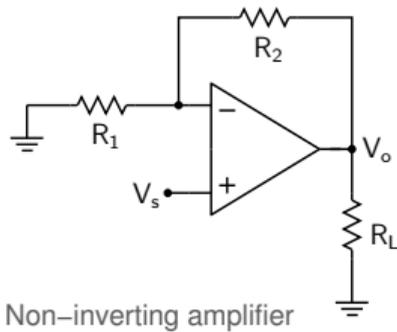
# Op-amp buffer: output resistance (continued)



$$V_i = -\frac{(R_i \parallel R_1)}{R_2 + (R_i \parallel R_1)} V' \equiv -kV'$$

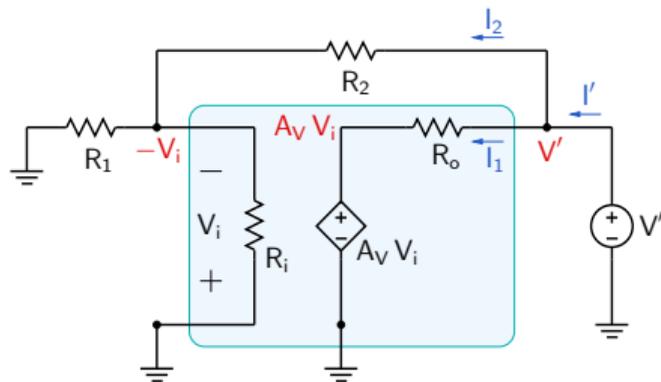
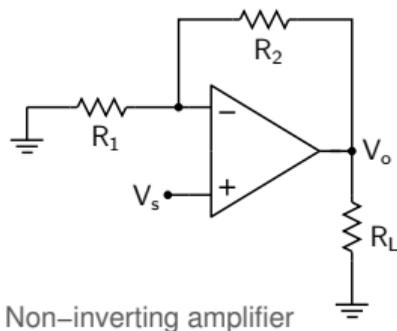
# Op-amp buffer: output resistance (continued)



$$V_i = -\frac{(R_i \parallel R_1)}{R_2 + (R_i \parallel R_1)} V' \equiv -kV'$$

$$I' = I_1 + I_2 = \frac{V' - A_V V_i}{R_o} + \frac{V' - (-V_i)}{R_2} = \frac{1}{R_o} (V' + kA_V V') + \frac{1}{R_2} (V' - kV')$$
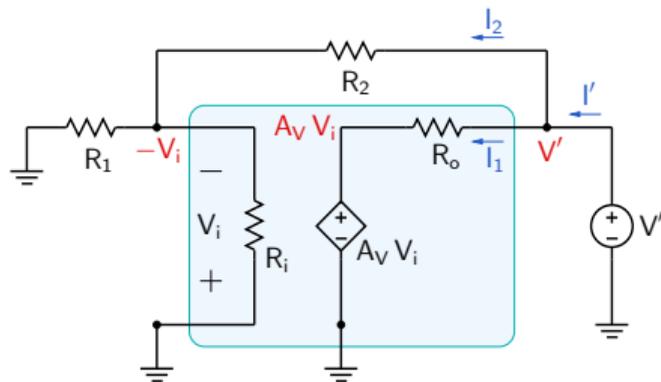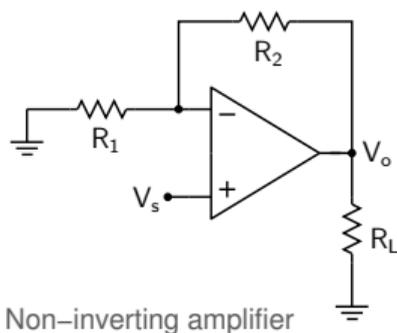
# Op-amp buffer: output resistance (continued)





$$V_i = -\frac{(R_i \parallel R_1)}{R_2 + (R_i \parallel R_1)} V' \equiv -kV'$$

$$I' = I_1 + I_2 = \frac{V' - A_V V_i}{R_o} + \frac{V' - (-V_i)}{R_2} = \frac{1}{R_o} (V' + kA_V V') + \frac{1}{R_2} (V' - kV')$$

$$\frac{I'}{V'} = \frac{1}{R_o} (1 + kA_V) + \frac{1}{R_2} (1 - k) \rightarrow R_{out} = \frac{V'}{I'} = \frac{R_o}{(1 + kA_V)} \parallel \frac{R_2}{(1 - k)} \approx \frac{R_o}{(1 + kA_V)}$$
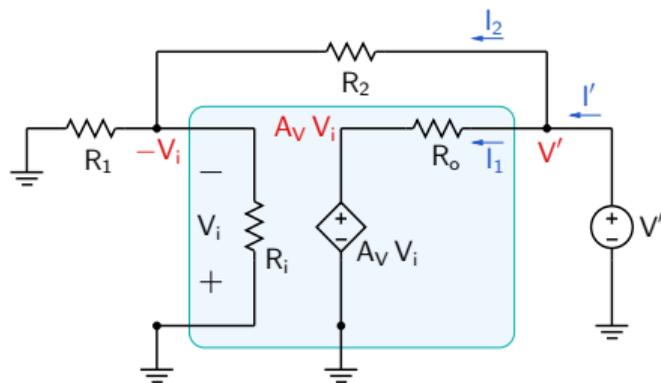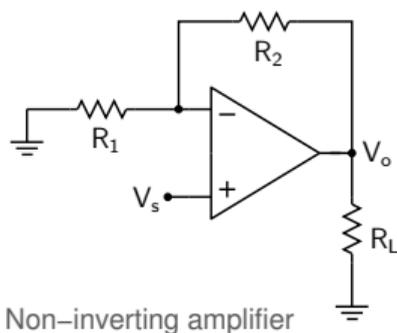
## Op-amp buffer: output resistance (continued)



$$V_i = -\frac{(R_i \parallel R_1)}{R_2 + (R_i \parallel R_1)} V' \equiv -kV'$$


$$I' = I_1 + I_2 = \frac{V' - A_V V_i}{R_o} + \frac{V' - (-V_i)}{R_2} = \frac{1}{R_o} (V' + kA_V V') + \frac{1}{R_2} (V' - kV')$$

$$\frac{I'}{V'} = \frac{1}{R_o} (1 + kA_V) + \frac{1}{R_2} (1 - k) \rightarrow R_{out} = \frac{V'}{I'} = \frac{R_o}{(1 + kA_V)} \parallel \frac{R_2}{(1 - k)} \approx \frac{R_o}{(1 + kA_V)}$$

Special case: Op-amp buffer


$$k = \frac{(R_i \parallel R_1)}{R_2 + (R_i \parallel R_1)} \rightarrow 1 \Rightarrow \boxed{R_{out} \approx \frac{R_o}{1 + A_V}}$$

## Op-amp buffer

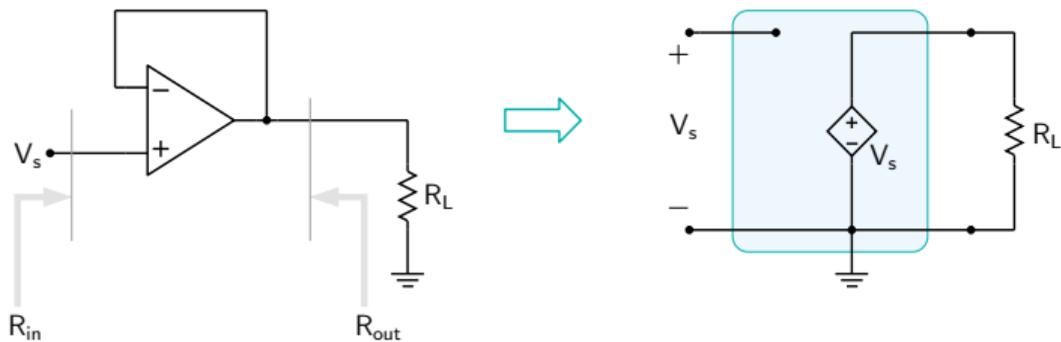


In summary, the buffer (voltage follower) provides

## Op-amp buffer

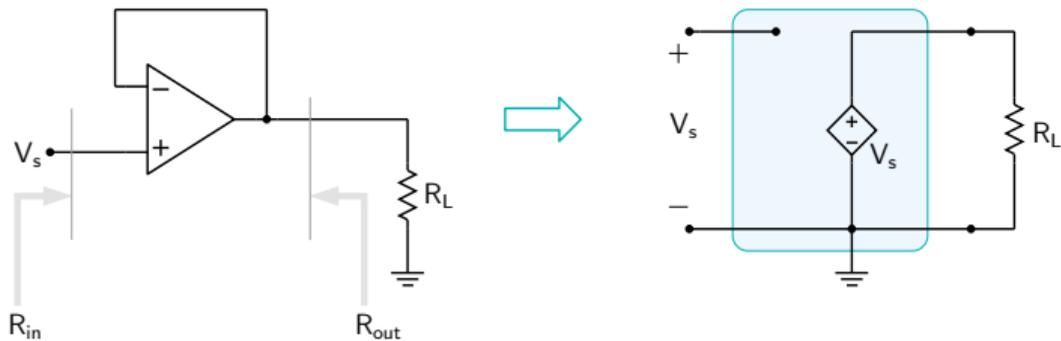


In summary, the buffer (voltage follower) provides

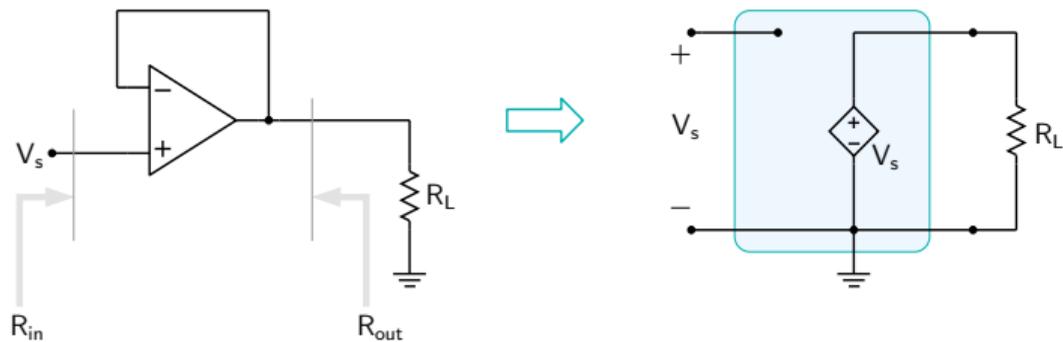- \* a large input resistance  $R_{in}$  as seen from the source.



In summary, the buffer (voltage follower) provides

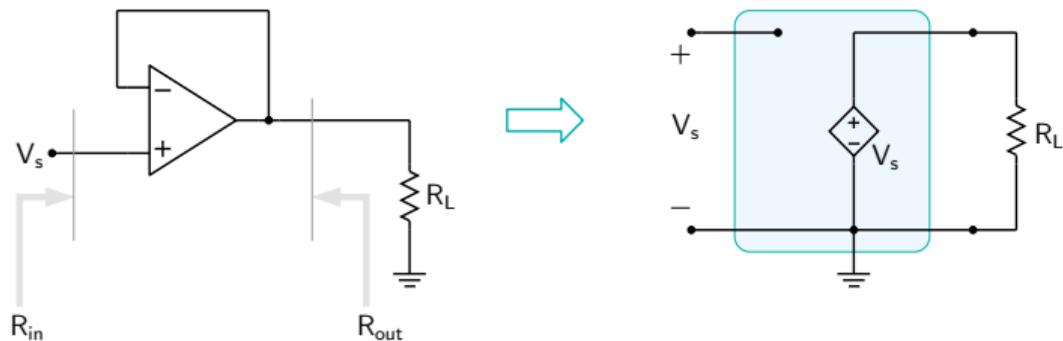
- \* a large input resistance  $R_{in}$  as seen from the source.
- \* a small output resistance  $R_{out}$  as seen from the load.



In summary, the buffer (voltage follower) provides


- \* a large input resistance  $R_{in}$  as seen from the source.
- \* a small output resistance  $R_{out}$  as seen from the load.
- \* a gain of 1, i.e., the output voltage simply follows the input voltage.

## Loading effects (revisited)

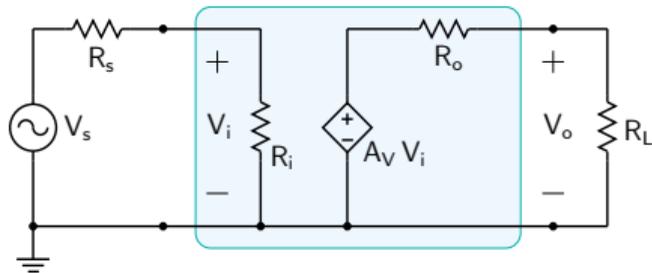

Problem: We would like to have  $V_o = A_V V_s$ .

## Loading effects (revisited)

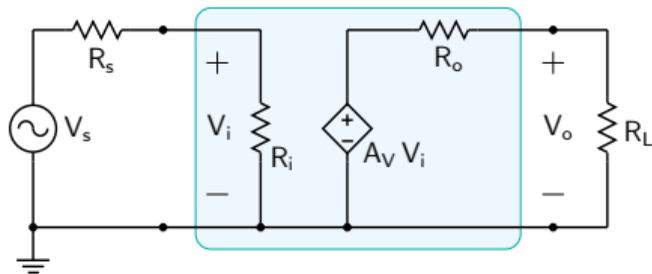


Problem: We would like to have  $V_o = A_V V_s$ .


But the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} A_V V_i = A_V \frac{R_L}{R_o + R_L} \frac{R_i}{R_i + R_s} V_s.$$


# Op-amp buffer

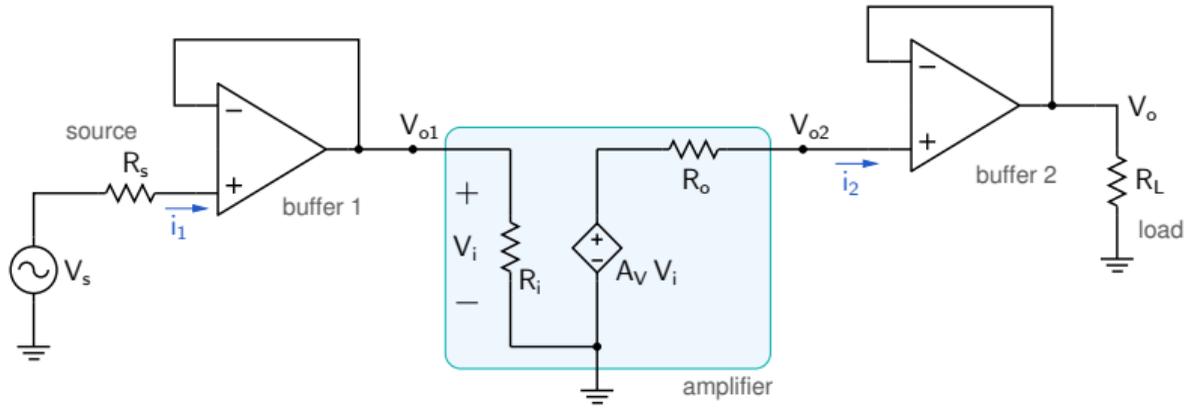


## Op-amp buffer

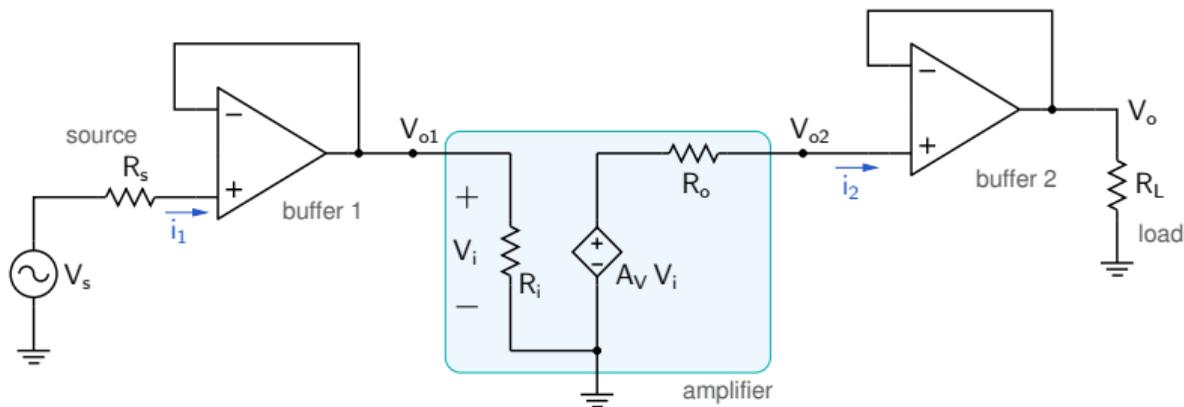

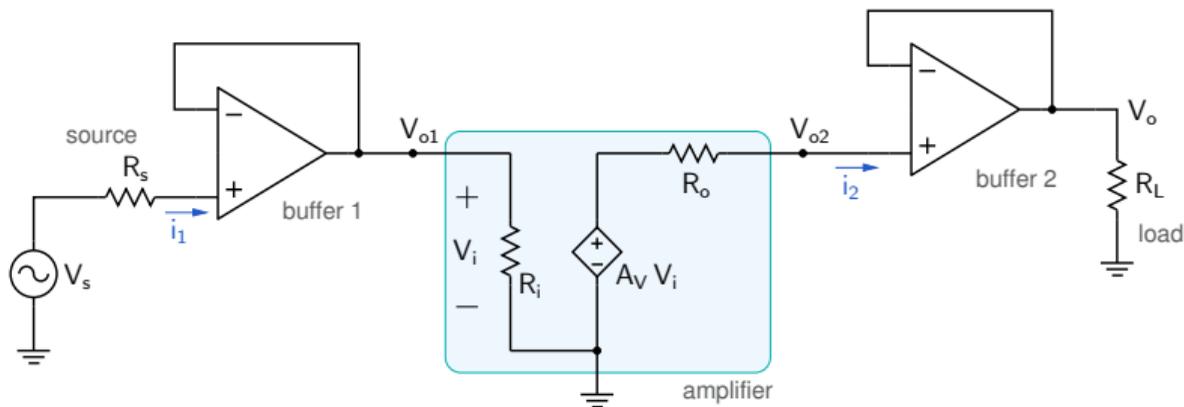Since the buffer has a large input resistance,  $i_1 \approx 0$  A,  
and  $V_+$  (on the source side) =  $V_s \rightarrow V_{o1} = V_s$ .



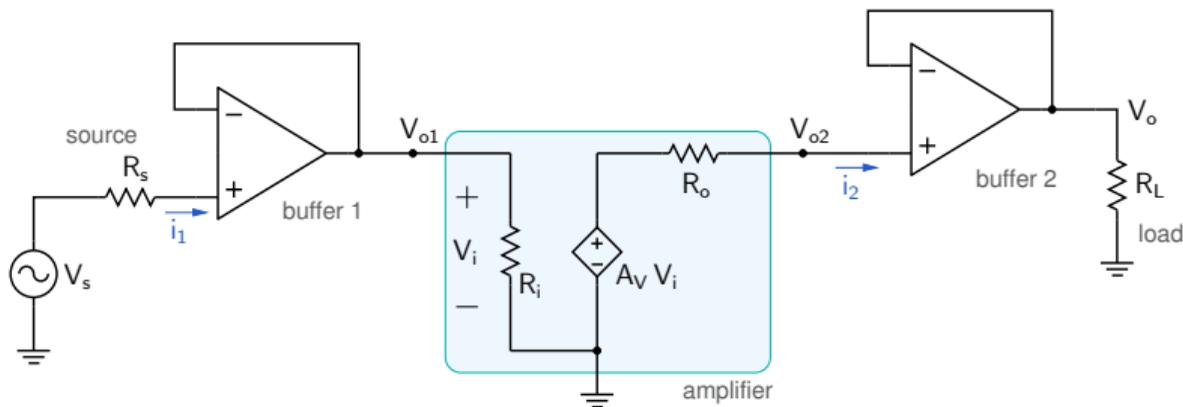Since the buffer has a large input resistance,  $i_1 \approx 0 \text{ A}$ ,  
 and  $V_+$  (on the source side) =  $V_s \rightarrow V_{o1} = V_s$ .  
 Similarly,  $i_2 \approx 0 \text{ A}$ , and  $V_{o2} = A_V V_i = A_V V_s$ .




Since the buffer has a large input resistance,  $i_1 \approx 0 \text{ A}$ ,

and  $V_+$  (on the source side) =  $V_s \rightarrow V_{o1} = V_s$ .

Similarly,  $i_2 \approx 0 \text{ A}$ , and  $V_{o2} = A_V V_i = A_V V_s$ .

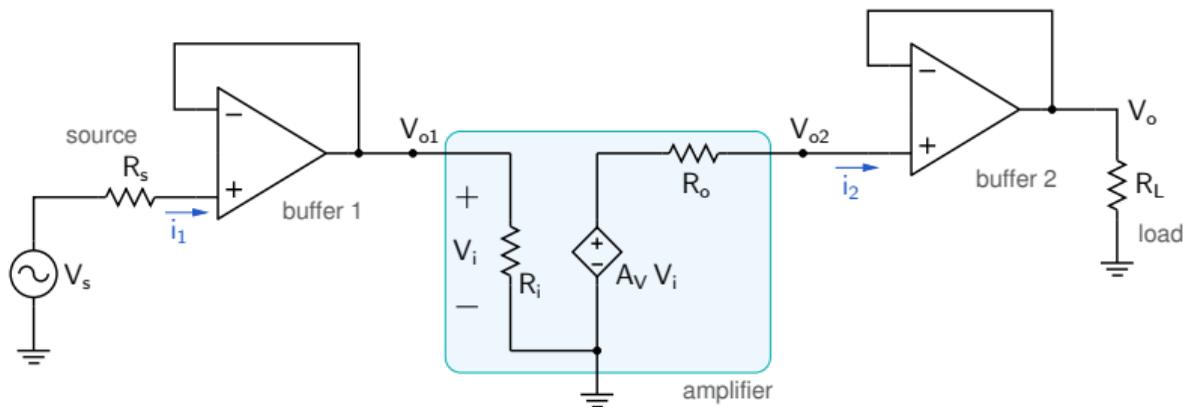Finally,  $V_o = V_{o2} = A_V V_s$ , as desired, *irrespective of  $R_S$  and  $R_L$ .*



Since the buffer has a large input resistance,  $i_1 \approx 0 \text{ A}$ ,


and  $V_+$  (on the source side) =  $V_s \rightarrow V_{o1} = V_s$ .

Similarly,  $i_2 \approx 0 \text{ A}$ , and  $V_{o2} = A_V V_i = A_V V_s$ .


Finally,  $V_o = V_{o2} = A_V V_s$ , as desired, *irrespective of  $R_S$  and  $R_L$ .*

Note that the load current is supplied by the second buffer which acts as a voltage source ( $= A_V V_s$ ) with zero source resistance.

## Op-amp circuits (linear region)

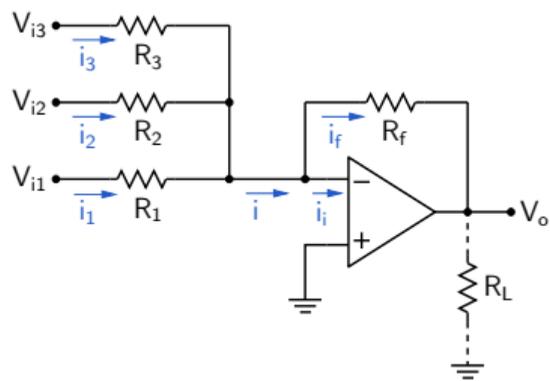


## Op-amp circuits (linear region)

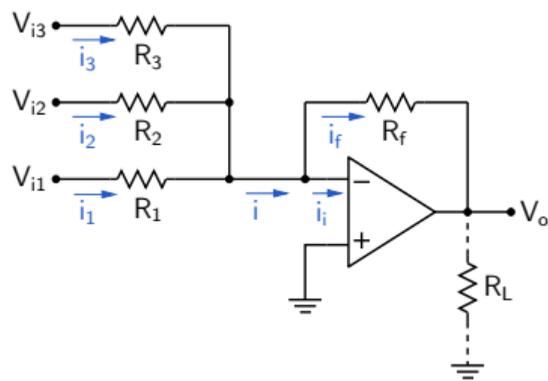

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$


## Op-amp circuits (linear region)

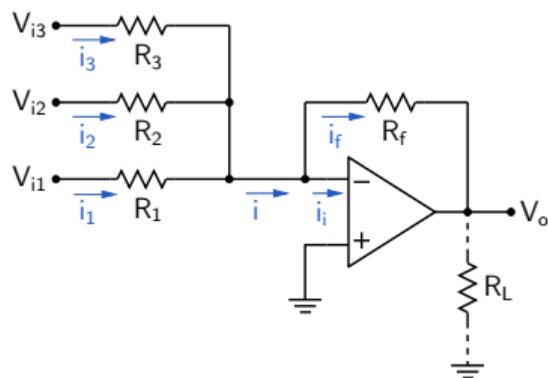

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

## Op-amp circuits (linear region)

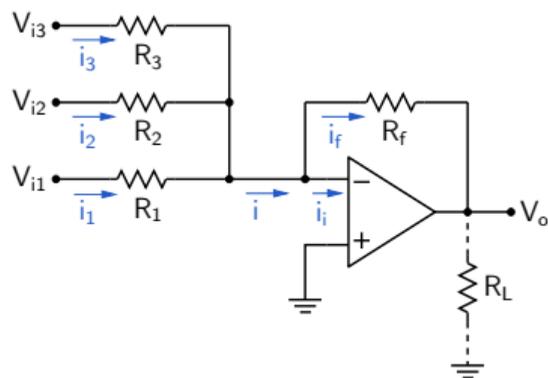


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the op-amp,  $i_i \approx 0 \rightarrow i_f = i$ , which gives

## Op-amp circuits (linear region)

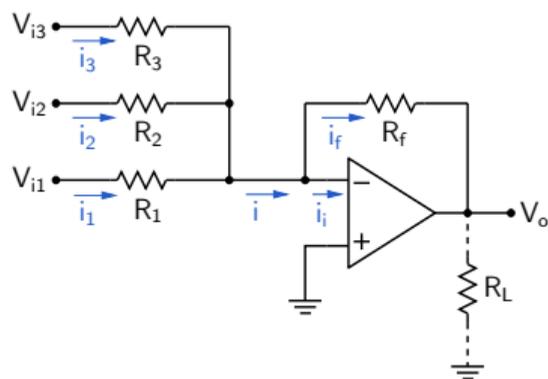

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$


$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the op-amp,  $i_i \approx 0 \rightarrow i_f = i$ , which gives

$$V_o = V_- - i_f R_f = 0 - \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right) R_f = - \left( \frac{R_f}{R_1} V_{i1} + \frac{R_f}{R_2} V_{i2} + \frac{R_f}{R_3} V_{i3} \right),$$

i.e.,  $V_o$  is a *weighted sum* of  $V_{i1}$ ,  $V_{i2}$ ,  $V_{i3}$ .

## Op-amp circuits (linear region)

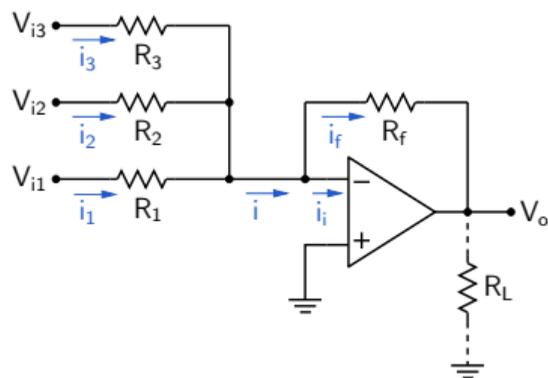

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the op-amp,  $i_i \approx 0 \rightarrow i_f = i$ , which gives


$$V_o = V_- - i_f R_f = 0 - \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right) R_f = - \left( \frac{R_f}{R_1} V_{i1} + \frac{R_f}{R_2} V_{i2} + \frac{R_f}{R_3} V_{i3} \right),$$

i.e.,  $V_o$  is a *weighted sum* of  $V_{i1}$ ,  $V_{i2}$ ,  $V_{i3}$ .

If  $R_1 = R_2 = R_3 = R$ , the circuit acts as a summer, giving

$$V_o = -K (V_{i1} + V_{i2} + V_{i3}) \quad \text{with } K = R_f/R.$$

# Summer example

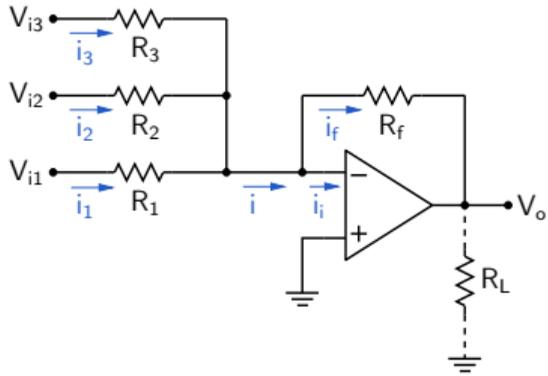


$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$


$$R_f = 2 \text{ k}\Omega$$

$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$

SEQUEL file: ee101\_summer.sqproj

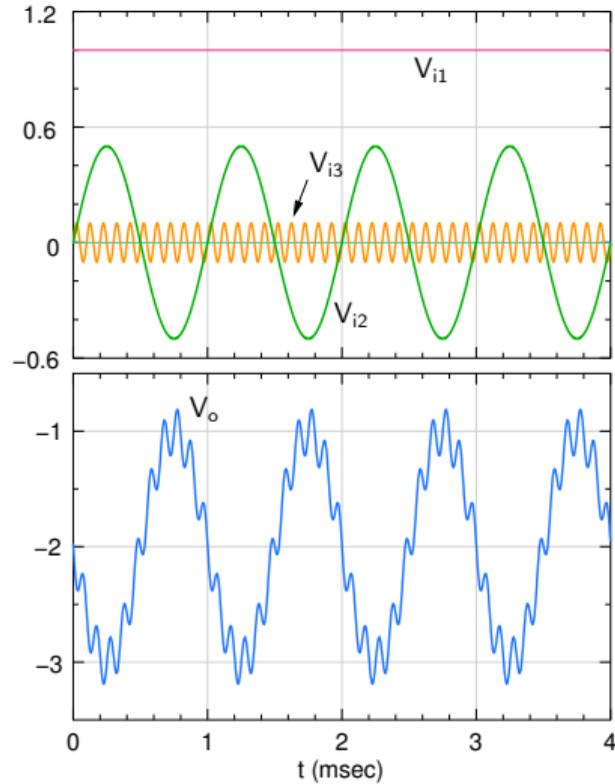

# Summer example

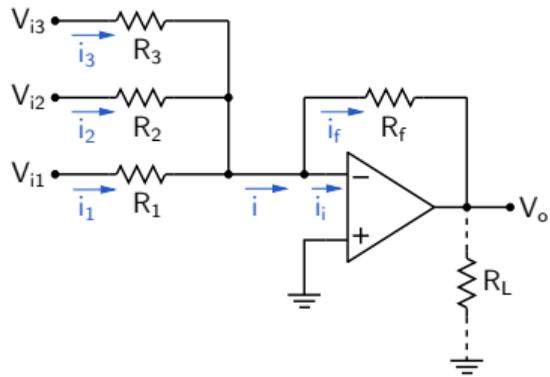


$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

$$R_f = 2 \text{ k}\Omega$$


$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$

SEQUEL file: ee101\_summer.sqproj

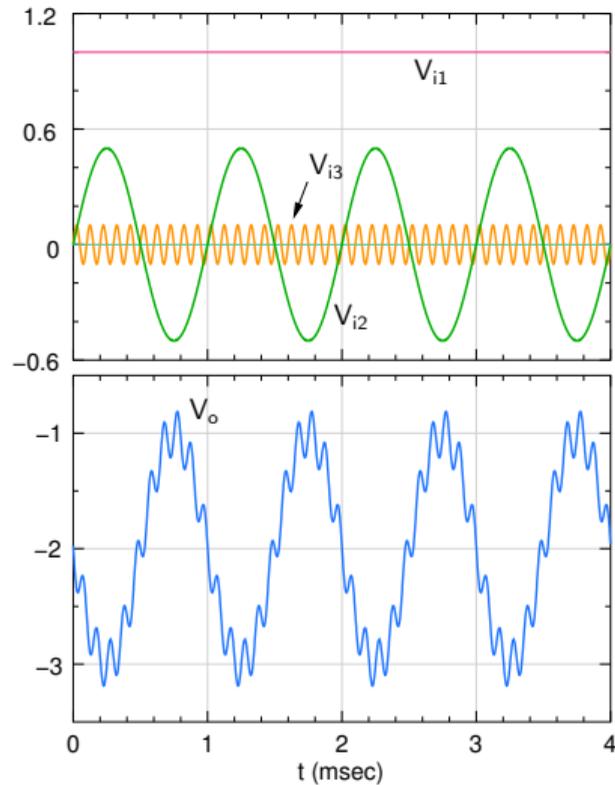

\* Note that the summer also works with DC inputs (so do inverting and non-inverting amplifiers).

## Summer example

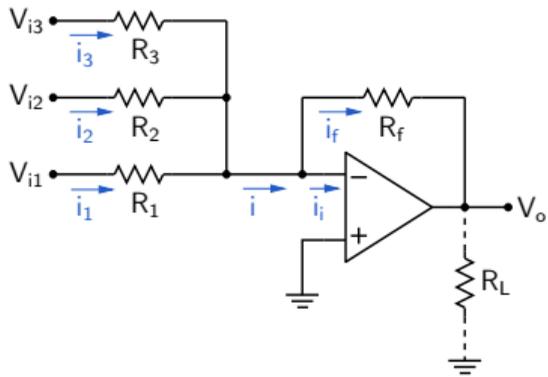


$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

$$R_f = 2 \text{ k}\Omega$$

$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$

SEQUEL file: ee101\_summer.sqproj

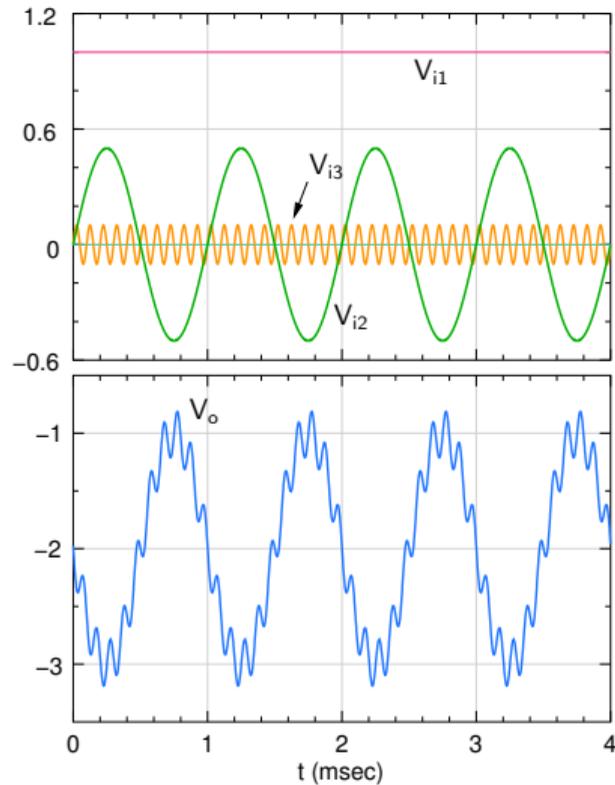

- \* Note that the summer also works with DC inputs (so do inverting and non-inverting amplifiers).
- \* Op-amps make life simpler! Think of adding voltages in any other way.

- \* If resistances are too small, they draw larger currents  $\rightarrow$  increased power dissipation

- \* If resistances are too small, they draw larger currents  $\rightarrow$  increased power dissipation
- \* If resistances are too large,

- \* If resistances are too small, they draw larger currents → increased power dissipation
- \* If resistances are too large,
  - The effect of offset voltage and input bias currents becomes more pronounced (to be discussed).


- \* If resistances are too small, they draw larger currents → increased power dissipation
- \* If resistances are too large,
  - The effect of offset voltage and input bias currents becomes more pronounced (to be discussed).
  - Combined with parasitic (wiring) capacitances, large resistances can affect the frequency response and stability of the circuit.

- \* If resistances are too small, they draw larger currents → increased power dissipation
- \* If resistances are too large,
  - The effect of offset voltage and input bias currents becomes more pronounced (to be discussed).
  - Combined with parasitic (wiring) capacitances, large resistances can affect the frequency response and stability of the circuit.
  - Thermal noise increases as  $R$  increases, and it may not be desirable in some applications.


- \* If resistances are too small, they draw larger currents → increased power dissipation
- \* If resistances are too large,
  - The effect of offset voltage and input bias currents becomes more pronounced (to be discussed).
  - Combined with parasitic (wiring) capacitances, large resistances can affect the frequency response and stability of the circuit.
  - Thermal noise increases as  $R$  increases, and it may not be desirable in some applications.
- \* Typical resistance values: 0.1 k to 100 k.

Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .

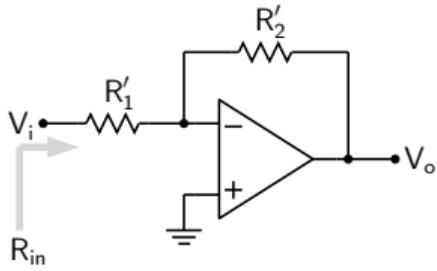Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .




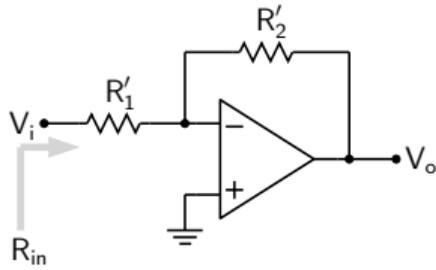Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .



$$R_{in} = R'_1 = 10\text{ k.}$$

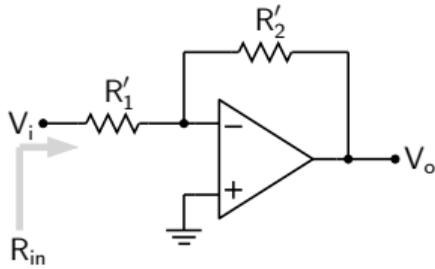
Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .



$$R_{in} = R'_1 = 10\text{ k}.$$

$$A_V = -\frac{R'_2}{R'_1} = -100 \rightarrow R'_2 = 100 \times 10\text{ k} = 1\text{ M}\Omega$$

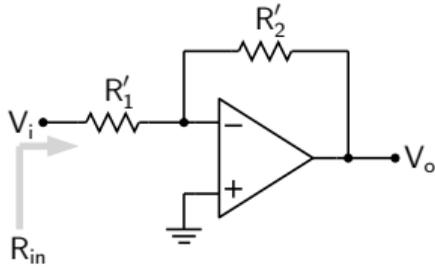Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .




$$R_{in} = R'_1 = 10\text{ k}.$$

$$A_V = -\frac{R'_2}{R'_1} = -100 \rightarrow R'_2 = 100 \times 10\text{ k} = 1\text{ M}\Omega$$

$R'_2$  may be unacceptable from practical considerations.

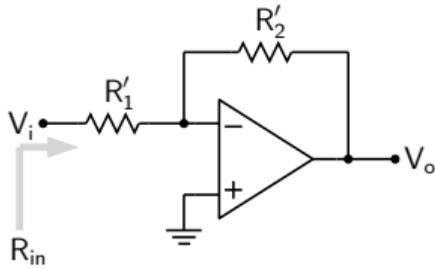Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .




$$R_{in} = R'_1 = 10\text{ k}.$$

$$A_V = -\frac{R'_2}{R'_1} = -100 \rightarrow R'_2 = 100 \times 10\text{ k} = 1\text{ M}\Omega$$

$R'_2$  may be unacceptable from practical considerations.

→ need a design with smaller resistances.

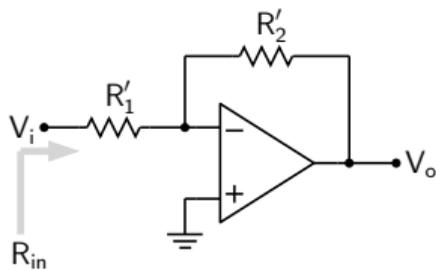Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .




$$R_{in} = R'_1 = 10\text{ k}.$$


$$A_V = -\frac{R'_2}{R'_1} = -100 \rightarrow R'_2 = 100 \times 10\text{ k} = 1\text{ M}\Omega$$

$R'_2$  may be unacceptable from practical considerations.

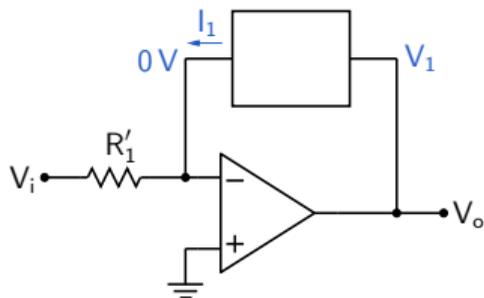→ need a design with smaller resistances.



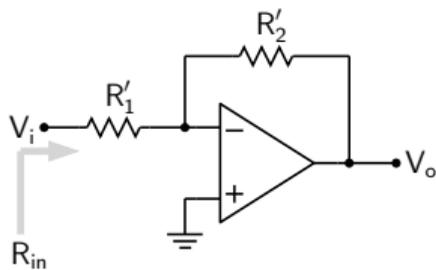Design an amplifier with  $R_{in} = 10\text{ k}$  and  $A_V = -100$ .




$$R_{in} = R'_1 = 10\text{ k}.$$


$$A_V = -\frac{R'_2}{R'_1} = -100 \rightarrow R'_2 = 100 \times 10\text{ k} = 1\text{ M}\Omega$$


$R'_2$  may be unacceptable from practical considerations.

→ need a design with smaller resistances.

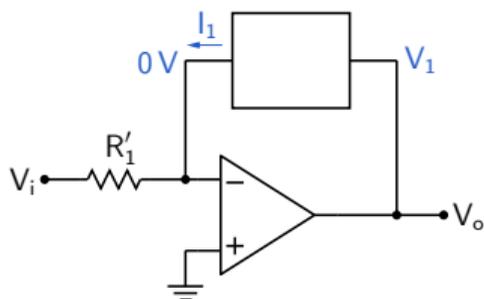
If we ensure  $\frac{V_1}{I_1} = R'_2$ , we will satisfy the gain condition.



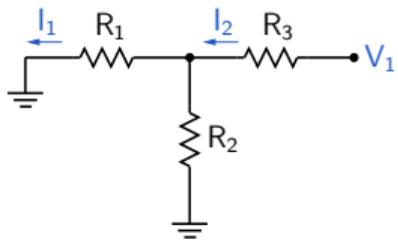

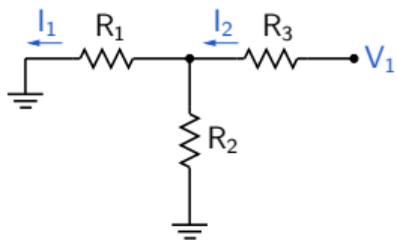

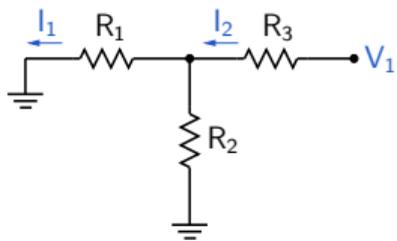
$$I_2 = \frac{V_1}{R_3 + (R_1 \parallel R_2)}$$



$$I_2 = \frac{V_1}{R_3 + (R_1 \parallel R_2)}$$

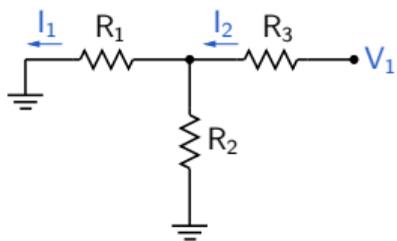
$$I_1 = \frac{R_2}{R_1 + R_2} I_2 = \frac{R_2}{R_1 + R_2} \times \frac{R_1 + R_2}{R_3(R_1 + R_2) + R_1 R_2} V_1$$



$$I_2 = \frac{V_1}{R_3 + (R_1 \parallel R_2)}$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_2 = \frac{R_2}{R_1 + R_2} \times \frac{R_1 + R_2}{R_3(R_1 + R_2) + R_1 R_2} V_1$$
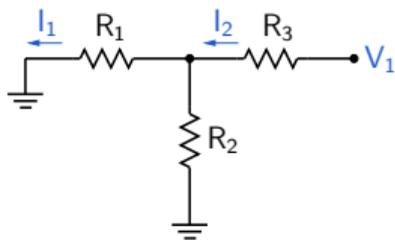
$$R_{\text{eff}} \equiv \frac{V_1}{I_1} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$




$$I_2 = \frac{V_1}{R_3 + (R_1 \parallel R_2)}$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_2 = \frac{R_2}{R_1 + R_2} \times \frac{R_1 + R_2}{R_3(R_1 + R_2) + R_1 R_2} V_1$$

$$R_{\text{eff}} \equiv \frac{V_1}{I_1} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

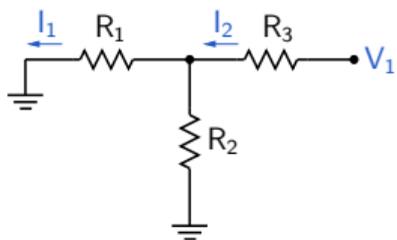→ Choose  $R_1$ ,  $R_2$ ,  $R_3$  such that  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .






$$I_2 = \frac{V_1}{R_3 + (R_1 \parallel R_2)}$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_2 = \frac{R_2}{R_1 + R_2} \times \frac{R_1 + R_2}{R_3(R_1 + R_2) + R_1 R_2} V_1$$

$$R_{\text{eff}} \equiv \frac{V_1}{I_1} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


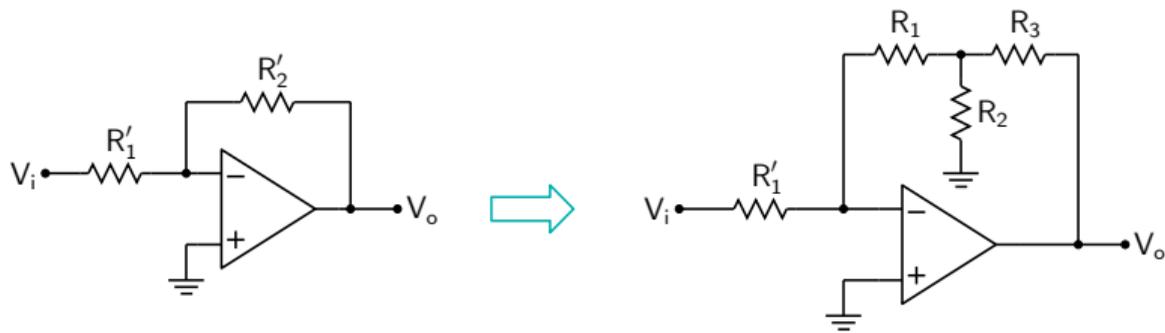
→ Choose  $R_1, R_2, R_3$  such that  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .



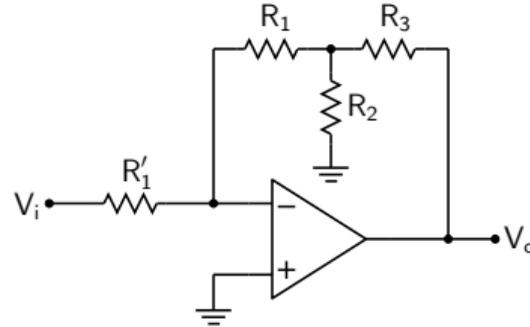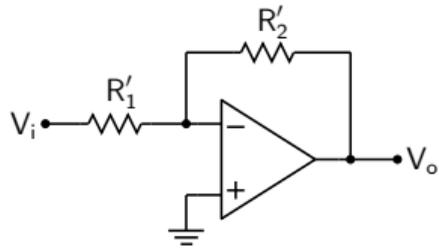

$$R_{\text{eff}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

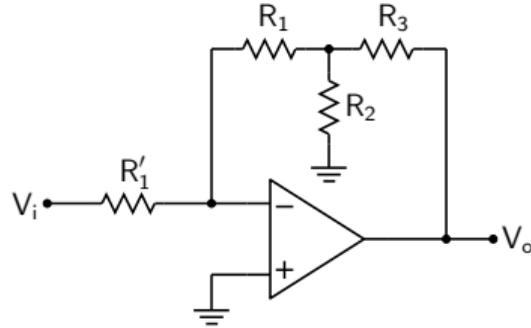
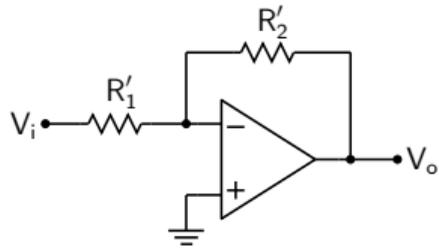
We want  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .



$$R_{\text{eff}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

We want  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .



Let  $R_1 = R_3 \equiv R$

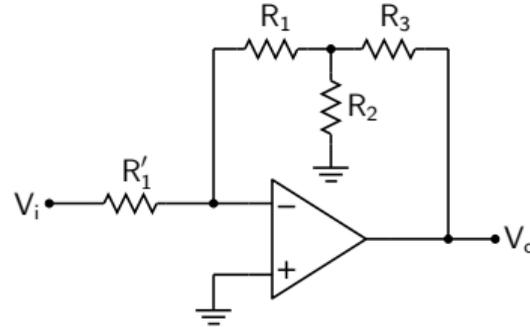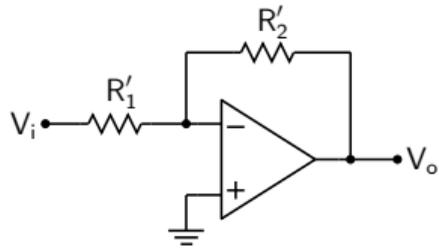

$$R_{\text{eff}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

We want  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .

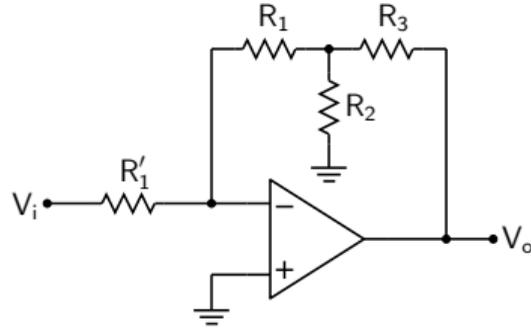
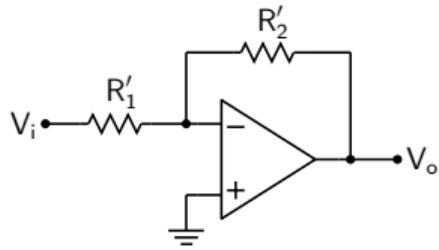
$$\text{Let } R_1 = R_3 \equiv R \rightarrow R_{\text{eff}} = \frac{R^2 + 2 R R_2}{R_2} = R \left( \frac{R}{R_2} + 2 \right)$$



$$R_{\text{eff}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

We want  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .
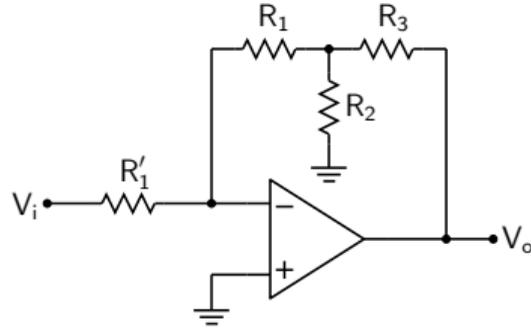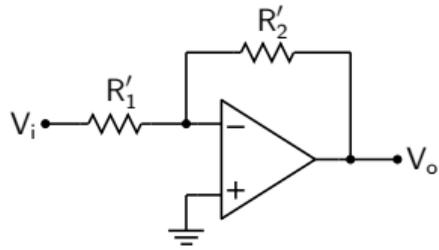
$$\text{Let } R_1 = R_3 \equiv R \rightarrow R_{\text{eff}} = \frac{R^2 + 2 R R_2}{R_2} = R \left( \frac{R}{R_2} + 2 \right) \rightarrow R_2 = \frac{R}{\frac{R_{\text{eff}}}{R} - 2}$$




$$R_{\text{eff}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

We want  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .

$$\text{Let } R_1 = R_3 \equiv R \rightarrow R_{\text{eff}} = \frac{R^2 + 2 R R_2}{R_2} = R \left( \frac{R}{R_2} + 2 \right) \rightarrow R_2 = \frac{R}{\frac{R_{\text{eff}}}{R} - 2}$$
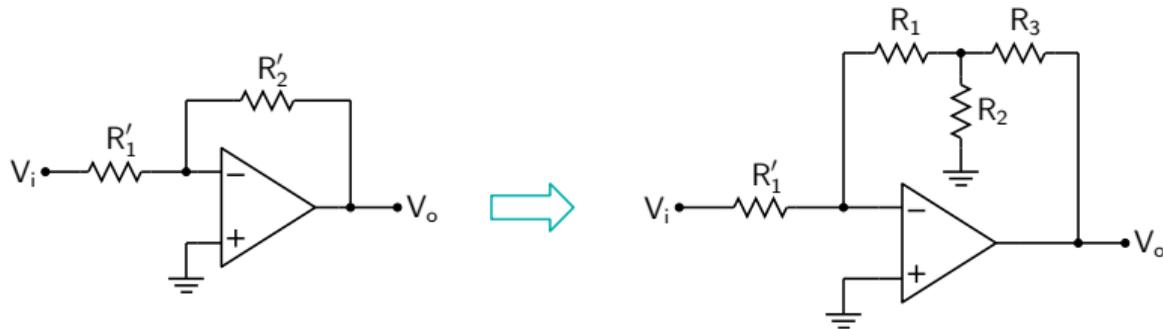
$$\text{For } R = 10 \text{ k}, R_2 = \frac{10 \text{ k}}{100 - 2} \approx 102 \Omega.$$




$$R_{\text{eff}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

We want  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .

$$\text{Let } R_1 = R_3 \equiv R \rightarrow R_{\text{eff}} = \frac{R^2 + 2 R R_2}{R_2} = R \left( \frac{R}{R_2} + 2 \right) \rightarrow R_2 = \frac{R}{\frac{R_{\text{eff}}}{R} - 2}$$

$$\text{For } R = 10 \text{ k}, R_2 = \frac{10 \text{ k}}{100 - 2} \approx 102 \Omega.$$

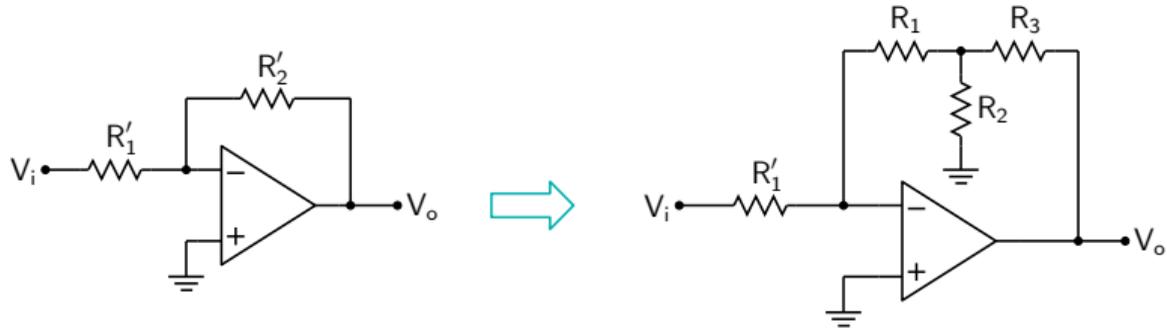Ref: Wait et al, *Introduction to op-amp theory and applications*, McGraw-Hill, 1992.



$$R_{\text{eff}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

We want  $R_{\text{eff}} = R'_2 = 1 \text{ M}\Omega$ .

$$\text{Let } R_1 = R_3 \equiv R \rightarrow R_{\text{eff}} = \frac{R^2 + 2 R R_2}{R_2} = R \left( \frac{R}{R_2} + 2 \right) \rightarrow R_2 = \frac{R}{\frac{R_{\text{eff}}}{R} - 2}$$

$$\text{For } R = 10 \text{ k}, R_2 = \frac{10 \text{ k}}{100 - 2} \approx 102 \Omega.$$

Ref: Wait et al, *Introduction to op-amp theory and applications*, McGraw-Hill, 1992.

