

One Qubit :

H - Gate

$$|0\rangle \mapsto \frac{|0\rangle + |1\rangle}{\sqrt{2}}$$

$$|1\rangle \mapsto \frac{|0\rangle - |1\rangle}{\sqrt{2}}$$

$$|0\rangle = \begin{pmatrix} 1 \\ 0 \end{pmatrix}$$

$$|1\rangle = \begin{pmatrix} 0 \\ 1 \end{pmatrix}$$

$$H = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$$


X - Gate $\begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$ $|0\rangle \leftrightarrow |1\rangle$

Y - Gate $\begin{pmatrix} 0 & -1 \\ 1 & 0 \end{pmatrix}$ $\sigma_y = \begin{pmatrix} 0 & -i \\ i & 0 \end{pmatrix}$

Z - Gate $\begin{pmatrix} 1 & 0 \\ 0 & -1 \end{pmatrix}$

2. Qubit Gates.


CNOT Gate

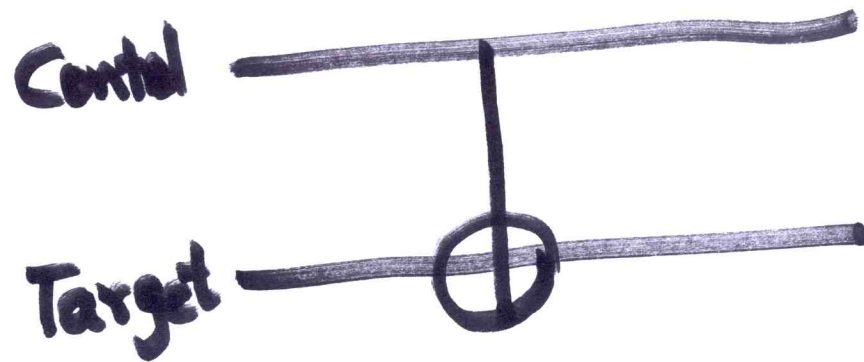

If $C=0$ No change


$C=1$
Target is
flipped


3. Qubit Gates : Toffoli (CCNOT)

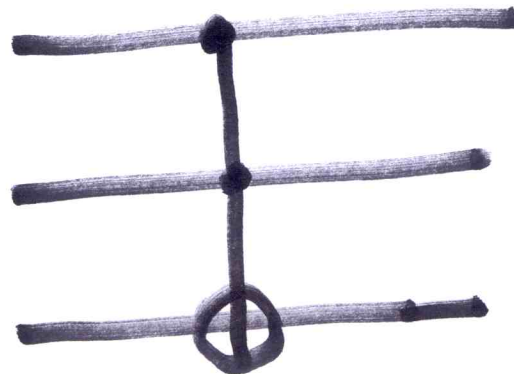


CSWAP (Fredkin)

.4.

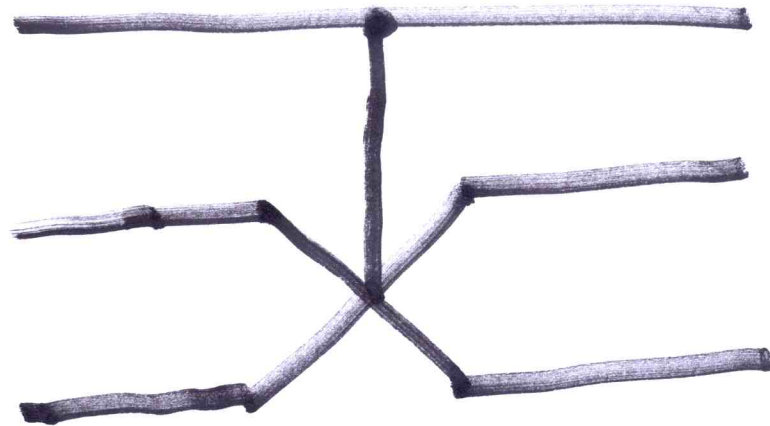

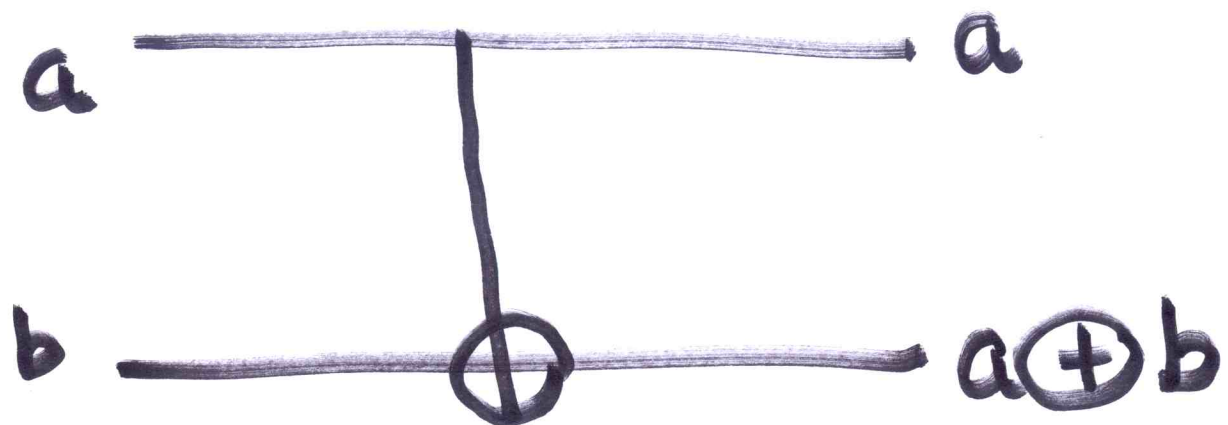


Half Adder :

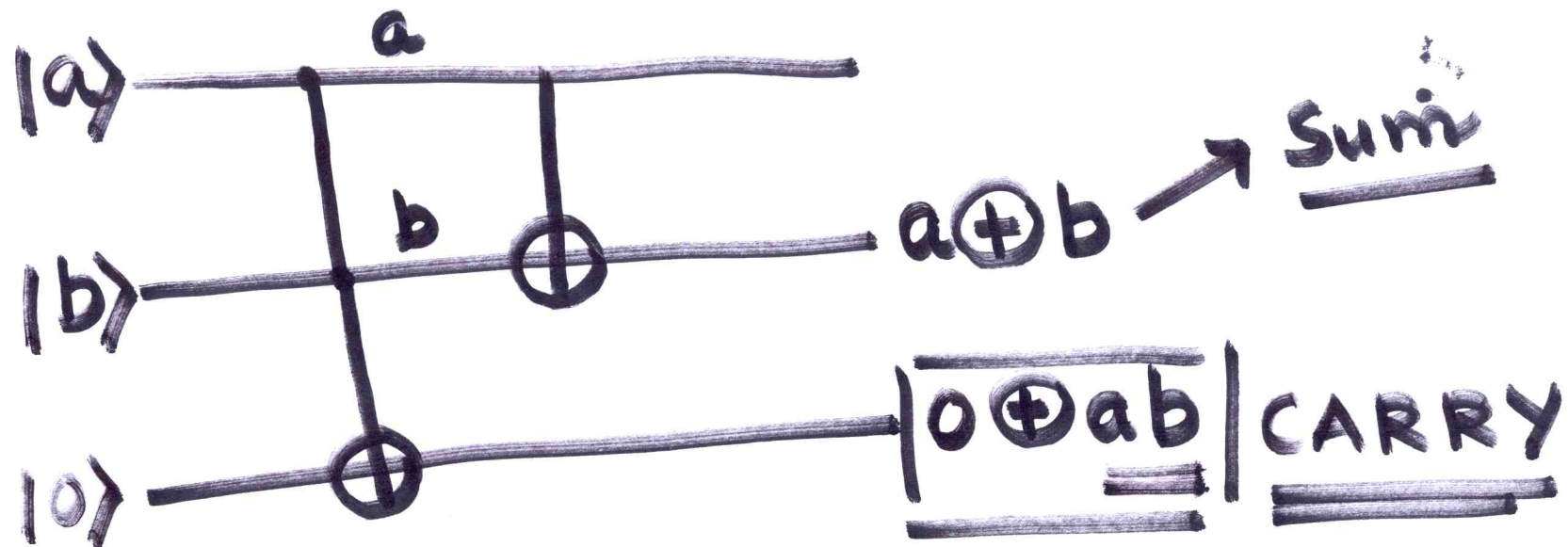


if $a = b = 1$



Oracle

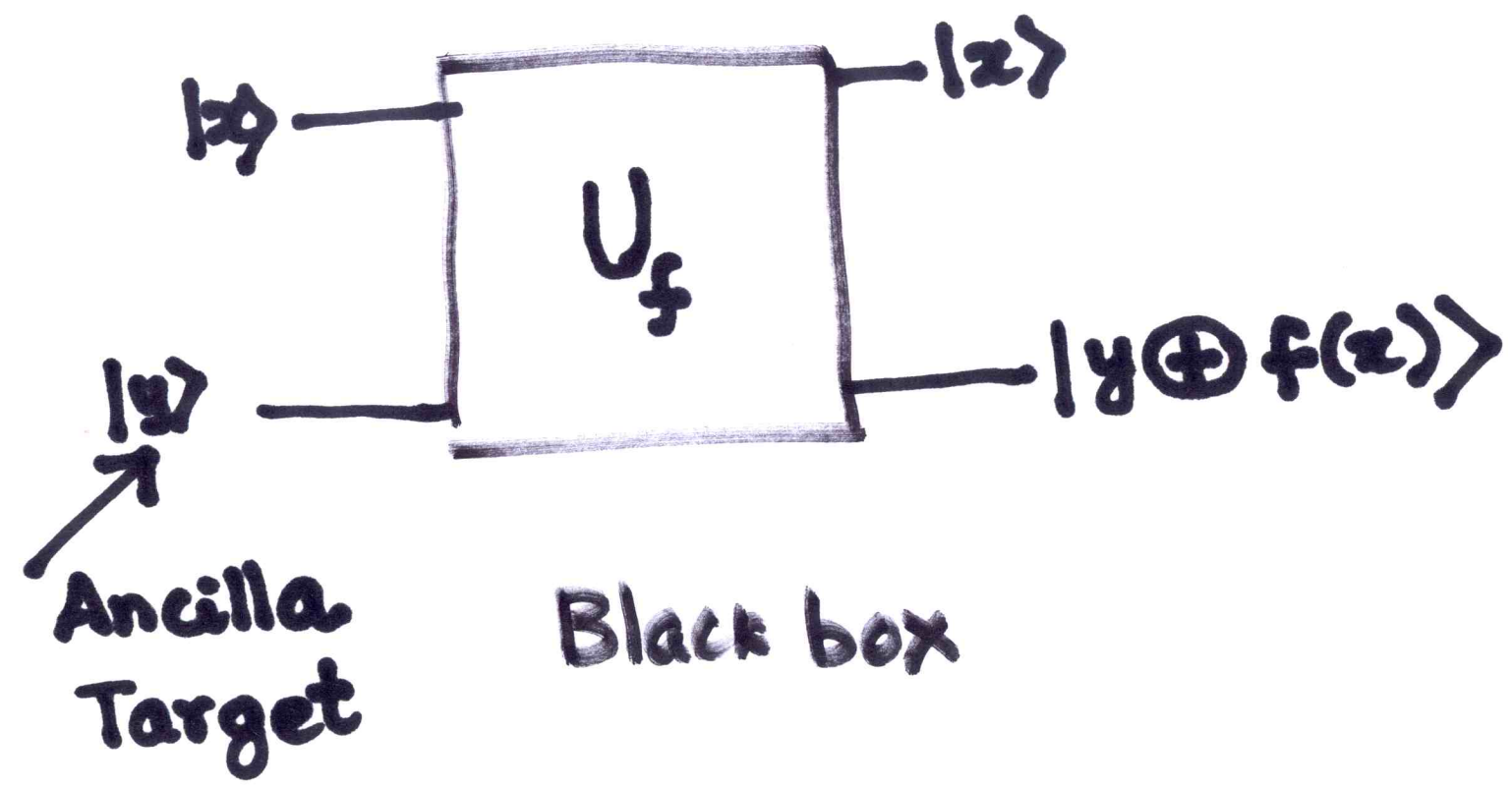

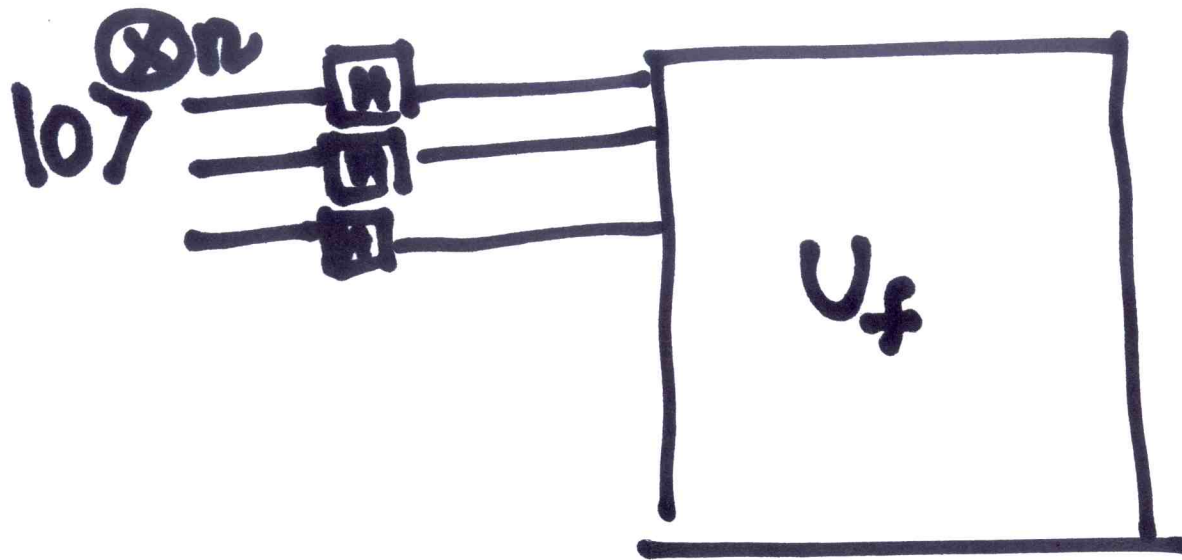

$$\begin{aligned}
 |0\rangle &= \frac{1}{\sqrt{2}} (|0\rangle + |1\rangle) \\
 |0\rangle \otimes |0\rangle &\xrightarrow{H^2} \left(\frac{1}{\sqrt{2}}\right)^2 (|0\rangle + |1\rangle) (|0\rangle + |1\rangle) \\
 &= \frac{1}{2} [|00\rangle + |01\rangle + |10\rangle + |11\rangle]
 \end{aligned}$$

Uniform superposition of 2
qubit basis

$$|0\rangle^{\otimes n} \xrightarrow{H^{\otimes n}} \frac{1}{\sqrt{2^n}} \sum_x |x\rangle$$

Uniform superposition of
 n -qubit basis