

Module – 5

UNIT -5

Field Effect Transistors

Review Questions:

1. Draw the structure of JFET and discuss its working.
2. What is 'pinch off' voltage? How to get its value experimentally?
3. An n-JFET is operated with negative gate voltage and not with positive one. Give reasons.
4. Give the structure of depletion MOSFET (D - MOSFET). How is D - MOSFET different from enhancement MOSFET (E - MOSFET)?
5. Draw and discuss drain characteristics for a D-MOSFET.
6. Discuss the formation of channel in E-MOSFET emphasizing the role of inversion layer.
7. Give self bias circuit for JFET and explain the biasing process.
8. How can we obtain negative or positive bias voltage with proper choice of resistors in a voltage divider bias?
9. Develop a simple small signal model/equivalent circuit for FET.
10. How are DMOSFET and EMOSFET connected in a circuit to work as resistors?
11. Derive expression for voltage gain for a common source amplifier.
12. Illustrate power efficiencies of CMOS devices through a CMOS inverter circuit.

Problems:-

5.1 The device parameters for an n-Channel JFET are: Maximum current $I_{DSS} = 10\text{mA}$, Pinch off voltage,

$$V_p = -4\text{V}$$

Calculate the drain current for

(a) $V_{GS} = 0$

(b) $V_{GS} = -1.0\text{V}$

(c) $V_{GS} = -4\text{V}$.

Solution:-

The expression for drain current I_D , in the saturation region is,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 \dots\dots\dots(A)$$

(a) When $V_{GS} = 0$, from Eq(A) above,

$$I_D = I_{DSS} = 10\text{mA}$$

(b) When $V_{GS} = -1.0\text{V}$, the drain current from Eq (A) is,

$$\begin{aligned} I_D &= 10 \times 10^{-3} \left[1 - \left(\frac{-1}{-4} \right) \right]^2 \\ &= 10\text{mA} \times 0.56 \\ \text{or } I_D &= 5.6 \text{ mA} \end{aligned}$$

(c) When $V_{GS} = -4\text{V} = V_p$, then from Eq(A),

$$\begin{aligned} I_D &= I_{DSS} \left[1 - \left(\frac{-4}{-4} \right) \right]^2 \\ \text{or, } I_D &= 0 \end{aligned}$$

5.2 A JFET produces gate current of 2nA when gate is reverse biased with 8V. Determine The resistance between gate and source.

Solution:-

Since reverse gate-source voltage, V_{GS} , of 8v produces gate current, I_G of 2nA, Therefore, gate-to-source resistance, R_{GS} , is

$$R_{GS} = \frac{V_{GS}}{I_G} = \frac{8V}{2nA} = 4000M\Omega$$

$$R_{GS} = 4000M\Omega$$

5.3 The reverse gate voltage of JFET when changes from 4.4V to 4.2V, the drain current changes from 2.2 mA to 2.6 mA. Find out the value of transconductance of the transistor.

Solution:-

The transconductance, g_m is defined as

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Where ΔI_D is change in drain current when change in gate-source voltage is ΔV_{GS} .

In the given problem,

$$\begin{aligned}\Delta I_D &= (2.6 - 2.2) \text{ mA} \\ &= 0.4 \text{ mA}\end{aligned}$$

And,

$$\begin{aligned}\Delta V_{GS} &= (4.4 - 4.2) \text{ V} \\ &= 0.2 \text{ V}\end{aligned}$$

Therefore,

$$g_m = \frac{0.4 \text{ mA}}{0.2 \text{ V}}$$

or , $g_m = 2.0 \text{ m mhos}$.

5.4 Find out the operating point current and voltage values (I_{DQ} and V_{DSQ}) for a self biased JFET having the supply voltage $V_{DD} = 20V$ and maximum value of drain current as 12 mA.

Solution:-

We know that the value of drain current at Q-point may be taken as half of the maximum current, that is,

$$I_{DQ} = \frac{I_{DSS}}{2} = \frac{12mA}{2} = 6.0mA$$

In the same way, the value of drain-source voltage at Q-point may be taken as half of supply voltage V_{DD} . That is,

$$V_{DSQ} = \frac{V_{DD}}{2} = \frac{20V}{2}$$

or, $V_{DSQ} = 10V$

Therefore,

$$I_{DQ} = 6.0 \text{ mA}$$

$$V_{DSQ} = 10.0 \text{ V}$$

5.5 Calculate the value of source resistance R_S required to self bias a n-JFET such that $V_{GSQ} = -3V$. The n-JFET has maximum drain-source current $I_{DSS} = 12\text{ mA}$, and pinch-off voltage, $V_p = -6V$

Solution:-

The drain current, I_D , in a JFET, in the saturation region is,

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2$$

We have, $I_{DSS} = 12\text{ mA}$, $V_{GS} = -3V$ and $V_p = -6V$, Therefore,

$$I_D = 12mA \left[1 - \left(\frac{-3}{-6} \right) \right]^2$$

or, $I_D = 9.0\text{ mA}$

Since the voltage V_{GS} is generated across the source resistor R_S , we have,


$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{3V}{9mA} \approx 333\Omega$$

$$R_S \approx 333\Omega$$

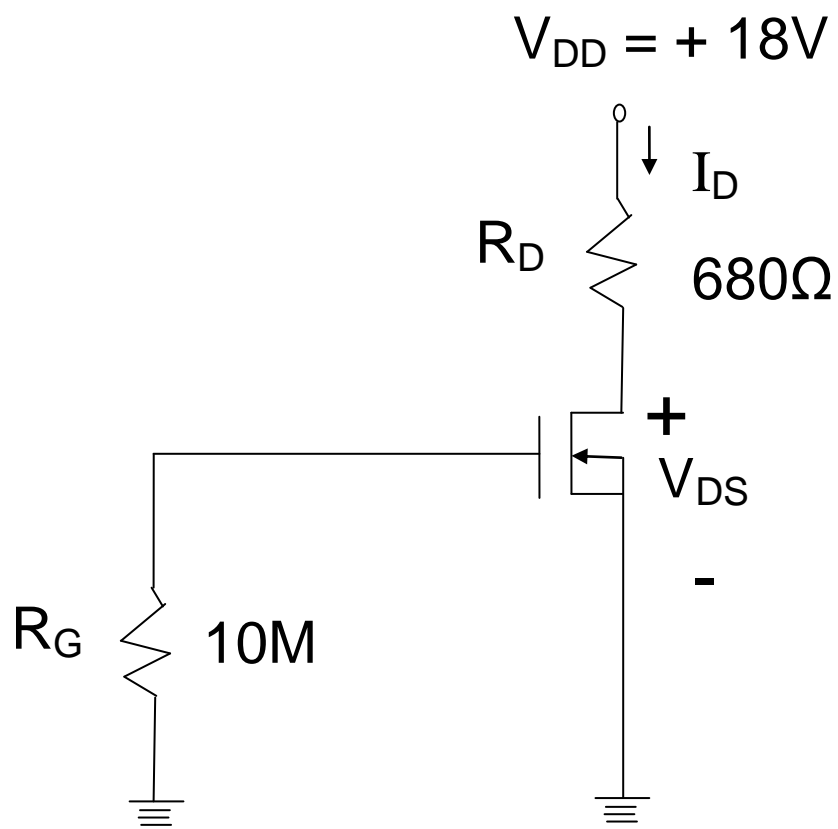5.6 For the DMOSFET circuit shown in fig., the device parameters are:

$$V_{GS(off)} = -8V, I_{DSS} = 10mA$$

Determine drain-to- source voltage V_{DS} .



Solution:-

In a MOSFET, there is no gate current. Therefore, there is no voltage drop across resistor R_G .

Thus, $V_{GS} = 0$.

Further, when $V_{GS} = 0$, $I_D = I_{DSS}$, the maximum drain current.

Summing up voltages in the output loop and using $I_D = I_{DSS}$,

We have,

$$I_{DSS} \cdot R_D + V_{DS} = V_{DD}$$

$$\text{or } V_{DS} = V_{DD} - I_{DSS} \cdot R_D$$

$$= 18 - 10 \times 10^{-3} \times 0.68 \times 10^3$$

$$= 18 - 6.8$$

$$\text{or } V_{DS} = 11.2 \text{ V}$$

5.7 Data sheet of an EMOSFET specifies following parameters:

$I_{D(on)} = 50 \text{ mA}$ at $V_{GS} = 6\text{V}$ and V_T , the threshold voltage for EMOSFET, 2V .

Determine the drain current at $V_{GS} = 3\text{V}$.

Solution:-

We first determine the conductance parameter k for the device using the relation,


$$\begin{aligned}k &= \frac{I_{D(ON)}}{V_{GS} - V_T}^2 \\ &= \frac{50 \text{ mA}}{(6-2)^2} \\ \text{or, } k &= 3.12 \text{ mA/V}^2\end{aligned}$$

Now, the drain current, I_D is expressed as,

$$\begin{aligned}I_D &= k (V_{GS} - V_T)^2 \\ &= 3.12 \times 10^{-3} (3-2)^2 \\ \text{or, } I_D &= 3.12 \text{ mA}\end{aligned}$$

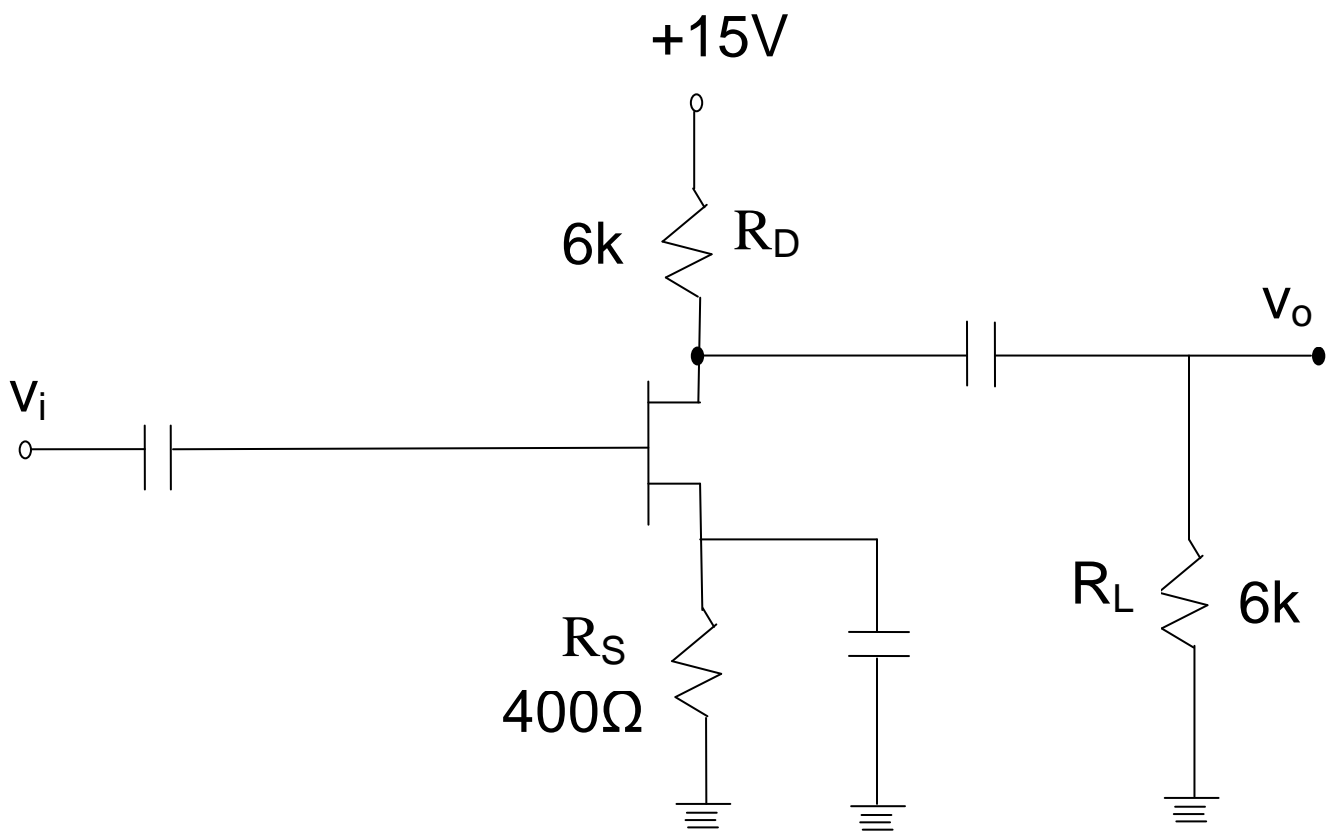5.8 The drain current changes from 5 mA to 7 mA when the gate voltage is changed from -4.0V to -3.7V in the amplifier circuit shown in fig.

Calculate the voltage gain of the amplifier.



Solution:-

In case, the source resistance R_S is ac grounded as done in the circuit of fig. the gain of amplifier is,

$$A_V = g_m \cdot r_D$$

Where g_m is transconductance of the transistor and r_D is effective ac resistance seen by the drain terminal.

Now,

$$\begin{aligned} g_m &= \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS}} \\ &= \frac{2 \text{ mA}}{0.3 \text{ V}} \\ \text{or, } g_m &= 6.66 \text{ mS} \end{aligned}$$

And,


$$r_D = R_D \parallel R_L = 6 \text{ k} \parallel 6 \text{ k} = 3 \text{ k}\Omega$$

Therefore,

$$A_V = g_m \times r_D = 6.66 \times 10^{-3} \times 3 \times 10^3$$

$$\text{or, } A_V = 20$$

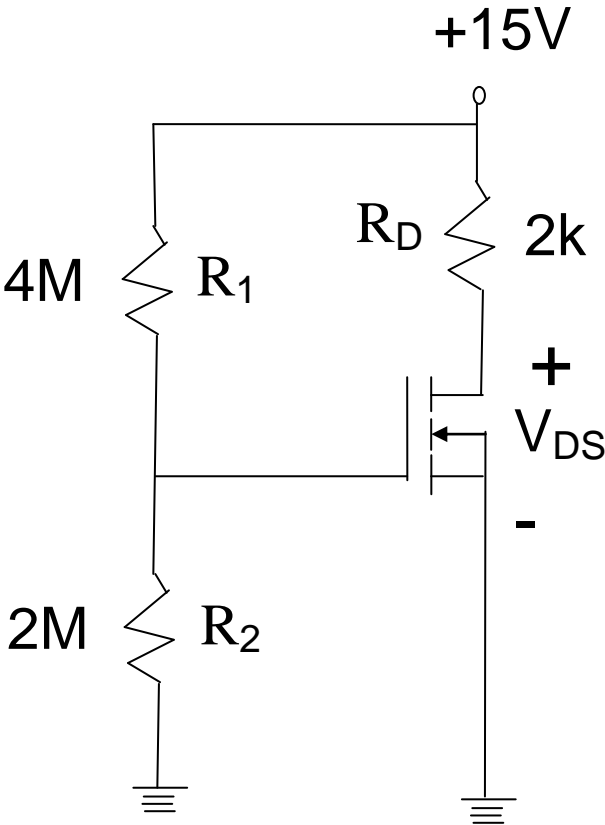5.9 Find the drain-source voltage, V_{DS} , for the NMOS transistor circuit shown in fig. The device parameters are: conductance parameter, $k = 600\mu\text{A}/\text{v}^2$ and $V_T = 2\text{V}$.



Solution:-

The gate current, I_G , is zero in a MOSFET. Then, from voltage divider network,

$$\begin{aligned} V_{GS} &= \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} \\ &= \left(\frac{2M\Omega}{4M\Omega + 2M\Omega} \right) \times 15V \end{aligned}$$

$$\text{or, } V_{GS} = 5V$$

And, as we know

$$\begin{aligned} I_D &= k (V_{GS} - V_T)^2 \\ &= 600 \times 10^{-6} \times (5 - 2)^2 \\ &= 5.4 \text{ mA} \end{aligned}$$

$$\text{or, } I_D = 5.4 \text{ mA}$$


Applying voltage summation in the output loop,

$$V_{DD} = I_D R_D + V_{DS}$$

$$\text{or, } V_{DS} = V_{DD} - I_D R_D = 15 - (5.4 \times 10^{-3} \times 2 \times 10^3)$$

$$\text{or, } V_{DS} = 4.2V$$

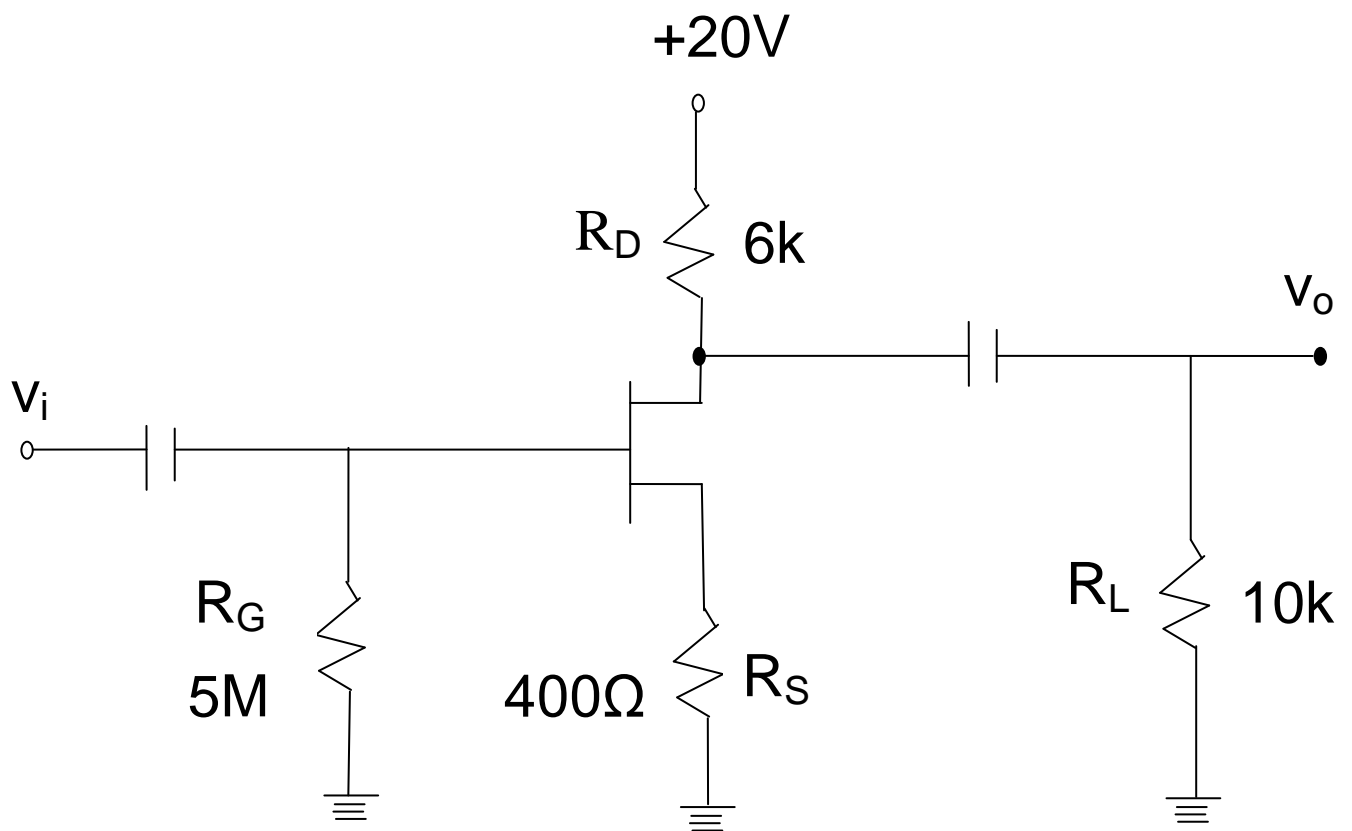5.10 Calculate the voltage gain in the amplifier shown in fig. The transconductance of the transistor is $4000\mu\text{s}$. If the 400Ω source resistance is by passed by an capacitor, how much is voltage gain now?



Solution:-

When the source resistance R_S is not bypassed, the voltage gain is,

$$A_V = \frac{g_m r_D}{1 + g_m r_s} \dots\dots\dots(A)$$

Where r_D and r_s are effective (ac) resistance seen by the drain and source of the transistor.

And,

$$\begin{aligned} r_D &= R_D \parallel R_L \\ &= 6k \parallel 10k = 3.75 \text{ k}\Omega \end{aligned}$$

And,

$$r_s = R_S = 400\Omega$$

Therefore

$$\begin{aligned} A_V &= \frac{4000 \times 10^{-6} \times 3.75 \times 10^3}{1 + 4000 \times 10^{-6} \times 400} \\ &= \frac{4 \times 3.75}{2.6} = 5.7 \\ A_V &= 5.7 \end{aligned}$$

In case, R_S is bypassed, the gain ($r_s = 0$ in the Eq(A)),

$$A_V = g_m r_D = 4000 \times 10^{-6} \times 3.75 \times 10^3$$

$$\text{or, } A_V = 15$$

