

# LOGIC REPRESENTATION OF ADDER



## 2 Bit Adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

With Initial carry  $C_{in}$


$$S = A \oplus B \oplus C_{in}$$
  
$$C_{out} = (A \oplus B) \cdot C_{in} + A \cdot B$$





Full Adder
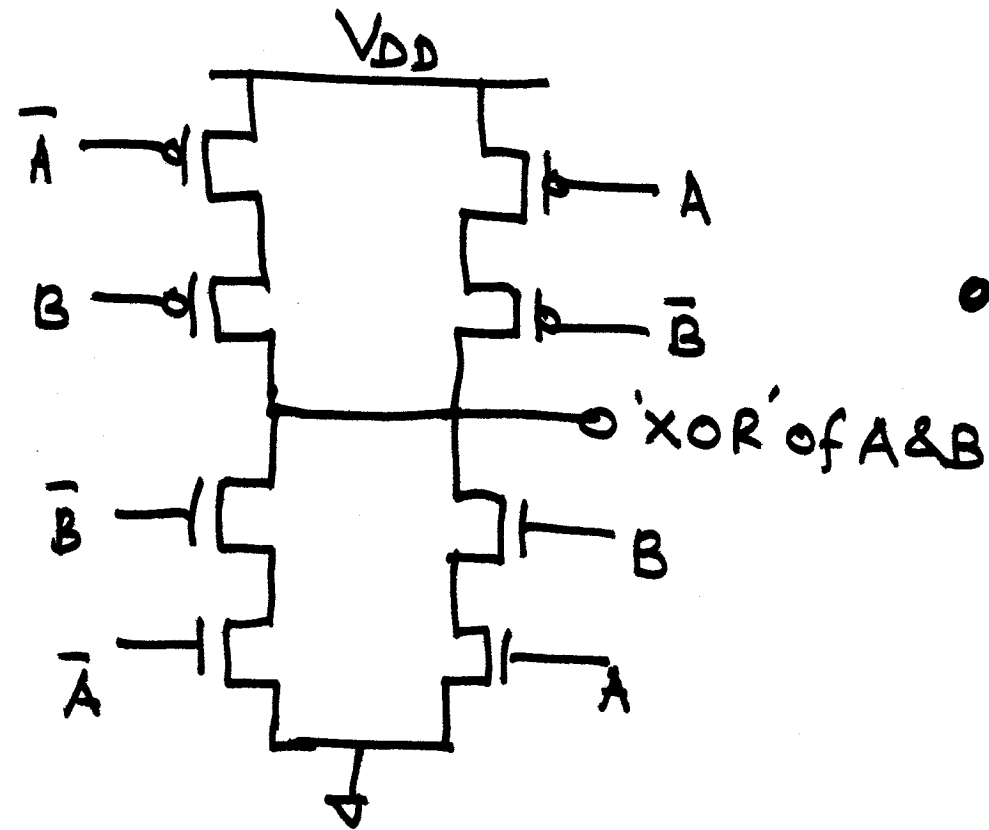
# DESIGN STYLE FOR 'XOR' IN CMOS Technology




Static CMOS
 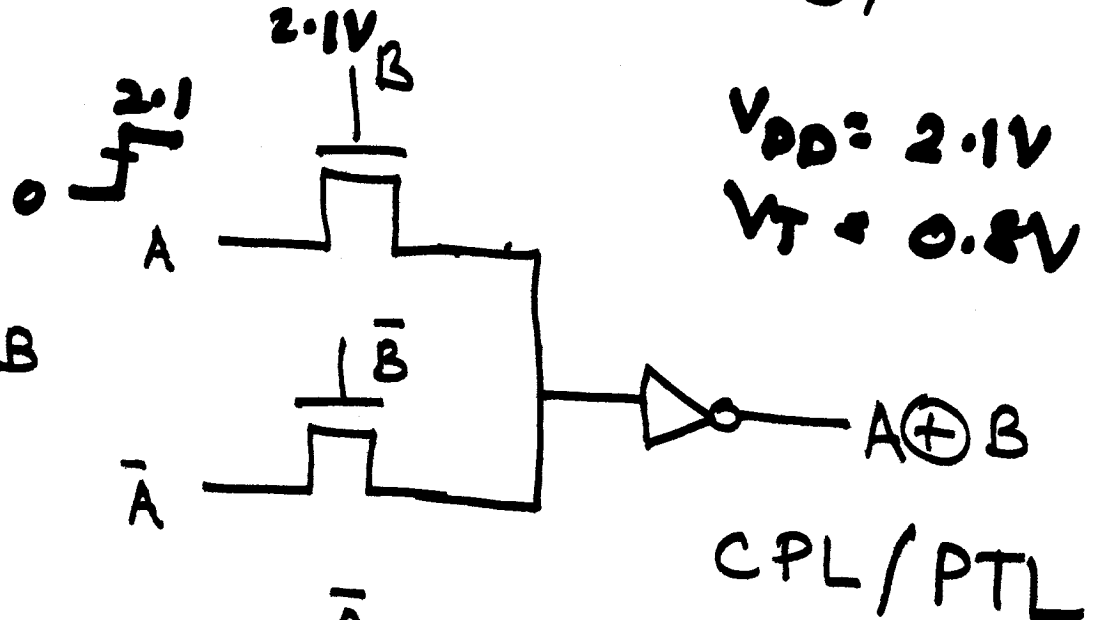
$$A \oplus B = \overline{(AB + \bar{A}\bar{B})}$$



# DUAL RAIL DOMINO

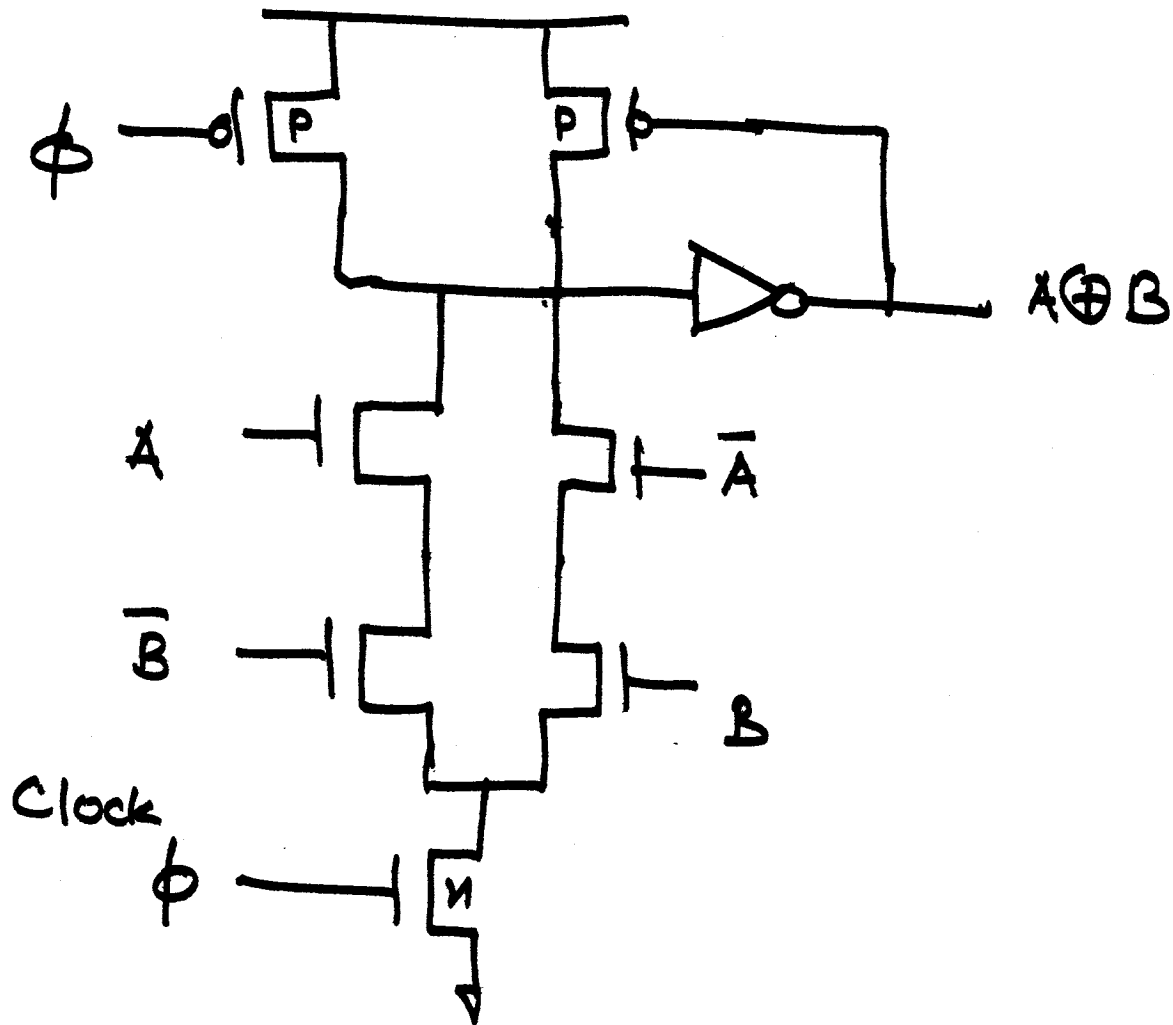

# COMPARISON OF DESIGN STYLES FOR ADDER CIRCUIT

Parameter	Static CMOS	CPL	DPL	Dual Rail DOMINO
Power (mW)	34.3	34.5	27.5	82.5
Worst Case Delay (ns)	2.33	2.24	1.98	1.78
Energy ( $\mu$ J)	79.9	77.3	54.5	146.9
Area: in Total Transistor Width ( $\mu$ m)	27355	17437	19117	32444

s. Technology :  $V_{DD} = 3.3V$ ,  $f = 100MHz$