 


Transfer to Left Register &




Mode = 0  
 No Addition is Desired  
 "NO ADD" &  
 Shift 1 bit on Right  
 Mode = 0 NoAdd &  
 1 bit on Right

Mode = 1 Add operation  
 of Multiplicand content  
 with Left Shift-Register

As status of Register  
 Now Shift bits to Right

Now Status is

 

Now  $M = 0$   
No 'Add', but Shift Right,  
But Operation is not needed  
As 3 bit operation is  
Completed

Final Status



$\therefore$  Final Number is 10100 which is Output

Decimal Numbers {  
Multiplicand 101  $\rightarrow$  5  
Multiplier 100  $\rightarrow$  4  
Multiplication Output =  $5 \times 4 = 20$   
= 10100

# ALGORITHM of Baugh-Wooley

## MULTIPLIER

X and Y are the Multiplicand and Multiplier  
2's Complemented Numbers. Then

$$X = -x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

$$Y = -y_{n-1}2^{n-1} + \sum_{j=0}^{n-2} y_j 2^j$$


Product  $P = X \cdot Y$

$$\therefore P = X_{n-1} Y_{n-1} 2^{2n-2} + \sum_{i=0}^{n-2} \sum_{j=0}^{n-2} x_i y_j 2^{i+j}$$


$$- X_{n-1} \sum_{j=0}^{n-2} y_j 2^{n+j-1} - Y_{n-1} \sum_{i=0}^{n-2} x_i 2^{n+i-1}$$

To Avoid Subtractor Cell use, we represent -ve quantities as

 
$$- X_{n-1} \sum_{j=0}^{n-2} y_j 2^{n+j-1} = X_{n-1} \left[ -2^{2n-2} + 2^{n-1} + \sum_{j=0}^{n-2} y_j 2^{n+j-1} \right]$$



Block cell - 3

 

Block Cell - 4

 


Block cell - 5


# FIVE BASIC OPERATION BLOCKS

In

## Baugh - Wooley Multiplier

 

Block Cell - 1

 

Block - cell - 2

In this Multiplier we need

1. 2's Complement Generator
2. AND GATES to get Partial Products
3. Full Adders

To Save Area and also to Improve Speed  
 $n \times m$  bit Multiplier is arranged in  
an ARRAY-FORM.





In Booth's MULTIPLIER we recode  
2's Complement Nos.

Since we use Binary Nos, we observe  
that :

$j$ -long sequence of 1's is equivalent to

$\Rightarrow$   $(j-1)$  long sequence of 0's.

Replacement of 1's by 0's reduce Partial  
Product Terms.

# Weakness of Booth's Simple Recoding Technique:

Technique:

It may create more 1's than initial number of 1's in the sequence after Recoding. This happens when in the number we have sparse 1's. Ex.


85  $\rightarrow$  001010101

$\rightarrow$  Number

0 1, -1, 1, -1, 1, -1

$\rightarrow$  Booth Coded

# MODIFIED BOOTH RECODING

 

Here  $x_0 - x_{n-1}$  are the Original Numbers

$y_0 - y_{n-2}$  are Modified Booth Recoded Numbers,

Example here uses Radix-4 Scheme

What we learn :- 3 bits inspected & 2 bits get eliminated


$x_i$	Inspected Bits		Recoded Bits		Recoded Digit.	
	$x_{i-1}$	$x_{i-2}$	$y_i$	$y_{i-1}$	times (A)	Multiplicand.
0	0	0	0	0	0	0
0	0	1	0	1	+ 1	1A
0	1	0	0	1	+ 1	1A
<del>0</del>	<del>1</del>	<del>1</del>	<del>1</del>	<del>0</del>	<del>+ 2</del>	<del>2A</del>
1	0	0	- 1	0	- 2	- 2A
1	0	1	0	- 1	- 1	- 1A
1	1	0	0	- 1	- 1	- 1A
1	1	1	0	0	0	0

# Example

Multiplicand A            0 0 1 1 0 1            (13)

Multiplier x            1 1 1 0 1 0            (-6)

Booth Recoding of x

 

Multiplicand A      0   0   1   1   0   1

Multiplier X      1   1   1   0   1   0

Decimal  
13

x - 6  
-----  
-78

OPERATION

0      -A      -2A

Initial 0      0   0   0   0   0   0

Add (-2A)      +    1   0   0   1   0   1

-----  
1   0   0   1   0   1

Shift 2 bits      1   1   0   1   0   0   1   0   1

Add (-1A)      +    1   1   0   0   1   1   0   0

-----  
Neglect 1 | 1 | 0   1   1   0   0   0   1  
← overflow →

Last

1 0 1 1 0 0 0 1

Shift 2  
bits

1 1 1 0 1 1 0 0 0 1

Add (0.A) +

0 0 0 0 0 0 0 0 0 0

Sign  
Bit:



1 1 | 1 0 1 1 0 0 0 1

⇨ -78





# Partial Product Generator

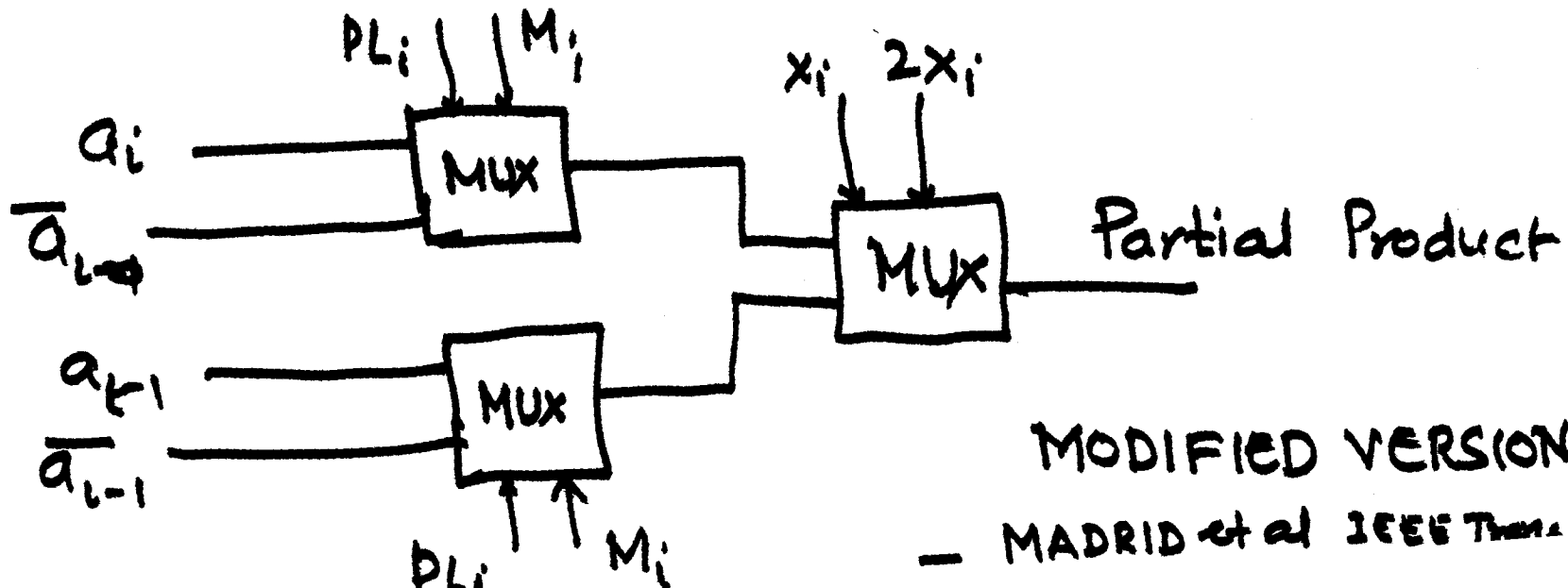 

MODIFIED VERSION

- MADRID et al IEEE Trans. 11/81 1002

Shifter uses Pass Gates & Buffer.

