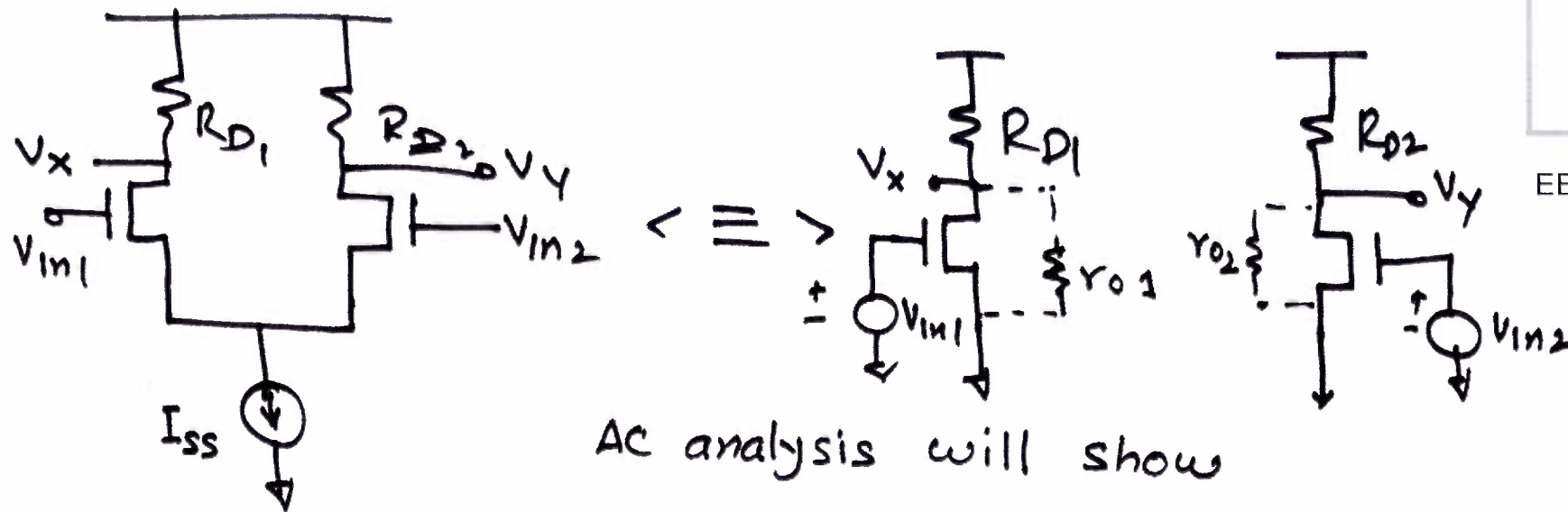




CDEEP
IIT Bombay

EE 618 L 11 / Slide 1



AC analysis will show


$$\frac{V_x}{\Delta V_{in1}} = -g_{m1} (R_{D1} \parallel r_{o1})$$

$$\& \quad \frac{V_y}{-\Delta V_{in1}} = \frac{V_y}{+\Delta V_{in2}} = -g_{m2} (R_{D2} \parallel r_{o2})$$


$$\text{or} \quad \frac{V_x - V_y}{\Delta V_{in1}} = \frac{V_x - V_y}{\Delta V_{in}} = \frac{\Delta V_o}{\Delta V_{in}} = A'_{Vo} = -g_{m1} (R_{D1} \parallel r_{o1}) - g_{m2} (R_{D2} \parallel r_{o2})$$

$$\text{or } A'_{Vo} = -2g_m (R_D \parallel r_o) \quad \text{if } g_m = g_{m1} = g_{m2} \quad \& \quad r_o = r_{o1} = r_{o2}, R_D = R_{D1} = R_{D2}$$

OR

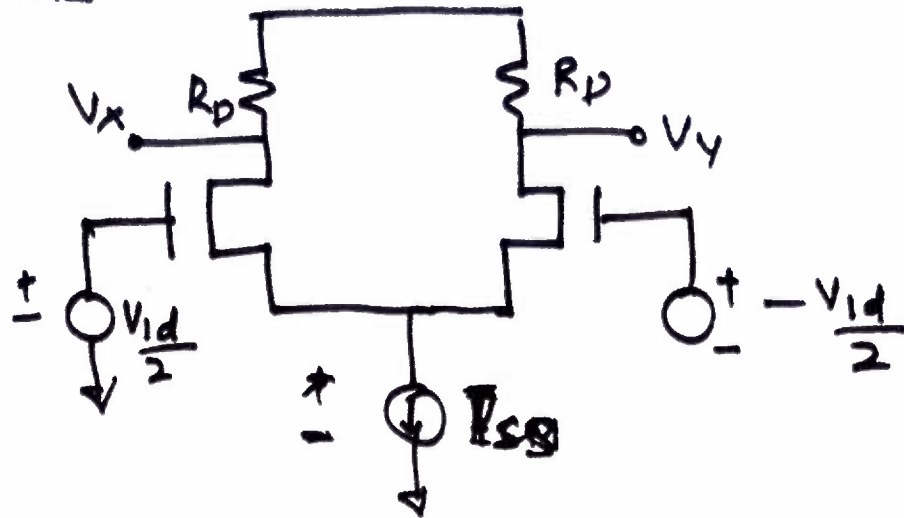

For Difference Mode case

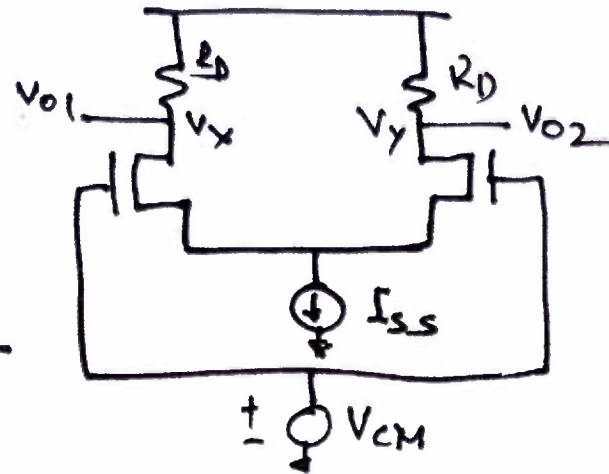

$$V_x = -g_{m1} (R_D \parallel r_{o1}) \frac{V_{id}}{2}$$

$$V_y = +g_{m2} (R_D \parallel r_{o2}) \frac{V_{id}}{2}$$

$$\text{or } \frac{V_x - V_y}{V_{id}} = -g_m (R_D \parallel r_o)$$

$$\begin{cases} g_m = g_{m1} = g_{m2} \\ r_{o1} = r_{o2} = r_o \end{cases}$$

$$\text{or } A_{v_{DM}} = -g_m R_D \quad \text{if } r_o \gg R_D$$

For Common Mode $V_{in1} = V_{in2} = V_{cm} = \frac{V_{in1} + V_{in2}}{2}$

$$\therefore A_{v_{CM}} = \frac{V_x - V_y}{V_{cm}} = \frac{V_x - V_x}{V_{cm}} = 0$$



CDEEP
IIT Bombay


EE 618 L 11 / Slide 2





However $A_{V_{DM}}$ is defined as $\frac{\Delta V_o}{2\Delta V_{in}}$

$$\text{or } \frac{V_{o1} - V_{o2}}{V_{in1} - V_{in2}} = \frac{V_x - V_y}{V_{in1} - V_{in2}} = A_{V_{DM}} = -g_m(R_D \parallel r_o)$$

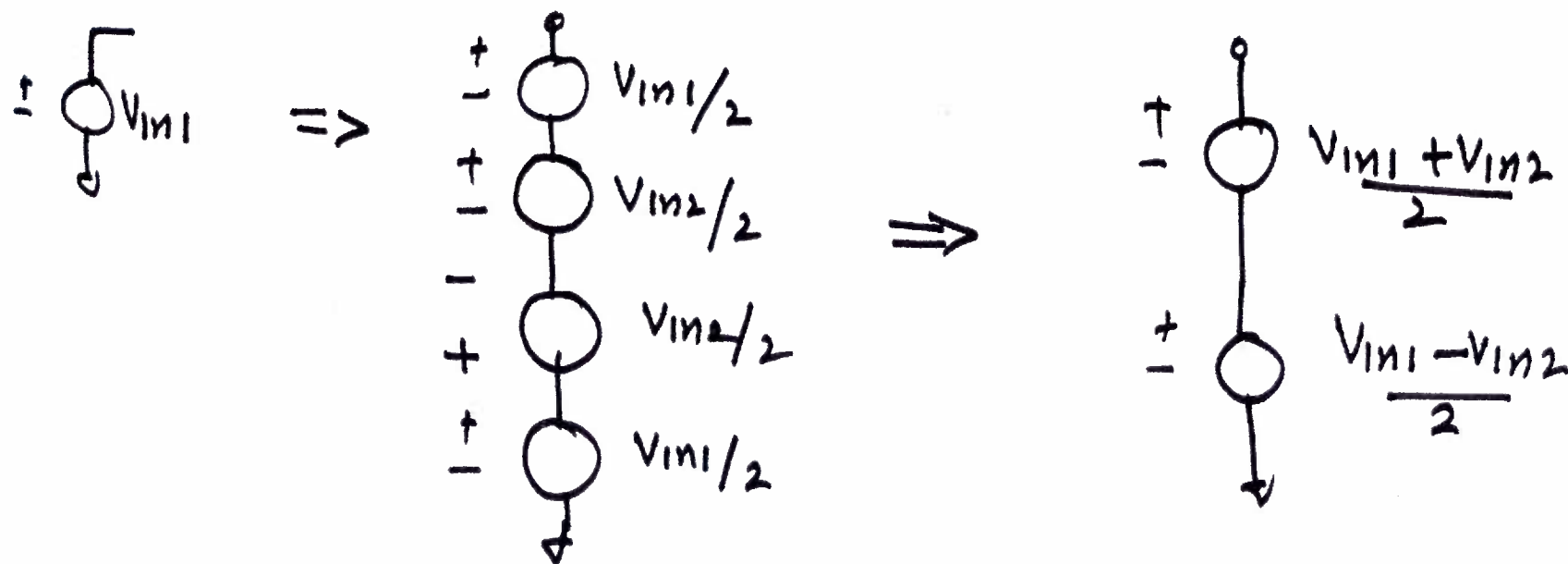In case two inputs are not Fully Differential, we still can use Half Ckt Concept-



Thus

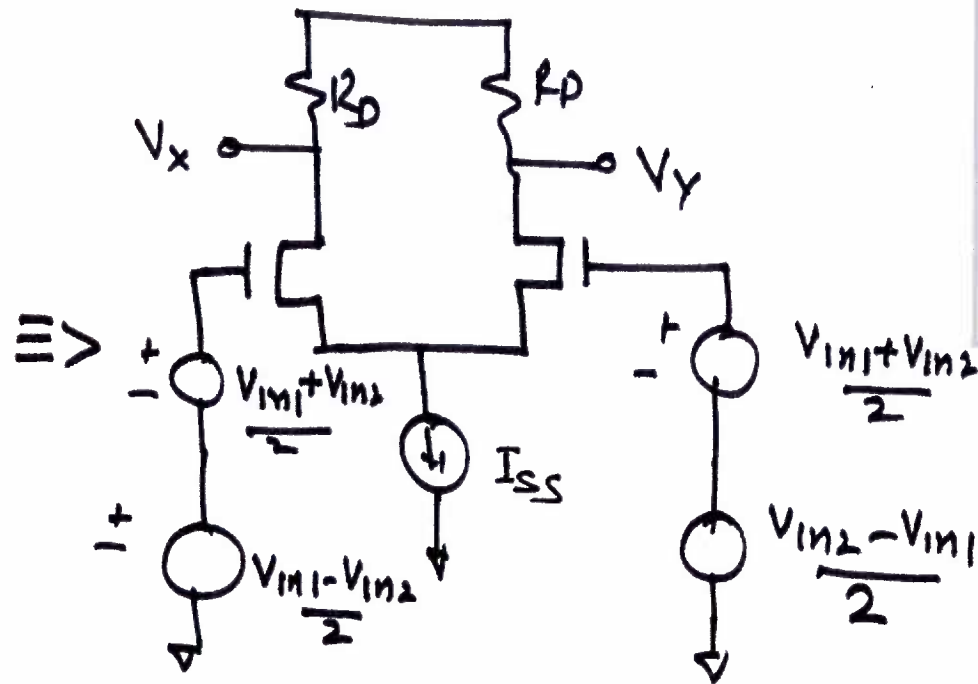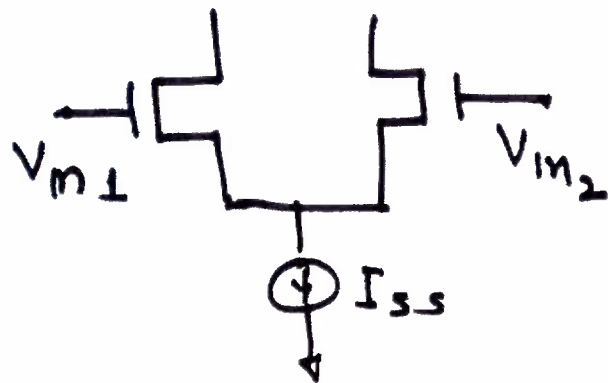

CDEEP
IIT Bombay

EE 618 L 11 / Slide 4

We define V_{CM} = Common Mode Voltage = $\frac{V_{in1} + V_{in2}}{2}$




V_{DM} = Difference Mode Voltage = $V_{id} = V_{in1} - V_{in2}$



CDEEP
IIT Bombay

EE 618 L II / Slide 5

We relook A_{vcm} again

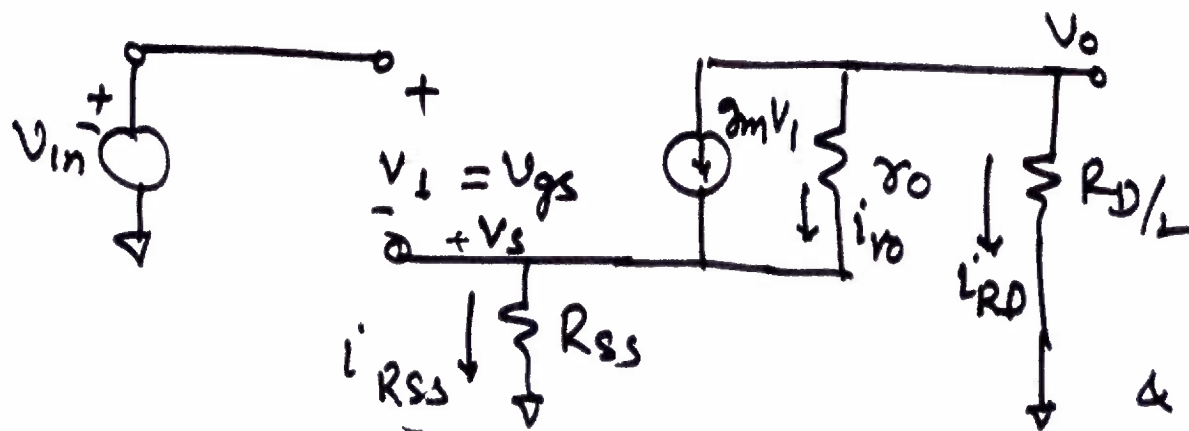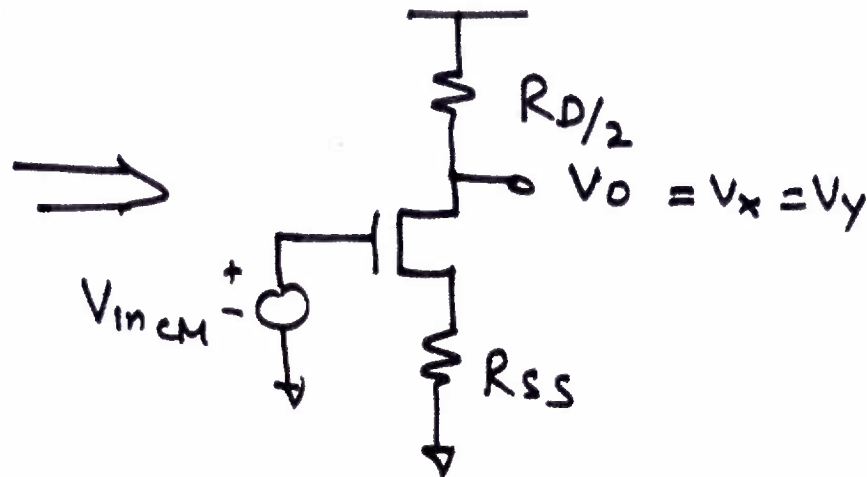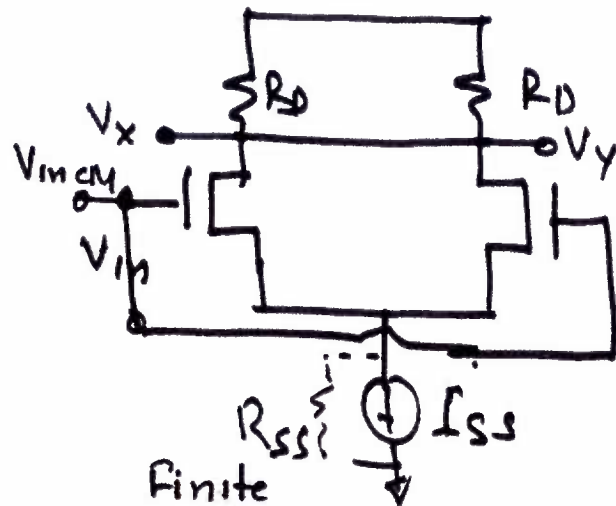

$$i_{RD} = -i_{RSS}$$

$$V_s = i_{RSS} \cdot R_{SS}$$

$$i_{RD} = \frac{V_o}{R_{D/2}}$$

$$\& \quad g_m V_1 + i_{ro} = i_{RSS} = -i_{RD}$$



CDEEP
IIT Bombay

EE 618 L 11 / Slide 6

$$V_1 = V_{in} - V_S = V_{in} + \frac{V_o}{R_{D/2}} R_{SS}$$

$$i_{r_o} = I_{R_{SS}} - g_m V_1$$

$$= -\frac{V_o}{R_{D/2}} - g_m \left(V_{in} + \frac{V_o R_{SS}}{R_{D/2}} \right)$$

$$= -\frac{2V_o}{R_D} (1 + g_m R_{SS}) - g_m V_{in}$$

$$\therefore V_o = V_S + i_{r_o} \cdot r_o$$

$$= -\frac{2V_o}{R_D} R_{SS} - \frac{2V_o}{R_D} (1 + g_m R_{SS}) r_o - g_m r_o V_{in}$$

$$\begin{aligned} \therefore \frac{V_o}{V_{inCM}} = A_{VCM} &= \frac{-2 g_m r_o (R_{D/2})}{R_D + 2R_{SS} + 2r_o(1 + g_m R_{SS})} \quad \text{If } R_{SS} \gg \frac{1}{g_m} \\ &= \frac{-R_{D/2}}{\frac{1}{g_m} + R_{SS}} \approx -\frac{R_D}{2R_{SS}} = \frac{-g_m R_D}{2(1 + g_m R_{SS})} \end{aligned}$$




CDEEP
IIT Bombay

EE 618 L II / Slide 7

If M_1 & M_2 do not have Identical Characteristics, due to Mismatches, then $V_x \neq V_y$

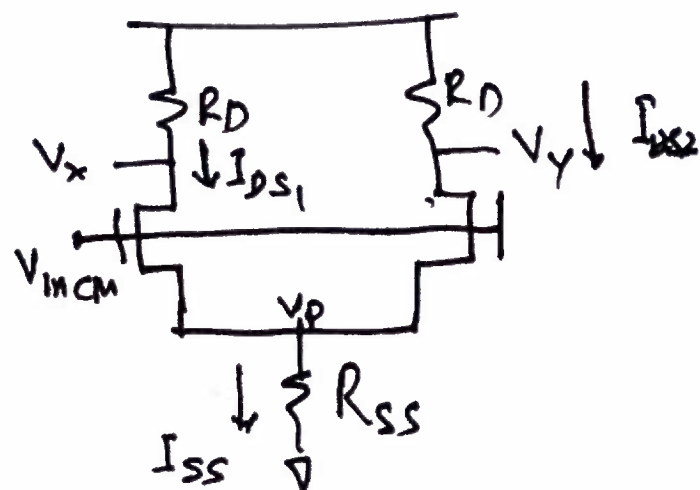Then from the eq. circuit of Symmetry cannot be used.



$$\therefore I_{DS1} = g_{m1} (V_{inCM} - V_P)$$

$$I_{DS2} = g_{m2} (V_{inCM} - V_P)$$

$$\therefore V_P = (I_{DS1} + I_{DS2}) \cdot R_{SS}$$

$$= \frac{(g_{m1} + g_{m2}) R_{SS}}{1 + (g_{m1} + g_{m2}) R_{SS}} V_{inCM}$$

$$\text{Then } V_x = -I_{DS1} \cdot R_D$$

$$V_x = -g_{m1} (V_{inCM} - V_P) R_D =$$

$$= \frac{-g_{m1} R_D}{1 + (g_{m1} + g_{m2}) R_{SS}} V_{inCM}$$

$$\text{Similarly } V_y = \frac{-g_{m2} R_D V_{inCM}}{1 + (g_{m1} + g_{m2}) R_{SS}}$$



CDEEP
IIT Bombay

EE 618 L II / Slide 8

$$\therefore V_x - V_y = - \frac{(g_{m1} - g_{m2}) R_D}{1 + (g_{m1} + g_{m2}) R_{SS}} V_{INCM}$$

$$\therefore A_{VCM-DM} = - \frac{\Delta g_m R_D}{1 + g_m R_{SS}}$$

Where $\Delta g_m = g_{m1} - g_{m2}$

$$g_m = g_{m1} + g_{m2}$$

Then we define $CMRR = \frac{A_{VDM}}{A_{VCM-DM}}$

$$\cong \frac{2g_m}{\Delta g_m} (1 + g_m R_{SS})$$


$\therefore$ For larger CMRR requirements

1. g_m 's be larger $\leftarrow \begin{matrix} I_{DS} \\ W/L \end{matrix}$


2. R_{SS} be large

3. Mismatch be minimised: $\Delta g_m \rightarrow$ smaller


DIFFAMP WITH DIFFERENT LOADS

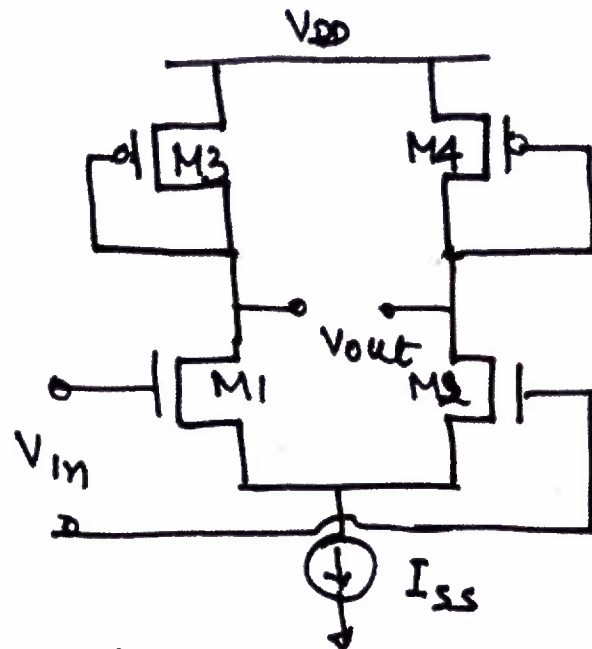

Diode Connected Load

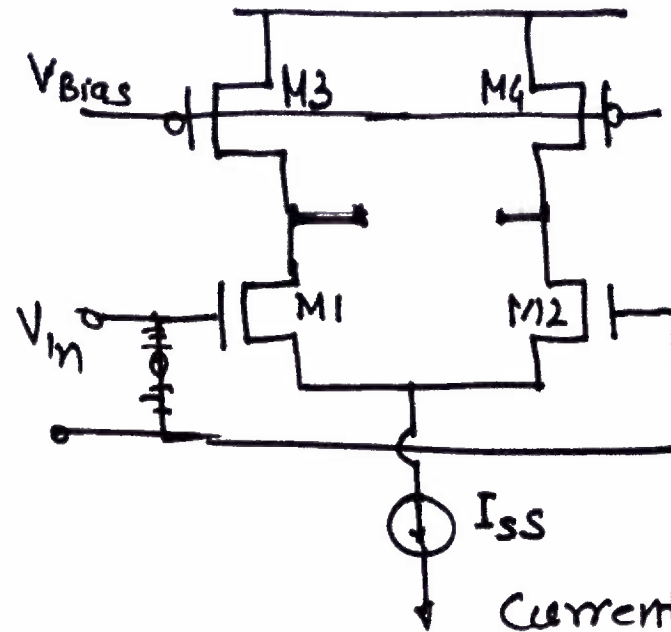

Current Source Load

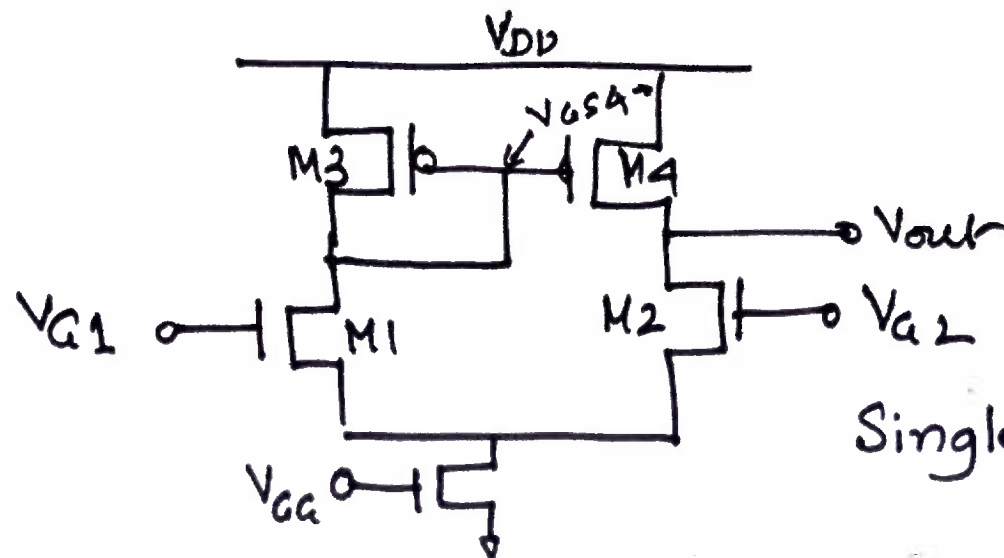

Single Ended DIFFAMP



CDEEP
IIT Bombay

EE 618 L 11 / Slide 9



CDEEP
IIT Bombay

EE 618 L 11 / Slide 10

For Diode connected load :—

$$R_{\text{Load}} = g_{mp}^{-1} \parallel r_{op} \approx g_{mp}^{-1}$$

$$\text{Then } A_v = -\frac{g_{mn}}{g_{mp}} = \sqrt{\frac{\mu_n}{\mu_p} \cdot \frac{(W/L)_n}{(W/L)_p}}$$

For Current Source load :

$$R_{\text{Load}} = r_{op}$$


$$\therefore A_v = -g_{mn} (r_{on} \parallel r_{op})$$

Current Sink (Current Mirror) DIFFAMP



CDEEP
IIT Bombay

EE 618 L 11 / Slide 11

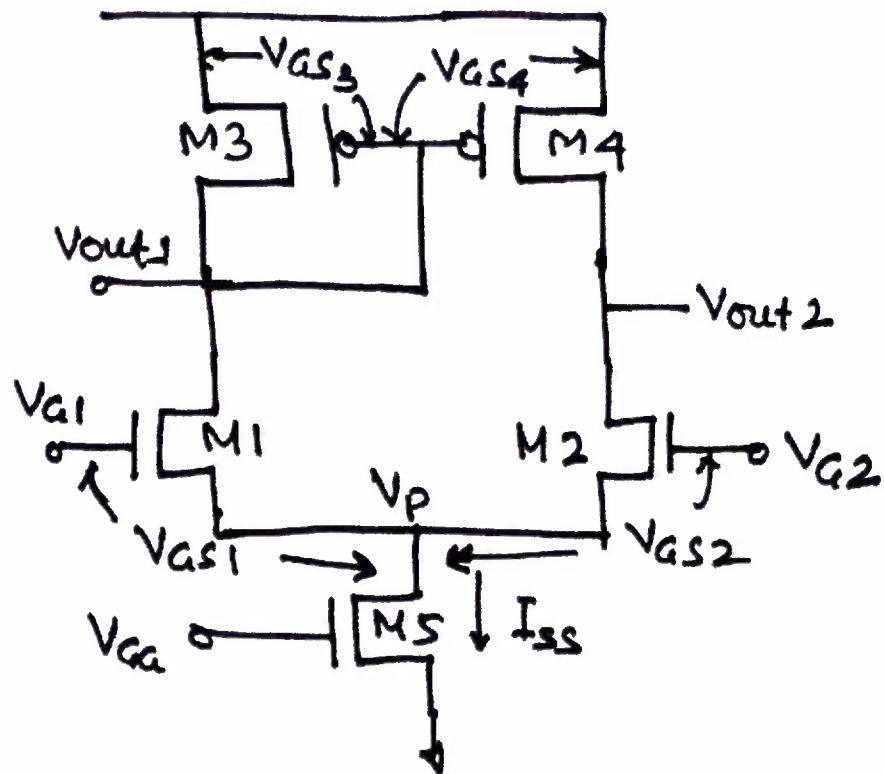

$$V_{a1} - V_{a2} = V_{id}$$

$$\therefore V_{G1} = +\frac{V_{id}}{2}$$

$$V_{G2} = -\frac{V_{id}}{2}$$


$$V_{GS1} = V_{a1} - V_p =$$

$$V_{GS2} = V_{a2} - V_p =$$

As M5 is acting as current source I_{ss} which gives

r_{os} = Output resistance of M5 based Current Source and $\rightarrow \infty$ (V. high)

Hence we can assume: $V_p \rightarrow 0$

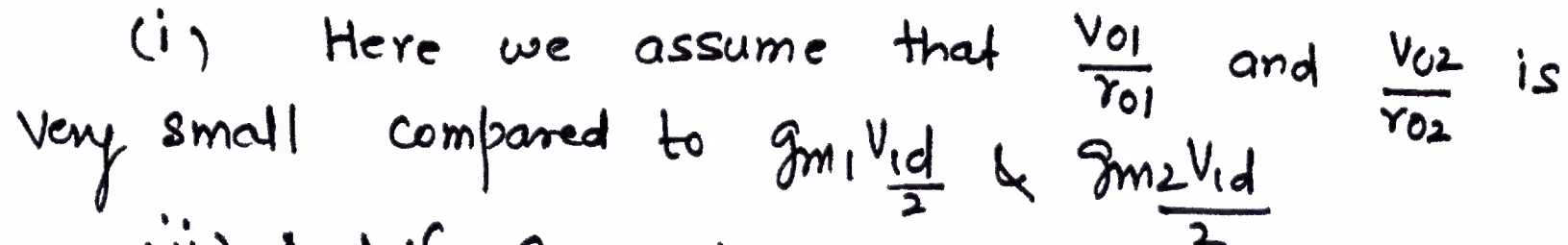EE 618 L 11 / Slide 12

Hence $V_p = V_c = 0$



CDEEP
IIT Bombay

EE 618 L 11 / Slide 13

