

As $\frac{g_m}{I_{DS}}$ is our Design Parameter, lets


see the Short channel effect in this perspective

For Degenerate Source resistance case

$$\frac{g_m}{I_{DS}} = \frac{1}{1+g_m R_{Sx}} \cdot \frac{2}{V_{OV}}$$

$$\text{or } \frac{1}{V_{OV}} = \frac{(1+g_m R_{Sx})}{2} \frac{g_m}{I_{DS}} \quad \text{or } \frac{1}{(1+g_m R_{Sx})} V_{OV} = \frac{g_m}{2 I_{DS}}$$

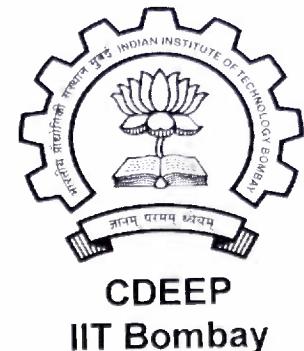Substituting this in $\frac{I_{DS}}{I_{SS}}$ expressions for Long & Short channel cases.





CDEEP
IIT Bombay

Long channel : $\frac{I_{ODS}}{I_{SS}} = \left[\frac{1}{2} \frac{g_m}{I_{DS}} V_{ID} \right] - \frac{1}{8} \left[\frac{1}{2} \frac{g_m}{I_{DS}} V_{ID} \right]^3$

Short Channel
case

$$\frac{I_{ODS}}{I_{SS}} = \left[\left(\frac{g_m}{2 I_{DS}} \cdot V_{ID} \right) - \frac{1}{8} \left(\frac{1}{1 + g_m R_{SX}} \right) \left(\frac{1}{2} \frac{g_m}{I_{DS}} \cdot V_{ID} \right)^3 \right]$$


so even with this design parameter ($\frac{g_m}{I_{DS}}$)

linearity ($\frac{I_{ODS}}{I_{SS}}$) definitely is better for

short channel case than Long channel one.

However this was found only with one effect.

Current Sources & Sinks

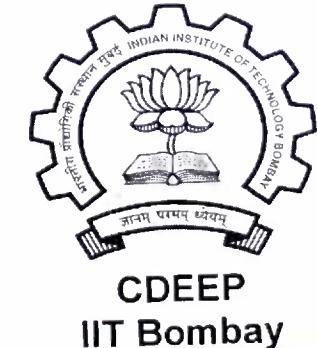

In CMOS Analog IC, current source/sink (CS) acts like a basic Building Block.


EE 618 L₁₃ / Slide 3

- (i) Major requirement for Good CS is, its Output Impedance be very high (Ideal $R_{out} = \infty$).
- (ii) To keep devices in Saturation, output swing be limited

→ The Current Mirror try to satisfy above needs but may face limits.

↑ (iii) V_{min} — Drop across Current Source

Current Mirror for I_0 Current Source

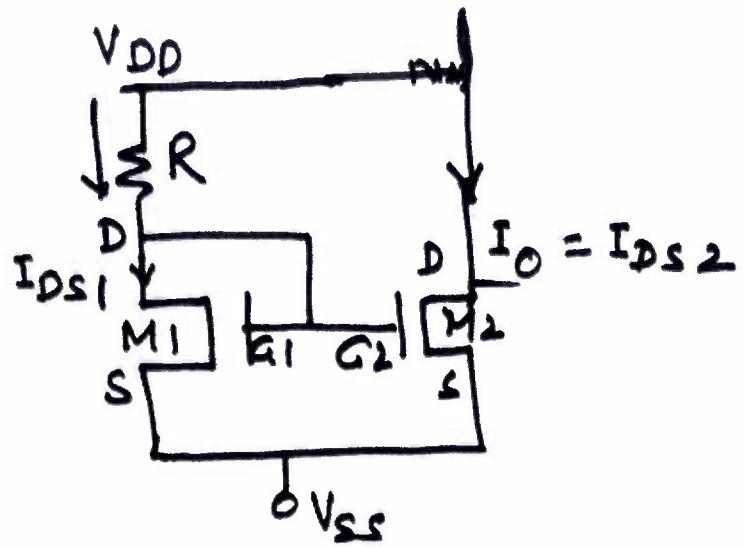

For M1

(i) Current through
R is same as
 I_{DS1} of M_1

(ii) $V_{DS1} = V_{GS1}$

Clearly M_1 is always in Saturation.

(iii) further $V_{GS1} = V_{GS2} = V_{DS1}$


Hence $I_{DS1} = I_{DS2}$ ($\text{If } \frac{W_2}{L_2} = \frac{W_1}{L_1}$)

$$(iv) I_{DS1} = \frac{V_{DD} - V_{GS1} - V_{SS}}{R} = \frac{\beta'}{2} \left(\frac{W_1}{L_1} \right) (V_{GS1} - V_{T1})^2 (1 + \lambda V_{DS1})$$

A

$$I_{DS2} = \frac{\beta'}{2} \left(\frac{W_2}{L_2} \right) (V_{GS2} - V_{T2})^2 (1 + \lambda V_{DS2})$$

$$\text{But } I_{DS2} = I_0$$

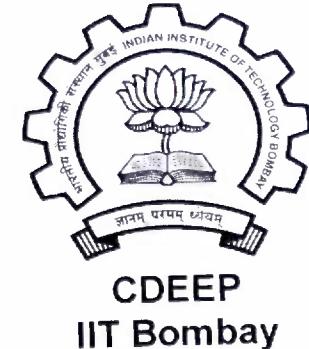

$$\therefore \frac{I_{DS2}}{I_{DS1}} = \frac{I_0}{I_{DS1}} = \frac{\frac{W_2}{L_2}}{\frac{W_1}{L_1}} \frac{(1+\lambda V_{DS2})(V_{GS2}-V_{T2})^2}{(1+\lambda V_{DS1})(V_{GS1}-V_{T1})^2} \frac{\beta'_2}{\beta'_1}$$

If $V_{T2} = V_{T1}$, $\beta'_2 = \beta'_1$



Further If λ is very small, then

$$\frac{I_0}{I_{DS1}} = \frac{(W_2/L_2)}{(W_1/L_1)}$$

$$\therefore I_0 = \frac{(W/L)_2}{(W/L)_1} \cdot \frac{V_{DD} - V_{GS1} - V_{SS}}{R}$$

$$R_{out} = r_{o2} = \frac{1}{\lambda I_{DS2}} = \frac{1}{\lambda I_0} = \frac{V_A}{I_0} \quad (V_A \Rightarrow \text{Early Voltage})$$

Hence

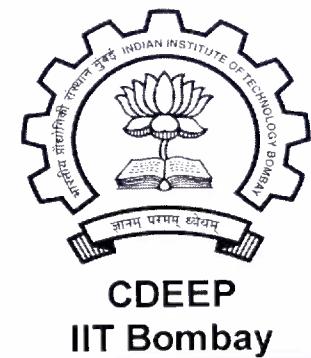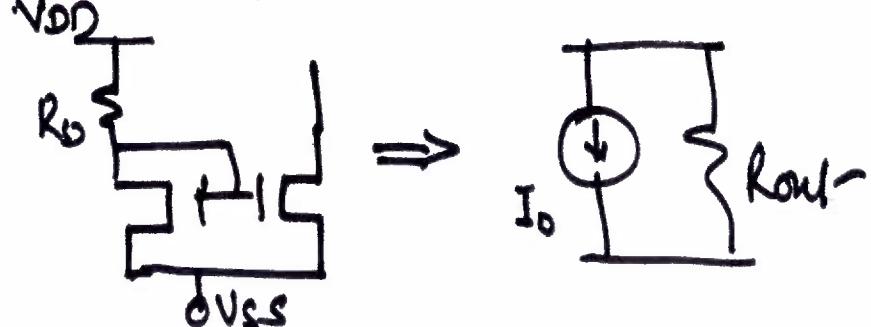

We take $V_{OV} = 200 \text{ mV}$, $V_T = 0.6 \text{ V}$, $\lambda = 0.06$

$$V_{DD} = 1.5 \text{ V} = -V_{SS}, I_{DS1} = 10 \mu\text{A}$$

$$\text{Then } V_{GS1} = 0.6 + 0.2 = 0.8 \text{ V} = V_{GS2}$$

$$R = \frac{3 - 0.8}{I_{DS1}} = \frac{2.2}{10 \mu\text{A}} = 220 \text{ k}\Omega$$

$$\text{Now } I_0 = 10 \mu\text{A} = \frac{\beta'}{2} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_T)^2$$


$$10^5 = \frac{110 \times 10^6}{2} \left(\frac{W}{L}\right)_2 (0.8 - 0.6)^2 = 11 \times 10^6 \left(\frac{W}{L}\right)_2 \times 0.2$$



$$\frac{10}{2.2} = \left(\frac{W}{L}\right)_2 \approx \left(\frac{W}{L}\right)_2 = \frac{50}{\pi} = 4.54 \approx 5 \mu\text{m}/\mu\text{m}$$

$$R_{out} = \frac{1}{\lambda I_0} = \frac{1}{0.06 \times 10^5} = 1.666 \text{ M}\Omega$$

$$\text{If } L = 0.25 \mu\text{m} \text{ then } W = 1.135 \mu\text{m} \cong 1.25 \mu\text{m}$$
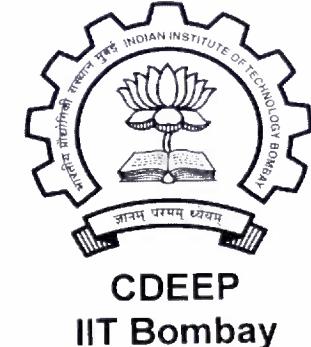
$$\text{Now } V_{DS2} \geq V_{GS2} - V_T \text{ for Saturation. Here } V_{DS2} \geq 200 \text{ mV}$$



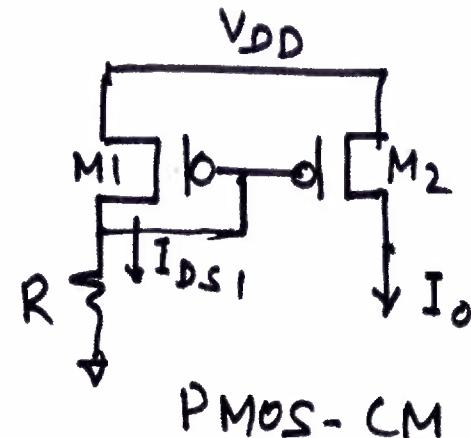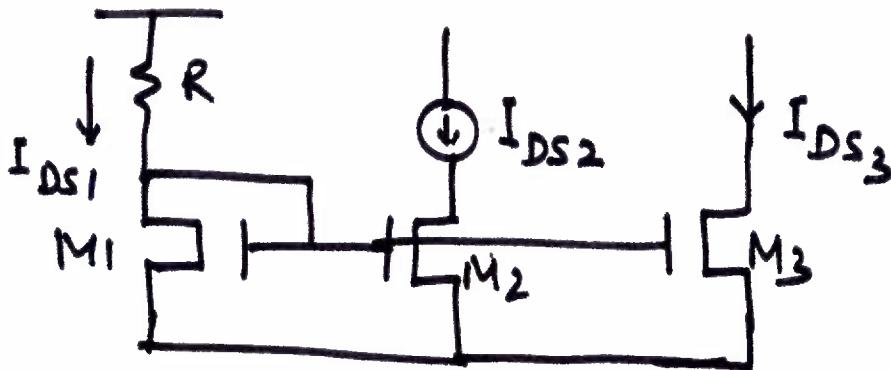

CDEEP
IIT Bombay


EE 618 L 13 / Slide 7

If $\frac{w_1}{L_1} = 10$, $\frac{w_2}{L_2} = 20$ and $\frac{w_3}{L_3} = 40$, then

$$\frac{I_{DS2}}{I_{DS1}} = \frac{20}{10} = 2 \quad \text{and} \quad \frac{I_{DS3}}{I_{DS1}} = \frac{40}{10} = 4$$

If $I_{DS1} = 10 \mu\text{A}$, then $I_{DS2} = 20 \mu\text{A}$ and $I_{DS3} = 40 \mu\text{A}$

This is the principle of Current Mirror.

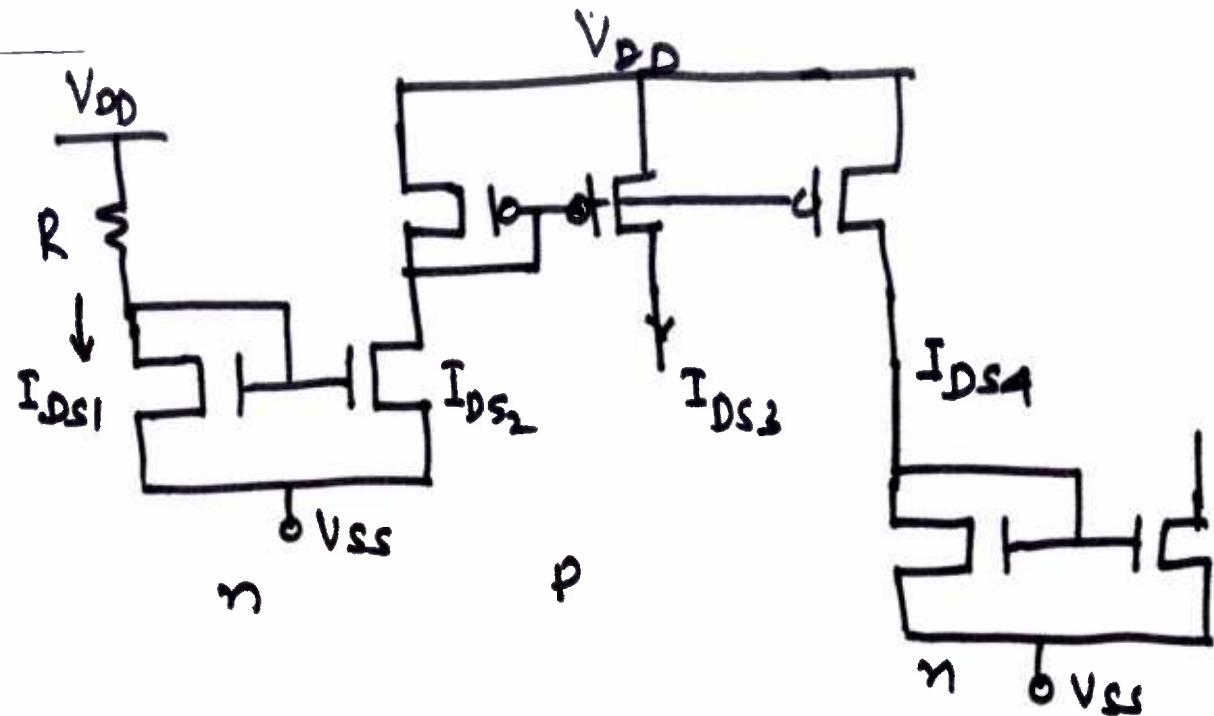

CDEEP
IIT Bombay

EE 618 L 13 / Slide 8

Typical Source/Sink Combination of Current Mirror

Matching Accuracies

M1 & M2 transistors in a Current Mirror are not identical, in some parameters due to Process Variabilities.


We have $V_{GS1} = V_{GS2} = V_{GS}$

Define $\Delta V_T = V_{T2} - V_{T1}$

$$\Delta \beta' = \beta'_2 - \beta'_1$$

Let us assume V_T variation is $\pm \Delta V_T / 2$ and
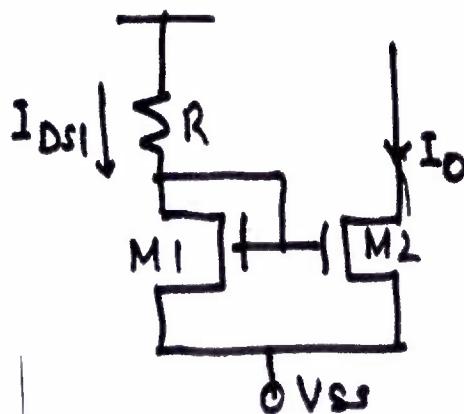
$$\beta' \text{ variation is } \pm \frac{\Delta \beta'}{2}$$



Then

$$\beta'_1 = \beta' - \Delta\beta'/2$$

$$\beta'_2 = \beta' + \Delta\beta'/2$$

$$V_{T1} = V_T - \frac{\Delta V_T}{2}$$

$$V_{T2} = V_T + \frac{\Delta V_T}{2}$$

$$\lambda_1 = \lambda - \frac{\Delta\lambda}{2}$$

$$\lambda_2 = \lambda + \frac{\Delta\lambda}{2}$$

Hence

$$\begin{aligned} \frac{I_o}{I_{DS1}} &= \frac{(\beta' + \Delta\beta'/2)(V_{GS} - V_T - 0.5\Delta V_T)^2 [1 + \lambda V_{DS} + \frac{\Delta\lambda}{2} V_{DS}]}{(\beta' - \Delta\beta'/2)(V_{GS} - V_T + 0.5\Delta V_T)^2 [1 + \lambda V_{DS} - \frac{\Delta\lambda}{2} V_{DS}]} \\ &= \frac{\beta' \left\{ 2(V_{GS} - V_T)^2 \right\} \left\{ 1 + \lambda V_{DS} \right\} \left(1 + \frac{\Delta\beta'}{2\beta'} \right) \left(1 - \frac{\Delta V_T}{1(V_{GS} - V_T)} \right)^2 \left(\frac{1 + \Delta\lambda V_{DS}}{1 + \lambda V_{DS}} \right)}{\beta' \left\{ 2(V_{GS} - V_T)^2 \right\} \left\{ 1 + \lambda V_{DS} \right\} \left(1 - \frac{\Delta\beta'}{2\beta'} \right) \left(1 + \frac{\Delta V_T}{1(V_{GS} - V_T)} \right)^2 \left(\frac{1 - \Delta\lambda V_{DS}}{1 + \lambda V_{DS}} \right)} \end{aligned}$$



CDEEP
IIT Bombay

EE 618 L 13 / Slide 10



CDEEP
IIT Bombay

$$\gamma = \frac{\left(1 + \frac{\Delta\beta'}{2\beta'}\right)\left(1 - \frac{\Delta V_T}{4(V_{GS} - V_T)}\right)^2\left(1 + \frac{\Delta\lambda V_{DS}}{1 + \lambda V_{DS}}\right)}{\left(1 - \frac{\Delta\beta'}{2\beta'}\right)\left(1 + \frac{\Delta V_T}{4(V_{GS} - V_T)}\right)^2\left(1 - \frac{\Delta\lambda V_{DS}}{1 + \lambda V_{DS}}\right)}$$

We know

$$\left(1 - \frac{\Delta x}{x}\right)^{-1} = 1 + \frac{\Delta x}{x} \quad \text{if } \Delta x \ll x$$

Then

$$\begin{aligned} \frac{I_0}{I_{DS1}} &= \left(1 + \frac{\Delta\beta'}{2\beta'}\right)^2 \left[1 - \frac{\Delta V_T}{4(V_{GS} - V_T)}\right]^4 \left[1 + \frac{\Delta\lambda V_{DS}}{1 + \lambda V_{DS}}\right]^2 \\ &= \left[1 + \frac{\Delta\beta'^2}{4\beta'^2} + \frac{\Delta\beta'}{\beta'}\right] \left[1 + \frac{\Delta V_T^2}{4(V_{GS} - V_T)^2} - \frac{\Delta V_T}{4(V_{GS} - V_T)}\right]^2 \left[1 + \frac{\Delta\lambda^2 V_{DS}^2}{(1 + \lambda V_{DS})^2}\right. \\ &\quad \left. + \frac{2\Delta\lambda V_{DS}}{1 + \lambda V_{DS}}\right] \end{aligned}$$

Since Δ terms are small, hence Δ^2 terms are even smaller & hence neglected

$$\frac{I_0}{I_{DS1}} = \left(1 + \frac{\Delta\beta'}{\beta'}\right) \left(1 - \frac{\Delta V_T}{2(V_{GS} - V_T)}\right)^2 \left(1 + \frac{2\Delta\lambda V_{DS}}{1 + \lambda V_{DS}}\right)$$

$$= \left(1 + \frac{\Delta\beta'}{\beta'}\right) \left[1 - \frac{2\Delta V_T}{2(V_{GS} - V_T)}\right] \left(1 + \frac{2\Delta\lambda}{\lambda}\right)$$

$$= 1 + \frac{\Delta\beta'}{\beta'} - \left(1 + \frac{\Delta\beta'}{\beta'}\right) \left(\frac{\Delta V_T}{V_{GS} - V_T}\right)$$

$$= 1 + \frac{\Delta\beta'}{\beta'} - \frac{2\Delta V_T}{(V_{GS} - V_T)} - \frac{\Delta\beta'}{\beta'} \frac{2\Delta V_T}{V_{GS} - V_T}$$

$$= 1 + \frac{\Delta\beta'}{\beta'} - \frac{2\Delta V_T}{V_T} \cdot \frac{1}{\left(\frac{V_{GS}}{V_T} - 1\right)} - \frac{\Delta\beta'}{\beta'} \cdot \frac{2\Delta V_T}{V_T} \cdot \frac{1}{\left(\frac{V_{GS}}{V_T} - 1\right)}$$

Typically $\frac{I_0}{I_{DS1}} = 1 \pm 0.04$ i.e. 4% error if $\Delta f = \pm 5\%$.



CDEEP
IIT Bombay

EE 618 L 13 / Slide n

We take
 $1 + \frac{2\Delta\lambda}{\lambda} \approx 1$