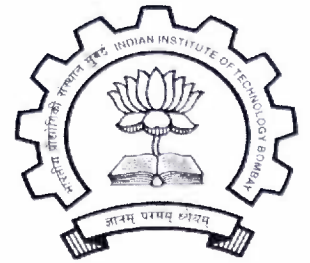


Frequency Response of Amplifiers



CDEEP
IIT Bombay

Concepts of Poles & Zeros.

A Transfer Fⁿ $A_v(s) = A_{vo} \cdot \frac{(s/\omega_z + 1)}{(\frac{s}{\omega_1} + 1)(\frac{s}{\omega_2} + 1)}$

EE 618 L 16 / Slide

ω_z is called 'zero' frequency at which $A_v(s) \rightarrow \infty$

ω_1, ω_2 - - are Poles (Pole frequencies) at which $A_v(s) \rightarrow 0$

In a typical MOS Amplifier we have around
Two 'Poles' and one 'zero'

Two Poles occur from Input Side & Output side

These can be termed as ω_{in} and ω_{out}

And ω_z is a 'zero' frequency occurring due to
Feedback.

Ref. : Sedra, Smith & Chandorkar

Page 34 / 35



CDEEP
IIT Bombay

SINGLE POLE TRANSFER FUNCTION

EE 618 L 16 / Slide

34 CHAPTER 1 INTRODUCTION TO ELECTRONICS

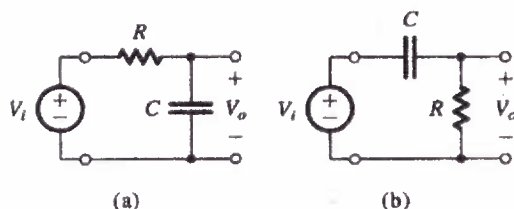


FIGURE 1.22 Two examples of STC networks: (a) a low-pass network and (b) a high-pass network.

TABLE 1.2 Frequency Response of STC Networks

	Low-Pass (LP)	High-Pass (HP)
Transfer Function $T(s)$	$\frac{K}{1 + (s/\omega_0)}$	$\frac{Ks}{s + \omega_0}$
Transfer Function (for physical frequencies) $T(j\omega)$	$\frac{K}{1 + j(\omega/\omega_0)}$	$\frac{K}{1 - j(\omega_0/\omega)}$
Magnitude Response $ T(j\omega) $	$\frac{ K }{\sqrt{1 + (\omega/\omega_0)^2}}$	$\frac{ K }{\sqrt{1 + (\omega_0/\omega)^2}}$
Phase Response $\angle T(j\omega)$	$-\tan^{-1}(\omega/\omega_0)$	$\tan^{-1}(\omega_0/\omega)$
Transmission at $\omega = 0$ (dc)	K	0
Transmission at $\omega = \infty$	0	K
3-dB Frequency	$\omega_0 = 1/\tau$; τ = time constant $\tau = CR$ or L/R	
Bode Plots	in Fig. 1.23	in Fig. 1.24

BODE PLOTS of STC

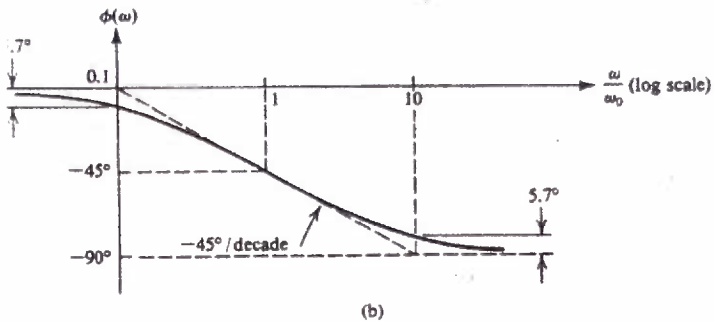
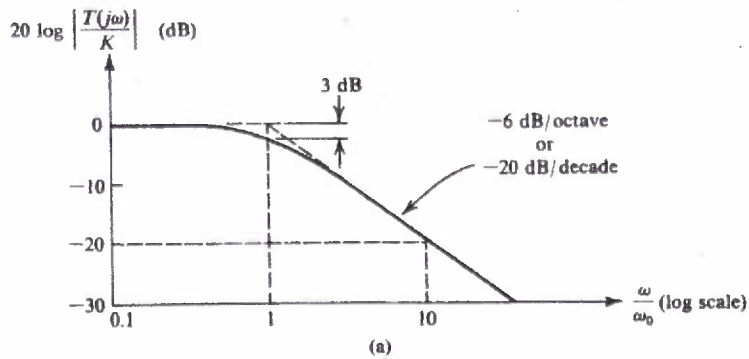


FIGURE 1.23 (a) Magnitude and (b) phase response of STC networks of the low-pass type.


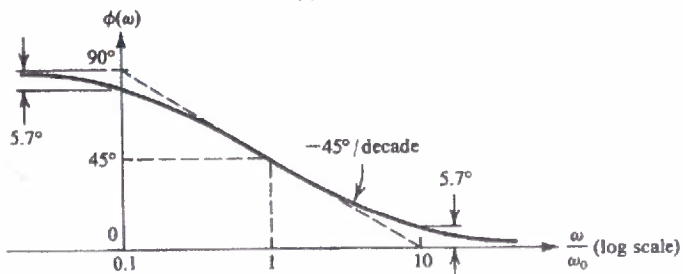


FIGURE 1.24 (a) Magnitude and (b) phase response of STC networks of the high-pass type.

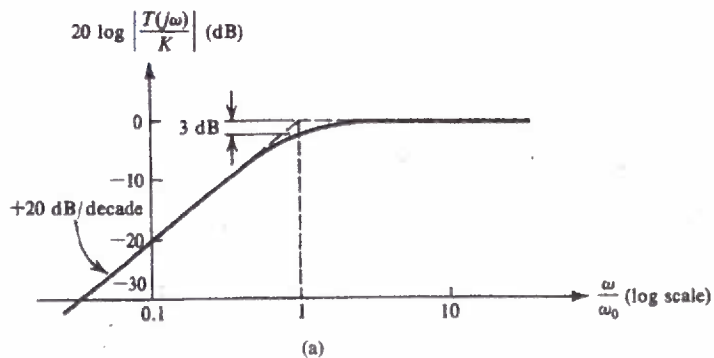

CDEEP
IIT Bombay


EE 618 L 16 / Slide




CDEEP
IIT Bombay

EE 618 L 16 / Slide


Input pole & Output Pole

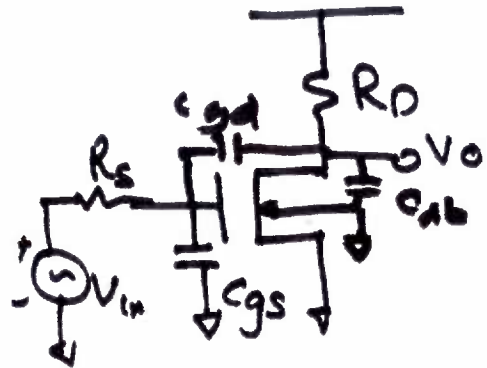

$$\omega_{in} = \frac{1}{R_S C_{gs}}$$

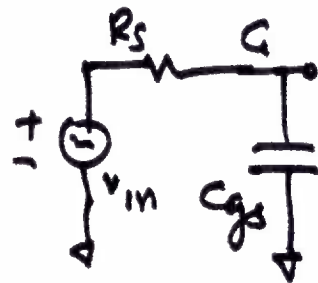

Input

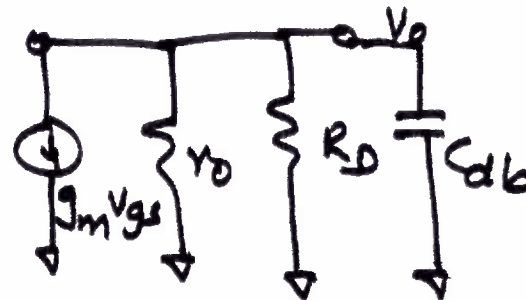


Output

$$r_o \parallel R_D \approx R_D$$

$$\omega_{out} = \frac{1}{R_D C_{db}}$$

However in equivalent ckt of Amplifier we also have capacitance C_{gd}

Then E_s Ckt looks like

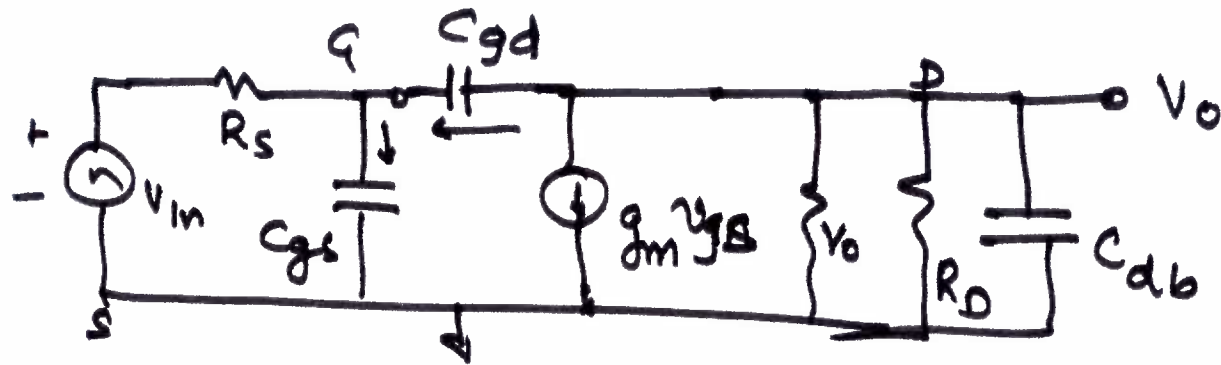

$$v_{gs} = \frac{\frac{1}{C_{gs} \cdot s}}{\frac{1}{s C_{gs}} + R_s} V_{in} = \frac{V_{in}}{1 + s \cdot R_s C_{gs}}$$

C_{gs} may include C_{gb} as it may occur in saturation.

$$\text{Then } A'_v(s) = \frac{V_o(s)}{V_{gs}(s)} = - \left\{ g_m R_D \right\} \left\{ \frac{1 - \frac{C_{gd} \cdot s}{g_m}}{1 + s \cdot C_{gd} \cdot R_D} \right\}$$

$$A_v(s) = \frac{V_o(s)}{V_{in}(s)} = - (g_m R_D) \frac{(1 - s \cdot C_{gd} / g_m)}{(1 + s R_s C_{gs})(1 + s \cdot R_D C_{gd})}$$



CDEEP
IIT Bombay

Assume EE 618 L 16 / Slide

roll $R_D = R_D$

Also C_{db} effect is neglected

Approximately looking at denominator we see

$$D = g_m (1 + s R_s C_{gs}) (1 + s R_D C_{gd})$$

$$\approx (1 + s R_s C_{gs}) (g_m + s \cdot g_m R_D C_{gd})$$

$$= (1 + s R_s C_{gs}) (g_m + (-A_{vo}) s \cdot C_{gd})$$

$$\approx 1 + s \{ C_{gs} + (1 + A_{vo}) C_{gd} \} R_s$$

$$= 1 + R_s (C_{gs} + (1 + g_m R_D) C_{gd}) \cdot s$$

$$= 1 + R_s C_{in} \cdot s$$

$$C_{in} = C_{gs} + (1 + g_m R_D) C_{gd}$$

$$\therefore \omega_{in} = \frac{1}{R_s C_{in}}$$




CDEEP
IIT Bombay

EE 618 L 16 / Slide

Similar Result we can attain by using
Miller's Theorem:

Given

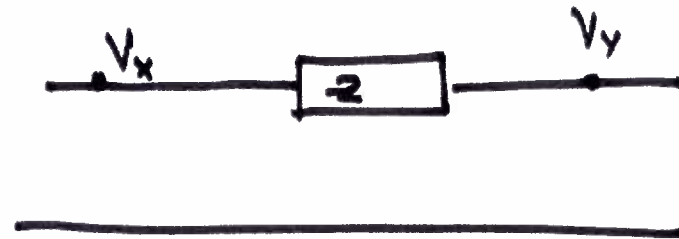

where

$$A = \frac{V_y}{V_x} \quad (\text{Gain F}^n)$$


EE 618 L 16 / Slide _____

We can convert this to

where

$$z_1 = \frac{z}{1-A}$$

$$\& \quad z_2 = \frac{A}{1-A} \cdot z$$

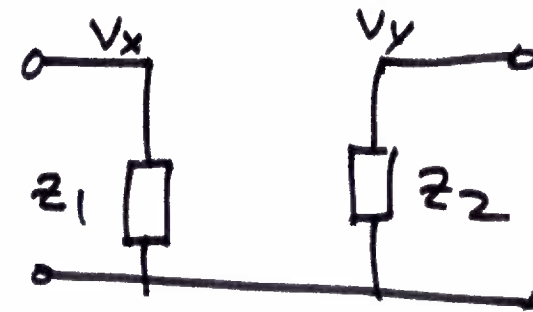

If z is capacitive C_{xy}




CDEEP
IIT Bombay




CDEEP
IIT Bombay

EE 618 L 16 / Slide

Limitations of Miller's Theorem

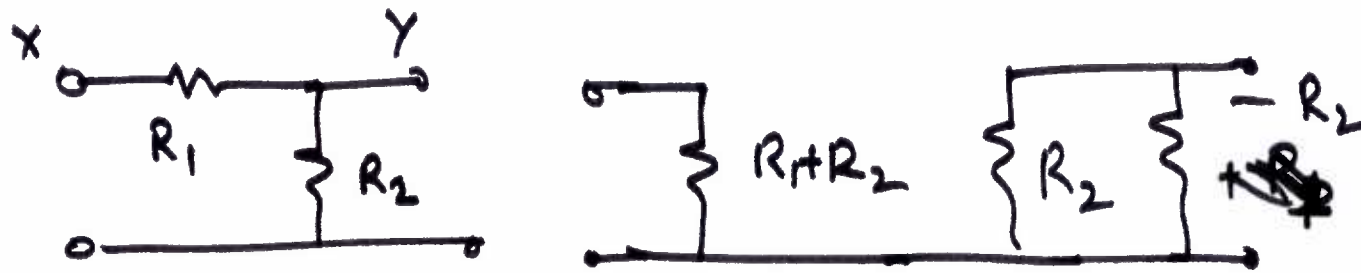

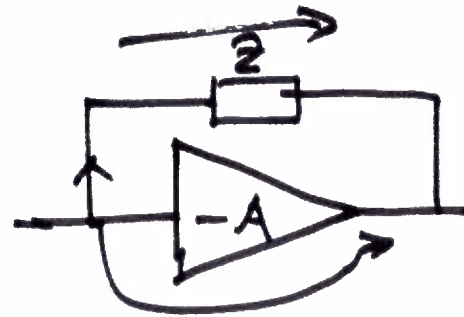We must have Two Paths from Input to Output for validity of Miller's theorem.






CDEEP
IIT Bombay

EE 618 L 16 / Slide

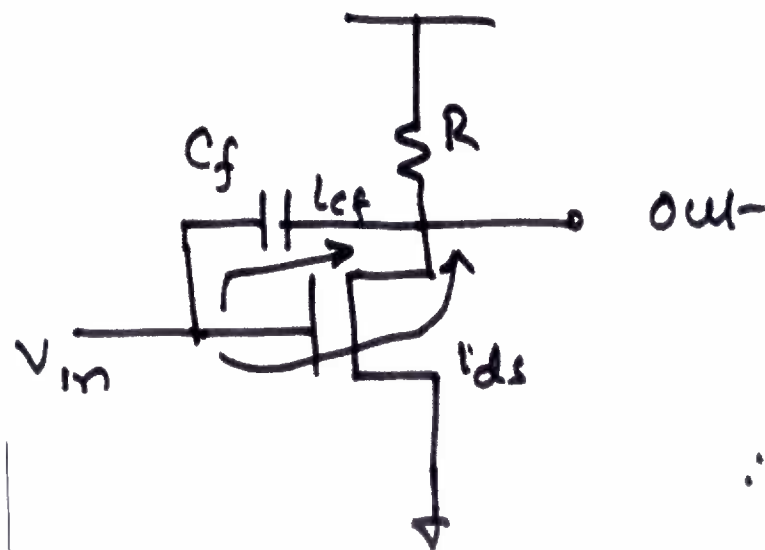Continuing similar argument, we can see that a 'zero' of Transfer Function is only possible if we have two paths from Input to Output and at a frequency the value of current in two paths are equal in magnitude and 180° out of phase.



This is due to effect of

"Feed Forward"

$$i_{Cf} = -i_{ds}$$

$\therefore i = 0 \quad \therefore V_{out} = 0 \rightarrow$ 'Zero' Occurrence





CDEEP
IIT Bombay


EE 618 L 16 / Slide

Returning to our problem of Frequency response of a CS Amplifier, whose HF

model can be shown as with ckt as —

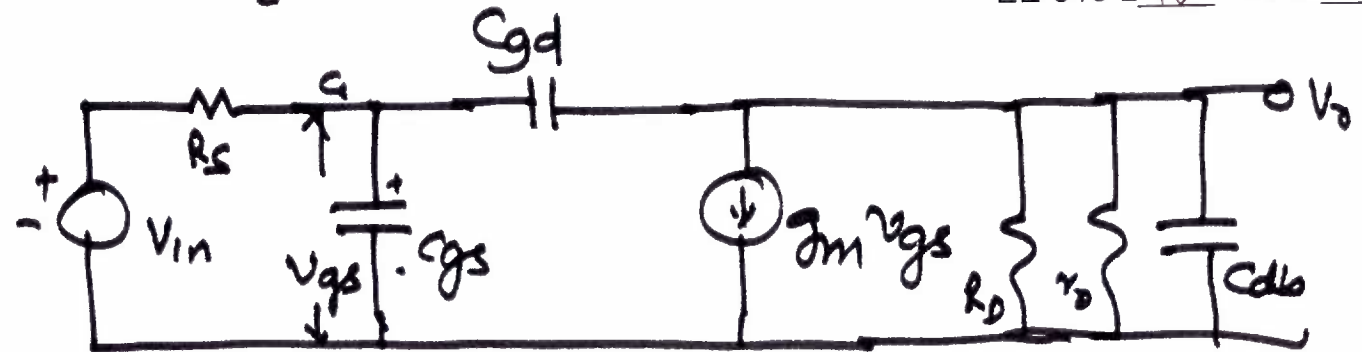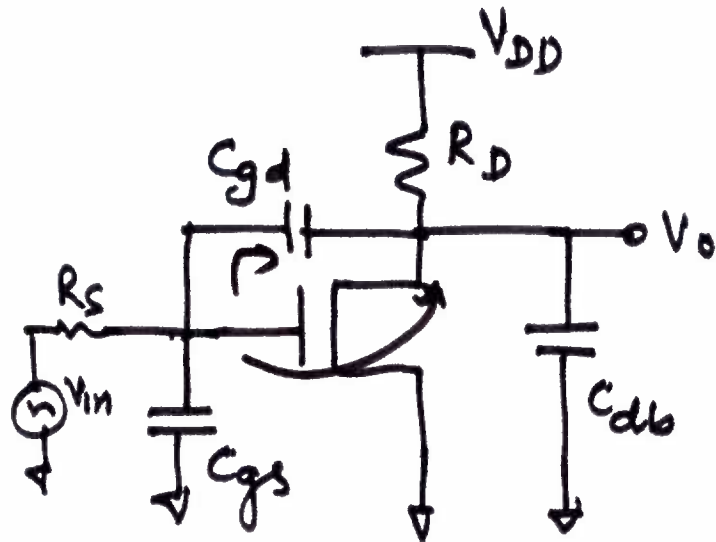

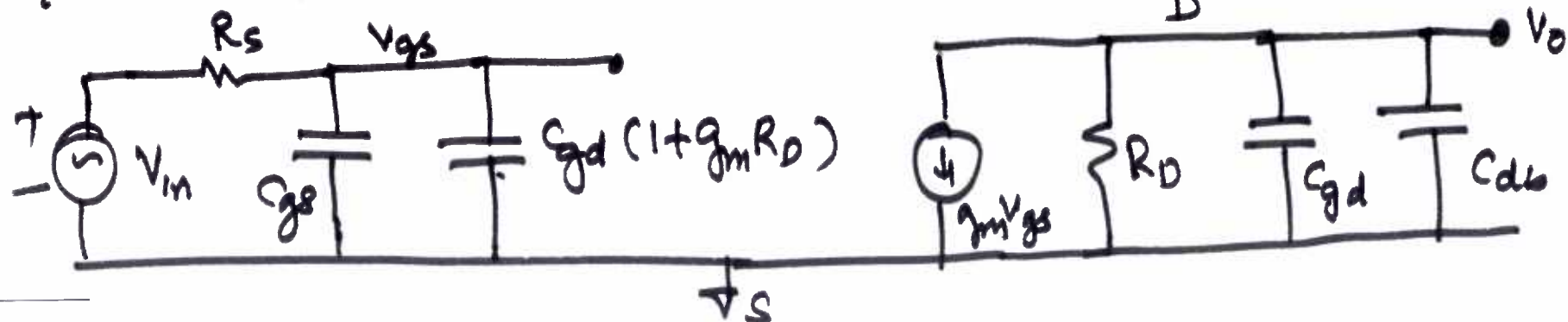Using DC Gain expression $A_{vo} = -g_m R_D$, we see that G_s ckt could be shown using Miller's theorem as:—





CDEEP
IIT Bombay

EE 618 L 16 / Slide

Then

$$\omega_{in} = \frac{1}{R_s [C_{gs} + (1 + g_m R_D) C_{gd}]}$$

$$\& \omega_{out} = \frac{1}{R_D (C_{gd} + C_{db})}$$

And Transfer F^n can be written as

$$A_v(s) = \frac{A_{vo}}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}, \quad A_{vo} = -g_m R_D$$

If we solve complete eq. circuit with node analysis, we get



CDEEP
IIT Bombay

EE 618 L 16 / Slide

$$A_v(s) = - \frac{g_m R_D - C_{gd} \cdot s}{1 + R_S \cdot R_D \cdot C_{cs} \cdot s^2 + [R_S \{1 + g_m R_D\} C_{gd} + R_S C_{gs} + R_D \{C_{gd} + C_{db}\}] s}$$

This leads to

$$\omega_{p1} = \frac{1}{R_S (1 + g_m R_D) C_{gd} + R_S C_{gs} + R_D (C_{gd} + C_{db})}$$

$$\omega_{p2} = \frac{1}{\omega_{p1} \cdot R_S R_D (C_{gs} C_{gd} + C_{gs} C_{db} + C_{gd} C_{db})}$$

$$C_{eq} = (C_{gs} C_{gd} + C_{gs} C_{db} + C_{gd} C_{db})$$

$$\text{If } R_D (C_{gd} + C_{db}) \ll R_S C_{gs} + R_S (1 + g_m R_D) C_{gd}$$

$$\text{and } C_{gs} \gg (1 + g_m R_D) C_{gd} + \frac{R_D}{R_S} (C_{gd} + C_{db})$$



CDEEP
IIT Bombay

EE 618 L 16 / Slide

$$\text{Then } \omega_{p1} = \frac{1}{R_S [C_{gs} + (1 + g_m R_D) C_{gd}]}$$

$$\& \omega_{p2} = \frac{1}{R_D (C_{gd} + C_{db})}$$

If we see values of ω_{in} & ω_{out} as obtained by Miller's theorem use, we observe that

$$\omega_m = \omega_{p1} \quad \& \quad \omega_{out} = \omega_{p2}$$



CDEEP
IIT Bombay

EE 618 L 16 / Slide

Hence in most cases we can find Dominant Pole, Non Dominant poles and even zeros using simple evaluations of ω_{in} and ω_{out} , which essentially are inversely related to Input Time constant $R_{in}C_{in}$ and $R_{out}C_{out}$, being output Time constant.


This suggests a simple Technique of evaluation of Poles using a technique called "Zero-Value Time Constant" analysis. This is also at times referred as "Open Circuit Time Constant analysis".



CDEEP
IIT Bombay

EE 618 L 16 / Slide

Step 2 :

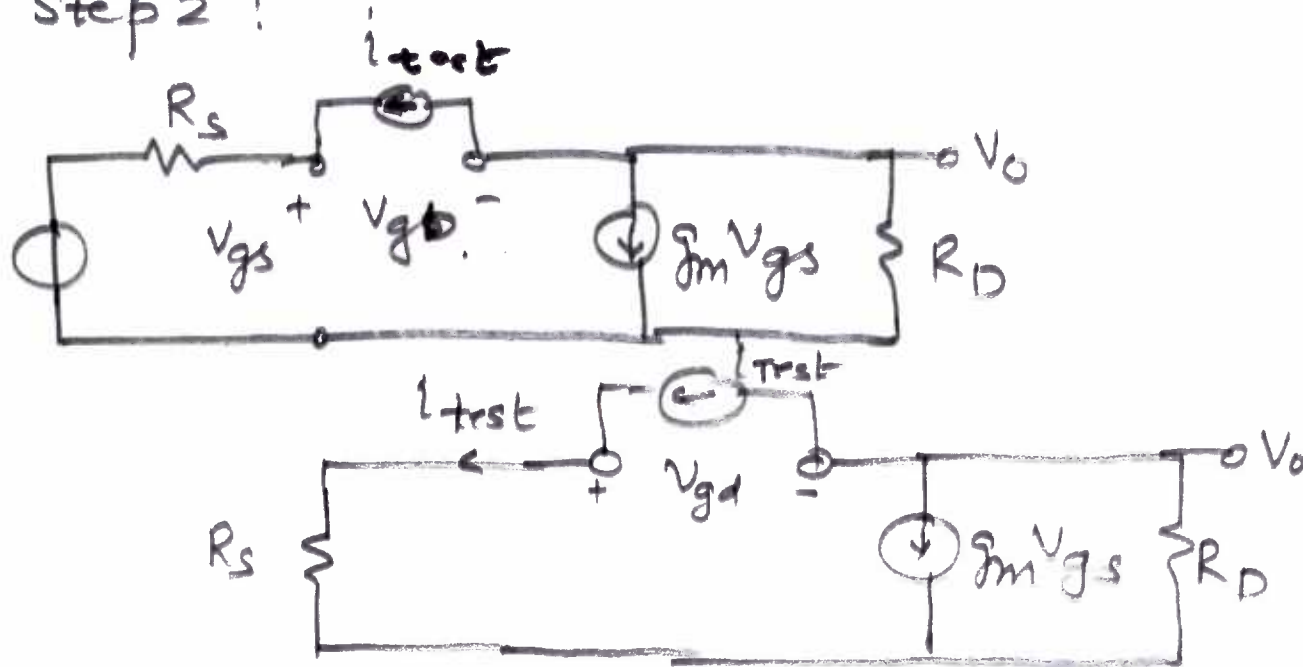

$$R_{cgd} = \frac{V_{gd}}{i_{test}} = \frac{i_{test} \cdot R_s + R_D (g_m V_{gs} + i_{test})}{i_{test}}$$

$$R_{cgd} = R_s + \frac{g_m R_D i_{test} \cdot R_s}{i_{test}} + R_D$$

$$R_{cgd} = R_s + R_D + g_m R_s R_D$$

ZVTC Technique :



CDEEP
IIT Bombay

EE 618 L 16 / Slide

1. Remove all but One Capacitor.
Short all independent Voltage Sources,
open all independent Current Sources.
2. Calculate resistance $^{(R_1)}$ seen by capacitor (C_1)
and then evaluate Time constant $\tau_1 = R_1 C_1$.
3. Repeat this for all Capacitors and obtain
 $\tau_j = R_j C_j$
4. Sum all the Time-Constants and then we

get $\omega_{-3db} = \frac{1}{\sum_{j=0}^N \tau_j}$

N is no. of Capacitors

'ZVTC and SCTC Techniques' — Limitations & Comments —



CDEEP
IIT Bombay

EE 618 L 16 / Slide


1. These do not lead to finding 'zeros' of the systems

2. It is accurate enough if there exists a Dominant pole separated by larger frequency to next Non-dominant pole.


In most Amplifiers which we use in Analog Systems, this condition is mostly met.

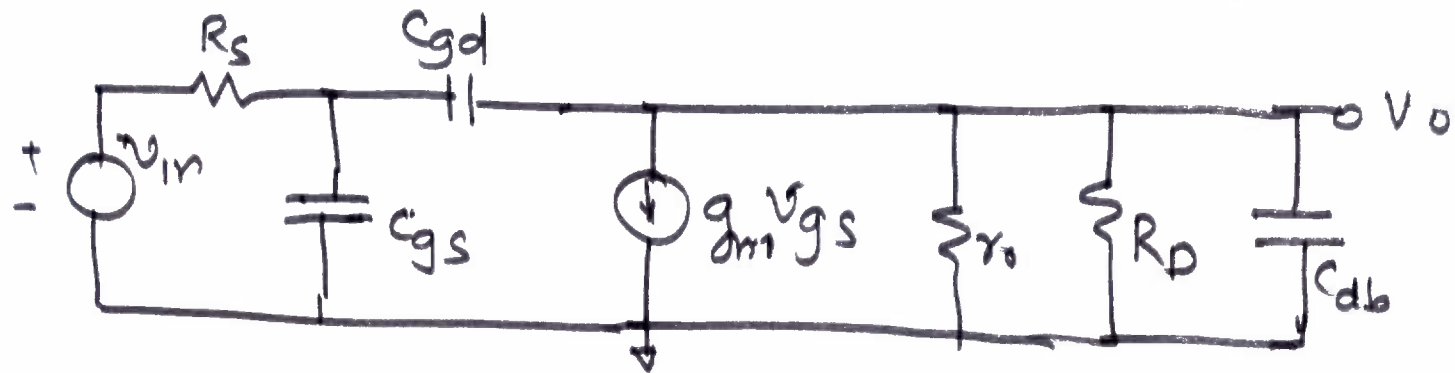3. In these techniques, remove Coupling capacitors from evaluation as they provide 'shorts' at higher frequency

For the ckt. of CS Amplifier, we obtain ω_{-3db} now using ZVTC technique.



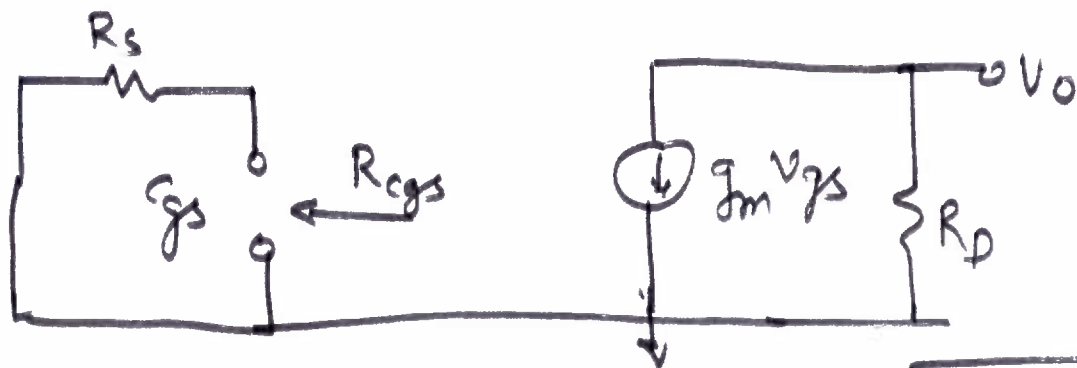Step 1: Time constant for C_{gs} . (Open C_{gd} & C_{db} arm for $C_{gd} = C_{db} = 0$)



Clearly $R_{cgs} = R_s$

$$\therefore \tau_1 = R_s C_{gs}$$

— ①



CDEEP
IIT Bombay

EE 618 L 16 / Slide



CDEEP
IIT Bombay

EE 618 L 16 / Slide

$$\therefore \omega_{-3db} = 2\pi f_{-3db}$$

$$= \frac{1}{R_s C_{gs} + R_D C_{db} + (R_s + R_D) C_{gd} + g_m R_s R_D C_{gd}}$$

Please pay attention to our earlier calculations of ω_{p1} . It seems that now we

get $\omega_{-3db} = \omega_{p1}$ This is a dominant Pole.


Hence ZVTC technique is good enough approximation to get Dominant Pole. ^{For} Nondominant pole too, we use technique called 'Short Circuit Time Constant' technique.

Example^{xx}: We continue with same amplifier design and neglect C_{db} for this example



CDEEP
IIT Bombay

EE 618 L 16 / Slide

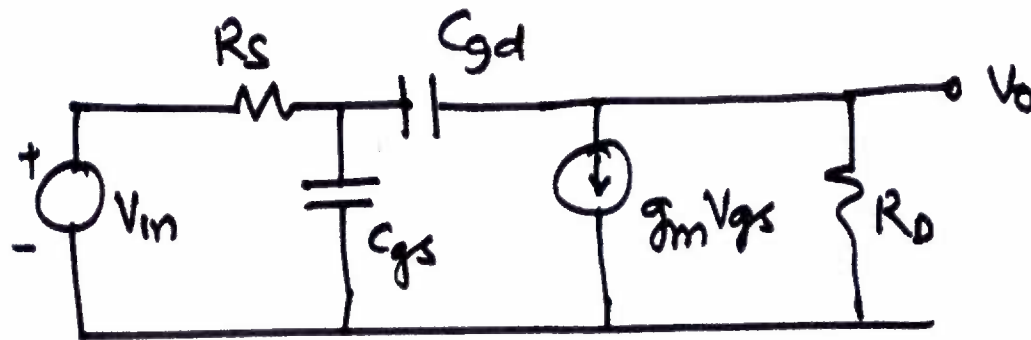

Solve for

$$\begin{cases} R_S = 10\text{K} = R_L \\ C_{gs} = 1\text{ pf} ; C_{gd} = 20\text{ pf} \\ g_m = 3\text{ mA/V} \end{cases}$$

We have Two capacitors in the circuit, and hence we have TWO poles, & one of them will be Dominant Pole and other Nondominant pole.

- (i) We use ZVTc technique to obtain Dominant Pole
- & (ii) We use 'Short Circuit Time Constant' technique to get Non Dominant Pole.

Data : $R_S = 1K$, $R_D = 5K$

$I_{D_S} = 1mA$, $\beta'(W/L) = 100 \mu A/V^2$

$C_{gd} = 0.5 pF$, $C_{gb} = 0$

$C_{gs} = 5.0 pF$

Now $g_m = \sqrt{2 \times 100 \times 10^{-3} \times 10^{-3}} = 14.1 \text{ mA/V}$

Using Miller Technique , the dominant pole is

$$\omega_{p1} = - \frac{1}{(1 + g_m R_D) R_S C_{gd} + R_S C_{gs} + R_D C_{gd}}$$

$1 + g_m R_D = 1 + 10^{-3} \times 14.1 \times 5 \times 10^3 = 71.5$

$(R_S + R_D) = 6K$; $(R_S + R_D) C_{gd} = 6 \times 10^3 \times 0.5 \times 10^{-12} = 3 \times 10^{-9}$

$R_S \cdot C_{gs} = 10^3 \times 5 \times 10^{-12} = 5 \times 10^{-9}$



CDEEP
IIT Bombay

EE 618 L 16 / Slide



CDEEP
IIT Bombay

EE 618 L 16 / Slide

$$g_m R_D = 70.5 \quad ; \quad R_S R_D = 5 \times 10^6$$

$$R_S R_D C_{gd} = 5 \times 10^6 \times 5 \times 10^{-13} = 2.5 \times 10^{-6}$$

$$\begin{aligned} g_m R_S R_D C_{gd} &= 14.1 \times 10^{-3} \times 2.5 \times 10^{-6} \\ &= 35.25 \times 10^{-9} \end{aligned}$$

$$\begin{aligned} \therefore \omega_{p1} &= \frac{1}{3 \times 10^{-9} + 5 \times 10^{-9} + 35.25 \times 10^{-9}} \\ &= \frac{10^9}{43.25 \times 10^{-9}} = 23.12 \times 10^6 \end{aligned}$$

$$\therefore f_{p1} = \frac{1}{2\pi} 23.12 \times 10^6 = 3.68 \text{ MHz}$$

$$\begin{aligned} \alpha \quad \omega_{p2} &\approx \frac{1}{R_D C_{gd}} = \frac{1}{5 \times 10^3 \times 5 \times 10^{-13}} = \frac{10^{10}}{25} = 4 \times 10^8 \\ f_{p2} &= \frac{1}{2\pi} \cdot 4 \times 10^8 = 63.6 \text{ MHz} \end{aligned}$$

We compare these values with 2VTC & SCTC ('Short Ckt Time constant') technique based evaluations of f_{p1} & f_{p2}



CDEEP
IIT Bombay

EE 618 L 16 / Slide

[1] 2 VTC technique gives Dominant Pole:

$$\text{Here } \tau_1 = R_s C_{gs} = 5 \times 10^{-9}$$

$$\begin{aligned} \tau_2 &= (R_s + R_D) C_{gd} + \tau_m R_s R_D C_{gd} \\ &= 3 \times 10^{-9} + 35.25 \times 10^{-9} \end{aligned}$$

$$\therefore \omega_{p1} = \frac{1}{\sum \tau_j} = \frac{1}{\tau_1 + \tau_2} = \frac{1}{43.25 \times 10^{-9}}$$

$$\therefore \boxed{f_{p1} = 3.68 \text{ MHz}} \quad \text{Dominant Pole}$$

[2] Short Circuit Time Const. Technique:—


This gives Non dominant Pole.



CDEEP
IIT Bombay

EE 618 L 16 / Slide

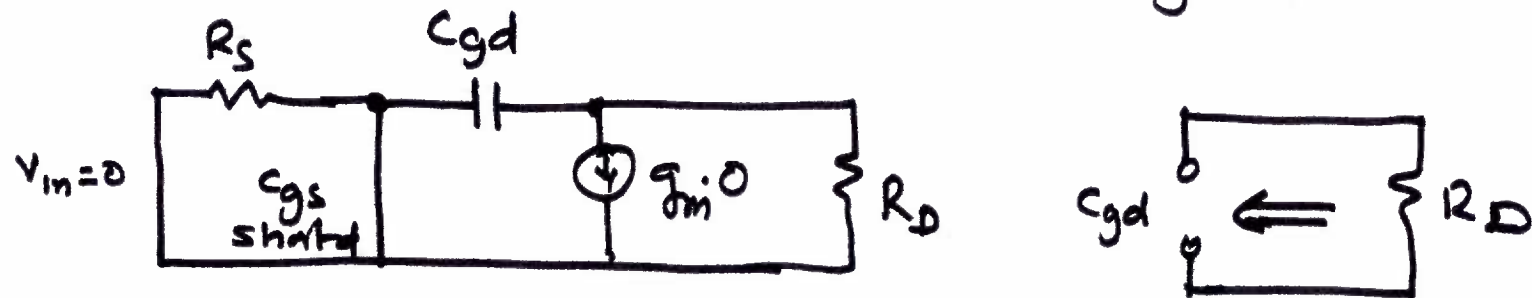(a) C_{gd} seen Resistance when C_{gs} is shorted



$$\therefore R_{cgd} = R_D$$

$$\therefore \tau_{cgd} = R_D C_{gd} = 5 \times 10^3 \times 0.5 \times 10^{-12} = 2.5 \times 10^{-9}$$

(b) C_{gs} seen Resistance when C_{gd} is shorted





CDEEP
IIT Bombay

EE 618 L 16 / Slide

$$\begin{aligned}\therefore \tau_{cgs} &= R_{cgs} \cdot C_{gs} \\ &= 65 \times 0.5 \times 10^{-12} \times 10 = 0.325 \times 10^{-9}\end{aligned}$$

$$\begin{aligned}\tau_{sc} &= 2.5 \times 10^{-9} + 0.325 \times 10^{-9} \\ &= 2.825 \times 10^{-9}\end{aligned}$$

$$\therefore \omega_{\text{non dom}} = \omega_{p2} = \frac{1}{2.825 \times 10^{-9}}$$

$$\therefore f_{p2} = \frac{10^9}{6.28 \times 2.825} = 56.3 \text{ MHz}$$

f_{p2} we obtained earlier with nodal analysis
= 63.6 MHz




CDEEP
IIT Bombay

EE 618 L 16 / Slide

$$\therefore \tau_2 = R_{cgd} \cdot C_{gd}$$

$$\therefore \tau_2 = (R_S + R_D + g_m R_S R_D) C_{gd} \quad \text{--- (2)}$$

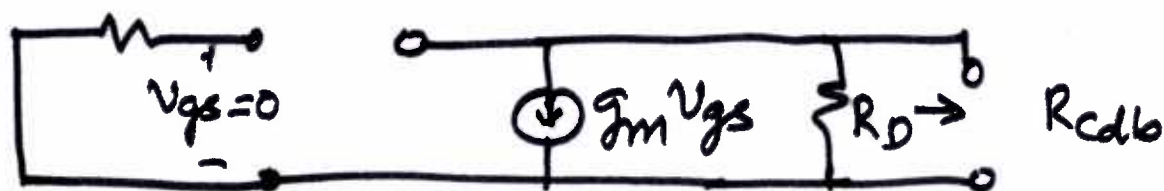Step 3 : We get Time constant as seen by C_{db}



$$\therefore R_{cdb} = R_D$$

$$\therefore \tau_3 = R_D \cdot C_{db} \quad \text{--- (3)}$$

$$\therefore \frac{1}{\tau_{-3db}} = \frac{1}{\cancel{\tau_1}} + \frac{1}{\cancel{\tau_2}} + \frac{1}{\cancel{\tau_3}} = \frac{1}{\tau_1 + \tau_2 + \tau_3}$$