


## CMOS OPAMP : Two Stage OPAMP

Typically Double-ended CMOS uses Current Source biasing, while Single-ended OPAMP uses current Mirror Biasing



CDEEP  
IIT Bombay


EE 618 L \_\_\_\_\_ / Slide \_\_\_\_\_

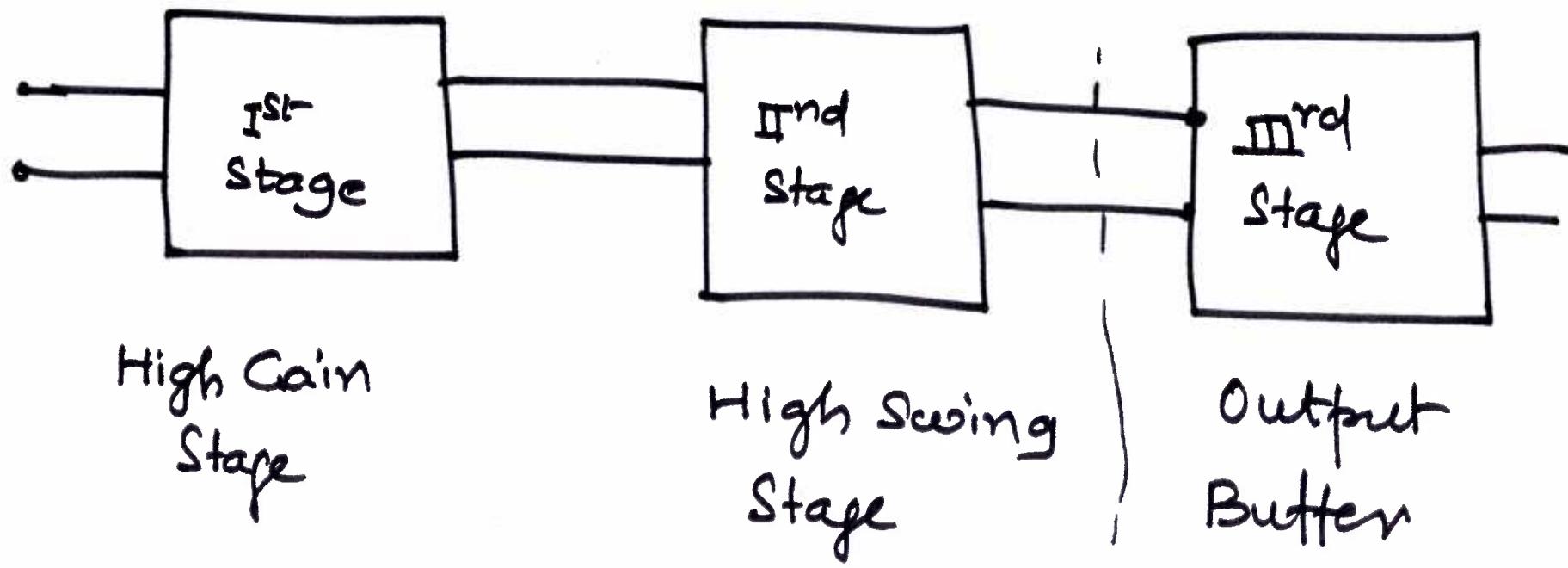


# Block Diagram of OPAMP




CDEEP  
IIT Bombay

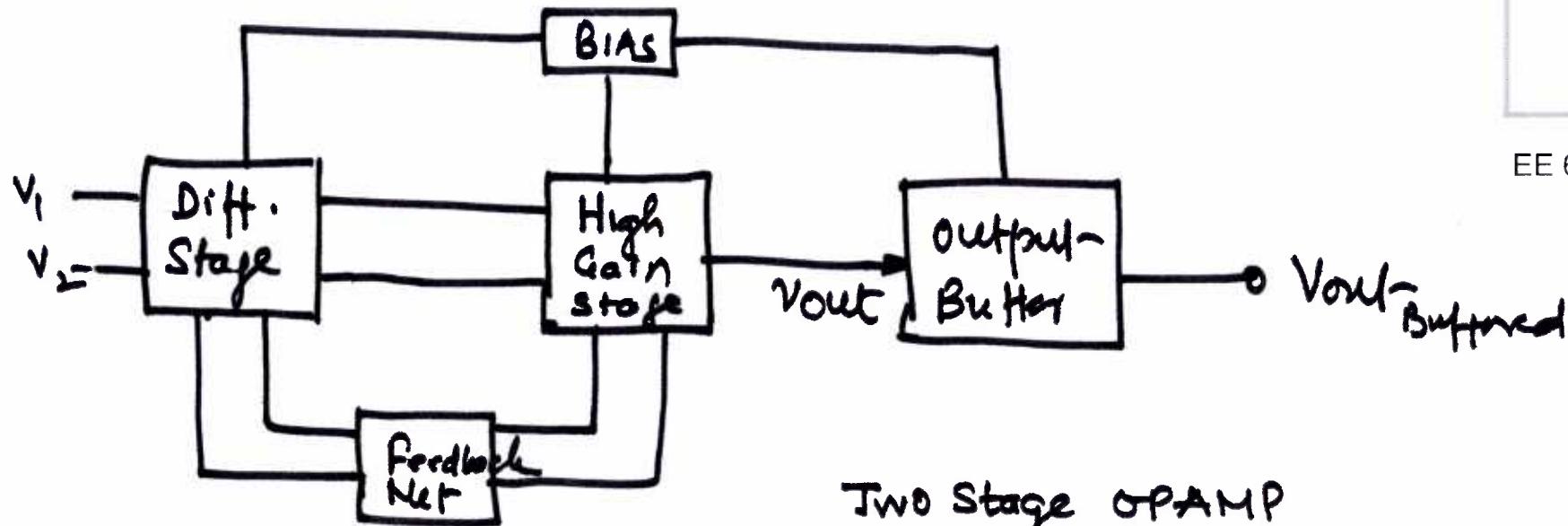


EE 618 L\_\_\_\_ / Slide \_\_\_\_

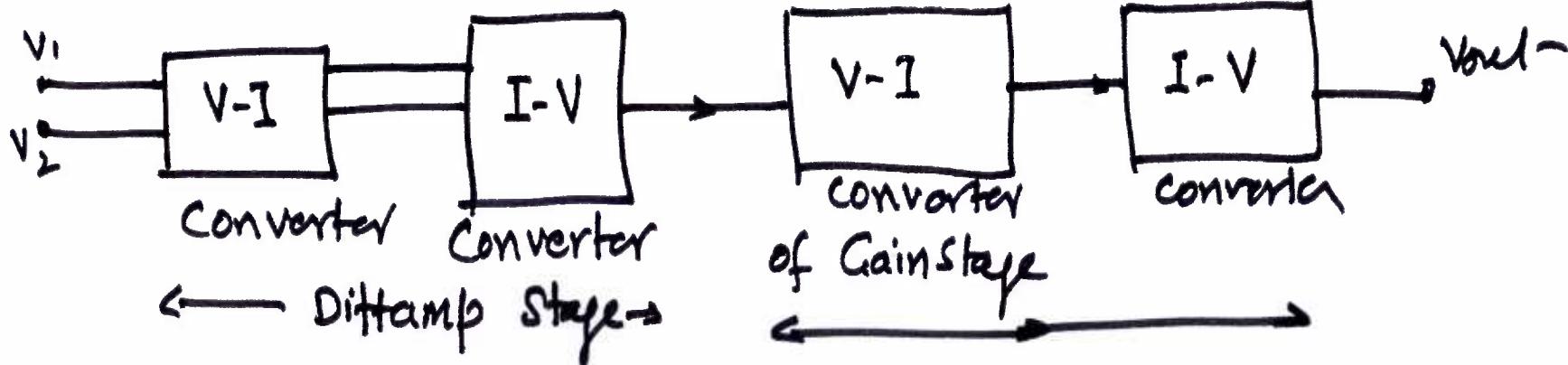

Two Stage Double-ended OPAMP

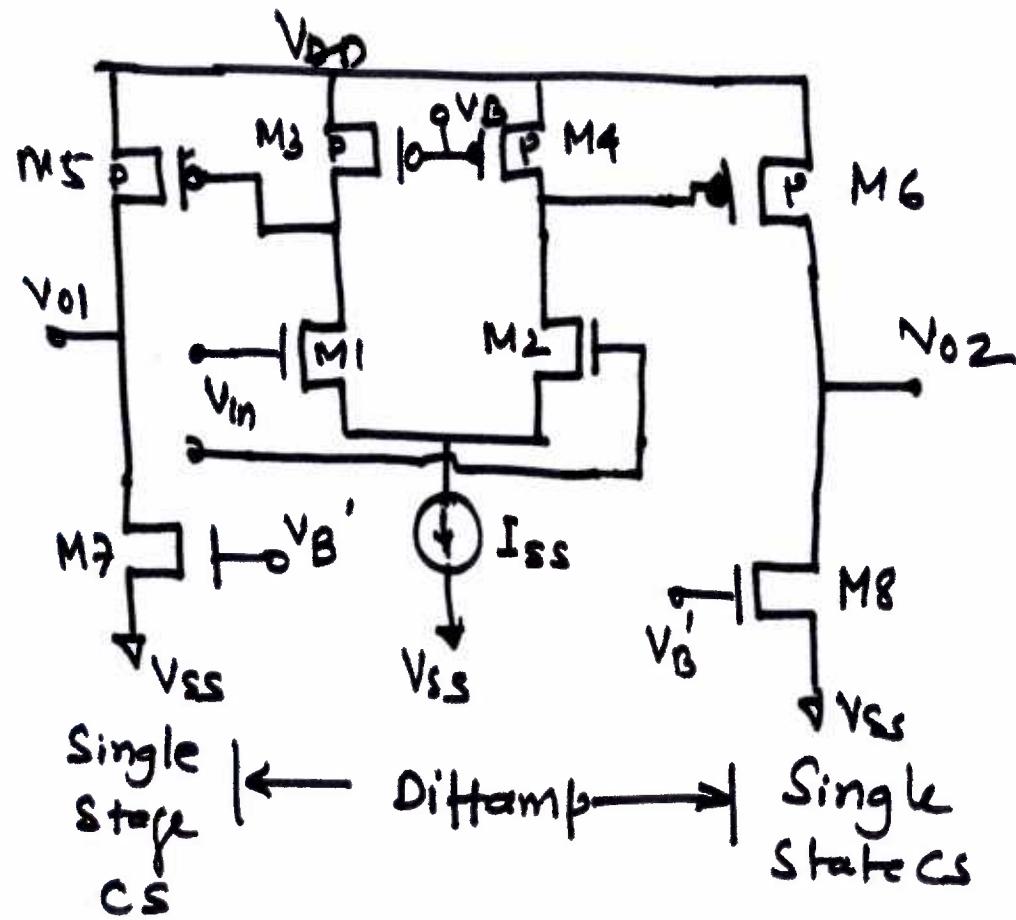

Two Stage Single-ended OPAMP

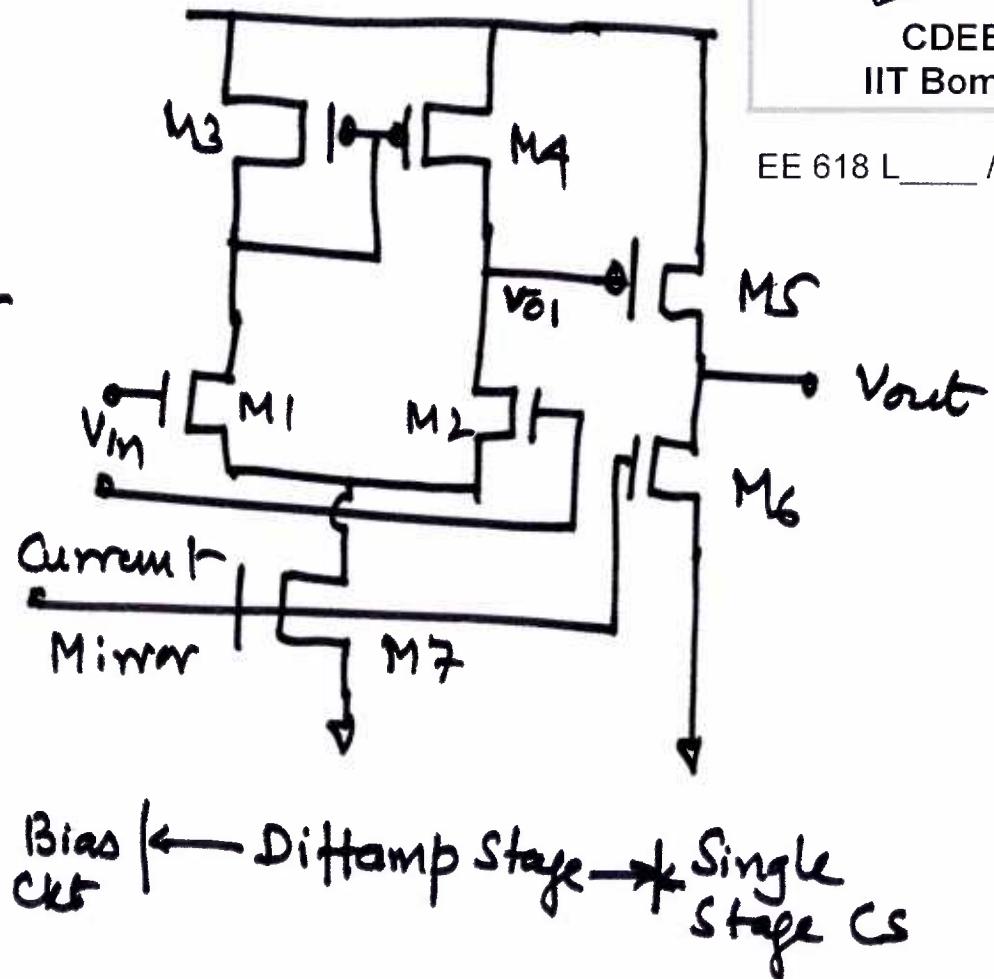

CDEEP  
IIT Bombay

EE 618 L \_\_\_ / Slide \_\_\_

For double ended case

$$V_{o1} = -g_{m1} (r_{o1} \parallel r_{o3}) V_{in}$$

$$V_{o2} = -g_{m2} (r_{o2} \parallel r_{o4}) (-V_{o1})$$

$$V_{o2} = +g_1 g_{m_5} (r_{o1} \parallel r_{o3}) (r_{o2} \parallel r_{o4}) V_m$$

$$\therefore A_{v1} = A_{v2} = \frac{V_{o1}}{V_m} = \frac{V_{o2}}{V_m} = g_{m1} g_{m_5} (r_{o5} \parallel r_{o7}) (r_{o2} \parallel r_{o4})$$

$$= g_{m2} g_{m_6} (r_{o6} \parallel r_{o8}) (r_{o2} \parallel r_{o4})$$

$$r_{o1} = \frac{1}{\lambda_1 I_{SS/2}} \text{ and } r_{o3} = \frac{1}{\lambda_3 I_{SS/2}}, \quad r_{o5} = \frac{1}{\lambda_5 I_{DS/2}}$$

$$r_{o2} = \frac{1}{\lambda_2 I_{SS/2}}, \quad r_{o4} = \frac{1}{\lambda_4 I_{SS/2}}; \quad r_{o6} = \frac{1}{\lambda_6 I_{DS/2}}$$



CDEEP  
IIT Bombay

EE 618 L\_\_\_\_\_ / Slide\_\_\_\_\_

Here for Single ended case

$$A_V = A_{V1} \cdot A_{V2}$$

$$A_{V1} = \frac{V_{O1}}{V_{In}} = -g_{m1} \cdot (\gamma_{o2} || \gamma_{o4})$$


However  $V_{O1} = V_{In2}$  for CS Amplifier

$$\therefore A_{V2} = \frac{V_{Out}}{V_{O1}} = -g_{m5} \cdot (\gamma_{o5} || \gamma_{o6})$$

$$\therefore A_V = +g_{m1} g_{m5} (\gamma_{o2} || \gamma_{o4}) (\gamma_{o5} || \gamma_{o6})$$

$$g_{m1} = \sqrt{2\beta_1 I_{DS1}} = \sqrt{2\beta_2 I_{DS2}} = g_{m2}$$
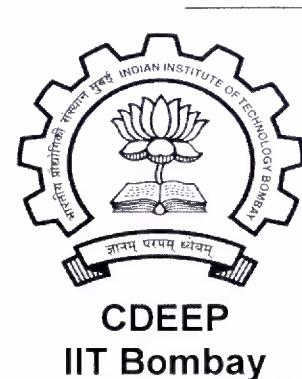
$$I_{DS1} = I_{DS2} = \frac{I_{SS}}{2} \quad \therefore g_{m1} = \sqrt{\beta_1 I_{SS}} = g_{m2}$$



If Bias current is chosen as  $20 \mu\text{A}$

$$\therefore I_{SS} = 20 \mu\text{A}, \therefore \frac{I_{SS}}{2} = 10 \mu\text{A}.$$

$$\therefore I_{DS1} = I_{DS3} = I_{DS2} = I_{DS4} = 10 \mu\text{A} \text{ (at } V_D = 0)$$



CDEEP  
IIT Bombay

EE 618 L\_\_\_ / Slide \_\_\_

$$\therefore g_m = \sqrt{2B_1 I_{SS}/2}$$

We choose Technology of  $5 \mu\text{m}$ .

$$B_m^1 = 50 \mu\text{A/V}^2 \quad \lambda_1 = \lambda_2 = 0.06$$

$$B_p^1 = 16 \mu\text{A/V}^2 \quad \lambda_3 = \lambda_4 = 0.06/\nu$$

$$\gamma_{O1} = \gamma_{O2} = \sqrt{\frac{1}{\lambda_2}}$$

$$= \frac{1}{\lambda_2 I_{SS}/2}$$

$$\gamma_{O4} = \lambda_4 I_{SS}/2 \quad \therefore$$

$$\gamma_{O2} || \gamma_{O4} = \frac{1}{(\lambda_2 + \lambda_4)} I_{SS}/2$$

$$\frac{I_{SS}}{2} = \frac{B_1}{2} \cdot (V_{GS1} - V_{TN})^2 \quad \propto \sqrt{I_{SS}} = \sqrt{\frac{B_1}{2}} (V_{GS1} - V_{TN})$$

Using Data from Boyce, Baker, Li's book,

$$\text{For } V_{OV} = 0.37 \text{ V}, V_{T_N} = 0.83 \text{ V}, V_{TP} = -0.9 \text{ V}$$

$$V_{GS1} = V_{GS2} = 0.83 + 0.37 \text{ V} = 1.2 \text{ V}$$

$$\text{For } I_{SS} = 20 \text{ mA, or } I_{DS1} = I_{DS2} = +\frac{I_{SS}}{2}$$

$$\text{we get } \left(\frac{W}{L}\right)_N = \frac{15}{5} \quad \text{and} \quad \left(\frac{W}{L}\right)_P = \frac{70}{5}$$

Thus Open Loop Gain of Two stage OPAMP can be found =  $|A_{OL}|$

$$= \sqrt{2 \times 50 \times 10^6 \left(\frac{15}{5}\right) 10 \times 10^6} \times \sqrt{2 \times 16 \times 10^6 \left(\frac{70}{5}\right) 10 \times 10^6}$$

$$\xleftarrow{\qquad g_{m1} \qquad} \rightarrow \quad \xleftarrow{\qquad g_{m2} \qquad}$$

$$* \left[ \frac{1}{(0.06 + 0.06) \times 10 \times 10^6} \right]^2$$

$$\frac{(r_{O2} || r_{O4})(r_{O5} || r_{O6})}{}$$



Then  $|A_{OL}| \approx 2500$  V/V


It is obvious from AOL expression that


$$A_{OL} \propto \frac{1}{I_{SS}}$$

Hence increase of  $I_{SS}$  may improve Bandwidth  
but decrease AOL, or Vice-a-Versa.

In real life OPAMP, one wishes to improve  
the Stability of Gain against any variations,

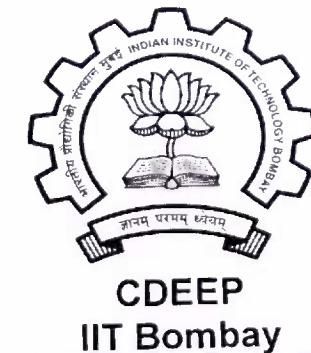So we wish to visit 'Feedback & Stability'  
issue in Brief, so that we can achieve desired  
Gain, Bandwidth and other specs, and also System is Stable.



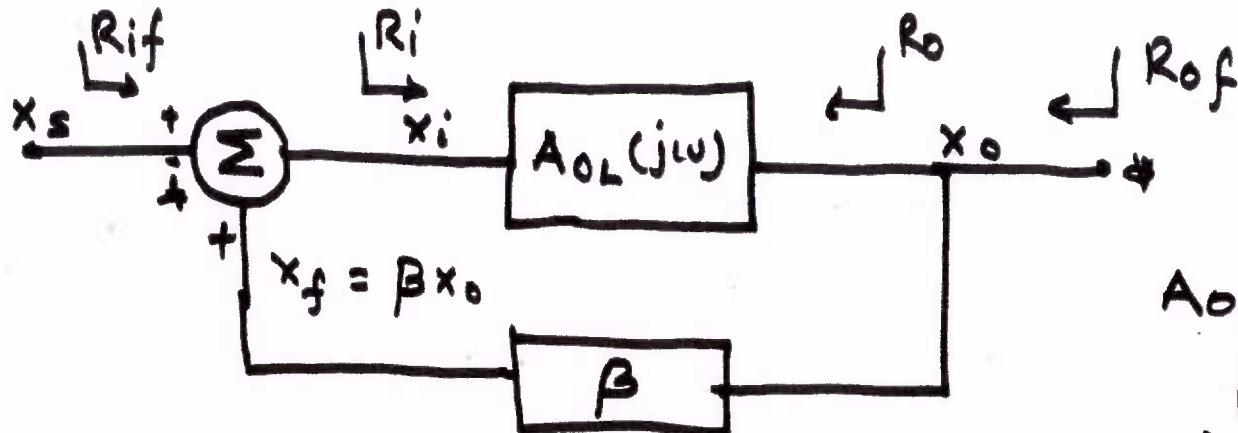FeedbackCDEEP  
IIT Bombay $A_{OL}(j\omega)$  = Open Loop Gain $\beta$  = Feedback factor $A_{CL}(j\omega)$  = Closed Loop Gain


## General Feedback System

$$x_o = A_{OL}(j\omega) \cdot x_i = A_{OL}(j\omega) [x_s - x_f]$$

Here  $x_i = x_s - x_f$  And  $x_f = \beta x_o$

$$\therefore x_o = A_{OL}x_s - A_{OL}\beta x_o \quad \therefore A_{CL}(j\omega) = \frac{x_o}{x_s} = \frac{A_{OL}}{1 + A_{OL}\beta}$$

## Definitions

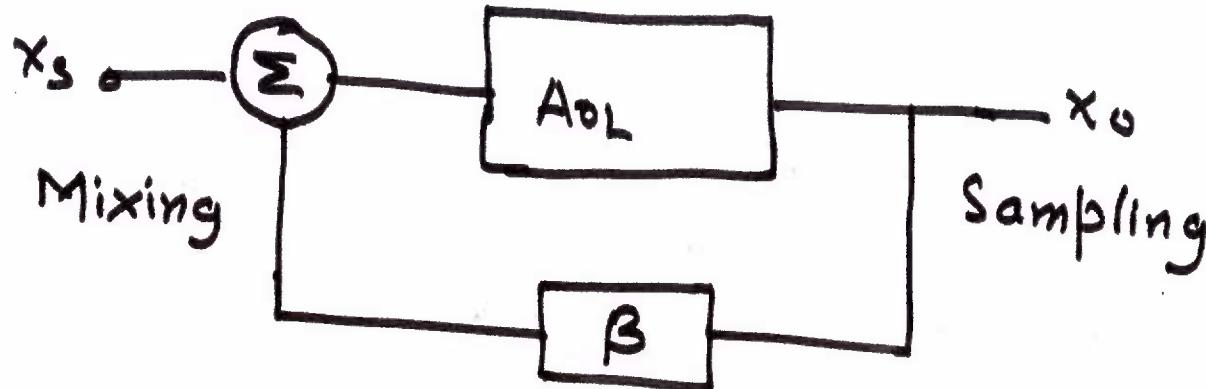

$A_{OL} = A_o$  = Gain without feedback

$A_{CL}$  = Closed Loop Gain

$A_{OL}\beta$  = Loop Gain

$1 + A_{OL}\beta$  = Amount of Feedback

$A_{OL}\beta$  = Loop Gain  
 $A_{OL}\beta$  = Return Ratio



CDEEP  
IIT Bombay

If  $A_o\beta \gg 1$

$$\text{Then } A_{CL} \cong \frac{A_o}{A_o\beta} = \frac{1}{\beta}$$

This means that Gain of Feedback Amplifier ( $A_{CL}$ ) is only decided by Passive Feedback network gain  $\beta$ .

$$\text{As } \beta < 1 \quad A_{CL} > 1$$

However  $A_{CL} = \frac{A_o}{1+A_o\beta}$  can change with  $\beta$  & value & sign of  $A_o$

① Negative Feedback

(ii) Positive Feedback



CDEEP  
IIT Bombay

# Properties of Negative Feedback

## [1] Gain Desensitivity

We have  $A_{CL} = \frac{A_0}{1 + A_0\beta}$

$$\text{or } dA_{CL} = \frac{dA_0}{(1 + A_0\beta)^2} \left[ \frac{1}{1 + A_0\beta} - \frac{A_0\beta}{(1 + A_0\beta)^2} \right]$$

$$\text{or } dA_{CL} = \frac{dA_0}{(1 + A_0\beta)^2}$$

$$\therefore \frac{dA_{CL}}{A_{CL}} = \frac{dA_0}{(1 + A_0\beta)^2} \cdot \frac{(1 + A_0\beta)}{A_0} = \frac{1}{(1 + A_0\beta)} \cdot \frac{dA_0}{A_0}$$

Clearly % change in  $A_{CL}$  is Always Less than % change in  $A_0$   
 $\therefore (1 + A_0\beta)$  is also called Degensitinty factor



$$x_t = x_s + x_f$$



## [2] Bandwidth Enhancement

$$A_{OL}(s) = \frac{A_{Midband}}{1 + s/\omega_0} = \frac{A_M}{1 + s/\omega_0} = A_0$$

$\omega_0$  is Dominant Pole

Then with Negative Feedback

$$\begin{aligned} A_{CL}(s) &= \frac{A_{OL}(s)}{1 + A_{OL}(s)\beta} = \frac{A_M / (1 + s/\omega_0)}{1 + \frac{A_M}{1 + s/\omega_0} \cdot \beta} \\ &= \frac{A_M / (1 + A_M \beta)}{s / (1 + A_M \beta) \omega_0 + 1} \\ &= \frac{A_{CL0}}{1 + s / [(1 + A_M \beta) \omega_0]} \quad A_{CL0} = \frac{A_M}{1 + A_M \beta} \end{aligned}$$

$$\text{Clearly Gain (OL)} = \frac{A_M}{1 + A_M \beta}$$

∴ New Pole =  $\omega_0(1 + A_M \beta) = \omega_f$

As  $A_M \beta > 1$


$$\therefore \omega_0(1 + A_M \beta) = \omega_f > \omega_0$$

∴ Bandwidth extension is seen.
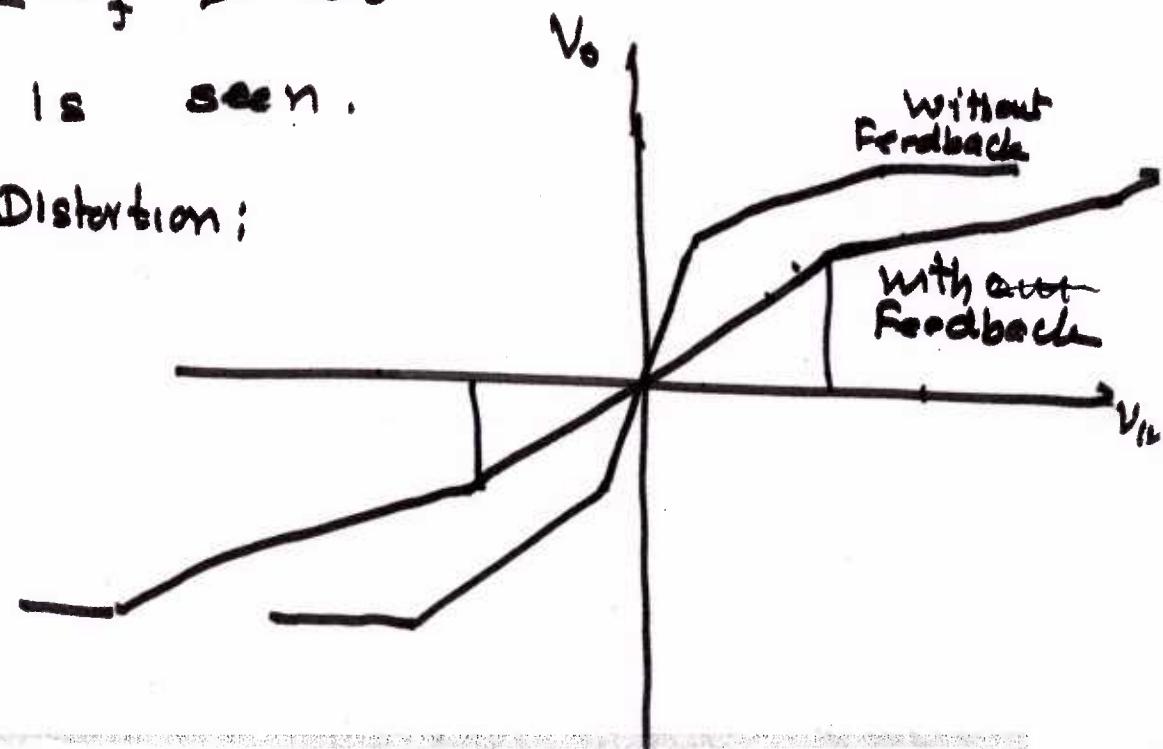
### [3] Reductions in Non-Linear Distortion;

→ Linearization?

Reduced Feedback Gain ( $\frac{dV_o}{dV_{in}}$ )  
increases 'linearity' for  
larger  $V_{in}$  range.



If this condition is met, the Feedback System is said to be Stable




**CDEEP**

EE618  
Sl. No.

$|L(j\omega)|$

LoopGain  
in db

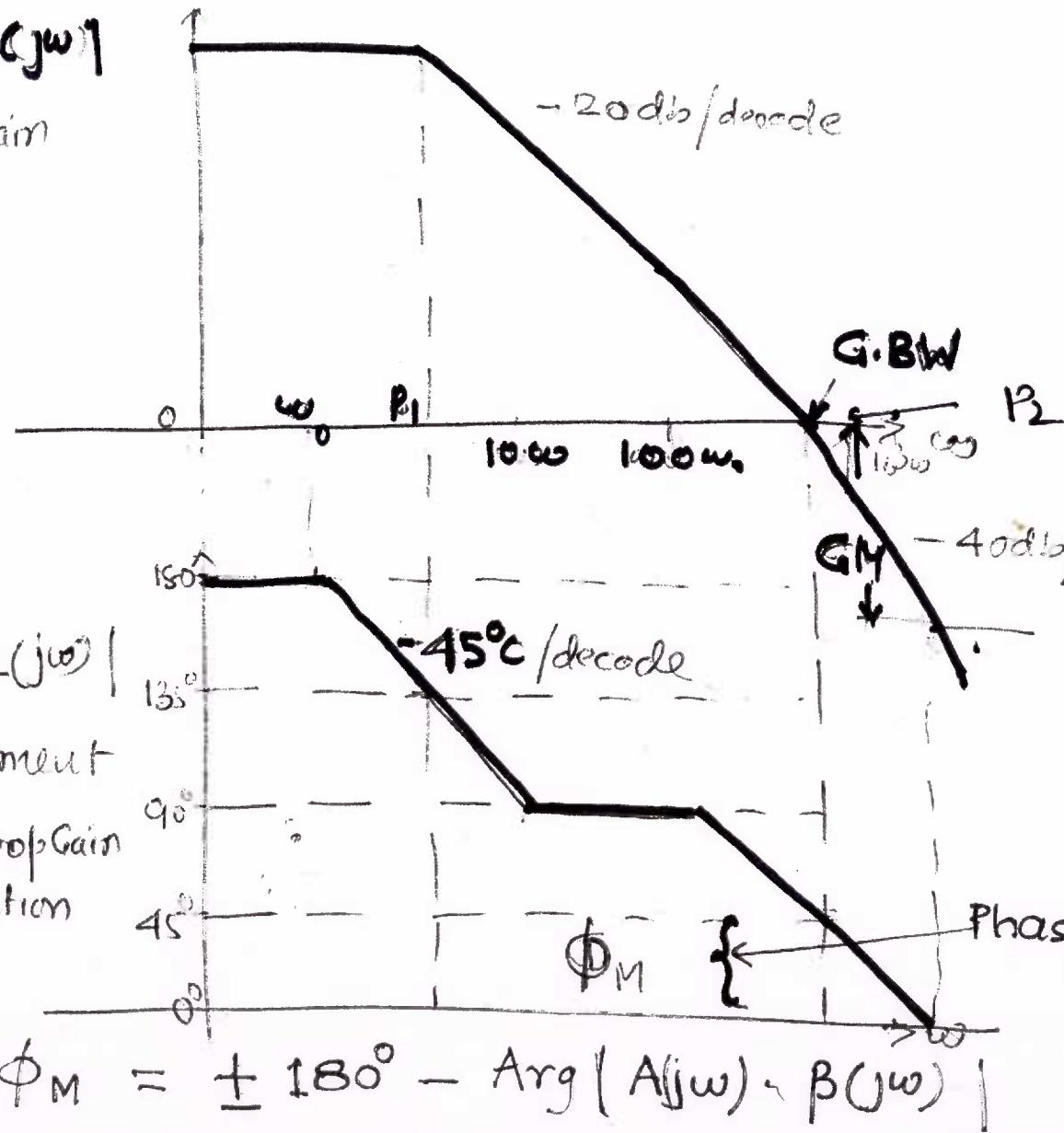

Two pole System

Phase goes as

$-45^\circ/\text{decade}$

Argument  
of Loop Gain  
function