

Stability Studies using Bode's Frequency Plots.



CDEEP
IIT Bombay

EE 618 L 18 / Slide 1

For an Amplifier with feedback, we have

$$\text{T. Function: } A_{eL}(s) = \frac{A_o(s)}{1 + A_o(s)\beta(s)}$$

We have defined $L(s)$ as Loop Gain $= A_o(s)\beta(s)$

$$\begin{aligned} \gamma \quad L(j\omega) &= A_o(j\omega)\beta(j\omega) \\ &= |A_o(j\omega) \cdot \beta(j\omega)| e^{j\phi(\omega)} \quad \text{Phasor} \end{aligned}$$

$\phi(\omega)$ is the Phase angle

$$\text{If } \phi(\omega_0) = 180^\circ \quad \text{Then } |A_o(j\omega_0)\beta(j\omega_0)| \cdot e^{j(180^\circ)}$$

Which means $L(j\omega_0) = - \underline{\text{Real}}$

Thus we can say Positive feedback commences,



CDEEP
IIT Bombay



EE 618 L 19 / Slide 2

As then we observe that the Denominator reduces $[1 - \{A_o(j\omega_o)\beta(j\omega_o)\}]$, and thus

$$\text{Then } A_{CL}(j\omega_o) > A_o(j\omega_o)$$

$A_o \equiv$ openloop Gain.

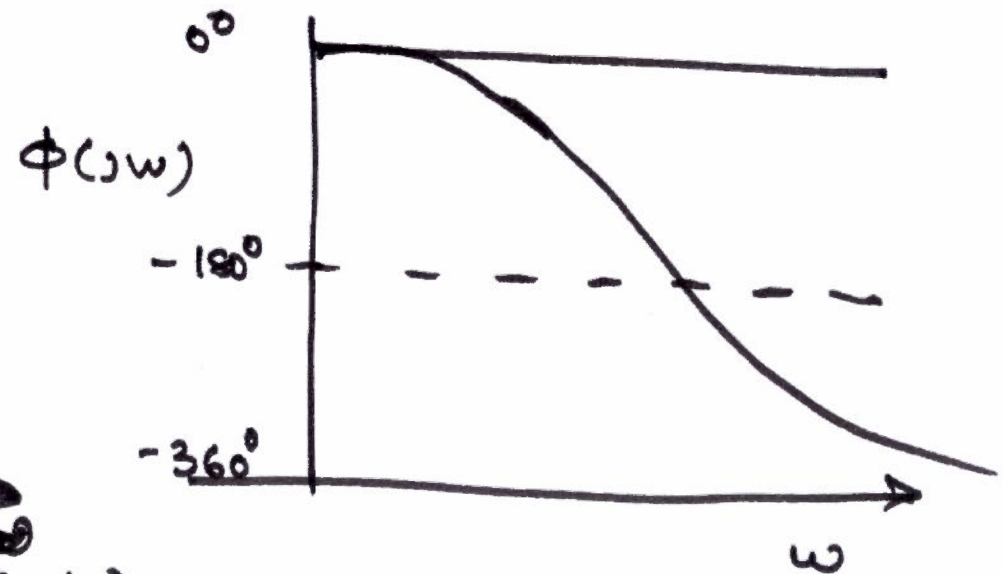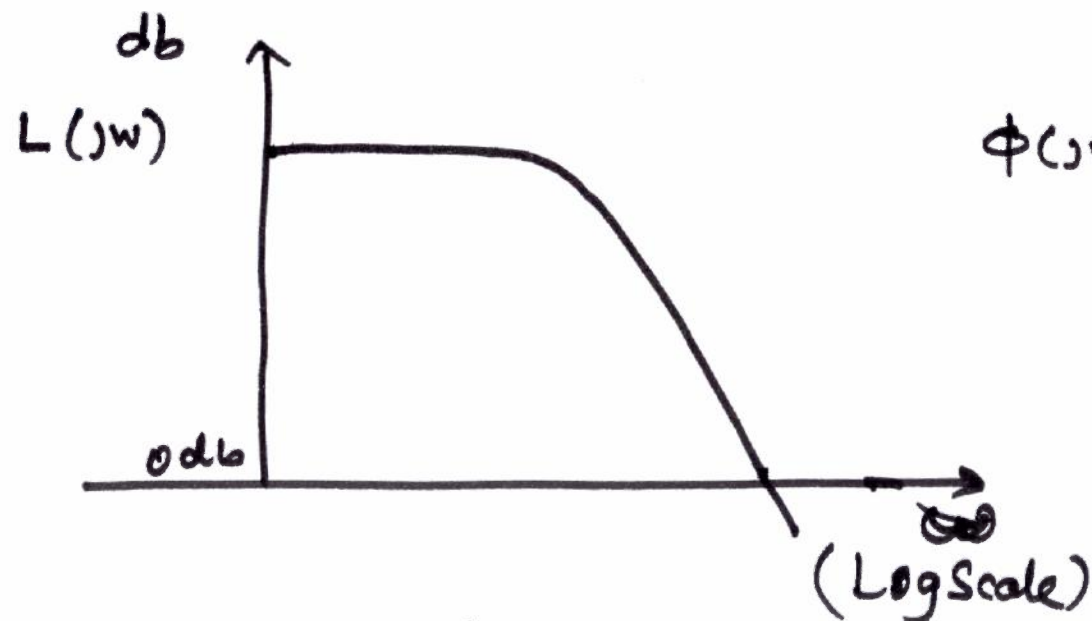This is the case of Positive Feedback which will then make Amplifier Unstable.



Bode's Plot for Loop Gain


If this condition is met, the Feedback System is said to be Stable



CDEEP

Two pole System

EE618: 20-15
SI No. 3

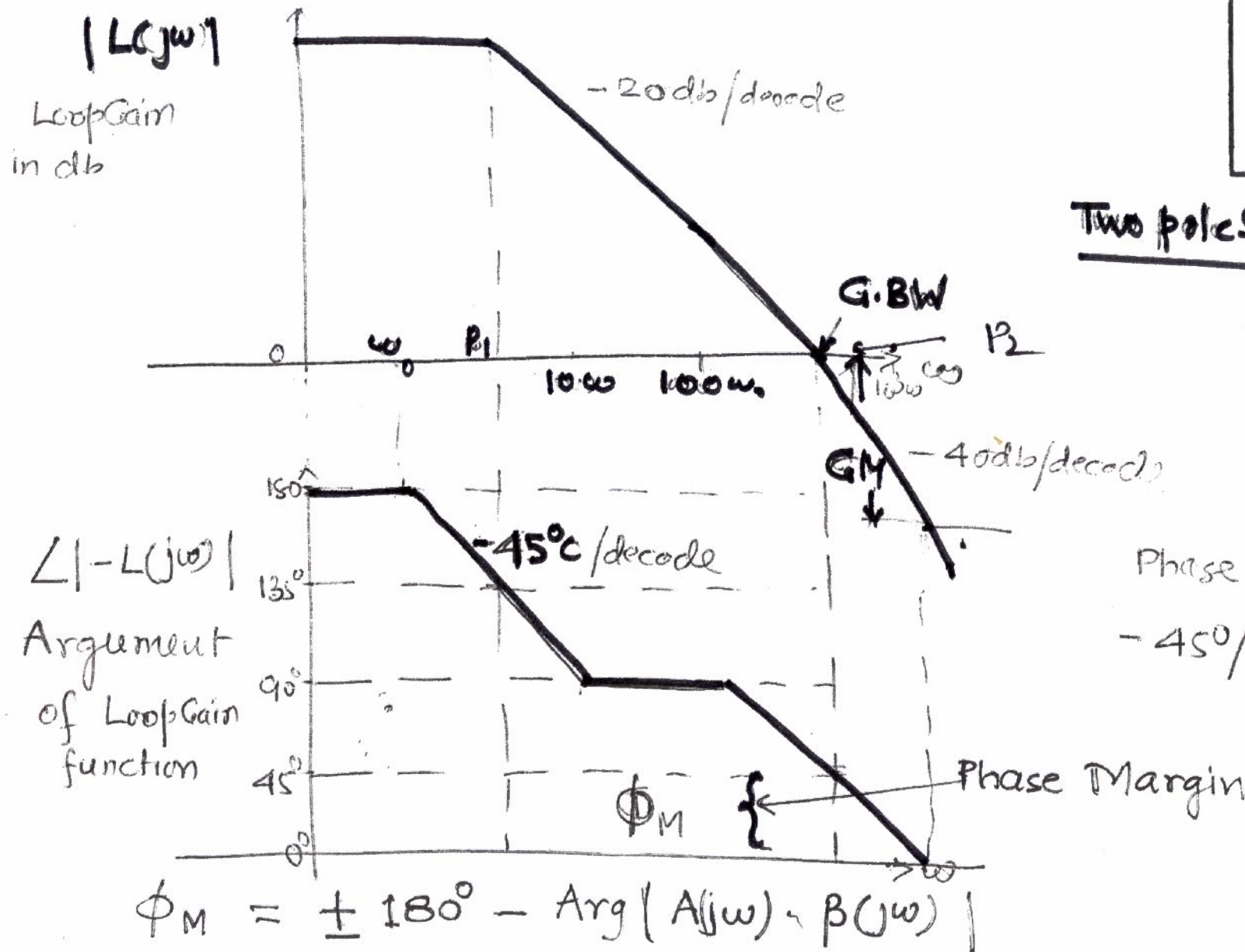


Stability looking from open-loop Bode plot

$$\log(A\beta) = \log A - \log(1/\beta)$$



CDEEP
IIT Bombay

EE 618 L 18 / Slide 4

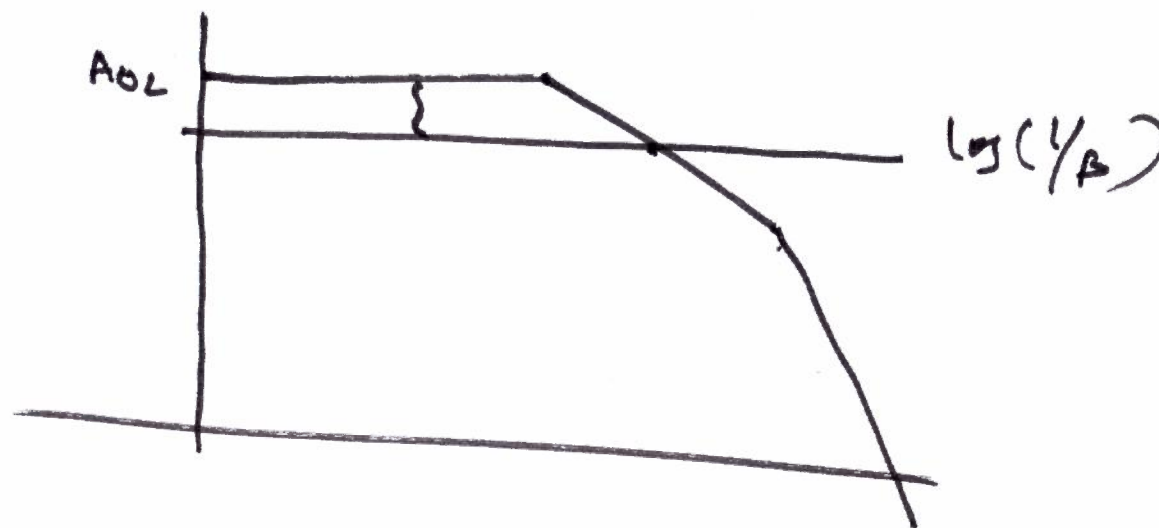


Time Response of Loop Gain with ϕ_M varying from 45° to 90° (Stability Requirement)



CDEEP
IIT Bombay

EE 618 L 18 / Slide 5

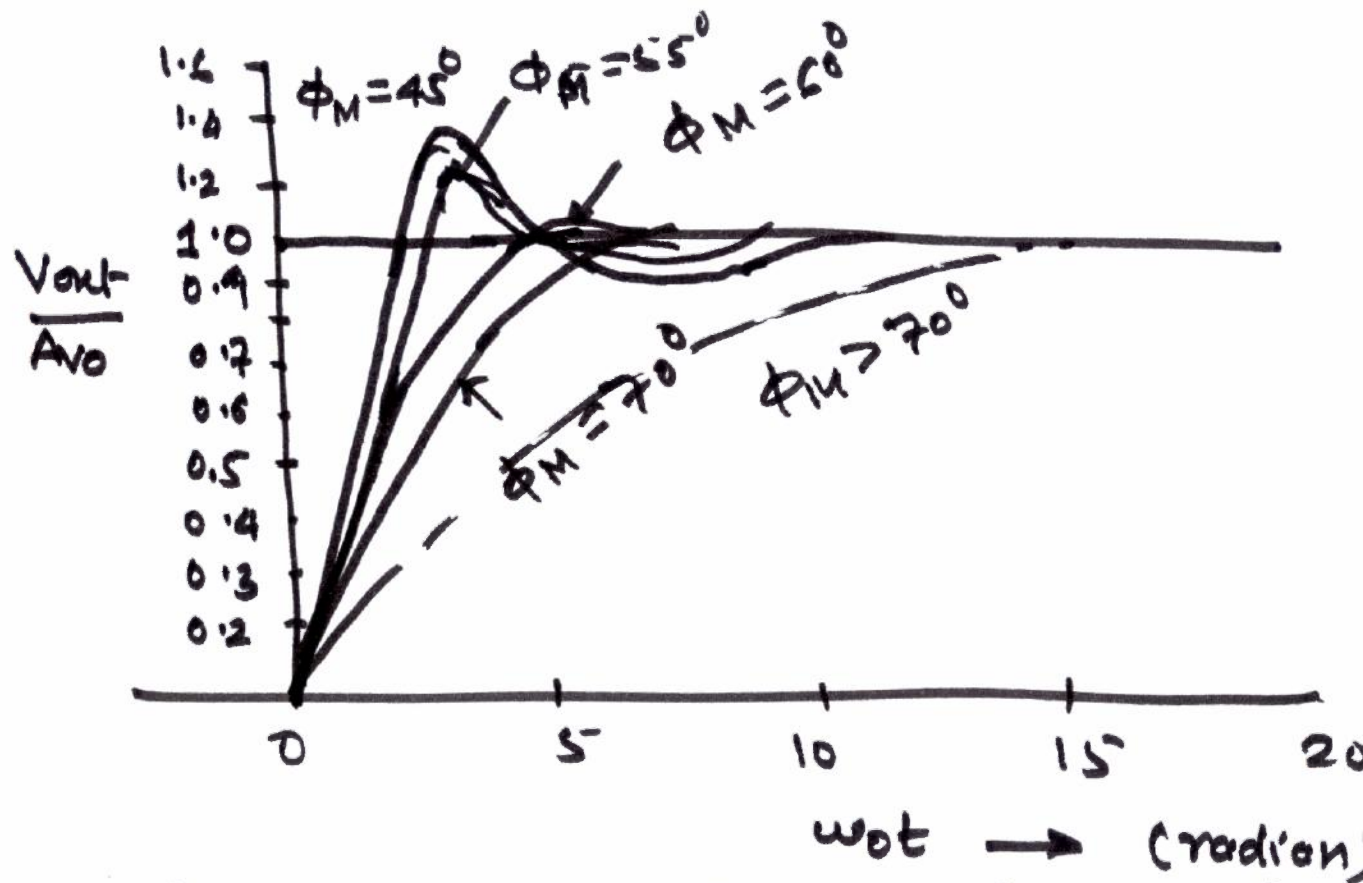


$\therefore \phi_M$ is normally chosen from 55° to 70°

Two stage Single-ended OPAMP with Parasitics




CDEEP
IIT Bombay

EE 618 L 18 / Slide 06

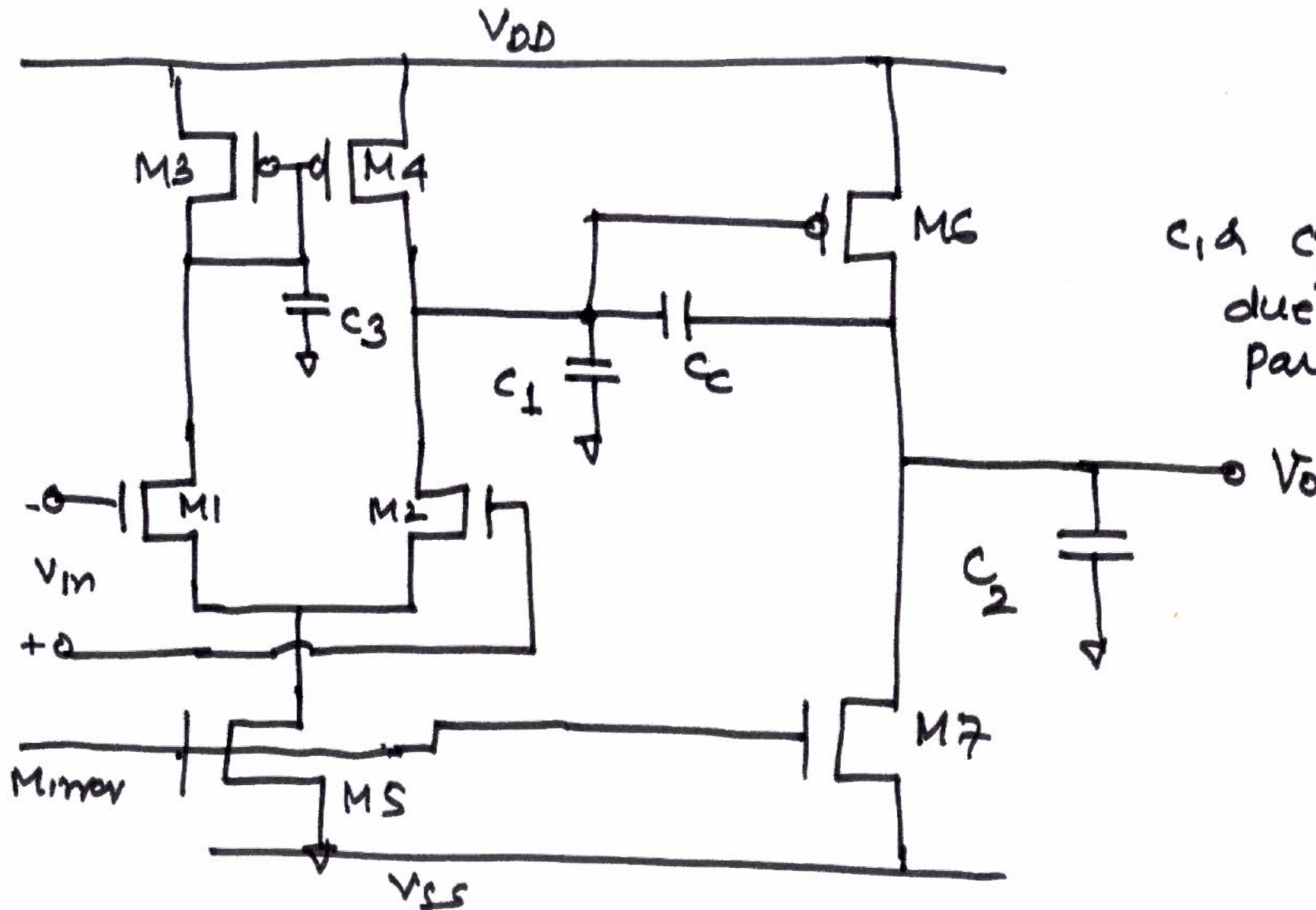

C_1 & C_2 could be due to C_{gd} , & other parasitics.

Poles and Zeros of Two Stage OPAMP

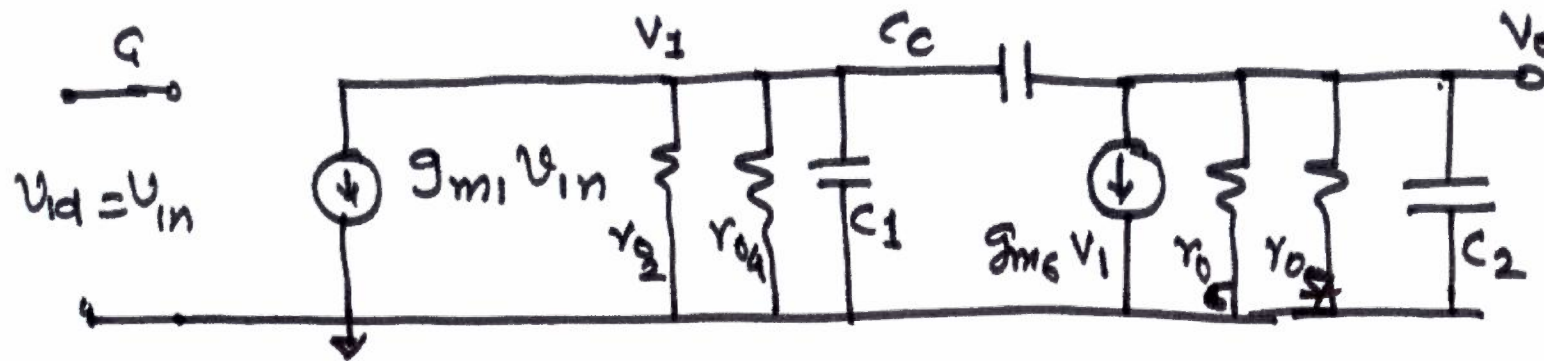

CDEEP
IIT Bombay

EE 618 L 18 / Slide 7

Take $R_1 = r_{o2} || r_{o4}$; $R_2 = r_{o6} || r_{o7}$

$$C_1 = C_{gs5} + C_{gd5}(1 + |A_{v20}|) + C_{db4} + C_{gd4} + C_{bd2} + C_{gd2}$$

$$C_2 = \overset{(C_{gd6})}{\downarrow} C_{gd6} (1 + \frac{1}{|A_{v20}|}) + \overset{(C_{db6})}{\downarrow} C_{db6} + C_{db7} + C_{ext}$$

We use nodal analysis to solve this Network



CDEEP
IIT Bombay

EE 618 L 18 / Slide 08

$$g_{m1} V_{in} + \frac{V_1}{R_1} + sC_1 V_1 + sC_c (V_1 - V_o) = 0 \quad - (1)$$

$$g_{m6} V_1 + \frac{V_o}{R_2} + sC_2 V_o + sC_c (V_o - V_1) = 0 \quad - (2)$$

From (1)

$$V_1 = \frac{(V_o sC_c - g_{m1} V_{in}) R_1}{[1 + R_1 s(C_1 + C_c)]} \quad - (3)$$

Substituting (3) in (2)

$$g_{m6} \left[\frac{(V_o sC_c - g_{m1} V_{in}) R_1}{[1 + R_1 s(C_1 + C_c)]} + V_o \left[\frac{1}{R_2} + sC_2 + sC_c \right] - sC_c \left[\frac{R_1 (V_o sC_c - g_{m1} V_{in})}{[1 + R_1 s(C_1 + C_c)]} \right] \right] = 0 \quad - (4)$$

From ④, we get

$$\frac{V_o(s)}{V_{in}(s)} = \frac{R_1 R_2 g_{m1} g_{m6} - g_{m1} R_1 R_2 s C_c}{g_{m6} R_1 R_2 s C_c + [(1 + R_1 s C_1 + C_c)][1 + R_2 s (C_2 + C_c)] - R_1 R_2 s^2 C_c^2}$$



CDEEP
IIT Bombay

EE 618 L 18 / Slide 19

If we define

$$m = g_{m1} g_{m6} R_1 R_2$$
$$n = R_2 (C_2 + C_c) + R_1 (C_1 + C_c) + g_{m6} R_1 R_2 s C_c$$

$$Q = R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)$$

Then Gain Transfer function $A_v(s)$ can be written as

$$A_v(s) = m(1 - s C_c / g_{m6}) / [1 + n s + Q s^2]$$

We have Denominator of $A_v(s)$ as

$$= 1 + ns + Qs^2$$

$$\rightarrow D = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right)$$

$$= 1 - \left(\frac{s}{p_1} + \frac{s}{p_2}\right) + \frac{s^2}{p_1 p_2}$$

If we assume that $|p_1| \gg |p_2|$

$$\text{Then } D = 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$$

$$\therefore p_1 = -\frac{1}{n} \quad \text{and} \quad \frac{1}{p_1 p_2} = Q$$

$$\text{or } p_2 = \frac{1}{p_1 Q} = -\frac{n}{Q}$$



CDEEP
IIT Bombay

EE 618 L 18 / Slide 10



CDEEP
IIT Bombay

EE 618 L 18 / Slide 11

$$\therefore |p_1| = \frac{1}{R_2(C_2 + C_c) + R_1(C_1 + C_c) + g_{m6} R_1 R_2 C_c}$$

$$D_n = (g_{m6} R_1 R_2 + R_2 + R_1) C_c + R_2 C_2 + R_1 C_1$$

For typical Amplifier

$$(g_{m6} R_1 R_2 + R_1 + R_2) C_c \gg R_1 C_1 + R_2 C_2$$

a. Further $g_{m6} R_1 R_2 \gg (R_1 + R_2)$

$$\therefore |p_1| = \frac{1}{g_{m6} R_1 R_2 C_c} \quad \text{or} \quad p_1 = \frac{-1}{g_{m6} C_c R_1 R_2}$$

now $p_2 = -\frac{\gamma}{Q} = +\frac{1}{p_1 Q}$

$$p_2 = \frac{-g_{m6} R_1 R_2 C_c}{R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)}$$

$$\text{or } p_2 = \frac{-g_{m6} C_c}{(C_1 C_2 + C_1 C_c + C_2 C_c)}$$

If $C_2 \gg C_1$ & $C_c \gg C_1$

$$\text{then } p_2 = \frac{-g_{m6} C_c}{C_2 C_c} = -\frac{g_{m6}}{C_2}$$

Further a zero $z_1 = \frac{g_{m6}}{C_c}$ exist as

at this frequency, Numerator of $A_v(s)$ becomes zero.



CDEEP
IIT Bombay

EE 618 L 18 / Slide 12

$$A_v(s) = \frac{m \left(1 - \frac{s C_c}{g_{m6}} \right)}{1 + n s + Q s^2}$$

Clearly this is Second Order system
which has One Zero and Two Poles,

$$P_1 = \frac{-1}{g_{m6} R_1 R_2 C_c}$$

$$P_2 = \frac{-g_{m6} \cdot C_c}{C_1 C_2 + C_2 C_c + C_1 C_c}$$

$$= - \frac{g_{m6}}{C_2}$$

if $C_2 \gg$ both C_1 & C_c
& $C_c \gg C_1$



CDEEP
IIT Bombay

EE 618 L 18 / Slide 13

$$\text{And } Z_1 = \frac{g_{m2}}{C_c}$$

The coupling Capacitor C_c is called
Compensating Capacitor and is used
in improving Stability.



CDEEP
IIT Bombay

EE 618 L 18 / Slide 14

With TWO POLES p_1, p_2 and a zero z_1



CDEEP
IIT Bombay

EE 618 L 18 / Slide 15


$$\phi_M = 180 - \tan^{-1}\left(\frac{\omega}{|p_1|}\right) - \tan^{-1}\left(\frac{\omega}{|p_2|}\right) + \tan^{-1}\left(\frac{\omega}{|z_1|}\right)$$

At $\omega = \text{GBW}$

{ Generally $z_1 \gg \text{GB}$
is attempted

$$\phi_M = 180 - \tan^{-1}\left(\frac{\text{GBW}}{|p_1|}\right) - \tan^{-1}\left(\frac{\text{GBW}}{|p_2|}\right) + \tan^{-1}\left(\frac{\text{GB}}{z_1}\right)$$

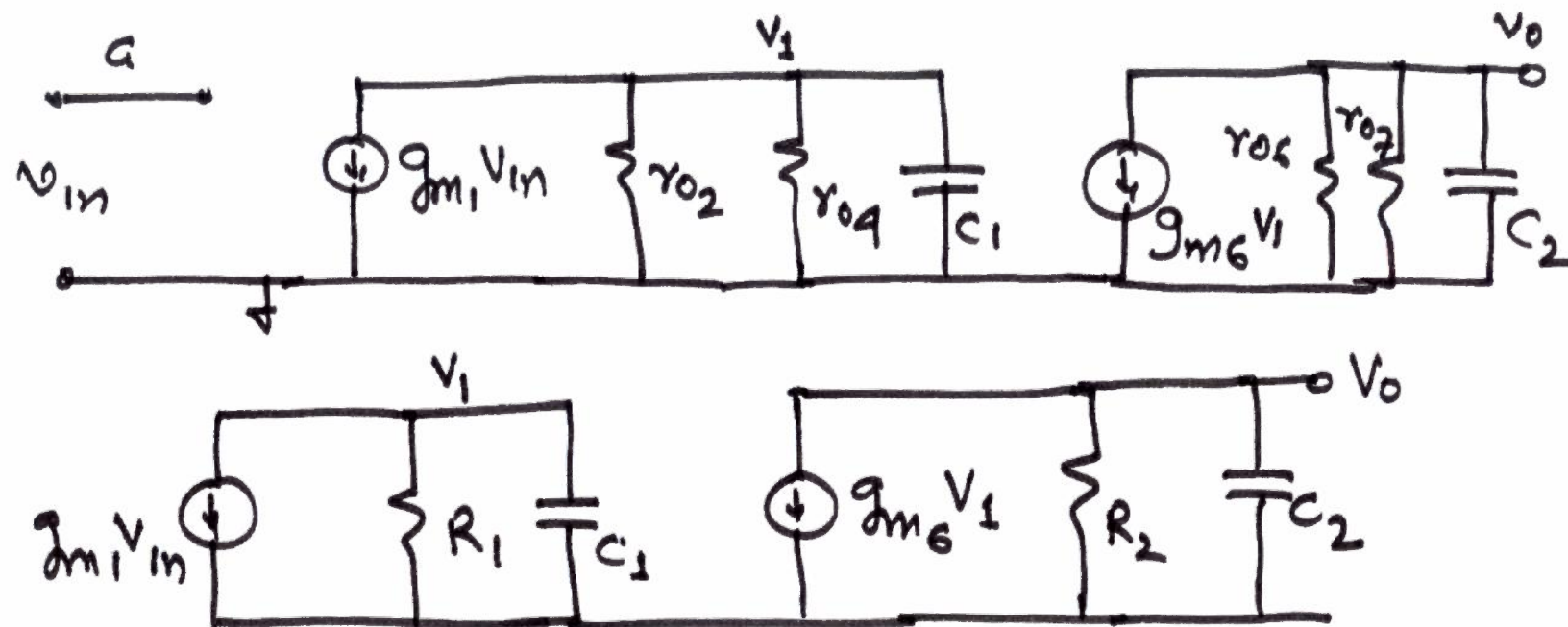If Miller Capacitor C_c is not present then the circuit equivalent looks like :



Poles P_1 & P_2 are then given by

$$|P_1| = \frac{1}{R_1 C_1} \quad \text{and} \quad |P_2| = \frac{1}{R_2 C_2}$$



CDEEP
IIT Bombay

EE 618 L 18 / Slide 16



CDEEP
IIT Bombay

EE 618 L 18 / Slide 17

With C_c we found, the poles are

$$|P_1'| = \frac{1}{g_{m6} R_2 (R_1 C_1) \frac{C_c}{C_1}}$$

$$|P_2'| = \frac{g_{m6}}{C_2}$$

clearly $|P_1| > |P_1'|$

Further with $g_{m6} > \frac{1}{R_2}$

Then $|P_2'| > |P_2|$

This shows that Miller Capacitance C_c in circuit allows 'Pole-Splitting'


We know

$$g_{m6} > \frac{1}{R_2} = (r_{o6} || r_{o7})^{-1}$$

looks like as:

C_c causes poles, Ca
Result :-

Result :- ① Bandwidth Reduction

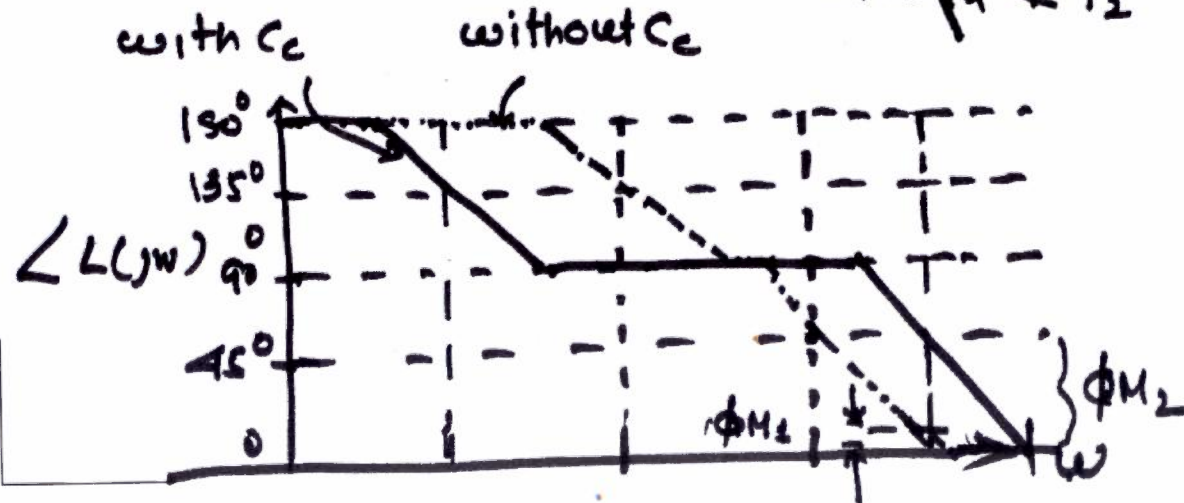
$$\phi_{M1} \text{ due to absence of } C_c$$
$$\phi_{m_2} \text{ due to Presence of } C_c$$

Clearly $\phi_{m2} > \phi_{M1}$
 $\therefore$ Stability Improves

In this case we chose position of new second pole p_2' placed at GBW point (0db Loop Gain)

$$\text{Without } C_c, \text{ GBW} = \frac{g_{m1}}{C_1 + C_c} \approx \frac{g_{m1}}{C_c}$$

$$\text{And } |p_2'| = \frac{g_{m6}}{C_2}$$

$\therefore$ For this case

$$\boxed{\frac{g_{m1}}{g_{m6}} = \frac{C_2}{C_c}}$$

For further improvement in ϕ_M

we can increase C_c , but we may lose Bandwidth.

Hence to avoid reduction of Bandwidth, but to

improve ϕ_M for Stability, we can convert RHP 'zero' to bring it towards LHP. A Series Resistance to C_c may do that.



CDEEP
IIT Bombay

EE 618 L 18 / Slide 19