



CDEEP
IIT Bombay

EE 618 L 20 / Slide 01

$I_{DS_1} = I_{SS}$, which means

$$I_{DS_1} = I_{DS_2} = \frac{I_{SS}}{2} = \frac{25}{2} \mu A = 12.5 \mu A \quad [3]$$

Neglecting $(1 + \lambda V_{DS})$ (λ = small) from Saturated Transistor Current, we get

$$V_{GS} = V_T + \sqrt{\frac{2 I_{DS}}{\beta'(W/L)}} \quad \text{i.e. } V_{OV} = \sqrt{\frac{2 I_{DS}}{\beta'(W/L)}}$$

c) ICMR evaluation.

$$\text{Given } V_{in\min} = -1.15 \text{ V} \quad V_{in\max} = 2 \text{ V}$$

$$\begin{aligned} \text{Now } V_{in\min} &= V_{SS} + V_{DSat_5} + V_{GS1} \\ &= V_{SS} + V_{DSat_5} + V_{T1} + \sqrt{\frac{2 I_{DS1}}{\beta'(W/L)_1}} = -1.15 \text{ V} \end{aligned}$$

Also

$$V_{inmax} = V_{DD} - V_{TP3} - \sqrt{\frac{2 I_{DS3}}{\beta_p'(W/L)_3}} - V_{DSatE} + V_{GS1} = 2V$$

$$2 = V_{DD} - V_{TP3} - \sqrt{\frac{2 I_{DS3}}{\beta_p'(W/L)_3}} + V_{TN1}$$

by using $V_{DSat} = V_{GS} - V_T$ relation,

$$2 = V_{DD} - V_{TP3} + V_{TN1} - \sqrt{\frac{I_{DS5}}{\beta_p'(W/L)_3}}$$

$$2 = 2.5 - 0.7 + 0.7 - \sqrt{\frac{I_{DS5}}{\beta_p'(W/L)_3}}$$

$$\therefore \frac{I_{DS5}}{\beta_p'(W/L)_3} = (0.5)^2 \quad \text{or} \quad \beta_p'(W/L)_3 = 2 I_{DS5} = 150 \mu A$$

$$\therefore (W/L)_3 = \frac{2 \times 50 \mu A}{50 \times 10^{-6}} = 2$$



CDEEP
IIT Bombay

EE 618 L 20 / Slide 02

If we include Body Bias effect

$$V_{TP_{max}} = -0.85$$

$$V_{TP_{min}} = -0.55 \text{ V}$$

$$V_{TN_{min}} = +0.55$$

$$V_{TN_{max}} = +0.85 \text{ V}$$



CDEEP
IIT Bombay

EE 618 L 20 / Slide 03

Then $2 = 2.5 - 0.85 + 0.55 - \sqrt{\frac{I_{DS3}}{\beta'_p (W/L)_3}}$


$$\frac{I_{DS3}}{\beta'_p (W/L)_3} = 0.04$$

$$\text{or } (W/L)_3 = \frac{2.5 \times 10^6}{50 \times 10^6 \times 0.04}$$

Then $(W/L)_3 = 12.5 \approx 12$


Hence $(W/L)_3 = (W/L)_4 = \text{Either 2 or 12}$
 depends upon accuracy

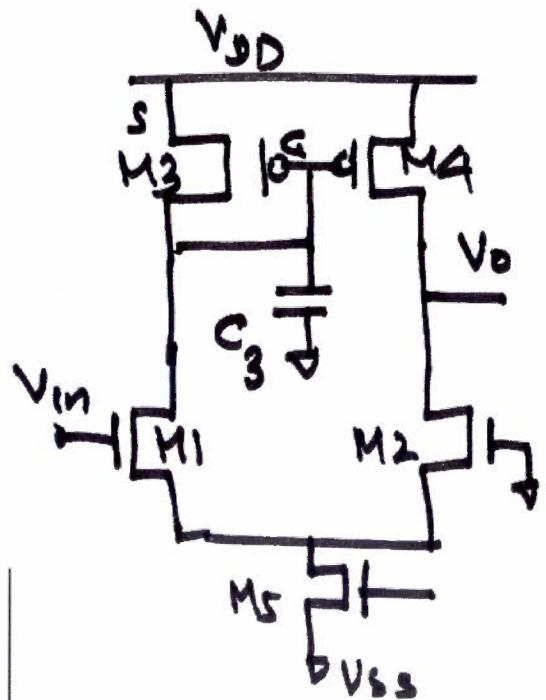Before we proceed further for evaluations of other (W/L)s of transistors, we wish to confirm that poles & zeros due to capacitor C_3 in the Diffamp ($M_1 - M_3$ arm) are far away from GBW, so that they can be neglected in overall response evaluations,



Here
 $C_3 = 2 C_{GS3}$

Eq. Cut α_S

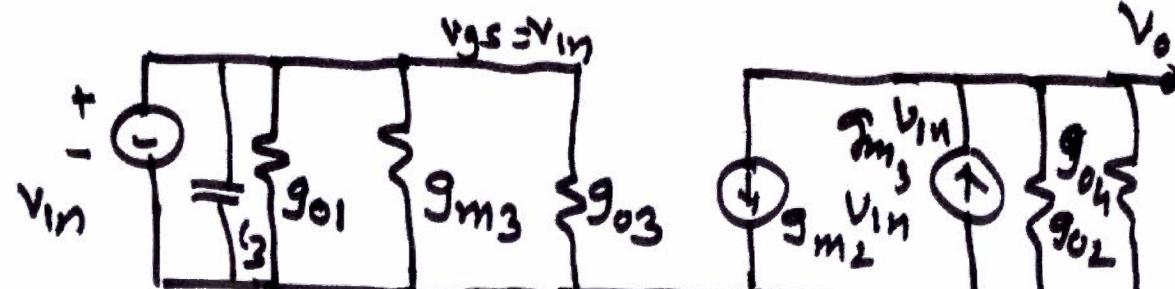

\therefore Gain Transfer F H $A_1(s)$ is :

$$A_1(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{g_{m1}}{2(g_{o2} + g_{o4})} \left[\frac{g_{m3} + g_{o1} + g_{o3}}{g_{m3} + g_{o1} + g_{o3} + sC_3} + 1 \right]$$

$$\approx -\frac{g_{m1}}{2(g_{o2} + g_{o4})} \cdot \frac{2g_{m3} + sC_3}{g_{m3} + sC_3}$$

$$\therefore P_3 = -\frac{g_{m3}}{C_3} = -\frac{g_{m3}}{2Cg_{s3}}$$

$$Z_3 = -\frac{2g_{m3}}{2Cg_{s3}} = -\frac{g_{m3}}{Cg_{s3}}$$

$$\text{Clearly } Z_3 = 2P_3$$



CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L~~20~~ / Slide ~~06~~

Given: $C_{ox} = 2.47 \times 10^{-15} / \mu^2$

$$\begin{aligned}\therefore C_{gs} &= \frac{2}{3} C_{ox} \cdot w_3 L_3 \\ &= \frac{2}{3} \times 2.47 \times 10^{-15} \times 12 \times 0.8 \\ &= 15.6 \text{ fF}\end{aligned}$$

$$\begin{aligned}g_{m3} &= \sqrt{2 \times \beta_p' \left(\frac{w_3}{L_3} \right) I_{DS3}} \\ &= \sqrt{2 \times 50 \times 12 \times 12.5 \times 10^{-6} \times 10^{-6}} \\ &= 3.877 \text{ mS } 12.24 \times 10^{-5} \text{ S}\end{aligned}$$

$$\therefore P_3 = \frac{g_{m3}}{2 \times C_{gs}} = \frac{6.12 \times 10^{-5}}{15.6 \times 10^{-15}} = 3.9 \text{ GHz}$$

If we add parasitics to C_{gs} (overlap caps) $\begin{cases} P_3 \approx 1.8 \text{ GHz, radials} \\ Z_3 = 3.9 \text{ GHz, radials} \end{cases}$

$$f_{p3} = \frac{3.9 \times 10^9}{6.28} \text{ Hz} = 625 \text{ MHz}$$

$$f_{23} = 1.25 \text{ kHz}$$

Thus C_3 capacitor does not interfere with
stability of 2 stage single ended OPAMP.

Evaluation of $(w/L)_1$ & $(w/L)_2$ (They are equal)

$$\text{Given } GBW = \frac{g_m_1}{C_c} = \frac{g_m_2}{C_c} = 8 \text{ MHz}$$

$$C_c = 2\pi \times 6 \times 10^6 \text{ rad/s.}$$

$$\text{or } g_m_1 = g_m_2 = 2 \cdot 5 \times 10^{-12} \times 6 \times 10^6 \times 6 \cdot 28 = 94 \cdot 2 \mu\text{s.}$$

EE 618 L 1-20 / Slide 08

$$\text{or } 6 \cdot 28 \times 1 \cdot 5 \times 10^{-5} = \sqrt{2 \beta_n (w/L)_1 I_{DS1}}$$

$$= \sqrt{2 \times 110 \times 10^{-6} \times (w/L)_1 \times 12 \cdot 5 \times 10^{-6}}$$

$$(6 \cdot 28)^2 2 \cdot 25 \times 10^{-10} = 220 \times 12 \cdot 5 \times 10^{-12} (w/L)_1$$

$$(w/L)_1 = \frac{2 \cdot 25 \times 10^{-10} \times 6 \cdot 28 \times 6 \cdot 28}{2 \cdot 20 \times 12 \cdot 5 \times 10^{-10}} = 3.23$$

$$\therefore (w/L)_1 = (w/L)_2 = 3.$$



CDEEP
IIT Bombay

Evaluation of $(W/L)_S$:

ICMR gives to us is -1.125 to $2V$

We know

EE 618 L~~20~~ / Slide ~~59~~

$$\begin{aligned}
 V_{in\min} &= -1.125 = V_{DSatS} + V_{SS} + V_{T_{nmax}} + \sqrt{\frac{2 I_{DSI}}{\beta_n C W/L}} \\
 \text{or } V_{DSatS} &= -1.125 - (-2.5) - 0.85 - \sqrt{\frac{2 \times 12.5 \times 10^6}{110 \times 10^6 \times 3}} \\
 &= 2.5 - 1.975 - \sqrt{\frac{25}{110 \times 3}} \\
 &= 2.5 - 1.975 - 0.275 \\
 &= 0.246 V
 \end{aligned}$$



CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L20 / Slide 10

$$\text{Now } I_{DS5} = \frac{\beta_n}{2} \left(\frac{W}{L}\right)_5 [V_{DSat_5}]^2$$

$$\therefore \left(\frac{W}{L}\right)_5 = \frac{2 \times 25 \times 10^{-6}}{110 \times 10^{-6} \times 0.060} = 7.58$$

$$\therefore \left(\frac{W}{L}\right)_5 \approx 8$$

Evaluation of $(W/L)_6$:

From Phase Margin & zero placement chosen by us (ϕ_m & z_1), we have obtained

$$\frac{g_{m6}}{g_{m1}} \geq 10 \quad \therefore g_{m6} = 10 g_{m1}$$

$$\therefore g_{m6} = 94.2 \times 10 \times 10^{-6} = 942 \mu\text{Amperes.}$$

$$\text{Now } I_{DS_C} = \frac{1}{2} \beta_p \left(\frac{W}{L}\right)_C (V_{DSat_C})^2 (1 + \lambda V_{DS}) \\ = \frac{1}{2} \beta_{p_C} (V_{GS_C} - V_{T_C})^2 (1 + \lambda V_{DSat_F})$$

$$\frac{\partial I_{DS_C}}{\partial V_{GS_C}} = g_{mC} = \frac{1}{2} \beta_{p_C} \cdot 2 (V_{GS_C} - V_{T_C})$$



CDEEP
IIT Bombay

EE 618 L 20 / Slide 11

$$g_{mC} = \beta_{p_C} V_{DSat_C}$$

$$\therefore \left(\frac{W}{L}\right)_C = \frac{g_{mC}}{\beta'_{p_C} V_{DSat_C}}$$

Hence we must evaluate V_{DSat_C} first.

We have $V_{out_{max}} = V_{DD} - V_{DSat_C}$

$$\therefore V_{DSat_C} = V_{DD} - V_{out_{max}} = 2.5 - 2.0 = 0.5V$$



CDEEP
IIT Bombay

EE 618 L 20 / Slide 12

$$\text{Hence } \left(\frac{W}{L}\right)_c = \frac{g_{m6}}{\beta_p' V_{Dsat6}}$$

$$= \frac{942 \times 10^{-6}}{50 \times 10^{-6} \times 0.5}$$

$$\left(\frac{W}{L}\right)_c = 37.7 \approx 40$$

$$I_{DS6} = 25 \times 10^{-6} \times 40 \times 0.25 = 235 \mu\text{A} \rightarrow \text{However this is V.V. High}$$

However $(W/L)_c$ can also be found through g_{m6} and g_{mq} relationship

We see M_6 & M_5 are also in Mirror Configuration

$$\therefore \frac{I_{DS6}}{I_{DS4}} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4}$$



CDEEP
IIT Bombay

EE 618 L20 / Slide 13

However that means

$$V_{SG_6} = V_{SG_4}$$

But

$$\text{at } g_{ms} = \beta'_p \left(\frac{W}{L}\right)_6 (V_{SG_6} - V_{TP_6})$$

$$g_{m_4} = \beta'_p \left(\frac{W}{L}\right)_4 (V_{SG_4} - V_{TP_4})$$

$$\therefore \frac{g_{ms}}{g_{m_4}} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4}$$

$$\text{However we know } g_{m_4} = \sqrt{2 \beta'_p \left(\frac{W}{L}\right)_4 I_{DS_4}}$$

$$= \sqrt{2 \times 12.5 \times 10^{-6} \times 50 \times 10^{-6} \times 12}$$

$$= 12.24 \times 10^{-5} \text{ S}$$

We have $g_{m6} = 942 \times 10^6 \text{ S}$

$$\begin{aligned}\therefore \left(\frac{W}{L}\right)_6 &= \frac{g_{m6}}{g_{m4}} \cdot \left(\frac{W}{L}\right)_4 \\ &= \frac{942 \times 10^6}{122 \times 10^6} \cdot 12\end{aligned}$$

$$\text{or } \left(\frac{W}{L}\right)_6 = 92.65 \approx 92$$

We find out V_{DSat6} by using expression

$$\begin{aligned}V_{DSat6} &= \frac{g_{m6}}{\left(\frac{W}{L}\right)_6 \cdot \beta'_p} = \frac{942 \times 10^6}{92.65 \times 50 \times 10^{-6}} \\ &= 0.2 \times \frac{942}{926.5} = 0.203 \text{ V}\end{aligned}$$

Then $I_{DS6} = \frac{\beta'_p}{2} \left(\frac{W}{L}\right)_6 (V_{DSat6})^2 = 95.8 \mu\text{A}$ which is OK by magnitude





CDEEP
IIT Bombay

EE 618 L 20 / Slide 15

Since M_5 & M_7 are in C.Major configuration

Assuming $I_6 = I_7$ we get

$$\frac{(\frac{W}{L})_7}{(\frac{W}{L})_5} = \frac{I_{DS6}}{I_{DS5}}$$

$$\text{or } (\frac{W}{L})_7 = 8 \cdot \frac{I_{DS6}}{I_{DS5}} = 8 \cdot \frac{95.8 \times 10^{-6}}{25 \times 10^{-6}} = 30.65$$

$$\therefore (\frac{W}{L})_7 = 30$$

$$\text{From } I_{DS7} = \frac{1}{2} \beta'_n (\frac{W}{L})_7 (V_{DSat7})^2$$

$$\text{or } V_{DSat7} = \sqrt{\frac{2 I_{DS7}}{\beta'_n (\frac{W}{L})_7}} = \sqrt{0.05663} = 0.23 \text{ V}$$

$$\therefore V_{out\min} = V_{DSat7} = 0.23 \text{ V} - 2.5 \text{ V} \rightarrow 2.27 \text{ V}$$

Power Dissipation Evaluation

$$P_{Diss\ max} = 2.5 \text{ mW}$$

$$P_{Diss} = (I_{Bias\ ckt} + I_{Diffamp} + I_{cain stage})(V_{DD} - V_{SS})$$

$$= [I_{Bias\ ckt} + (I_{DS_S} + I_{DS_Q})](V_{DD} - V_{SS})$$

$$I_{Bias\ ckt} = I_{DS_{12}} + I_{DS_Q}$$

Since M_S & M_Q - M₁₂ are in mirror conf.

We can assume $(\frac{W}{L})_{12} = (\frac{W}{L})_Q$

∴ $I_{DS_Q} = I_{DS_{12}}$ by Mirror



CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L 20 / Slide 17

However M_S is carrying $12.5 \times 2 = 25 \mu A$ current

If we choose

$$\left(\frac{W}{L}\right)_q = \left(\frac{W}{L}\right)_{12} = \frac{1}{2} \left(\frac{W}{L}\right)_{S'} = \frac{8}{2} = 4$$

$$\text{Then } I_{DSq} = I_{DS_{12}} = \frac{I_{DS_{S'}}}{2} = 12.5 \mu A$$

$$\therefore \text{Bias Current}_{\text{Total}} = (12.5 + 12.5) \mu A$$

$$\therefore P_{\text{Diss,Bias}} = 25 \times 10^{-3} \times 5 = 0.125 \text{ mW.}$$

$$\text{Now } V_{DSat_S} = 0.246 \text{ V} \quad \text{Hence } V_{G12} = V_{GSq} = V_{GS_S}$$

At edge J Sat case

$$V_{GS} - V_T = V_{DSat} \quad \therefore V_{GS} = V_{DSat} + V_{T_{min.}}$$

$$\therefore V_{GS_{12}} = 0.246 + 0.7 = 0.946 \text{ V}$$



CDEEP
IIT Bombay

EE 618 L²⁰ / Slide 18

$$V_{GS12} = V_{DS12}$$

$$\therefore R = \frac{(V_{DD} - V_{SS}) - V_{DS12}}{I_{DS12}}$$

$$= \frac{5 - 0.946}{12.5 \times 10^{-6}}$$

$$= \frac{4.054}{12.5} \text{ M}\Omega = 325 \text{ k}\Omega$$

Given

$$\text{Total } P_{Diss} \leq 2.5 \text{ mW}$$

$$\therefore P_{Diss_T} - P_{Diss_{Bias}} \leq 2.5 \text{ mW} - 0.125 \text{ mW}$$

$$\leq 2.375 \text{ mW}$$

or $P_{Diss_{Diffamp}} + P_{Diss_{GS}} \leq 2.375 \text{ mW}$

$$5(25 + 95.8) \times 10^{-6} = 0.6 \text{ mW which is certainly } < 2.375 \text{ mW}$$

Now DC Gain of Two Stage OPAMP is

$$A_{v(0)} = \frac{g_{m1}}{g_{o2} + g_{o4}} * \frac{g_{m5}}{g_{o2} + g_{o7}}$$

$$= \frac{2g_{m1} g_{m5}}{(\lambda_2 + \lambda_4) I_{DS5} * (\lambda_6 + \lambda_7) I_{DS6}}$$

$$\lambda_2 \& \lambda_7 \Rightarrow \lambda_n = 0.04$$

$$\lambda_4 \& \lambda_6 \Rightarrow \lambda_p = 0.05$$

$$A_{v(0)} = \frac{2 \times 94.2 \times 942 \times 10^{-12}}{25 \times 10^6 (0.09)^2 * 95 \times 10^{-12}}$$

$\therefore A_{v(0)} = 9225 \text{ V/V}$ which is much greater than $A(g^0)_{\text{spec}} = 4000 \text{ V/V}$



CDEEP
IIT Bombay

EE 618 L 20 / Slide 19

Design Output


- ① choice of $C_C = 2.5 \text{ pf}$, $\phi_H = 60^\circ$, $Z_1 = 10 \text{ GSW}$
- ② DC Gain $A_V(0) = 9225$ (4000) at $I_{SS} = 25 \mu\text{A}$
- ③ Bandwidth = 4 kHz (9 kHz desired)
- ④ $V_{out, max} = 2.3 \text{ V}$ (+2V)
- ⑤ $V_{out, min} = 0.23 \text{ V} - 2.5 \text{ V} = -2.27 \text{ V}$ (-2V)
- ⑥ $P_{diss} = 0.725 \text{ mW}$ (2.5 mW)
- (7) Channeled Length $L = 0.8 \mu$
- (8) Sizes: $(w/L)_1 = (w/L)_2 = 3$; $(w/L)_3 = (w/L)_4 = 12$
 $(w/L)_5 = 8$; $(w/L)_6 = 92$; $(w/L)_7 = 30$
 $(w/L)_8 = ?$; $(w/L)_9 = 4 = (w/L)_{12}$ & Bias Resistor = 325 k



CDEEP
IIT Bombay

EE 618 L 20 / Slide 20

full OPAMP schematic is shown below

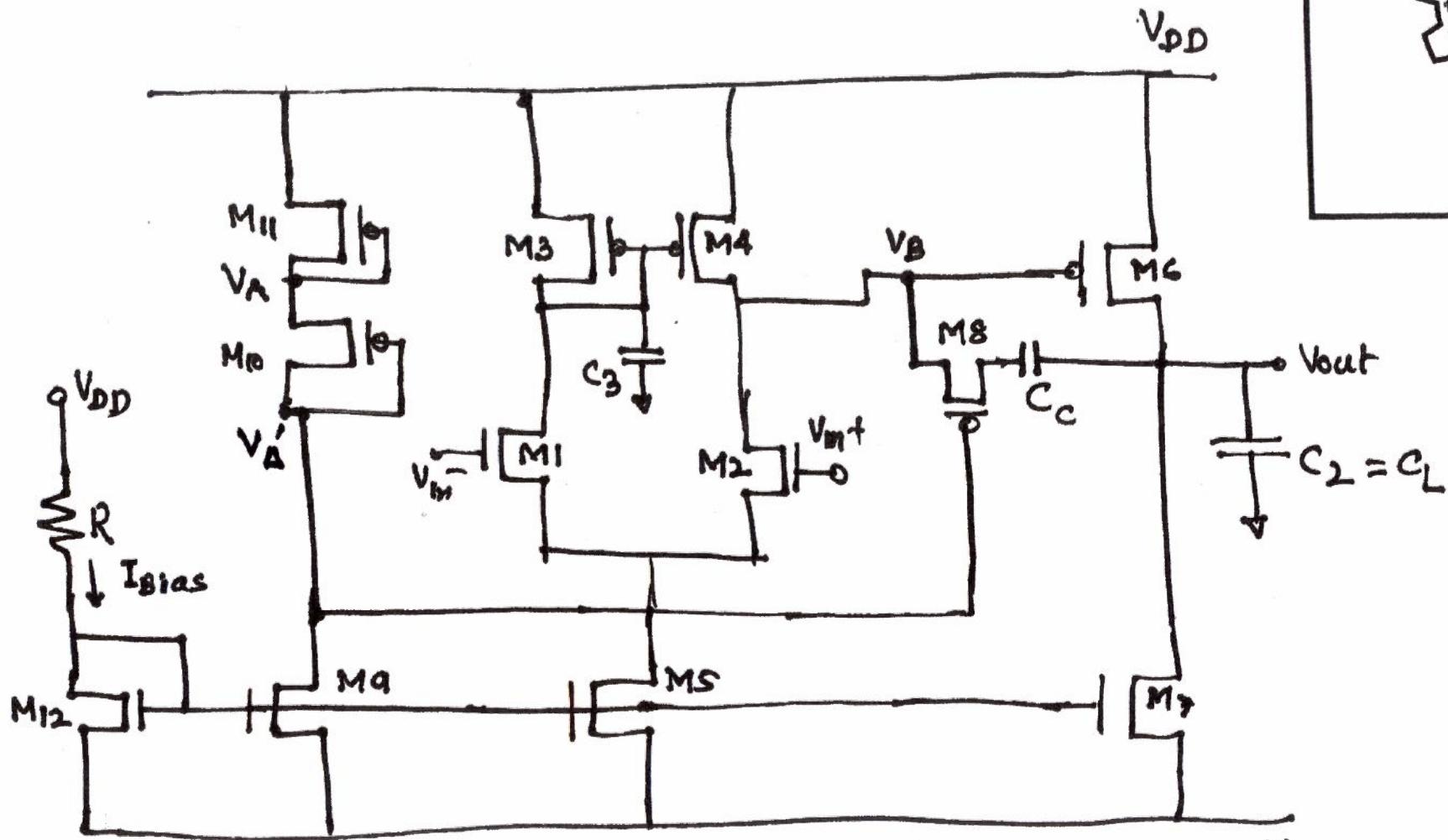

20-21

We set $V_A = V_B \approx V'_A = V_B$
such that $(W/L)_8$ can be evaluated