



CDEEP
IIT Bombay

EE 618 L 22 / Slide 01

OTA Applications

OTA use in Realisation of Active Filters
Continuous (Analog) Filters are mostly
used in cases which have lower cut-off.

For example a RC filter is a passive continuous filter.
The cut-off frequency is function of RC time constant.

For higher frequency cut-offs, one must get v. small
values of R and C. R realisation on silicon has limits
of getting extreme value of R (larger & v. smaller).

Thus frequency response of filters are limited
bandwidths one.


On silicon an Active filter can satisfy both input-
output relations by realising Resistors by $1/q_m$ values.



Such filters are also called g_m -C continuous filters.

OTA is a device, whose output could be controlled 'transconductance'.

Take an OTA as shown

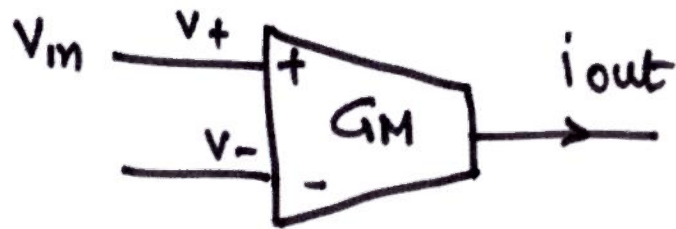

$$i_{out} = G_M \cdot (V_+ - V_-)$$

If we put $V_- = 0$

$$\text{Then } i_{out} = G_M \cdot V_{in}$$




CDEEP
IIT Bombay

EE 618 L 22 / Slide 03



CDEEP
IIT Bombay


EE 618 L 22 / Slide 04

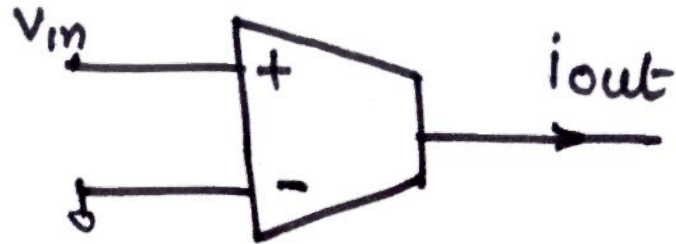

$$G_m = g_{m1}$$


Unloaded

$$i_{out} = g_{m1} V_{in}$$

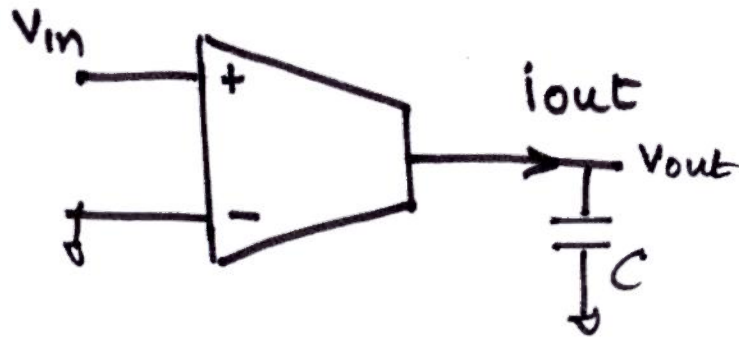


Loaded

$$V_{out} = i_{out} / j\omega C$$

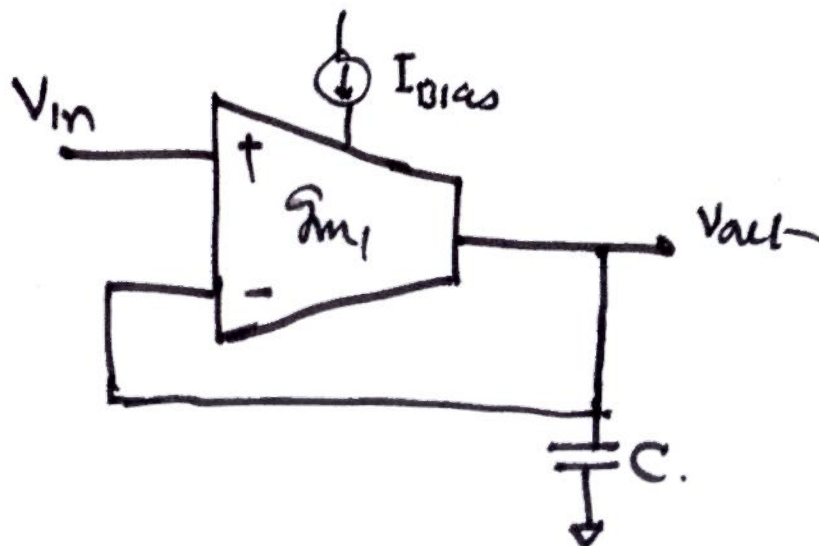

Loaded with -ve
Feedback

Low Pass Filter

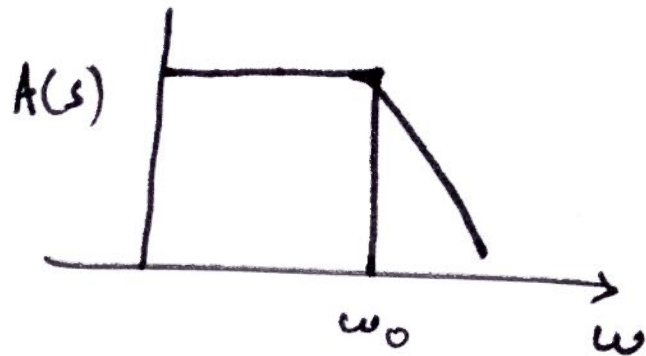

$$\omega_0 = \frac{g_{m1}}{C}$$



CDEEP
IIT Bombay

EE 618 L 22 / Slide 05

$$v_- = v_{out}$$


$$\begin{aligned} i_{out} &= g_{m1} (v_+ - v_-) \\ &= g_{m1} (v_{in} - v_{out}) \end{aligned}$$

$$v_{out} = i_{out} \cdot \frac{L}{j\omega C} = \frac{g_{m1}}{j\omega C} (v_{in} - v_{out})$$

$$v_{out} \left[1 + \frac{g_{m1}}{j\omega C} \right] = \frac{g_{m1}}{j\omega C} v_{in}$$

$$A(s) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{\frac{g_{m1}}{j\omega C}}{1 + \frac{g_{m1}}{j\omega C}} = \frac{1}{1 + j\omega C \frac{1}{g_m}} = \frac{1}{1 + j(\omega/\omega_0)}$$

High Pass Filter

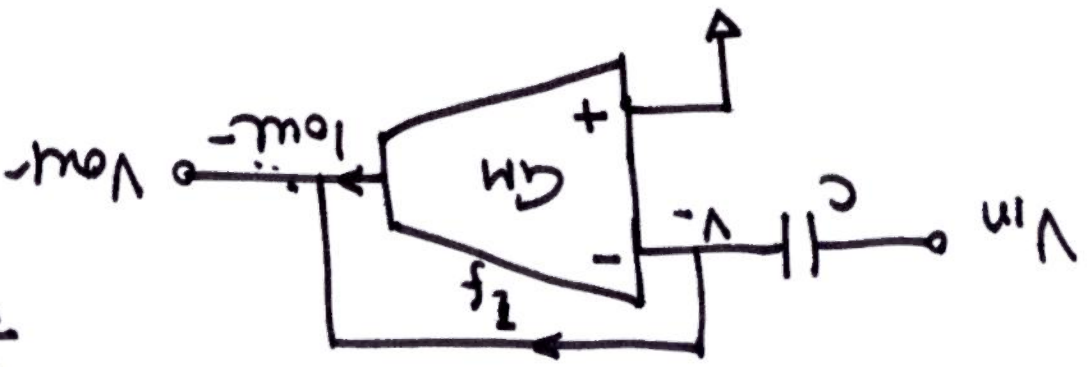

$$V_{out} = G_M (V_+ - V_-) = -G_M V_{out}$$


$$-V_{out} = +I_f = +(V_{in} - V_-) g_m C = g_m C (V_{in} - V_{out})$$


$$\therefore G_M V_{out} = g_m C V_{in} - g_m C V_{out}$$

$$V_{out} (1 + g_m C) = g_m C V_{in}$$

$$V_{out} = \frac{g_m C V_{in}}{1 + g_m C}$$

High Pass response

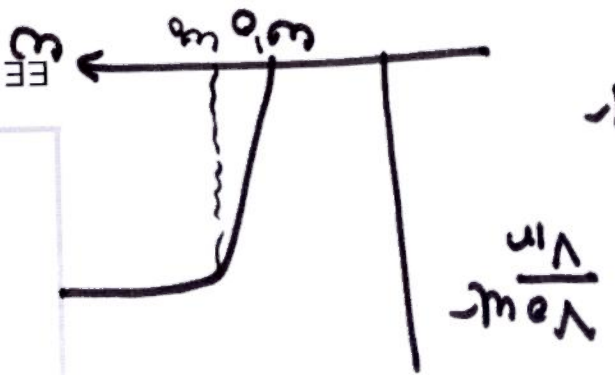

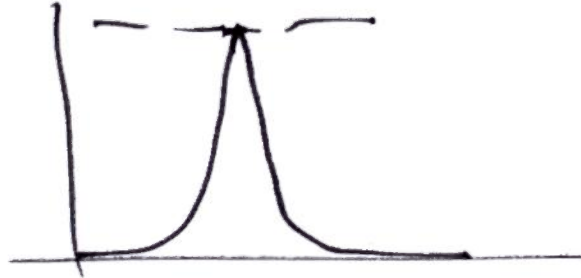

CDEEP
IIT Bombay

EE 618 L 22 / Slide 07


"General Purpose Biquad Filter with OTA"

Combining LP & HP filter architectures as seen earlier, we can create, both Band Pass and Band Reject filters.




CDEEP
IIT Bombay

EE 618 L 22 / Slide 08

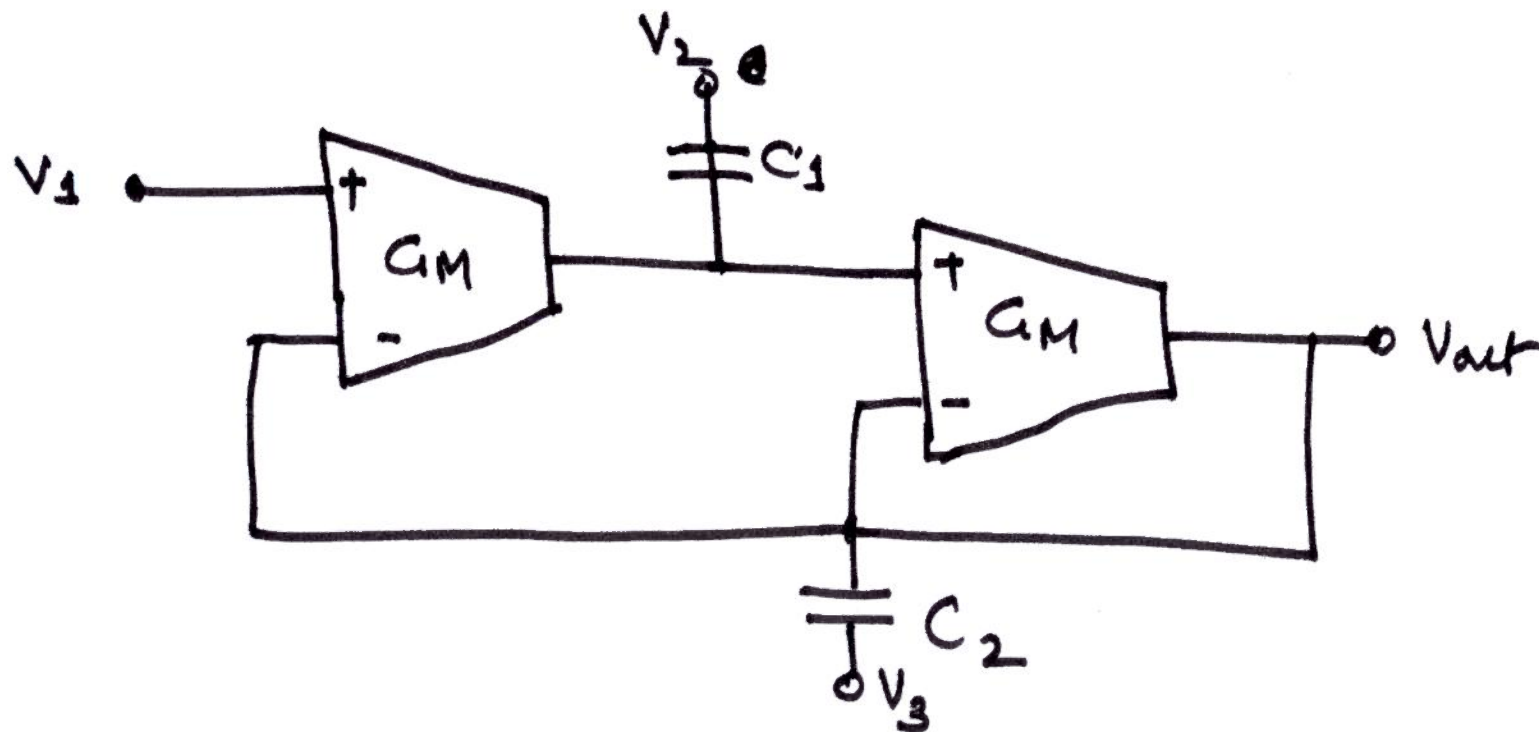

If we put V_2 and V_3 to Ground, we get-

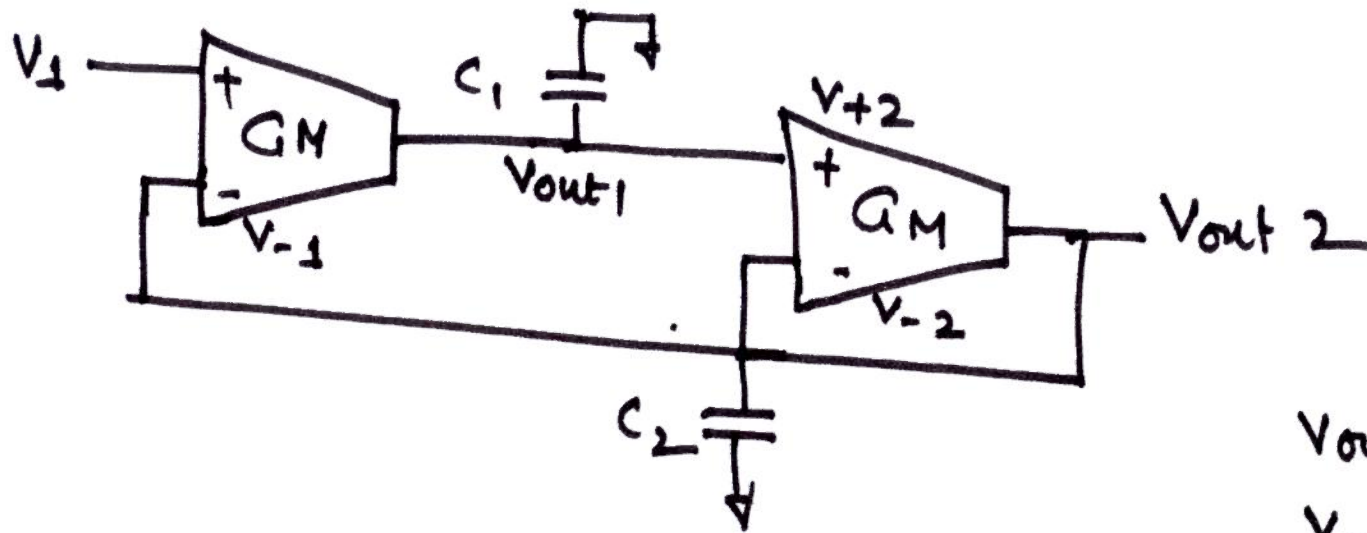

CDEEP
IIT Bombay

EE 618 L 22 / Slide 09

We have

$$V_{out1} = V_{+2}$$

$$V_{-1} = +V_{-2} = V_{out2}$$

$$V_1 = V_{in}$$

— (1)

$$V_{out1} = G_M (V_1 - V_{-1}) \cdot \frac{1}{j\omega C_1}$$

$$V_{out1} = G_M (V_{in} - V_{out2}) \cdot \frac{1}{j\omega C_1}$$

$$V_{out2} = G_M (V_{+2} - V_{-2}) \cdot \frac{1}{j\omega C_2}$$

$$= G_M (V_{out1} - V_{out2}) \cdot \frac{1}{j\omega C_2}$$

— (2)

Substituting ① in ②

$$V_{out2} = \frac{g_m}{j\omega C_2} \left[\frac{g_m}{j\omega C_1} (V_{in} - V_{out2}) - V_{out2} \right]$$

or $j\omega C_2 \cdot \frac{V_{out2}}{g_m} = \frac{g_m V_{in}}{j\omega C_1}$ Taking $g_m = g_{m1}$

$$- \left[+ \frac{g_{m1}}{j\omega C_1} + 1 \right] V_{out2}$$

$$\therefore V_{out2} \left[1 + \frac{g_{m1}}{j\omega C_1} + \frac{j\omega C_2}{g_{m1}} \right] = \frac{g_{m1}}{j\omega C_1} \cdot V_{in}$$

$$\therefore \text{Trans. fn } \frac{V_{out2}}{V_{in}} = \frac{g_{m1}/j\omega C_1}{1 + \frac{g_{m1}}{j\omega C_1} + \frac{j\omega C_2}{g_{m1}}} = A(j\omega)$$



CDEEP
IIT Bombay

EE 618 L 22 / Slide 10

$$\Rightarrow A(s) = A(j\omega) = \frac{g_{m1}/sC_1}{1 + \frac{g_{m1}}{sC_1} + \frac{sC_2}{g_{m1}}}$$

$$= \frac{g_{m1}}{sC_1 + g_{m1} + \frac{s^2 C_1 C_2}{g_{m1}}}$$

$$= \frac{g_{m1}^2}{s^2 C_1 C_2 + s g_{m1} C_1 + g_{m1}^2}$$

$$\Rightarrow H(s) = \frac{c}{as^2 + bs + c}$$

→ Two poles only.
Dominant pole is
cut-off frequency

∴ This is a Low Pass filter.



CDEEP
IIT Bombay


EE 618 L 22 / Slide 11



CDEEP
IIT Bombay

EE 618 L 22 / Slide 12

Case II : $V_2 = V_m$, $V_1 = V_3 = 0$

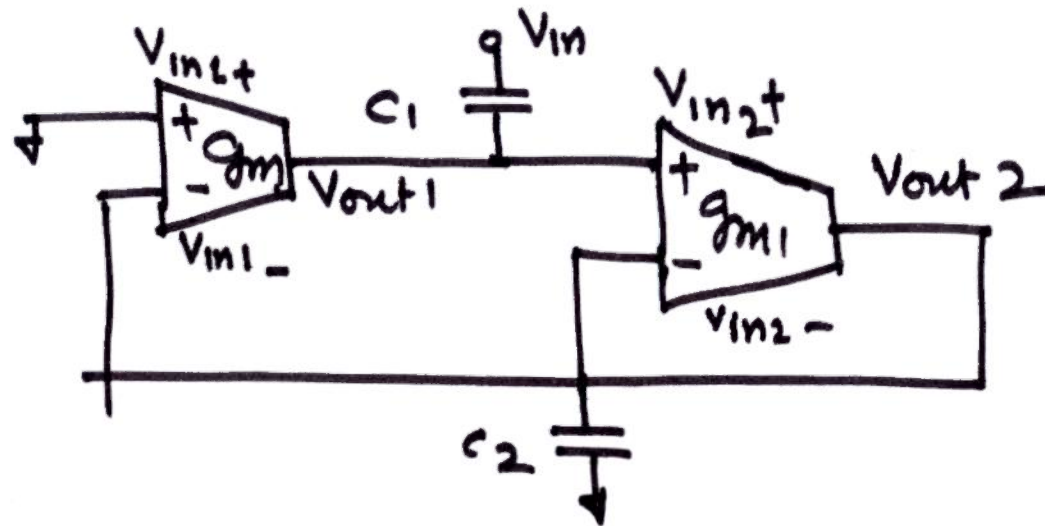

$$V_{out1} = g_{m1} (0 - V_{out2}) \cdot \frac{1}{j\omega C_1} + V_{in}$$

$$V_{out1} = -\frac{g_{m1} V_{out2}}{j\omega C_1} + V_{in} \quad \text{--- (1)}$$

$$V_{out2} = g_{m1} (V_{out1} - V_{out2}) \cdot \frac{1}{j\omega C_2} \quad \text{--- (2)}$$

Substituting ① in ②

$$V_{out2} = \frac{g_{m1}}{j\omega C_2} \left[-\frac{g_{m1} V_{out2}}{j\omega C_1} + V_{in} - V_{out2} \right]$$

$$\left[1 + \frac{j\omega C_2}{g_{m1}} + \frac{g_{m1}}{j\omega C_1} \right] V_{out} = \cancel{V_{in}} V_{in}$$

$$\left[1 + \frac{sC_2}{g_{m1}} + \frac{g_{m1}}{sC_1} \right] V_{out} = V_{in}$$

$$\alpha \quad \frac{V_{out}}{V_{in}} = A(s) = \frac{1}{1 + \frac{sC_2}{g_{m1}} + \frac{g_{m1}}{sC_1}}$$

$$= \frac{s}{a_0 s^2 + b_0 s + c_0} = \frac{g_{m1} s C_1}{s^2 C_1 C_2 + s g_{m1} C_1 + g_{m1}^2} = \frac{\text{zeros: } s}{a s^2 + b s + c}$$



CDEEP
IIT Bombay

EE 618 L 22 / Slide 13

$H(s) = \frac{s}{as^2 + bs + c}$ is for Bandpass filter case.

∴ If we set $V_2 = V_{in}$ & $V_1 = V_3 = 0$

The TWO OTA architecture behaves as Bandpass filter.

Similarly if $V_3 = V_{in}$ & $V_1 = V_2 = 0$, we get

$$A(s) = \frac{s^2 C_1 C_2}{s^2 C_1 C_2 + s C_1 g_{m1} + g_{m1}^2} \quad \text{which is}$$


a transfer function for High pass filter



CDEEP
IIT Bombay

EE 618 L 22 / Slide 14

OTA as Voltage Amplifier

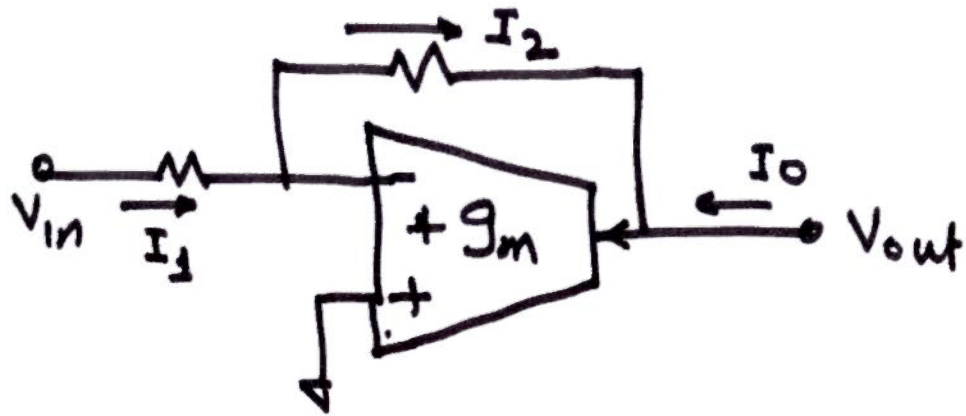

$$I_0 = g_m (V^+ - V^-) = -g_m V^-$$

$$\alpha \quad \frac{V_{in} - V_-}{R_1} = I_1 = I_2 = \frac{V_- - V_{out}}{R_2}$$

$$\text{But } I_0 = -I_2$$

$$\therefore \frac{V_- - V_{out}}{R_2} = g_m V_- \quad \text{or} \quad \frac{V_{out}}{R_2} = V_- \left(\frac{1}{R_2} - g_m \right)$$
$$\text{or } V_- = V_0 / (1 - g_m R_2)$$



CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L 22 / Slide 16

$$\text{Also } I_1 = \frac{V_{in} - V_-}{R_1} = \frac{V_{in}}{R_1} - \frac{V_{out}}{R_1(1 - g_m R_2)}$$

$$I_2 = \frac{V_- - V_{out}}{R_2} = \frac{V_{out}}{R_2(1 - g_m R_2)} - V_{out}$$

$$= \frac{V_{out}}{R_2} \left[\frac{1}{1 - g_m R_2} - 1 \right] = \frac{V_{out}}{R_2} \cdot \frac{g_m R_2}{1 - g_m R_2}$$

$$= V_{out} \frac{g_m}{1 - g_m R_2}$$

Equating $I_1 = I_2$

$$\frac{V_{in}}{R_1} - \frac{V_{out}}{R_1} \cdot \frac{1}{(1 - g_m R_2)} = \frac{g_m}{1 - g_m R_2} \cdot V_{out}$$



CDEEP
IIT Bombay

EE 618 L 22 / Slide 17

$$\therefore V_{in} = \frac{1 + g_m R_1}{1 - g_m R_2} V_{out}$$


$$\text{or } \frac{V_{out}}{V_{in}} = \frac{1 - g_m R_2}{1 + g_m R_1}$$

If $g_m R_2$ & $g_m R_1 \gg 1$

$$\text{then } \frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1}$$

Same as OPAMP
based Amplifier.

Fully Differential OPAMP

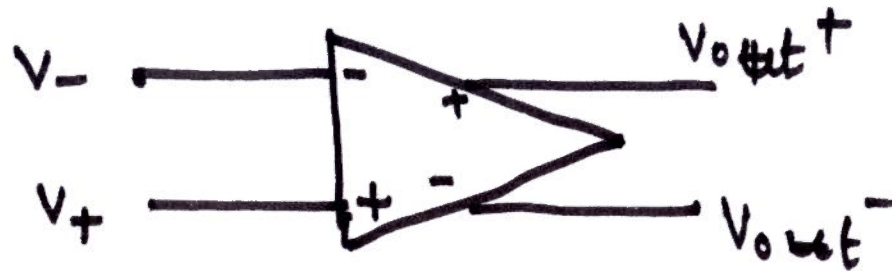

CDEEP
IIT Bombay

EE 618 L 22 / Slide 18

Fully differential (outputs) Amplifiers have certain advantages over Single ended OPAMPs.


1. Larger Output Swings as V_{out}^+ & V_{out}^- are independently handled
2. May result in Better or Superior Frequency performance as 'No' Miller Capacitance is used



CDEEP
IIT Bombay

EE 618 L 22 / Slide 39

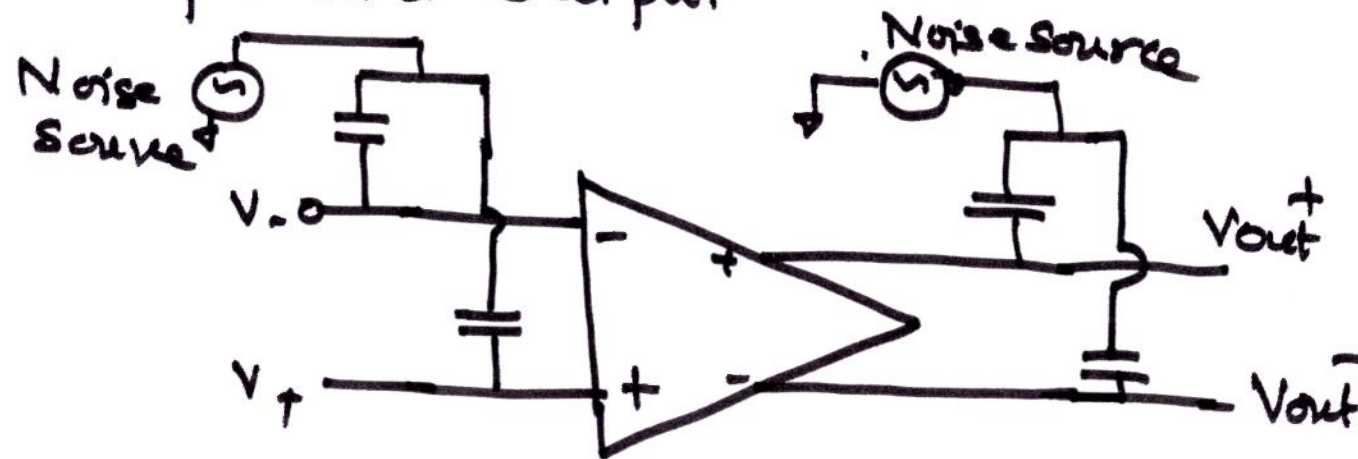The biggest advantage of fully Differential System is Rejection of Noise overriding at parasitic capacitances both at the Input and output.



$$V'_- = V_- + V_N \quad , \quad V'_+ = V_+ + V_N$$

$$\therefore V_+^+ - V_-^+ = V_+ - V_-$$

Same way $V_{out}^+ - V_{out}^- = V_{out}^+ - V_{out}^-$



CDEEP
IIT Bombay

(20)

EE 618 L 22 / Slide 4

However to achieve these better properties we need to create a 'COMMON MODE FEEDBACK' circuit (CMFB) which maintains

For Fully Differential OPAMP, the Open-Loop Gain (DC) A_{OLDC} is


$$A_{OL} = \frac{V_{out}^+ - V_{out}^-}{V_+ - V_-}$$

If we have single-ended OPAMP, then

$$A_{OL} = \frac{V_{out}^+}{V_+ - V_-}$$

Hence if we only consider one of the output V_+ in fully differential case

and use -ve feedback similar to that

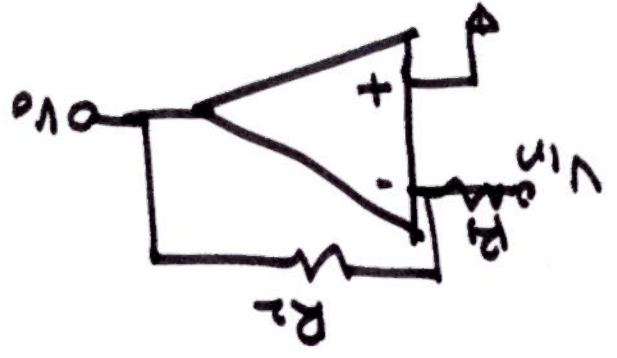

$$A_{oCL} = -\frac{R_2}{R_1}$$

$$A_{oOL} = -\frac{V_o}{V_{in}}$$

we use in single-ended OPAMP based amplifier.

Here we invoke the rule that

R_{in} is very very large, or to

say currents don't enter in OPAMP for -ve or +ve inputs, then

we get $V_- = V_+$

extending this to differential case we can say $V_+ = -V_-$






CDEEP
IIT Bombay

(22

EE 618 L 22 / Slide 5

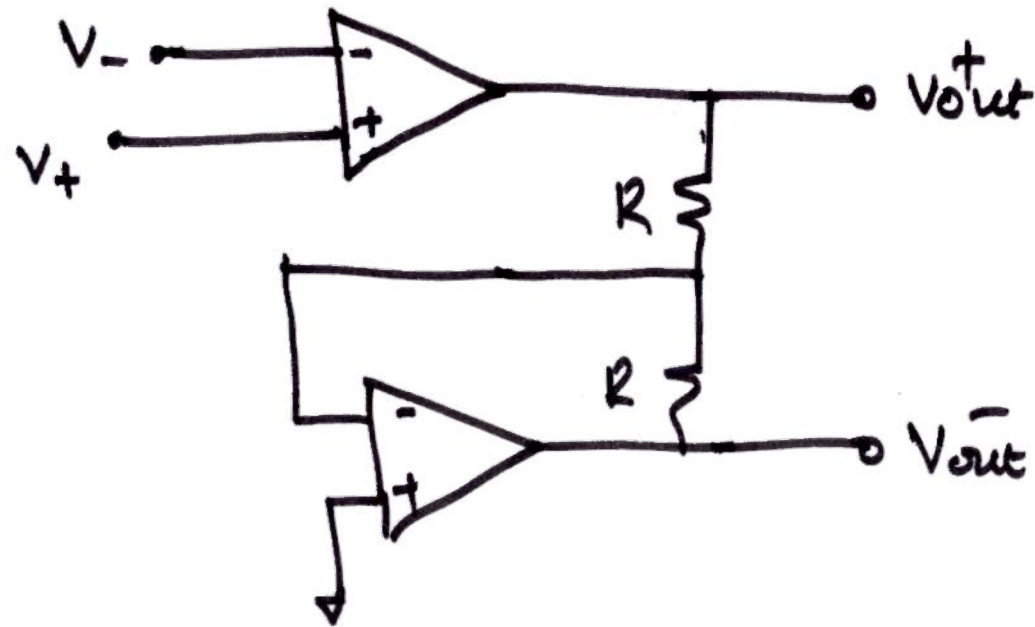This is equivalently saying, a Differential Amplifier can be realised by two single ended Amplifiers



Due to difference in Input connectivity in two OPAMPs, the Phase Margins for two Differs a lot and hence Bandwidth observed for this case is very much limited.