
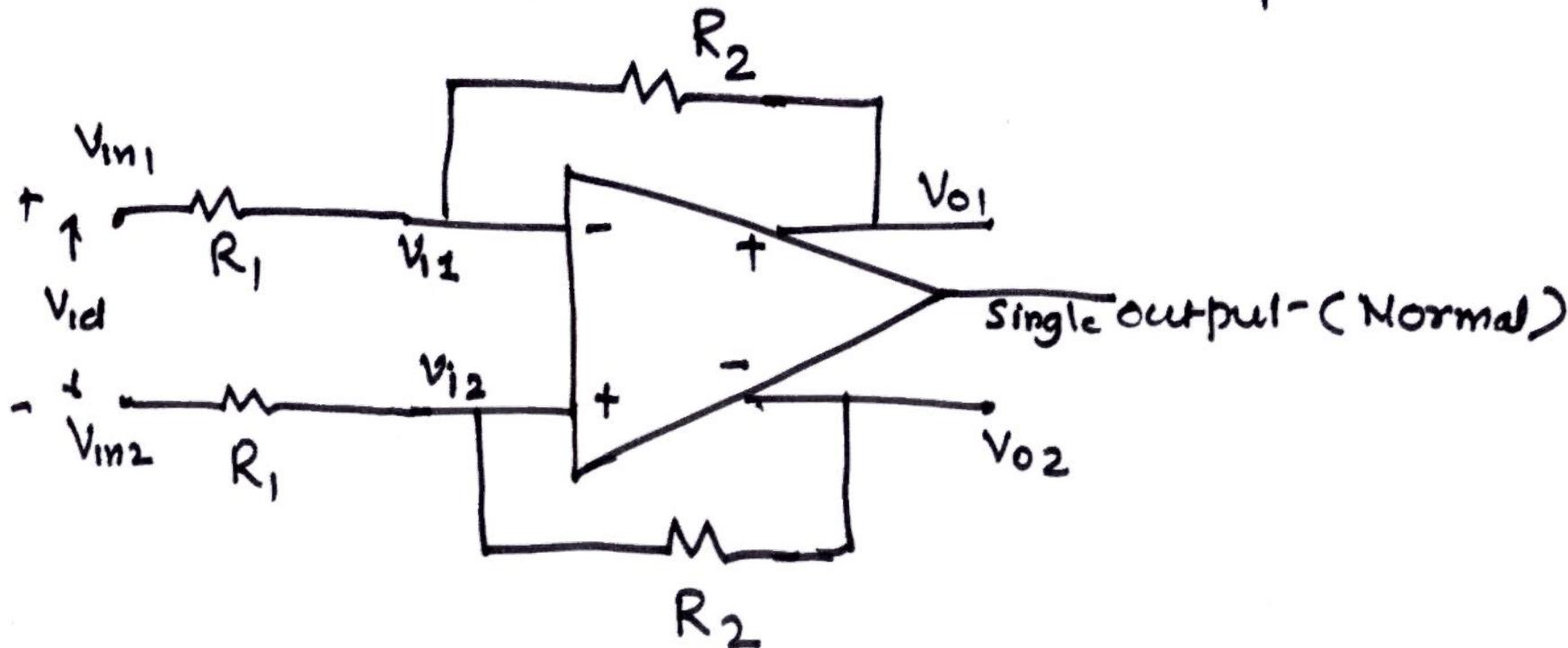


Fully Differential OPAMP

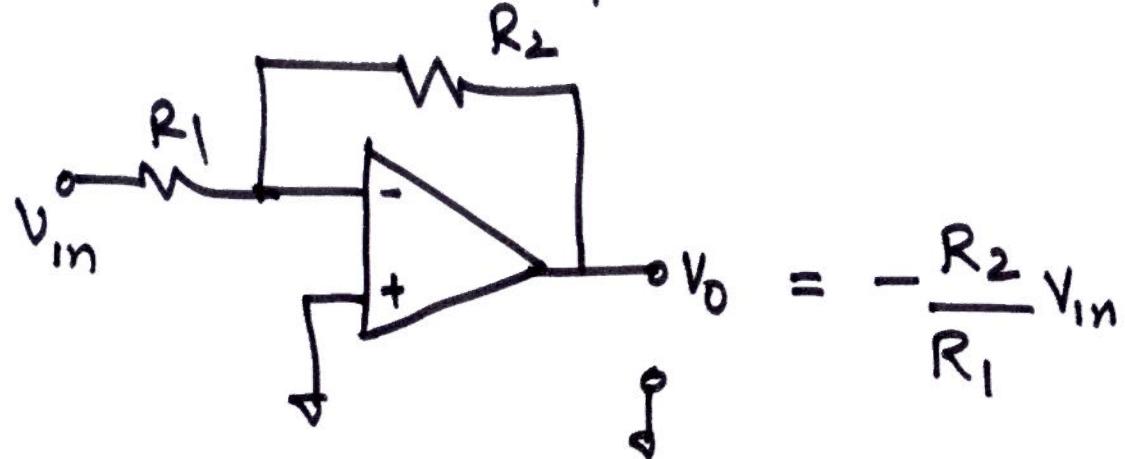It's generally operated with Balance Input and produces Balance Output



For single output OPAMP as Amplifier is



$$V_{ocommon} = \frac{V_{omax} + V_{omin}}{2}$$


i.e. $V_{OCM} = 0$ If $V_{omax} = -V_{omin}$



In case of Balanced (Symmetric) Fully Differential System, V_{o1} & V_{o2} look like :



CDEEP
IIT Bombay


EE 618 L 23 / Slide 2

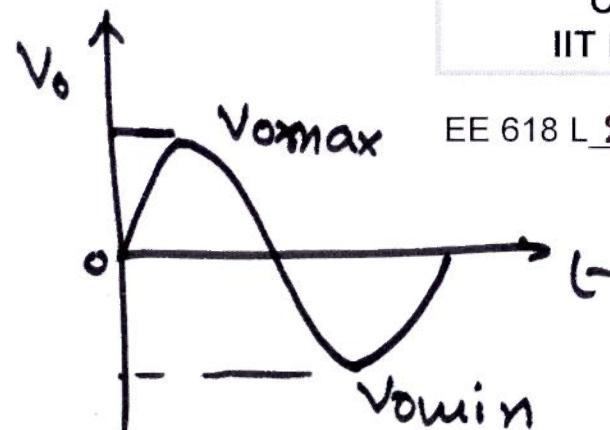

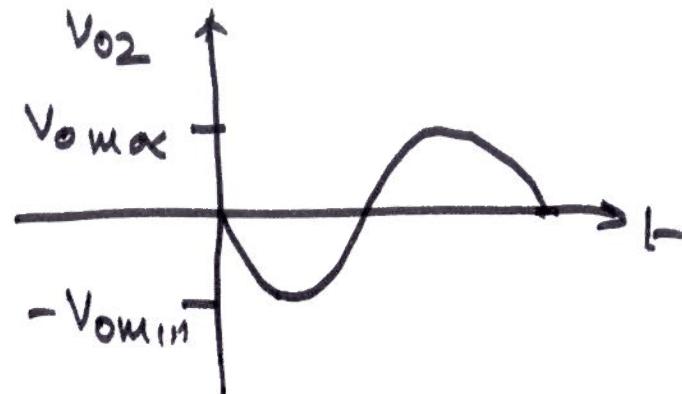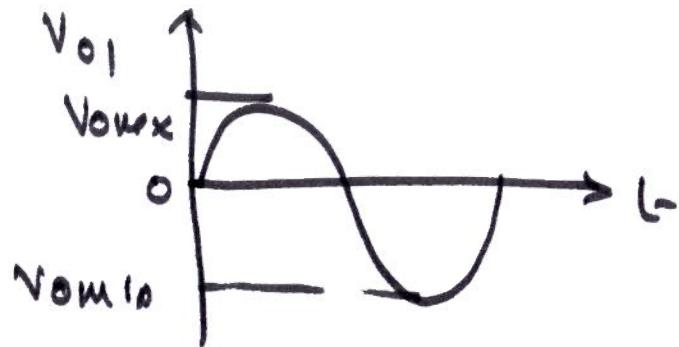


CDEEP
IIT Bombay

EE 618 L 23 / Slide 3

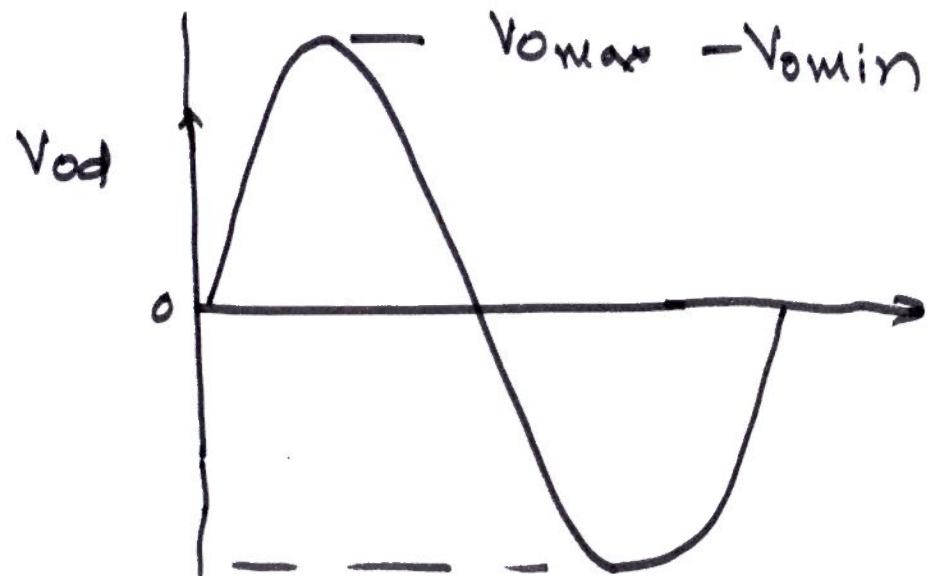

Difference Mode
Output

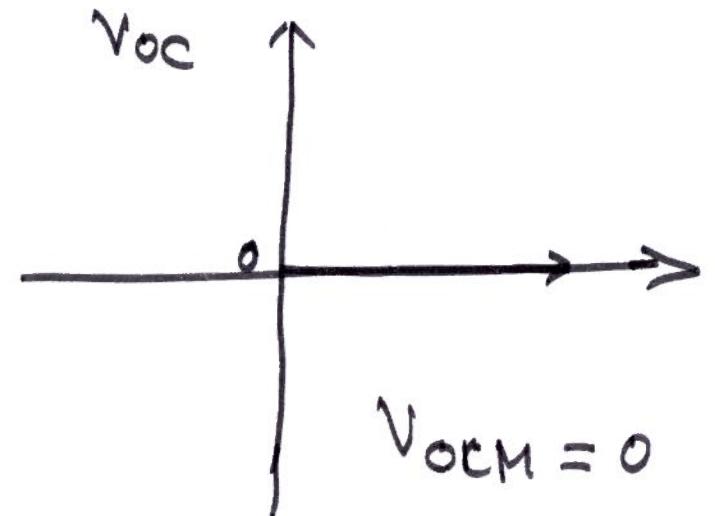


$V_{ocm} = 0$
If V_{omax}
 $= -V_{omin}$

Common Mode
Output

We may need Amplifier with

① Higher Gain

② Higher SNR (Signal to Noise Ratio)

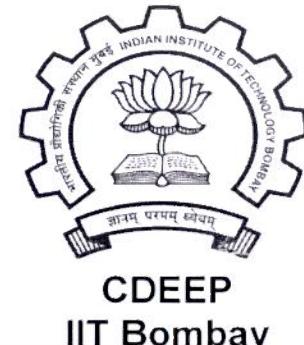

EE 618 L 23 / Slide 04

where $\text{SNR} = \frac{\text{Max. Signal Output Power} (\sqrt{V_{\text{sigm}}/2})}{\text{Output Noise Power} (\bar{V}_{\text{ON}}^2)}$

where $\bar{V}_{\text{ON}}^2 \text{ (Single ended)} = \square (1 + \frac{R_2}{R_1})^2 4 k T R_1 f_N$

$$\bar{V}_{\text{ON}}^2 \text{ (Full Differential)} = 2 (1 + \frac{R_2}{R_1})^2 4 k T R_1 f_N$$


$$V_{\text{signal (peak)}} \text{ for } \blacksquare \text{ Single ended} = V_{\text{omax}} - V_{\text{omin}}$$

$$\therefore F. \text{ Differential} = 2 (V_{\text{oxm}} - V_{\text{omin}})$$

Thus SNR of Fully Differential Amplifier is Twice that of Single output amplifier.

We can model the Input side of

Fully Differential Amplifier (FDA) as

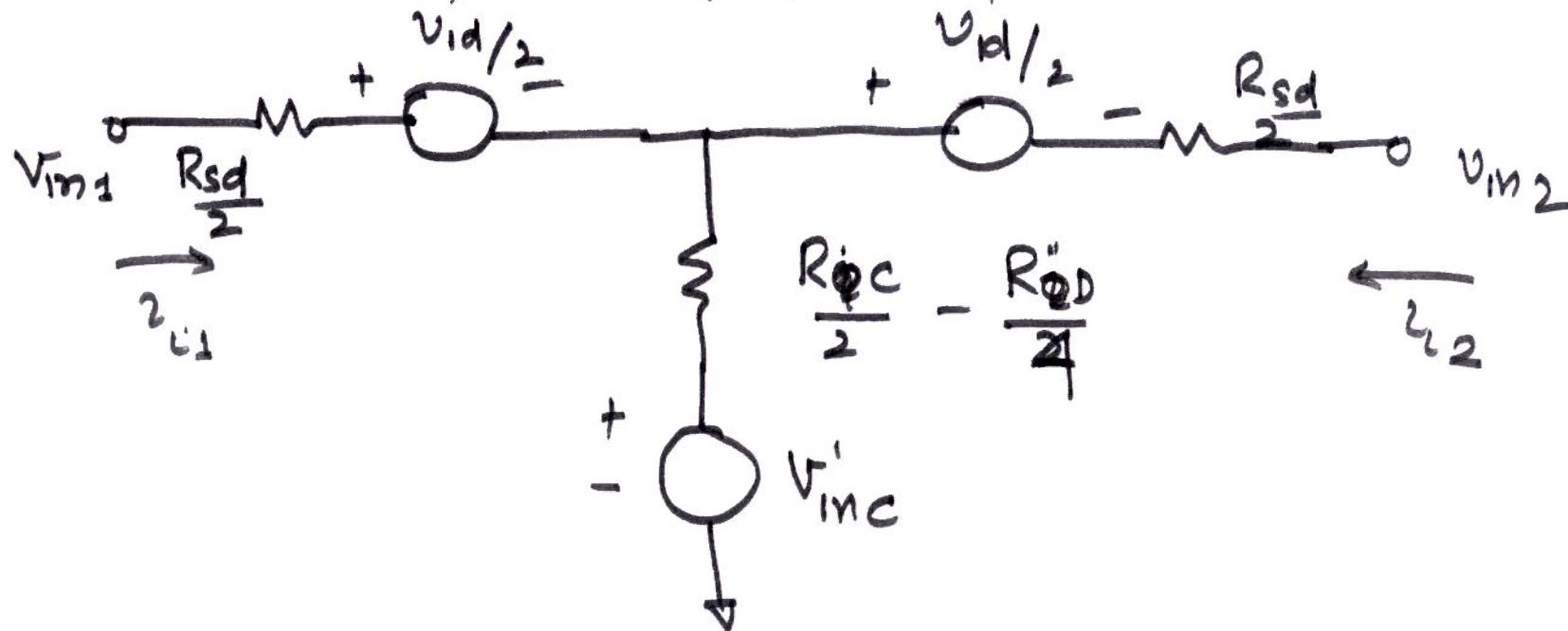

CDEEP
IIT Bombay

EE 618 L 23 / Slide 05


COMMON MODE FEEDBACK (CMFB)

For fully Differential Amplifier with

need of Higher Gains, we use

Current Source Loads instead of Diode Connected Loads.

EE 618 L 28 / Slide 06

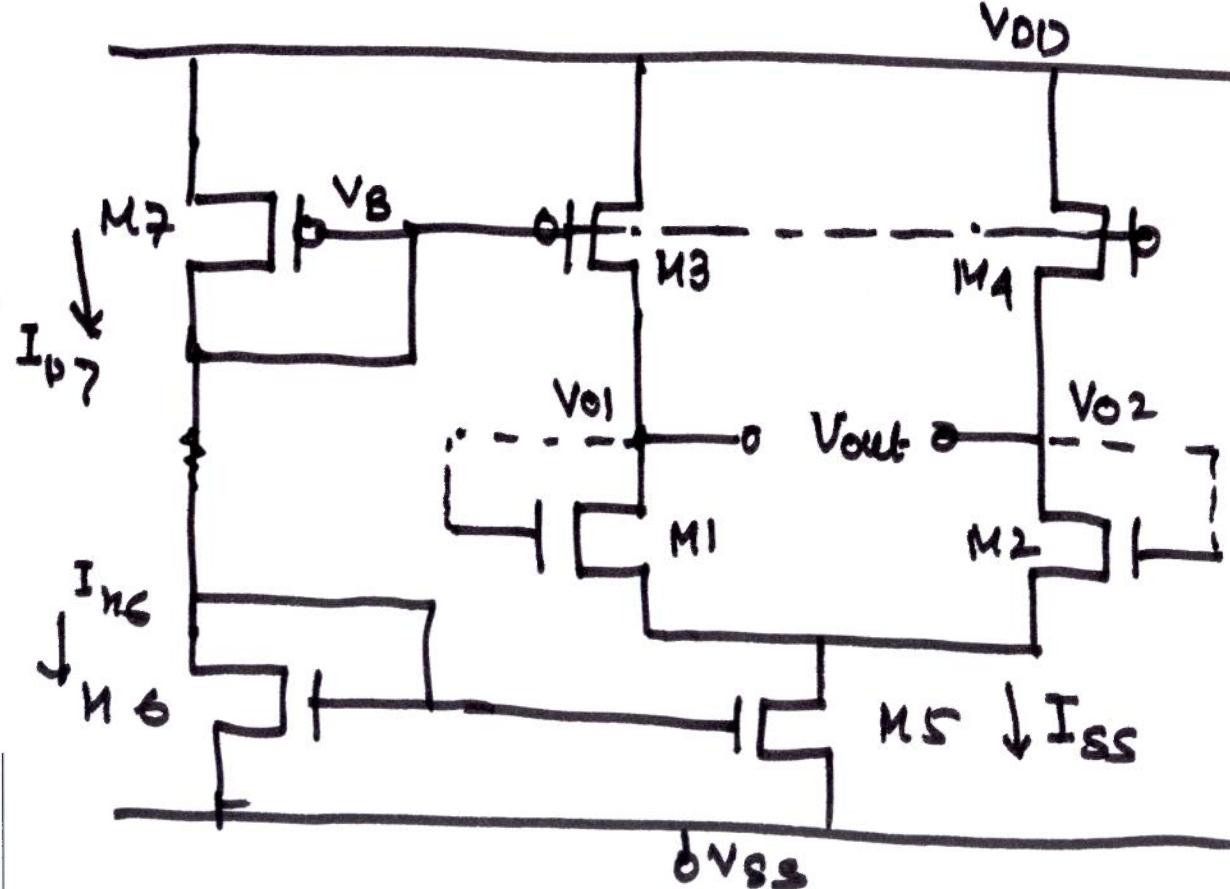

$$\begin{aligned}V_{in1} &= V_{O1} \\V_{in2} &= V_{O2}\end{aligned}$$

Then :

$$V_{out} = V_{O1} - V_{O2}$$

$$\frac{V_{id}}{2} = \frac{(V_{in1} - V_{in2})}{2}$$

$$\frac{V_{ic}}{2} = \frac{V_{in1} + V_{in2}}{2}$$

For Differamp, with M_1 & M_2 identical,

$$I_{DS1} = I_{DS2} = \frac{I_{SS}}{2} \quad \left(= \frac{I_{DS_{CE}}}{2} \right)$$

Since we have connected inputs to outputs

$$\therefore V_{CM} = \frac{I_{SS}}{2} \cdot (\gamma_{O3} || \gamma_{O1}) = \frac{I_{SS}}{2} (\gamma_{O4} || \gamma_{O2})$$

However if γ_{O3} is governed by I_{DS_7} (same as γ_{O4}) and γ_{O1} by I_{DS_6} (n -mirror), then issue may come that, in case M_6 & M_7 are generating n -mirror current I_{SS} and γ_{O3} ($\approx \gamma_{O4}$) created by M_6 , are not generating $I_{DS_6} = I_{DS_7}$

Then we have two cases $I_{DS_{3,4}} > \frac{I_{SS}}{2}$ or $I_{DS_{3,4}} < \frac{I_{SS}}{2}$



Case 1: If $I_{DS_{3,4}} > \frac{I_{SS}}{2}$

i.e. $I_p = I_{DS_7}$ is larger than $I_n = I_{DS_5} = I_{SS}$

Then $(I_p - I_n)$ current flows in $R_{out_7} \parallel R_{out_5}$


creating a voltage, which may not be small

For $I_{DS_{3,4}} > \frac{I_{SS}}{2}$, the natural cas will be


to restore $I_{DS_{3,4}} = \frac{I_{SS}}{2}$

Which means V_{O1} & V_{O2} to be same as normal cas,
currents in M_3 & M_4 must reduce. This may
bring these transistors Out of Saturation

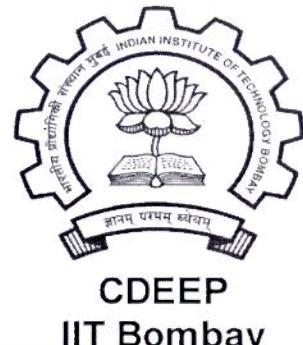This may reduce R_{O3} , R_{O4} & hence
fall in Gain



EE 618 L 23 / Slide 08

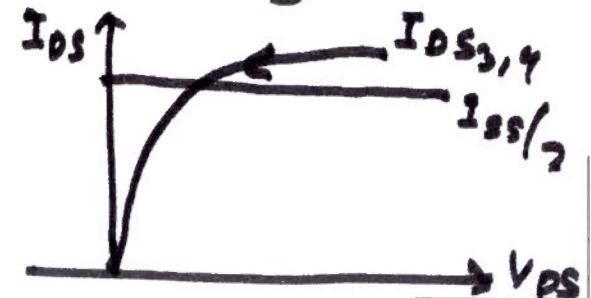


$$\text{Case II : } I_{DS_{34}} < \frac{I_{SS}}{2}$$

Now I_{SS} is supplied by MS.

If $I_{DS_{34}}$ is smaller, then MS must supply smaller current to restore

$$I_{DS_{3,4}} = \frac{I_{SS}}{2}$$

This may bring out MS from Saturation.

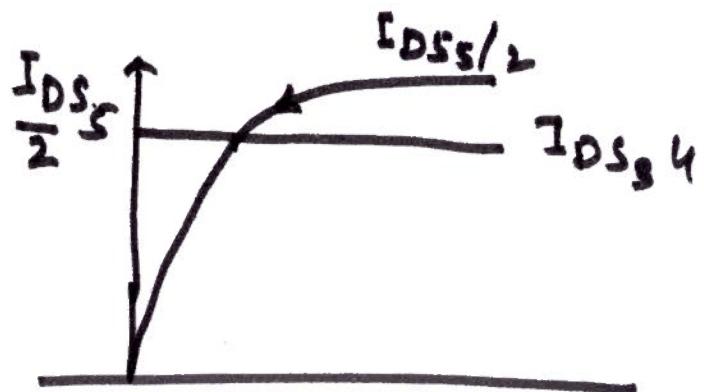

Reduction in R_{DS} of MS will reduce CMRR as common mode gain will Increase



Average of OPAMP outputs is termed
of Common-Mode Output

$$V_{CM} = \frac{V_o^+ + V_o^-}{2}$$


If $V_{DD} = | -V_{SS} |$ & $V_o^+ \rightarrow V_{DD}$ & $V_o^- \rightarrow V_{SS}$
 $= 2.5V$

$$\text{Then } V_{CM} = \frac{V_{DD} + V_{SS}}{2} = \frac{2.5 - 2.5}{2} = 0$$

But if $V_{DD} = 5$ & $V_{SS} = 0$ $V_{CM} = 2.5V$

It is necessary that for FD Amplifier to be
stable, just Differential Feedback is not
good enough but one needs Common Mode
Feedback. This allows a fixed value of V_{CM} .


Typical Common Mode Feedback works
Like

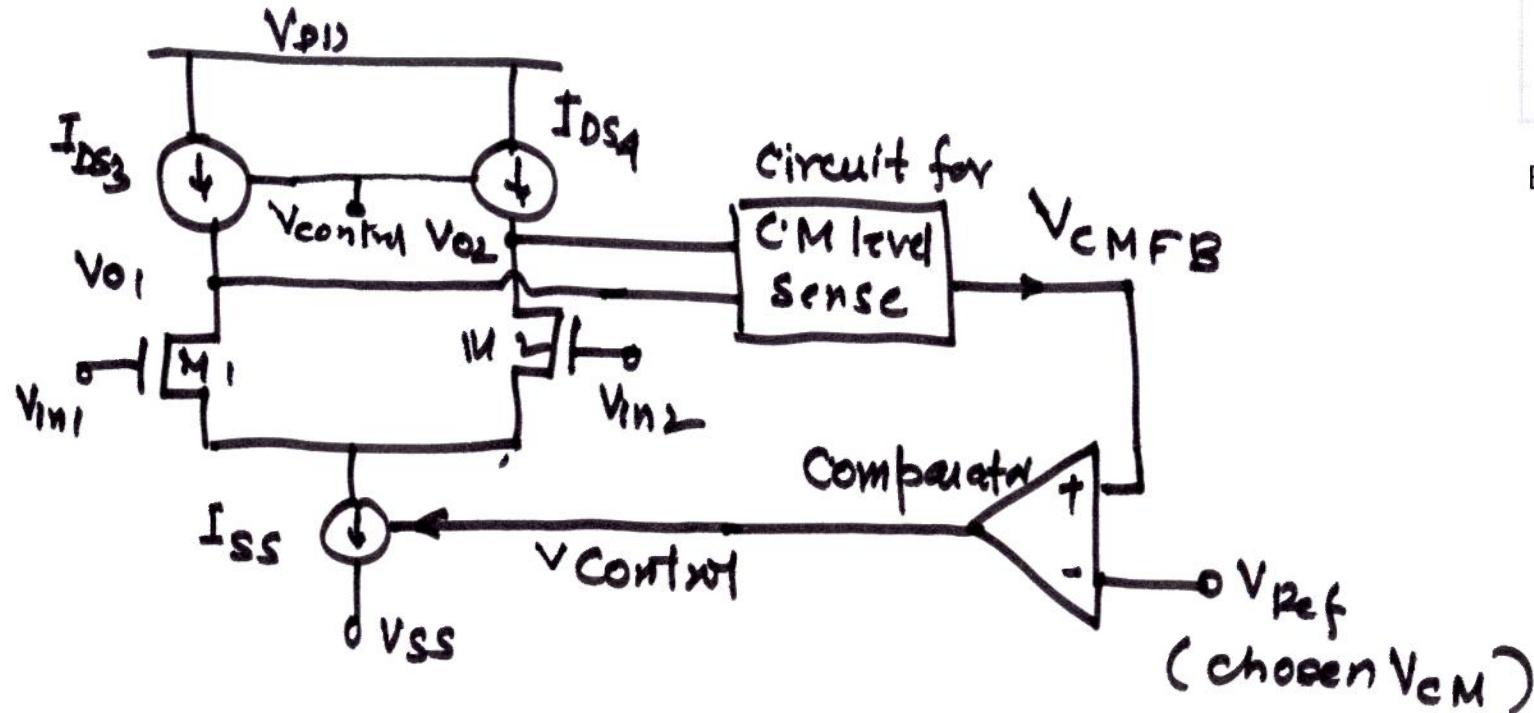

We sense V_{o1} and V_{o2} and generate V_{CMFB} .
This is compared with Set V_{CM} (V_{Ref}) and
depending upon $V_{CMFB} >$ or $< V_{CM}$ we increase
or decrease bias for Tail Current Source I_{ss} .



A CMFB Circuit Using CMOS technology

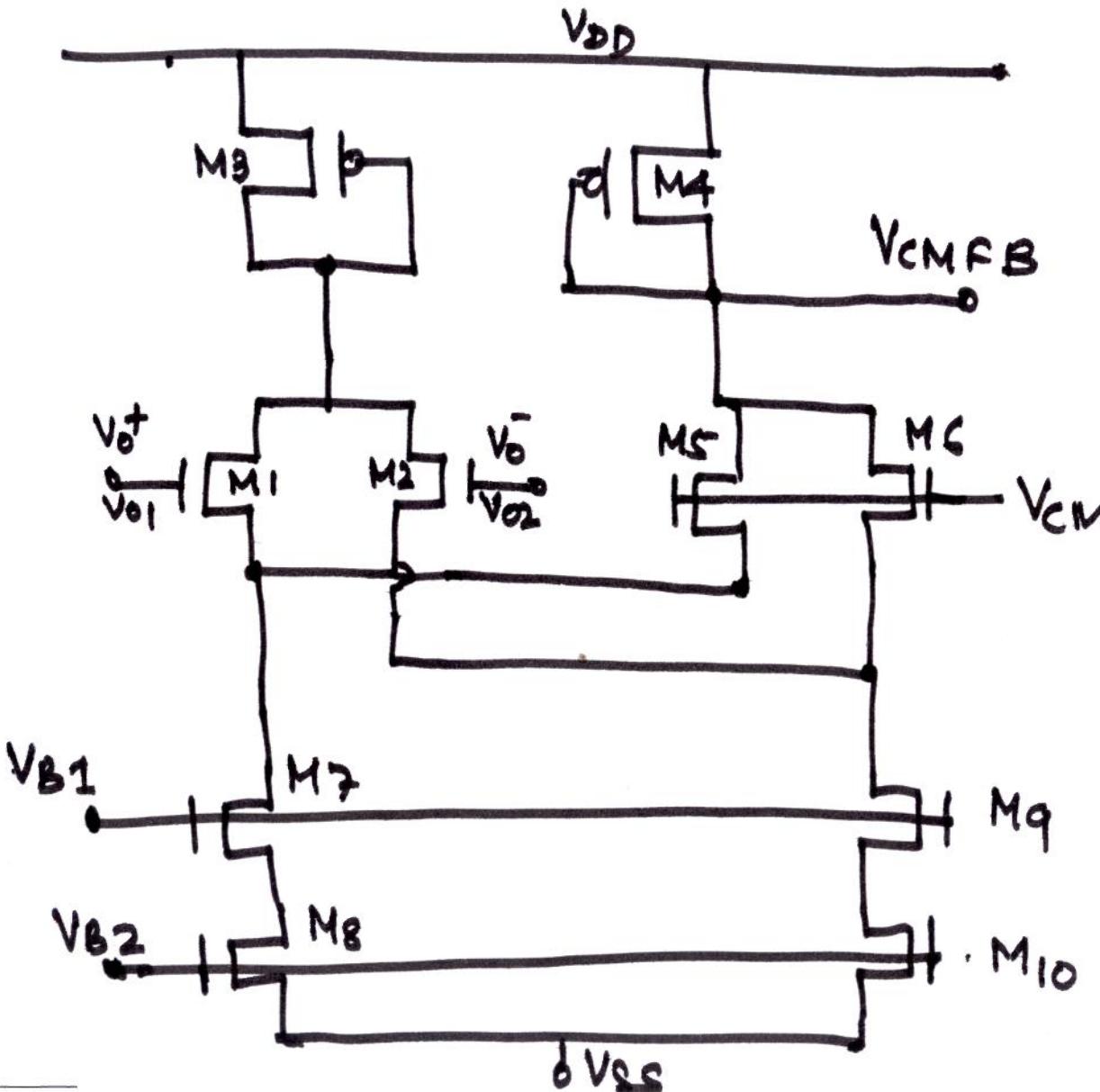

M_7 to M_{10}
are providing
constant current
sources

- ① V_o^+ & V_o^- are such that av. value $> V_{CM}$
- ② V_o^+ & V_o^- are such that their av. value $< V_{CM}$.



CDEEP
IIT Bombay

EE 618 L 23 / Slide 13


"NOISE"

1. Concept
2. Types of Noise
3. MOS MODELS FOR NOISE
4. Noise evaluation in Circuits.

Noise:- Any Unwanted or Undesired Signal couples with Desired Signal is termed as Noise.

"Noise is generated due to a Random Process and limits the Minimum Signal (Desired) level that a Circuit can process with reasonable but acceptable Quality."

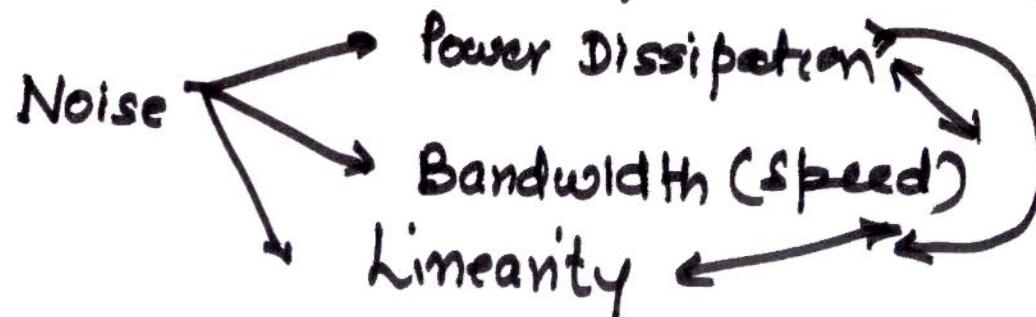In Analog Circuit the Design Trade-off is between




EE 618 L28 / Slide 14



If we have Signal $x(t)$, which is periodic
Then we can deterministically
say that at $t=t_1$

$$x(t) = x(t_1)$$

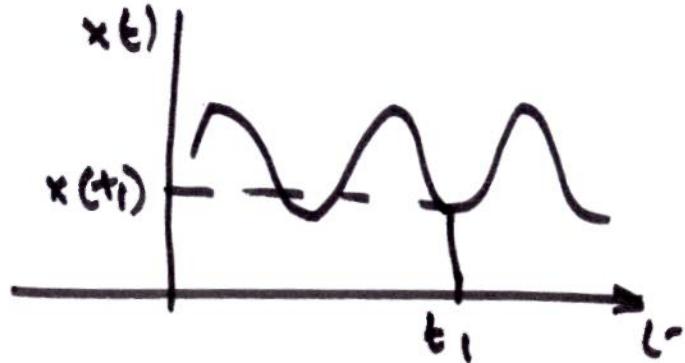

EE 618 L 23 / Slide 15


However if the signal is random in nature
we can predict $x(t_1)$ or $x(t_2)$. We then say
that Signal is 'Noise Signal'.



'Correlated Noise' ??

It is interesting that most noise sources show constant average power over a period. i.e.


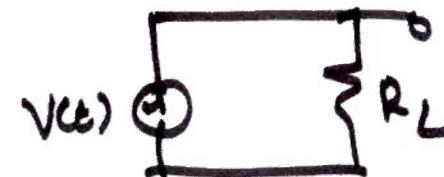
$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{+T/2} \frac{v^2(t)}{R_L} dt$$



EE 618 L 23 / Slide 16

$$P = \frac{v^2(t)}{R_L}$$

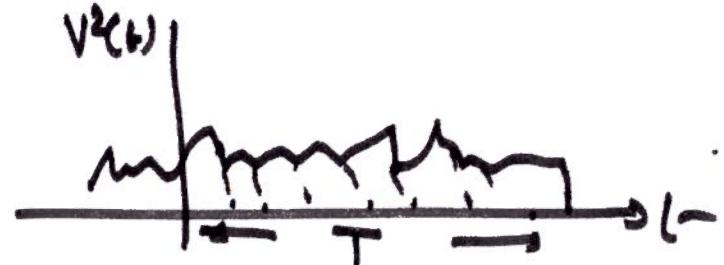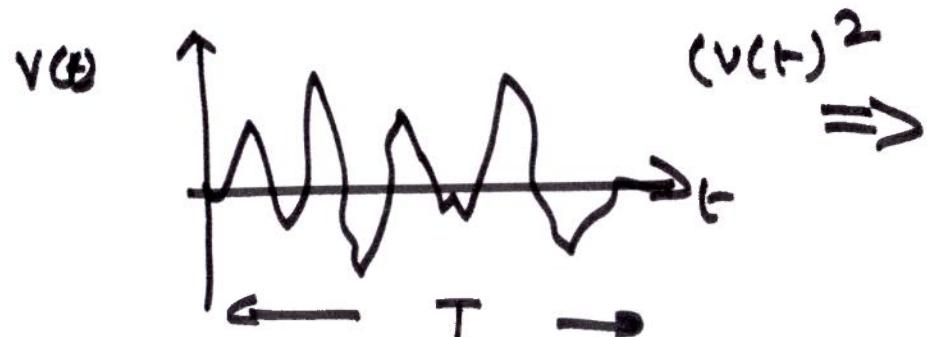That is averaging is done for long period of time.



$\sqrt{P_{av}}$ = Voltage which is called Noise (rms) Voltage / load.




CDEEP
IIT Bombay

Concept of Noise Spectrum

If Noise av. power is defined in frequency domain, we get Noise Spectrum, which is called Power Spectral Density (PSD).

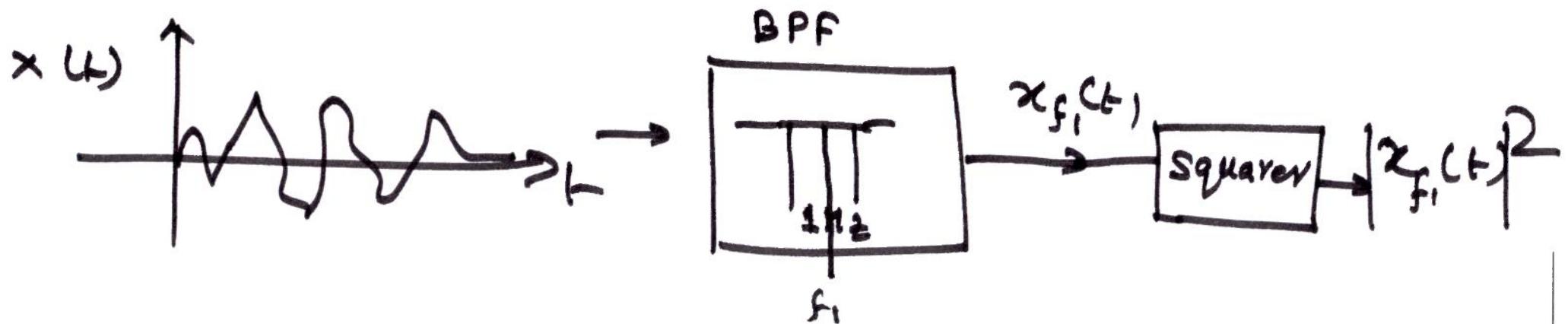PSD is defined as $S_x(f)$ of a noise waveform $x(t)$, Av. Power here is carried by $x(t)$ in bandwidth of 1 Hz, around centre frequency f .






CDEEP
IIT Bombay

EE 618 L 23 / Slide 18

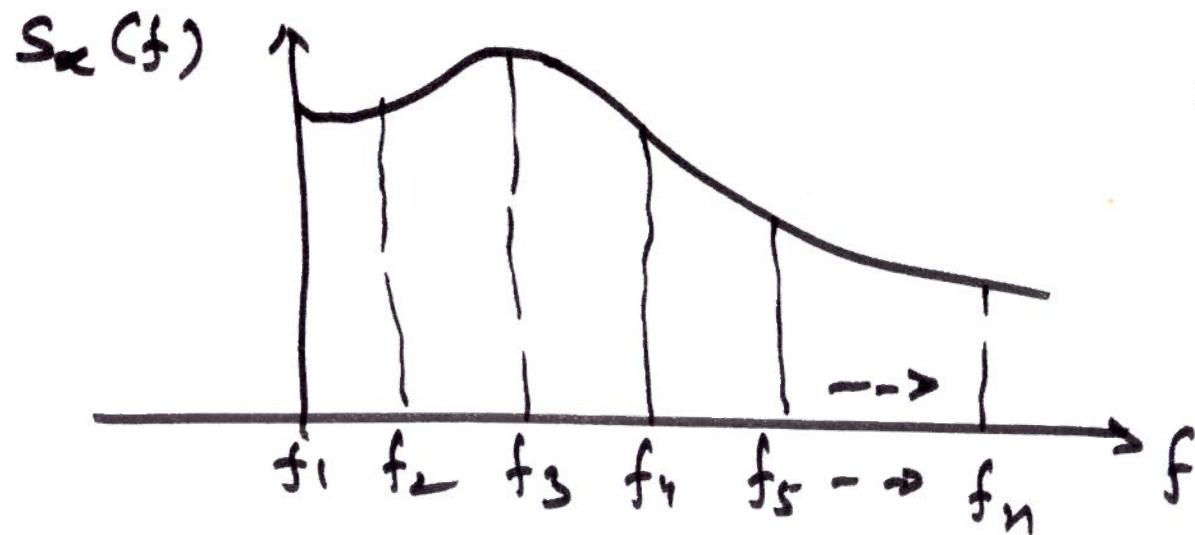Then we can evaluate Power Spectral Density $S_x(f)$
if we obtain PSD at various values of $f \Rightarrow f_1, f_2, \dots, f_n$



$S_x(f)$ is expressed
as V^2/H_z

$\therefore \sqrt{S_x(f)}$ has
units of $V/\sqrt{H_z}$

White Noise has spectrum

$$\text{S}_n(f) \xrightarrow[f]{\rightarrow} +\infty$$

Generally we limit the spectrum frequency to large values.



CDEEP
IIT Bombay


EE 618 L 28 / Slide 29

Response of PSD input to a system with Transferfn $H(f)$.

$$S_F(f) = S_n(f) \cdot |H(f)|^2$$

where $H(f) = H(s=2\pi jf)$

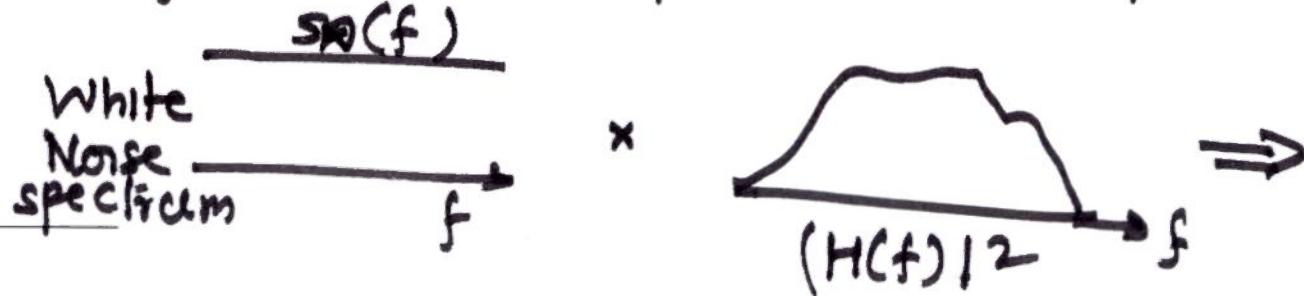If White noise spectrum is inputted to Transferfn



Two sided Symmetric spectral function can
be transformed to Single sided Sp.f'n
by doubling the magnitude



CDEEP
IIT Bombay


EE 618 L 23 / Slide 20

Distinction between Device Noise, Distortion and Interference due to signals,



CDEEP
IIT Bombay

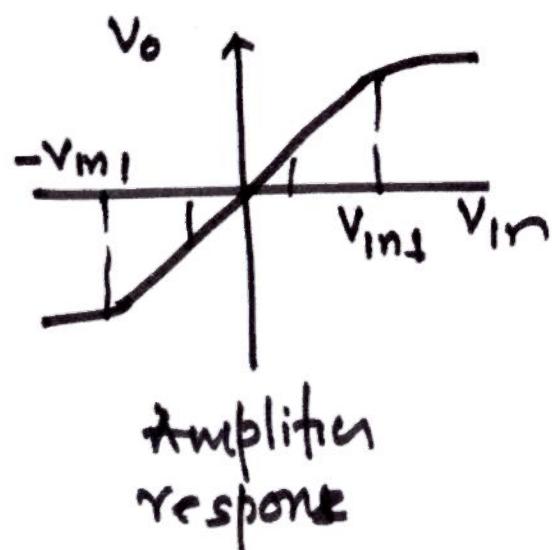1. Distortion : If the Output signal waveform departs from expected waveform which should have occurred due to Input signal operated on a Transistor function. Example :



For V_{in} between $-V_{in1}$ to V_{in1}

$$V_o = \text{Gain} \cdot V_{in} \quad \text{where Gain} = \frac{dV_o}{dV_{in}}$$


However beyond $V_{in} > V_{in1}$ or $< -V_{in1}$, $\frac{dV_o}{dV_{in}}$ keeps changing. This is due to non-linear behavior of the system. The output will then have Non-linear Distortion.

Thus Distortion occurs due to

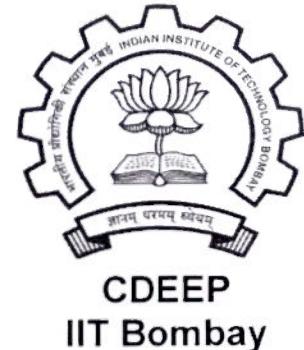1. Nonlinearities in the Transfer Function of Active Devices
 2. Distortion due passive components like cable or by Inhomogeneities in the Propagation Path.
2. Interference :

In a spectrum, nearby Signal frequency interferes in the interest band

Eg. Intermodulation in a RF receiver Input leads to Interference.



3. Noise :

Electronic Components produce combination of Three Noise spectra

i $S_n(f) = \text{const.}$ White Noise

ii $S_n(f) \propto \frac{1}{f}$ $\frac{1}{f}$ Noise

iii $S_n(f) \propto \frac{1}{f^2}$ Popcorn Noise

However we have another class of Noise which are categorised as Thermal Noise types. Overall we have number 2 Noisez :—

(a) Shot Noise (b) Johnson Noise (Most commonly called Thermal Noise)

Third type of Noise is called G-R noise and finally we have noise called kT/C noise.

