

② Shot Noise:

$$i_n = \sqrt{2q I_D \Delta f}$$

This noise occurs due to quantum nature of Electron Flow through a Potential Barrier.

Carriers exhibit average rate (DC value) of crossing, but individual carriers cross barrier as random events

In above equation I_D is the forward current in the device, and Δf is measurement bandwidth.

Clearly Shot noise $\propto \sqrt{I_D}$, but it is $\neq f(T_{\text{emp}})$

In MOSFET, Subthreshold current exhibits Shot Noise.



CDEEP
IIT Bombay


EE 618 L 24 / Slide 01

(b) Johnson Noise (Thermal Noise):

Random carrier motion (Drift, Diffusion) gives rms Noise power as

$$S_n(f) = \int_{f_1}^{f_2} kT df = kT \Delta f$$

$\therefore S_n(f) \propto T \Rightarrow$ Thermal Noise

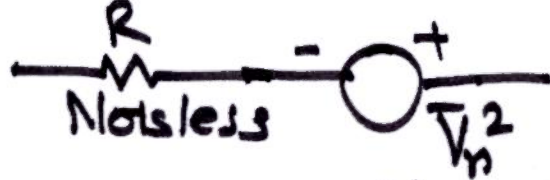A resistor can be modeled as  spectral density

$$S_v(f) = kT \Delta f = \frac{\bar{V}_n^2}{R}$$

$$\text{or } \bar{V}_n^2 = kTR \Delta f$$

If V_n is expressed in rms value & $\Delta f = 1\text{Hz}$

then $\bar{V}_n^2 = 4kTR$



CDEEP
IIT Bombay

EE 618 L 24 / Slide 02

$$\text{As } \bar{i}_n^2 = \frac{\bar{V}_n^2}{R^2}$$

Current noise source

$$\therefore \bar{i}_n^2 = \frac{4kT}{R} = 4kT \cdot G \quad (G = \frac{1}{R})$$



CDEEP
IIT Bombay

EE 618 L 24 / Slide 33

(c) $1/f$ Noise (Flicker Noise)

Due to number fluctuations occurring due to Defects, Contaminants and Interface States, one observe $1/f$ noise. Johnson invented it in 1923 is Vacuum Tubes. Exact nature is not very much known, but at low frequencies, the noise shows inverse proportion to frequency ($1/f$ behavior), and hence called $1/f$ Noise





CDEEP
IIT Bombay

EE 618 L 24 / Slide 04

(d) G-R Noise :

Generation - Recombination of Carriers in Semiconductors (Devices) results in

Statistical variation of number density,

This leads to Noise, also known as Random Telegraph Noise (RTN)

(e) Popcorn noise : Also known as Burst Noise, show $1/f^2$ dependance

A typical origin of such noise is seen in channel current of a MOSFET.

Discrete modulation of Channel Current by capture and Emission of Carriers in the Channel leads to Popcorn Noise

Two Types of Noise can be

[A] "Man Made Noise"

- Signal coupling
- Substrate coupling
- Finite Power Supply Rejection

Possible methods of Eliminations

- (i) Fully Differential Circuits
- ii) Proper Layout of the Circuit

[B] "Electronic Noise due to Devices"



CDEEP
IIT Bombay

EE 618 L 24 / Slide 05



CDEEP
IIT Bombay


EE 618 L 24 / Slide 06

Noise due to Components



CDEEP
IIT Bombay

EE 618 L 24 / Slide 07

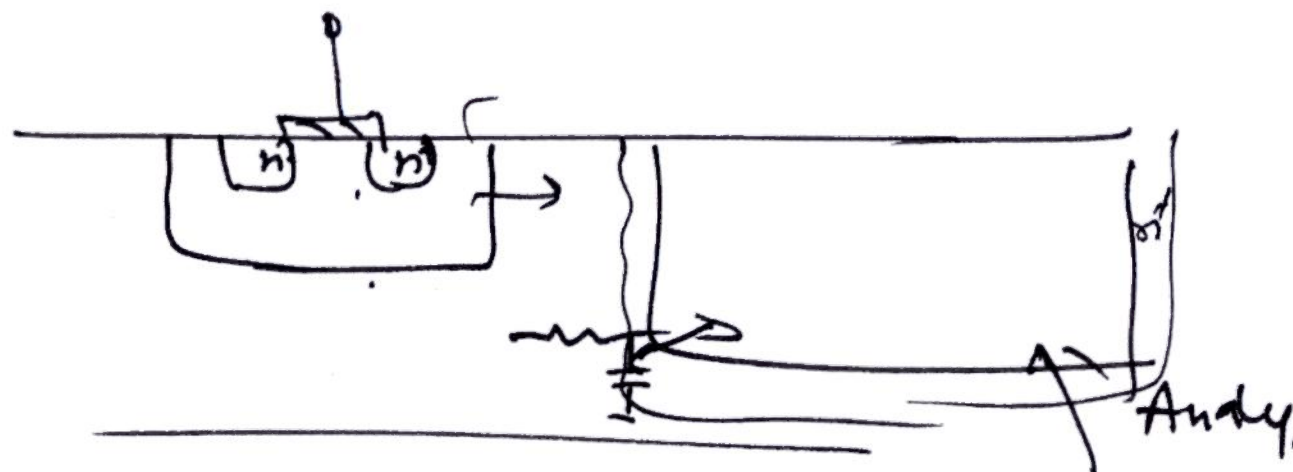

$$Q = \frac{\Delta T}{\Delta P}$$

Effects of Electronic Noise on Circuits



CDEEP
IIT Bombay

EE 618 L 24 / Slide 08

(a) Minimum Detectable / Processed Signal is limited

(b) Noise Directly shows Trade-off with Power Dissipation and Speed

— Low Noise requirement dictates the use of Large Capacitors and or large $I_m \Rightarrow$ Both leads to High Power Dissipation

(c) With Scaledown technology, Power Supply voltage also decreases, thus Reducing SNR.




Hence Design of Low Power (Low Voltage), precision circuit has strong dependance on Electronic Noise

Thermal Noise due to Resistor



CDEEP
IIT Bombay

EE 618 L 24 / Slide 09

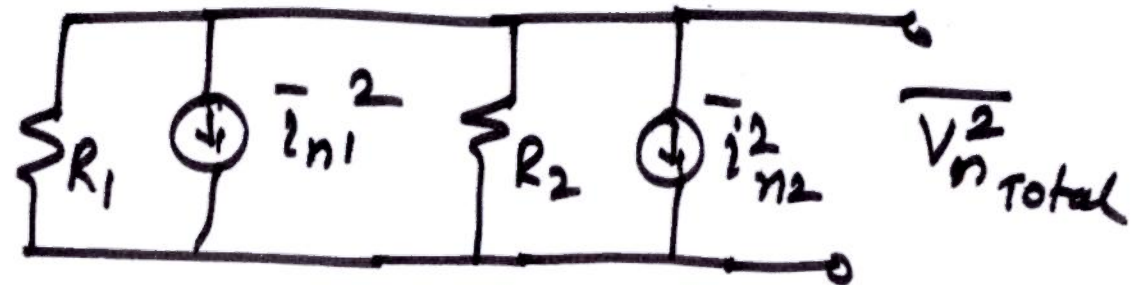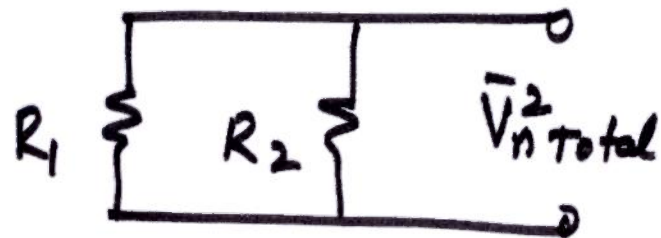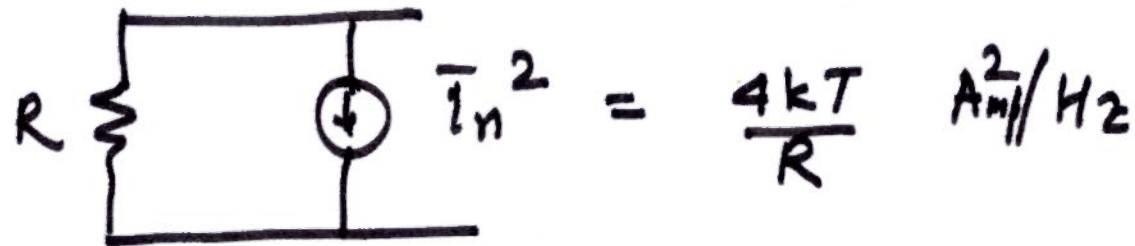

$$\bar{i}_{n\text{Total}}^2 = \bar{i}_{n1}^2 + \bar{i}_{n2}^2$$

$$\bar{V}_{n\text{Total}}^2 = \bar{i}_{n\text{Total}}^2 \cdot (R_1 || R_2)^2 = \bar{i}_{n\text{Total}}^2 \left(\frac{R_1 R_2}{R_1 + R_2} \right)^2$$

$$= 4kT \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = 4kT (R_1 + R_2) / R_1 R_2$$

$$\therefore \overline{V_{n\text{Total}}^2} = \frac{4kT(R_1 + R_2)}{R_1 R_2} \cdot \frac{(R_1 R_2)^2}{(R_1 + R_2)^2}$$

$$\overline{V_{n\text{Total}}^2} = 4kT (R_1 \parallel R_2)$$





CDEEP
IIT Bombay

EE 618 L 24 / Slide 19

Properties of Thermal Noise

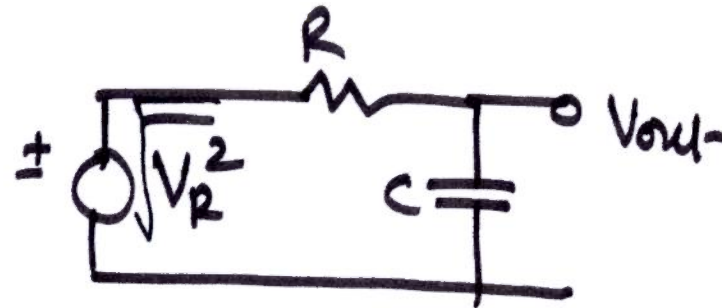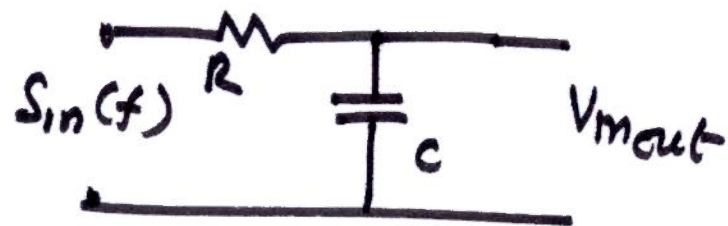- i Every Conductor is source of Thermal Noise
- ii This Noise is not dependent on DC current.
- iii Instantaneous value is Indeterministic
- iv Thermal Noise has Average Power.



CDEEP
IIT Bombay

EE 618 L 24 / Slide 11

$$\frac{V_{out}}{V_R} = \frac{1}{1 + RCs} = \text{Transfer } F^n$$

$$\text{or } S_{out}(f) = S_R(f) \left| \frac{V_{out}}{V_R}(j\omega) \right|^2$$

$$= 4kTR \frac{1}{4\pi^2 R^2 C^2 f^2 + 1}$$

$$\therefore P_n(out) = \int_0^\infty S_{out}(f) df$$



CDEEP
IIT Bombay

EE 618 L 24 / Slide 12

$$\therefore P_{out} = \int_0^{+\infty} \frac{4kTR}{1 + 4\pi^2 R^2 C^2 f^2} df$$

$$= \int_0^{\infty} \frac{4kTR df}{1 + (2\pi RCf)^2}$$

$$x = 2\pi RCf$$

$$\text{or } dx = 2\pi RC df \quad \text{or } df = \frac{dx}{2\pi RC}$$

$$\therefore 4kTR df = \frac{4kTR dx}{2\pi RC}$$

$$= \frac{2kT}{C} \cdot \frac{1}{\pi} dx$$

$$\therefore P_{out} = \int_0^{\infty} \frac{2kT}{C} \cdot \frac{1}{\pi} \frac{dx}{1+x^2} = \frac{2kT}{C} \cdot \frac{\pi}{2\pi} = \frac{kT}{C} \text{ (V}^2\text{)}$$



$\neq f(R)$



CDEEP
IIT Bombay



EE 618 L24 / Slide 13
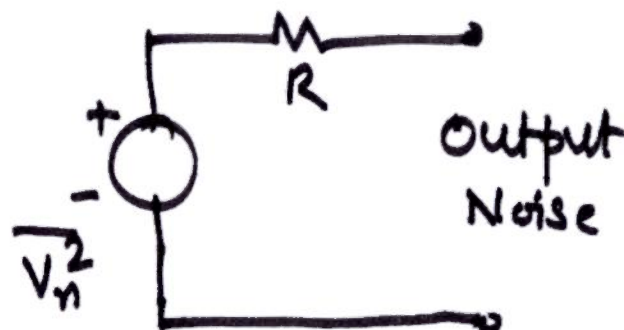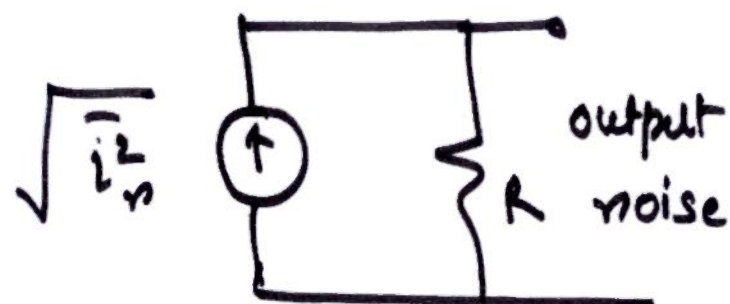
$$\overline{V_n^2} = 4kT \cdot R = \overline{i_n^2} \cdot R^2$$



Noise Voltage of Potential Divider

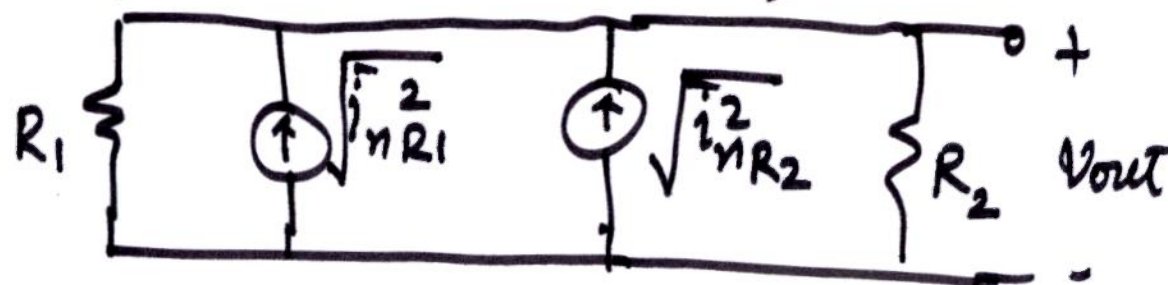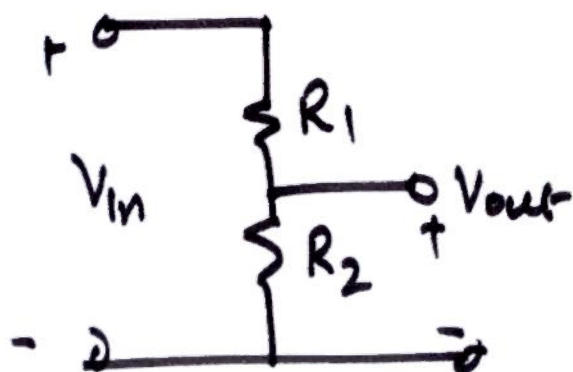Noise Eq. Ckt will be as shown (for the output node)



Evaluate noise RMS voltage at output from Bandwidth of DC to 1 kHz



CDEEP
IIT Bombay

EE 618 L 24 / Slide 14

We have:

$$\sqrt{\overline{i_{nR_1}^2}} = \sqrt{\frac{4kT}{R_1}} \quad A/\sqrt{Hz}$$

$$\sqrt{\overline{i_{nR_2}^2}} = \sqrt{\frac{4kT}{R_2}} \quad A/\sqrt{Hz}$$

$$\sqrt{\overline{V_{nR_1}^2}} = \sqrt{\overline{i_{nR_1}^2}} \cdot \frac{R_1 R_2}{R_1 + R_2} \quad V/\sqrt{Hz}$$

$$\sqrt{\overline{V_{nR_2}^2}} = \sqrt{\overline{i_{nR_2}^2}} \cdot \frac{R_1 R_2}{R_1 + R_2} \quad V/\sqrt{Hz}$$

Total RMS squared Output noise voltage over a Bandwidth f_0 is given by

$$\overline{V_{on}^2} = \int_{f_L}^{f_H} (\overline{V_{nR1}^2} + \overline{V_{nR2}^2}) df$$

then $\sqrt{\overline{V_{on}^2}} \Rightarrow \text{Voltage} / \sqrt{\text{Hz}}$

Here $f_L = 0$ $f_H = f_0$

We may at times want to know effective input noise for the divider. we have

$$\sqrt{\overline{V_{in}^2}} \cdot \frac{R_2}{R_1 + R_2} = \sqrt{\overline{V_{outn}^2}}$$

Problem $R_1 = 5k$ $R_2 = 0.5k$



CDEEP
IIT Bombay

EE 618 L 24 / Slide 15



CDEEP
IIT Bombay

EE 618 L 24 / Slide 16

$$\begin{aligned}\sqrt{i_{nR1}^2} &= \sqrt{\frac{4kT}{R_1}} = \frac{1.28 \times 10^{-10}}{\sqrt{R_1}} = \frac{1.28 \times 10^{-10}}{2.236} \\ &= \frac{5.72}{31.622} \text{ nA}/\sqrt{H_z} = 0.18 \times 10^{-9} / \sqrt{H_z}\end{aligned}$$

$$\sqrt{i_{nR2}^2} = \sqrt{\frac{4kT}{R_2}} = \frac{1.28 \times 10^{-10}}{22.36} = 0.057 \text{ nA}/\sqrt{H_z}$$

$$\frac{R_1 R_2}{R_1 + R_2} = \frac{2.5 \times 10^6}{5.5 \times 10^3} = 455$$

$$\therefore \sqrt{V_{nR1}^2} = 0.18 \times 10^{-9} \times 455 = 206.8 \text{ nV}/\sqrt{H_z}$$

$$\sqrt{V_{nR2}^2} = 0.057 \times 10^{-9} \times 455 = 25.33 \text{ nV}/\sqrt{H_z}$$

$$\begin{aligned}\overline{V_{on}^2} &= \int_0^{10^3} (4.748) \times 10^{-14} df \\ &= 47.48 \times 10^{-12} \text{ V}^2/\text{Hz}\end{aligned}$$

$$\overline{V_{on}} = 6.9 \times 10^{-6} \mu\text{V}/\sqrt{\text{Hz}}$$



CDEEP
IIT Bombay

EE 618 L 24 / Slide 17


MOSFET Noise Model

MOSFET behaves as voltage dependent Resistor and hence show Thermal Noise as noise source.



CDEEP
IIT Bombay


EE 618 L 24 / Slide 18

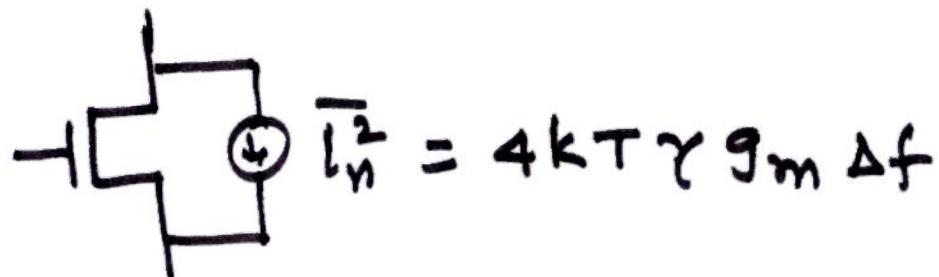

$$g_m = g_m \text{ in Sat. Mode}$$

$$\Delta f = 1 \text{ Hz normally}$$

$$\gamma = \text{Noise Coefficient}$$

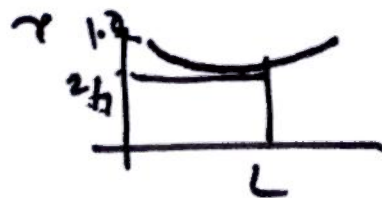

$$\text{For long channel device } \gamma = 2/3$$

$$\text{For longer channel } \gamma \rightarrow \text{Enhances}$$


In short channel case, hot carrier effects dominates

and we see γ increasing towards $2 \rightarrow 5$ or so
In reality $\gamma = 1$ for sch. case

A simple CS Amplifier noise can be now evaluated.



CDEEP
IIT Bombay

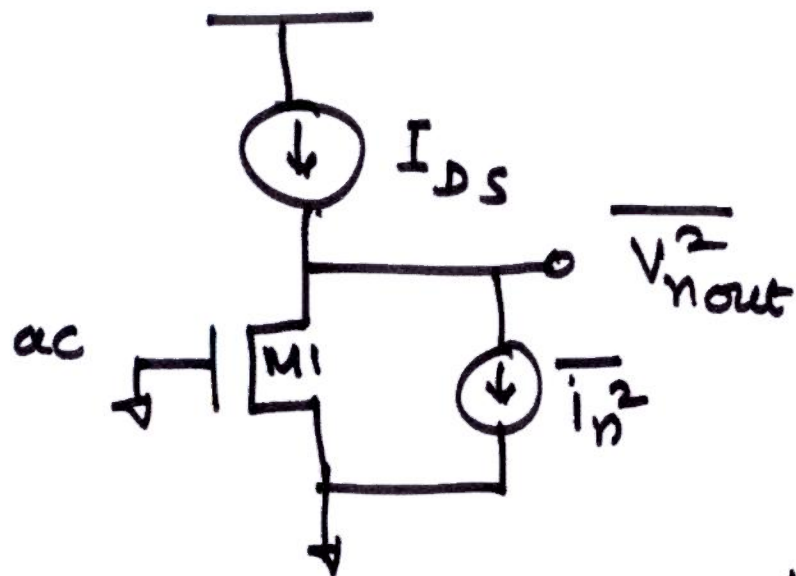

If R_{out} is output resistance of $M1$ (r_{o1}) EE 618 L 24 / Slide 19

& Current Source has $R_{out} \rightarrow \infty$
Then Noise current $\sqrt{i_n^2}$ flows through r_{o1} output resistance

$$\therefore \overline{V_{nout}^2} = \overline{i_n^2} \cdot r_{o1}^2$$

$$= 4kT \left(\frac{2}{3} g_m \right) r_{o1}^2$$

$$\text{or } \sqrt{\overline{V_{nout}^2}} = \sqrt{\frac{8}{3} kT g_m} \cdot r_{o1} \quad V/\sqrt{Hz}$$

$\therefore$ Low Noise $\Rightarrow$ low g_m , (Lower Gains)

Design Specifications :

1. DC Gain 2a. Bandwidth
- 2(b) Gain Bandwidth Product GBW
3. Input Common-Mode Range ICMR
4. Slew Rate
5. Output Load Capacitance
6. Output Voltage Swing ($V_{outmax} - V_{outmin}$)
7. Power Dissipation P_D
8. Common Mode Rejection Ratio CMRR



CDEEP
IIT Bombay

EE 618 L 24 / Slide 20