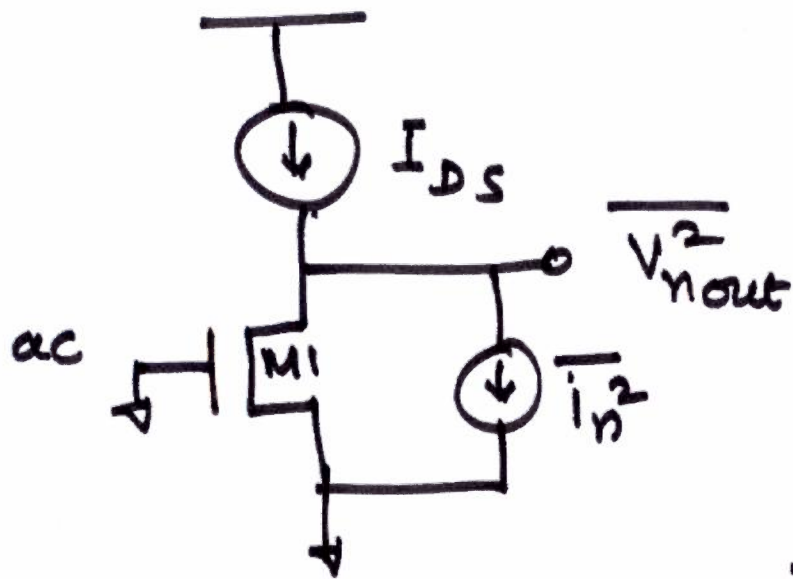




CDEEP  
IIT Bombay

A simple CS Amplifier noise can be now evaluated.



If  $R_{out}$  is output resistance of  $M1$  ( $r_{o1}$ )  
 & Current source has  $R_{out} \rightarrow \infty$   
 then Noise current  $\sqrt{i_n^2}$  flows through  $r_{o1}$  output resistance

$$\therefore \overline{V_{nout}^2} = \overline{i_n^2} \cdot r_{o1}^2$$

$$= 4kT \left( \frac{2}{3} g_m \right) r_{o1}^2$$

$$\text{or } \sqrt{\overline{V_{nout}^2}} = \sqrt{\frac{8}{3} kT g_m} \cdot r_{o1} \quad V/\sqrt{Hz}$$

$\therefore$  Low Noise  $\Rightarrow$  low  $g_m$ , (Lower Gains)

## 1/f Noise

- Famously known as Flicker Noise.
- Most Believe that this Noise is due to random carrier trapping at Interface States ( Insulator / Semiconductor Interface ) in MOS device.
- It is difficult to accurately predict the Noise Power due to 1/f Noise , as 'Interface' property is strongly dependent on Process Technology.
- This noise power is seen to follow 1/f relation with frequency.



CDEEP  
IIT Bombay

EE 618 L 25 / Slide 01



CDEEP  
IIT Bombay

EE 618 L 25 / Slide 02

- In general one models this noise by Noise Voltage source in series to Gate terminal.

- Typically it can be represented as

$$\overline{V_{n1/f}^2} = \frac{K}{C_{ox} W \cdot L} \cdot \frac{1}{f}$$

$$\Delta \quad \overline{i_{n1/f}^2} = \frac{K}{C_{ox} W \cdot L} \cdot g_m^2 \cdot \frac{1}{f}$$

- The spectral density of Flicker Noise current source is given by

$$\overline{i_{n1/f}^2} = \int_{f_1}^{f_2} \frac{K_1}{L^2} \cdot \frac{I_{DS}}{C_{ox}} \frac{df}{f}$$

$$\overline{i_{n,1/f}^2} = \frac{K_1}{L^2} \frac{I_{DS}}{C_{OX}} \ln(f_2/f_1)$$

$$\overline{i_{n,1/f}^2} = \frac{K_2}{L^2} \frac{I_{DS}}{C_{OX}} \log(f_2/f_1)$$

We also know that Thermal Noise ~~voltage~~ <sup>current</sup> in a frequency band can be written as

$$\overline{i_{n,th}^2} = 4KT \left( \frac{2}{3} g_m \right)$$

At a frequency  $f_c$  called  $1/f$  Noise corner frequency

the two noise voltages are equal

$$\text{or } 4KT \left( \frac{2}{3} g_m \right) = \frac{K}{C_{OX} W \cdot L} \cdot \frac{1}{f_c} g_m^2$$

$$\text{or } f_c = \frac{K g_m}{C_{OX} W \cdot L} \cdot \frac{3}{8KT}$$



CDEEP  
IIT Bombay


EE 618 L 25 / Slide 03.





CDEEP  
IIT Bombay

EE 618 L 25 / Slide 04

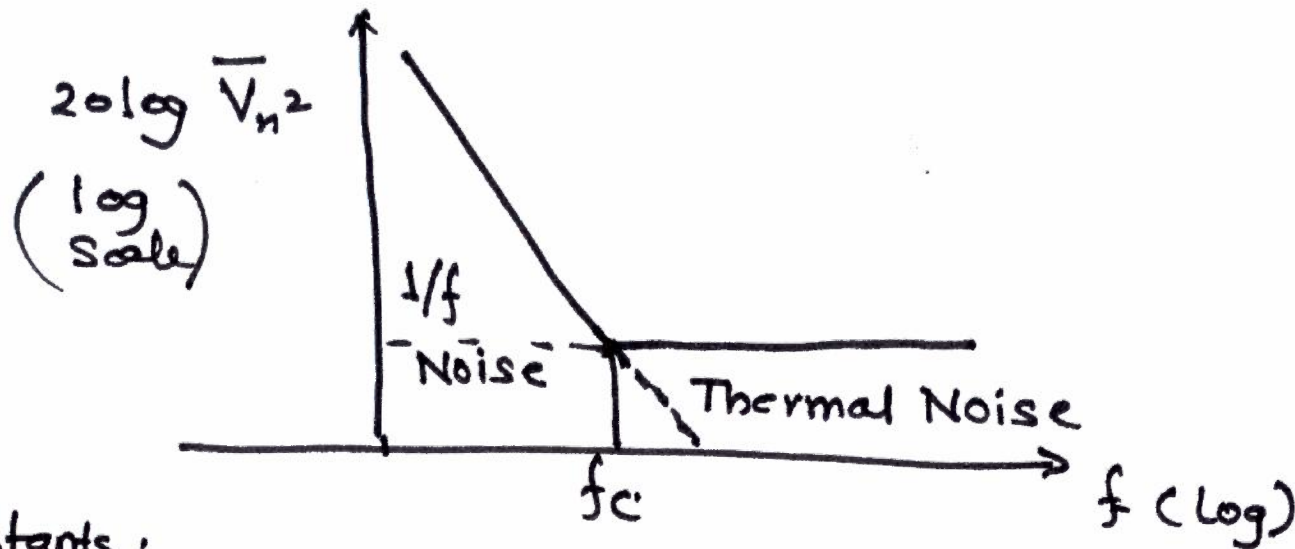

Constants :

$$K_{1\text{NMOS}} = 2 \times 10^{-29} \text{ A}\cdot\text{F}$$

$$K_{1\text{PMOS}} = 3.5 \times 10^{-30} \text{ A}\cdot\text{F}$$

}  $0.25 \mu$

$$K = 1.06 \times 10^{-25} \text{ V}^2\cdot\text{F} \quad (\text{90 nm Tech.})$$

(i) As  $K_1$  values are larger for NMOS devices compared to PMOS devices,  $f_c$  for NMOS devices is larger than that for PMOS devices.

(ii) Further  $f_c \propto \frac{1}{L^2}$  i.e.  $f_c$  increases with Technology Scaling.



(iii) Finally  $f_c \propto \frac{1}{g_m/I_{D5}}$ , gives understanding that larger  $g_m$  devices reduces  $f_c$ , meaning  $1/f$  noise dominates over thermal noise



CDEEP  
IIT Bombay

EE 618 L 05 / Slide 05

# Noise in CS Amplifier

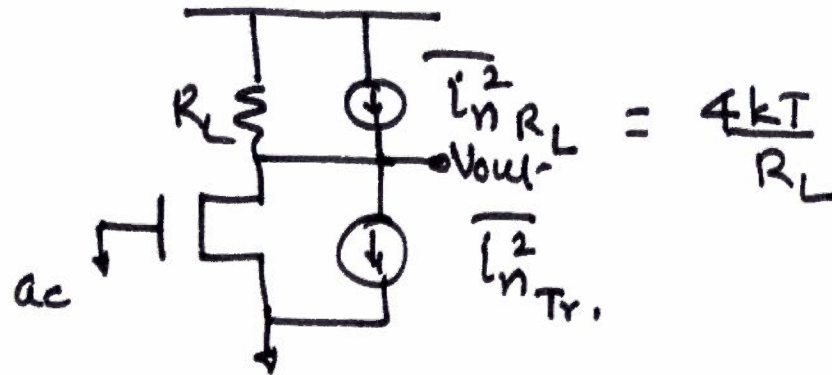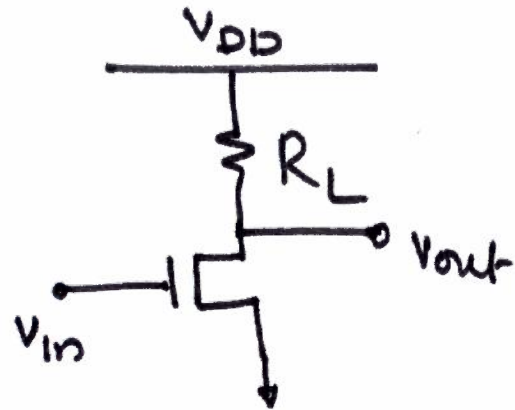

$$\therefore \overline{V_{n_{out}}^2} = \left[ 4kT \frac{2}{3} g_m + \frac{K}{C_{ox} W \cdot L} \cdot \frac{1}{f} g_m^2 + \frac{4kT}{R_L} \right] R_L^2$$


Input Referred Noise

$$\overline{V_{n_{in}}^2} = \overline{V_{n_{out}}^2} / A_{vo}^2, \quad A_{vo} = -g_m R_L$$

$$= \left[ 4kT \left( \frac{2}{3} g_m \right) + \frac{K}{C_{ox} W \cdot L} \cdot \frac{g_m^2}{f} + \frac{4kT}{R_L} \right] \frac{R_L^2}{g_m^2 R_L^2}$$



CDEEP  
IIT Bombay


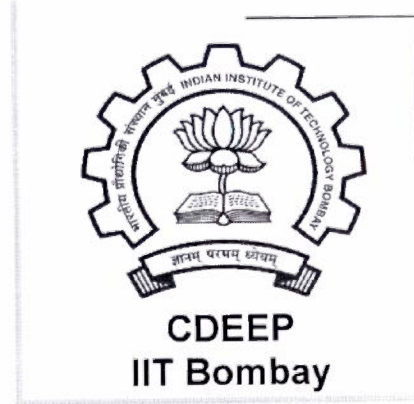


$$\sigma \sqrt{V_{n_{in}}^2} = \frac{8}{3} \frac{kT}{g_m} + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} + \frac{4kT}{g_m^2 R_L}$$

∴ For CS Amplifier

$$\sqrt{V_{n_{in}}^2} = 4kT \left( \frac{2}{3g_m} + \frac{1}{g_m^2 R_L} \right) + \frac{K}{C_{ox}WL} \cdot \frac{1}{f}$$

gives Input Referred Noise.

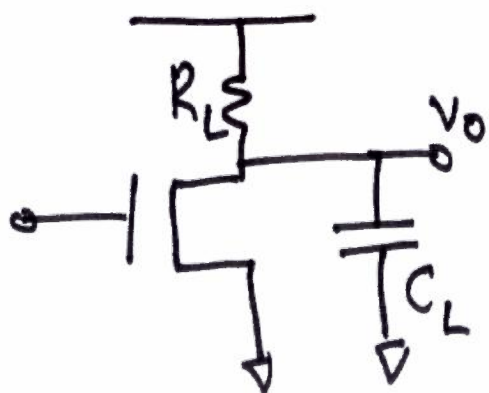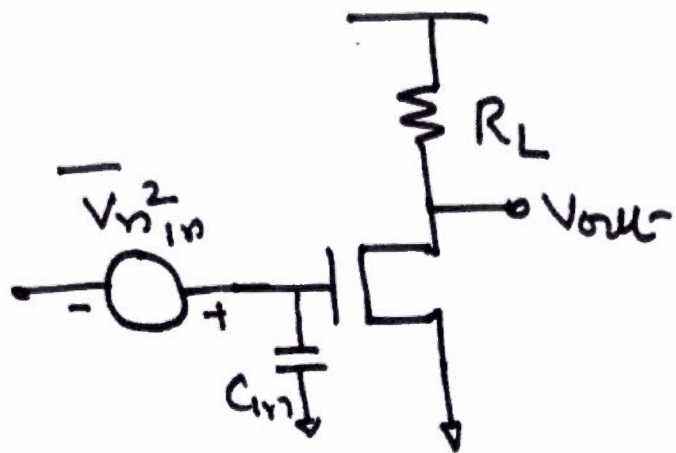

$$\sqrt{V_{n_{out}}^2} = \left[ \frac{8}{3} kTg_m + \frac{4kT}{R_L} \right] \left[ \frac{R_L}{1 + j\omega R_L C_L} \right]^2 df$$

(~~ω > fc~~) ω > fc is assumed

$$\begin{aligned} \therefore \sqrt{V_{n_{out}}^2} &= \int_0^\infty 4kT \left( \frac{1}{R_L} + \frac{2}{3} g_m \right) \left| \frac{R_L}{1 + j\omega R_L C_L} \right|^2 df \\ &= \frac{kT}{C_L} \left( 1 + g_m \cdot \frac{2}{3} R_L \right) \approx \frac{kT}{C} (1 + |A_{vol}|) \end{aligned}$$




# Noise in DIFFAMP



CDEEP  
IIT Bombay

EE 618 L 05 / Slide 06

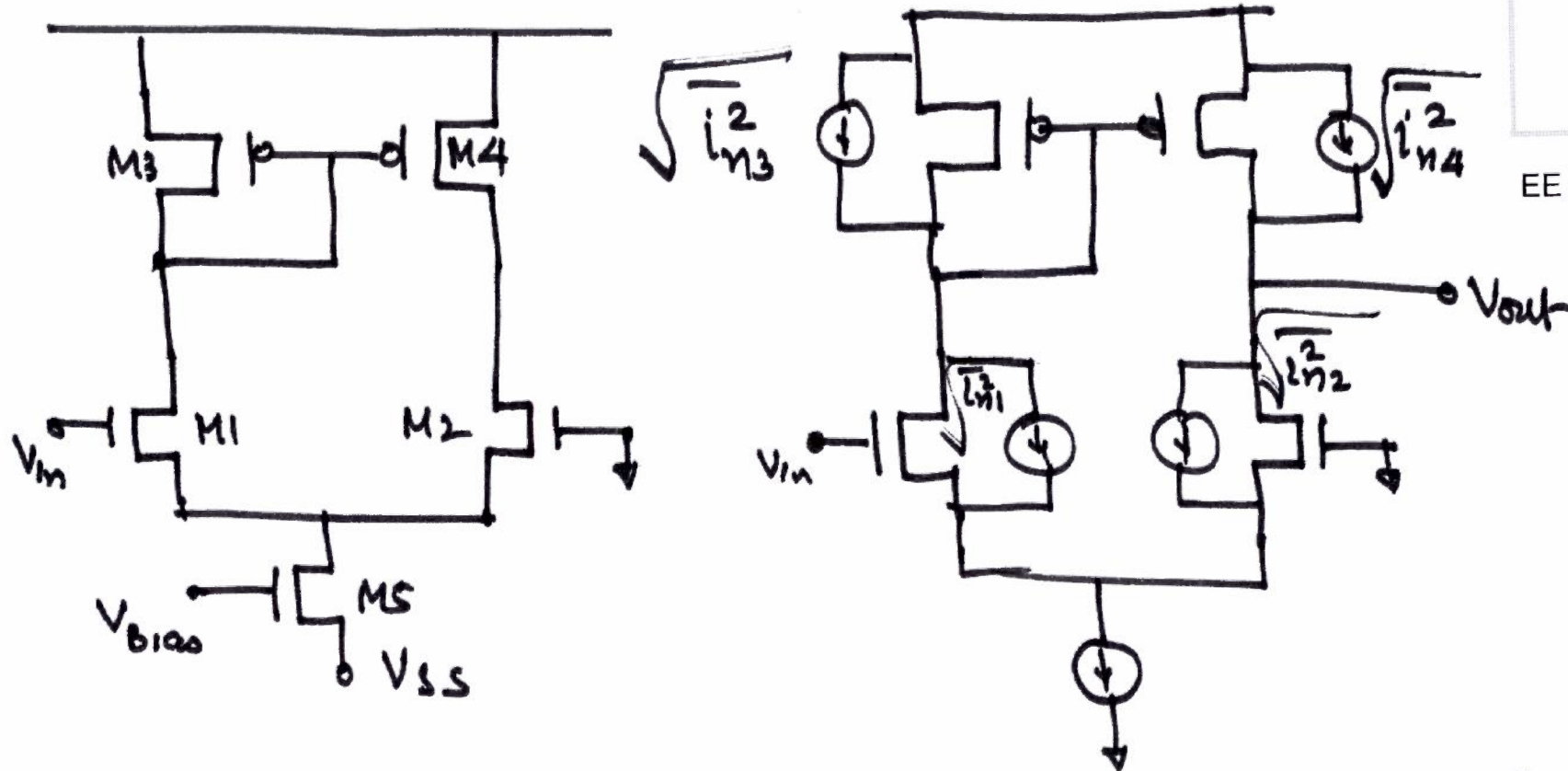

$$\overline{i_{n\text{out}}^2} = \overline{i_{n1}^2} + \overline{i_{n2}^2} + \overline{i_{n3}^2} + \overline{i_{n4}^2}$$

$$\overline{i_n^2} = 4kT \left( \frac{2}{3} g_m \right) + \frac{K}{C_{ox} W \cdot L} \frac{g_m^2}{f} \quad A^2/Hz$$



CDEEP  
IIT Bombay

EE 618 L 25 / Slide 09

$$\overline{V_{\text{Total out}}^2} = \overline{i_{\text{nout}}^2} \cdot (r_{o2} \parallel r_{o4})^2 \quad V^2/Hz$$

$$\therefore \overline{V_{\text{TMIR}}^2} = \frac{V_{\text{Total out}}^2}{A_{V0}^2} = \frac{1}{g_{m1}^2 (r_{o2} \parallel r_{o4})^2} \cdot \overline{V_{\text{Total out}}^2}$$

$$\therefore \overline{V_{\text{TMIR}}^2} = \frac{\overline{i_{\text{nout}}^2} \cdot (r_{o2} \parallel r_{o4})^2}{g_{m1}^2 (r_{o2} \parallel r_{o4})^2}$$

$$= \frac{\overline{i_{\text{nout}}^2}}{g_{m1}^2}$$

$$\begin{aligned} \overline{i_{\text{nout}}^2} &= 4kT \left( \frac{2}{3} g_{m1} \right) + \frac{k}{C_{ox} W_1 L_1} \cdot \frac{g_{m1}^2}{f} + 4kT \left( \frac{2}{3} g_{m2} \right) \\ &+ \frac{k}{C_{ox} W_2 L_2} \cdot \frac{g_{m2}^2}{f} + 4kT \left( \frac{2}{3} g_{m3} \right) + \frac{k}{C_{ox} W_3 L_3} \cdot \frac{g_{m3}^2}{f} \\ &+ 4kT \left( \frac{2}{3} g_{m4} \right) + \frac{k}{C_{ox} W_4 L_4} \cdot \frac{g_{m4}^2}{f} \end{aligned}$$

$$g_{m1} = g_{m2} \quad , \quad \frac{W_1}{L_1} = \frac{W_2}{L_2}$$

$$g_{m3} = g_{m4} \quad ; \quad \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$$

$$\begin{aligned} \therefore \overline{i_{nout}^2} &= 8kT \left(\frac{2}{3} g_{m1}\right) + \frac{2k g_{m1}^2}{f} \cdot \frac{1}{C_{ox} W_1 L_1} \\ &+ 8kT \left(\frac{2}{3} g_{m3}\right) + \frac{2k g_{m3}^2}{f} \cdot \frac{1}{C_{ox} W_3 L_3} \end{aligned}$$

$$\begin{aligned} \therefore \overline{V_{TNINR}^2} &= \frac{16kT}{3g_{m1}} + \frac{2k}{C_{ox} W_1 L_1} \cdot \frac{1}{f} \\ &+ \frac{16kT}{3} \cdot \frac{g_{m3}}{g_{m1}^2} + 2k \left(\frac{g_{m3}}{g_{m1}}\right)^2 \cdot \frac{1}{C_{ox} W_3 L_3} \cdot \frac{1}{f} \end{aligned}$$



CDEEP  
IIT Bombay


EE 618 L 25 / Slide 10




CDEEP  
IIT Bombay

EE 618 L 25 / Slide 11

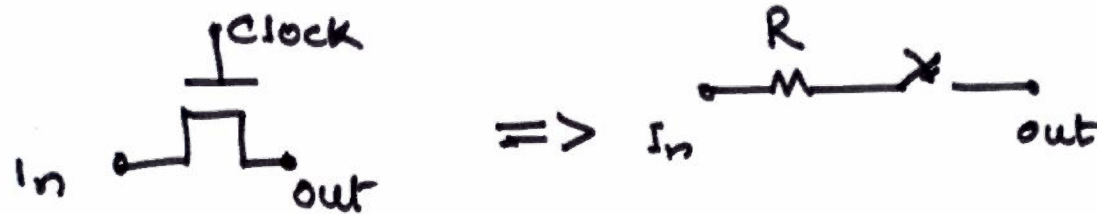In Sampling Mode, the MOS Transistor is used as Switch. Switch is characterised as



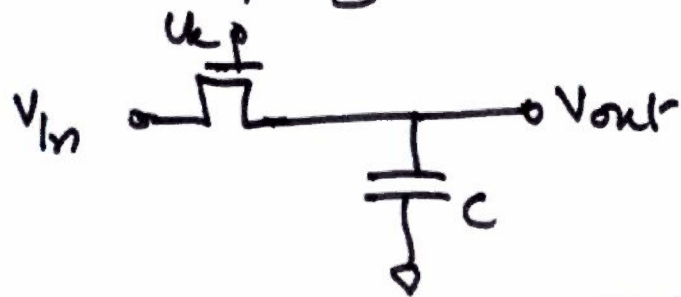In sampling we have circuit like shown. When Switch is 'ON', C charges to  $V_{in} = V_{out}$  and when Switch is 'OFF', last  $V_{out}$  is retained or 'hold'.



This RC circuit gives  $\frac{kT}{C}$  noise.

For such a circuit

$$SNR = \frac{P_{av}}{P_{noise}} = \frac{\frac{1}{2} \overline{V_{out}^2}}{\frac{kT}{C}} \propto C \overline{V_{out}^2} \text{ at a Temp.}$$

SNR obtained is around 80db.