

OSCILLATORS


$$A_{CL}(s) = \frac{H(s)}{1 + H(s)}$$

Unity Gain
Feedback

If $s = j\omega_0$ and $H(j\omega_0) = -1$

then $A_{CL}(j\omega_0) = \infty$ at $\omega = \omega_0$

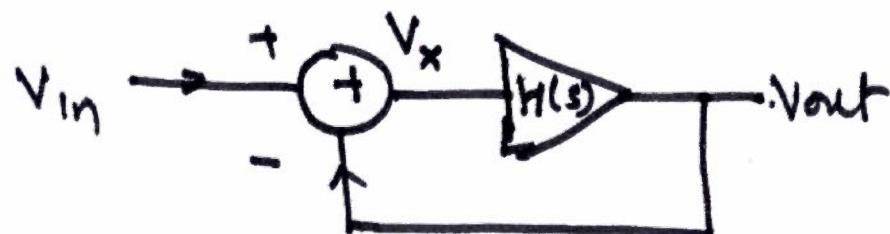This condn is essentially condition for oscillations.



Negative
A typical feedback
system is shown
here. Here

$$V_x = V_{out} + |H(j\omega_0)|V_{out} + |H(j\omega_0)|^2V_{out} + \dots$$

(Geometric Series)



CDEEP
IIT Bombay

If $|H(j\omega_0)| > 1$, then V_x is having a Diverging series.

while $|H(j\omega_0)| < 1$, then V_x has converging series representation, and its magnitude is Finite.

We write


$$V_x = \frac{V_{out}}{1 - |H(j\omega_0)|} = \text{Finite } \left\{ \text{if } |H(j\omega_0)| < 1 \right\}$$

Barkhausen Criteria :

In a Negative feedback System, if


TWO conditions $\rightarrow \Delta < H(j\omega_0) = 180^\circ$ are satisfied

then the system will Oscillate

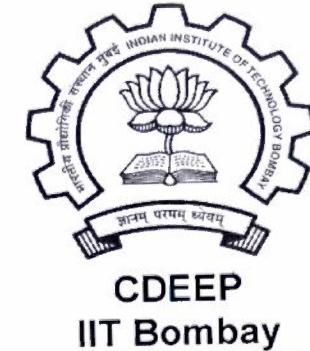

Ring Oscillator

1.

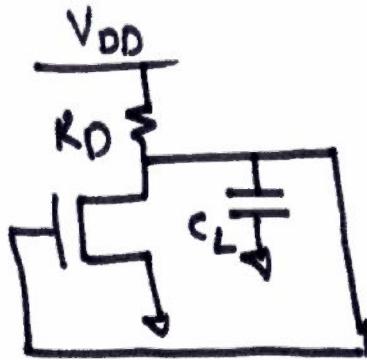


$$\text{Pole } p_1 = \frac{1}{R_D C_L}$$

Phase shift at Pole is 45°
 & total Phase Shift is 90° ,
 plus 180° from Transistor = 270°

Hence Loop does not sustain oscillation.

2

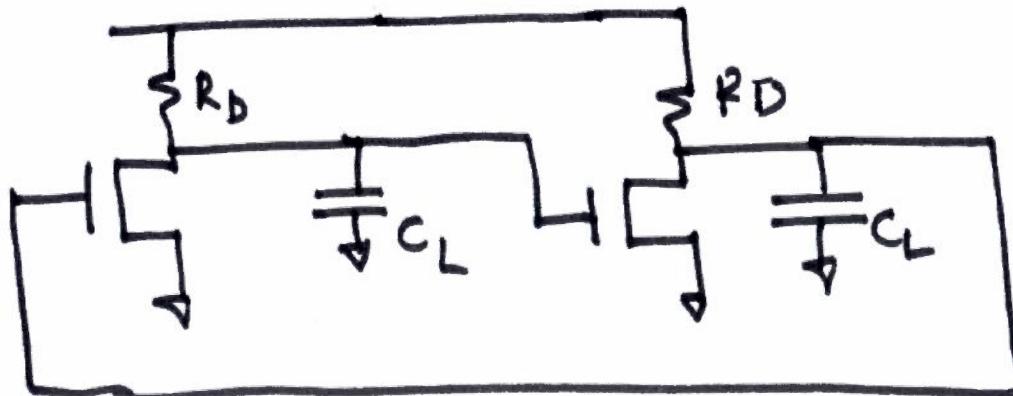

2 poles will give

total Phase shift of
 $180^\circ + 180^\circ = 360^\circ$. This
 satisfies Oscillation Cond!
 However one does not
 observe Oscillations here.


The Feedback satisfies Barkhausen Criterion only at
 $\omega_0 = 0$. The circuit therefore exhibits Latch Action.



CDEEP
IIT Bombay

EE 618 L 27 / Slide 03

3.

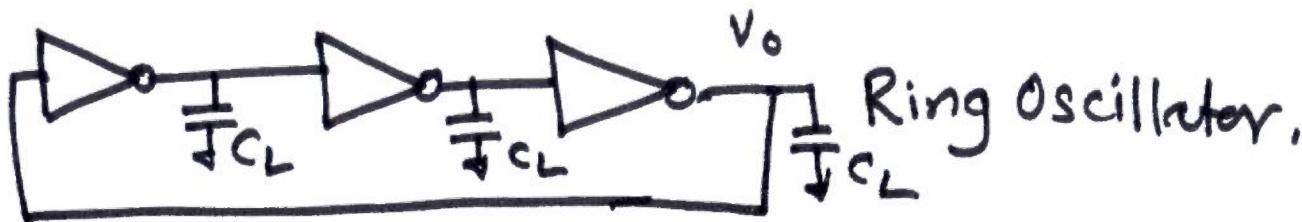

Ring Oscillator.

$$\omega_0 = \frac{1}{R_D C_L} \quad \text{and transfer function show}$$

Triple pole at ω_0 .

$$\text{or } H(s) = \frac{-A_{v0}^3}{[1 + (\frac{s}{\omega_0})]^3}$$

We can see that for oscillation to sustain,

$$A_{v0} = 2 \quad \text{and} \quad \omega_{osc} = \sqrt{3} \omega_0$$

It means that each stage must contribute 60° from one RC combination



CDEEP
IIT Bombay

EE 618 L 27 / Slide 09

Let us look into a Negative Feedback system with Triple Pole at P_1 .

i We start with Open Loop Gain with Triple Pole

$$A_{OL}(s) = \frac{A_{VO}}{\left(1 - \frac{s}{P_1}\right)^3} \quad -(i)$$

A_{VO} is a DC Gain (or Call 'Low Frequency Gain')

ii If this OPEN Loop Amplifier gets a feedback with feedback Network Gain of β [Assume $\beta \neq F(f)$], then Closed Loop Gain is :

$$A_{CL}(s) = \frac{A_{OL}(s)}{1 + A_{OL}(s)\beta} \quad -(ii)$$



CDEEP
IIT Bombay

EE 618 L 17 / Slide 05

$$\text{or } A_{CL}(s) = \frac{\frac{A_{v0}}{(1 - \frac{s}{P_1})^3}}{1 + \frac{A_{v0}\beta}{(1 - \frac{s}{P_1})^3}}$$


$$= \frac{A_{v0}}{(1 - \frac{s}{P_1})^3 + A_{v0}\beta} \quad - (\text{iii})$$

we define Loop Gain $T_0 = A_{v0}\beta$ — (iv)

At any other Frequency

$$T(s) = T(j\omega) = \frac{T_0}{(1 - \frac{s}{P_1})^3} = \left(\frac{T_0}{1 + j \frac{\omega}{|P_1|}} \right)^3$$

-- (v)

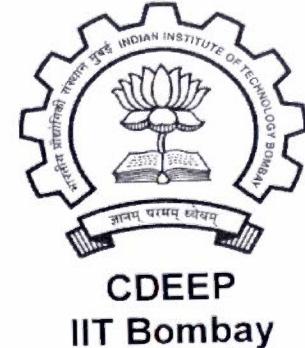

We observe Poles $A_{CL}(s)$ as are obtained from ϵ_3 (iii), or to say

$$(1 - \frac{s}{P_1})^3 + T_0 = 0 \quad - (vi)$$

$$\text{or } (1 - \frac{s}{P_1})^3 = -T_0$$

$$\text{or } 1 - \frac{s}{P_1} = \sqrt[3]{-T_0}$$

$$\text{or } s = |P_1| \left(1 + \sqrt[3]{-T_0} \right)$$

Using Algebra we know if $x = \sqrt[3]{-y}$

$$\text{then } x^3 + y = 0$$

$$\text{or } x^3 + (y^{1/3})^3 = 0$$



CDEEP
IIT Bombay

$$\text{or } (x + y^{1/3})(x^2 + xy^{1/3} + y^{2/3}) = 0$$

$$\therefore x_1 = -y^{1/3}$$

$$x_2 = -y^{1/3} e^{j\frac{\pi}{3}}$$

$$x_3 = -y^{1/3} e^{-j\frac{\pi}{3}}$$

\therefore Three roots of eq (vi) are

$$s_1 = P_1 \left(1 + \sqrt[3]{T_0} \right)$$

$$s_2 = P_1 \left(1 + \sqrt[3]{T_0} e^{j\frac{\pi}{3}} \right)$$


$$s_3 = P_1 \left(1 + \sqrt[3]{T_0} e^{-j\frac{\pi}{3}} \right)$$



CDEEP
IIT Bombay

EE 618 L 27 / Slide 02

The Root Locus looks like

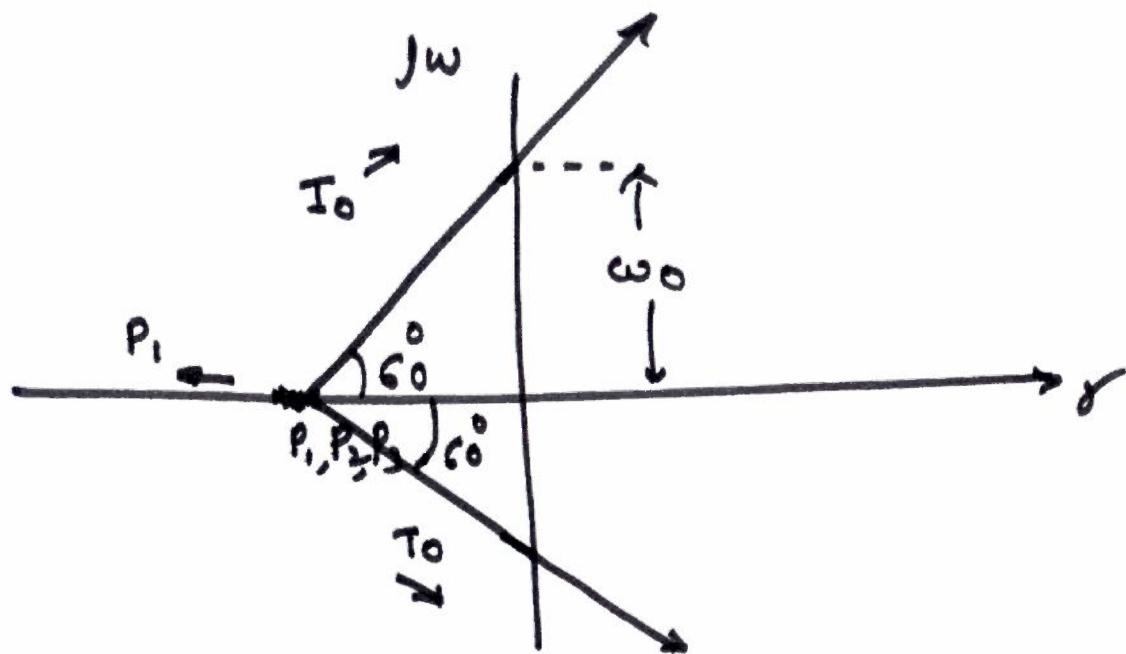

CDEEP
IIT Bombay

EE 618 L 27 / Slide 09

At $\omega = \omega_0$, one observe locus intersects jw axis.

clearly here Real value vanishes at $\omega = \omega_0$

$$\text{or to say } 1 - \operatorname{Re}(\sqrt[3]{T_0} e^{j\frac{\pi}{3}}) = 0 \text{ or } \sqrt[3]{T_0} \cos 60^\circ = 1$$

$$\therefore \boxed{T_0 = 8} \quad \text{at } \omega = \omega_0$$

Clearly beyond $T_0 > 8$, the system will be unstable, and at $T_0 = 8$, it is critically stable.

From the 'R-Locus' figure

$$\tan \zeta^{\circ} = \frac{\omega_0}{|P_1|}$$

$$\propto \omega_0 = \sqrt{3}|P_1| = 1.73205|P_1|$$

Just above frequency above of ω_0 , δ is v.small positive and imaginary part exists. This is like Positive feedback and System will show Growth response, as

$$\propto e^{\sigma t} \sin \omega_0 t \quad (\text{Growing Sinusoid})$$



CDEEP
IIT Bombay

EE 618 L 27 / Slide 10


We can use Bode's plot to get this result.


We have

$$T(s) = T(j\omega) = \frac{T_0}{(1 + j \frac{\omega}{\omega_{p1}})^3}$$

We plot $|T(j\omega)|$ and $\angle T(j\omega)$ as function of Frequency (Bode Plot)

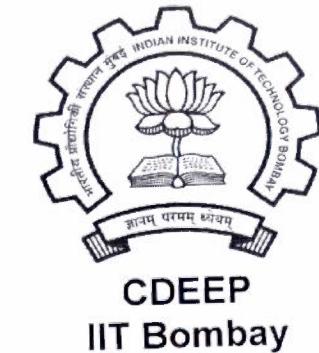- (A) We observe that at Pole frequency ω_{p1} , the phase is -135° . (Triple pole: Each pole $45^\circ/\text{decade}$)
- (B) And $T(j\omega_{180})$ is Positive at $\omega = \omega_{180^\circ}$
 ω_{180° is the Frequency at which $\angle T(j\omega) = -180^\circ$




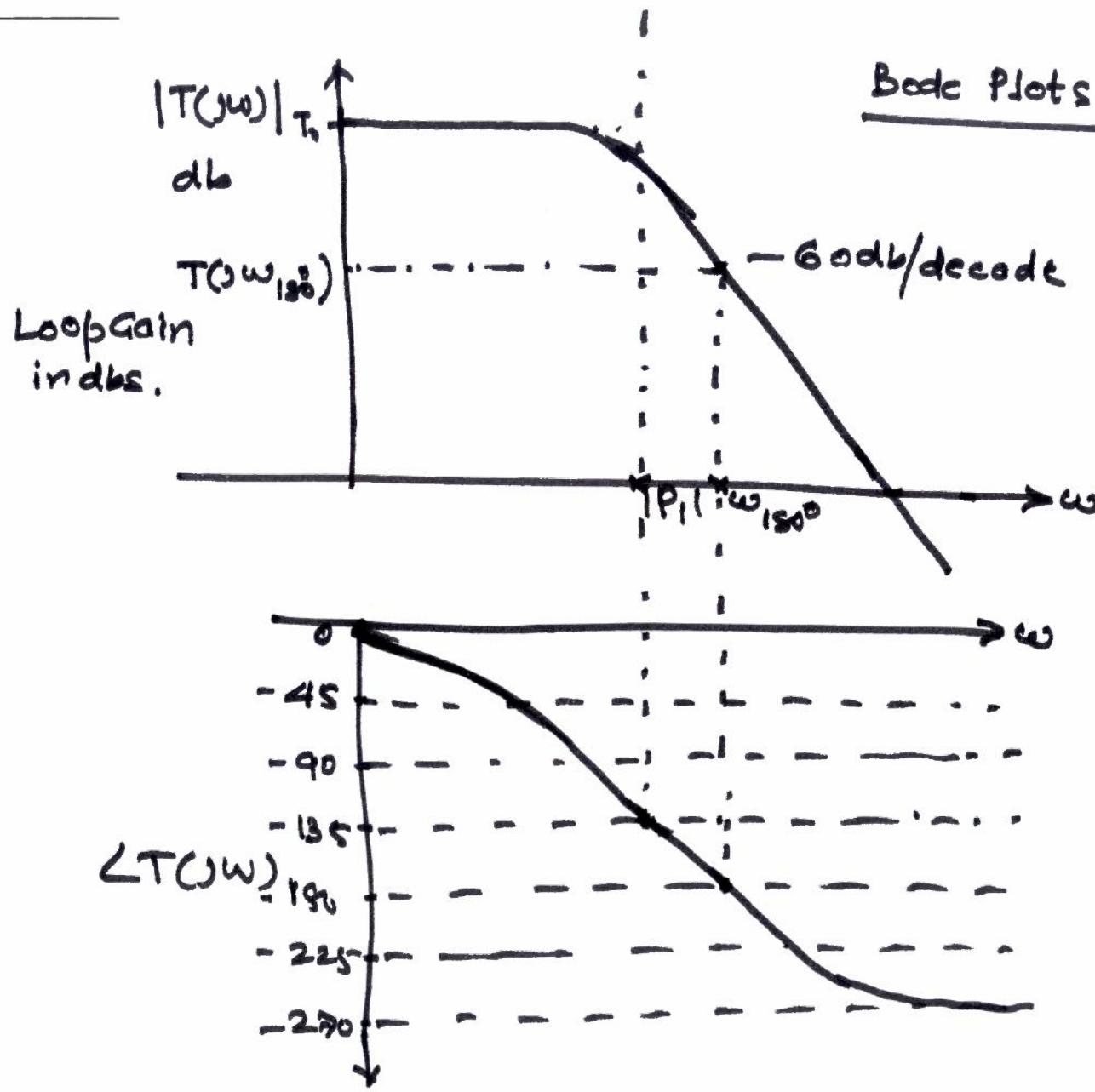

CDEEP
IIT Bombay

EE 618 L 27 / Slide 12

We return to Ring Oscillator case as

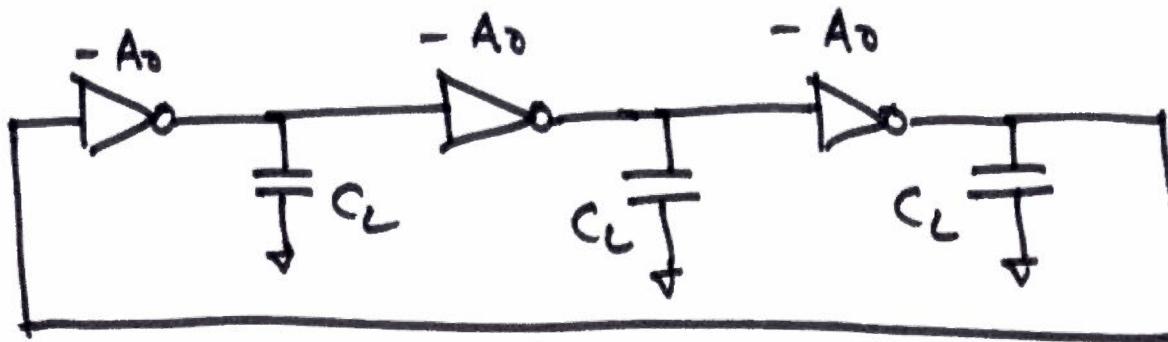

Here $\omega_0 = (\gamma_{out} \cdot C_L)^{-1}$; A_0 is a Stage Gain

$$\therefore H(s) = \frac{-A_0^3}{\left[1 + \left(\frac{s}{\omega_0}\right)\right]^3}$$

is the net Transfer fn
 ω_0 used here is $|\omega_0|$

Each stage should contribute 60° Phase, then

$$\omega_{osc} = \omega_0 \tan^{-1} \frac{\pi}{3} = \sqrt{3} \omega_0$$

And at $\omega = \omega_{osc}$, Loop Gain = 1

$$\therefore 1 = \frac{A_0^3}{8}$$

or $A_0 = 2$

\therefore Ring Oscillator thus will oscillate

at frequency $= \frac{2\pi \cdot \omega_0 \cdot \sqrt{3}}{2\pi}$ if the stage Gain is ≥ 2
and each stage gives $\frac{\pi}{3}$ phase shift.

Clearly from earlier discussion of Triple Pole case,
we can say that

$$V_o = a e^{(\frac{A_0-2}{2})\omega_0 t} \cdot \cos\left(\frac{\sqrt{3} A_0}{2} \omega_0 t\right)$$

which means for $A_0 < 2$ — Damping

$A_0 > 2$ — Growth uncontrolled
 $A_0 = 2$ — Oscillation.

Most commonly used VCO Oscillators

1. Source Coupled - Multivibrators

2. Current Starved VCO ,



CDEEP
IIT Bombay


EE 618 L 27 / Slide 15

The word VCO \rightarrow Voltage Controlled Oscillators

which essentially means tuning of Frequency of oscillator using voltage control.


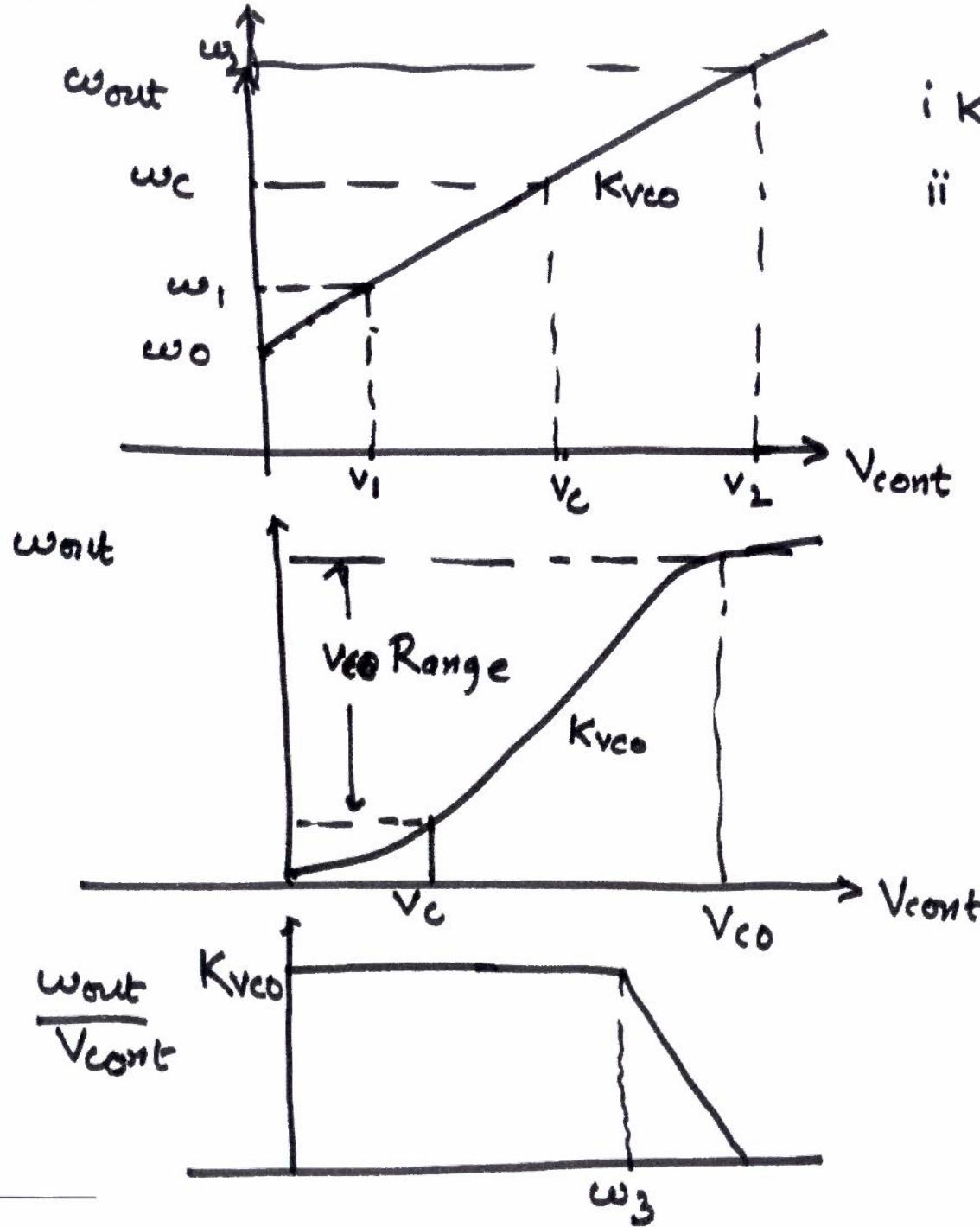
$$\omega_{\text{out}} = \omega_0 + K_{\text{VCO}} \cdot V_{\text{cont}}$$



- i $K_{VCO} = VCO$ gain
ii Range = $\omega_2 - \omega_1$



CDEEP
IIT Bombay

EE 618 L 27 / Slide 16

$$K_{VCO} = \frac{2\pi(f_{max} - f_{min})}{V_{max} - V_{min}}$$

Typical Power ~~used~~
^{Used}

= 1 to 10 mW

Generally VCO operates
from 1 M radian/sec

to 10 M radian/sec

$K_{VCO} \sim 0$ to 5 M radian/sec/V


Terminology for VCO

- (i) Centre Frequency : \rightarrow Midrange Value
- (ii) Tuning Range :— Decided by
 - (a) Variation of VCO centre frequency with Process and Temperature variation
 - (b) Frequency range needed for an Application

Major worry: Variation of Output Phase and Frequency as a result of Noise superposition on $V_{control}$,


Frequency - noise at Output $\propto K_{VCO}$

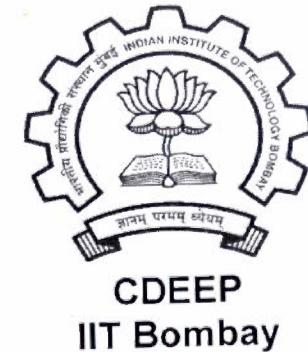Hence for this Noise to reduce, K_{VCO} be smaller



However the Tuning Range $\propto K_{VCO}$

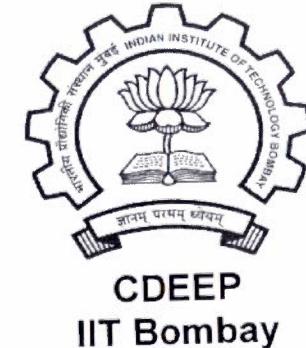\therefore For larger Tuning Range , we need
Higher K_{VCO} .



EE 618 L 27 / Slide 18

(iii) Tuning Linearity

$$K_{VCO} = \frac{\partial \omega_{out}}{\partial V_{DD}} = \frac{\partial \omega_{out}}{\partial C} \cdot \frac{\partial C}{\partial V_{DD}} \quad C = f(V_{DD})$$

Which means K_{VCO} is not constant.

(iv) Output Amplitude :— Larger Amplitude be desired.

(v) Power Dissipation :— 1 to 10mW

Trade-off: Power - Frequency - Noise

(vi) Signal Purity :

Even with a constant K_{vco} & V_{cont} , the output signal is not always Periodic (Perfect). One sees 'Noise' both in Phase & Frequency. These are called Phase Noise and Jitter.





CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L 27 / Slide 20

Source Coupled VCO

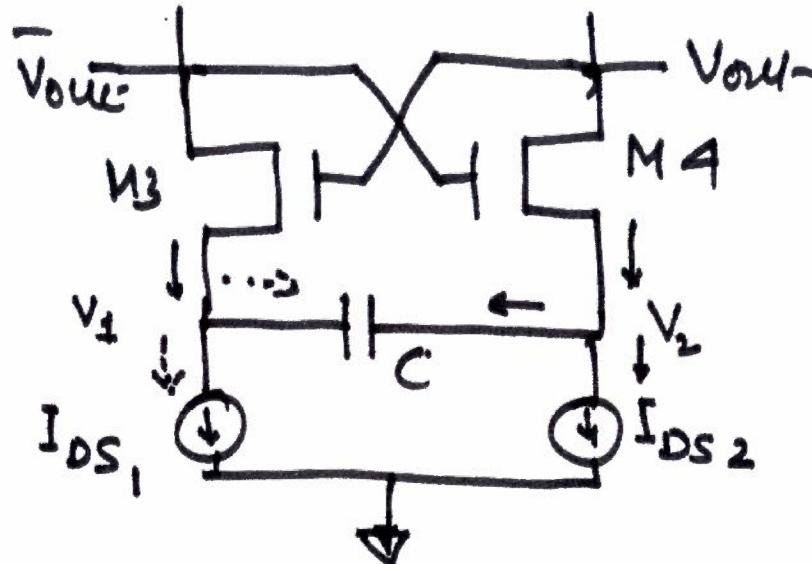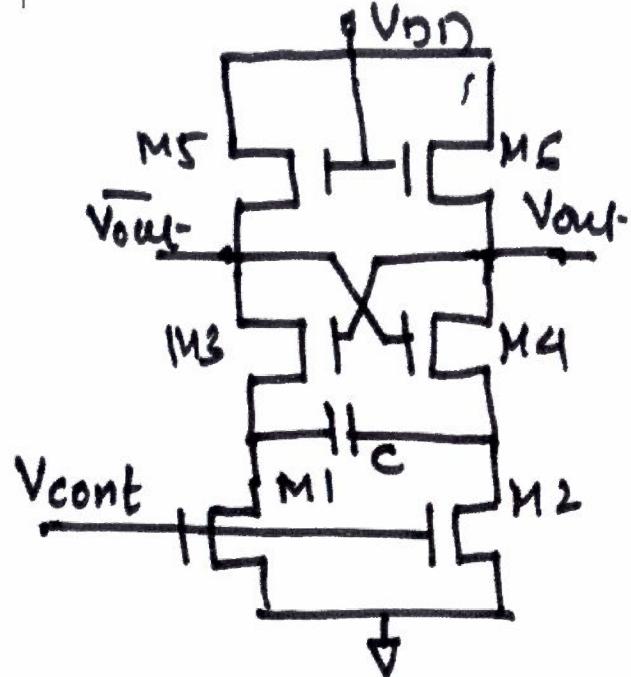

Here V_{cont} provides Bias to M1 & M2 such that

$I_{DS1} = I_{DS2}$ is Current Source biasing scheme

As $M5 \& M6$ are in saturation (N -channel), hence

$$V_{out\max} (\text{or } \bar{V}_{out\max}) = V_{DD} - V_{TN}$$

where V_{TN} is threshold of all N -channel devices