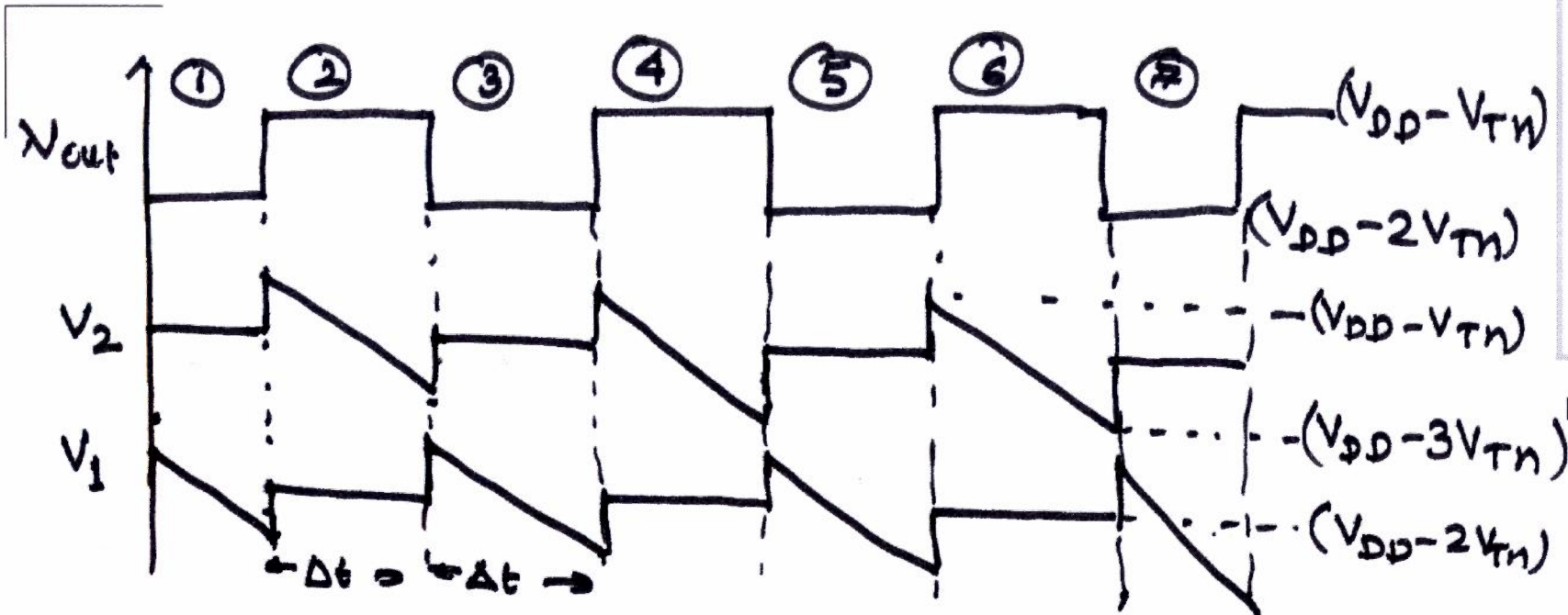




CDEEP
IIT Bombay

EE 618 L 28 / Slide 07




① If M_3 is OFF & M_4 ~~are~~ is ON

Then $V_{out} = V_{DD} - V_{TN_{M_6}} - V_{TN_4} = V_{DD} - 2V_{TN}$

Then no current goes through M_3 . But M_4 must provide $2I_{DS}$ current, as it must cater to

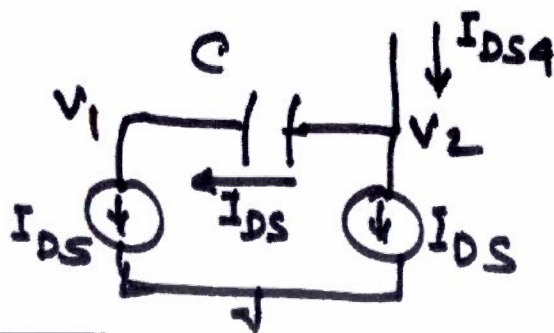I_{DS_2} & I_{DS_1} currents. I_{DS_1} comes through charging of Capacitor C .



Case 2 Now if M3 is ON and M4 is OFF

Then $\bar{V}_{out}$ will be similar to that of V_{out} as in case 1.

Hence V_1 and V_2 will alternate in time frame.

Since I_{Ds} charges capacitor in time Δt , hence delivered charge in capacitor $C = I_{Ds} \cdot \Delta t$

However capacitor sees change of $V_{DD} - V_{Th} - V_{DD} - 3V_{Th}$
 $= 2V_{Th}$

$\therefore$ charge in capacitor $= C \cdot 2V_{Th}$

$\therefore \Delta t = \frac{2CV_{Th}}{I_{Ds}}$. But Frequency $f = \frac{1}{2\Delta t} = \frac{I_{Ds}}{4CV_{Th}}$




CDEEP
IIT Bombay

EE 618 L 28 / Slide 2

Current Starved VCO

This is essentially a Ring Oscillator

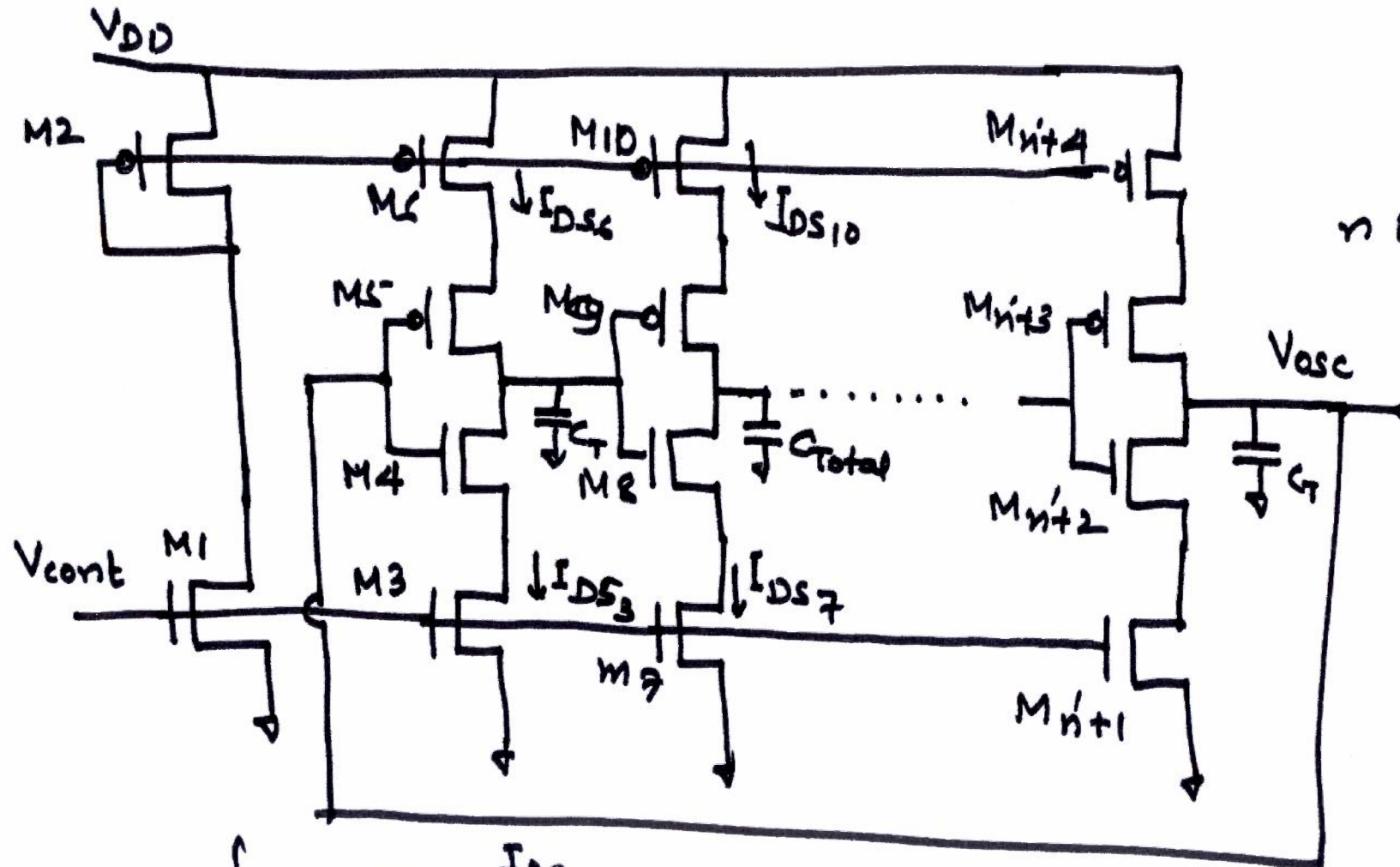

$$f_{osc} = \frac{I_{DS}}{N \cdot C_{Total} \cdot V_{DD}}$$




CDEEP
IIT Bombay

EE 618 L 28 / Slide 3

n is no. of Column.


LC Oscillators

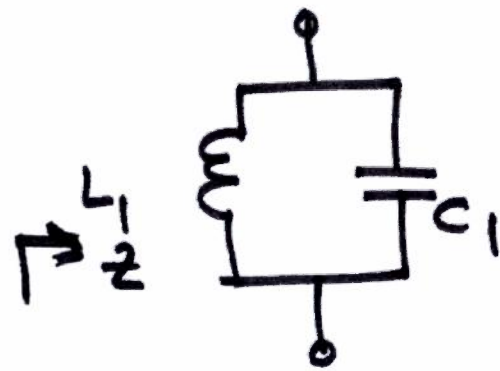All LC Oscillators use Resonant Tank Circuit to sustain Oscillation.



Ideal Inductor

$$f = \frac{1}{2\pi\sqrt{LC}}$$

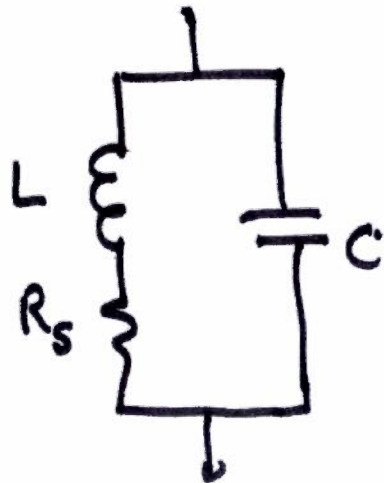

Series resistance of Inductor coil.

In IC chips, Spiral Inductor Coils are printed to have desired Inductance value



CDEEP
IIT Bombay

EE 618 L 08 / Slide 4

For the Non-Ideal Tank circuit


$$Z_{TC}(s) = \frac{R_s + L_1 s}{1 + L_1 C_1 s^2 + R_s C_1 s} = ((R_s + j\omega L_1) \parallel \frac{1}{j\omega C_1})$$



CDEEP
IIT Bombay

EE 618 L 28 / Slide 5


$$\begin{aligned} \therefore |Z_{TC}(j\omega)|^2 &= \left| \frac{R_s + j\omega L_1}{1 - L_1 C_1 \omega^2 + j\omega R_s C_1} \right|^2 \\ &= \frac{R_s^2 + L_1^2 \omega^2}{(1 - \omega^2 L_1 C_1)^2 + R_s^2 C_1^2 \omega^2} \end{aligned}$$

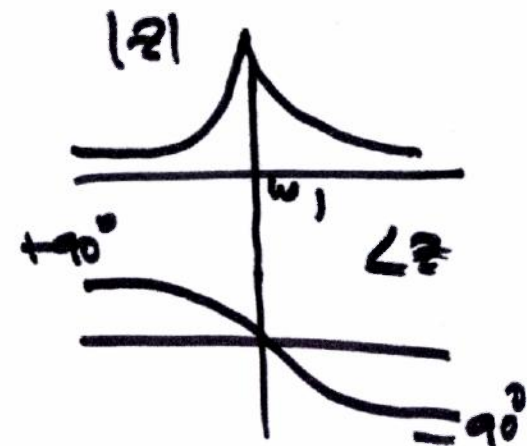

In Ideal LC circuit at oscillation frequency the Z_{TC} (Z for Tuned Circuit) is Infinite.

But in non Ideal case as above $Z_{TC}(j\omega) \neq \infty$ at any frequency. Which essentially means circuit has finite Q

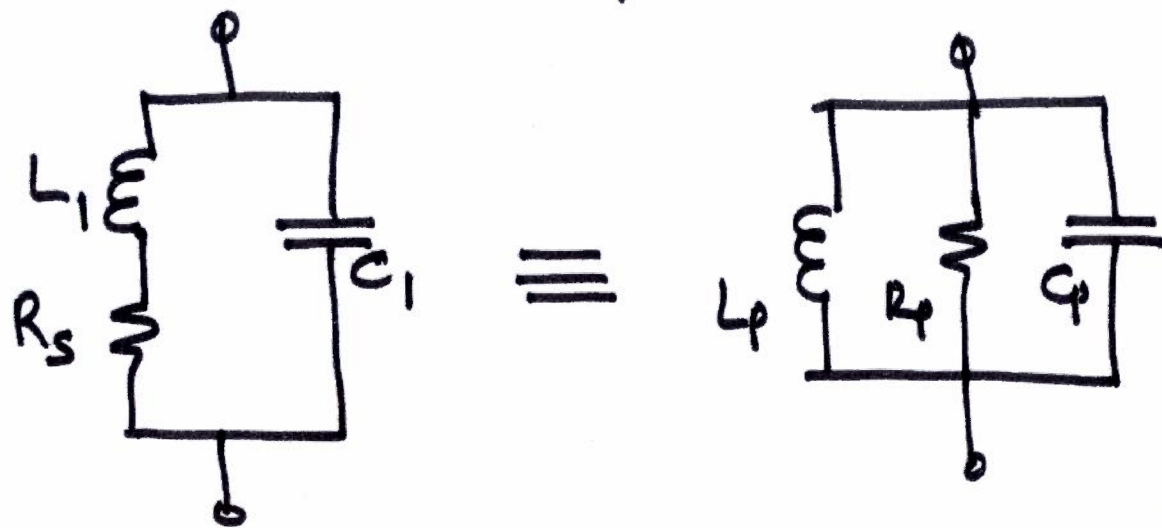
Tank circuit representation in Parallel form.



CDEEP
IIT Bombay

EE 618 L 28 / Slide 6

Let us keep $C_1 = C_p$, then

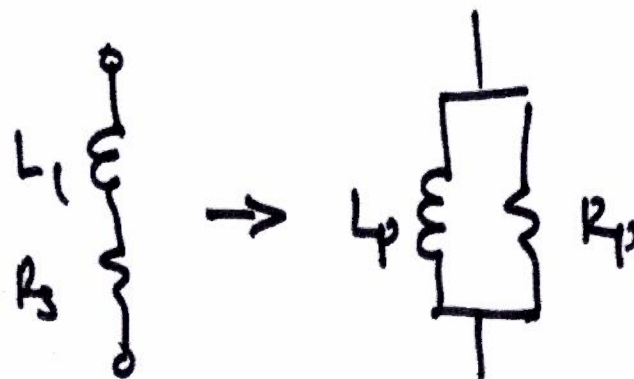

$$\begin{aligned}
 \text{or } R_s + j\omega L_1 &= \frac{R_p L_p s}{R_p + L_p s} = \frac{j\omega R_p L_p}{R_p + j\omega L_p} \quad \text{--- (1)} \\
 &= \frac{j\omega R_p L_p (L_p - j\omega L_p)}{R_p^2 + \omega^2 L_p^2}
 \end{aligned}$$

From ①

$$(R_s + j\omega L_1)(R_p + j\omega L_p) = j\omega R_p L_p$$

$$\text{or } R_s R_p - \omega^2 L_1 L_p + j\omega (L_p R_s + L_1 R_p) = j\omega (R_p L_p) \quad \text{--- cii)}$$

Equating Real & Imaginary parts in cii)

$$L_p R_s + L_1 R_p = R_p L_p \quad \text{--- ciii)}$$

$$\text{and } R_s R_p - \omega^2 L_1 L_p = 0 \quad \text{--- civ)}$$

$$\text{From (iv)} \quad \omega^2 L_1 L_p = R_s R_p$$

$$\therefore L_p = \frac{R_s R_p}{\omega^2 L_1} \Rightarrow \quad \text{(v)}$$



CDEEP
IIT Bombay

$$\text{or } R_p = \frac{\omega^2 L_1 L_p}{R_s} \quad \text{--- (vi)}$$

Substituting R_p in ciii)

$$\sqrt{L_p R_s + L_1 \frac{\omega^2 L_1 L_p}{R_s}} = \frac{\omega^2 L_1 L_p}{R_s} \cdot L_p$$

$$\left[L_p R_s + \frac{\omega^2 L_1^2 L_p^2}{R_s \cdot L_p} \right] = \frac{\omega^2 L_1^2 L_p^2}{R_s \cdot L_1}$$

$$L_p R_s + \frac{\omega^2 L_1^2 L_p^2}{R_s} \left(\frac{1}{L_p} - \frac{1}{L_1} \right) = 0$$

$$\rightarrow L_p^2 R_s^2 + \omega^2 L_1^2 L_p^2 = \frac{R_s L_p}{R_s L_1} \omega^2 L_1^2 L_p^2$$

$$1 + \frac{L_p^2 R_s^2}{\omega^2 L_1^2 L_p^2} = \frac{L_p}{L_1} \frac{\omega^2 L_1^2 L_p^2}{\omega^2 L_1^2 L_p^2}$$



CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L 28 / Slide 9

$$\text{or } 1 + \frac{R_s^2}{\omega^2 L_1^2} = \frac{L_p}{L_1}$$

$$\text{or } L_p = L_1 \left(1 + \frac{1}{Q^2} \right)$$

we have

$$Q = \frac{\omega L_1}{R_s}$$

Since $Q \gg 1$ (Typical Q of spiral inductor on Silicon is ≥ 3)

$$\therefore L_p \cong L_1$$

substituting this in eq. (vi)

$$R_p = \frac{\omega^2 L_1 L_p}{R_s} = \frac{\omega^2 L_1^2}{R_s} = \frac{\omega^2 L_1^2}{R_s^2} \cdot R_s = Q^2 R_s$$

$$R_p = Q^2 R_s$$


And $C_p = C_1$

The Magnitude & Phase of Input Impedance Z of Parallel Tank Circuit is like:



CDEEP
IIT Bombay

EE 618 L 28 / Slide 10

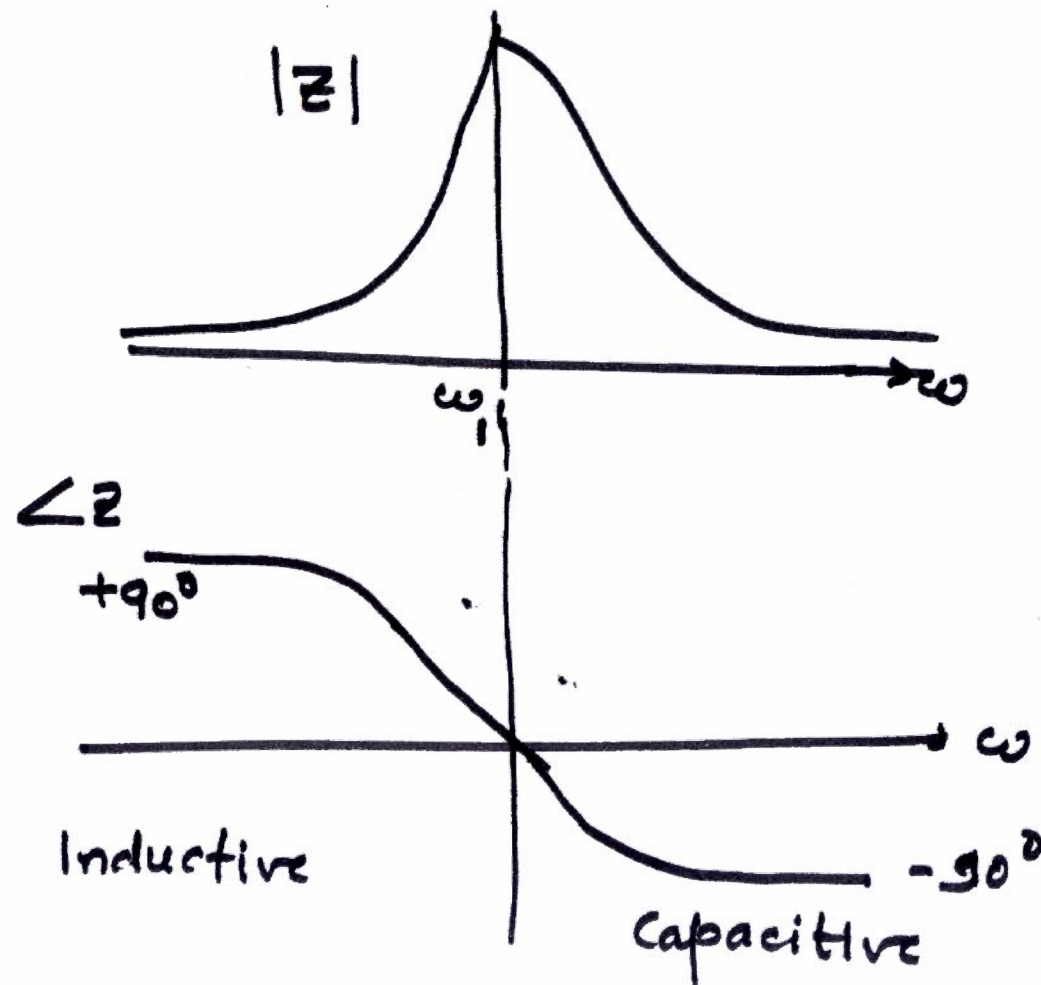


$$\omega_1 = \frac{1}{\sqrt{LC}}$$

$$f_{os} = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{L_p C_p}}$$

Cross Coupled Oscillator

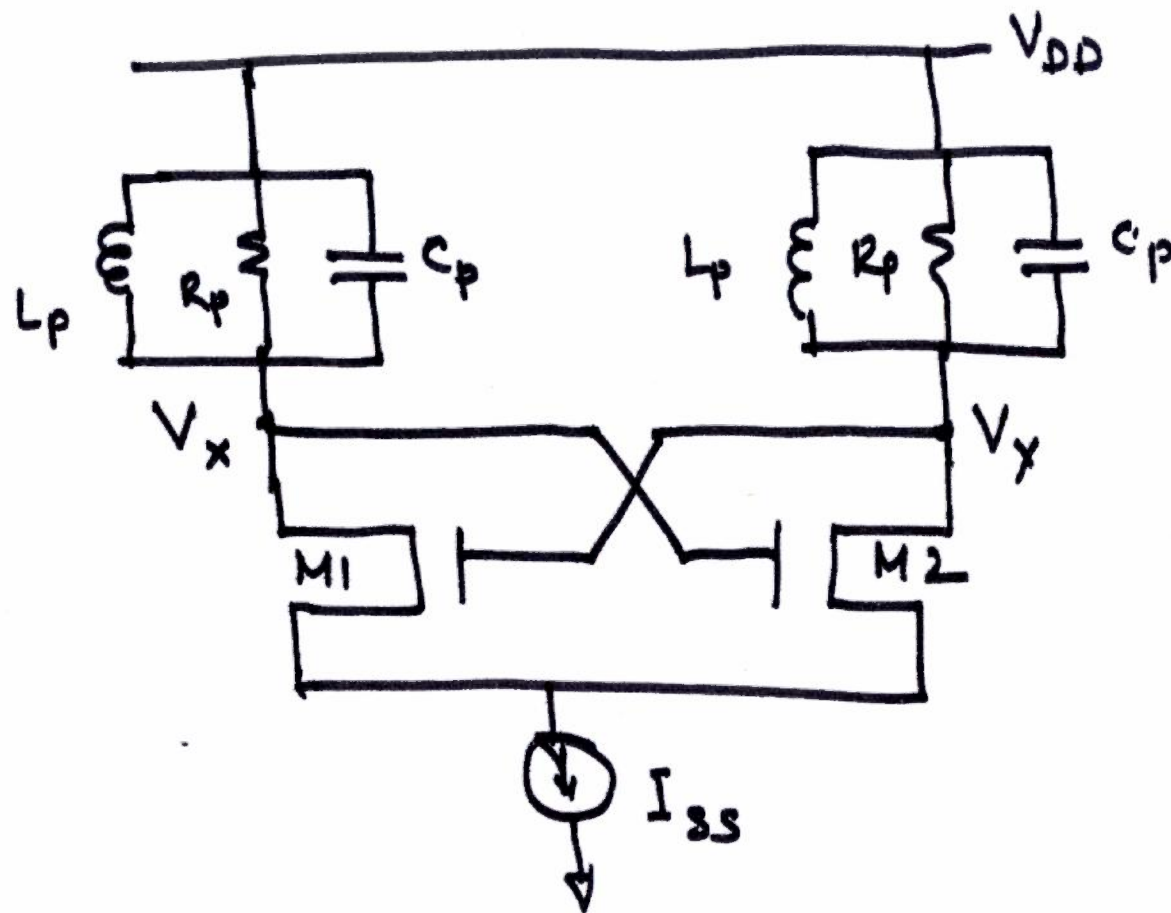

CDEEP
IIT Bombay

EE 618 L 28 / Slide 11

$$H(j\omega) = H_1(j\omega) \cdot H_2(j\omega)$$

$$H_0 = g_{m1} R_p \cdot g_{m2} R_p$$

$$\text{If } H(0) \geq 1$$

Then Oscillation will
be Sustained.


Colpitts and Hartley Oscillators are
example for Cross Coupled LC Oscillators




CDEEP
IIT Bombay

EE 618 L 28 / Slide 12

Principle :

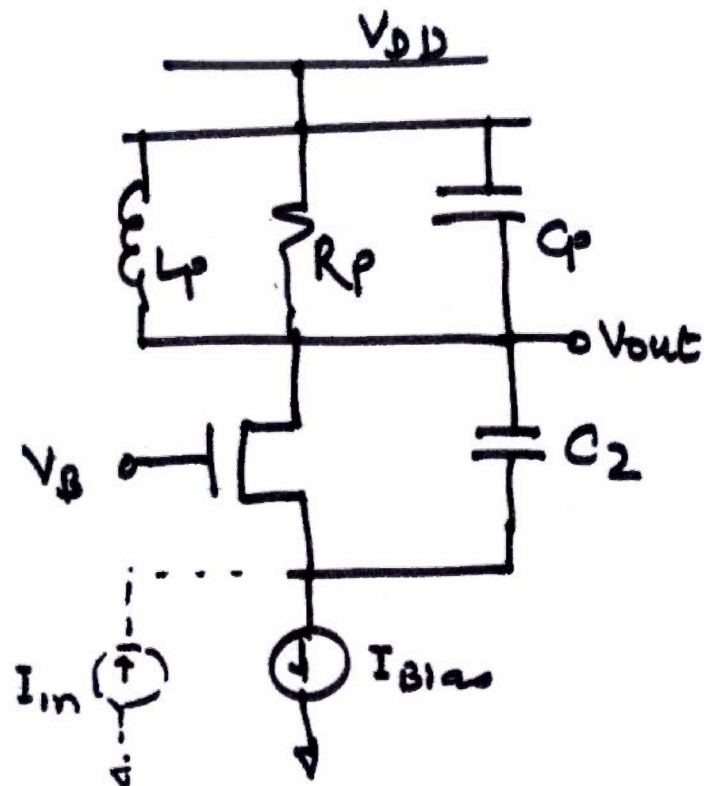
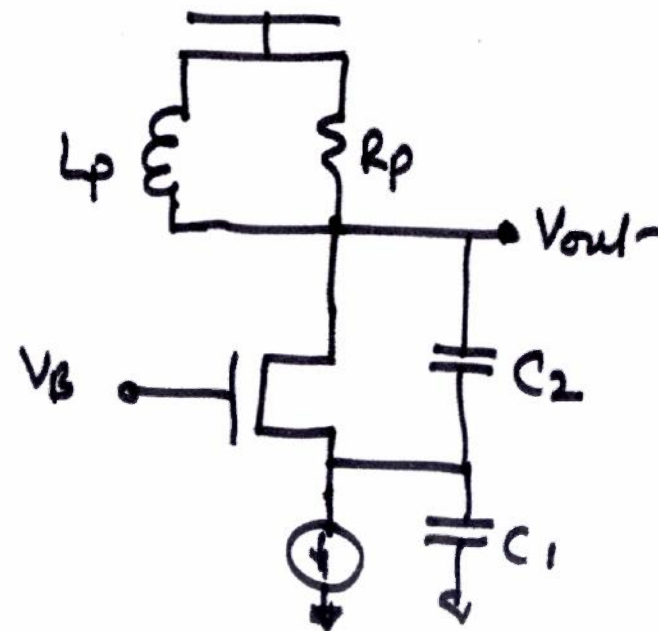
$$\Rightarrow \frac{V_{out}}{I_{in}} = L_p s \parallel R_p \parallel \frac{1}{C_p s}$$




Colpitts Oscillator



CDEEP
IIT Bombay

EE 618 L 28 / Slide 13

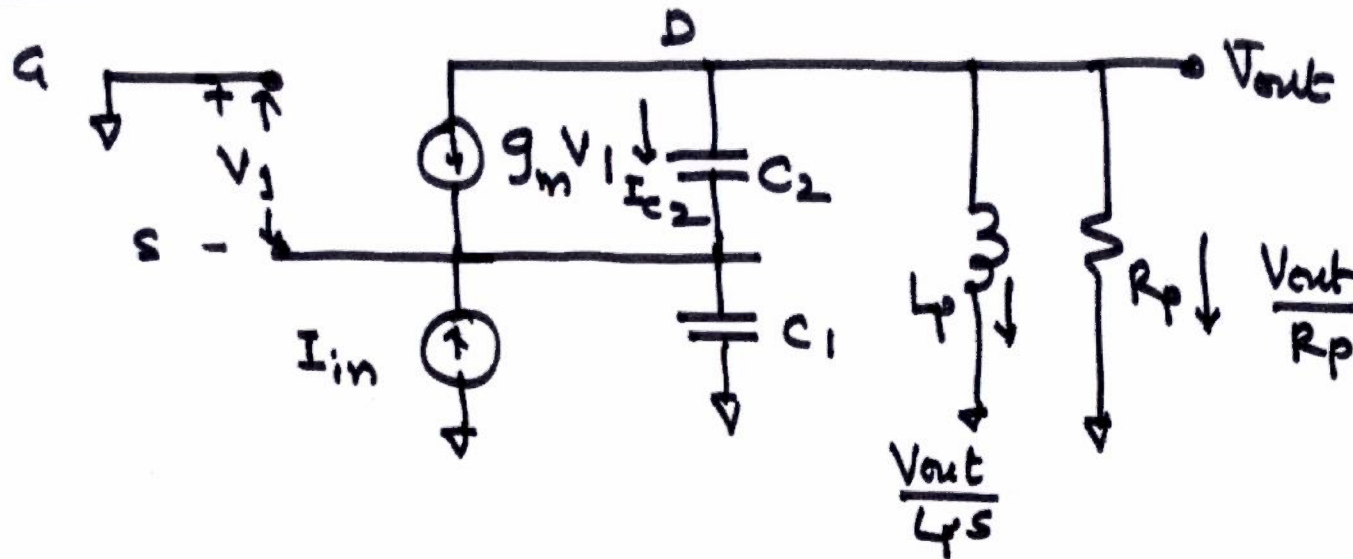

$$\therefore V_1 = - \left(I_{in} - \frac{V_{out}}{L_p s} - \frac{V_{out}}{R_p} \right) \cdot \frac{1}{C_1 s}$$

$$I_{C_2} = \{ V_{out} - (-V_1) \} C_2 s = (V_{out} + V_1) C_2 s$$

$$\therefore I_{C_2} = \left[V_{out} - \left(I_{in} - \frac{V_{out}}{L_p s} - \frac{V_{out}}{R_p} \right) \frac{1}{C_1 s} \right] C_2 s$$

Using Kirschoff's law at node V_{out} -

We have

$$g_m V_1 + I_{c2} + \frac{V_{out}}{L_p s} + \frac{V_{out}}{R_p} = 0$$

Solving this equation we get-

$$\frac{V_{out}}{I_{in}} = \frac{R_p L_p s (g_m + C_2 s)}{R_p C_1 C_2 L_p s^3 + (C_1 + C_2) L_p s^2 + [g_m L_p + R_p (C_1 + C_2)] s + g_m R_p}$$

For Oscillation $\frac{V_{out}}{I_{in}} \rightarrow \infty$ at oscillating frequency ω_R

We obtain

$$\omega_R^2 = \frac{1}{L_p \frac{C_1 C_2}{C_1 + C_2}} \quad \& \quad g_m R_p = \frac{C_1}{C_2} \left(1 + \frac{C_2}{C_1}\right)^2$$


Minimum required DC Gain gives $g_m R_p \geq 4$ when $\frac{C_2}{C_1} = 1$
With C_p present $\omega_R^2 = 1 / [C_p + \frac{C_1 C_2}{C_1 + C_2}] L_p$



CDEEP
IIT Bombay

EE 618 L 28 / Slide 14

Single Port Oscillators.

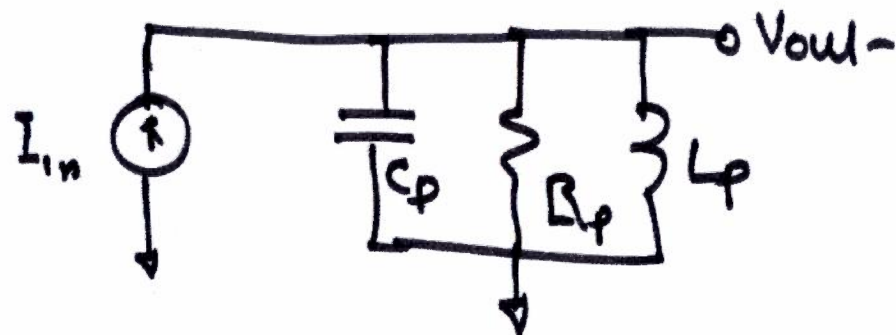


Oscillations die as R_p dissipates power




CDEEP
IIT Bombay

EE 618 L 28 / Slide 15


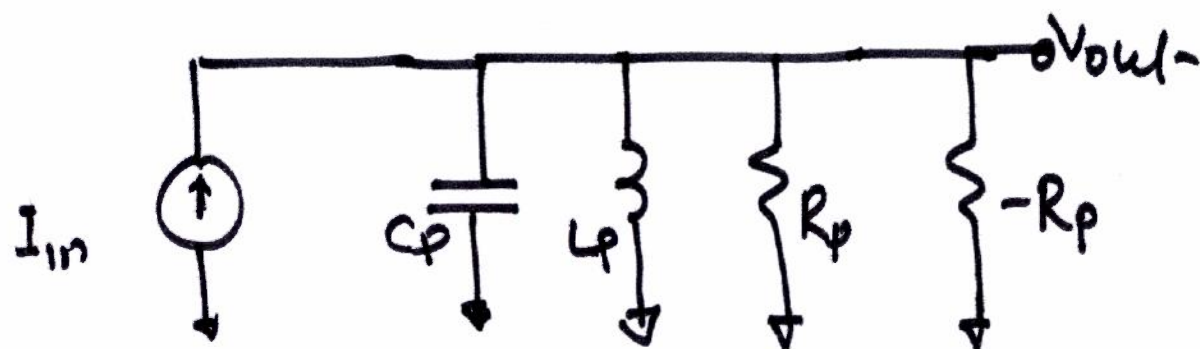


$$f_{osc} = \frac{1}{2\pi\sqrt{L_p C_p}}$$

-ve Resistance

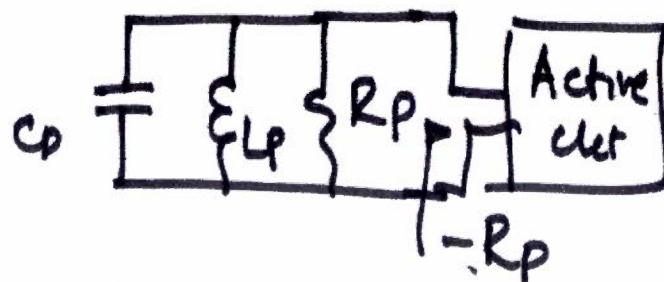

Negative Impedance Generator

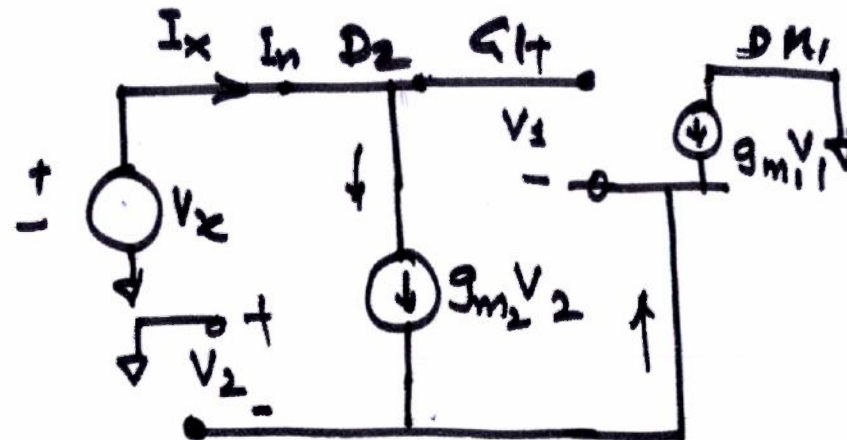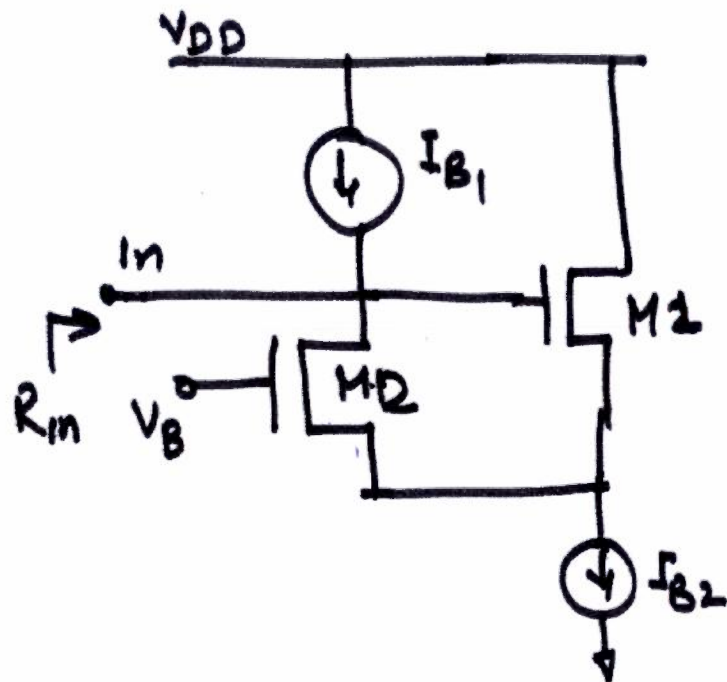

$$I_x = g_{m2} V_2 = -g_{m1} V_1$$

$$\text{But } V_x = V_1 - V_2$$

$$= \frac{I_x}{-g_{m1}} - \frac{I_x}{g_{m2}}$$

$$\text{or } \frac{V_x}{I_x} = -\left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}}\right)$$

$$\therefore R_{in} = -\frac{2}{g_m}$$



CDEEP
IIT Bombay

EE 618 L 28 / Slide 16

