

A simple Design Example for a CS Amplifier

Given $\mu C_{ox} = 100 \mu A/V^2$, $L = 0.8 \mu$


$$V_A = 50V$$

$$\alpha = 1.25$$

$$C_L = 0.1 \text{ pF}$$

$$BW = 2 \text{ MHz}$$

$$\text{Gain} \geq 200$$

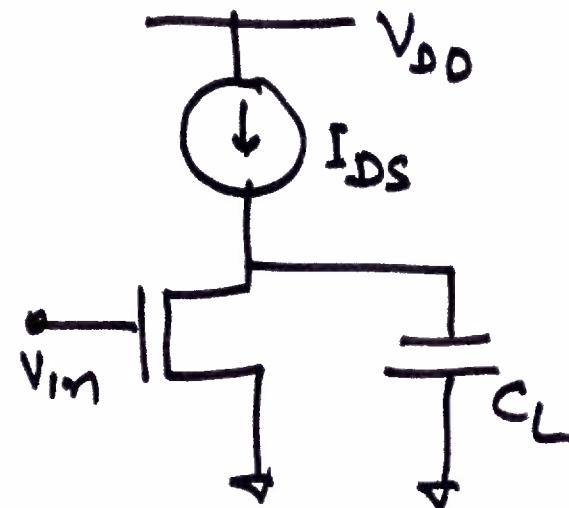


CDEEP
IIT Bombay

EE 618 L 7 / Slide 1



CDEEP
IIT Bombay

EE 618 L 7 / Slide 2

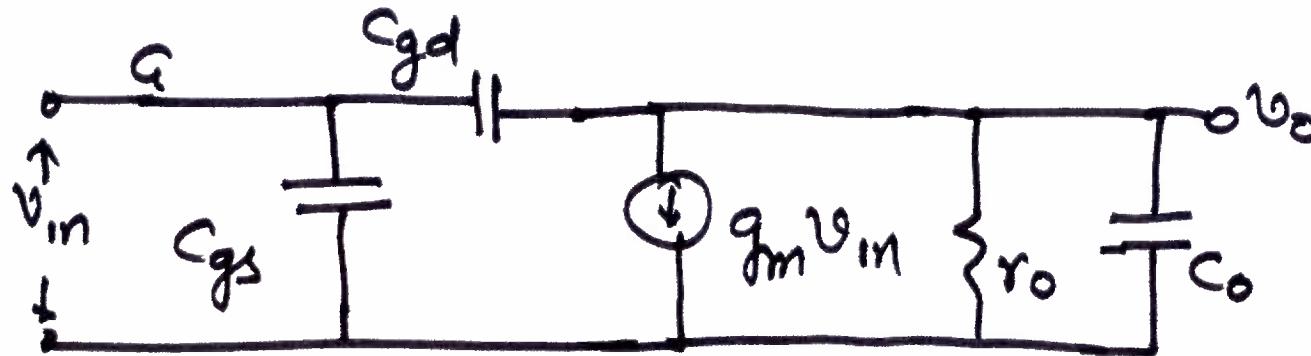

Using Kirchoff Law

Assume
 $\frac{1}{\omega C_{gs}} \rightarrow \infty$

$$sC_{gd}(v_{in} - v_o) - g_m v_{in} - \frac{v_o}{r_o} - sC_o v_o = 0$$

$$v_m(sC_{gd} - g_m) - v_o(sC_{gd} + \frac{1}{r_o} + sC_o) = 0$$

or $\frac{v_o}{v_{in}} = - \frac{g_m - sC_{gd}}{\frac{1}{r_o} + s(C_{gd} + C_o)}$

$$\text{or } A_V(s) = \frac{V_o(s)}{V_{in}(s)} = -g_m r_o \frac{1 - s C_{gd}/g_m}{1 + s r_o (C_{gd} + C_o)}$$



CDEEP
IIT Bombay

EE 618 L 7 / Slide 3

$$A_V(s) = + A_V(0) \frac{1 - s C_{gd}/g_m}{1 + s (r_o \cdot C_L)}$$

$$C_o + C_{gd} = C_L$$

We have 1 'zero' and 1 'pole.'

Neglect 'zero' assuming it is far off compared to pole frequency

This is possible in most cases as $r_o \gg \frac{1}{g_m}$

$$\text{Then } A_V(s) = A_{V_0} \frac{1}{1 + s \cdot r_o C_L}$$

$$\therefore \text{Bandwidth} = \frac{1}{r_o C_L} \approx \omega_{-3\text{db}}$$

and DC Gain = $A_{V_0} = -g_m r_o$

Then Gain Bandwidth Product GBW is

$$= \frac{g_m}{C_L}$$

Using these expressions we solve our
problem



CDEEP
IIT Bombay

EE 618 L 7 / Slide 4

$$q_m = \sqrt{2 \frac{\beta}{\alpha} I_{DS}}$$

Fixed I_{DS} biasing

$$\gamma_0 \equiv \frac{V_A}{I_{DS}}$$

(i) We start with γ_0

$$\gamma_0 = \frac{1}{2\pi \cdot BN \cdot C_L} = \frac{1}{6.28 \times 2 \times 10^6 \times 10^{-13}} \\ \approx 0.8 \text{ Mu}$$

(ii) I_{DS} evaluation

$$I_{DS} = \frac{V_A}{\gamma_0} = \frac{50}{0.8 \times 10^6} \approx 62.5 \mu\text{A} = 62.5 \mu\text{A}$$



CDEEP
IIT Bombay

EE 618 L7 / Slide 5



CDEEP
IIT Bombay

EE 618 L 7 / Slide 6

$$\text{Now } |A_{\text{Vol}}| = g_m \gamma_0$$

$$\therefore g_m = \frac{240}{0.8 \times 10^6} = 300 \times 10^{-6} \text{ s}$$

$$\text{But } g_m = \sqrt{\frac{2 \mu_{\text{Cox}} (W/L)}{\alpha} I_{DS}}$$

$$\therefore \frac{W}{L} = \frac{g_m^2 \alpha}{2 \mu_{\text{Cox}} I_{DS}} = \frac{(300 \times 10^{-6})^2 \times 1.25}{2 \times 100 \times 10^{-6} \times 2.5 \times 10^{-6}}$$

in g

$$\text{Given } L = 0.8 \mu \quad \therefore W = 0.72 \mu$$



CDEEP
IIT Bombay

EE 618 L 7 / Slide 2

We see

$$\frac{g_m}{I_{DS}} = \frac{300 \times 10^4}{62.5 \times 10^6} = \frac{600}{125} = \frac{24}{5}$$

$$= 4.8 \text{ (Per Volt)}$$

Modification

lets put limit on I_{DS} to lower value (Lower Power)
Dissipation

We have seen that $W \propto \frac{1}{V_{ov}} \sim \frac{g_m}{I_{DS}}$

\therefore If I use lower I_{DS} , I need Larger Width Device.
If Specs say 'Reduced Area' is necessary

This can be actually done by optimisation.

However Long Channel Model may not suffice

If Design requires smaller area for the circuit, ~~then~~ as well as Low Power, we have trade-off at hand.

For lower Power, we reduce I_{DS}


Hence for a fixed g_m (Gain constant), $\frac{g_m}{I_{DS}}$ increases. Since $\frac{1}{V_{OV}} \propto \frac{g_m}{I_{DS}}$, reduction in V_{OV} will occur at lower I_{DS} .

But $W \propto \frac{1}{V_{OV}}$, which means W will increase at reduced I_{DS} . Which in turns means Increase of area



We use $\frac{g_m}{I_{DS}}$ as Design Variable , then

We plot I_{DS}/W as $\frac{g_m}{I_{DS}}$ (For a Tech node)

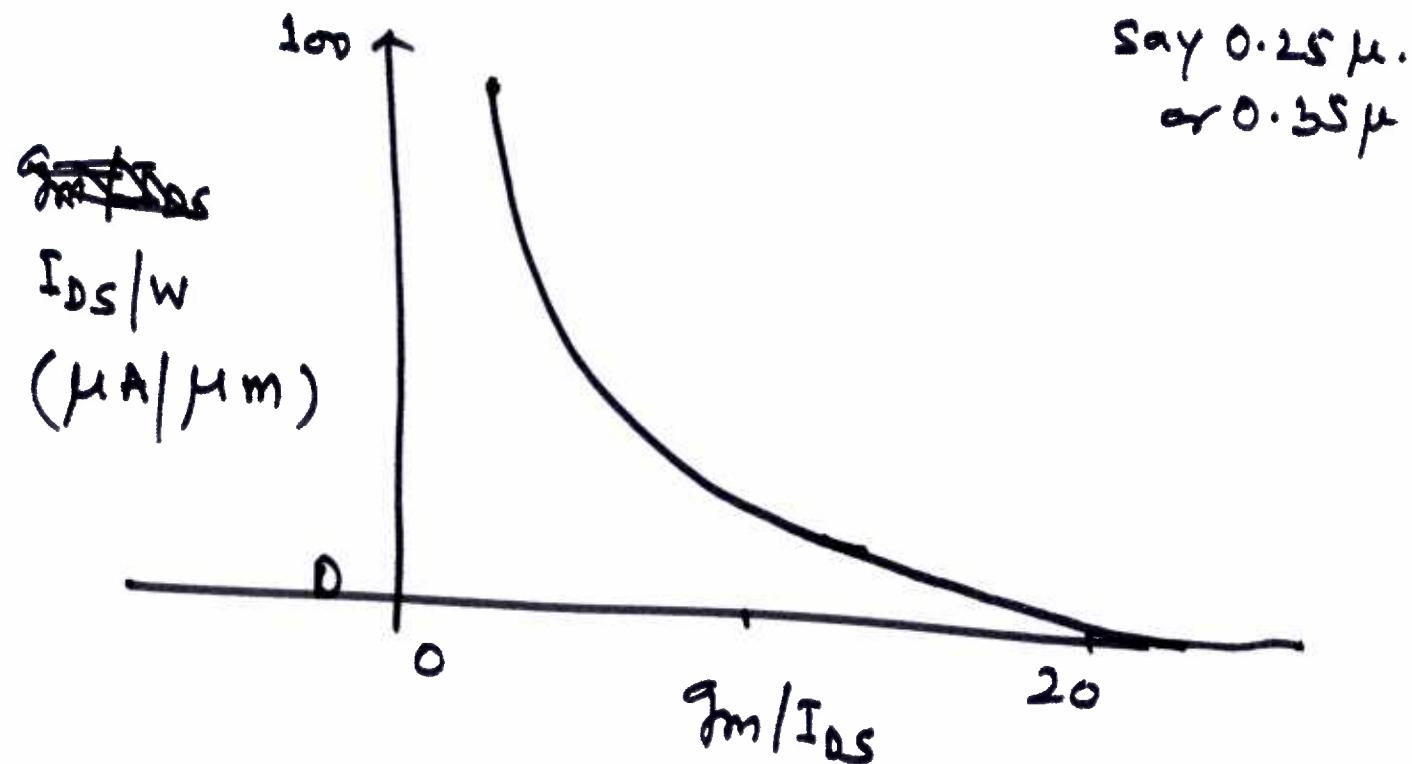

Say 0.25μ .
or 0.35μ




CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L 7 / Slide 10

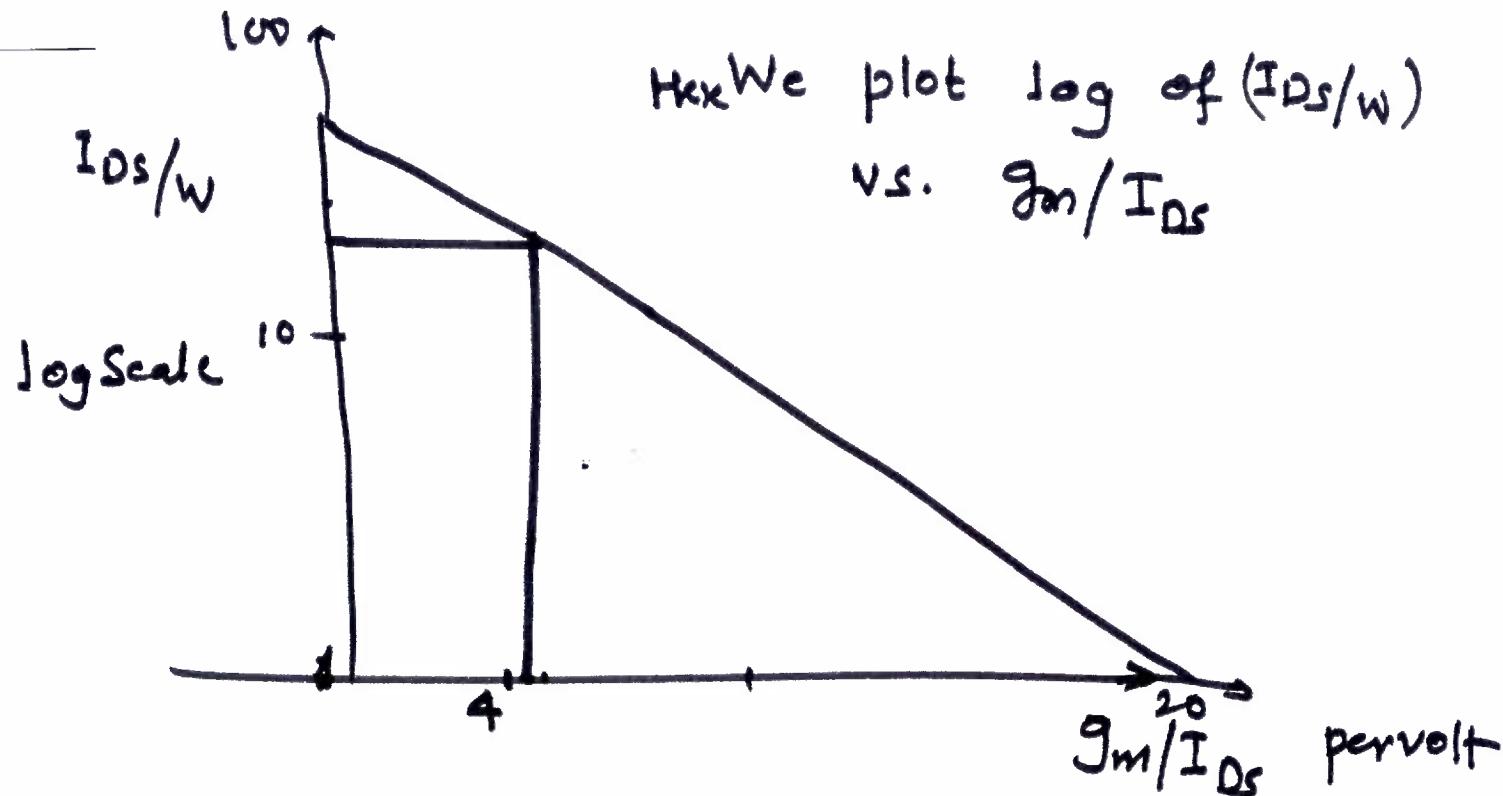

For our problem $g_m/I_{DS} = 4.8 \text{ V}^{-1}$
Let us say from Graph

We have

$$\frac{I_{DS}}{W} \approx 40 \mu\text{A}/\mu\text{m} \quad \text{for } g_m/I_{DS} = 4.8 \text{ /V}$$

But we have $I_{DS} = 62.5 \mu\text{A}$ $\therefore W = \frac{I_{DS}}{I_{DS}/W} = \frac{62.5}{40}$

$$\text{or } W = \frac{62.5}{40} = 1.56 \text{ mm.}$$