

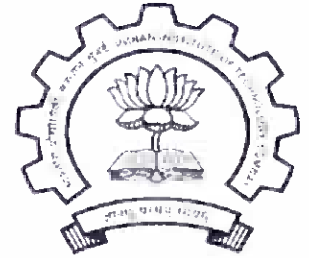


Slide No: 1

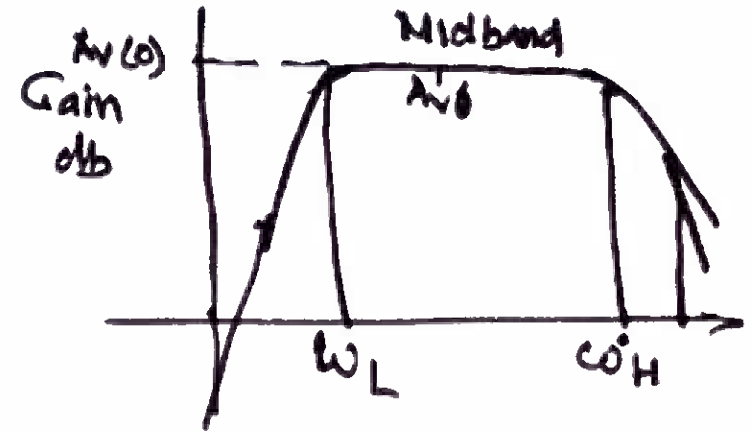
High Frequency Response of a MOS Amplifier (Common Source Type)



CDEEP
IIT Bombay

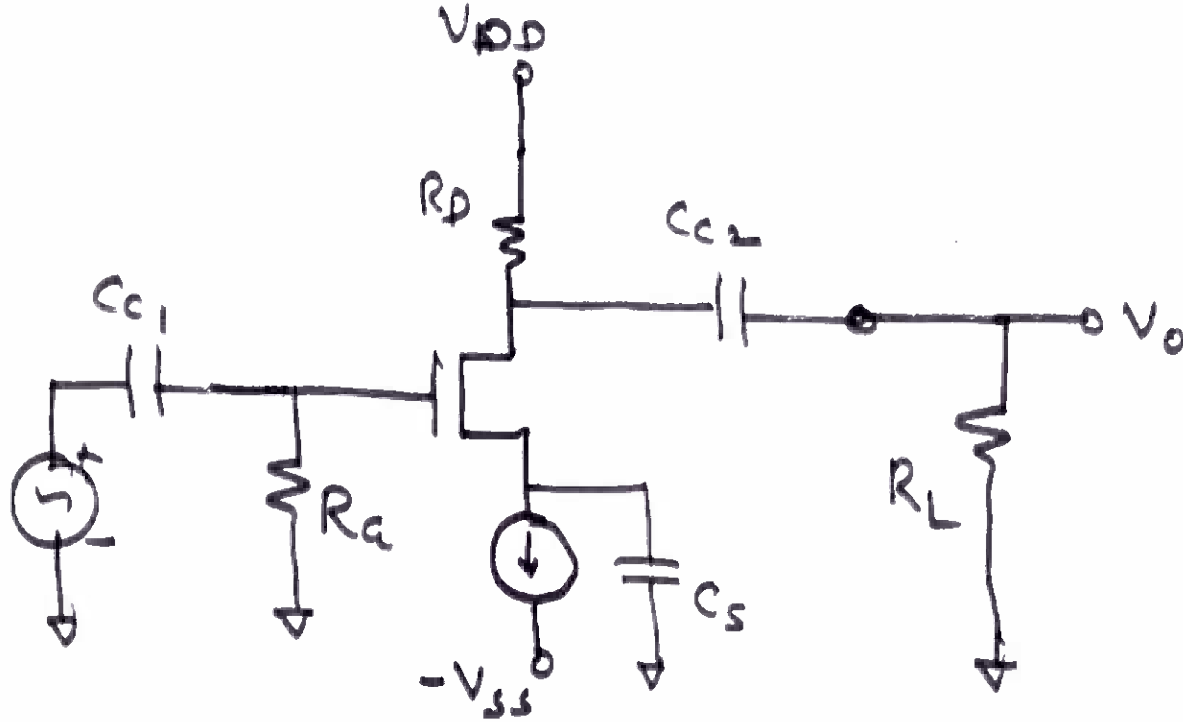

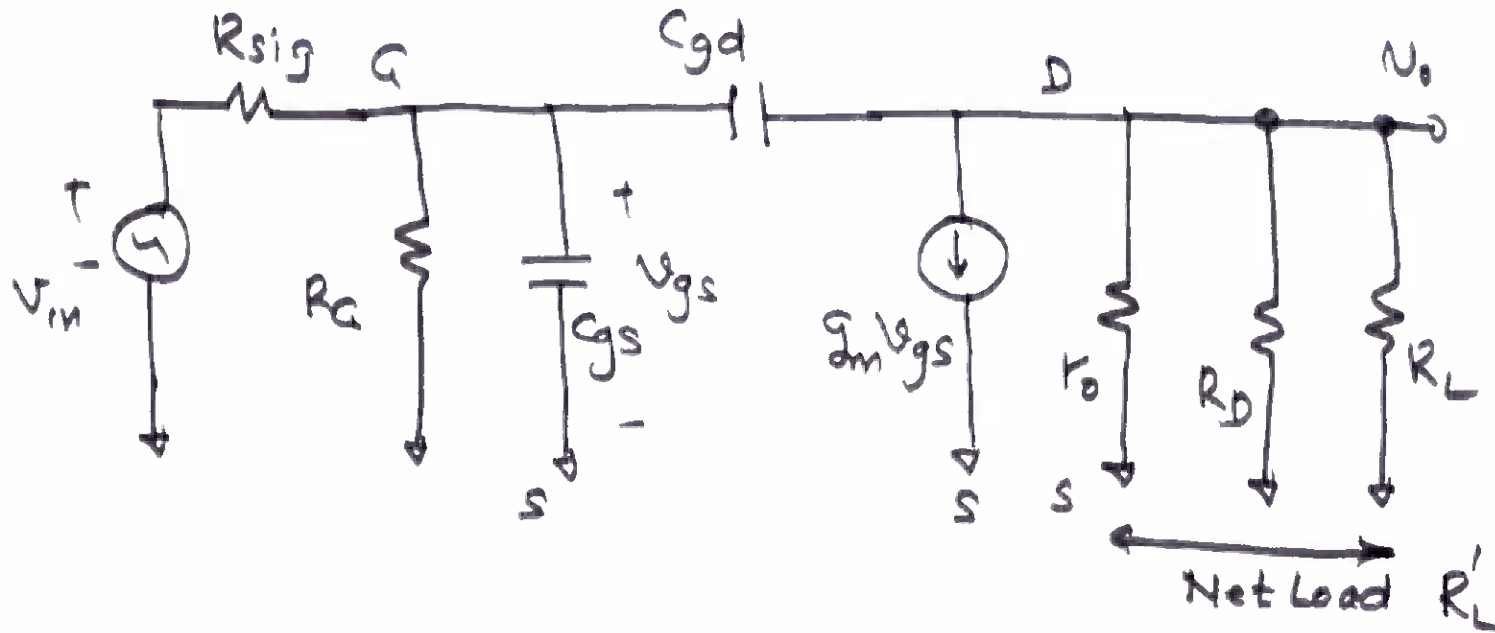
$$\text{Bandwidth} = \omega_H - \omega_L$$



①

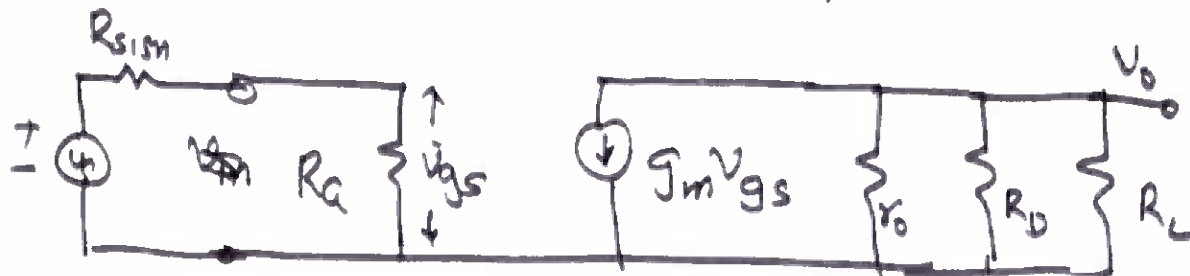DC Gain A_{vo} : — All capacitors are omitted appropriately. ($R_G \gg R_{sig}$)
Normally



$$R'_L = r_o \parallel R_D \parallel R_L$$

$$A_{v(0)} = -\frac{R_G}{R_G + R_{sig}} \cdot g_m R'_L$$


$$v_{gs} = \frac{R_C}{R_C + R_{s_{ign}}} \cdot v_{in} \quad \text{--- (1)}$$

Then

$$v_o = -g_m v_{gs} \cdot R'_L \quad \text{--- (2)}$$

$$\therefore \frac{v_o}{v_{gs}} = A'_{v_o} = -g_m R'_L \quad \text{--- (3)}$$

Using Miller's theorem between GND

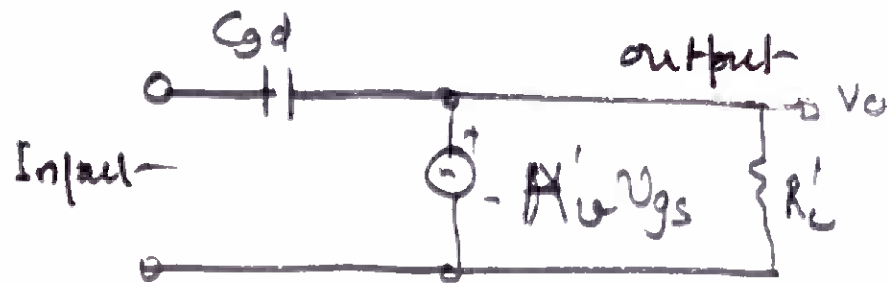


$$= C (1 + g_m R'_L) C_{gd}$$




CDEEP
IIT Bombay

Slide No: 4

Hence Equivalent Ckt is

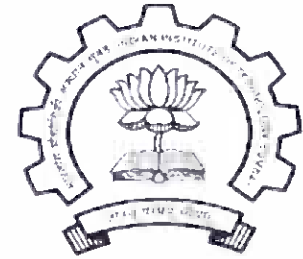

CDEEP
IIT Bombay

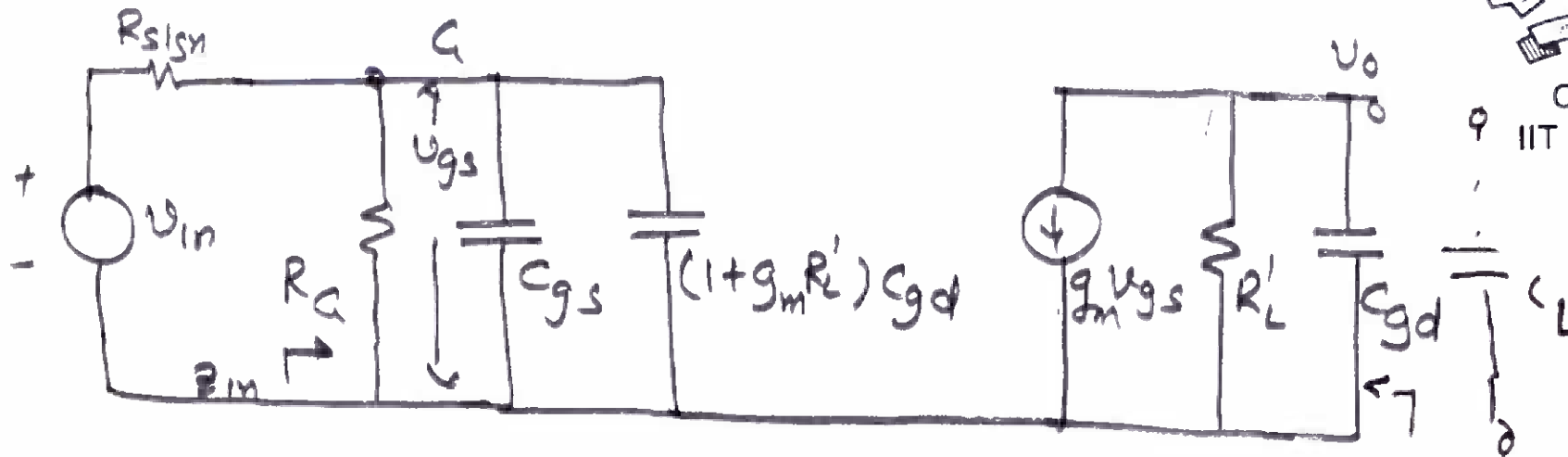

$$\therefore Z_{in} = \left(R_a \parallel \frac{1}{C_{eq} s} \right) \quad \text{where } C_{eq} = C_{gs} + (1 + g_m R'_L) C_{gd}$$

$$\therefore v_{gs} = \frac{Z_{in}}{Z_{in} + R_{s|n}} \cdot v_{in}$$

Slide No: 5


$$z_o = (R_L' \parallel \frac{1}{C_{gd} s})$$

$$\frac{1}{z_o} = \frac{1}{R_L'} + C_{gd} s$$

$$\therefore z_o = \frac{R_L'}{1 + R_L' C_{gd} s}$$

&
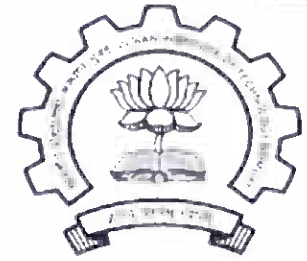
$$z_{in} = \frac{R_c}{1 + R_c C_{ce} s}$$



CDEEP
IIT Bombay

Course Name


Analog Circuits

Lecture No.

11

Instructor's Name

Prof. A. N. Chandorkar

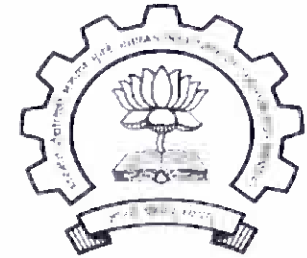


$$A_v(s) = \frac{A_{vo}(0)}{(1 + R_L' C_{gd} s) \left[1 + \frac{R_{sig}}{R_g} + R_{sig} C_{eq} s \right]}$$

$$= \frac{A_{vo}(0)}{R_L' C_{gd} \left(s + \frac{1}{R_L' C_{gd}} \right) R_{sig} C_{eq} \left[s + \frac{\left(1 + \frac{R_{sig}}{R_g} \right)}{R_{sig} C_{eq}} \right]}$$

$$= \frac{A_{vo}(0)}{R_L' R_{sig} C_{gd} C_{eq}} \cdot \frac{1}{\left(s + \frac{1}{R_L' C_{gd}} \right) \left(s + \frac{1}{R_{in} C_{eq}} \right)}$$

$$R_{in}' = R_g \parallel R_{sig}$$

Slide No: 7

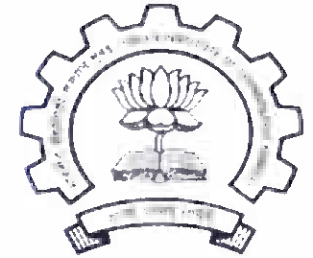

CDEEP
IIT Bombay

We define $\omega_0 = \frac{1}{R_{in}' C_{eg}}$

$$\omega_1 = \frac{1}{R_L' C_{gd}}$$

$$A_V(s) = \frac{A_V(0)}{R_{sig}' R_L' C_{gd} C_{eg}} \cdot \frac{1}{(s + \omega_0)(s + \omega_1)}$$

$$= [A_V(0) \omega_0 \omega_1] \cdot \frac{1}{(s + \omega_0)(s + \omega_1)}$$

$$\omega = \omega_0$$

$$j\omega + 1 = 0$$

$$= A_{midband} = A_V(0) \cdot \frac{1}{\left(\frac{s}{\omega_0} + 1\right) \left(\frac{s}{\omega_1} + 1\right)}$$

$$\begin{aligned} \therefore V_o &= -g_m z_o \cdot V_{gs} \\ &= -\frac{g_m R_L'}{1 + R_L' C_{gd} s} \cdot \frac{R_G / (1 + R_G C_{gs} s)}{\frac{R_G}{1 + R_G C_{gs} s} + R_{sig}} \cdot V_{in} \end{aligned}$$

$$\therefore A_{v_g}(s) = \frac{V_o(s)}{V_{in}(s)} = -\frac{g_m R_L'}{1 + R_L' C_{gd} \cdot s} \cdot \frac{R_G}{R_G + R_{sig} (1 + R_G C_{gs} s)}$$

$$\frac{A_{v_g}(0)}{A_{v_g}'(0)}$$

$$A_{v_g}'(0)$$

$$= -\frac{A_{v_g}(0) \cdot R_G}{(1 + R_L' C_{gd} s) [R_G + R_{sig} (1 + R_G C_{gs} s)]}$$



We observe from G values & Components

$$\omega_{p1} \ll \omega_{p2}$$

where

$$\omega_{p1} = \frac{1}{R_{s15} (1 + g_m R_L') C_{gd} + R_{s15} C_{gs} + R_L' (C_{gd} + C_{db})}$$

Then we call ω_{p1} as Dominant Pole.



Zero's Presence:

$$\omega_z = \frac{g_m}{C_{gd}} \approx \frac{10^3}{10^{12}} \left(\frac{g_m \omega_z}{\omega} + 1 \right)$$

$$f_z \approx \frac{1}{2\pi} \times 10^9 = 1.5 \times 10^8$$

$$\sqrt{4+1}$$


Full Circuit Analysis without use of Miller's Theorem**

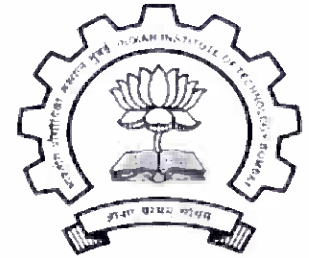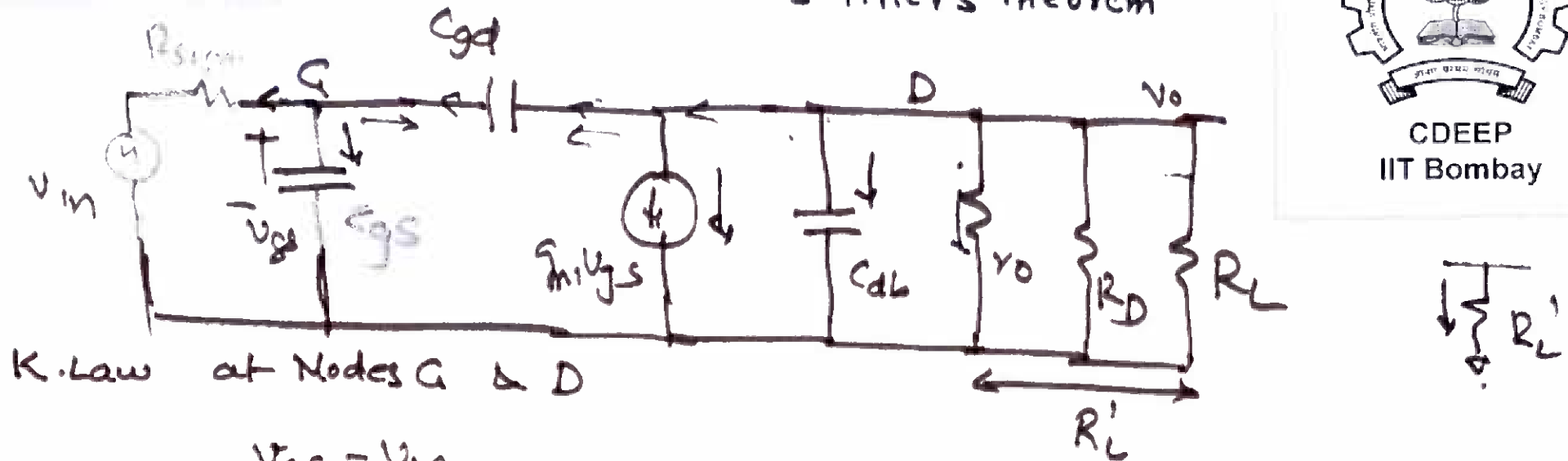CDEEP
IIT Bombay

$$\frac{V_{gs} - V_{in}}{R_{sigm}} + V_{gs} \cdot C_{gs} \cdot s + (V_{gs} - V_o) C_{gd} \cdot s \quad \text{--- (i)}$$

$$(V_o - V_{gs}) C_{ds} \cdot s + g_m V_{gs} + V_o \left(\frac{1}{R'_L} + C_{db} \cdot s \right)$$

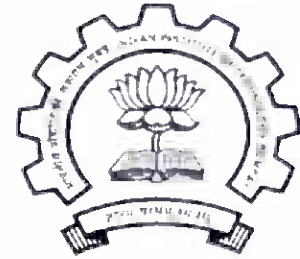** Miller Theorem's use earlier, we lost track of 'zero'. --- (ii)



From equ. (ii)

$$v_{gs} = - \frac{v_o (C_{gd} \cdot s + \frac{1}{R_L'} + C_{db} \cdot s)}{g_m - C_{gd} \cdot s}$$

substituting this in (i)

$$\frac{-v_o}{g_m - C_{gd} \cdot s} \cdot \left[\frac{1}{R_{si}} + (C_{gs} + C_{gd}) \cdot s \right] \left[(C_{gd} + C_{db}) \cdot s \right]$$

$$-v_o C_{gd} \cdot s = \frac{v_{in}}{R_{si} \cdot s}$$

$$\therefore \frac{v_o(s)}{v_{in}(s)} = A_v(s) = \frac{(C_{gd} \cdot s - g_m) R_L'}{R_{si} R_L' s^2 + [R_{si} (1 + g_m R_L') C_{gd} + R_{si} C_{gs} + R_L' (C_{gd} + C_{db})] \cdot s}$$


$$\text{Where } \Sigma = C_{gd} C_{gs} + C_{gs} C_{db} + C_{gd} C_{db}$$

Looking at Denominator

$$D = \left(\frac{s}{\omega_{p1}} + 1 \right) \left(\frac{s}{\omega_{p2}} + 1 \right)$$

$$= \frac{s^2}{\omega_{p1} \omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1$$
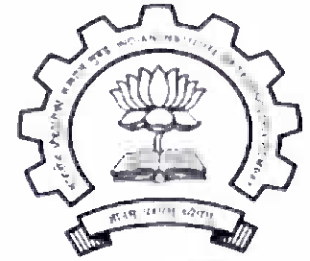
$$\frac{1}{as^2 + bs + c} \equiv k \frac{1}{(s + \omega_1)(s + \omega_2)}$$



CDEEP
IIT Bombay

Slide No: 13

Thus apart from Two Poles, the circuit has a Zero at

$$s_z = \frac{g_m}{C_{gd}}$$

The Two poles, include 'Dominant Pole' which we found out using ① Dominant Pole approximation and ② Use of Miller's Theorem

The Complete Nodal Analysis, thus is more 'Accurate' as it does not do any 'Assumption'.



CDEEP
IIT Bombay

Course Name
Analog Circuits

Lecture No.


11

Instructor's Name
Prof. A. N. Chandorkar


Frequency Response of the CE Amplifier





CDEEP
IIT Bombay

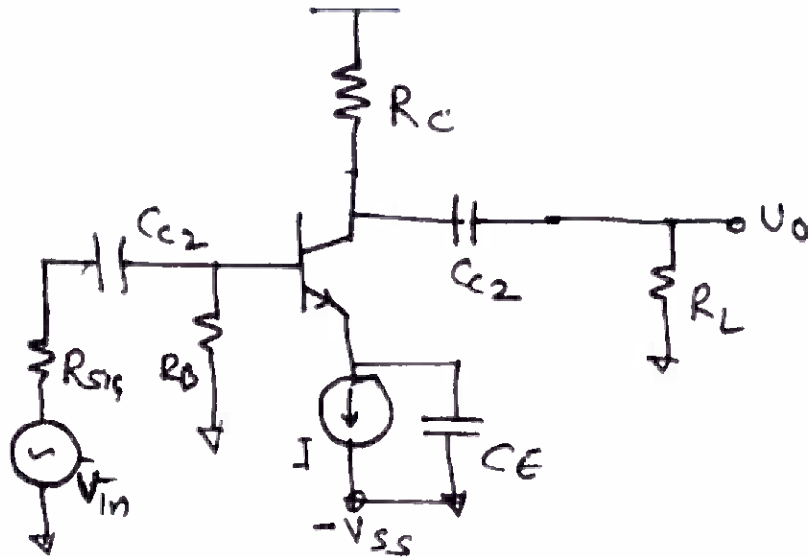

Gain
indb

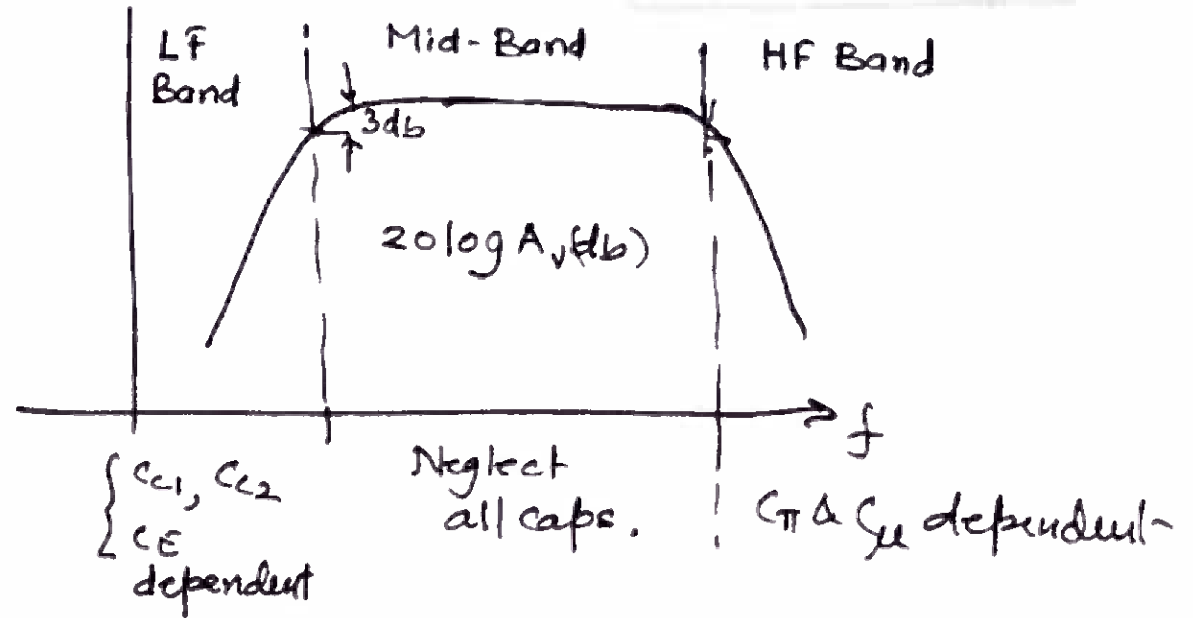


Eq. CKT is:

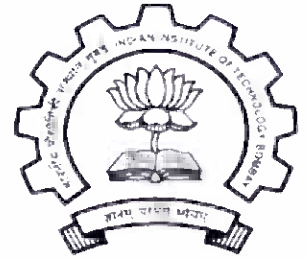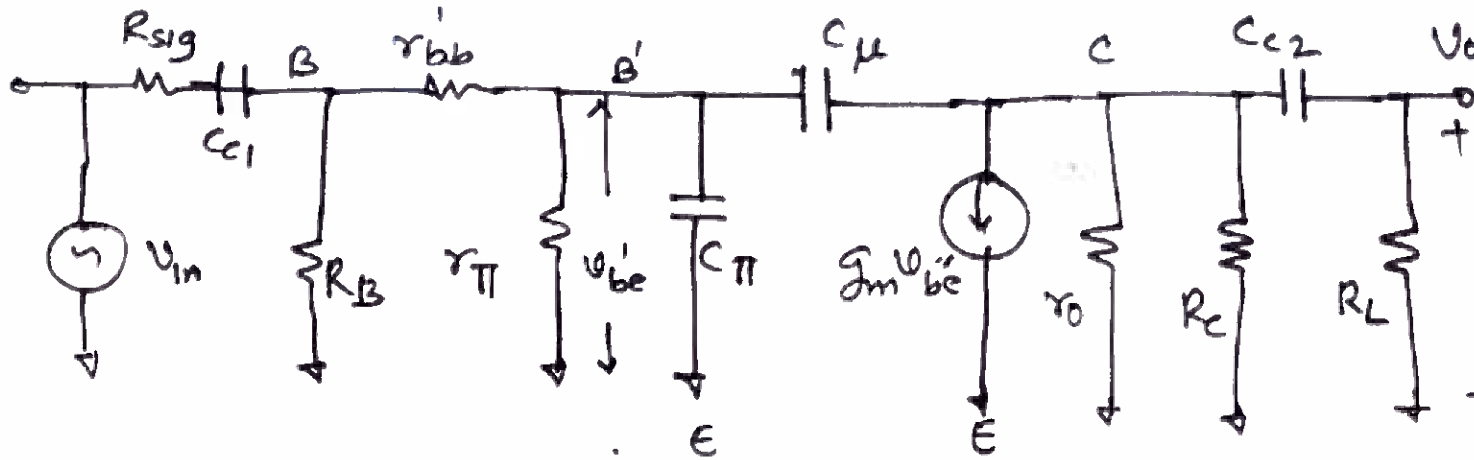

CDEEP
IIT Bombay

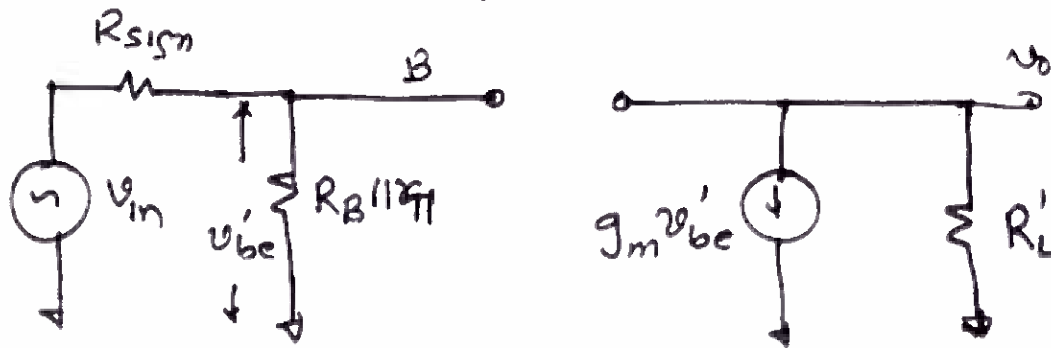① DC Gain : Neglect all capacitors appropriately.
Neglect r_{bb}' as we assume $i_b = 0$ (V. small.)



$$\frac{1}{R_L'} = \frac{1}{r_o} + \frac{1}{R_c} + \frac{1}{R_L}$$

$$v_o = -g_m R_L' v_{bc}'$$

$$v_{bc}' = \frac{R_{B\pi}}{R_{S\pi} + R_{B\pi}} v_{in}$$

where $R_{B\pi} = R_B \parallel r_{\pi}$

$$\therefore v_o = -g_m R_L' \cdot \frac{R_{B\pi}}{R_{B\pi} + R_{S\pi}} \cdot v_{in}$$

$$\therefore A_v(\omega) = \frac{v_o}{v_{in}} = -\frac{R_{B\pi}}{R_{B\pi} + R_{S\pi}} \cdot g_m R_L'$$



Slide No: 17


HF response

We have values of C_{c1} & C_{c2} high enough
to give $\frac{1}{j\omega C_{c1}}$ & $\frac{1}{j\omega C_{c2}}$ at high frequencies
 \Rightarrow Short ckt.

Similarly Bypass Capacitor C_E too is high & at High Freq.
its impedance = 0



In fact the values of C_{c1} , C_{c2} & C_E are normally v. high
so that they provide 'short' ckt from Midband to HF.

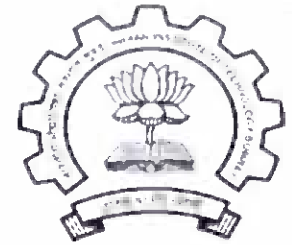Using Miller's theorem for C_{μ} , we have equivalent-
ckt of the BJT Amplifier as



CDEEP
IIT Bombay

Slide No: 18

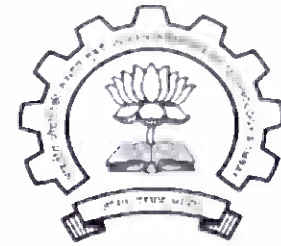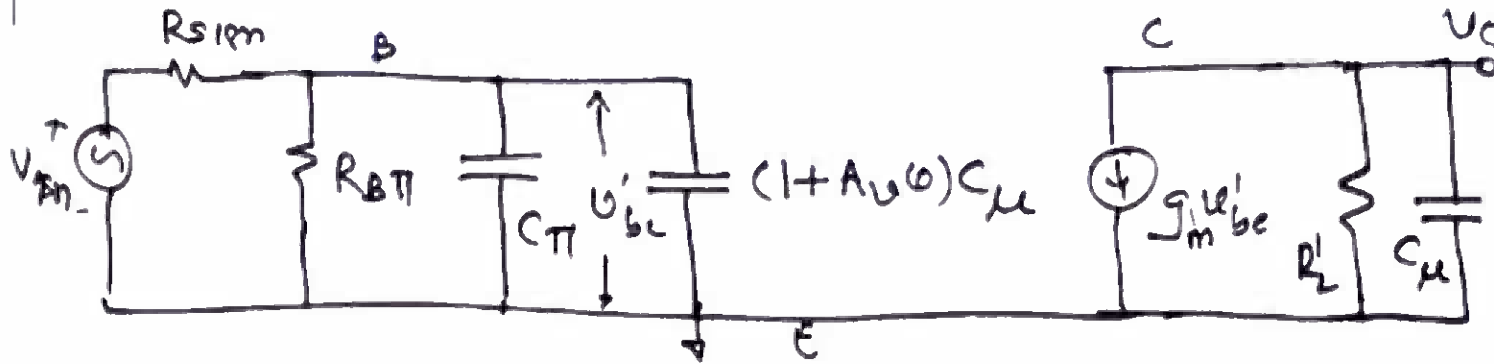

CDEEP
IIT Bombay

$$\text{Load Imp.} = R'_L \parallel \frac{1}{C_{\mu} s} = \frac{R'_L}{1 + R'_L C_{\mu} s}$$

$$\text{Further } v'_{be} = \frac{\left(R_{B\pi} \parallel \frac{1}{C_{\pi} \mu s} \right)}{\left(R_{B\pi} \parallel \frac{1}{C_{\pi} \mu s} \right) + R_{s\text{igm}}} \cdot v_{in}$$

$$\text{where } C_{\pi\mu} = \frac{1}{C_{\pi} + C_{\mu}(1+A_{vo})}$$

$$\therefore v_o = - \frac{g_m R'_L}{1 + R'_L C_{\mu} s} v'_{be}$$


Slide No: 19

$$R_{B\pi} \parallel \frac{1}{C_{\pi\mu}}$$

$$\text{or } v_o = - \frac{g_m R_L'}{1 + R_L' C_{\mu} s} \left(\frac{R_{B\pi}}{1 + R_{B\pi} C_{\pi\mu} s} \right) v_m$$
$$R_{sig.} + \frac{R_{B\pi}}{(1 + R_{B\pi} C_{\pi\mu} s)}$$

$$\text{or } \frac{v_o}{v_{in}} = A_v(s) = - \frac{g_m R_L'}{1 + R_L' C_{\mu} s} \cdot \frac{R_{B\pi}}{R_{B\pi} + R_{sig} + R_{sig} R_{B\pi} C_{\pi\mu} s}$$
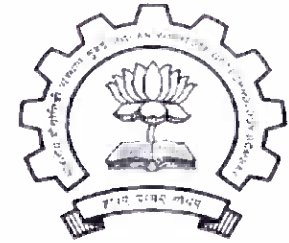
$$A_v(s) = \frac{-g_m R_L'}{1 + \frac{R_s}{R_{B\pi}} + \left[R_s C_{\pi\mu} + \left(1 + \frac{R_L}{R_{B\pi}}\right) R_L' C_{\mu} \right] s + R_s R_L' C_{\mu} C_{\pi\mu} s^2}$$



CDEEP
IIT Bombay

There are Two Poles

$$\omega_2 = \frac{1}{R_L' C_\mu} \quad (\text{output Pole})$$

$$b \quad \omega_1' = \frac{1}{\frac{1}{R_S C_{\pi\mu}} \left(1 + \frac{R_S}{R_{B\pi}}\right)}$$

$$\text{or } \omega_1 = \frac{\left(1 + R_S/R_{B\pi}\right)}{R_S C_{\pi\mu}} \approx \frac{1}{R_S' C_{\pi\mu}}$$

$$= \frac{1}{R_S' \left[C_{\pi} + \{1 + A_v(\omega)\} C_{\mu} \right]}$$

$$R_S' = \frac{R_S}{R_S \parallel R_{B\pi}}$$


CDEEP
IIT Bombay

Slide No: 21

As $A_v(\omega) \gg 1$

$\omega_2 \gg \omega_1$

$\therefore \omega_1$ is Dominant Pole

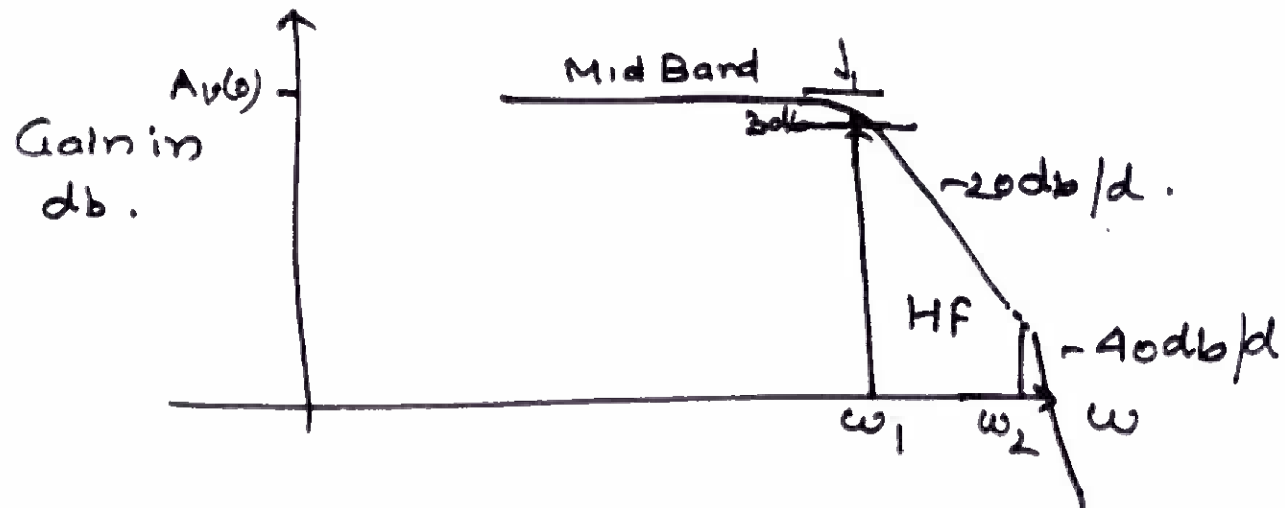




CDEEP
IIT Bombay

Low frequency Response

Due to C_{c1} , C_{c2} and C_E . We use

Superposition Theorem.

C_{c1} :-

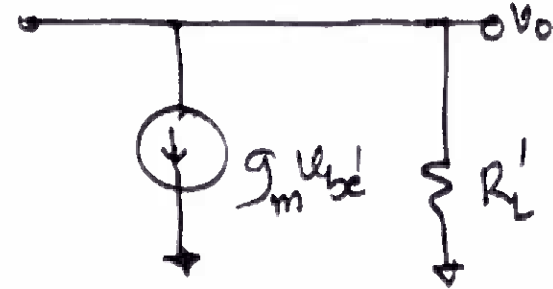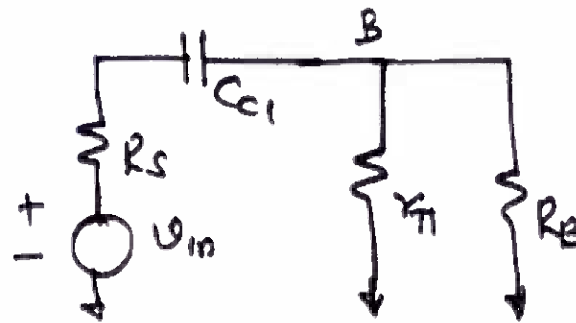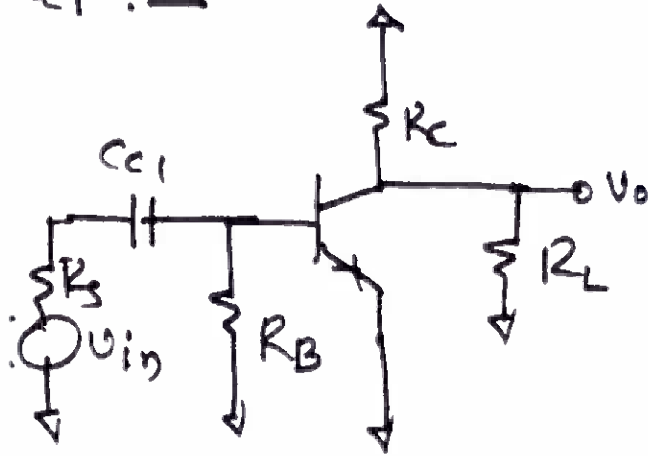


\therefore Pole is on the Input Side is

$$\omega_{p1} = 2\pi f_{p1} = \frac{1}{C_{c1} [R_{B\pi} + R_s]}$$



CDEEP
IIT Bombay

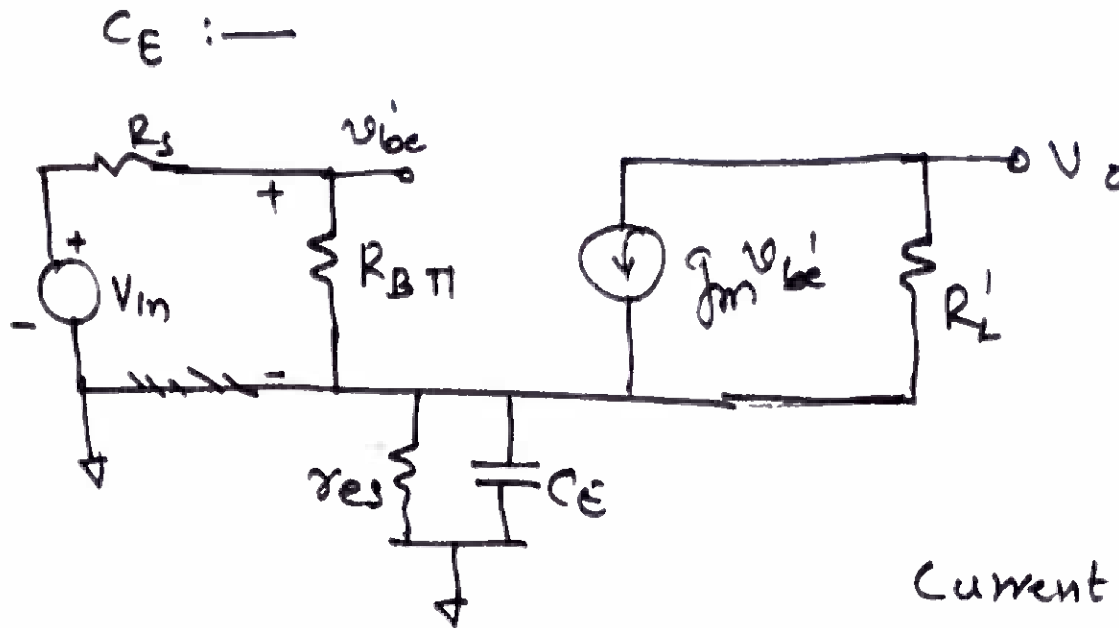


$$\begin{aligned} g_m v'_{be} &\supset g_m v_{\pi} = \frac{v_{\pi}}{R_{B\pi}} \\ &= g_m \cdot i_b \cdot R_{B\pi} \\ &= \beta i_b \frac{R_{B\pi}}{\beta} \end{aligned}$$

Current through $(C_E \parallel r_{es})$

$$= i_b + \beta i_b = (\beta + 1) i_b$$

Solving, Second Pole will be

$$\omega_{p2} = \frac{1}{C_E \left[r_{es} + \frac{R_{B\pi}}{\beta + 1} \right]} = \frac{\beta + 1}{R_{B\pi} C_E} \quad (r_{es} \text{ Small})$$


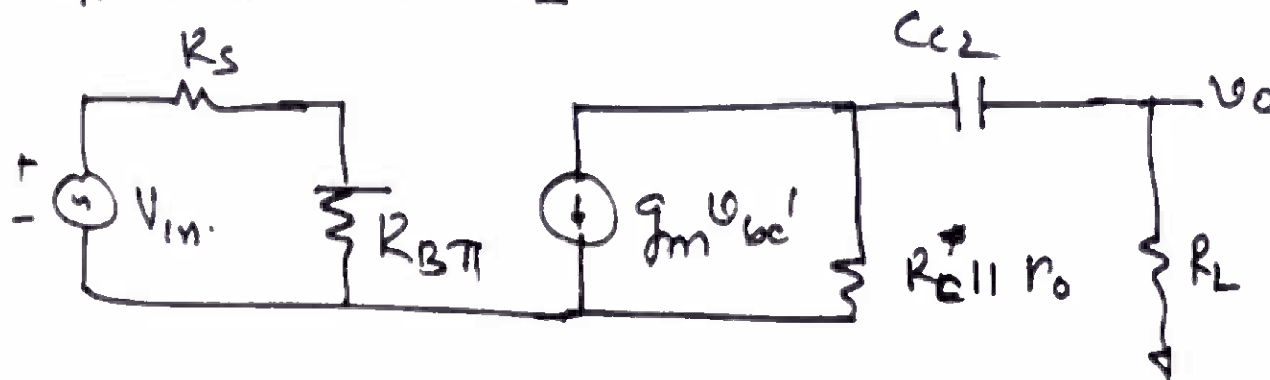
Effect due to C_{c2} 

$$\therefore \text{output pole } \omega_{p3} = \frac{1}{C_{c2} (R_{c1} \parallel r_o + R_L)}$$

It is observed that for Typical BJT Parameters & Values of Bias & Load networks,

$$\omega_{p2} \gg \omega_{p3} \gg \omega_{p1} \quad \omega_{p2} > \omega_{p1} > \omega_{p3}$$

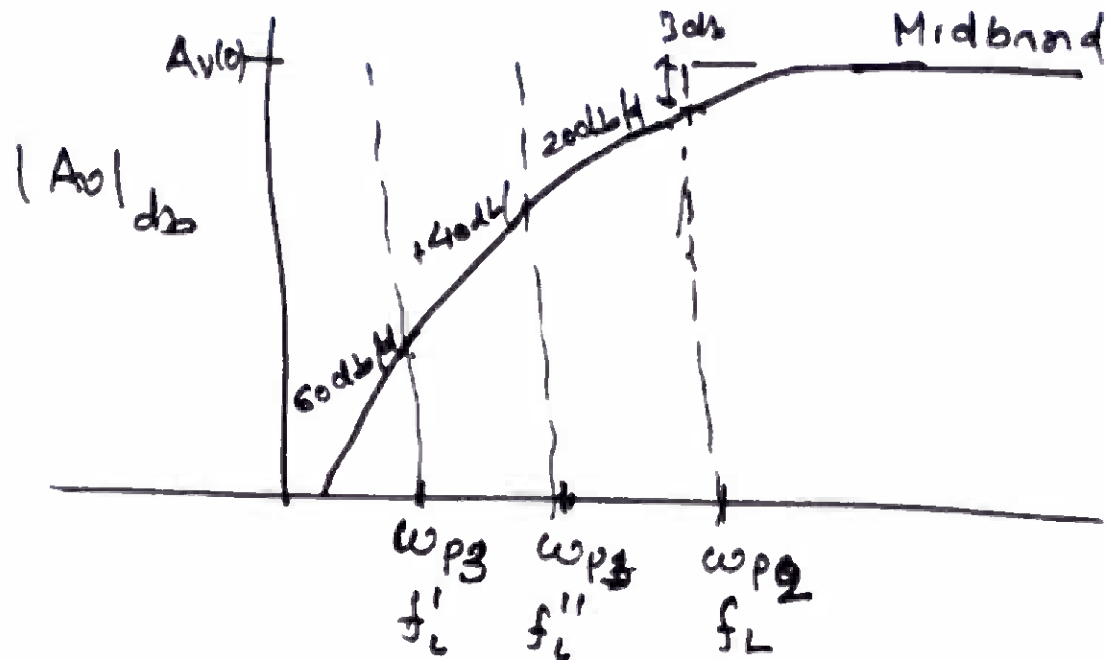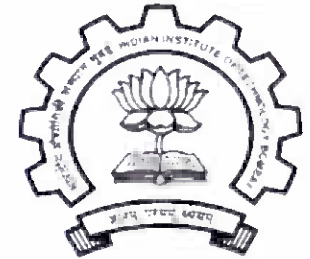$\therefore C_E$ dominates the f_L value's estimation



LF response

Clearly ω_{p3} is of reference for evaluating Bandwidth

$$\text{Bandwidth} = \underline{\underline{\omega_1 - \omega_{p3}}} = f_H - f_L$$