
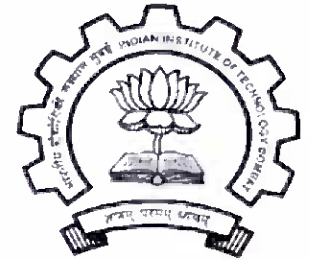


Low frequency Response of CS Amplifier

CDEEP
IIT Bombay

AC circuit :

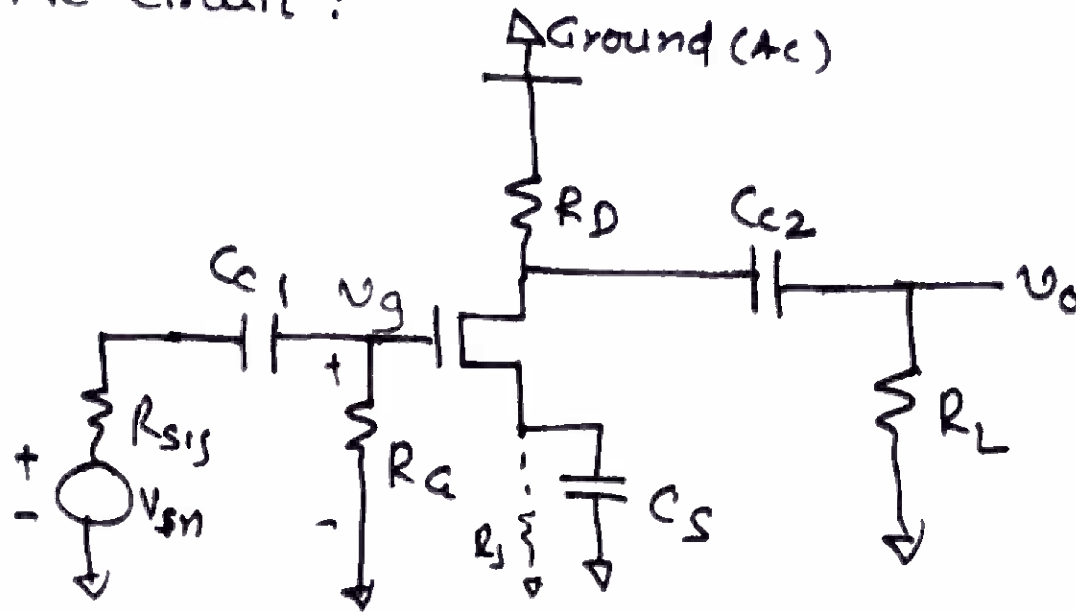


$$v_g = \frac{R_G}{R_G + R_{s1s} + \frac{1}{s C_{c1}}} v_{in} = \frac{R_G}{R_G + R_{s1s}} \frac{s}{s + \frac{1}{C_{c1}(R_G + R_{s1s})}} v_{in}$$

$$\text{Clearly } \frac{v_o}{v_{in}} = R_k \cdot \frac{s}{s + \omega_0} = \frac{1}{1 + \frac{\omega_0}{s}}$$


$$\text{where } R_k = \frac{R_c}{R_c + R_{s1s}}, \quad \omega_0 = \frac{1}{C_1 (R_c + R_{s1s})}$$

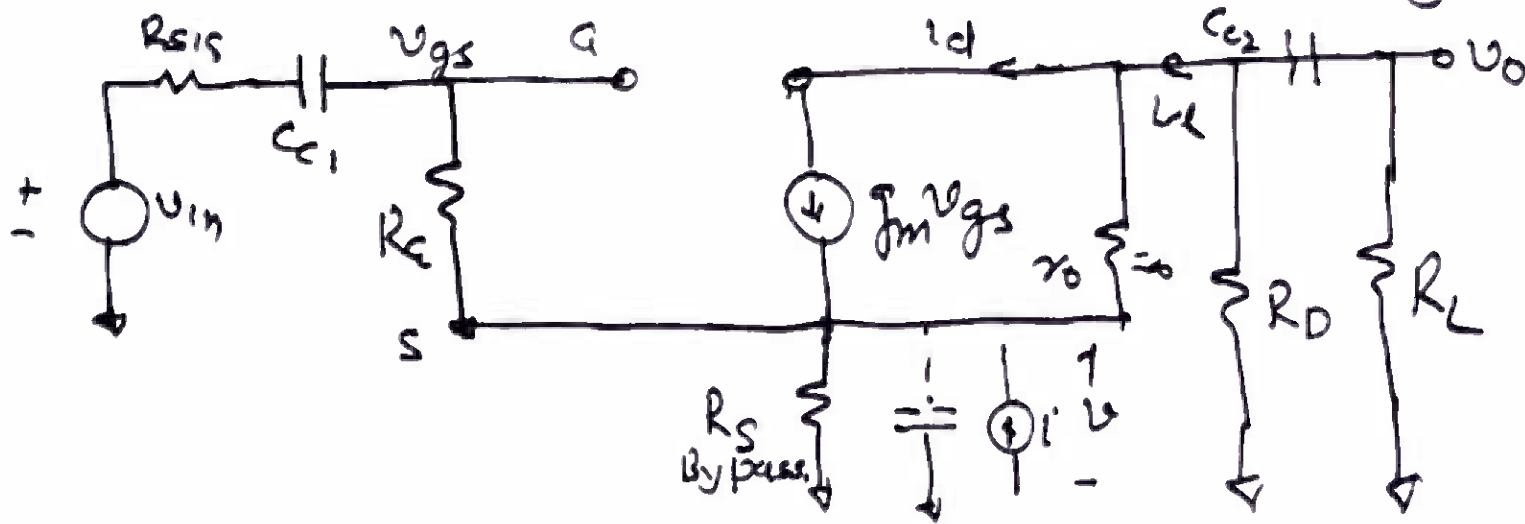∴ This transfer function represents a High Pass Filter.


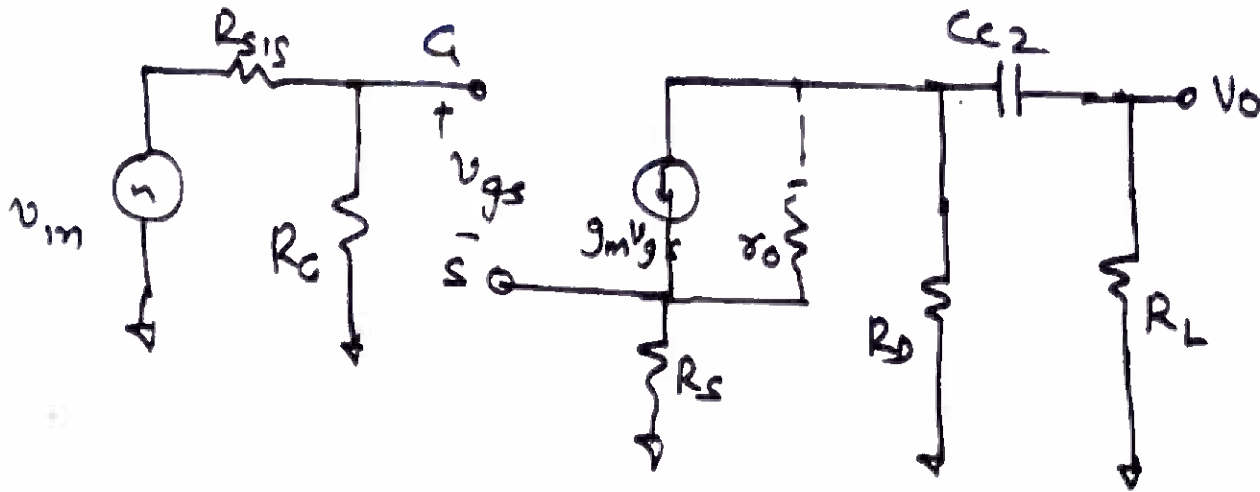
$$\omega_{p1} = \frac{1}{(R_c + R_{s1s}) C_{c1}}$$





Assume
 $g_m v_{gs} > \frac{V_o}{r_o}$

$$v_{in} = v_{gs} + g_m v_{gs} \cdot R_S = (1 + g_m R_S) v_{gs}$$


For DC Gain

$$|A_{vo}| = \frac{V_o}{v_{in}} = \frac{g_m (R_D || R_L)}{1 + g_m R_S}$$



CDEEP
IIT Bombay

Using zero time constant method

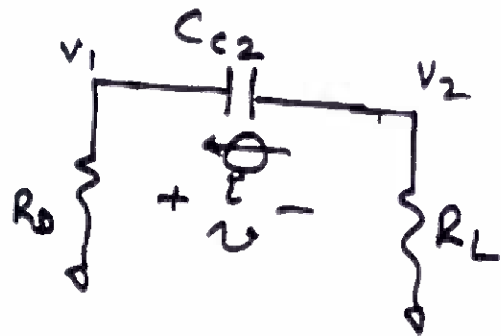Resistance seen by C_{c2} (short input-

$$\therefore R_{eq} = R_{cc2} = R_D + R_L$$

$$\text{as } V_1 = i R_D \quad \& \quad V_2 = -i R_L$$


$$\therefore -\frac{V_2 - V_1}{i} = \frac{U}{i} = R_{eq} = R_D + R_L$$

$$\therefore \tau_{cc2} = R_{cc2} \cdot C_{c2}$$

$$\therefore f_{L_{cc2}} = \frac{1}{2\pi (R_{cc2} C_{c2})}$$

$$\text{Similarly } f_{L_{cs}} = \frac{g_m / C_s}{2\pi}$$

$$\text{or } \omega_{L_{cs}} = \frac{g_m}{C_s}$$

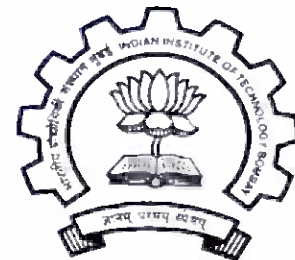
CDEEP
IIT Bombay

Hence we have Three Poles


$$\omega_{p1_{C_{c1}}} = \frac{1}{(R_a + R_{s1})C_{c1}}$$

$$\omega_{p2_{C_s}} = \frac{g_m}{C_s}$$
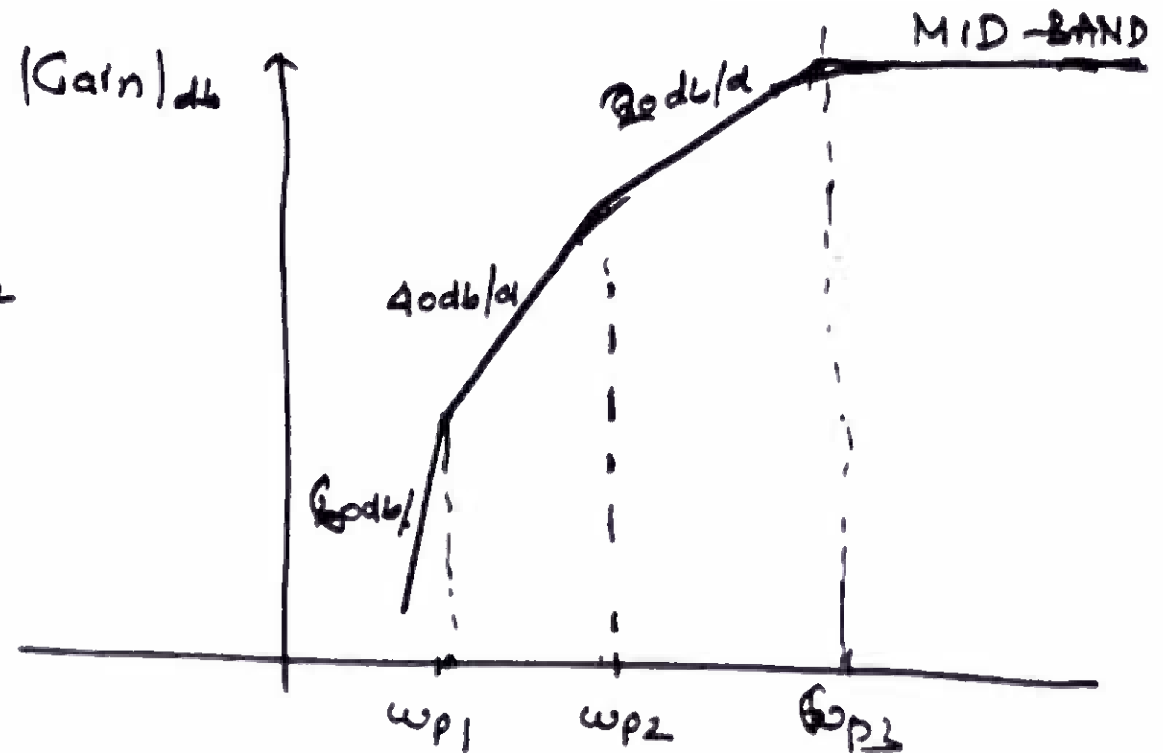
$$\omega_{p3_{C_{c2}}} = \frac{1}{(R_D + R_L)C_{c2}}$$



CDEEP
IIT Bombay

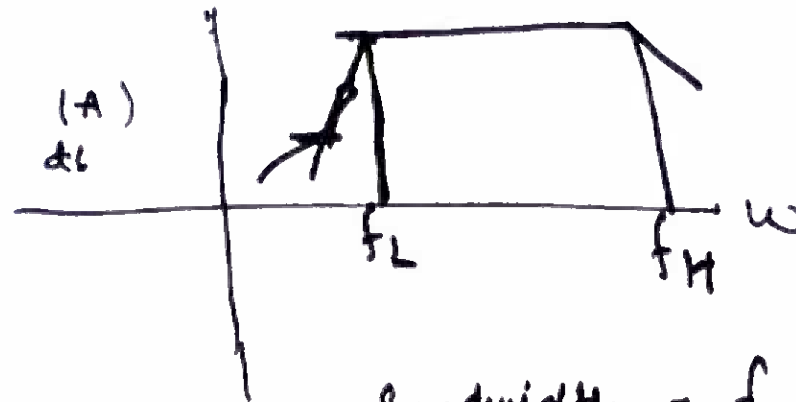


$$\text{Bandwidth} = f_H - f_L$$

1 MHz - 600 kHz





CDEEP
IIT Bombay

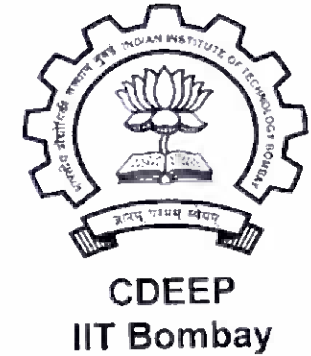

Zero-Value Time Constant Analysis To Get Dominant Pole of a System


- ① Evaluate 'Resistance' as seen by a capacitor after removing (open or short) all other capacitors,
- ② Then the associated Time-Constant = $R_{\text{seen}} \cdot C_{U1}$
- ③ Evaluate similar to ① all other resistances seen by capacitances and evaluate respective Time-Constants,
- ④ Then get net Time constant $\tau = \sum \tau_i$
- ⑤ Then the pole frequency $\omega_p = \frac{1}{\tau}$ is the Dominant Pole.

Example of 2-Stage Amplifier (CE Type)

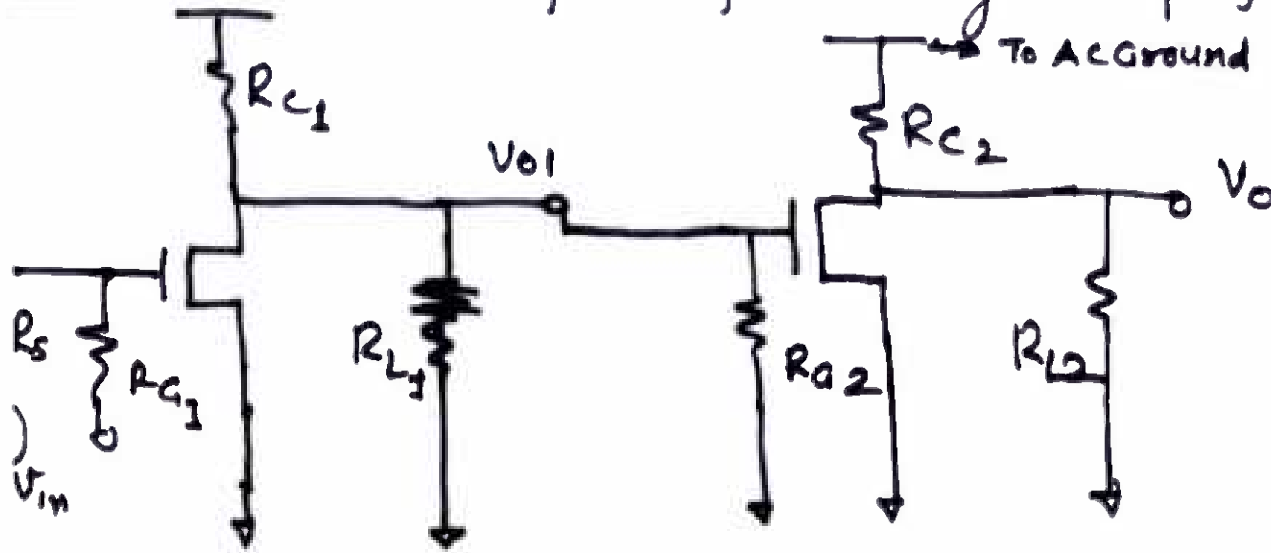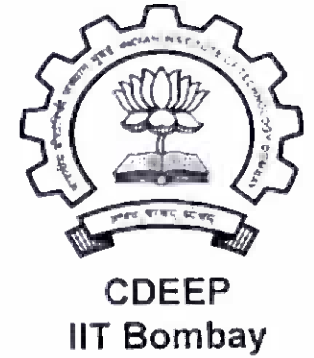

AC Diagram

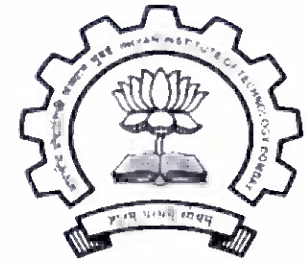We wish to know Dominant pole of this system




CDEEP
IIT Bombay


Slide No: 9

Zero-Value Time Constant Analysis

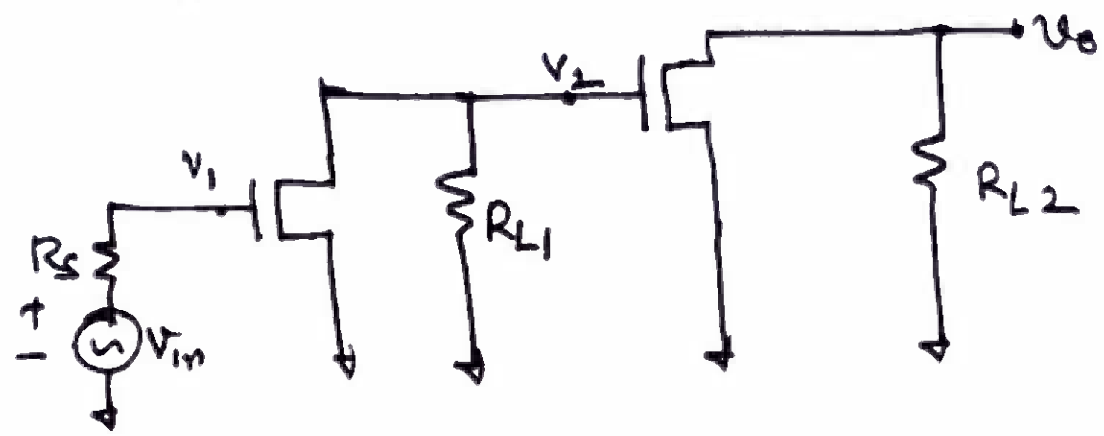Ex. Multistage Cascode Amplifier (AC circuit)



Equivalent Circuit

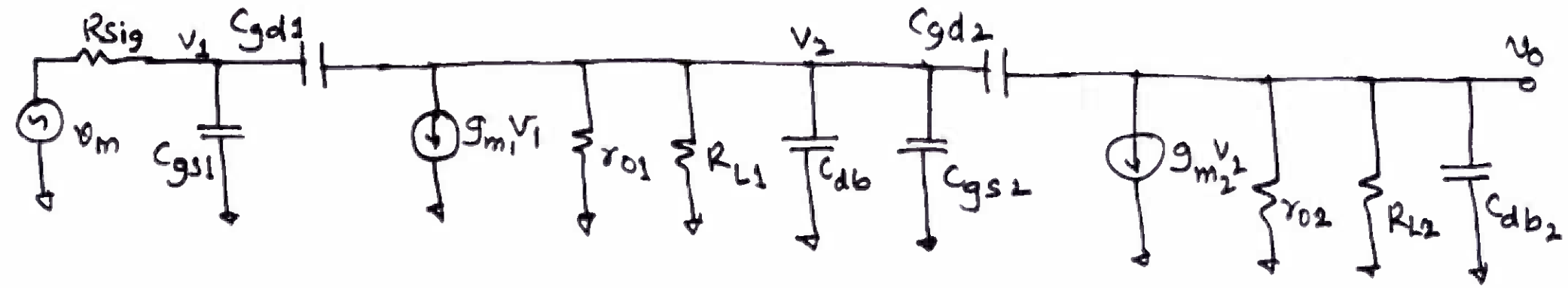

Approx. Method to estimate presence of a Dominant Pole

If there are no Dominant Zeros, then

$$\omega_{-3db} = p_1 \quad \text{Dominant pole}$$

and $p_1 < p_2 < p_3 \dots$. We observe that Gain T.F is

$$A_V(s) = \frac{N(s)}{D(s)} = \frac{A_{vo}}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right) \dots \left(1 - \frac{s}{p_n}\right)}$$

Typical TF

$$= \frac{a_0 + a_1 s + a_2 s^2 + \dots + a_n s^n}{1 + b_1 s + b_2 s^2 + \dots + b_n s^n}$$


$$s \left(\frac{1}{p_1} + \frac{1}{p_2} \right)$$

$$\therefore b_1 = \sum_{i=1}^n \left(-\frac{1}{p_i} \right) = \left| \frac{1}{p_1} \right|$$




CDEEP
IIT Bombay
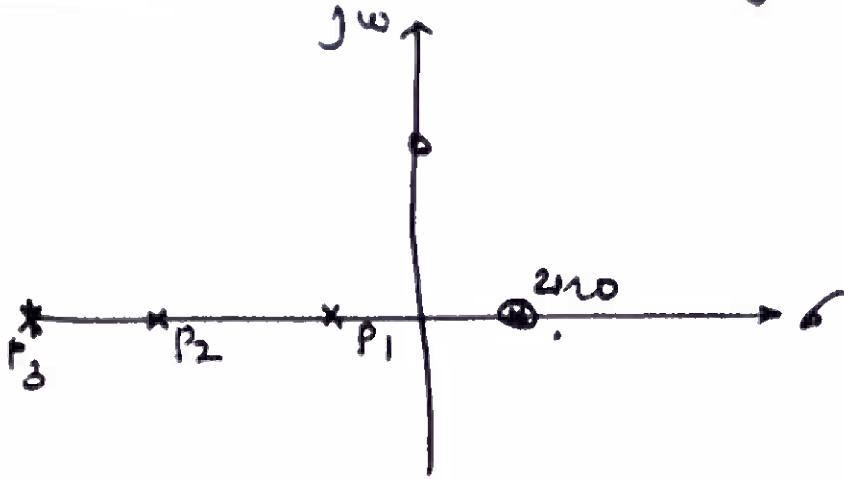
$$s = \sigma + j\omega \quad (\text{s-plane})$$



$$|A(j\omega)| = \frac{A_{v0}}{\sqrt{1 + \left(\frac{\omega}{p_1}\right)^2}}$$

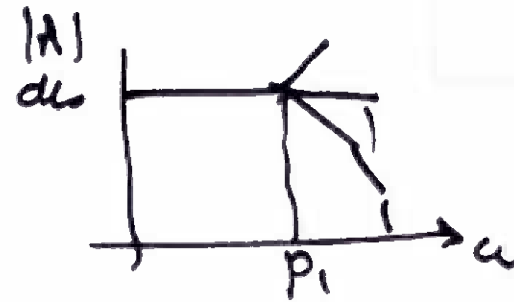

\therefore Bode Plot is correct
as long as $\omega \leq |p_1|$



CDEEP
IIT Bombay

In zero-value time constant analysis every capacitor sees some equivalent

Resistance, R , then $\tau = R_{eq} \cdot C$

We evaluate R_{eq} for each capacitor and

get $\tau_1 = R_{eq1} C_1$, $\tau_2 = R_{eq2} C_2$..., $\tau_n = R_{eqn} C_n$



Then net $\tau = \sum \tau_i$ & then the Dominant Pole p_1

$$p_1 = \frac{1}{\tau}$$

For our circuit we evaluate R_{eq} seen by C_{gd1} ; ... C_{db2}

(i) $R_{gd01} = R_{eq}$ seen by C_{gd1}

Here $R_{gd01} = \frac{v}{i}$

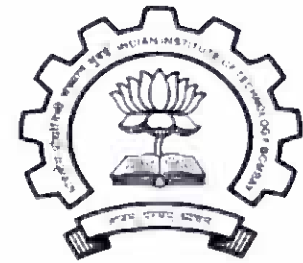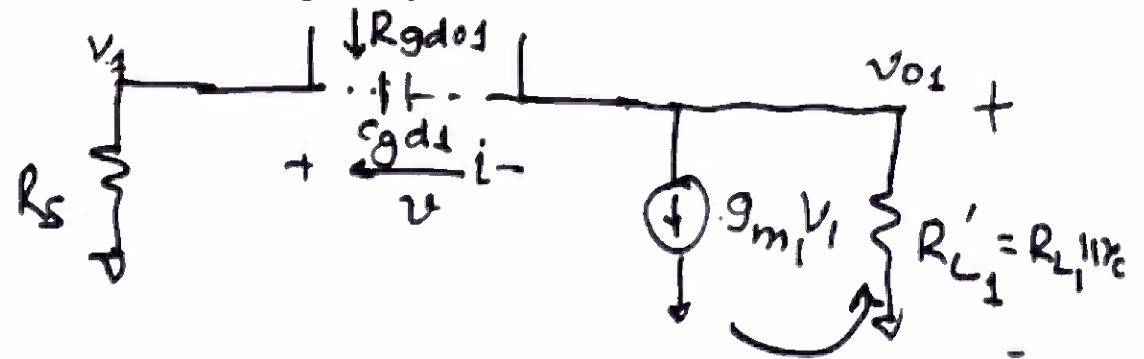

$$i \cdot R_S = V_1 \quad \text{--- (i)}$$

$$(-i - g_{m1} V_1) R_{L1}' = V_{o1} \quad \text{--- (ii)}$$

$$\Delta R_{gdol} = \frac{V_1 - V_{o1}}{i} \quad \text{--- (iii)}$$

$$\text{From (ii)} \quad - (i + g_{m1} V_1) R_{L1}' = V_{o1}$$

$$\therefore - \frac{V_{o1}}{i} = (1 + g_{m1} R_S) R_{L1}' \quad \text{--- (iv)}$$

$$+ \frac{V_1}{i} = R_S \quad \text{--- (v)}$$

$$\therefore \frac{V_1 - V_{o1}}{i} = R_S + (1 + g_{m1} R_S) R_{L1}'$$

$$\therefore R_{gdol} = R_S + R_{L1}' + g_{m1} R_S R_{L1}'$$



Slide No: 14

Similarly R_{gd2} is seen by C_{gd2} & is given by $R_{gd2} = R'_{L1} + R'_{L2} + g_{m2} R'_{L1} R'_{L2}$

$R_{gs01} = R_{e1}$ seen by C_{gs1}

$$\therefore R_{gs01} = R_S$$

similarly

$R_{gs02} = R'_{L1}$ — seen by C_{gs2}

& $R_{db01} = R'_{L1}$ — " " C_{db1}

$R_{db02} = R'_{L2}$ — " " C_{db2}



CDEEP
IIT Bombay

Then time constants are

$$\tau_{gs1} = R_{gs01} \cdot C_{gs1}$$

$$\tau_{gs2} = R_{gs02} \cdot C_{gs2}$$

$$\tau_{gd1} = R_{gd01} \cdot C_{gd1} = (R_s + R'_{L1} + g_{m1} R'_{L1} R_s) C_{gd1}$$

$$\tau_{gd2} = R_{gd02} \cdot C_{gd2} = (R'_{L1} + R'_{L2} + g_{m2} R'_{L2} R'_{L1}) C_{gd2}$$

$$\tau_{db1} = R_{db1} \cdot C_{db1} = R'_{L1} C_{db1}$$

$$\tau_{db2} = R_{db2} C_{db2} = R'_{L2} C_{db2}$$



$$\text{Then } \tau = \sum_{i=1}^6 \tau_i = \tau_{gs1} + \tau_{gs2} + \tau_{gd1} + \tau_{gd2} + \tau_{db1} + \tau_{db2}$$

$$\text{Then the Dominant Pole} = \frac{1}{\tau} = \omega_{-3db}$$



CDEEP
IIT Bombay

Equivalent Ckt

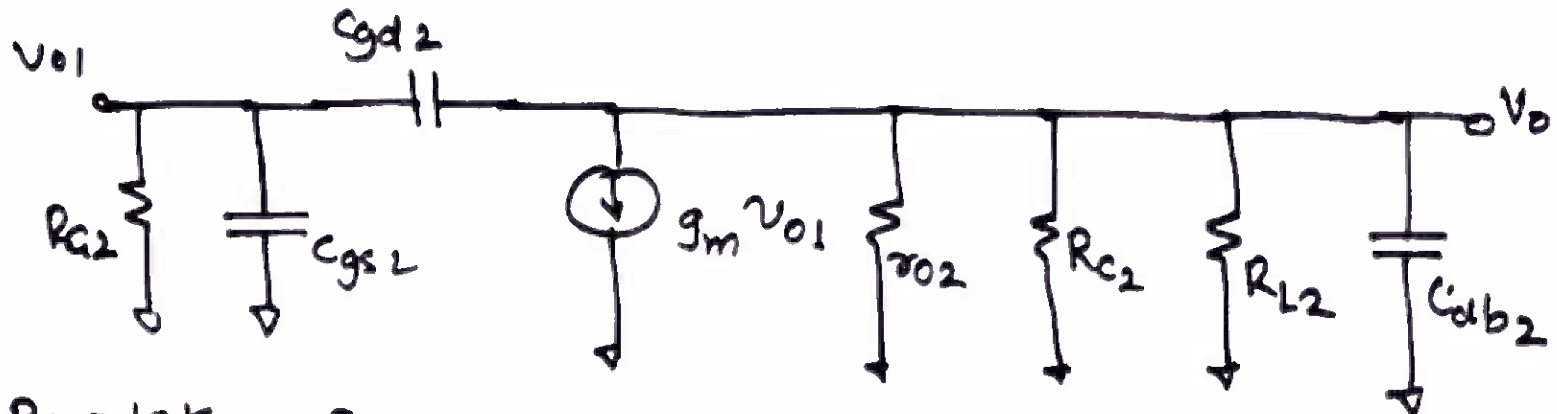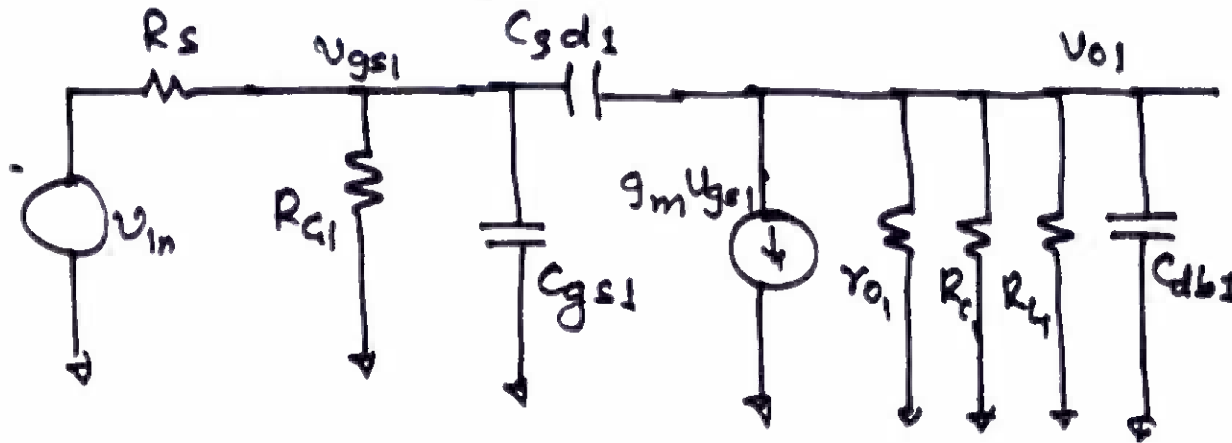

Given $R_s = 10k$, $R_{G1} = 1M\Omega$, $R_{L1} = 10k$, $R_{L2} = 5k$, $R_{G2} = 1M$
 $C_{gs1} = 5\text{ pf}$, $C_{gs2} = 10\text{ pf}$, $C_{gd1} = C_{gd2} = 1\text{ pf}$, $C_{db1} = C_{db2} = 2\text{ pf}$




CDEEP
IIT Bombay

$$\tau_{o1} = \tau_{o2} = 5 \text{ M}\Omega$$

$$g_{m1} = 3 \text{ mA/V}, \quad g_{m2} = 6 \text{ mA/V}$$

As $R_s \ll R_{c1}$, we need neglect R_{c1} in evaluations.

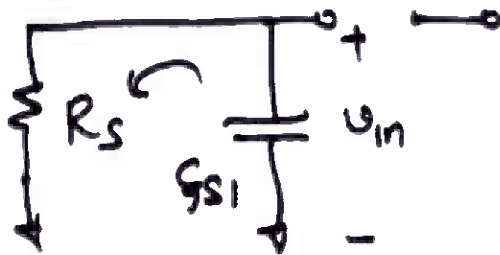
① Capacitance C_{gs1} related R_{gs01} is found as



$$R_{gs01} = R_s$$

(could be $R_s \parallel R_{c1}$)
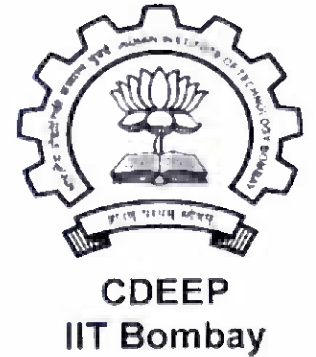
$$\therefore \tau_{C_{gs1}} = R_s C_{gs1}$$



Then repeating this procedure for all capacitors



$$\begin{aligned}\tau_{c_{gd1}} &= R_{c_{gd1}} \cdot C_{gd1} \\ &= (R_s + R'_{L1} + g_{m1} R'_{L1} R_s) C_{gd1} = 320 \text{ ns.}\end{aligned}$$

$$\begin{aligned}\tau_{c_{gd2}} &= R_{c_{gd2}} C_{gd2} = (R'_{L1} + R'_{L2} + g_{m2} R'_{L2} R'_{L1}) C_{gd2} \\ &= 315 \text{ ns.}\end{aligned}$$

$$\tau_{c_{gs1}} = R_{c_{gs1}} \cdot C_{gs1} = 50 \text{ ns}$$

$$\tau_{c_{gs2}} = R_{c_{gs2}} \cdot C_{gs2} = 100 \text{ ns}$$



$$\tau_{cdb1} = R_{cdb01} \cdot C_{db1} = R_{L1}' C_{db1}$$

$$= 20 \text{ ns}$$

$$\tau_{cdb2} = R_{cdb02} \cdot C_{db2} = R_{L2}' C_{db2}$$

$$= 10 \text{ ns}$$

$$\therefore \tau = \sum \text{All } \tau = 320 + 315 + 50 + 100 + 20 + 10 \text{ ns}$$

$$= 815 \text{ ns}$$

$$\therefore \omega_p = \text{Dominant Pole} = \frac{1}{815 \text{ ns}} = 1.2 \times 10^6 \text{ rad/s}$$

$$\therefore f_p \approx 196 \text{ kHz}$$