
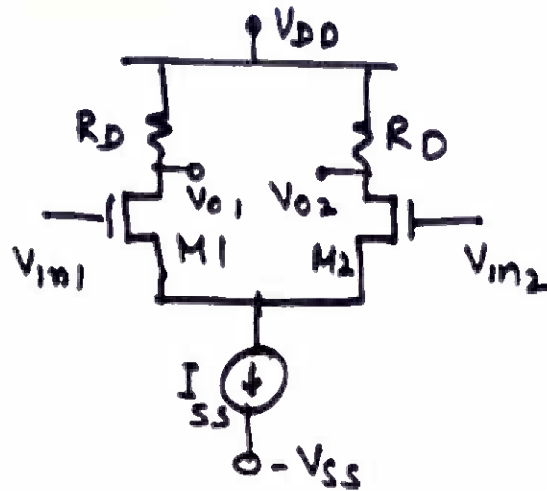



Small Signal Analysis of DIFFAMP

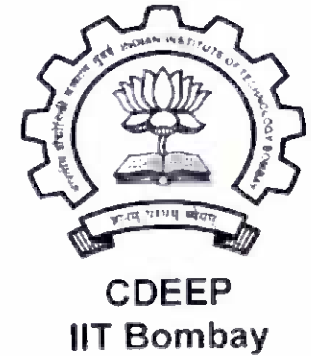

A Method of Superposition

We evaluate V_{O1} & V_{O2} with each input individually & then add the two.

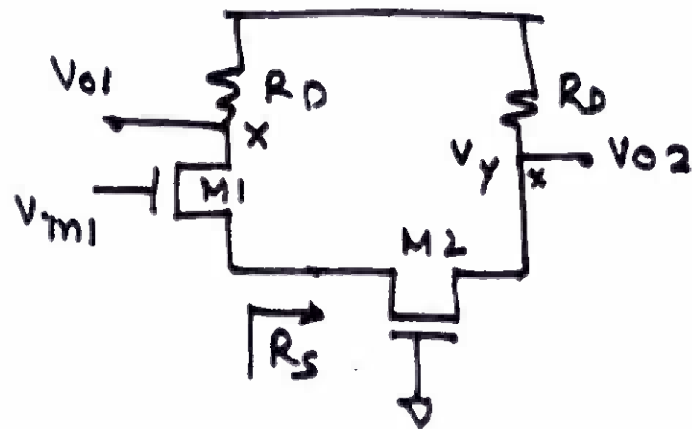
Step 1: Set $V_{i2} = V_{in2} = 0$ (We only take ac eq. circuit)



Step 2 :- Evaluate V_{O1} & V_{O2} as f^n of V_{in1}

Step 3: We observe ^{that} M_2 acts like Source Resistance for M_1 driver, forming CS Amplifier with Source Degeneration

Eq. Circuit is

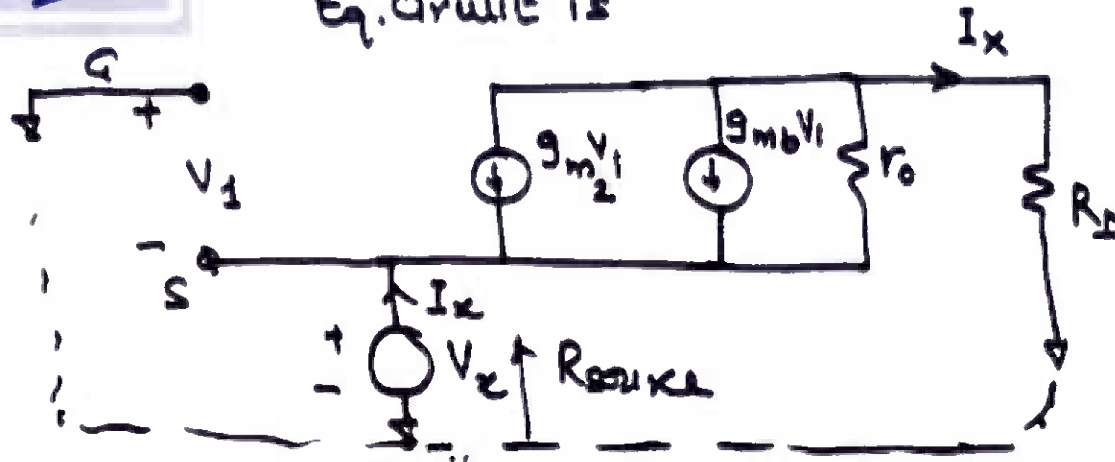

$$\therefore I_x R_D + [I_x - (g_m + g_{m2}) V_x] r_o = V_x$$

$$\left[\begin{array}{l} \text{Since } V_x = -V_1 \text{ and current through } r_o = I_x + (g_m + g_{m2}) V_1 \\ = I_x - (g_m + g_{m2}) V_x \\ \text{and } V_x = V_{r_o} + V_{R_D} \end{array} \right]$$


$$\therefore \frac{V_x}{I_x} = R_{source} || R_D = \frac{R_D + r_o}{1 + (g_{m2} + g_m) r_o}$$

CDEEP
IIT Bombay

$$R_{\text{source } M1} = \frac{R_D / r_o}{g_{m2} + g_{mb}} + \frac{1}{g_{m2} + g_{mb}}$$

If $R_D \ll r_o$, then $R_{\text{source } M1} \approx \frac{1}{g_{m2} + g_{mb}}$
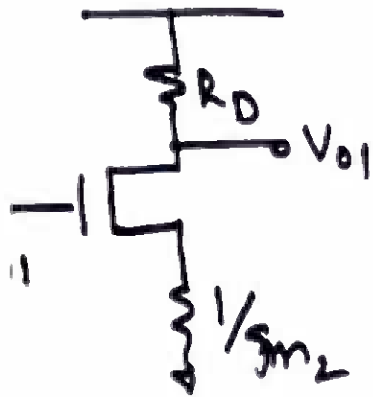
$$\approx \frac{1}{g_{m2}} \quad \text{if } g_{m2} \gg g_{mb}$$



$$\therefore \frac{V_{o1}}{V_{in1}} = - \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$


$$\left[- \frac{g_{m1} R_D}{1 + g_{m1} R_S} \right]$$

Now we calculate $\frac{V_{o2}}{V_{in1}}$


Step 4. Now we can say that M_2 is driven by M_1 as Source Follower.



Half Circuit Analysis

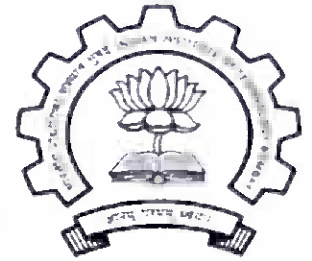


CDEEP
IIT Bombay

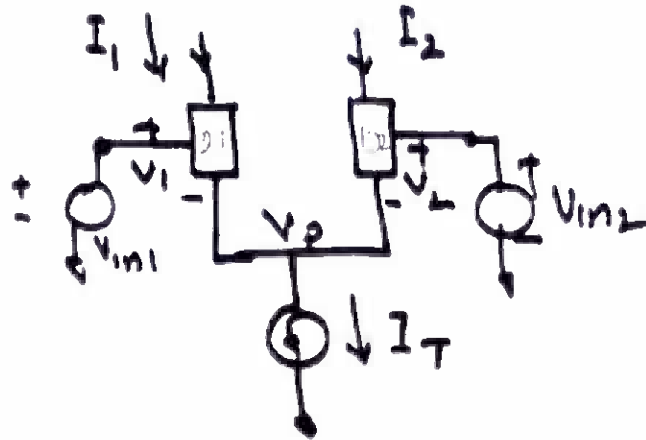

Lemma: Consider the symmetric circuit with $D1$ & $D2$. If V_{in1} changes from its equilibrium value V_0 to $V_0 + \Delta V_{in}$ and similarly V_{in2} changes to $V_0 - \Delta V_{in}$, then by this Lemma, if circuit still remains linear (i.e. g_m constant), then node voltage V_p does not change.



Equivalently saying

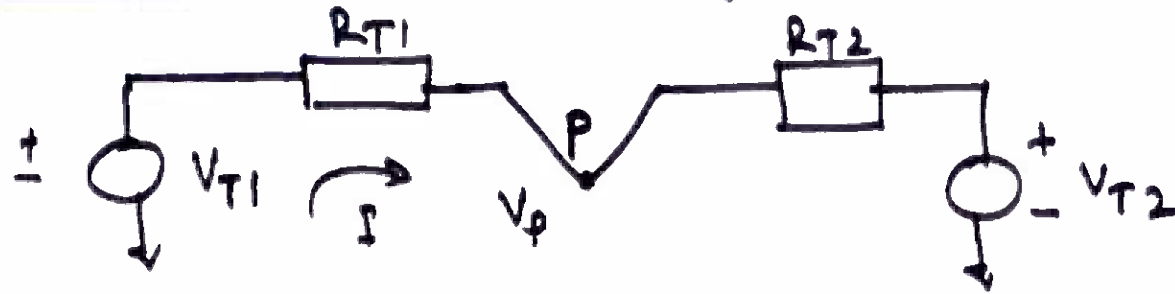

$$V_P = V_{T1} - I R_{T1} \quad \text{--- (1)}$$


$$V_P = I R_{T2} - V_{T2} \quad \text{--- (2)}$$

$$\text{or } 2V_P = V_{T1} - V_{T2} \quad \text{If } R_{T1} = R_{T2}$$

$$\text{or } V_P = \frac{V_{ID}}{2} \quad \text{Now } V_{ID} = V_{T1} + \Delta V_T - (V_{T2} - \Delta V_T)$$



$\therefore V_P$ remains constant

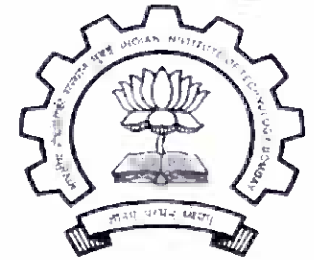If V_{T1} changes to $V_{T1} + \Delta V_T$
 \wedge V_{T2} " " to $V_{T2} - \Delta V_T$



CDEEP
IIT Bombay

Using Half Circuit Method

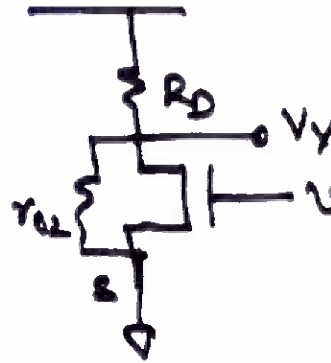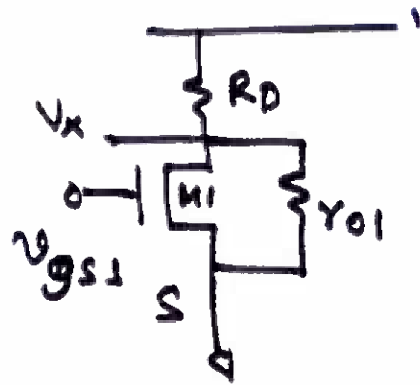CDEEP
IIT Bombay

Symmetry

Now V_p is at Ground
(AC circuit)


$$\text{Then } \frac{V_x}{V_{gs1}} = -g_{m1} (R_D \parallel r_{O1})$$

$$\& \frac{V_y}{-V_{gs1}} = -g_{m2} (R_D \parallel r_{O2})$$

$$\text{or } \frac{V_x - V_y}{2 V_{gs1}} = -\frac{1}{2} [g_{m1} (R_D \parallel r_{O1}) + g_{m2} (R_D \parallel r_{O2})]$$

If $g_{m1} = g_{m2} = g_m$ and $r_{O1} = r_{O2} = r_o$
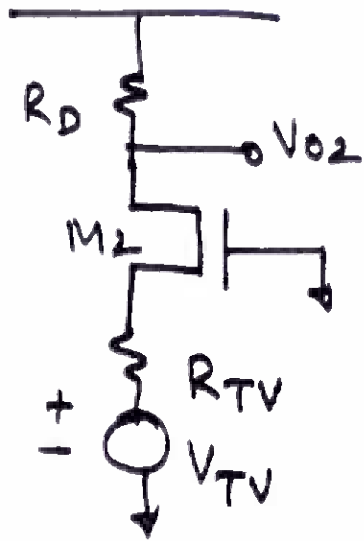
$$\text{Then } \frac{V_x - V_y}{2 V_{gs1}} = -g_m (r_o \parallel R_D) = \frac{V_x - V_y}{V_{gs1} - V_{gs2}} = \frac{V_{out}}{V_{diff}}$$



R_{TV} & V_{TV} are Thevenin's Resistance & Voltage Source

clearly $V_{TV} = V_{in1}$

and $R_{TV} = 1/g_{m1} = R_{source}$.

$$\text{Then } \frac{V_{o2}}{V_{in1}} = \frac{g_{m2} r_{o2} R_D}{r_{o2}(1 + g_{m2} R_S) + R_S + R_D}$$

$$\cong \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

Step V

Differential Gain

$$= \frac{V_{o1} - V_{o2}}{V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} = -g_m R_D$$

if $g_m = g_{m1} = g_{m2}$
 \downarrow



CDEEP
IIT Bombay

Hence for Common Source Amplifier
with source degeneration

$$A_{vcm} = \frac{V_o}{V_{incm}} = - \frac{g_m R_D / 2}{1 + 2 R_{SS} g_m}$$

$$A_{vcm} \approx - \frac{2 g_m R_D / 2}{2 R_{SS} g_m} = - \frac{R_D}{2 R_{SS}}$$


If $R_{SS} \rightarrow \infty$ $A_{vcm} \rightarrow 0$ Or Else A_{vcm} is small but Finite

$$\therefore CMRR = \frac{A_{vdm}}{A_{vcm}} \text{ is } \underline{\text{Finite}}$$




CDEEP
IIT Bombay

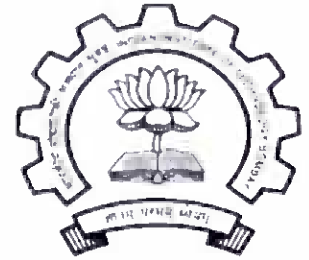
Differential Amplifier with Different Kind of Loads (Active)



CDEEP
IIT Bombay

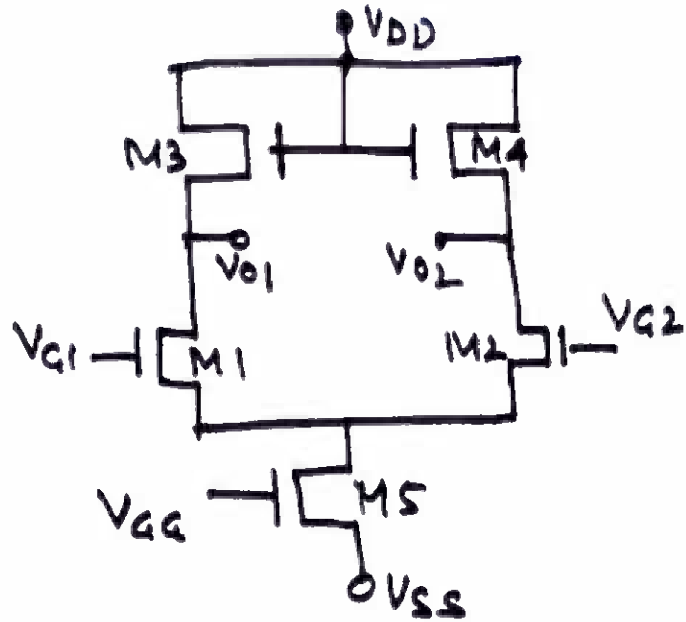


Normal Active Load


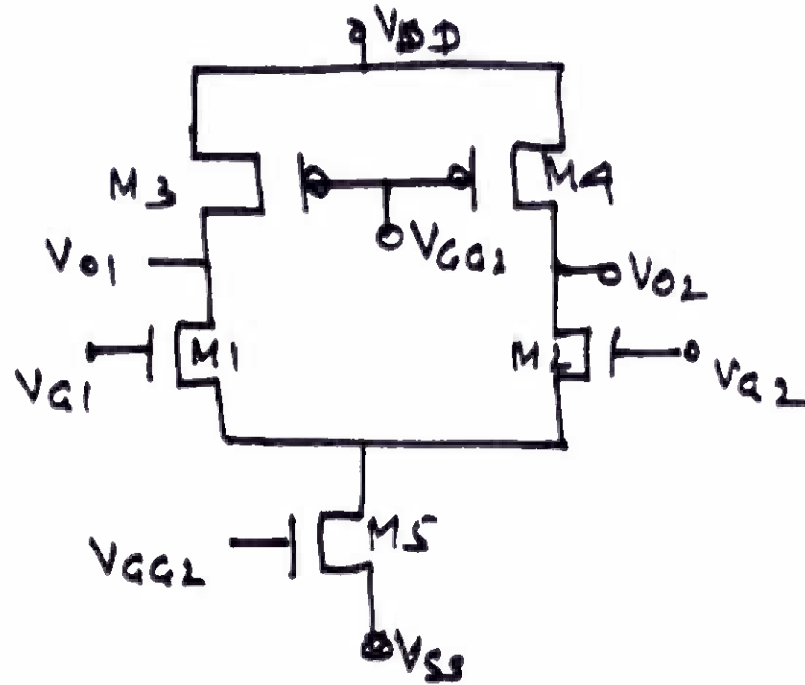


Current Source Load



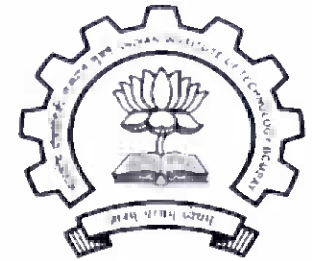

Current Mirror Load

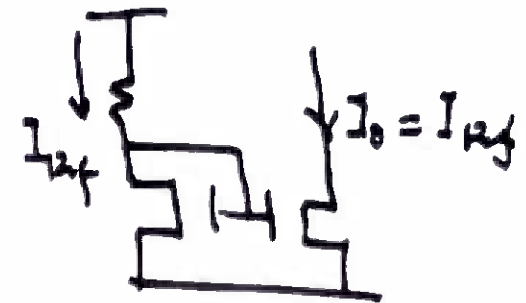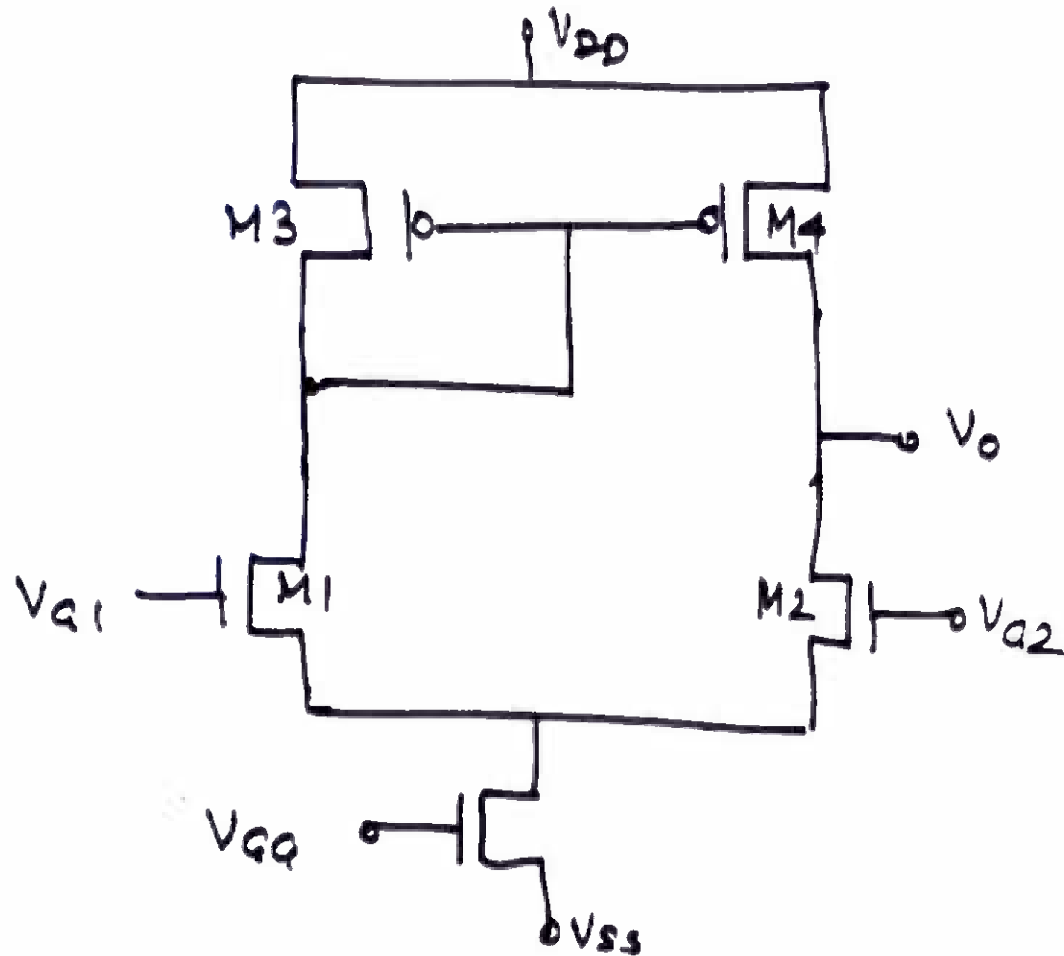

M_1 & M_2 being in parallel, We say

$$W_1 + W_2 = 2W$$

and current in each is $\frac{I_{SS}}{2}$ or in

$$(M_1 + M_2) = \frac{I_{SS}}{2} + \frac{I_{SS}}{2} = I_{SS}$$

We have $g_m = \sqrt{2\beta_n' \left(\frac{W}{L}\right) I_{DS}}$

$$\therefore g_{m_{(M_1+M_2)}} = \sqrt{2\beta_n' \left(\frac{2W}{L}\right) \cdot 2\left(\frac{I_{SS}}{2}\right)}$$

where $g_{m_{M_1}} = g_{m_{M_2}} = \sqrt{2\beta_n' \left(\frac{W}{L}\right) \left(\frac{I_{SS}}{2}\right)} = g_m$

$$\therefore g_{m_{(M_1+M_2)}} = 2g_{m_1} = 2g_{m_2} = 2g_m$$



If current source I_{SS} is not ideal we see DIFFAMP as shown for Common Mode Input







CDEEP
IIT Bombay

$$V_{inCM} = V_{in1} = V_{in2}$$

Due to symmetry $V_x = V_y = V_{o1} = V_{o2}$
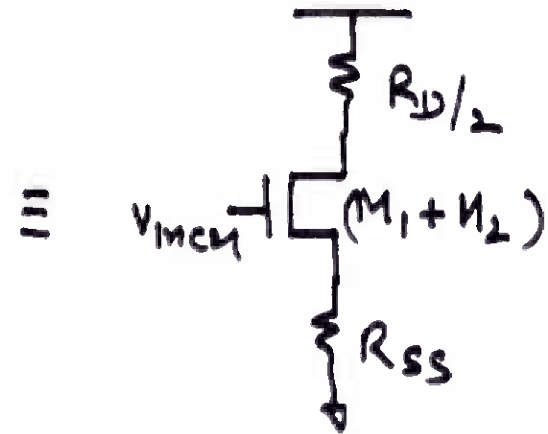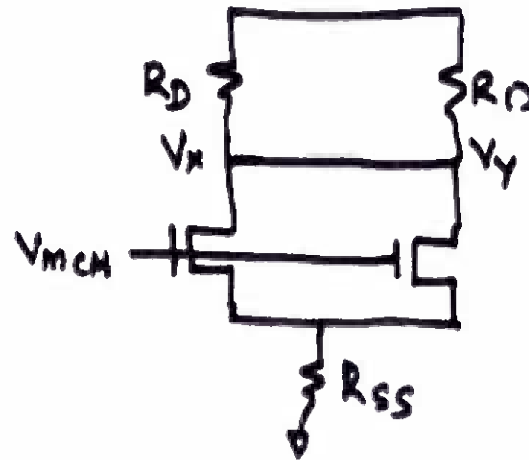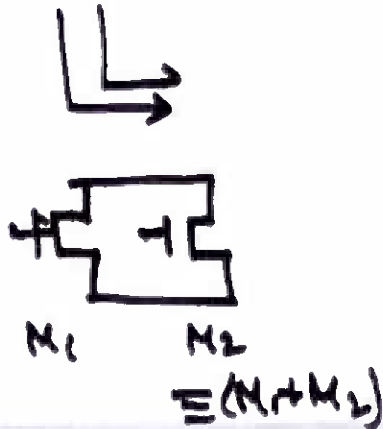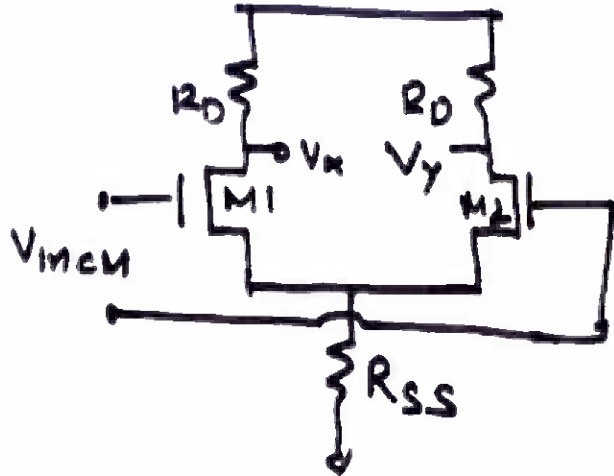
$$\text{Then } V_z - V_y = 0 = V_{o1} - V_{o2}$$





$$\text{Then } V_o = V_x - V_y = V_{o1} - V_{o2}$$


$$V_{diff} = V_{id} = V_{in1} - V_{in2}$$

$$\therefore \frac{V_o}{V_{id}} = -\frac{1}{2} [g_{m1}(R_{D1} || r_{o1}) + g_{m2}(R_{D2} || r_{o2})]$$

$$\text{If } g_m = g_{m1} = g_{m2} \quad \& \quad r_{o1} = r_{o2} = r_o$$

$$\text{Then } \frac{V_o}{V_{id}} = -g_m (R_D || r_o) = A_{dm} = A_{vdm}$$

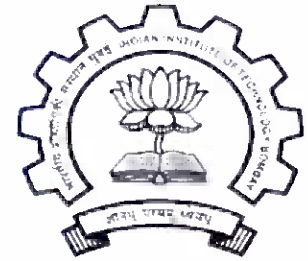for identical M1 & M2 $A_{cm} = \text{Common Mode Gain} = A_{vcm} = 0$



$$\therefore V_{in1} = \frac{(V_{in1} - V_{in2})}{2} + \frac{(V_{in1} + V_{in2})}{2}$$



$$V_{in2} = \frac{(V_{in2} - V_{in1})}{2} + \frac{(V_{in1} + V_{in2})}{2}$$

Difference
Signal


Common Mode
Signal

We use Superposition Theorem for each type of Signal.

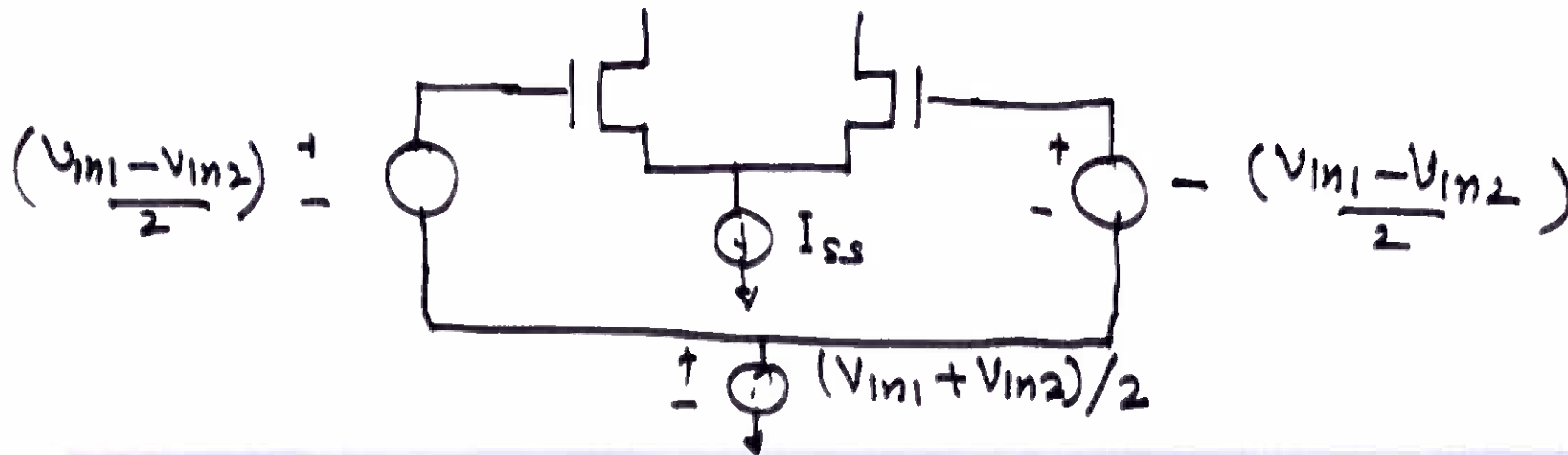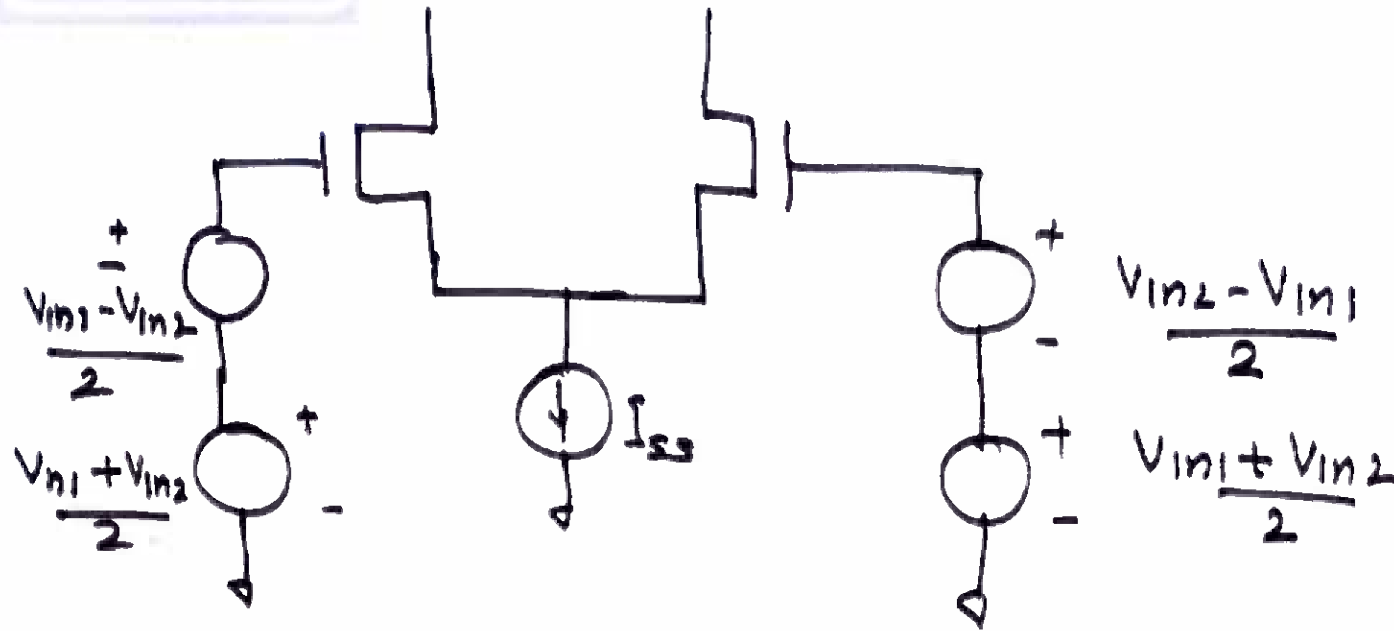
$$\begin{aligned} \text{Then } V_x = V_{o1} &= -g_m (R_D \parallel r_{o1}) \left(\frac{V_{in1} - V_{in2}}{2} \right) \\ V_y = V_{o2} &= -g_m (R_D \parallel r_{o2}) \left(\frac{V_{in2} - V_{in1}}{2} \right) \end{aligned} \quad \left. \vphantom{\begin{aligned} V_x = V_{o1} \\ V_y = V_{o2} \end{aligned}} \right\} \text{Difference Signal}$$



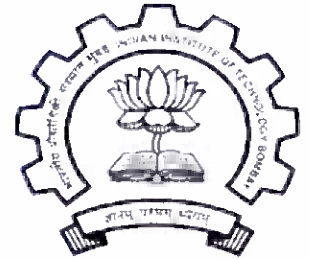Even if circuit is not fully Differential, we can see that Symmetry can be achieved.



CDEEP
IIT Bombay

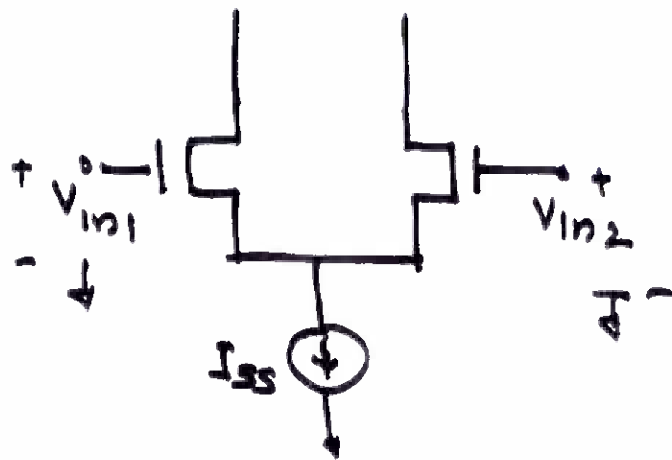

Now say $v_{in1} \neq v_{in2}$

|||

