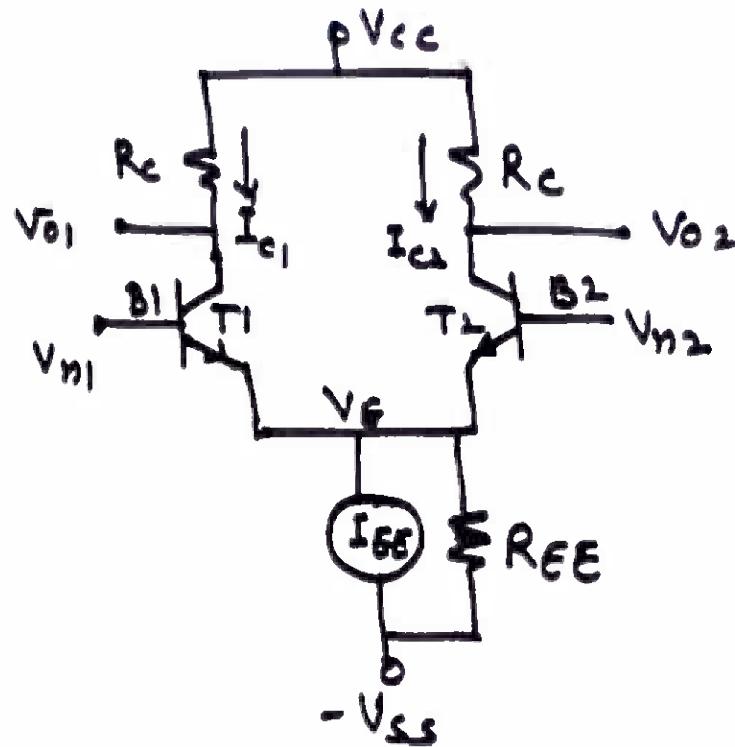


## Bipolar Diffamp




$$V_{01} - V_{02} = V_{id}$$

Hence we apply


$$V_{in1} = \frac{V_{id}}{2} \quad \& \quad V_{in2} = -\frac{V_{id}}{2}$$

to keep  $V_{id} = V_{in1} - V_{in2}$  intact.

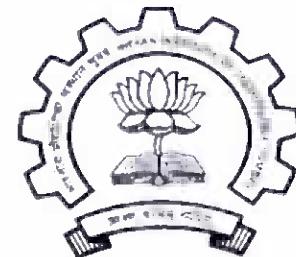
T1 has  $\beta(g_m r_i)$  which is same as for T2



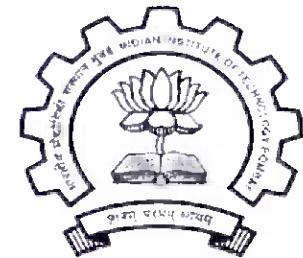AC Circuit equivalent for BJT  
DIFFAMP in two Modes of Inputs  
is shown below:




CDEEP  
IIT Bombay

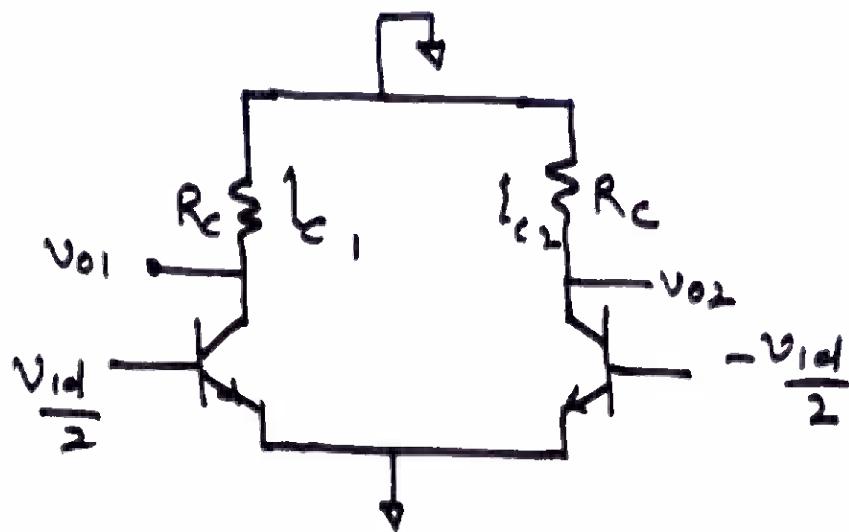

$$I_{C1} = I_{C2} - \Delta I_C$$

$$I_{C2} = -\Delta I_C$$

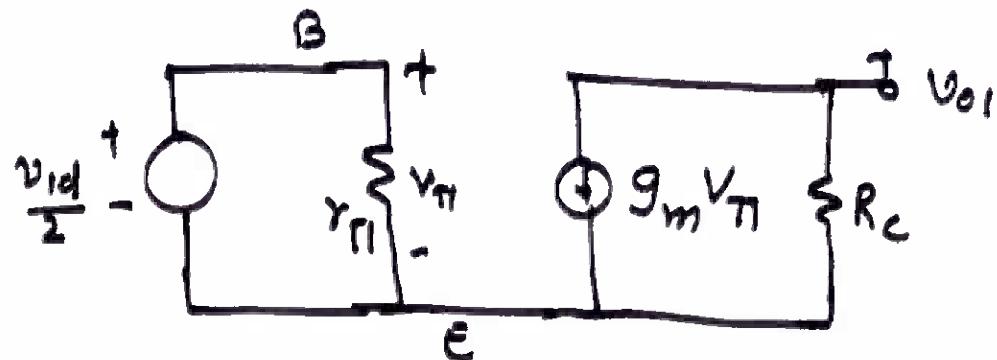

Difference Input


$$\text{Clearly } V_{\pi} = \frac{V_{id}}{2}$$

$$\therefore A_{Vdd} = \frac{V_{o1}}{\frac{V_{id}}{2}} = \frac{-g_m V_{\pi} R_c}{\frac{V_{id}}{2}} = -g_m R_c$$


For Common Mode, the equ. ckt is



CDEEP  
IIT Bombay

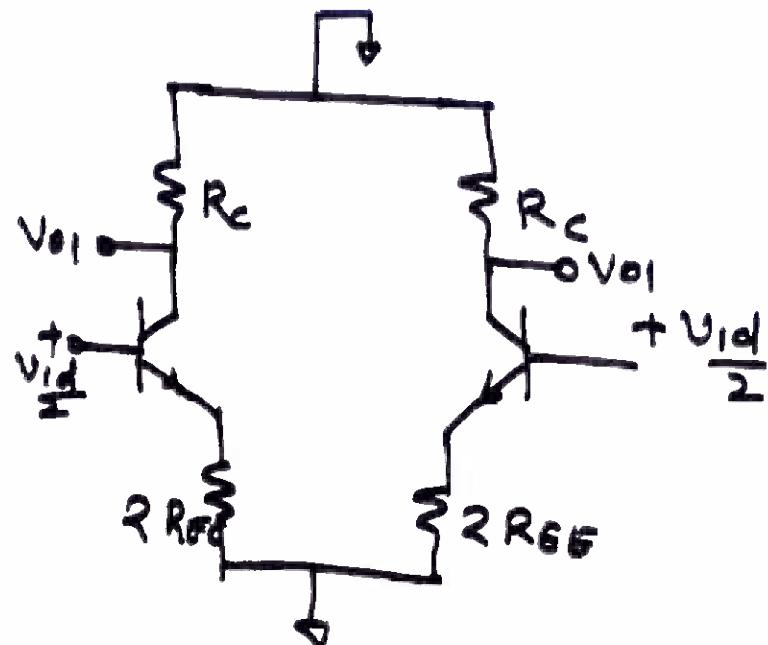

$$V_{CM} = \frac{V_{id}}{2}$$

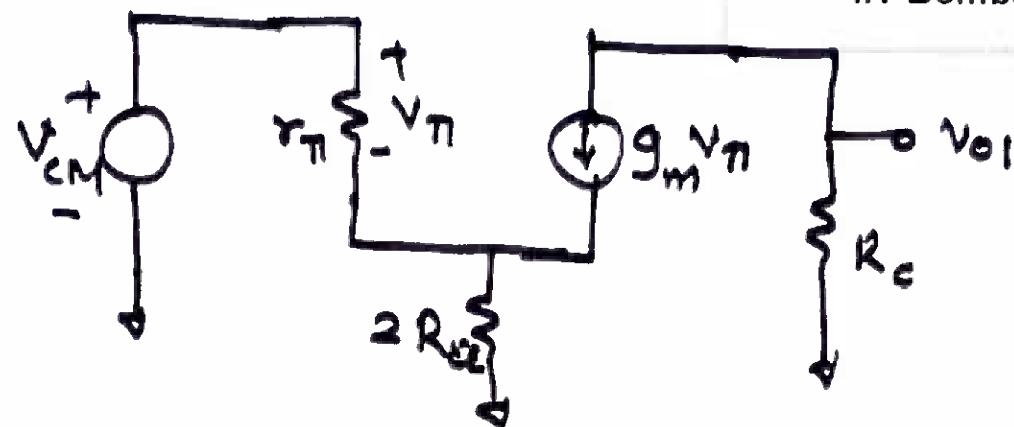


$$A_{VCM} = \frac{V_{O1}}{V_{CM}} = \frac{-\beta R_C}{r_\pi + 2R_{EE}(\beta+1)} = \frac{-R_C}{2R_{EE}}$$

$$\therefore CMRR = \frac{A_{Vdd}}{A_{VCM}} = \frac{-g_m R_C}{\left[ \frac{-g_m R_C}{1 + 2g_m R_{EE}} \right]} = 1 + 2g_m R_{EE}$$

If  $R_{EE} \rightarrow \infty$   $CMRR \rightarrow \infty$   
Else  $CMRR$  is finite and around 80-120dB

## Current Mirror CMOS Diffamp.

Example

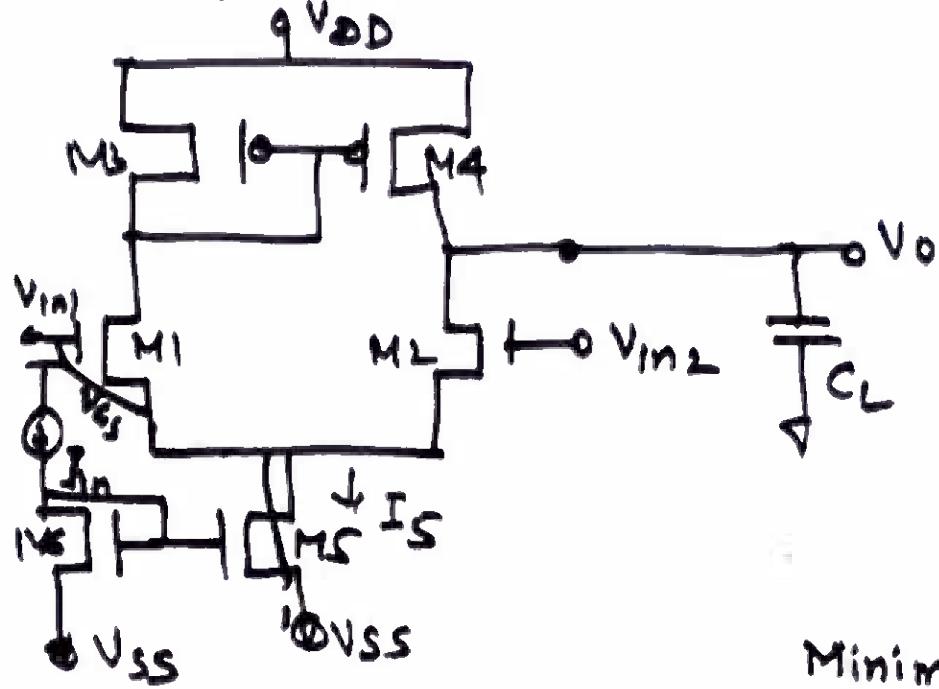Given  $C_L = 5 \text{ pF}$ Slew Rate  $\geq 10 \text{ V}/\mu\text{s}$ .

$$V_{DD} = -V_{SS} = 2.5 \text{ V}$$

$$\beta'_n = 110 \mu\text{A}/\text{V}^2, \quad \beta'_p = 50 \mu\text{A}/\text{V}^2$$


$$V_T = 0.7 \text{ V} = |V_{TP}|$$

$$\lambda_n = 0.04/\text{V} \quad \& \quad \lambda_p = 0.05/\text{V}$$

frequency for Dominant Pole  
 $\geq 100 \text{ kHz}$  (Bandwidth Minimum)

For Diffamp in DC case

$$I_{DS1} = I_{DS2} = \frac{I_S}{2}$$

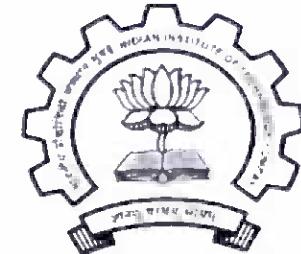

## CHOICE OF $I_S$

Slide No: 5 ① From Maximum Power Dissipation

of 1mW, we have

$$I_S(V_{DD} - V_{SS}) \leq 1 \text{ mW}$$

$$\text{or } I_S \leq \frac{1}{5} \times 10^{-3}$$

$\therefore I_S \leq 200 \mu\text{A}$  — PD requirement

② Skew Rate  $SR \geq 10\text{V}/\mu\text{s}$


$$\text{Skew Rate} = SR = \frac{I_S}{C_L} \quad \text{or} \quad I_S = SR \cdot C_L$$

$$\therefore I_S \geq 10 \times 10^6 \times 5 \times 10^{-12}$$
$$\geq 50 \mu\text{A}$$

③ We assume Dominant Pole (Bandwidth is due to heavy load capacitance  $C_L = 5 \text{ pF}$ )



CDEEP  
IIT Bombay

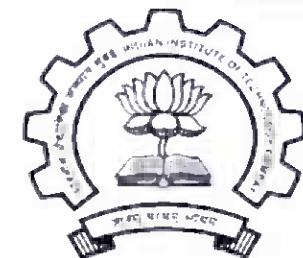

CDEEP  
IIT Bombay

or

$$f_{BW} = \frac{1}{2\pi R_{out} C_L}$$

$$\begin{aligned} \text{But } R_{out} &= R_{O2} \parallel R_{O4} = \frac{1}{g_{O2} + g_{O4}} \\ &= \frac{1}{\lambda_n \frac{I_S S}{2} + \lambda_p \frac{I_S S}{2}} = \frac{1}{(\lambda_n + \lambda_p) I_S / 2} = \frac{2}{(0.04 + 0.05) I_S} \\ &= \frac{22.22}{I_S} \end{aligned}$$


$\therefore$  For  $f_{BW} \geq 100 \text{ kHz}$

$$100 \times 10^3 \geq \frac{I_S}{2\pi \times 22.22 \times 5 \times 10^{-12}}$$

$$\therefore I_S \geq 70 \mu\text{A}$$

To satisfy 'All THREE' Requirements

We choose  $I_S = 100 \mu A$

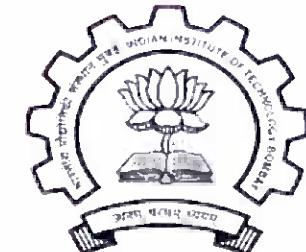

CDEEP  
IIT Bombay

$\therefore \frac{I_S}{2} = 50 \mu A$  In our further calculation of Gain

$$\text{Given } (W/L)_1 = (W/L)_2 = 18.4$$

$$\text{and } (W/L)_3 = (W/L)_4 = 8$$

$$\text{Then DC Gain} = g_{m_1} R_{out} = \sqrt{\frac{2 \beta n (W/L)_1 I_S / 2}{(\lambda_n + \lambda_p) I_S / 2}}$$

$$Av_{do} = \sqrt{\frac{2 \times 110 \times 10^6 \times 18.4 \times 50 \times 10^{-6}}{(0.09) \times \frac{100}{2} \times 10^{-6}}} \approx 100$$

Given  $V_{ICM_{min}} = -1.5 \text{ V}$

$$\therefore -1.5 = V_{DSatS} + V_{SS} + V_{GS1}$$


$$\text{or } V_{DSatS} = 1 - V_{GS1}$$

$$\text{But } V_{GS1} = \sqrt{\frac{I_S/2}{\frac{1}{2} \beta_n' (W/L)_1}} + V_{TH}$$

$$= \sqrt{\frac{2 \times 50 \times 10^{-6}}{1 \times 110 \times 10^6 \times 18.4}} + 0.7$$

$$\therefore V_{GS1} \approx 0.222 + 0.7 = 0.922 \text{ V}$$
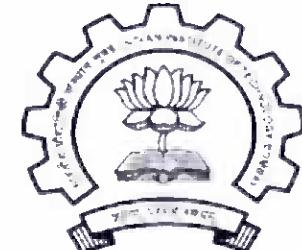
$$\therefore V_{DSatS} = 1 - 0.922 \approx 0.08 \text{ V}$$



CDEEP  
IIT Bombay

$$I_S = \frac{1}{2} \beta_n' (W/L)_S V_{DSat}^2$$

$$2 \times 100 \times 10^{-6} = 110 \times 10^{-6} (W/L)_S \times (0.08)^2$$

$\therefore (W/L)_S \approx 300$  Too high !!



CDEEP  
IIT Bombay