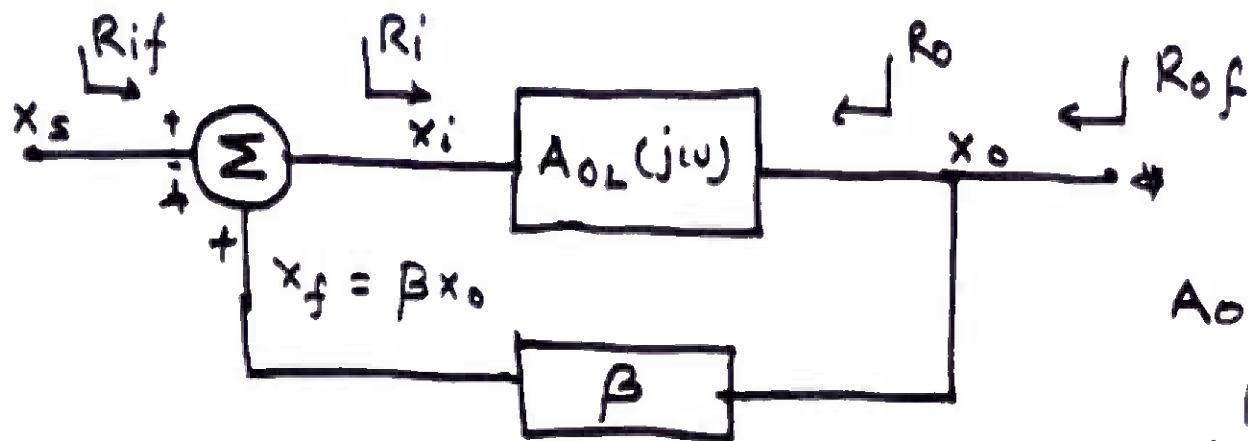


Feedback


$A_{OL}(j\omega)$ = Open Loop Gain
 β = Feedback factor
 $A_{CL}(j\omega)$ = Closed Loop Gain

General Feedback System

$$x_o = A_{OL}(j\omega) \cdot x_i = A_{OL}(j\omega) [x_s - x_f]$$


Here $x_i = x_s - x_f$ And $x_f = \beta x_o$
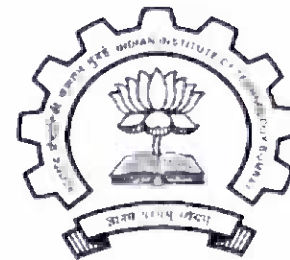
$$\therefore x_o = A_{OL} x_s - A_{OL} \beta x_o \quad \therefore A_{CL}(j\omega) = \frac{x_o}{x_s} = \frac{A_{OL}}{1 + A_{OL} \beta}$$



CDEEP
IIT Bombay

Definitions

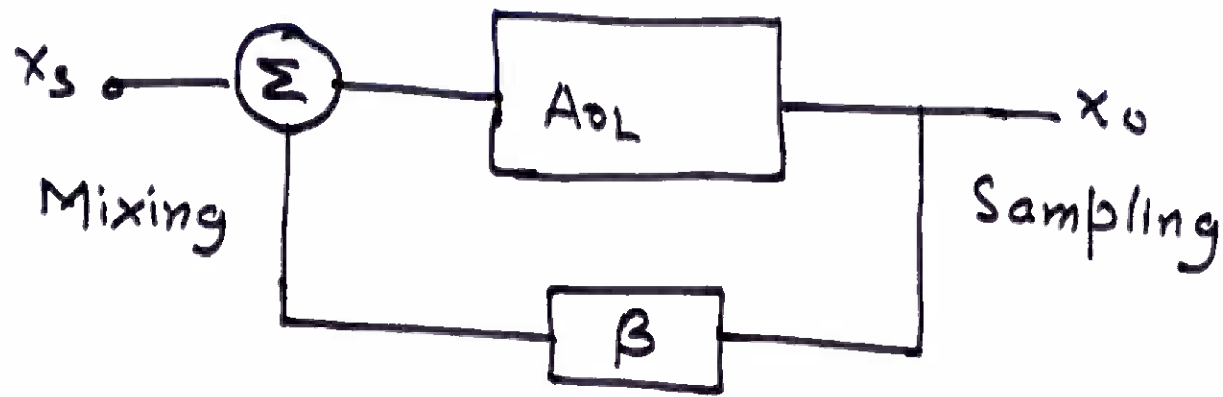


$A_{OL} = A_o = \text{Gain without feedback}$

$A_{CL} = \text{Closed Loop Gain}$

$A_{OL}\beta = \text{Loop Gain}$

$1 + A_{OL}\beta = \text{Amount of Feedback}$

$A_{OL}\beta = \text{Return Ratio}$

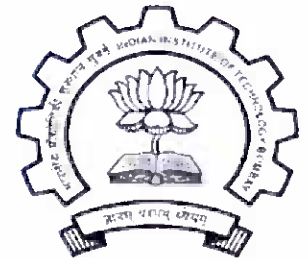

CDEEP
IIT Bombay

If $A_o\beta \gg 1$

$$\text{Then } A_{CL} \cong \frac{A_o}{A_o\beta} = \frac{1}{\beta}$$

This means that Gain of Feedback Amplifier (A_{CL}) is only decided by Passive Feedback network gain β .

$$\text{As } \beta < 1 \quad A_{CL} > 1$$

However $A_{CL} = \frac{A_o}{1 + A_o\beta}$ can change with β & value & sign of A_o

(i) Negative Feedback

(ii) Positive Feedback



Properties of Negative Feedback

[1] Gain Desensitivity

We have $A_{CL} = \frac{A_0}{1 + A_0\beta}$

$$\text{or } dA_{CL} = dA_0 \left[\frac{1}{1 + A_0\beta} - \frac{A_0\beta}{(1 + A_0\beta)^2} \right]$$


$$x_L = x_S + x_B$$

$$\text{or } dA_{CL} = \frac{dA_0}{(1 + A_0\beta)^2}$$


$$\therefore \frac{dA_{CL}}{A_{CL}} = \frac{dA_0}{(1 + A_0\beta)^2} \cdot \frac{(1 + A_0\beta)}{A_0} = \frac{1}{(1 + A_0\beta)} \cdot \frac{dA_0}{A_0}$$

Clearly % change in A_{CL} is Always Less than % change in A_0

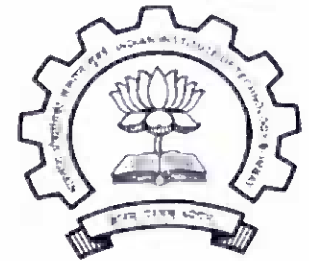$\therefore (1 + A_0\beta)$ is also called Desensitivity Factor



CDEEP
IIT Bombay

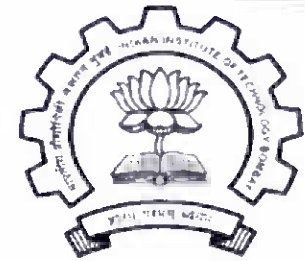

[2] Bandwidth Enhancement

$$A_{oL}(s) = \frac{A_{\text{Midband}}}{1 + s/\omega_0} = \frac{A_M}{1 + s/\omega_0} = A_0$$

ω_0 is Dominant Pole

Then with Negative Feedback

$$\begin{aligned} A_{cL}(s) &= \frac{A_{oL}(s)}{1 + A_{oL}(s)\beta} = \frac{A_M / (1 + s/\omega_0)}{1 + \frac{A_M \cdot \beta}{1 + s/\omega_0}} \\ &= \frac{A_M / (1 + A_M \beta)}{s / (1 + A_M \beta) \omega_0 + 1} \\ &= \frac{A_{cLO}}{1 + s / [(1 + A_M \beta) \omega_0]} \end{aligned} \quad A_{cLO} = \frac{A_M}{1 + A_M \beta}$$

clearly Gain (OL) = $\frac{AM}{1+AM\beta}$

↳ New Pole = $\omega_0(1+AM\beta) = \omega_f$


As $AM\beta > 1$

$\therefore \omega_0(1+AM\beta) = \omega_f > \omega_0$



\therefore Bandwidth extension is seen.

[3] Reduction in Non-Linear Distortion;

\therefore Linearization ?

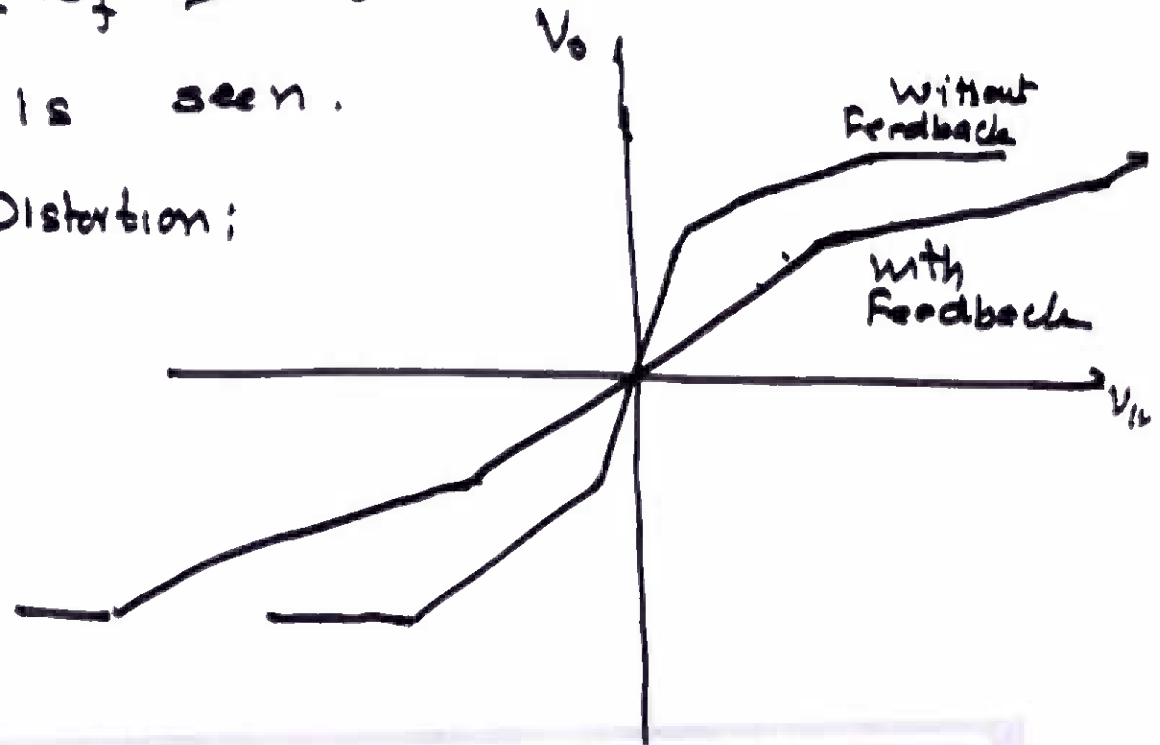

CDEEP
IIT Bombay

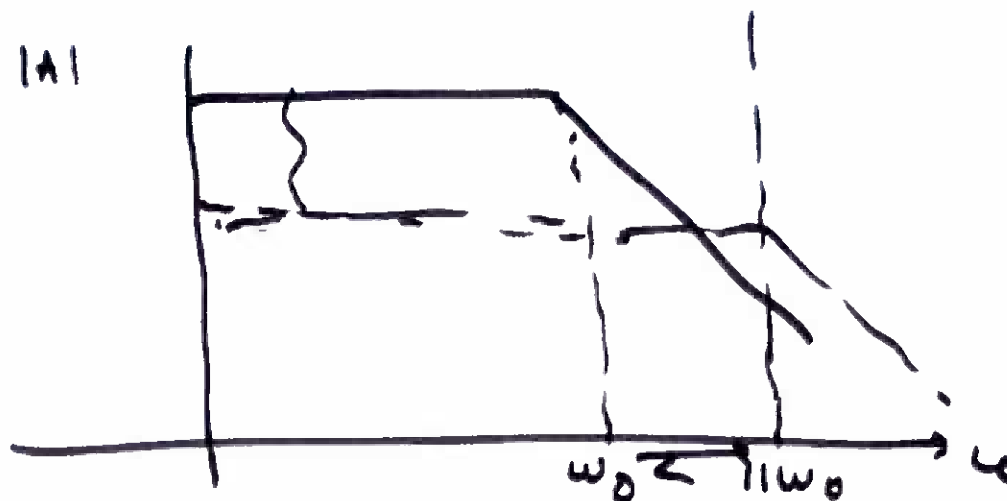
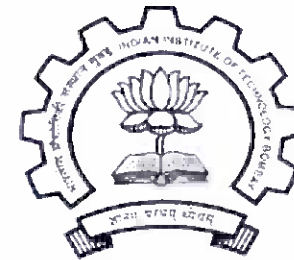


$$\angle_{0.2} \approx 10$$


$$\frac{k'}{(s/\omega - 1)} = \frac{1}{s - \omega} = \frac{k}{(s/\omega - 1)\omega}$$

$$k' = \frac{k}{\sqrt{3}}$$

Signal Flow Graph

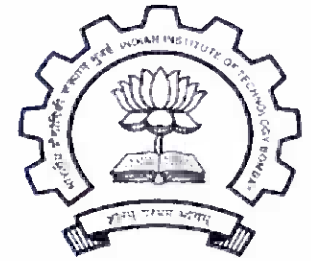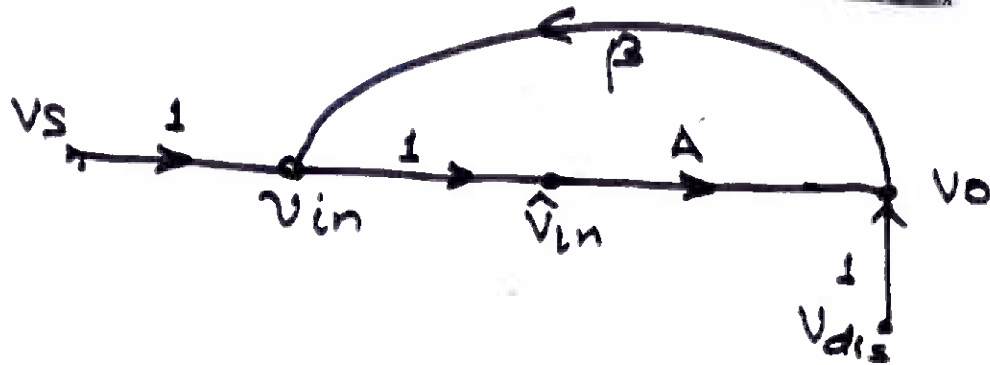

CDEEP
IIT Bombay

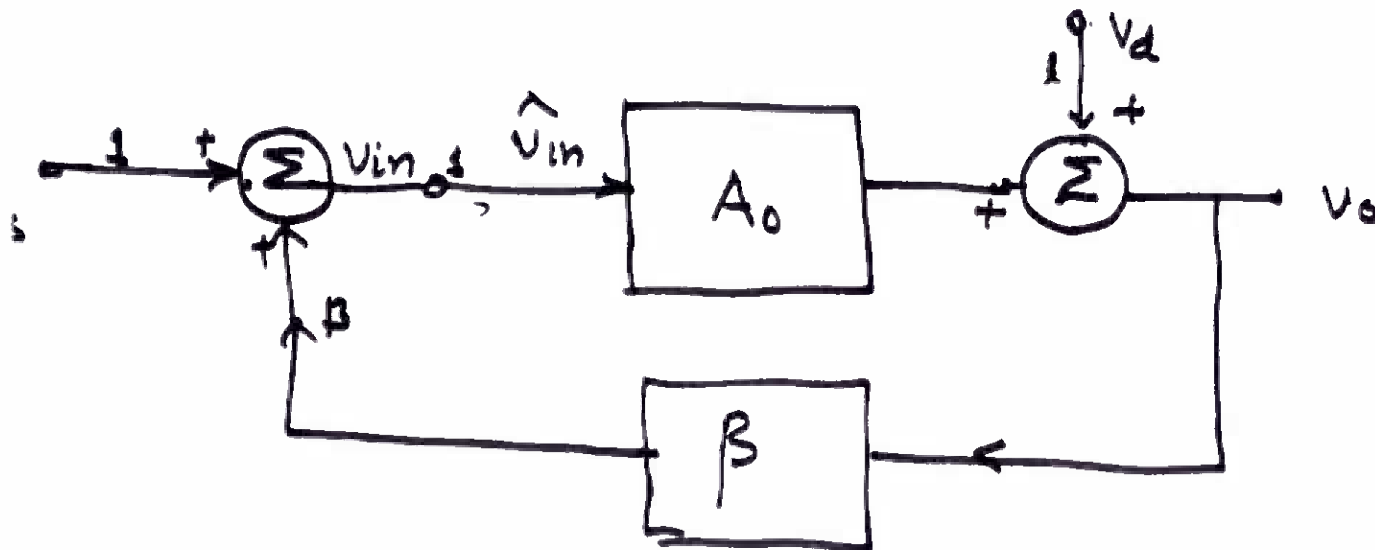


$$\therefore V_o = A_F V_s + \frac{V_d}{1 + A_0 \beta}$$


$$A_0 \beta = T \gg 1$$

$$V_o = A_F V_s + \frac{V_d}{T}$$


Circuit equivalent for Mixing & Sampling

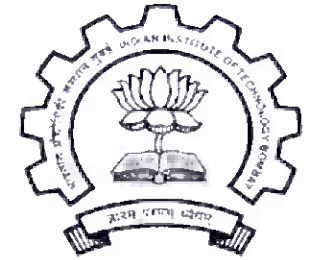


CDEEP
IIT Bombay

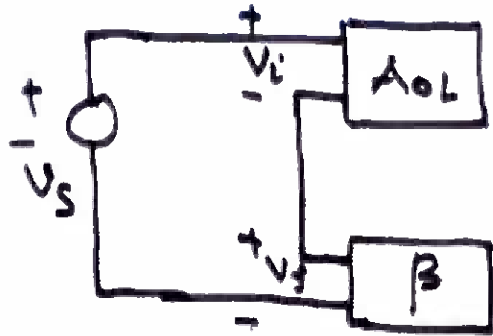


Series Mixing

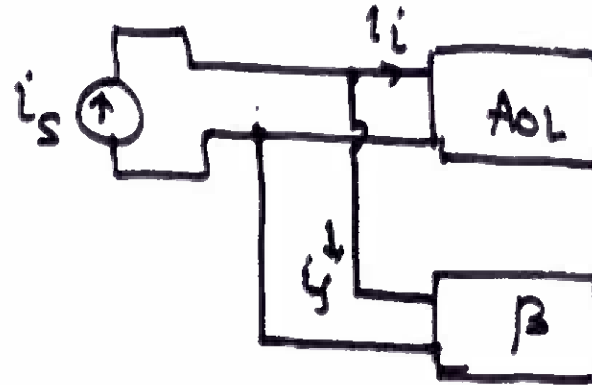

Shunt Mixing

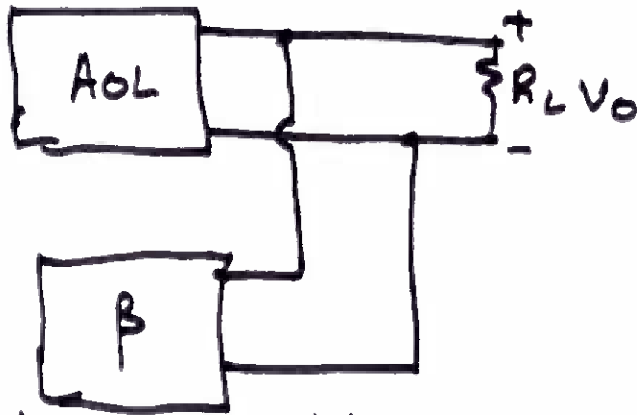


Shunt Sampling

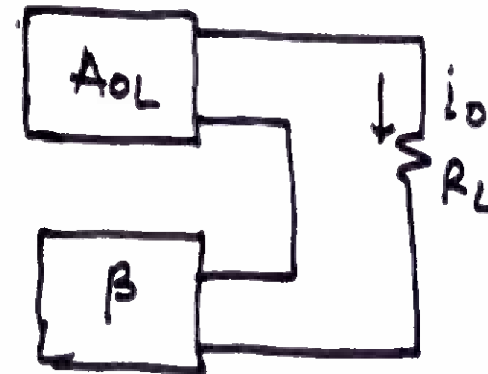


Series Sampling


Four Topologies for Feedback Amplifiers

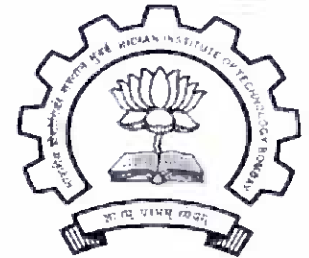


CDEEP
IIT Bombay

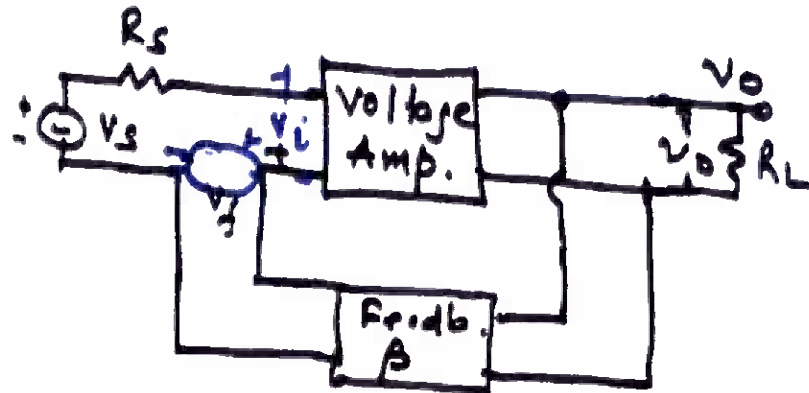


Series - shunt

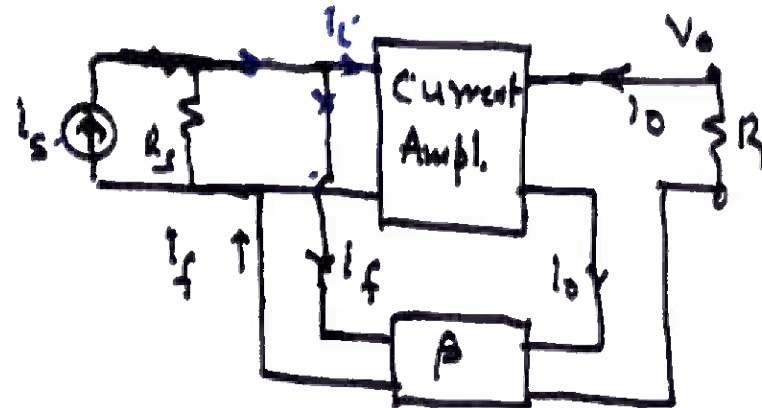


shunt - series

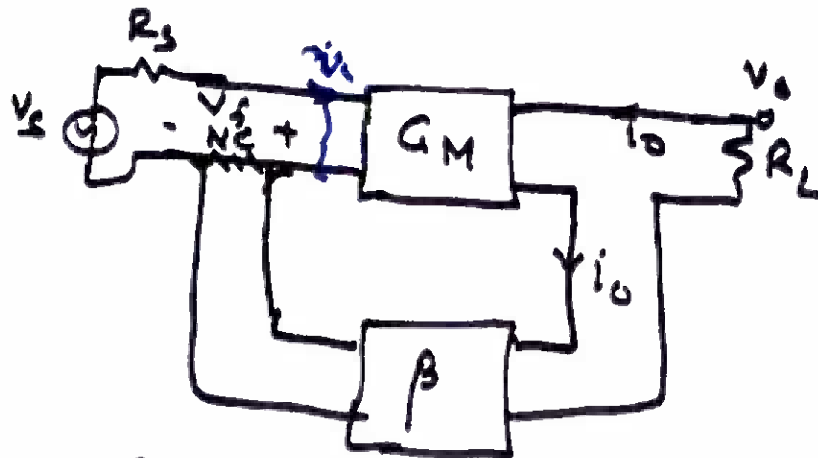

Series - series

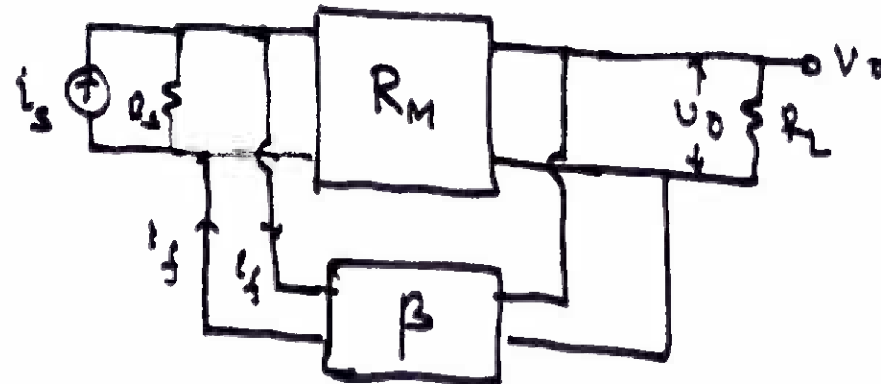

shunt - shunt

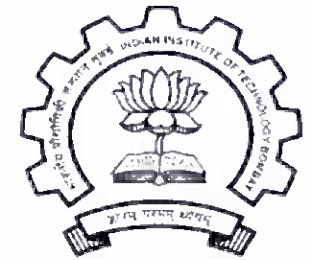

CDEEP
IIT Bombay



Slide No. 11

Types of Feedback Amplifiers

	x_s, x_i & x_f	x_o	Mixing	Sampling
①	Voltage	Voltage	Series -	Shunt
②	Voltage	Current	Series -	Series
③	Current	Current	Shunt -	Series
④	Current	Voltage	Shunt -	Shunt


- ① Voltage Amplifier ② Transconductance Amplifier
③ Current Amplifier ④ Trans Resistance Amplifier

Ideal Amplifier

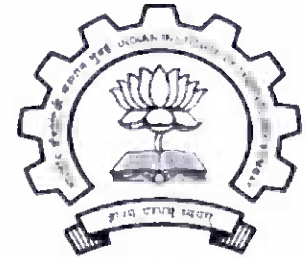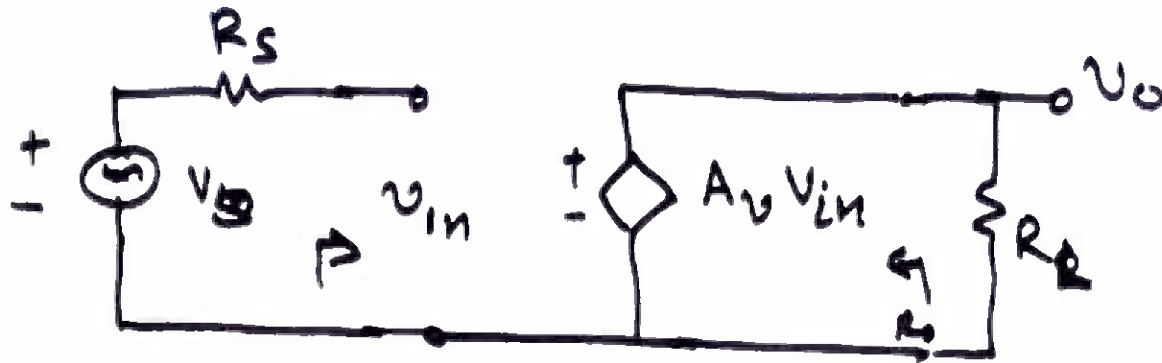


CDEEP
IIT Bombay

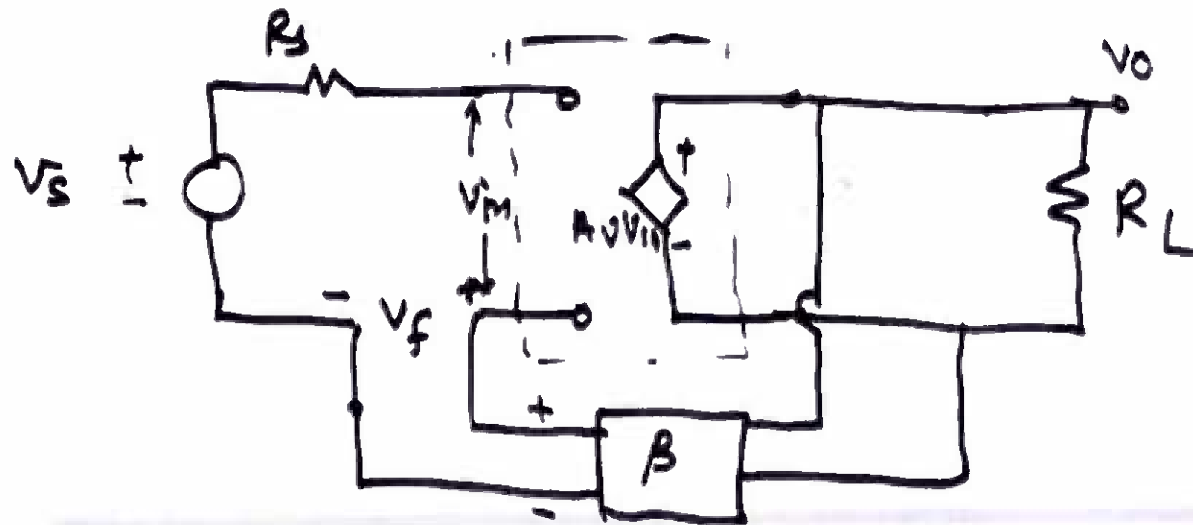Assumption $R_{in} = \infty$ $R_o = 0$. Now we apply Negative Feedback



Here Sampling is 'Shunt' (V_o)
& Mixing is Series

$$V_f = \beta V_o$$

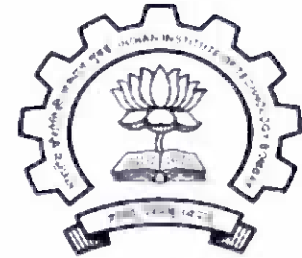


$$\begin{aligned} \text{Then } V_s &= V_{int} + V_f \\ &= V_{in} + 0.09 V_o \end{aligned} \quad \begin{array}{l} \text{Here} \\ \beta = 0.09 \end{array}$$

$$\begin{aligned} \text{If } V_o = 5V \quad \text{then } 0.09 \times 5 &= 0.45V \\ &= 450mV \end{aligned}$$


clearly for $V_s \leq 500mV$
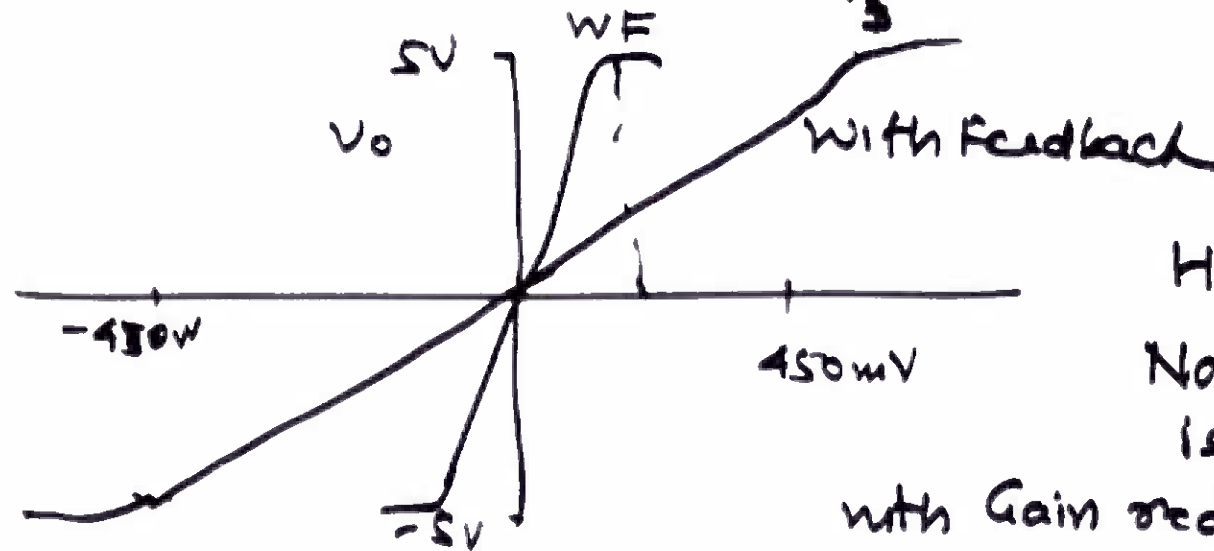
$$\frac{V_o}{V_s} = \text{constant} = A_f \approx 10$$




Hence we say
Nonlinear Distortion
is reduced.
with Gain reducing

Concept of Non Linear Distortion

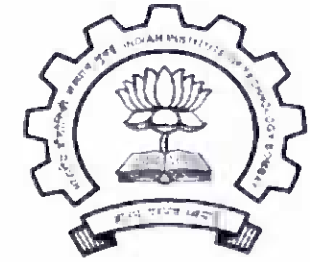

CDEEP
IIT Bombay

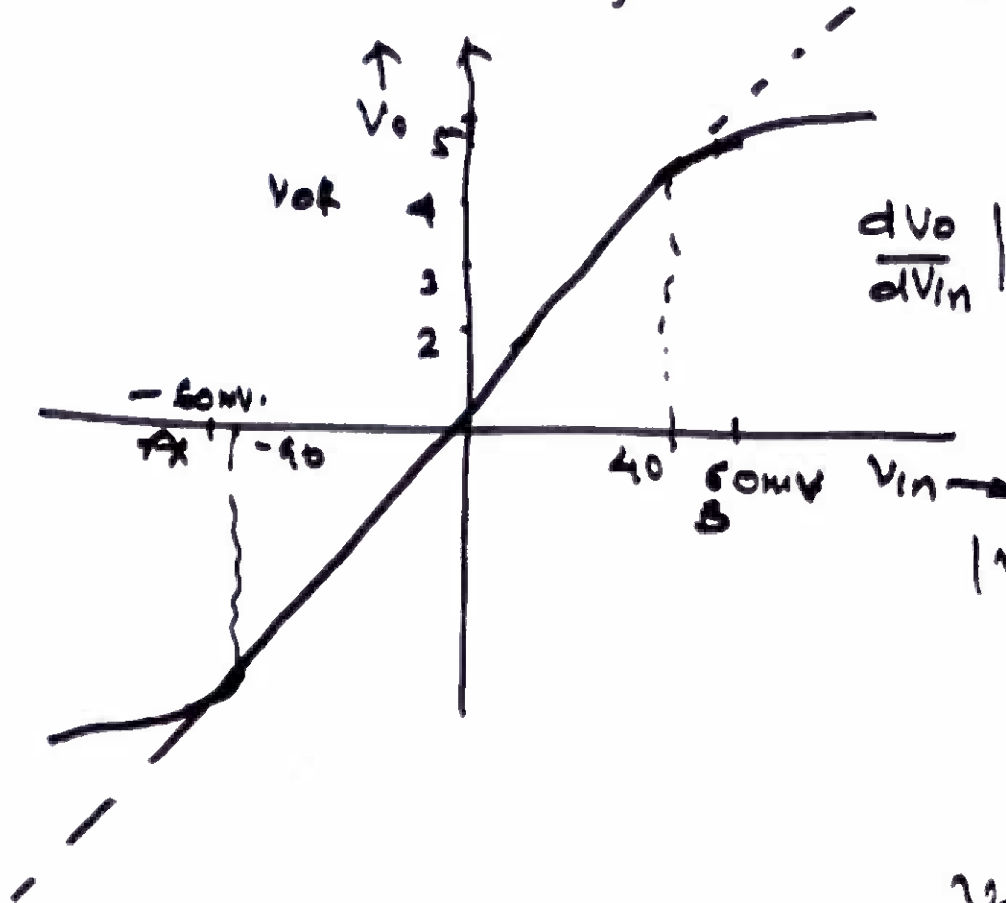

Let $\left. \frac{dV_o}{dV_{in}} \right|_{A \rightarrow B} = 100 = G_{lin}$

$$|V_o| = 100 \quad V_{in} - 40 \leq V_{in} \leq 40 \text{ mV}$$

$$|V_o| = 100 [V_i - 40 \text{ mV}]$$

$$- 2500 [V_{in} - 0.04]^2 + \dots$$

$$40 \leq V_{in} \leq 60 \text{ mV}$$


$$V_o = 5 \text{ V}$$

$$V_{in} \geq 60 \text{ mV}$$

$$f(x) = a_0 x + a_1 x^2$$

$$V_i = A \sin \omega t$$



Impedance in feedback Amplifiers

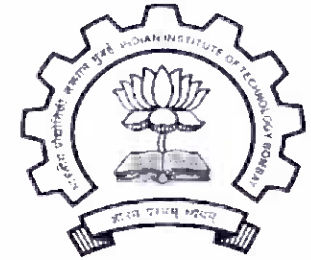

CDEEP
IIT Bombay

[A] Input Resistance

(a) Series Mixing & (Shunt Sampling)

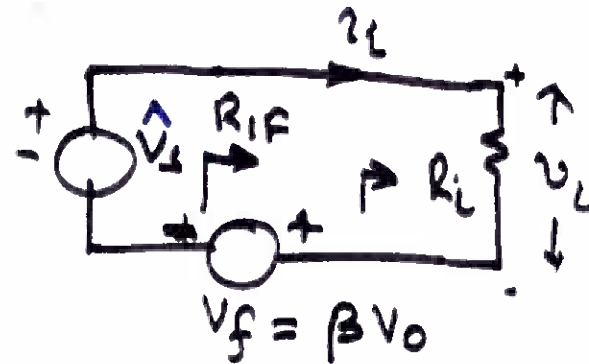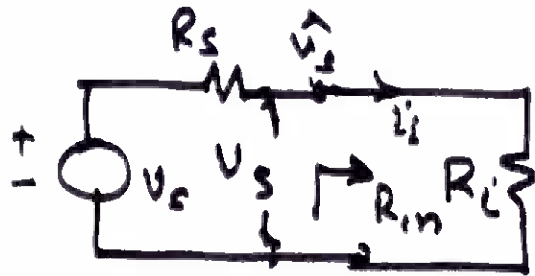

We have
 $\frac{V_o}{V_i} = A$

$$A_F = \frac{V_o}{V_s} = \frac{A_{OL}}{1 + A_{OL}\beta} = \frac{A}{1 + A\beta}$$

$$R_i = \frac{\hat{V}_s}{I_i} = R_i \quad R_{iF} = \frac{V_s}{I_i} = \frac{V_s}{I_i/R_i} = R_i \frac{V_s}{V_i} = (1 + A\beta)R_i$$

$$V_s + V_f = V_s = V_i + \beta V_o = (1 + A\beta)V_i$$

$$\therefore I_x = \frac{V_x + A\beta V_x}{R_o}$$

$$\Rightarrow \frac{V_x}{I_x} = \frac{R_o}{1+A\beta} = \frac{R_o}{1} = R_{of}$$

$$\therefore R_{of} < R_o$$



(b) Similarly we can show that Series Sampling
 $R_{of} = (1+A\beta) R_o$ & $R_{of} > R_o$





[B] Output Resistance

(a) Shunt Sampling

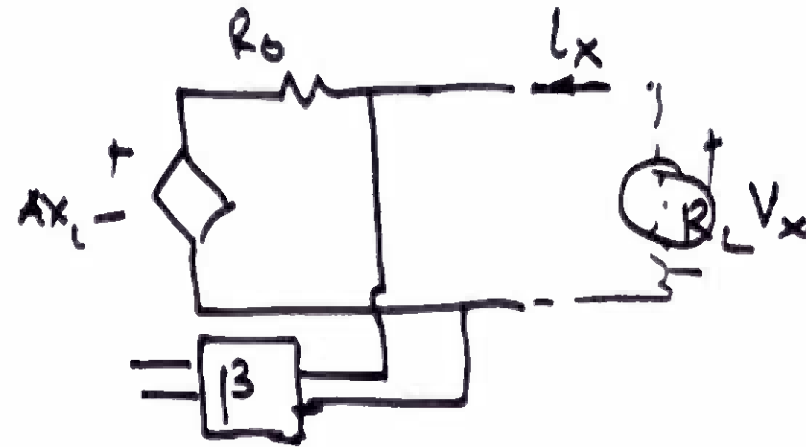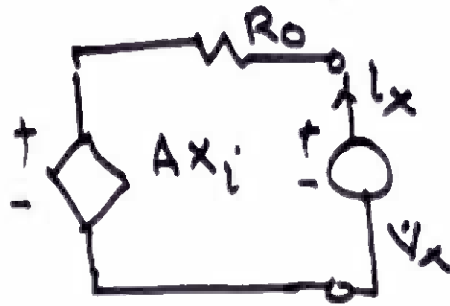

With $x_i = 0$
 $R_{o_{ol}} = R_o$

With feedback


$$R_{of} = \frac{V_x}{I_x}$$

$$x_o = x_i + x_f \quad \text{with } x_o = 0$$

$$-x_o = x_f = \beta V_o = \beta V_x$$

$$x_i = -\beta V_x$$

[B] Shunt Mixing

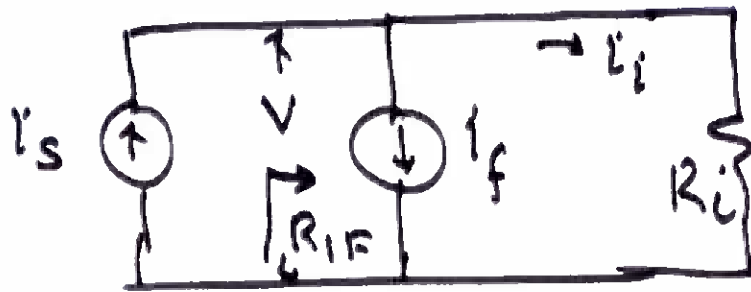

$$i_f = \beta x_o$$


$$x_o = A i_i$$

$$x_o \subset V_o \text{ or } i_o$$

$$i_i = i_s - i_f = i_s - \beta x_o = i_s - A\beta i_i$$

$$\text{or } (1 + A\beta) i_i = i_s$$
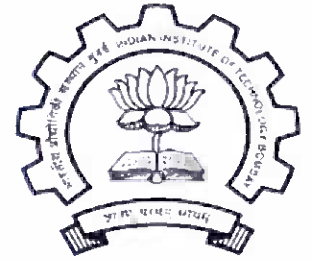
$$R_{1F} = \frac{V}{i_s} = \frac{V/i_i}{(1 + A\beta)} = \frac{R_i}{1 + A\beta}$$



CDEEP
IIT Bombay