

Analysis of Feedback Amplifier



CDEEP
IIT Bombay

1. Basic Amplifier is Unilateral, but the Gain is evaluated with Loading of
 - (i) feedback network
 - (ii) Source & Load Resistances
 2. Feedback network too is Unilateral. Essentially we say there is no or very little feed forward case
- Analysis Steps:-
- (a) Identify Topology - What is type of feedback (Sampling) and how it mixes at the Input.

Slide No. 2

You have a Series Mixing if in the input circuit, there is a circuit component (w) which is in Series with V_s . Then

$$x_f = V_f \text{ is Feedback signal}$$

You have Shunt Mixing at Input Circuit, if there is a connection between 'Input Node' (Base or Gate) and the output circuit, then

$$x_f = I_f \text{ current feedback}$$

We also talk for Sampling now:





CDEEP
IIT Bombay

(i) Set $V_o = 0$ ($R_{load} = 0$). If now x_f becomes 'Zero', then Sampling is Voltage kind
This is called Shunt Sampling

(ii) Set $I_0 = 0$ ($R_L \rightarrow \infty$), then if
 $x_f = 0$, then we have Current
Sampling or Series Sampling



CDEEP
IIT Bombay

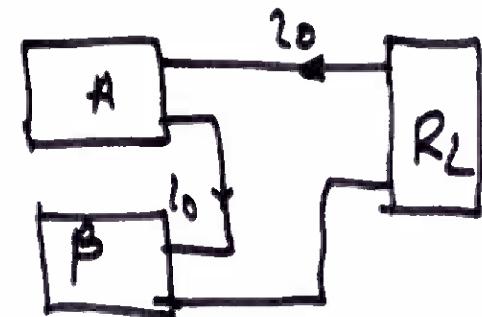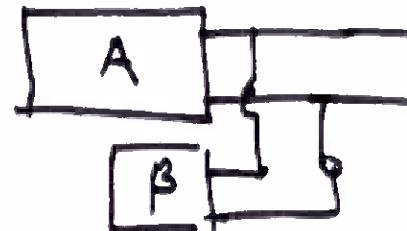

[2] Amplifier Without Feedback

Step (a) Find Input Circuit by

Setting $V_o = 0$ (Shunt Sampling)

$I_o = 0$ (Series Sampling)

Step (b) Find Output Circuit by

Setting $V_i = 0$ for Current Mixing (shunt)

or $I_i = 0$ for Voltage Mixing (series)




CDEEP
IIT Bombay

Slide No: 5

Then get AOL from this circuit.

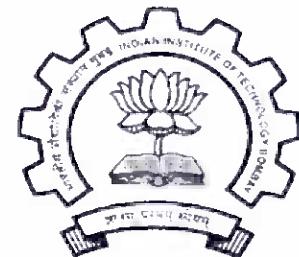- (c) Evaluate β for the topology = $\frac{x_f}{x_0}$
- (d) Get $AOL\beta = T$ for the amplifier
- (e) Evaluate $A_{CL} = A_F$ for the Amplifier
- (f) Evaluate R_{IF} and R_{OF} for the Amplifier



CDEEP
IIT Bombay

Slide No: 6


Since R_E is common between Input & Output Circuit, this amplifier is Voltage Amplifier.



CDEEP
IIT Bombay

Circuit without Feedback:

Input Circuit:— Set $V_o = 0$


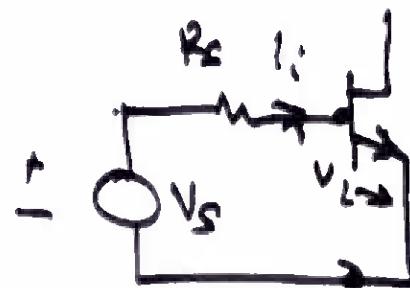


Output Circuit: Set $V_o = 0$ (current sampling) & $i_i = 0$ (voltage sampling)

If we make $i_i = 0$, there is dependent source in the output we have circuit with only load resistance R_E .

Slide No. 7

Example of Source/Emitter follower

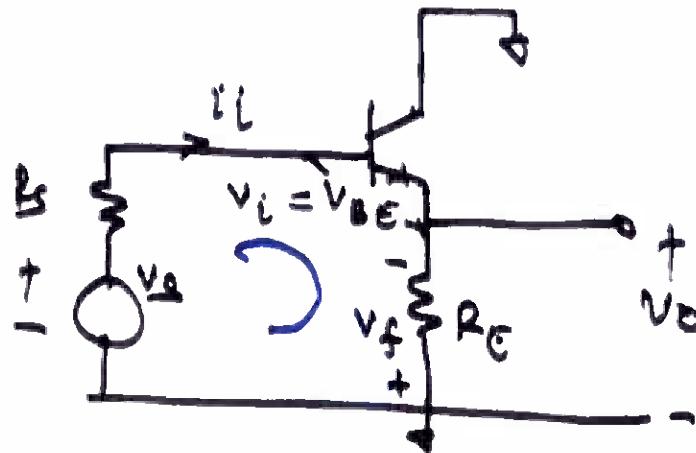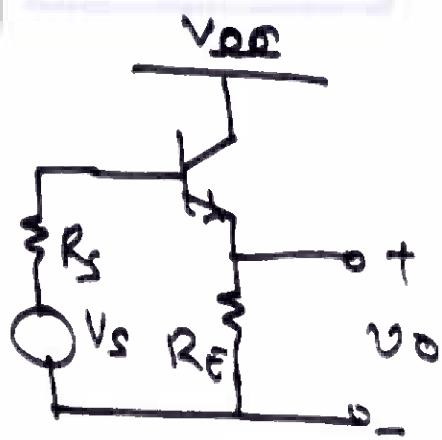CDEEP
IIT Bombay

If we want to make $V_0 = 0$, $V_f = 0$ hence Input has Series Mixing and Shunt Sampling
 \therefore It is Series - Shunt Amplifier


For 1 Shunt Sampling

$$R_{OF} = \frac{R_o}{1 + T}$$

$R_o = r_o$ for
our Voltage Amplifier.


$$= \frac{r_o}{1 + \frac{\beta R_{OE}}{r_n + R_s}} = \frac{r_o(r_n + R_s)}{r_n + R_s + \beta R_{OE}}$$
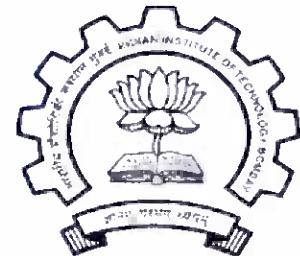
$$\approx \frac{R_s + r_n}{\beta} = \frac{2k}{10^6} = 20 \Omega$$




CDEEP
IIT Bombay

Shunt - Shunt Amplifier

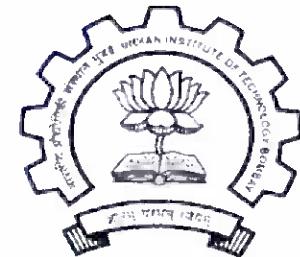

CDEEP
IIT Bombay

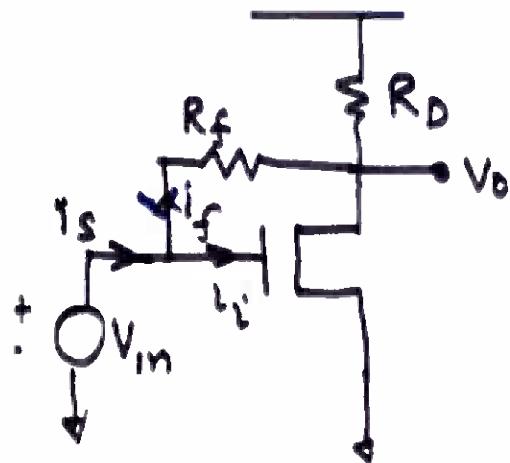

R_f sums currents at Gate Node

$$i_i = i_s - i_f$$

Since 'Input' circuit node is connected to 'output' node through R_f , then Feedback has Shunt Mixing

If we make $V_o = 0$, then there is no feedback.

Hence we have Shunt Sampling

Hence Amplifier without feedback has
eq. circuit as



$$\frac{1}{R_{ODF}} = \frac{1}{r_o} + \frac{1}{R_f} + \frac{1}{R_o}$$

$$\therefore A_{OL} = \frac{V_o^*}{i_s^*} = \frac{V_o^*}{V_{in}} \cdot \frac{V_{in}}{i_s^*} = -g_m R_{ODF} \cdot R_f$$

$$R_i^* = R_f \quad \& \quad R_o^* = R_{ODF}$$

$$\text{Feedback factor } \beta = \frac{i_f^*}{V_o^*} = \frac{1}{R_f}$$




CDEEP
IIT Bombay

$$\begin{aligned}
 \therefore A_{CL} &= \frac{V_o}{I_s} = \frac{A_{OL}}{1 + A_{OL}\beta} \\
 &= -\frac{g_m R_{ODF} \cdot R_f}{1 + g_m R_{ODF} \cdot R_f \cdot \frac{1}{R_f}} \\
 &= -R_f \quad \text{if } g_m R_{ODF} \gg 1
 \end{aligned}$$

Voltage Gain


$$\begin{aligned}
 A_{VCL} &= \frac{V_o}{V_{in}} = \frac{V_o}{I_s} \cdot \frac{I_s}{V_{in}} = A_{CL} \cdot \cancel{\frac{I_s}{V_{in}}} \\
 &= -\frac{g_m R_{ODF} \cdot R_f}{1 + g_m R_{ODF}} \cdot \frac{1}{R_f} = -\frac{g_m R_{ODF}}{1 + g_m R_{ODF}}
 \end{aligned}$$
18

ac equivalent circuit is

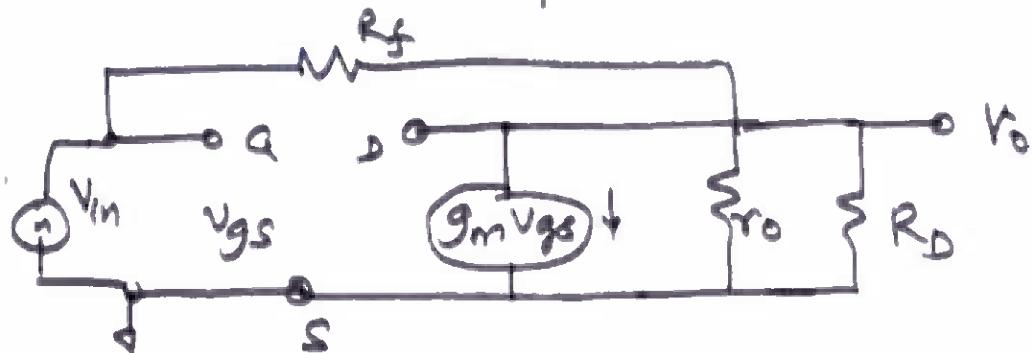


Open loop Amplifier will then be :

(a) Input Circuit : we set $V_o = 0$

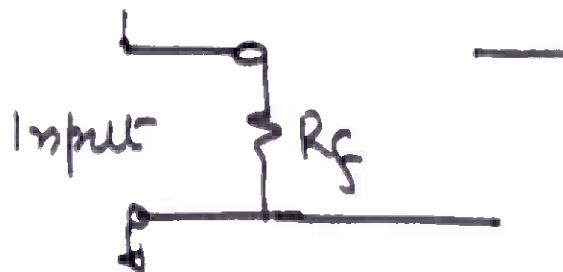



(b) Output Circuit : We set $V_{in} = 0$

(Shunt Sampling), then

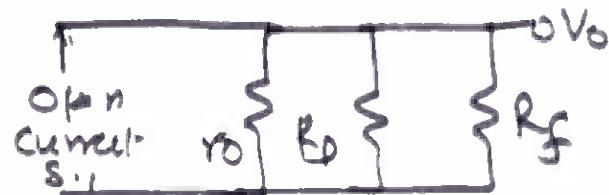

Session 13

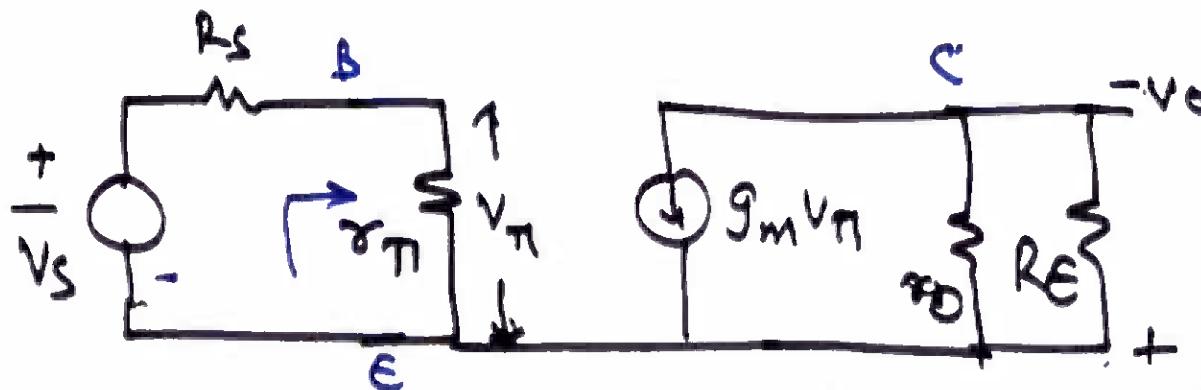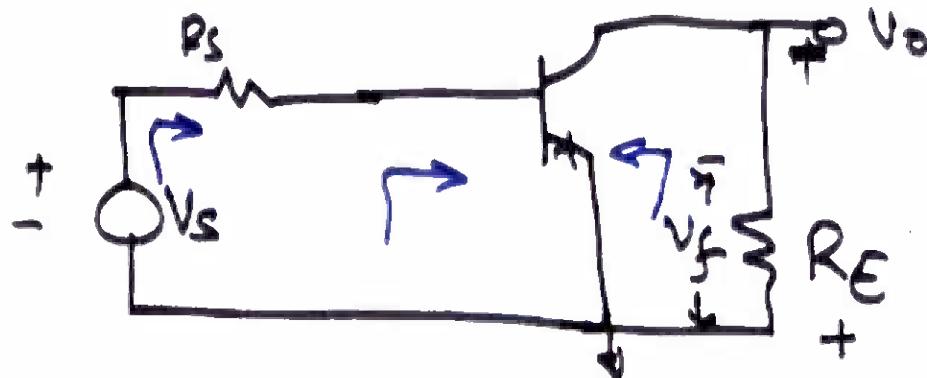Hence Amplifier without Feedback
has the Circuit



$$\therefore A_{OL} = \frac{V_o}{V_s} = + \frac{r_\pi}{r_\pi + R_s} \cdot g_m R_E$$

$$V_\pi = \frac{r_\pi}{r_\pi + R_s} V_s$$

$$R_{OE} = \pi_011 R_E$$



CDEEP
IIT Bombay

$$\beta = \frac{V_f}{V_o} = 1$$

$$\therefore T = AOL\beta = \frac{g_m r_{\pi} ROE}{r_{\pi} + R_s} = \frac{\beta ROE}{r_{\pi} + R_s}$$


Then Feedback Gain $A_{CL} = A_f$

$$\begin{aligned} &= \frac{AOL}{1+T} = \frac{\beta ROE / (r_{\pi} + R_s)}{1 + \frac{\beta ROE}{r_{\pi} + R_s}} \\ &= \frac{\beta ROE}{r_{\pi} + R_s + \beta ROE} \end{aligned}$$

$$R_{IF} = (1+T) R_i$$

We have $R_i = r_{\pi}$
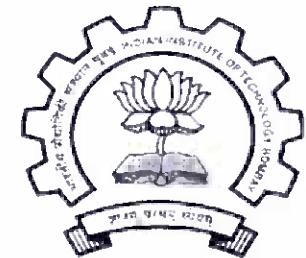
$$\begin{aligned} \therefore R_{IF} &= r_{\pi} \cdot \left[1 + \frac{\beta ROE}{(r_{\pi} + R_s)} \right] \\ &= r_{\pi} + \frac{r_{\pi}}{r_{\pi} + R_s} \cdot \beta ROE \approx r_{\pi} + \beta ROE \end{aligned}$$



CDEEP
IIT Bombay

$$R_{if} = \frac{V_{in}}{i_s} = \frac{R_f}{1 + g_m R_{odf} \cdot R_f / R_f}$$

$$= \frac{R_f}{1 + g_m R_{odf}}$$

$$\therefore A_{vcl} = - \frac{g_m R_{odf} R_f}{1 + g_m R_{odf}} \cdot \frac{1 + g_m R_{odf}}{R_f}$$

$$= - g_m R_{odf}$$



CDEEP
IIT Bombay

Stability

$$A_{CL} = \frac{A_{OL}}{1+T}$$

If $T > 0$ (+ive), we have negative feedback.


Then $A_{CL}(s) < A_{OL}(s)$ and feedback stabilises $A_{CL}(s)$.

If $T < 0$, we have Positive Feedback, then

$$A_{CL}(s) > A_{OL}(s) \quad \text{This leads to Instability}$$


Even without signal, small noise at Input ^{is} amplified and positive feedback increases Input to Amplifier, thus increasing output further. In a typical case the system may oscillate.

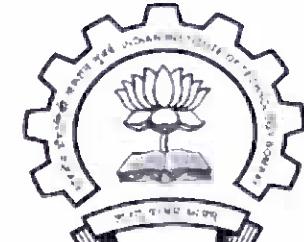We can find Stability condition in Negative Feedback Amplifier by observing Bode's Plots for Closed Loop Gain Transfer Function




CDEEP
IIT Bombay

Phase Margin & Gain Margin

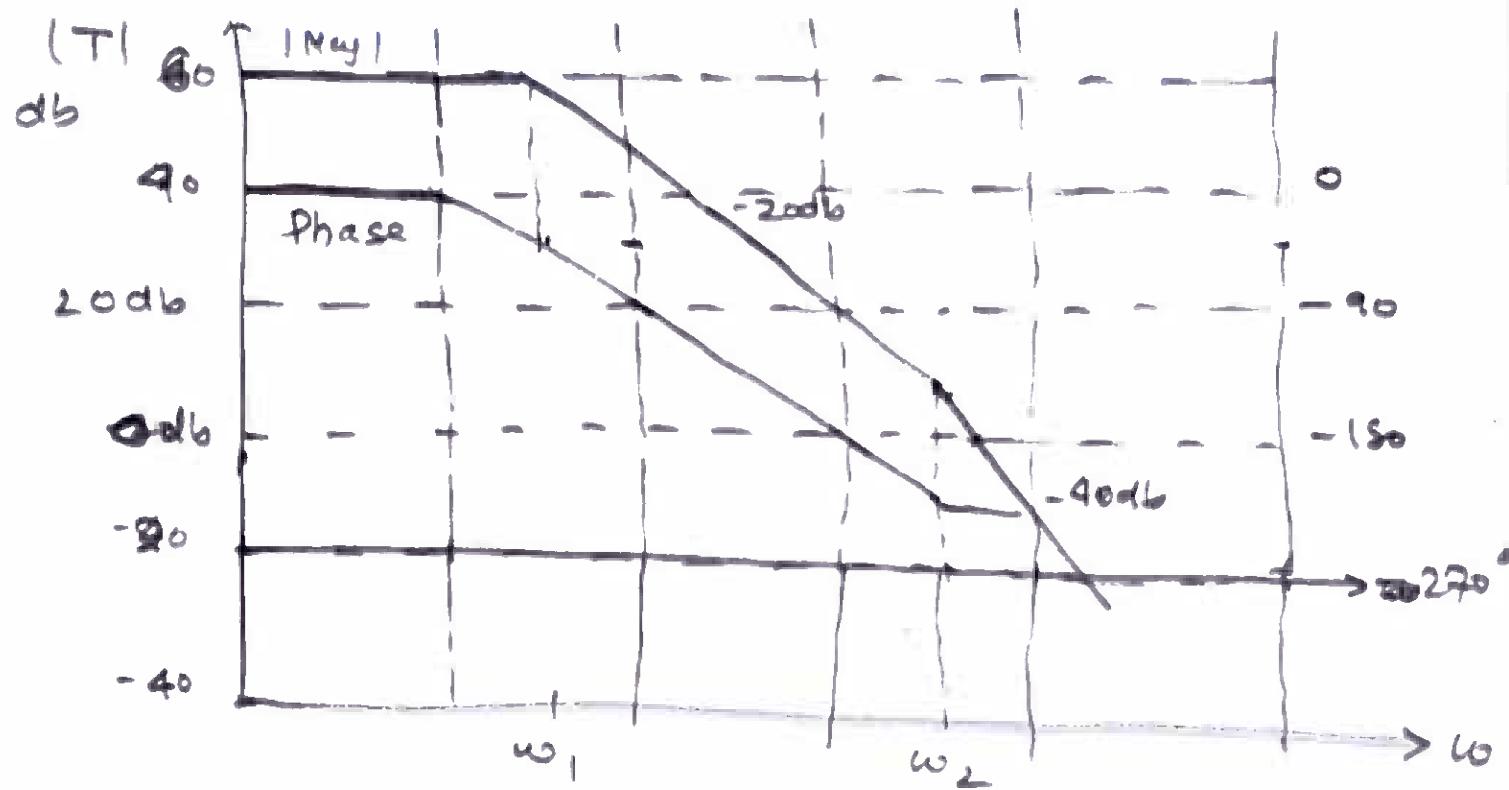

$$\phi_M = \angle T(j\omega_0) + 180^\circ ; GM = -20 \log T(j\omega_0)$$

Stability in Feedback Amplifiers

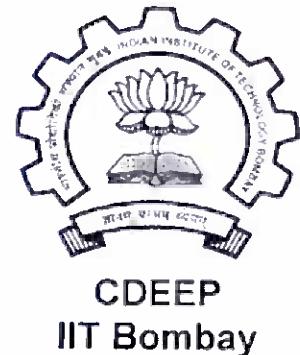

$$A_{CL}(s) = \frac{A_{OL}(s)}{1 + T(s)}$$

We see that 'zeros' of $(1+T(s))$ are poles of $A_{CL}(s)$, and Any Poles of $A_{OL}(s)$ are not common to $T(s)$

We assume AOL makes system stable, then on S-plane ($\sigma+j\omega$ plane) then Poles of AOL will be on the Left Half Plane

Typical

$$A_{CL}(s) = \frac{A_{FO}}{1 + \frac{a_1 s}{1 + T_0} + \frac{a_2 s^2}{1 + T_0} + \frac{a_3 s^3}{1 + T_0}}$$

Generalised Expressions for T.F.A Stability

$$A_{cl}(s) = \frac{A(s)}{1 + A(s)\beta(s)}$$

as $s = j\omega$

$$A_{cl}(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)\beta(j\omega)}$$

The Loop Gain $= T = A(j\omega)\beta(j\omega)$ is a complex fn.

$$\begin{aligned} T(j\omega) &= A(j\omega)\beta(j\omega) \\ &= |A(j\omega)\beta(j\omega)| e^{j\phi(j\omega)} \end{aligned}$$

Amplitude & Phase


If $\phi(j\omega) = 180^\circ$ for a frequency, $T(j\omega) = \text{Negative Real No.}$

Thus A_{cl} will increase as ω

If $|T(j\omega)| = 1$ at $\omega = \omega_{iso}$

Then $A_{av} = \frac{A(s)}{s} = 0$

\therefore amplifier becomes Oscillator

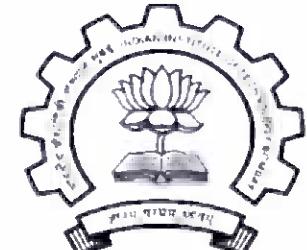


CDEEP
IIT Bombay



$$T = 1/\alpha$$


$\text{Gain}|\text{AB}|$
in db

0db

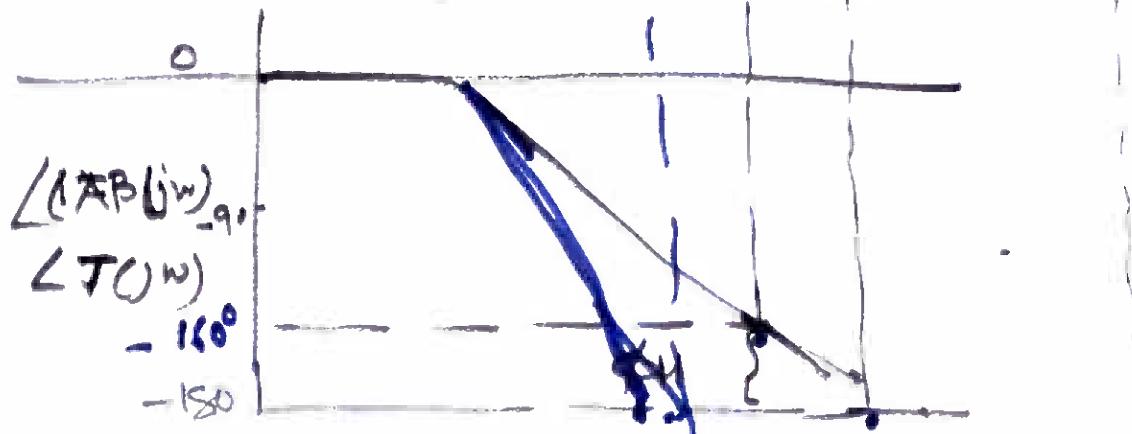


Compensation

① Miller Compensation & Pole splitting

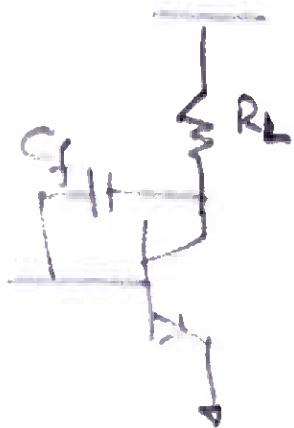

$$\omega_{P1} \approx \frac{1}{g_m R_2 C_f R_1}$$
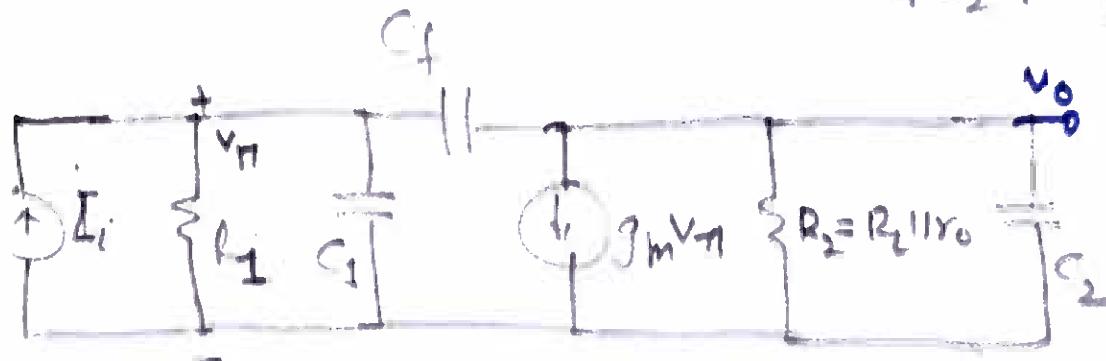
$$\omega_{P2} \approx \frac{g_m C_f}{C_1 C_2 + C_f (C_1 + C_2)}$$



$$= \frac{g_m}{\frac{C_1 C_2}{C_f} + (g_m + C_2)}$$



CDEEP
IIT Bombay

Without feedback

$$\omega_{P1} = \frac{1}{R_1 C_1}$$

$$\omega_{P2} = \frac{1}{R_2 C_2}$$