
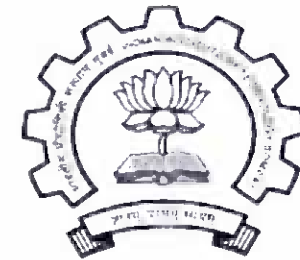


Slide No: 1


# OPAMP as Circuit Element

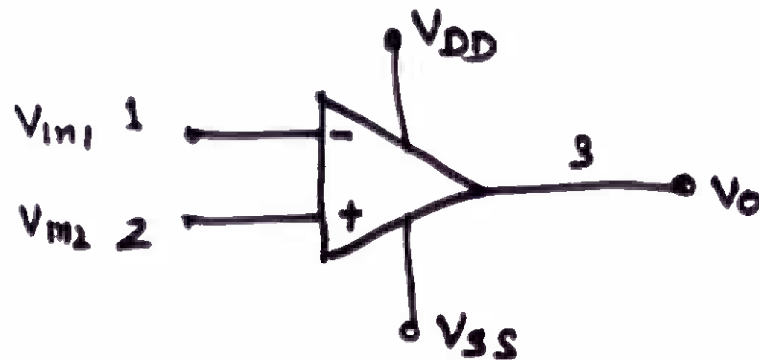

CDEEP  
IIT Bombay





Equivalent Circuit

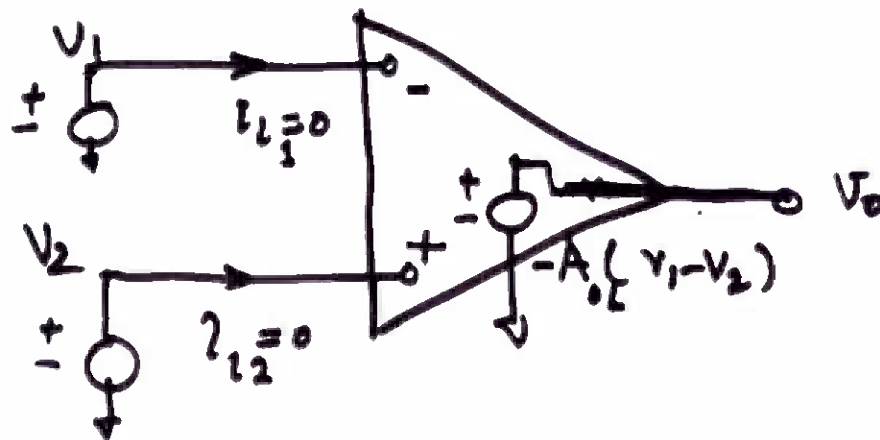

Slide No: 2

## Inverting & Non Inverting Amplifier

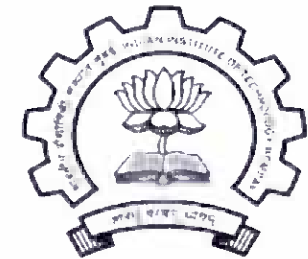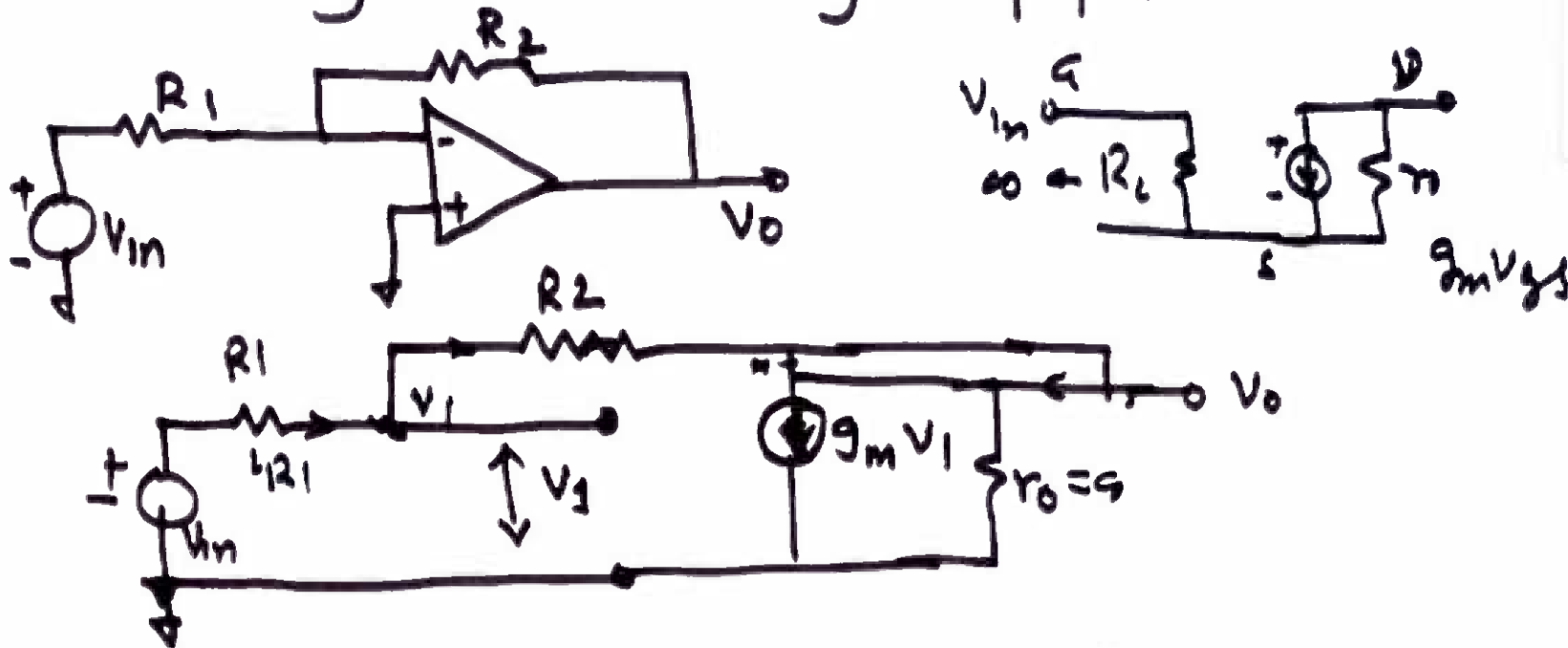

CDEEP  
IIT Bombay


$$\frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_o}{R_2} \quad \text{or} \quad \frac{V_{in}}{R_1} + \frac{V_o}{R_2} = \underline{V_1} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

## Ideal Parameters


$$R_i \rightarrow \infty$$

$$r_o \rightarrow 0$$

$A_v$  is very large

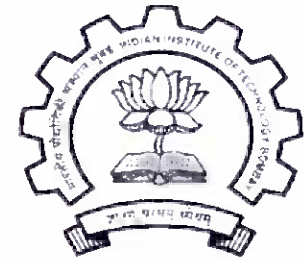

CDEEP  
IIT Bombay

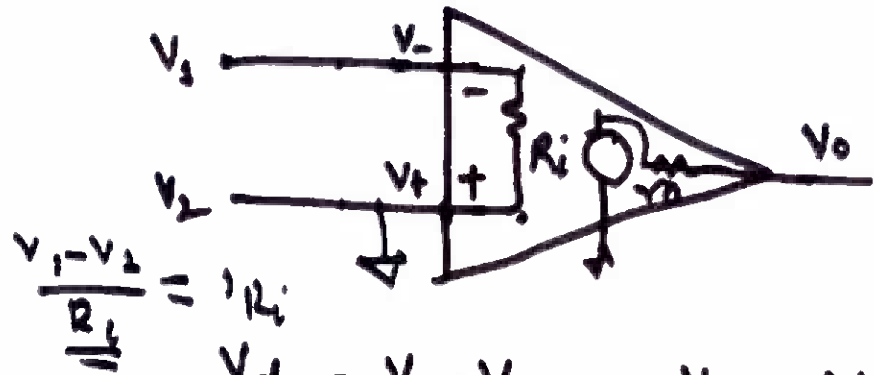

$$V_d = V_1 - V_2 = V_- - V_+$$

$$V_o = -A_v (V_- - V_+) = -A_v V_d$$

$$\text{or } V_d = -\frac{V_o}{A_v} \quad \text{If } A_v \rightarrow \infty \quad V_d \rightarrow 0$$

$$\boxed{\text{Then } V_- = V_+}$$


Hence if we Ground  $V_+ \Rightarrow 0$

$$\text{Then } V_- = 0$$

This is Concept of Virtual Ground.

Slide No: 4

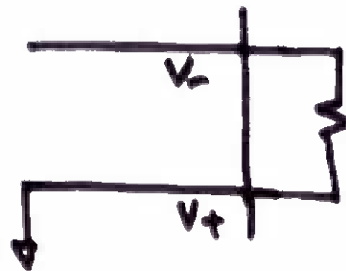
Alternatively as  $R_i \rightarrow \infty$ , no current passes through it



As  $I_i = 0$


$\therefore V_- = V_+ = 0$

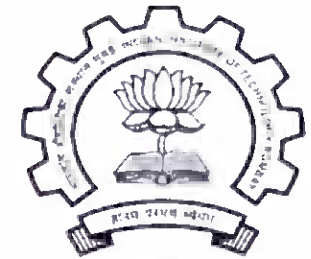$V_-$  getting 'Zero' potential.. This is called Virtual Ground.




CDEEP  
IIT Bombay

Slide No: 5

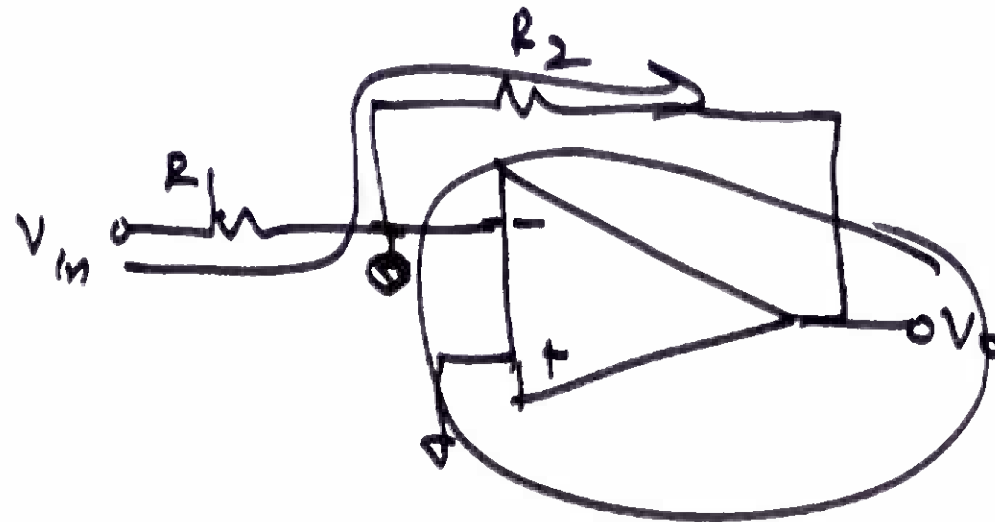


$$V_o = -\frac{R_2}{R_1} V_{in}$$

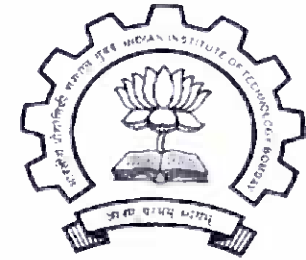

CDEEP  
IIT Bombay

## Amplifier with T-network in Feedback

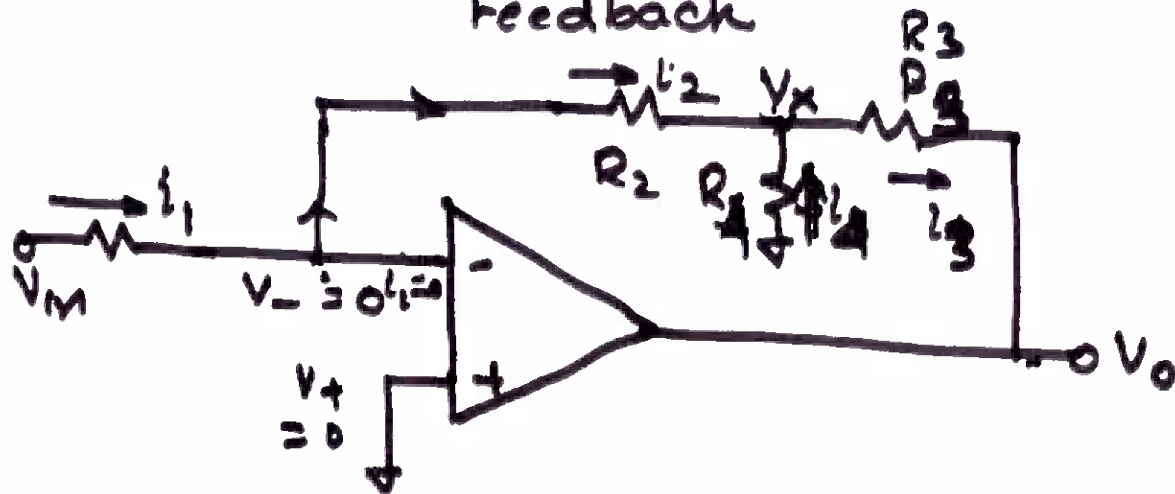


$i_1 = i_2$  as  $V_- = 0$   
 (V<sub>A</sub>)  
 No current enters  
 OPAMP inputs.

$$V_x = 0 - i_2 R_2 = -i_1 R_2 = -\frac{V_{in}}{R_1} \cdot R_2$$

At node  $V_x$   $i_2 + i_4 = i_3$
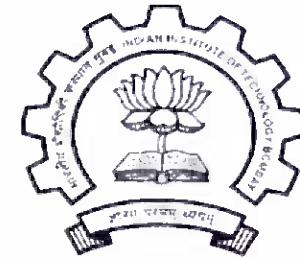
$$-\frac{V_x}{R_2} - \frac{V_x}{R_4} = \frac{V_x - V_O}{R_3} \quad \text{or} \quad V_x \left[ \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] = \frac{V_O}{R_3}$$



Slide No: 7

$$\approx -\frac{V_{in}}{R_1} R_2 \left[ \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] = \frac{V_o}{R_3}$$

$$\approx \frac{V_o}{V_{in}} = A_v = -\frac{R_2}{R_1} \left[ 1 + \frac{R_3}{R_4} + \frac{R_3}{R_2} \right]$$

Why T-Network ?


Larger Gain with . . .  
values of Resistors.



CDEEP  
IIT Bombay

Slide No: 8

## NonInverting Amplifier

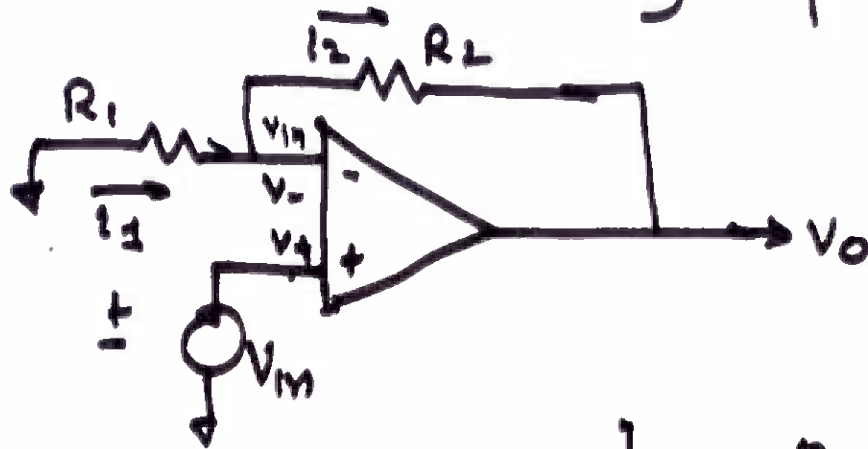

Assumption :


$R_1 \rightarrow \infty$   $\therefore$  no current enters  
OPAMP inputs.  $\therefore V_- = V_+$

$$i_1 = \frac{0 - V_-}{R_1} = -\frac{V_-}{R_1} = -\frac{V_+}{R_1} = -\frac{V_{in}}{R_1}$$

Then  $i_2 = \frac{V_- - V_o}{R_2} = \frac{V_{in} - V_o}{R_2}$

But  $i_1 = i_2$


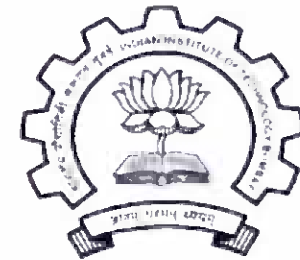
$$\therefore \frac{V_{in} - V_o}{R_2} = -\frac{V_{in}}{R_1} \quad \therefore \frac{V_o}{V_{in}} = \left(1 + \frac{R_2}{R_1}\right)$$



CDEEP  
IIT Bombay



## Interesting Circuit

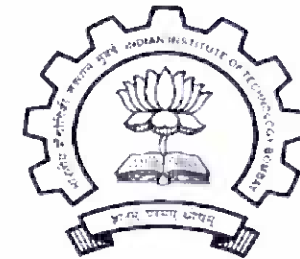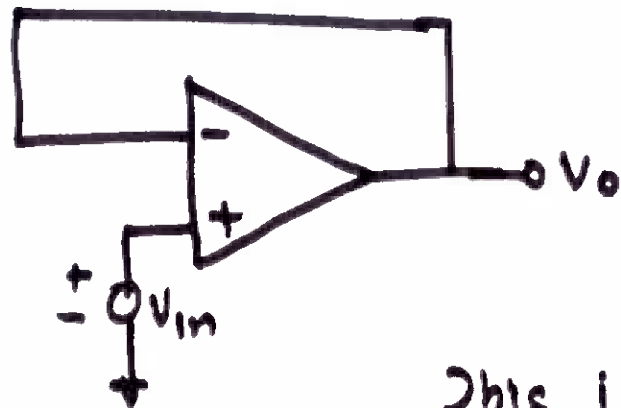
CDEEP  
IIT Bombay

$$\text{Here } V_o = V_- = V_+$$


$$\text{or } V_o = V_{in}$$

$$\therefore A_v = \frac{V_o}{V_{in}} = 1$$

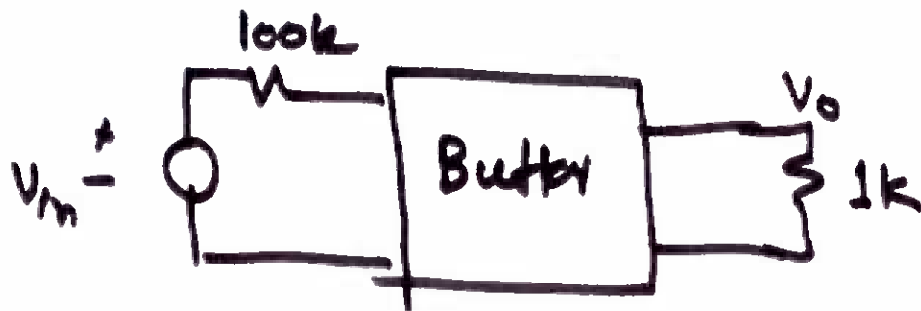This is called Voltage Follower or Buffer




Severe Loading

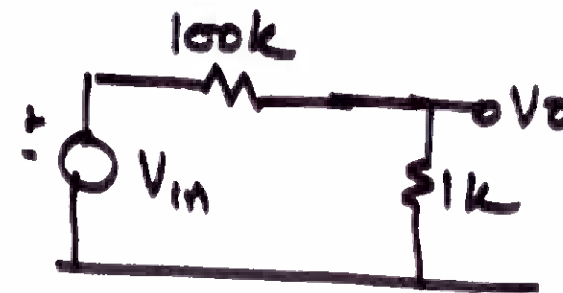


$$\frac{V_o}{V_{in}} = \frac{1k}{101k} = 0.01$$

Slide No: 10

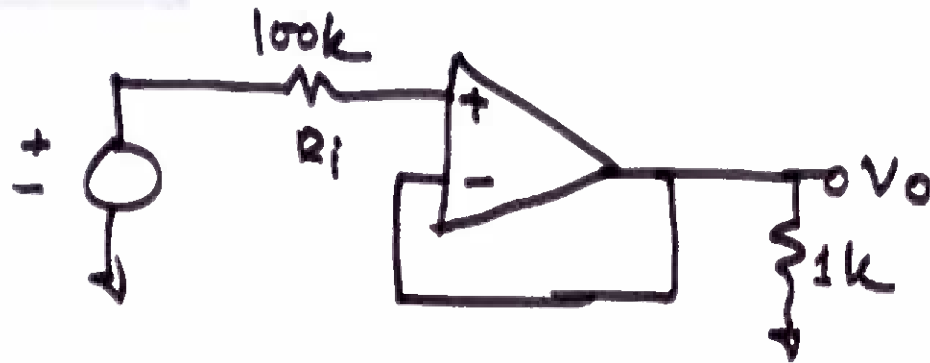

$$R_o \gg 100k \quad \therefore V_o \approx V_{in}$$

(ii) I-V Converter

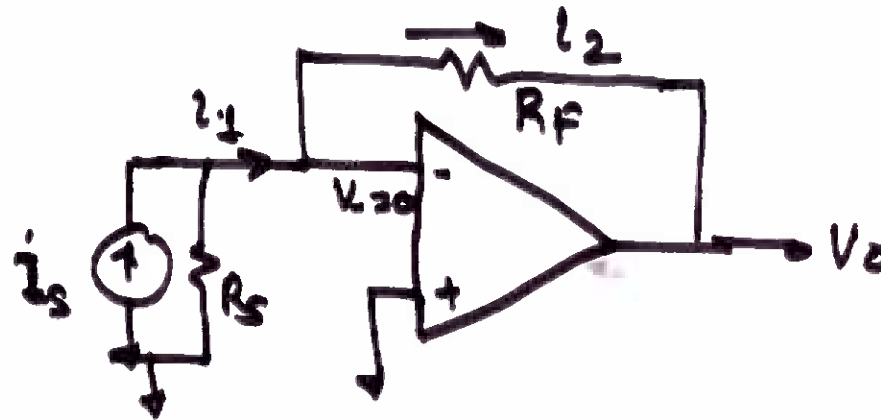

$$i_1 = i_2 = i_s$$

$$\text{But } i_2 = \frac{0 - V_o}{R_f}$$


$$\therefore V_o = -i_2 R_f = -i_s R_f$$




CDEEP  
IIT Bombay
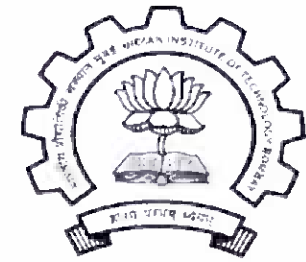
## V-I Converter

Requirement: I in Load should be independent of Load Value.



CDEEP  
IIT Bombay

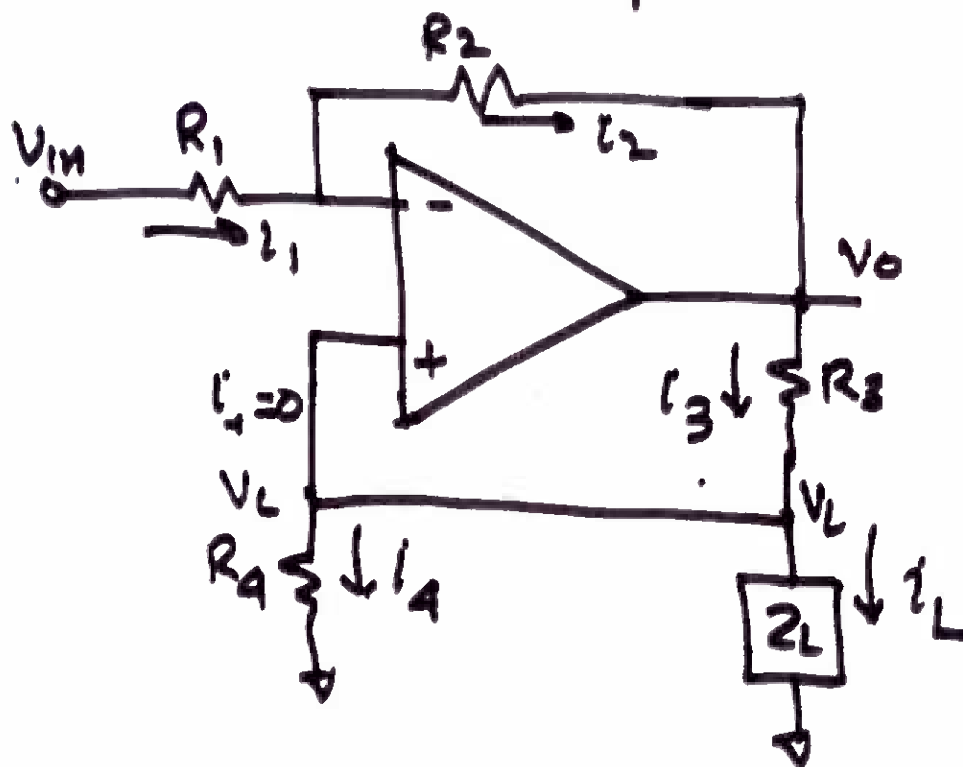

Clearly  $v_- = v_+ = v_L \neq 0$


$$\therefore v_- = v_+ = i_L Z_L = v_L$$

Also  $i_1 = i_2$

(No current enters)  
inputs

Slide No: 12
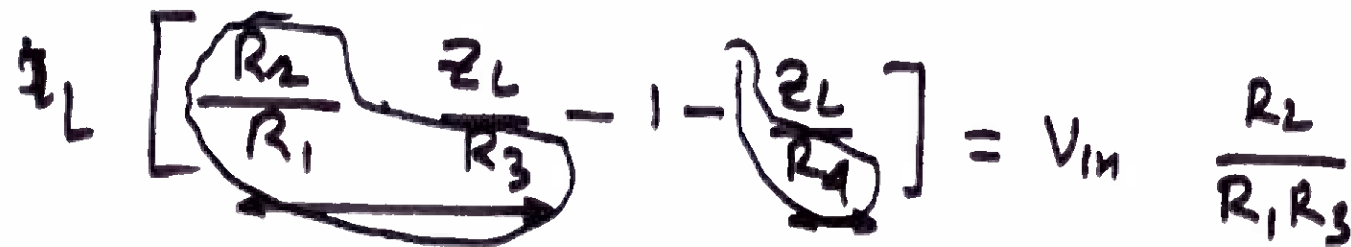
$$\sim \frac{R_2}{R_1} \cdot \left( i_L z_L - V_{in} \right) = i_L + \frac{i_L z_L}{R_4}$$



The diagram shows a circuit for applying the superposition theorem. A current source  $i_L$  is connected to a network of resistors and a load impedance  $z_L$ . The network consists of a parallel combination of  $R_2$  and  $R_1$  in series with  $z_L$  and  $R_3$ . This is followed by a series resistor  $R_4$ . The voltage across  $z_L$  is  $V_{in}$ .


$$i_L \left[ \frac{R_2}{R_1} z_L - 1 - \frac{z_L}{R_4} \right] = V_{in} \frac{R_2}{R_1 R_3}$$

for  $i_L$  to be independent of  $z_L$

$$\frac{R_2}{R_1 R_3} = \frac{1}{R_4}$$


Then

$$i_L = - \frac{1}{R_4} \cdot V_{in}$$

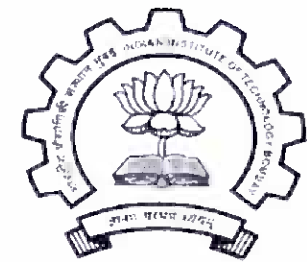


CDEEP  
IIT Bombay


# OPAMP Differentiator & Integrator

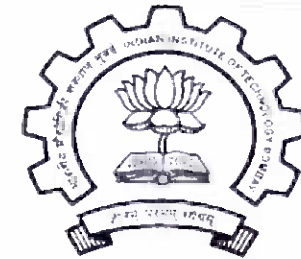

CDEEP  
IIT Bombay

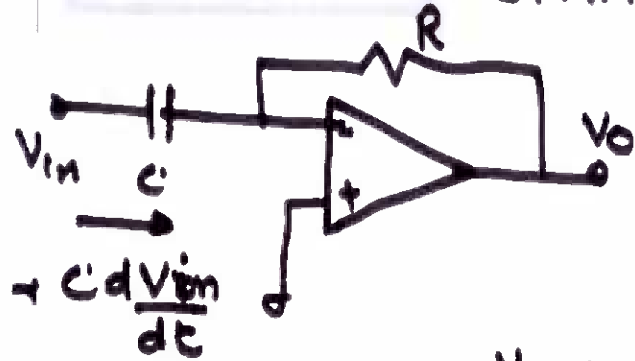

$$V_o(t) = -RC \frac{dV_{in}}{dt}$$

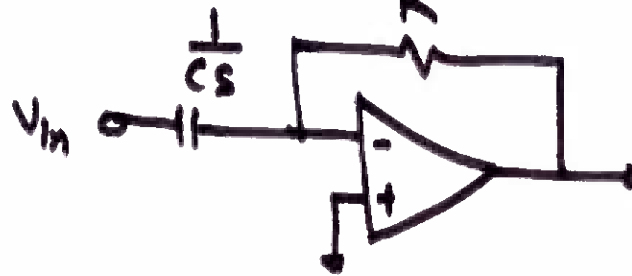

$$\frac{V_{in} - 0}{1/sC} = \frac{0 - V_o}{R}$$

or  $V_o = -RCs V_{in}$

$$\frac{V_o(s)}{V_{in}(s)} = RCs = -j\omega RC$$


$$\left| \frac{V_o(s)}{V_{in}(s)} \right| = \omega RC$$

$$\phi = \tan^{-1} \frac{\omega RC}{0} = -\tan^{-1} \infty = -\pi/2$$

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = RC \cdot s$$



$RC \Rightarrow$  Time constant

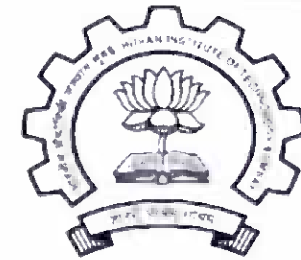

$$\therefore \frac{V_{in} - V_L}{R_1} = \frac{V_L - V_0}{R_2}$$

$$\text{or } \frac{V_{in} - i_L Z_L}{R_1} = \frac{i_L Z_L - V_0}{R_2} \quad - (1)$$


$$i_3 = \frac{V_0 - V_L}{R_3} = \frac{V_0 - i_L Z_L}{R_3} \quad - (2)$$

$$\text{But } i_3 = i_L + i_4$$

$$\text{But } i_4 = \frac{i_L Z_L}{R_4}$$

$$\therefore \frac{V_0 - i_L Z_L}{R_3} = i_L + \frac{i_L Z_L}{R_4} \quad - (3)$$

Slide No. 15

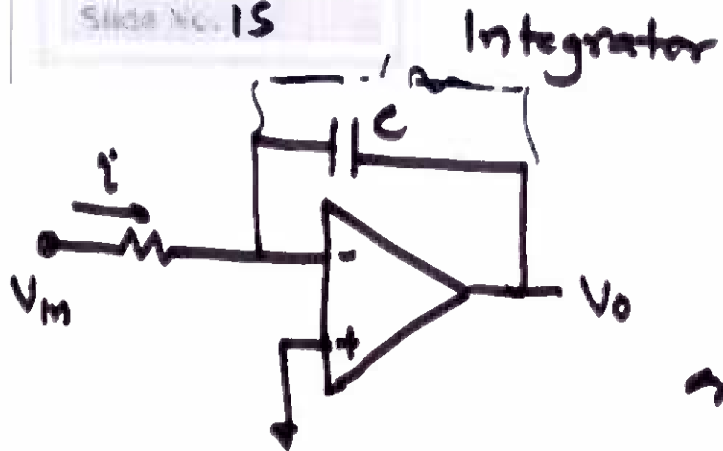



$$\frac{V_{in}}{R} = -C \frac{dV_o}{dt}$$

$$\Rightarrow V_o = -\left[ \frac{1}{RC} \int V_{in} dt + V_{co} \right]$$

$$\frac{V_o(s)}{V_{in}(s)} = -\frac{1}{sRC} = -\frac{1}{j\omega RC}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\omega RC}$$

$$\& \phi = +90^\circ$$

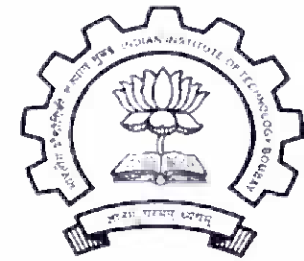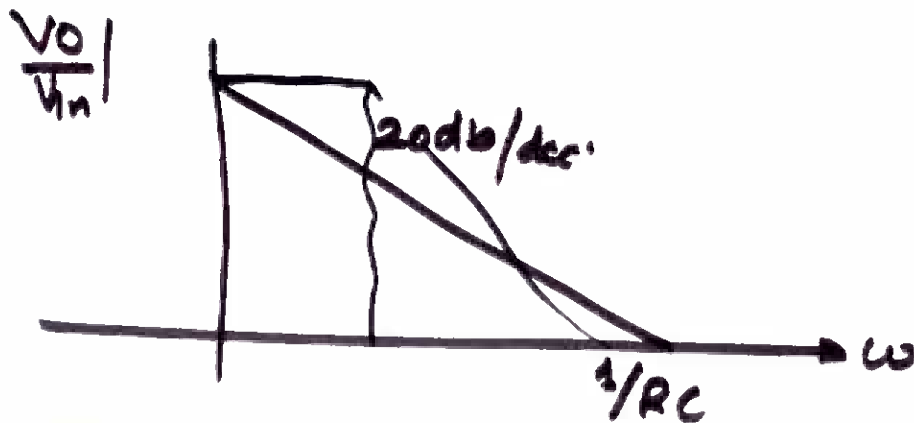


CDEEP  
IIT Bombay


# Precision Half Wave Rectifier



CDEEP  
IIT Bombay

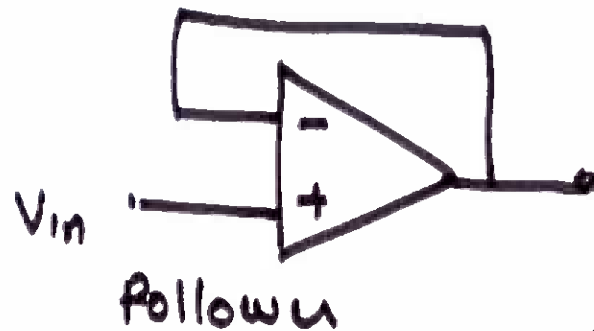

Modified V. Follower  
Circuit

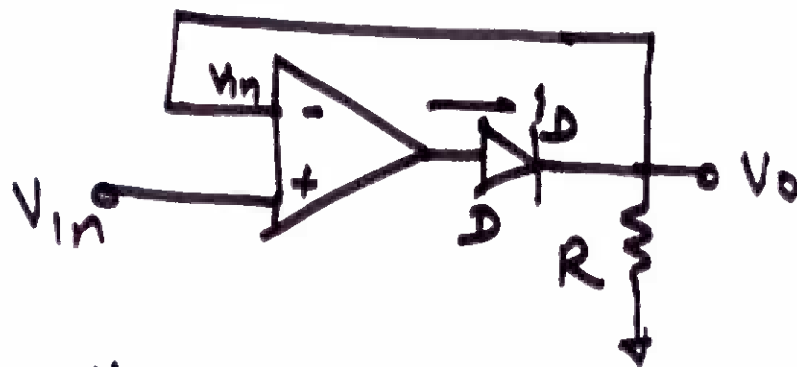

Diode current  $I = I_s \left( e^{\frac{qV_f}{\eta kT}} - 1 \right) \approx I_s e^{\frac{qV_f}{\eta kT}}$

$$\therefore \log I = \log I_s + \frac{qV_f}{\eta kT}$$

$$\therefore V_f = \frac{\eta(kT)}{q} \left[ \log I - \log I_s \right]$$

$V_m = + \text{tive}$


$V_d = V_{in} = V_-$



Slide No:

12

## Logarithmic Amplifier

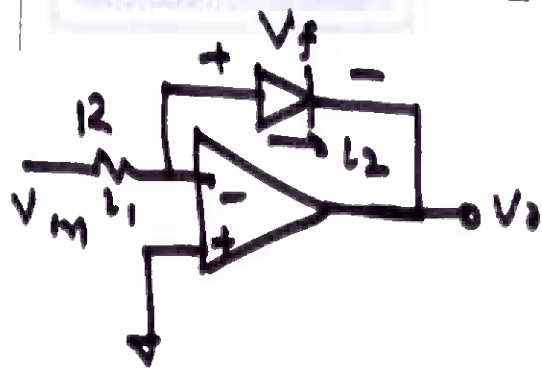

$$i_1 = \frac{V_{in}}{R} = i_2 = i_D$$

If  $i_D = 0$  then  $i_1 = 0$   
then  $V_0 = 0$


But if Diode conducts ( $V_- > V_0$ )

Then  $V_f + V_0 = 0$  or  $V_0 = -V_f = -\frac{\eta kT}{q} [\log i_2 - \log I_s]$

$$\therefore V_0 = -\frac{\eta kT}{q} [\log V_{in} - \log R - \log I_s]$$

$$V_0 = -\frac{\eta kT}{q} \left[ \log \frac{V_{in}}{R I_s} \right]$$


$$\therefore V_0 \propto \log(V_{in})$$

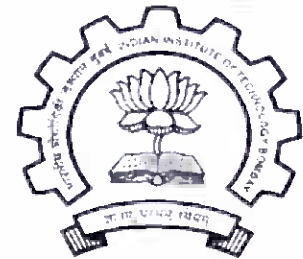

CDEEP  
IIT Bombay

## Antilog Amplifier

Basic amplifier

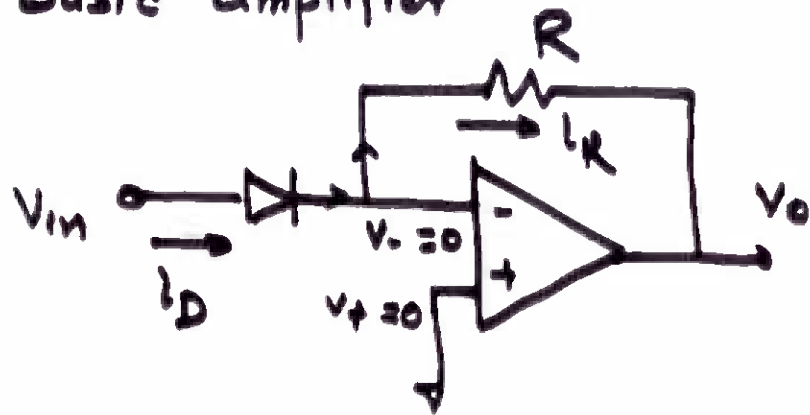


We have

$$i_D = I_S \exp\left(\frac{qV_f}{\eta kT}\right)$$

As  $V_+ = 0$ , Hence  $i_R \cdot R = -V_o = + i_D \cdot R$

$$\therefore V_o = -I_S R \exp\left(\frac{qV_f}{\eta kT}\right) \quad \therefore V_o \propto \exp(V_f)$$

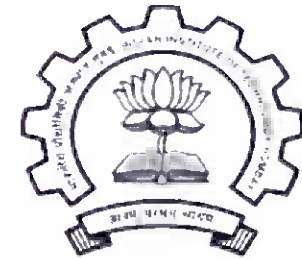CDEEP  
IIT Bombay


## Analog Multiplier

Mathematically  $\log(AB) = \log A + \log B$

$$\begin{aligned} \text{Also } AB &= \text{Antilog}(AB) \\ &= \text{Antilog}[\log A + \log B] \end{aligned}$$


Clearly we can get Multiplication of AB by using three amplifier and an Adder.

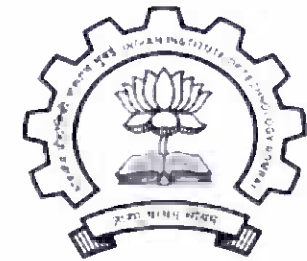- ① Create  $\log A$
- ② Create  $\log B$
- ③ Create  $(\log A + \log B)$
- ④ Create Antilog of  $[\log A + \log B]$




Slide No. 20

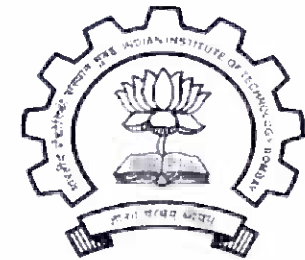We want Multiplication of  $V_1$  &  $V_2$



CDEEP  
IIT Bombay

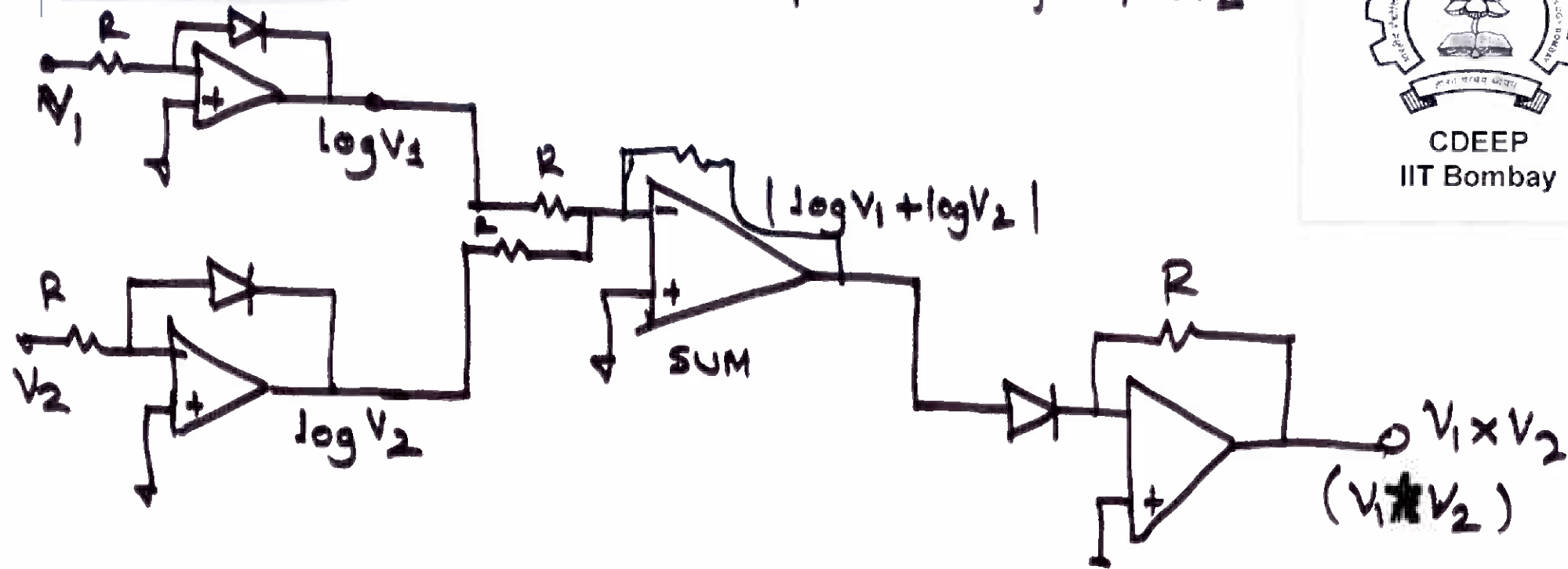


OPEN LOOP

$$A_{OL}(\omega) = \frac{A_0}{1 + j \frac{\omega}{\omega_0}}$$

$\omega_0$  is Dominant Pole.

Clearly  $\omega_0 \cdot A_0 = \omega_T$  from  
the Figure (Bode Plot)

$$A_0 \omega_0 = 1 \cdot \omega_T$$

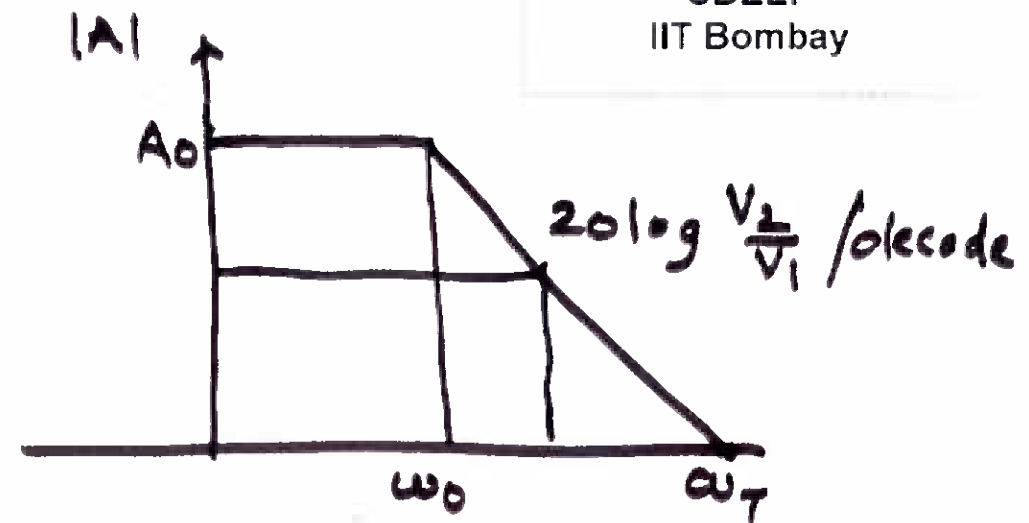


Slide No: 22

where  $\omega_T$  is unity Gain Bandwidth  
or Gain Bandwidth product, (GBW).

Assumptions : Other poles occur at  
 $\omega > \omega_T$  & System is Stable.

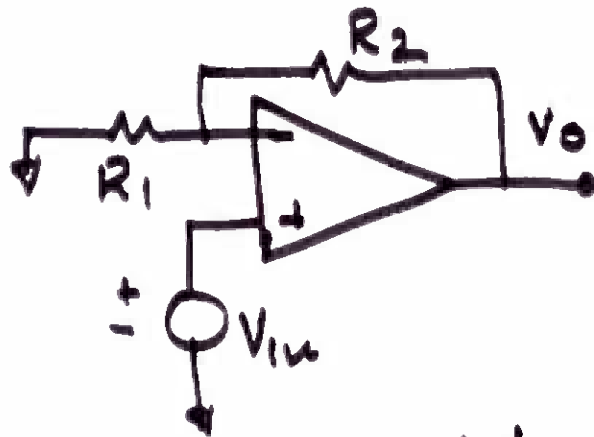
Closed Loop : Take a case of Non Inverting Amplifier



With  $R_2$  in feedback, the amplifier  
is Shunt Shunt Feedback Amplifier

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

Where  $A_{CL}$  is Closed Loop Gain

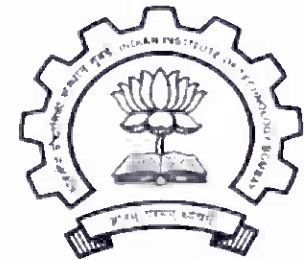

CDEEP  
IIT Bombay

Slide No. 23

The feedback factor  $\beta$  is

given by 
$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1}{1 + R_2/R_1}$$


$$\therefore A_{cl}(\omega) = \frac{A_0}{1 + \frac{A_0}{1 + R_2/R_1}} \cdot \frac{1}{1 + j \frac{\omega}{\omega_0 \left[ 1 + \frac{A_0}{1 + (R_2/R_1)} \right]}}$$

Normally


$$A_0 \gg (1 + R_2/R_1)$$

Then
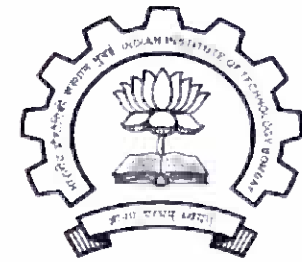
$$A_{cl0} = \frac{A_0}{1 + \frac{A_0}{1 + R_2/R_1}} \approx \left( 1 + \frac{R_2}{R_1} \right)$$




CDEEP  
IIT Bombay

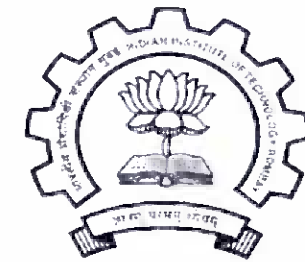

$$or A_{CL}(\omega) = \frac{A_{CLO}}{1 + j \frac{\omega}{\omega_0 (A_0/A_{CLO})}}$$

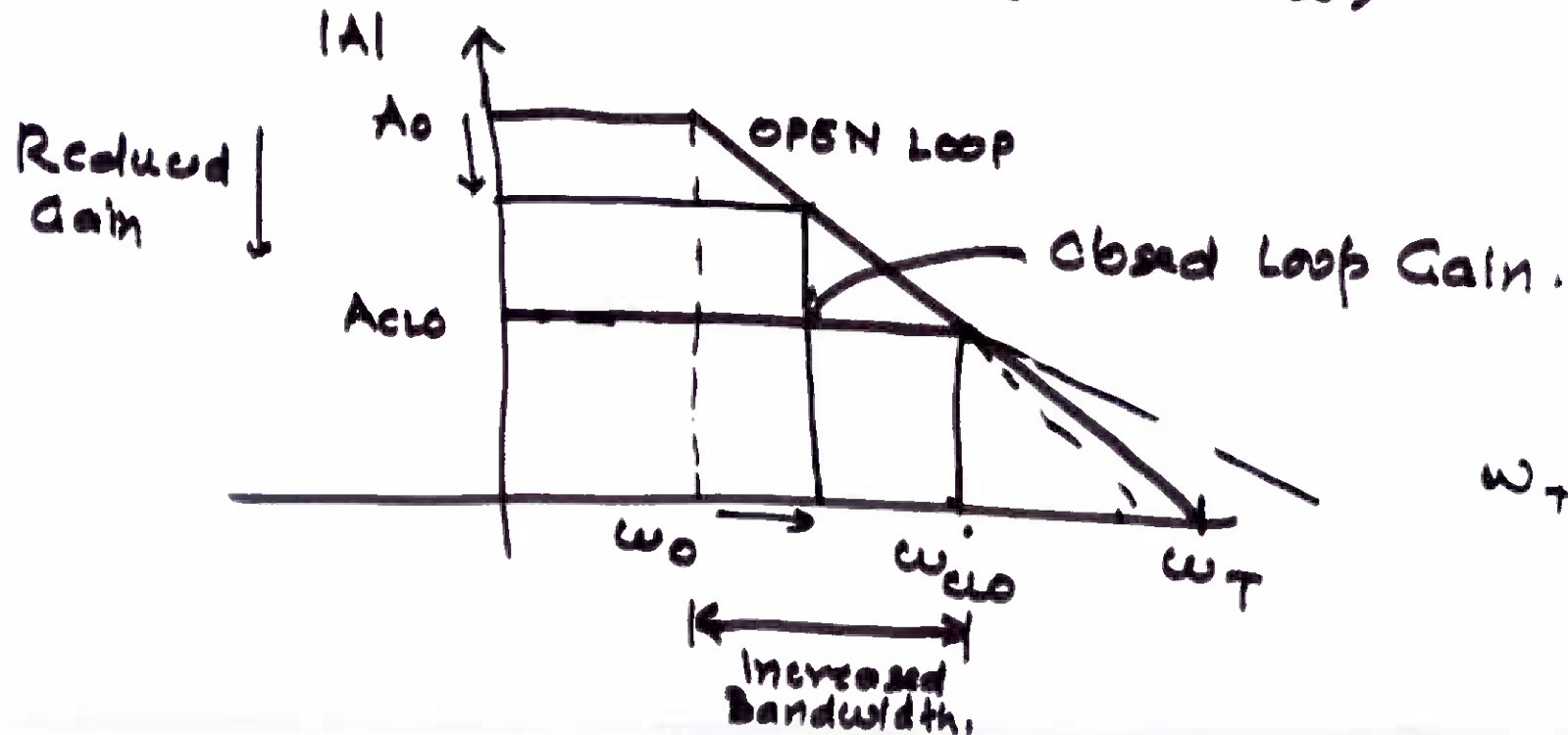New Bandwidth  $\omega_{CLO} = \omega_0 (A_0/A_{CLO})$




$$\omega_{TCL} = \omega_{TOL}$$



Slide No: 25

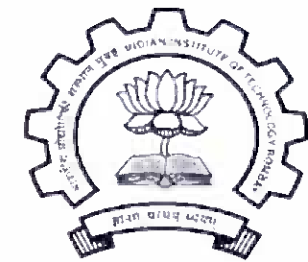Proof that:  
" $\omega_T$  is same for OPEN LOOP  
&  
Closed Loop Case"



CDEEP  
IIT Bombay




$$|A_{CL}(\omega = \omega_T')| = 1 = \frac{A_{CL0}}{\sqrt{1 + \left[ \frac{\omega_T'}{\omega_0 (A_0/A_{CL0})} \right]^2}}$$

$\omega_T'$  = Unity Gain Frequency  
for Closed Loop.

If square [ ] term is  $\gg 1$

Then  $A_{CL0} \approx \frac{\omega_T'}{\omega_0 (A_0/A_{CL0})}$
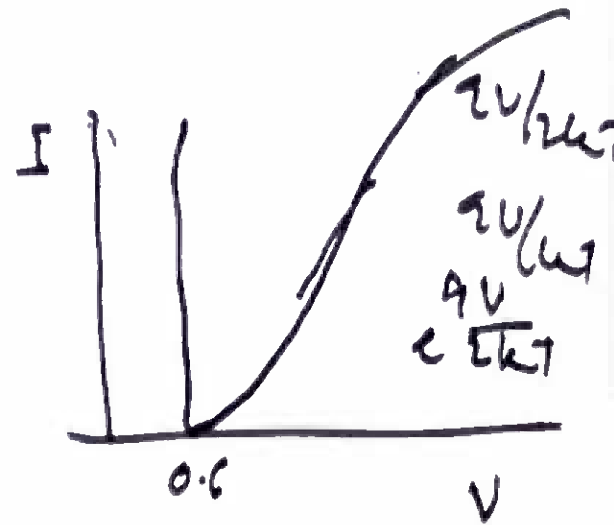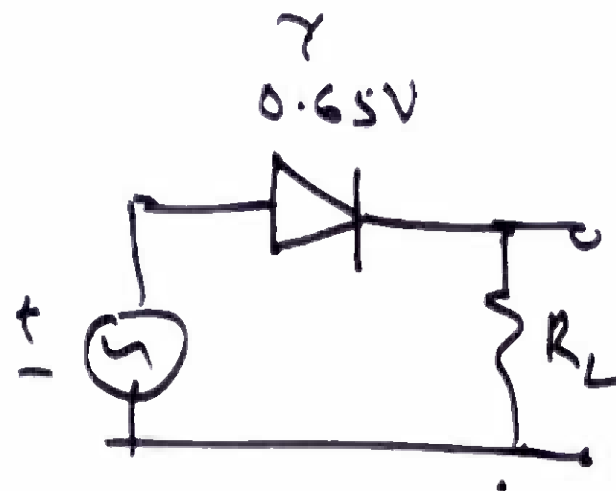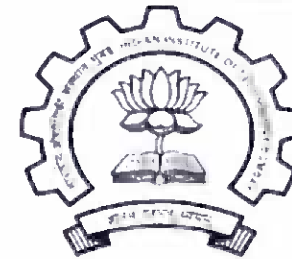
$$\therefore \omega_T' = A_{CL0} \cdot \omega_0 (A_0/A_{CL0}) = A_0 \cdot \omega_0 = \omega_T$$



$$V - V_f = V_d$$

$$= \frac{0.6}{10^5} = 60 \mu$$

