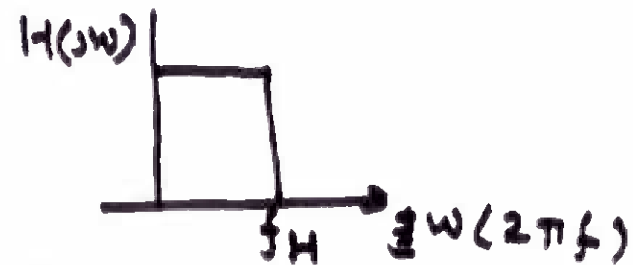



Slide No: 1

Active RC Filters


1. Low Pass





2 High Pass

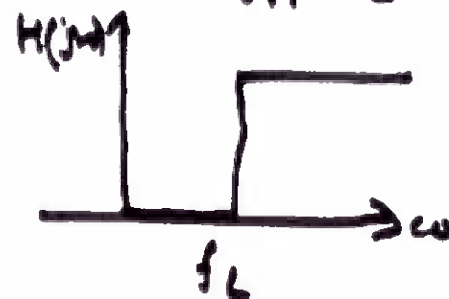

3 Band Pass

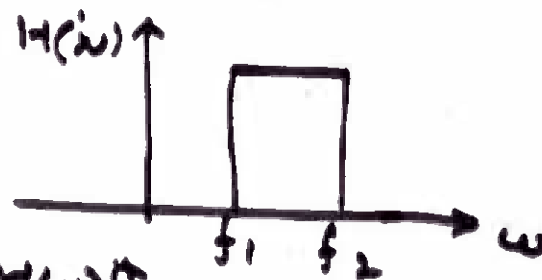

4 Band Reject

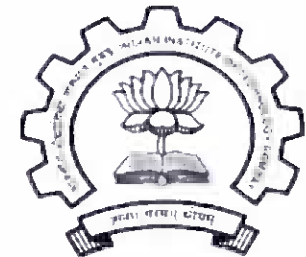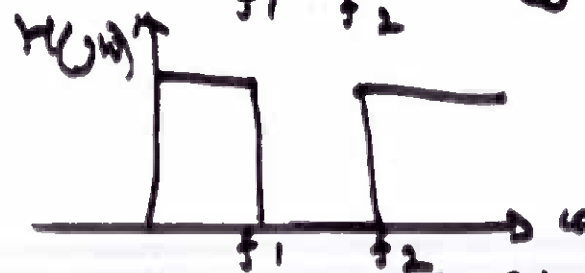

CDEEP
IIT Bombay


Course Name
Analog Circuits

Lecture No: 21


Instructor's Name
Prof. A. N. Chandorkar

Slide No: 2

Active Networks

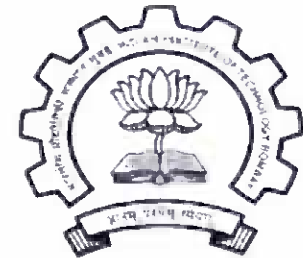

CDEEP
IIT Bombay


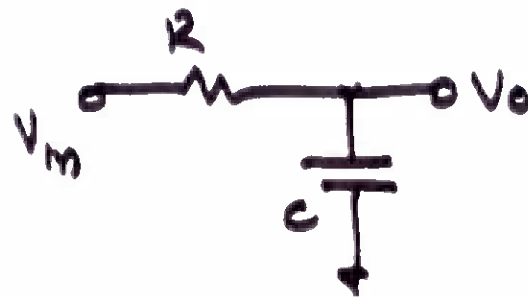


$$\therefore \frac{V_o(s)}{V_m(s)} = H(s) = \frac{1/s}{1/s + R} = \frac{1}{1 + RCs}$$

$$\text{or } H(s) = \frac{1}{1 + s/(1/RC)}$$

$\therefore \omega_0 = 1/RC$ is the Pole



For $\omega < \omega_0$ $|H(s)| = \left| \frac{RC}{j\omega + RC} \right| = \frac{RC}{\sqrt{\omega^2 + R^2C^2}}$

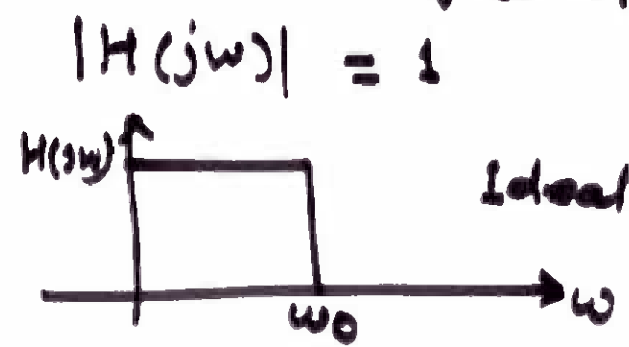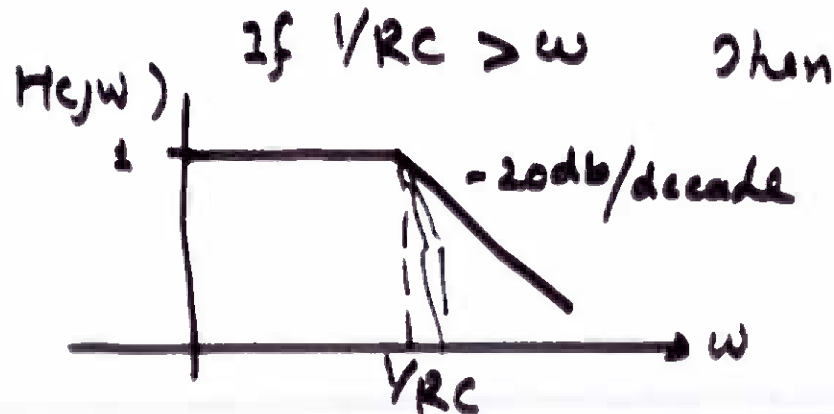

Slide No. **3**



CDEEP
IIT Bombay

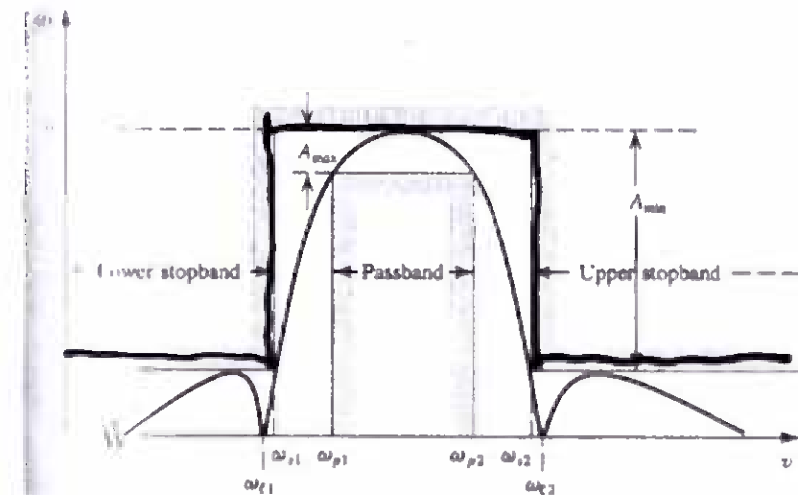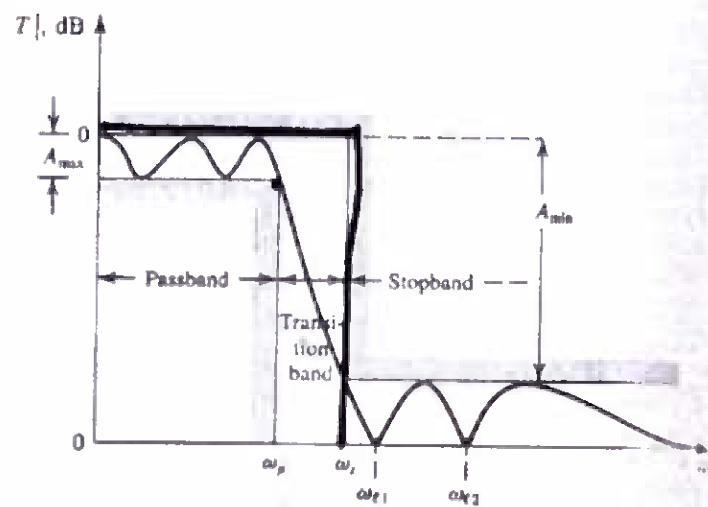


Course Name
Analog Circuits


Lecture No. **21**

Instructor's Name
Prof. A. N. Chandorkar

Slide No. 4

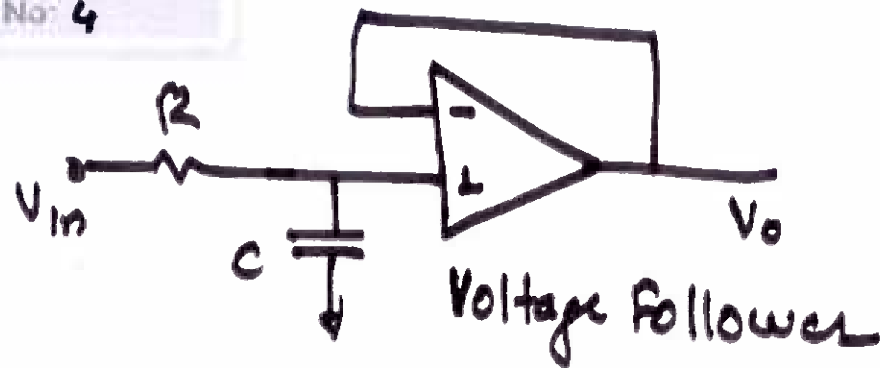


Low Pass Filter

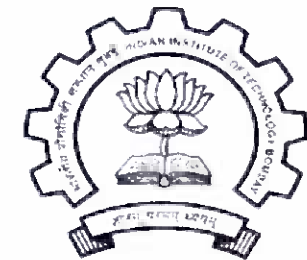

CDEEP
IIT Bombay

(2) High Pass

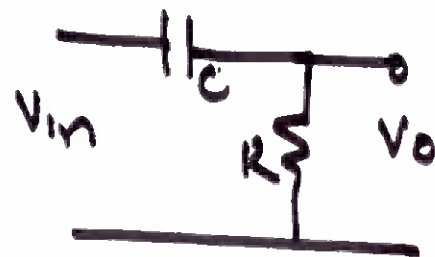



If $\omega > \omega_0$

$$H(\omega) = 1$$


$$\begin{aligned} \frac{V_o(s)}{V_{in}(s)} &= \frac{R}{R + \frac{1}{Cs}} = \frac{RCs}{RCs + 1} \\ &= \frac{\frac{s}{\omega_0}}{\frac{s}{\omega_0} + 1} = \frac{(s/\omega_0)}{(\frac{s}{\omega_0} + 1)} \end{aligned}$$

where $\omega_0 = 1/RC$ (rad/s)

Slide No: 5

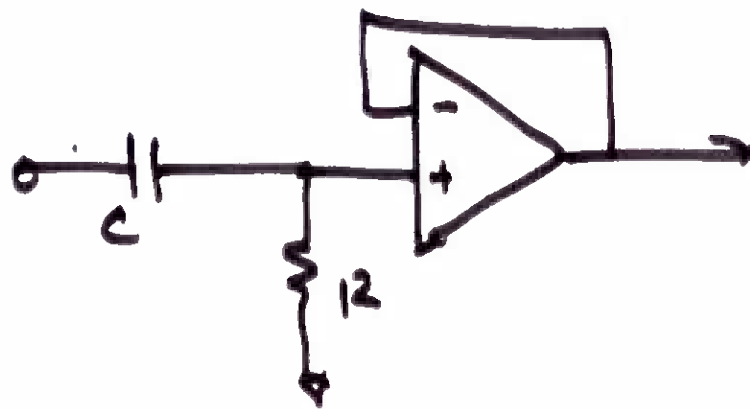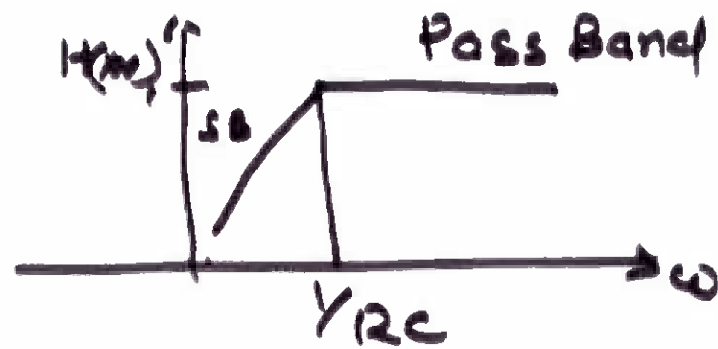



High Pass filter.

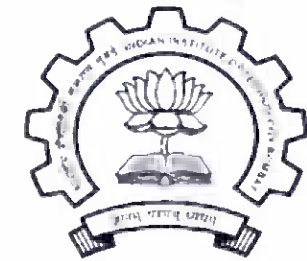

CDEEP
IIT Bombay

Generalised Two Pole Active Filter

Slide No: 6

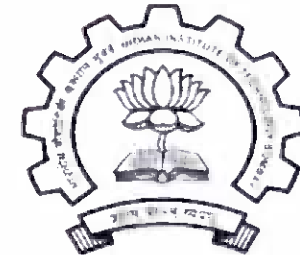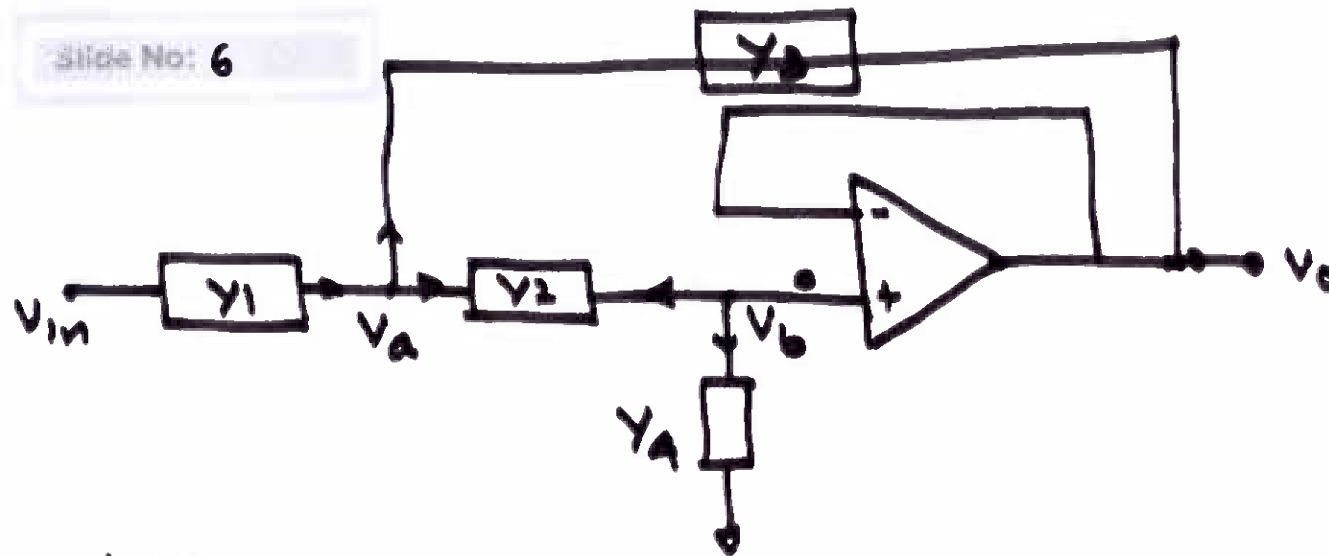

CDEEP
IIT Bombay

$$Y = G + jB$$

$$Z = R + jX$$

At Node V_a :

$$(V_{in} - V_a) Y_1 = (V_a - V_b) Y_2 + (V_a - V_o) Y_3 \quad \text{--- (i)}$$

At node V_b

$$-(V_b - V_a) Y_2 = V_b \cdot Y_4 \quad \text{--- (ii)}$$

Further $V_o = V_b$ --- (iii)

Slide No: 7

From eq. (ii) & (iii)


$$V_a Y_2 = V_b Y_2 + V_b Y_4 = (Y_2 + Y_4) V_b$$

$$\therefore V_a = V_b \left(\frac{Y_2 + Y_4}{Y_2} \right) \quad \text{--- (iv)}$$

Substituting V_a in eq (i)


$$V_{in} Y_1 - V_b \left(\frac{Y_2 + Y_4}{Y_2} \right) Y_1 = V_b \left(\frac{Y_2 + Y_4}{Y_2} \right) (Y_2 + Y_3)$$
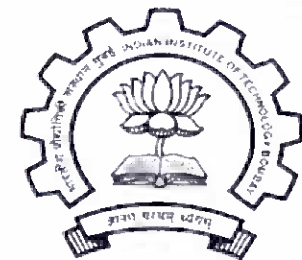
$$\therefore \frac{V_o(s)}{V_{in}(s)} = T(s) = \frac{Y_1 Y_2}{Y_1 Y_2 + (Y_1 + Y_2 + Y_3) Y_4} = H(s)$$



CDEEP
IIT Bombay


Slide No. 8

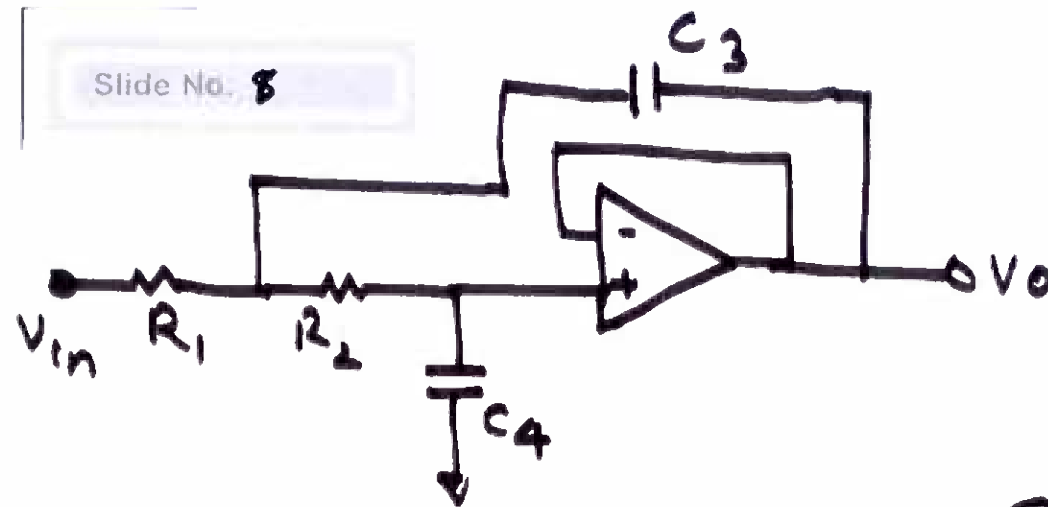

(Example)

$$G = \frac{1}{R}$$

$$Y = (Cs)$$

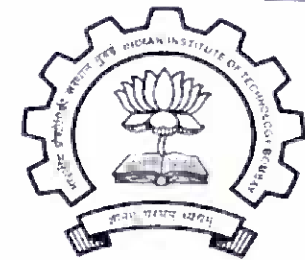

CDEEP
IIT Bombay

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{G_1 G_2}{G_1 G_2 + sC_4(G_1 + G_2 + sC_3)}$$

At $s = j\omega \rightarrow 0$

$$H(s) = \frac{G_1 G_2}{G_1 G_2} = 1$$

At $s = j\omega \rightarrow \infty$

$$H(s) \rightarrow 0$$

This is a Butterworth Filter

We assume $R_1 = R_2 = R$

Course Name

Analog Circuits

Lecture No. 2)

Instructor's Name

Prof. A. N. Chandorkar


Slide No. 9

We have then

$$H(s) = \frac{L/R^2}{\frac{1}{R^2} + sC_4\left(\frac{2}{R} + sC_3\right)}$$
$$= \frac{1}{1 + 2RC_4s + C_4C_3R^2s^2}$$

$$|H(j\omega)| = \frac{1}{\sqrt{(1 - \omega^2\tau_3\tau_4)^2 + (2\omega\tau_4)^2}}$$

For Maximally Flat Filter $\frac{d|H(j\omega)|}{d\omega} \rightarrow 0$

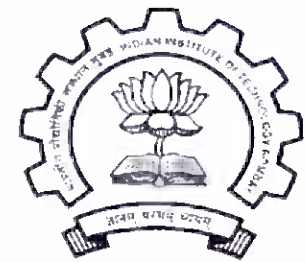

CDEEP
IIT Bombay

Define
 $\tau_3 = RC_3$
 $\tau_4 = RC_4$

Slide No. 10

Differentiating $|H(j\omega)|$ and putting it = 0, we get

$$0 = 4\omega\tau_4 [-\tau_3(1 - \omega^2\tau_3\tau_4) + 2\tau_4]$$

And at $\omega=0$ $\tau_3 = 2\tau_4$ or $C_3 = 2C_4$

Substituting this in $|H(j\omega)|$ function

$$|H(j\omega)| = \frac{1}{[1 + 4(\omega\tau_4)^4]^{1/2}}$$

Cut off or pole occurs when $|H(j\omega)| = 1/\sqrt{2}$ (-3db)





CDEEP
IIT Bombay

Slide No: 11

$$\therefore \omega_{\text{pole}} = \frac{1}{\sqrt{2} \tau_4} = \frac{1}{\sqrt{2} RC_4}$$

Using Bode's criterion
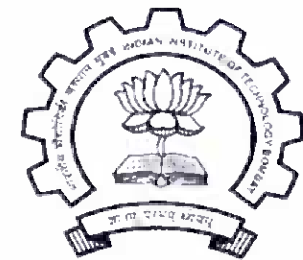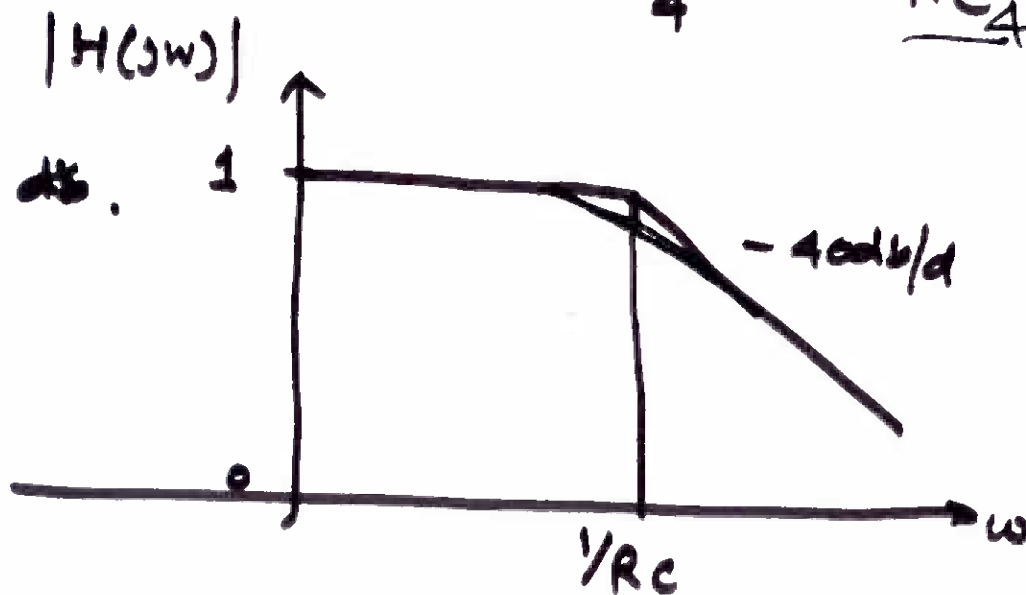
$$\omega_{\text{pole}} = \frac{1}{RC_4} = \underline{\underline{\frac{1}{RC_4}}}$$



CDEEP
IIT Bombay

Course Name

Analog Circuits


Lecture No. 21

Instructor's Name

Prof. A. N. Chandorkar

Biquadratic Function
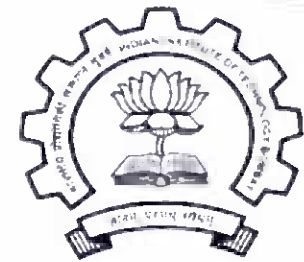
$$H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$$



CDEEP
IIT Bombay

Low Pass

$$\frac{K}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

or

$$\frac{K(s+z)}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

High Pass

$$\frac{Ks^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

or

$$\frac{Ks(s+z)}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

Bandpass

$$\frac{K \cdot s}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

Band Reject

$$\frac{K(s^2 + \omega_0^2)}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$\left\{ \begin{array}{l} \frac{1}{2Q} = \gamma \\ \text{is called} \\ \text{Damping factor} \end{array} \right.$

Slide No. 13

Then using KCL at nodes, we get-

$$H(s) = \frac{A_{vo}}{R_1 R_2 C_1 C_2 s^2 + s [C_2 (R_1 + R_2) + R_1 C_1 (1 - A_{vo})] + 1}$$


From Tr. F'n for LP Filter

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 C_1 (1 - A_{vo}) + (R_1 + R_2) C_2}$$

If we choose $R = R_1 = R_2$ & $C_1 = C_2 = C$

Then
$$H(s) = \frac{A_{vo}}{R^2 C^2 s^2 + RC(3 - A_{vo})s + 1}$$

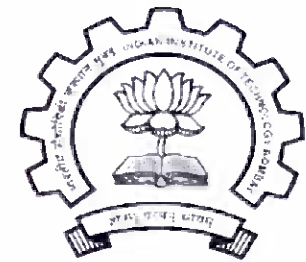& $\omega_0 = \frac{1}{RC}$ & $Q = \frac{1}{3 - A_{vo}}$ For stability $A_{vo} \leq 3$ @



CDEEP
IIT Bombay

Course Name

Analog Circuits

Lecture No. 21


Instructor's Name

Prof. A. N. Chandorkar

Slide No: 14


$$\text{Low Pass HCS)} = \frac{H_0}{\frac{s^2}{\omega_0^2} + \frac{1}{Q} \cdot \left(\frac{s}{\omega_0}\right) + 1}$$

where $k/\omega_0^2 = H_0$

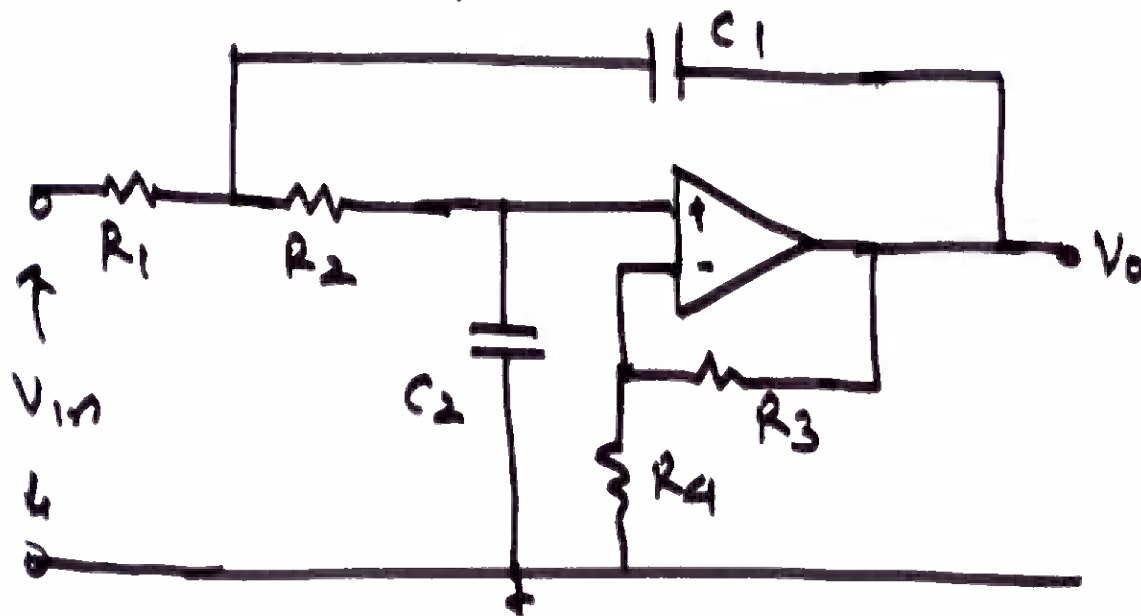


Low Pass - Section 1
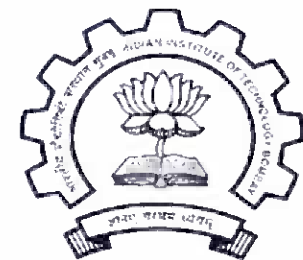
$$A_V(\omega) = \left(1 + \frac{R_3}{R_4}\right)$$




CDEEP
IIT Bombay

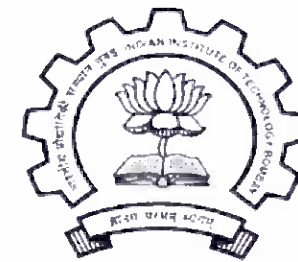Biquad Filter Implementation using OTA g_m/c or g_m-c Filter.




CDEEP
IIT Bombay

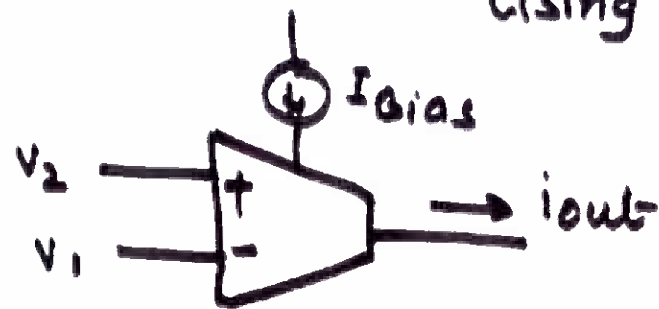


$$G_m = g_m K$$
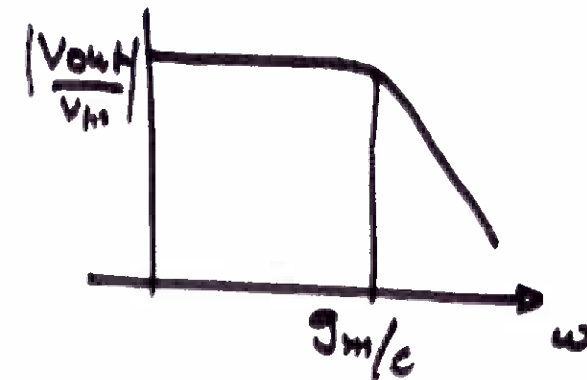
$$g_m = \sqrt{2 \beta' \left(\frac{W}{L}\right) I_{Bias}}$$



$$V_{out} = i_{out} \cdot \frac{1}{Cs}$$
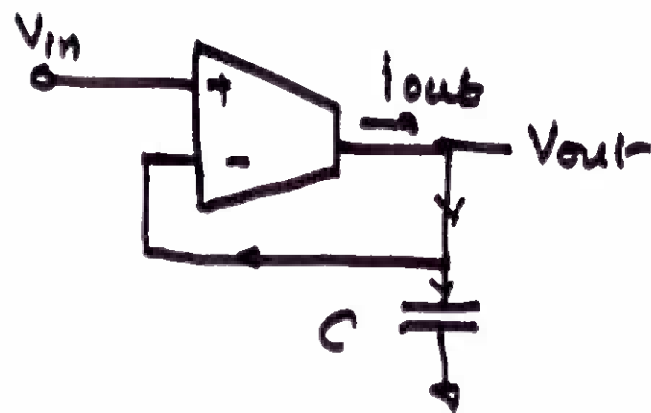
$$\frac{i_{out}}{V_{in}} = G_m = g_m \quad \text{if } K=1$$



This is Low Pass Filter.


However $i_{out} = g_m (V_{in} - V_{out})$ For OTA

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{1 + Cs \frac{1}{g_m}}$$


$$\text{Pole} = \omega_0 = \frac{1}{C/g_m} = \frac{g_m}{C}$$

Slide No: 16

Universal Filter

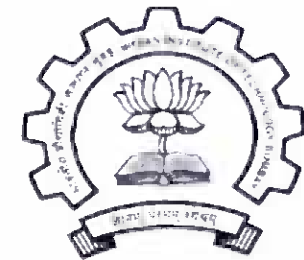

CDEEP
IIT Bombay

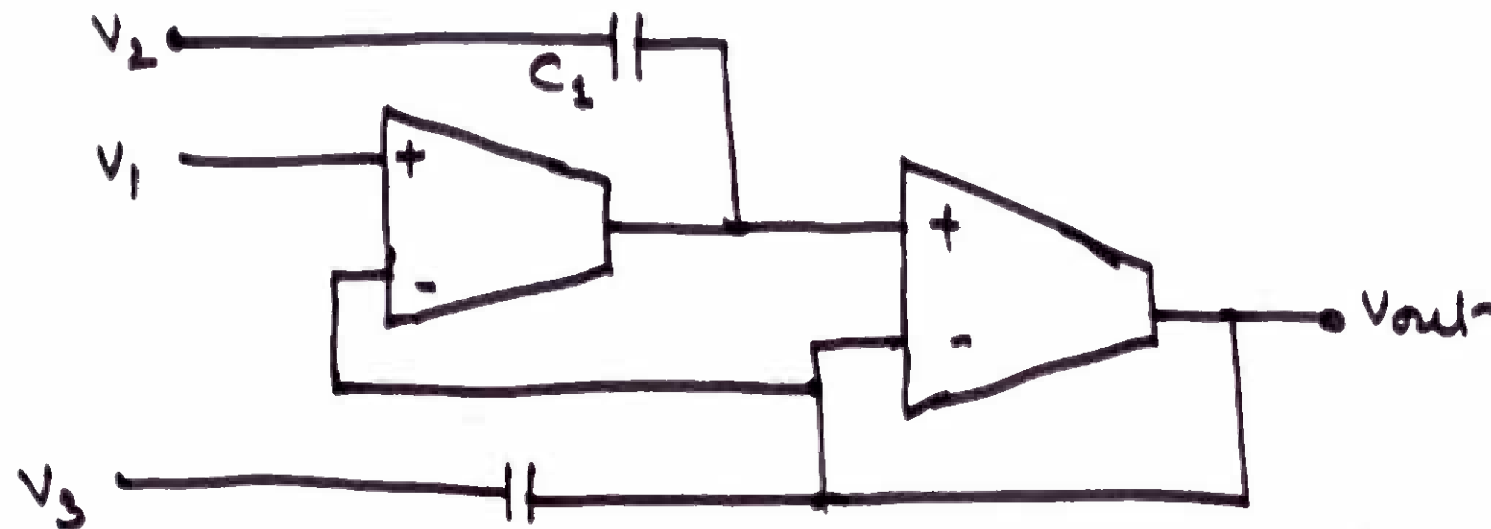

Filter

Input Conditions

Transfer FN

LP

$$V_{in} = V_1, V_2 = 0, V_3 = 0$$

$$g_m^2 / [s^2 C_1 C_2 + s C_1 g_m + g_m^2]$$

HP

$$V_{in} = V_3, V_1 = V_2 = 0$$

$$s^2 C_1 C_2 / [s^2 C_1 C_2 + s C_1 g_m + g_m^2]$$

BP

$$V_{in} = V_2, V_1 = V_3 = 0$$

$$s C_1 g_m / [s^2 C_1 C_2 + s C_1 g_m + g_m^2]$$

BR

$$V_{in} = V_1 = V_3, V_2 = 0$$

$$(s^2 C_1 C_2 + g_m^2) / [s^2 C_1 C_2 + s C_1 g_m + g_m^2]$$

Course Name

Analog Circuits

Lecture No. 21

Instructor's Name

Prof. A. N. Chandorkar