
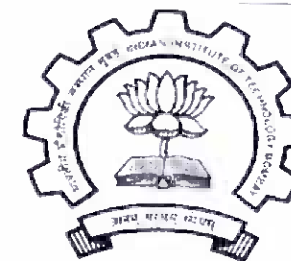


Sinusoidal Oscillators

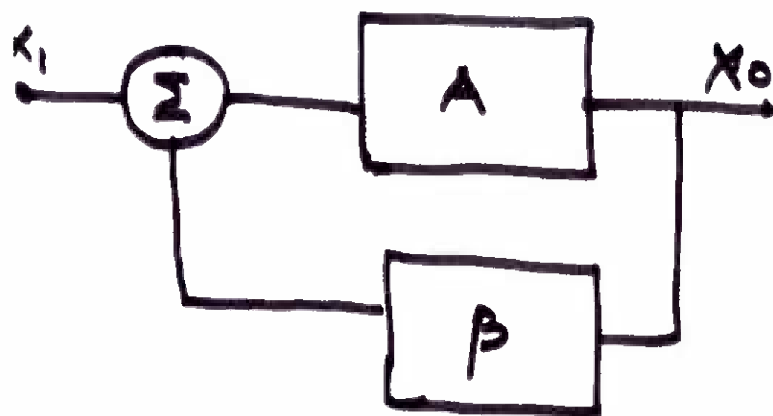

CDEEP
IIT Bombay



$$H(s) = \frac{x_o}{x_i}$$

$$= \frac{A(s)}{1 + A(s)\beta(s)}$$

$$T(s) = L(s) = A(s)\beta(s) \quad \text{Loop Gain}$$

Hence if $1 + A\beta = 0$, then $H(s) \rightarrow \infty$

or Loop Gain = -1, we have $H(s) \rightarrow \infty$

This condition will lead to Oscillation.

The Barkhausen Criterion

For Sinusoidal Oscillations will be possible
when $T(s) = -1$

$$\therefore |T(2\pi j f_1)| = 1 \quad \text{and} \quad \angle T(2\pi j f_1) = -180^\circ \quad \text{--- (A)}$$

At Oscillator Frequency f_1

$$\Rightarrow |T(2\pi j f_1)| = \text{Magnitude} \quad \& \quad \angle T(2\pi j f_1) = \text{Phase}$$

OR Real Part of $T(2\pi j f_1) = -1$

& Imaginary Part of $T(2\pi j f_1) = 0$ --- (B)



CDEEP
IIT Bombay


Slide No: 3

That is to say for Oscillations
Conditions be —

ci) Phase Shift through Amplifier and
Feedback Network must become 360°
(In Phase of Input)

cii) And $|A\beta| = 1$



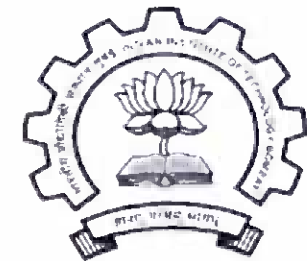
These conditions are called Barkhausen Criterion.



CDEEP
IIT Bombay

Slide No: 4

Phase - Shift Oscillator

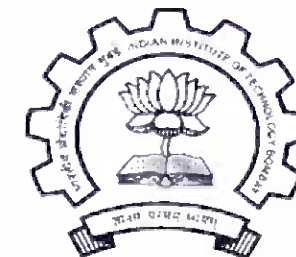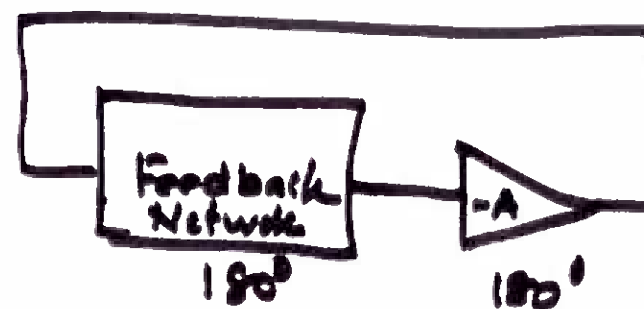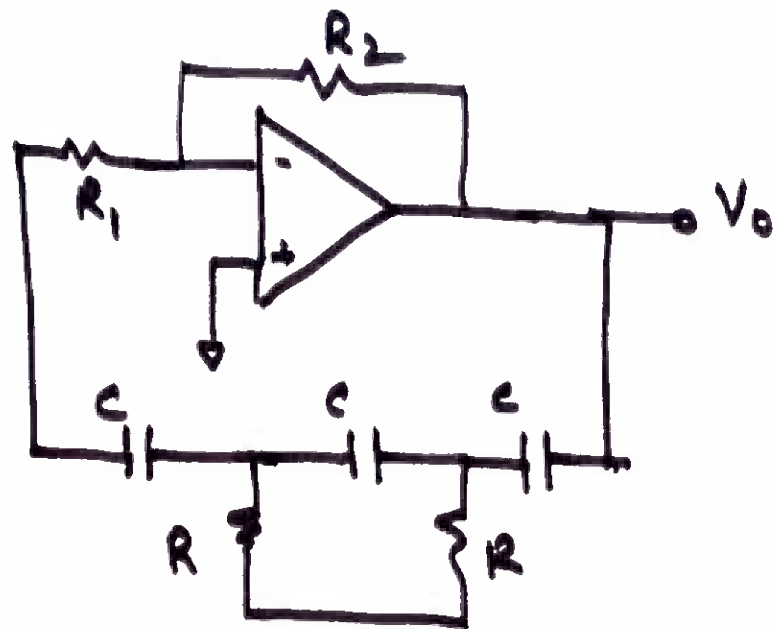

CDEEP
IIT Bombay

Course Name
Analog Circuits

Lecture No. 23


Instructor's Name
Prof. A. N. Chandorkar

Slide No: 5


MOSFET Phase Shift Oscillator



CDEEP
IIT Bombay

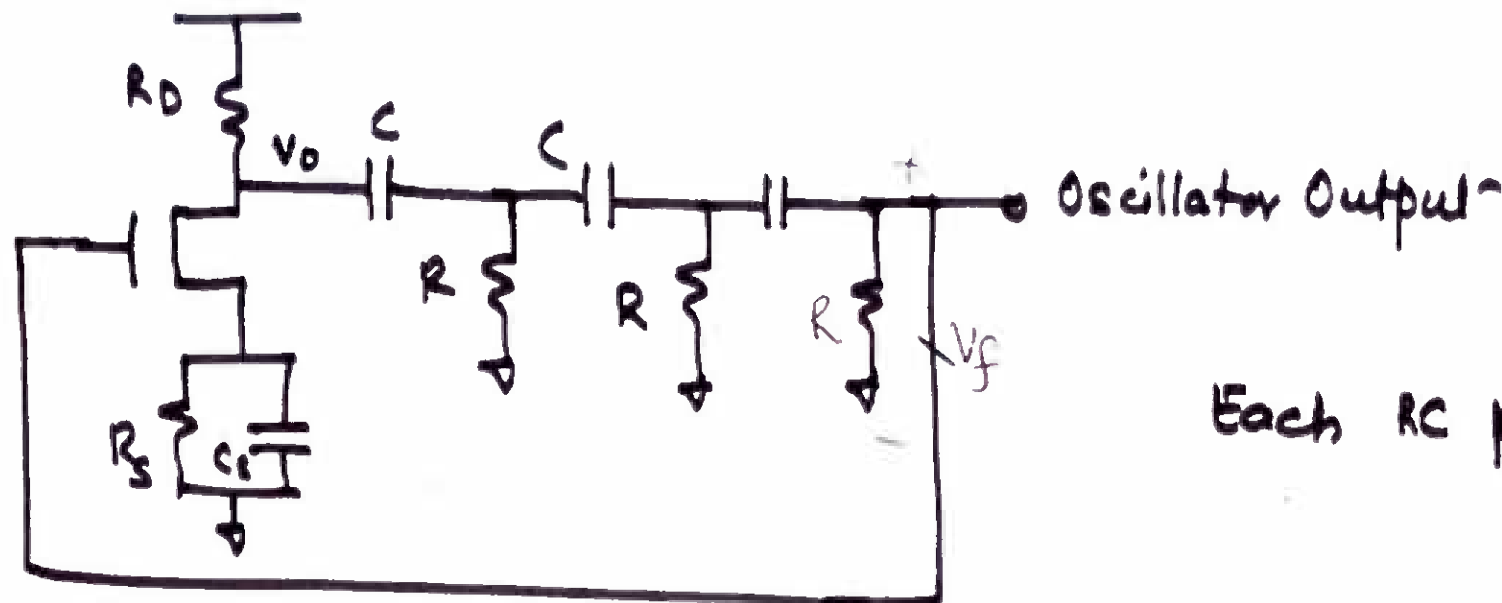


Each RC provides 60° Phase shift

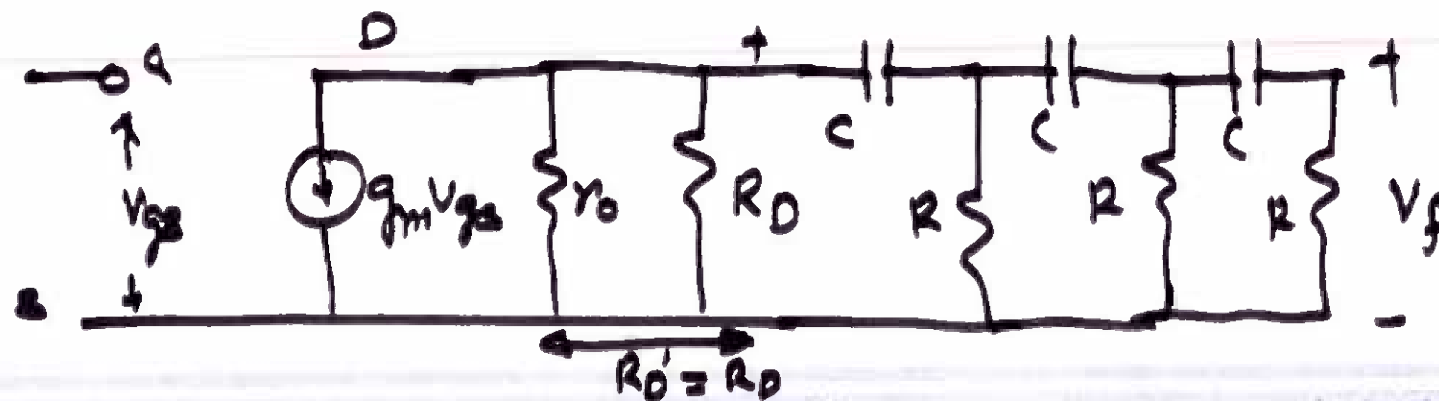

Slide No. 6



CDEEP
IIT Bombay

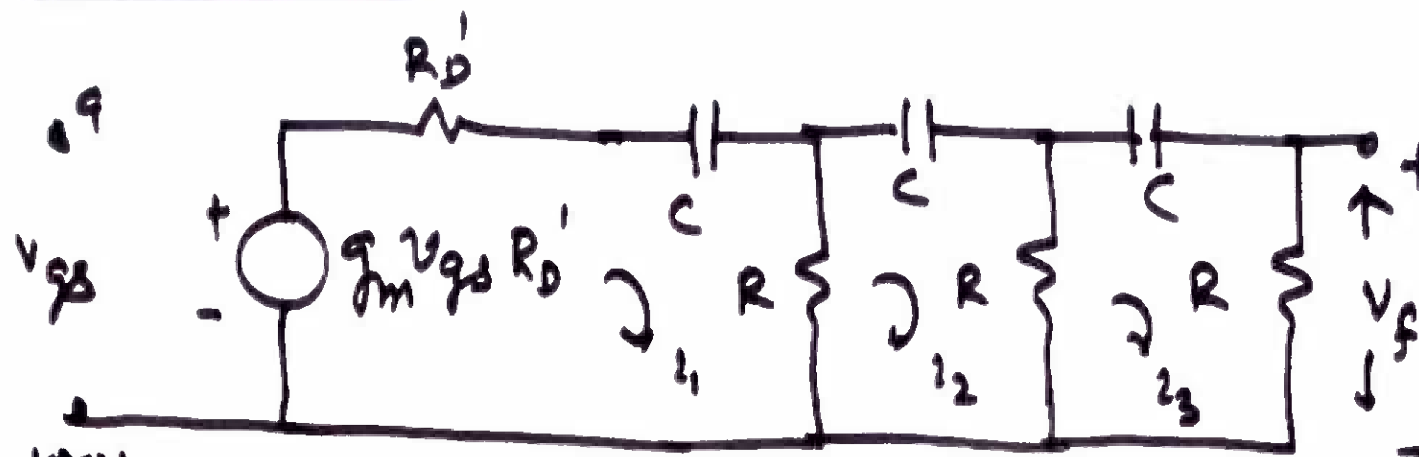

KVL :

$$i_1 \left(R_D' + \frac{1}{C s} \right) - i_2 R = -g_m R_D' v_{gs} \quad \text{--- (i)}$$

$$-i_1 R + i_2 \left(R + R + \frac{1}{C s} \right) - i_3 R = 0 \quad \text{--- (ii)}$$

$$-i_2 R + i_3 \left(2R + \frac{1}{C s} \right) = 0 \quad \text{--- (iii)}$$

Course Name

Analog Circuits

Lecture No. 23

Instructor's Name

Prof. A. N. Chandorkar

Slide No. 7

Feedback Voltage $V_f = i_3 R$ — (iv)

$$\begin{aligned} \therefore \text{Loop Gain } T(s) &= A_{OL} \beta = \frac{V_o}{V_{gs}} \frac{V_f}{V_o} \\ &= + \frac{V_f}{V_{gs}} = \frac{-g_m R_D'}{(1 - s/\omega^2 R^2 C^2) + j[(\frac{1}{\omega R C})^3 - 6(\frac{1}{\omega R C})]} \end{aligned}$$


For Loop Gain to be Real Quantity

$$(\frac{1}{\omega R C})^3 - \frac{6}{\omega R C} = 0 \quad \text{or} \quad \omega^2 R^2 C^2 = \frac{1}{6} \quad \text{or} \quad \omega^2 = \frac{1}{6 R^2 C^2}$$

$$\therefore \omega_0 = \frac{1}{\sqrt{6} R C}$$

$$\therefore |T(2\pi j \omega_0)| = - \frac{g_m R_D'}{-29} = \frac{g_m R_D'}{29}$$

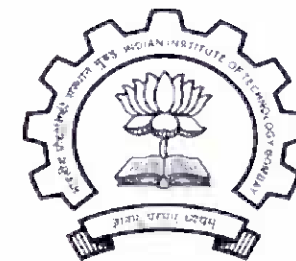
Hence for Sustained Oscillation $g_m R_D' = \text{Gain} \geq 29$




CDEEP
IIT Bombay

Slide No: 8

Wien Bridge Oscillator

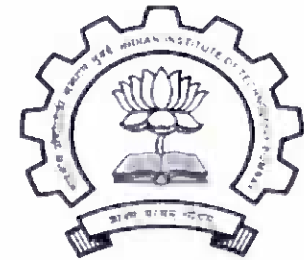

CDEEP
IIT Bombay

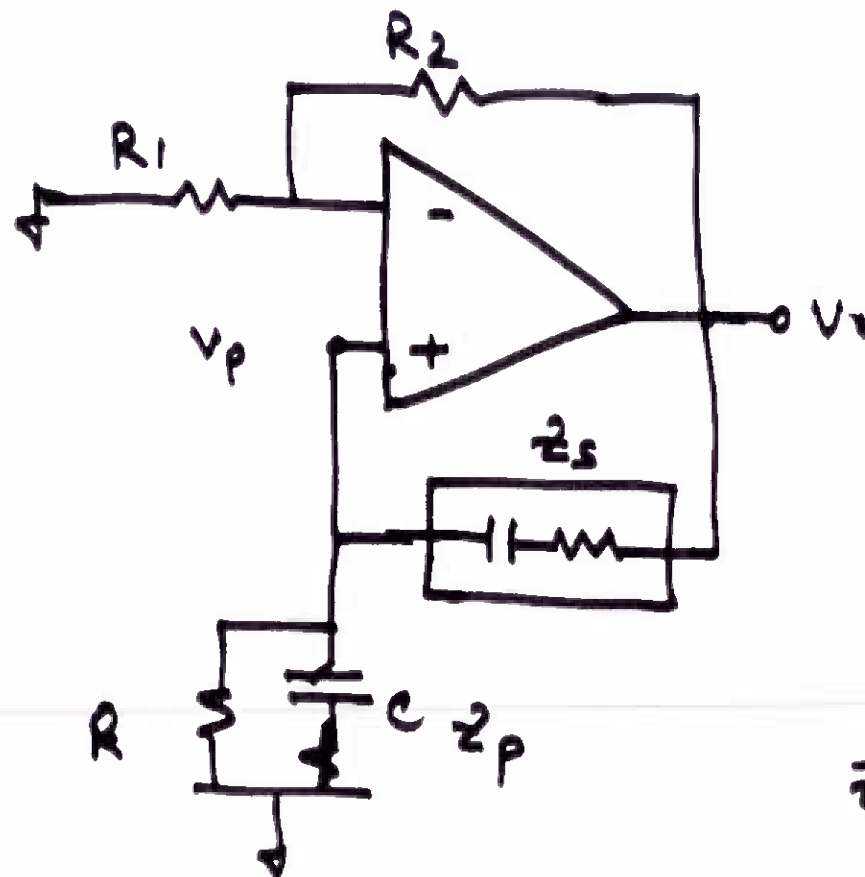


$$A_{OL} = \left(1 + \frac{R_2}{R_1} \right)$$

$$\beta = \frac{Z_p}{Z_p + Z_s}$$

$$Z_p = \frac{R}{1 + RCs}, \quad Z_s = \frac{1 + RCs}{sC}$$

Slide No: 9

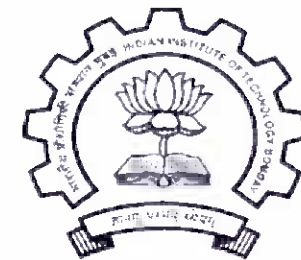

CDEEP
IIT Bombay

$$\therefore T(s) = \left(1 + \frac{R_2}{R_1}\right) \left[\frac{(R/1 + RCs)}{\left(\frac{R}{1+RCs}\right) + \frac{1+RCs}{sC}} \right]$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left[\frac{RCs}{RCs + (1+RCs)^2} \right]$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left[\frac{RCs}{RCs + 1 + 2RCs + R^2C^2s^2} \right]$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left[\frac{1}{\left(3 + RCs + \frac{1}{RCs}\right)} \right]$$

At Oscillation frequency ω_0

$$T(j\omega_0) = -1 \quad \text{and hence } \underline{\text{Real}}$$

$$\therefore j\omega_0 RC + \frac{1}{j\omega_0 RC} = 0$$

$$\text{or } \omega_0^2 R^2 C^2 = 1 \quad \therefore \omega_0 = \frac{1}{RC} \quad \text{or } f_0 = \frac{1}{2\pi RC}$$


$$\hookrightarrow |T(j\omega_0)| = 1$$

$$= \left(1 + \frac{R_2}{R_1}\right) \frac{1}{3}$$

$$\text{or } \boxed{\frac{R_2}{R_1} = 2}$$

for Sustained Oscillations
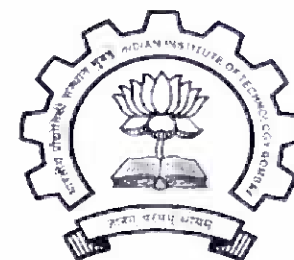
$$\text{To Start Oscillations } \frac{R_2}{R_1} \geq 2$$



CDEEP
IIT Bombay

LC Oscillators

(i) High Q - (than RC Oscillators)

$$\left(\frac{\omega L}{R}\right) \approx \left(\frac{1}{\omega RC}\right)$$


(ii) Higher Frequency possible

(iii) Tunable range smaller.

Two Famous LC Oscillators are

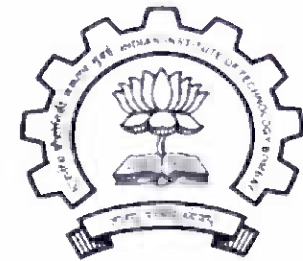(1) Colpitts Oscillator (2) Hartley Oscillator


Major Oscillator in Many Electronic Systems is
"CRYSTAL OSCILLATOR".




CDEEP
IIT Bombay

Slide No: 12


BJT based Oscillators are

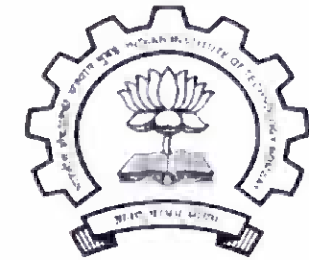

CDEEP
IIT Bombay

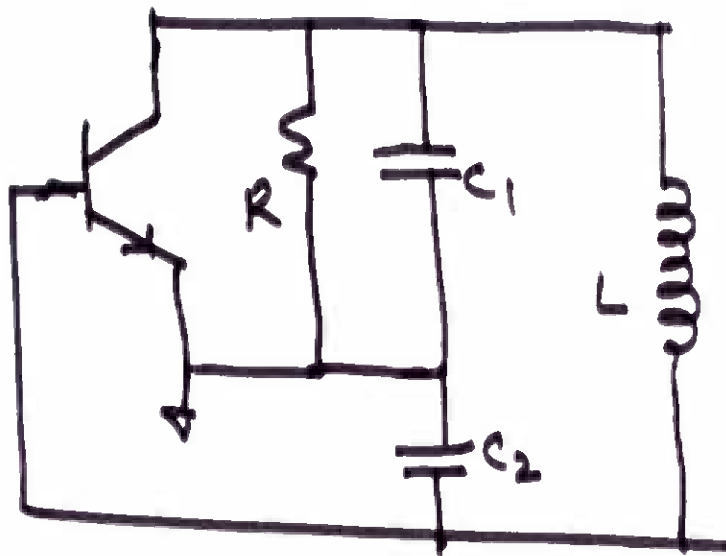


Colpitts Oscillator

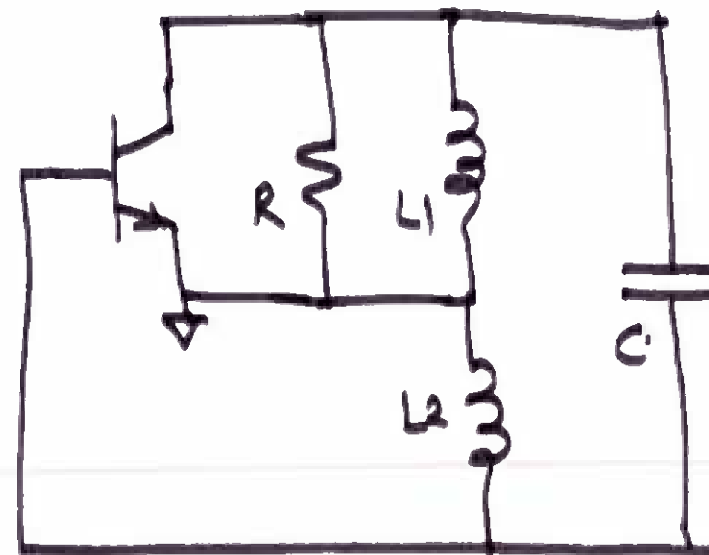



Hartley Oscillator

Slide No: 13

Colpitts Oscillator (LC Oscillator)

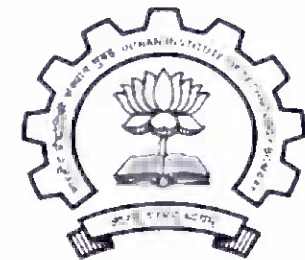

CDEEP
IIT Bombay

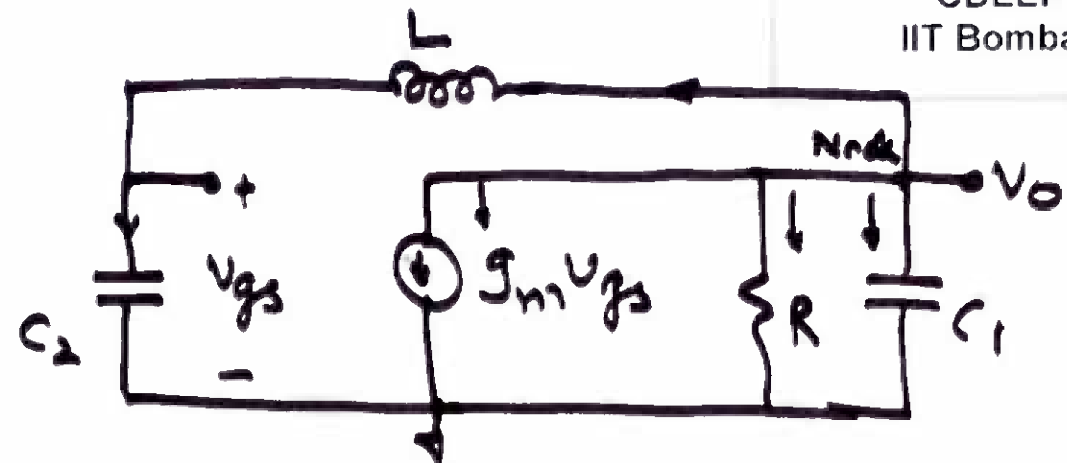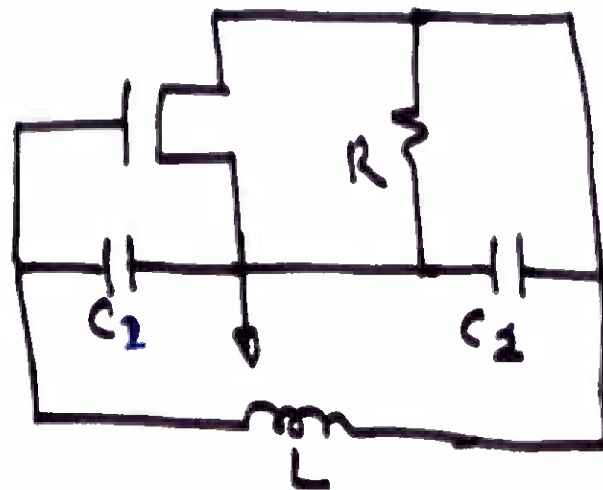

At Node V_o

$$\frac{V_o}{1/sC_1} + \frac{V_o}{R} + g_m v_{gs} + \frac{V_o}{Ls + \frac{1}{sC_2}} = 0 \quad \text{--- (1)}$$

$$\& \quad v_{gs} = \frac{1/sC_2}{Ls + \frac{1}{sC_2}} \cdot V_o = \frac{V_o}{LC_2 s^2 + 1} \quad \text{--- (2)}$$

Slide No: 14

substituting (ii) in (i)

$$V_0 \left[g_m + sC_2 + (1 + LC_2s^2) \left(\frac{1}{R} + sC_1 \right) \right] = 0$$


If oscillations has started then V_0 is finite

$$\therefore g_m + sC_2 + \frac{1}{R} + \frac{LC_2}{R} s^2 + sC_1 + LC_1C_2s^3 = 0$$

$$\text{or } \left(g_m + \frac{1}{R} - \frac{\omega^2 LC_2}{R} \right) + j\omega \left[(C_1 + C_2) - \omega^2 LC_1C_2 \right] = 0$$

at ω_0

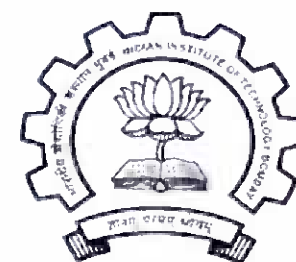For oscillations to sustain both 'Real' & 'Imaginary' parts be zero. Hence $\frac{\omega_0^2 LC_2}{R} = g_m + \frac{1}{R}$ or $\boxed{\omega_0^2 LC_2 = 1 + g_m R}$



CDEEP
IIT Bombay

Slide No: 15

* Imaginary part = 0


$$(C_1 + C_2) - \omega_0^2 L C_1 C_2 = 0$$

$$\therefore \omega_0^2 = \frac{C_1 + C_2}{L C_1 C_2}$$

$$\therefore \omega_0 = \frac{1}{\sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}}$$

Substituting ω_0 in Real part
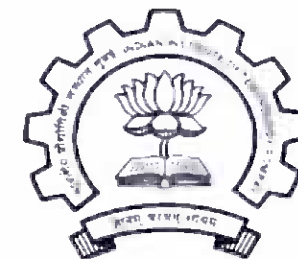
$$\therefore \frac{(C_1 + C_2)}{L C_1 C_2} L C_2 = 1 + g_m R \quad \therefore 1 + \frac{C_2}{C_1} = 1 + g_m R$$
$$\therefore \boxed{\frac{C_2}{C_1} = g_m R}$$



CDEEP
IIT Bombay

Hartley Oscillator

$$\omega_0 = \frac{1}{\sqrt{(L_1 + L_2)C}}$$

Crystal Oscillator

Quartz crystal exhibits Electro-mechanical Resonance.
It's natural frequency is stable with

(i) Temperature (ii) Time

The frequency depends upon 'size' (Mass) of the Crystal.
Most important Quality of this is that it has v. large 'Q'.





CDEEP
IIT Bombay


Slide No: 18




CDEEP
IIT Bombay

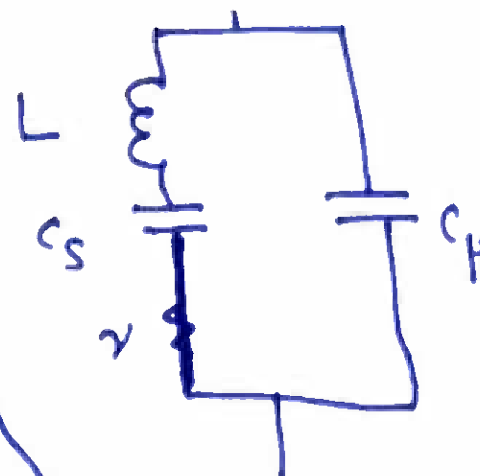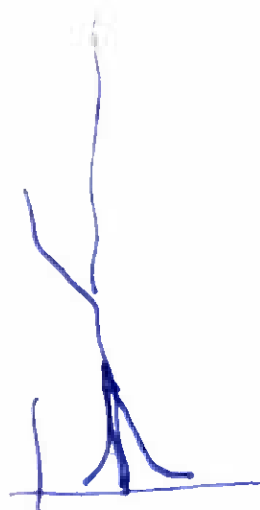

$$Q > 10^4$$

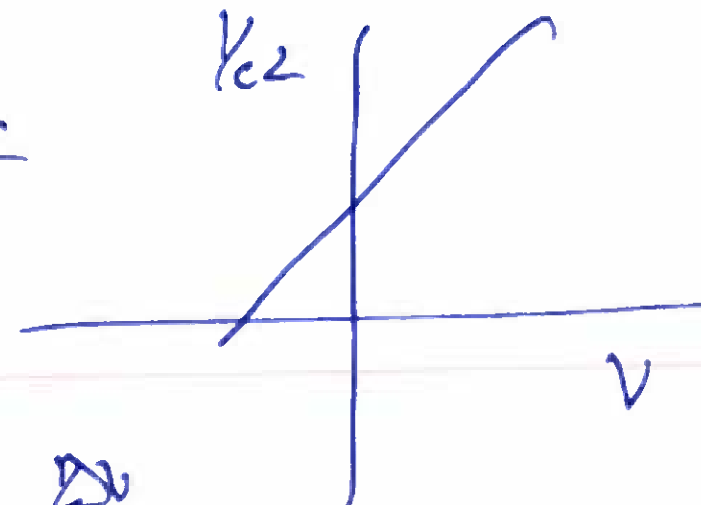
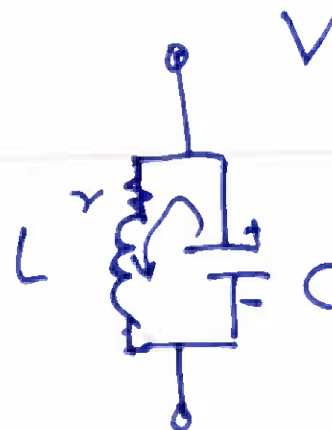
$$Q = \frac{1}{\sqrt{LC}} = \frac{\omega L}{R}$$



$$\frac{1}{2} C V^2$$

Slide No: 19

If 'r' is neglected (High $Q \approx 10^4$),
Impedance of the Circuit is

$$Z(s) = \frac{1}{[sC_p + \frac{1}{Ls + \frac{1}{C_s s}}]}$$
$$= \frac{1}{sC_p} \cdot \frac{s^2 + (1/LC_s)}{s^2 + [(C_p + C_s)/(LC_s C_p)]}$$

Series Resonance Occures at

$$\omega_s = \frac{1}{\sqrt{LC_s}}$$

Parallel resonance Occures

at

$$\omega_p = \frac{1}{\sqrt{L \left(\frac{C_s C_p}{C_s + C_p} \right)}}$$

$\omega_s \approx \omega_p$ if $C_p \gg C_s$




CDEEP
IIT Bombay

Slide No: 20

Crystal behaves as Inductor

for frequencies between ω_s & ω_p (Narrow Band)

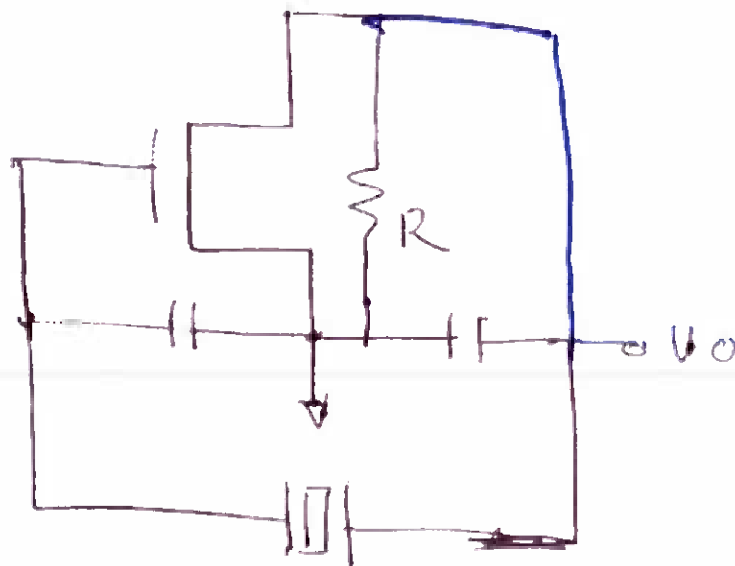We use this Inductor in Colpitts Oscillator for fixed Frequency Oscillator which is Stable



CDEEP
IIT Bombay

Course Name

Analog Circuits


Lecture No. 23

Instructor's Name

Prof. A. N. Chandorkar

Slide No: 21




Ring Oscillator (Sq. Wave Generator)

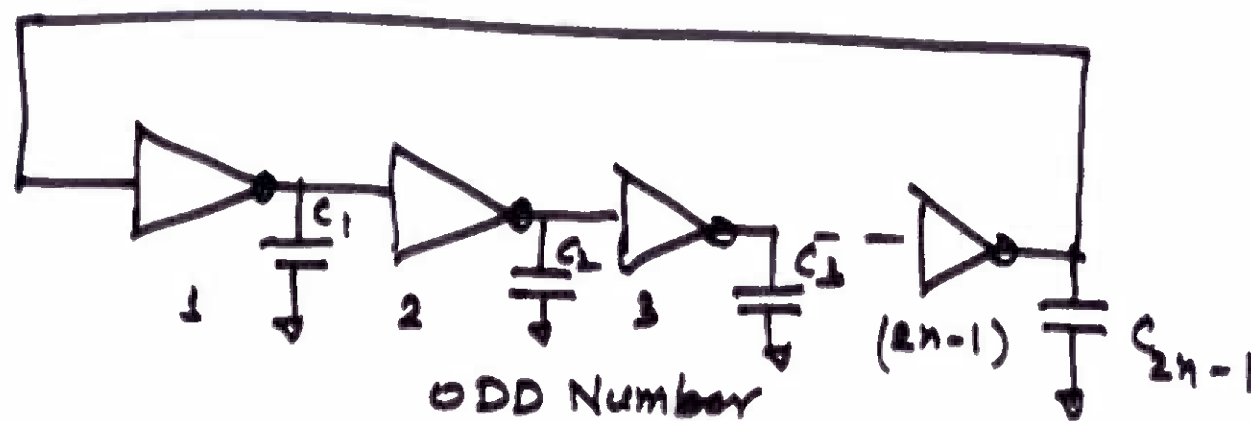


CDEEP
IIT Bombay

We now look into other Non Sinusoidal Oscillators.

Slide No. 22

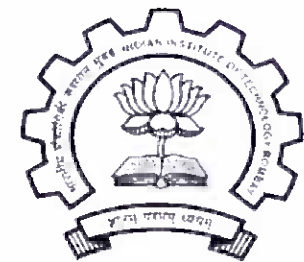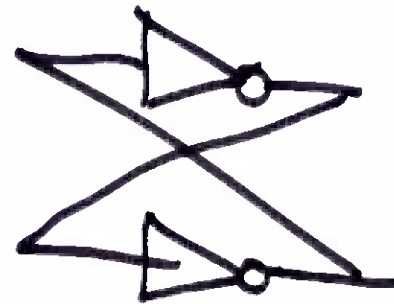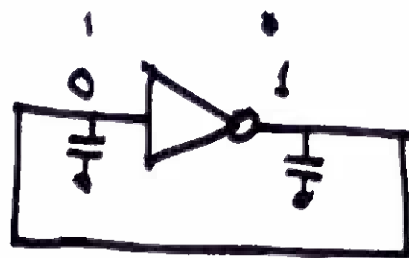

CDEEP
IIT Bombay

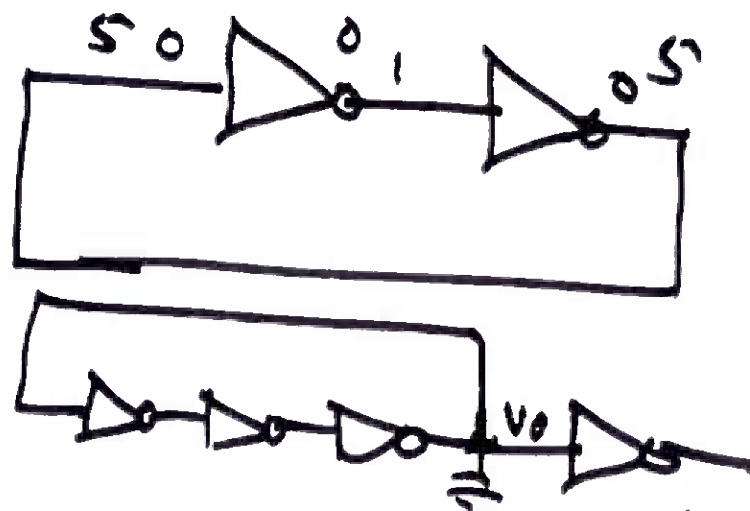

$$T(j\omega_0) = 1$$

$$\omega_0 = 0$$