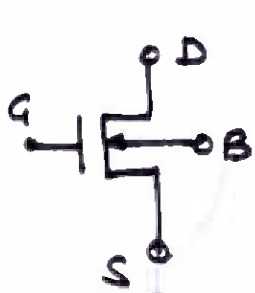


MOSFET as Amplifying Device.




CDEEP
IIT Bombay




NMOS

Enhancement

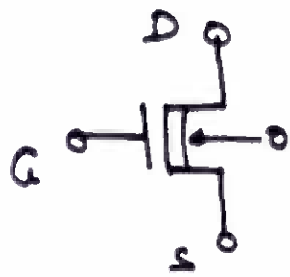


NMOS

Depletion

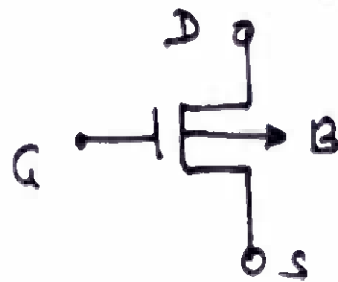


PMOS

Enhancement

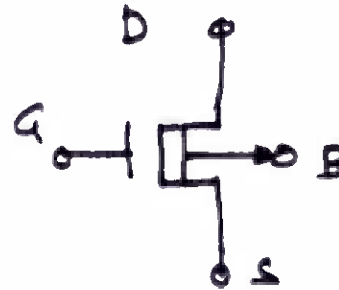


PMOS

Depletion

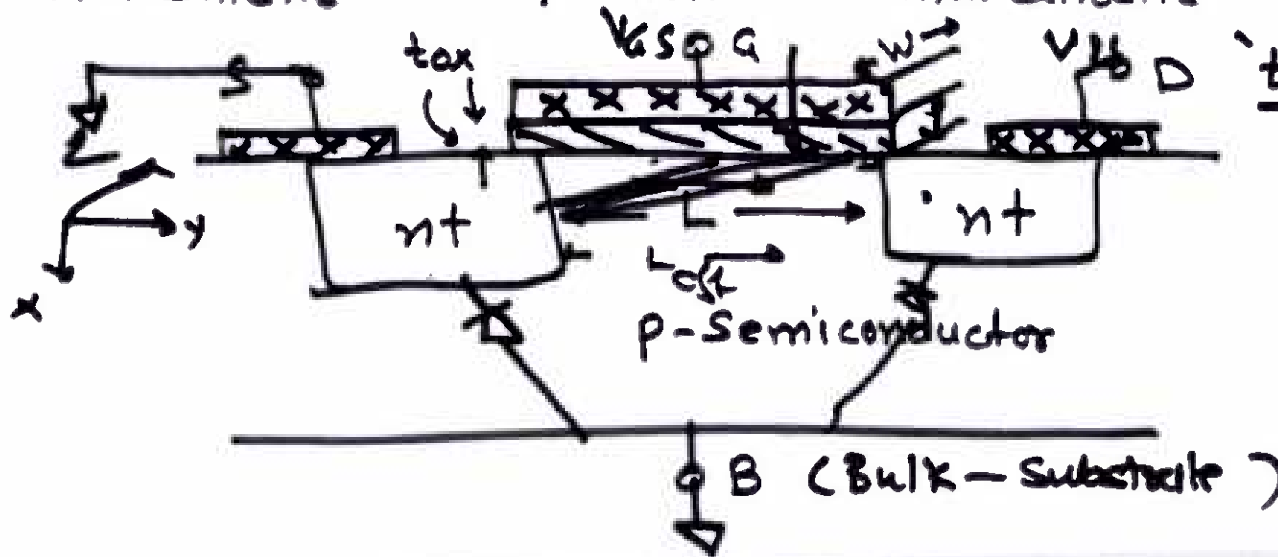

$V_{GS} - V_{DS} > V_T$
 $V_{GS} - V_T > V_{DS}$
 NMOS(EM) Transistor
 Cross-Section

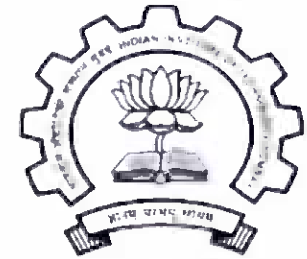Threshold Voltage V_T


$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \phi_{ms} \pm 2\phi_f - \frac{Q_{ox}}{C_{ox}} - \frac{\pm Q_B}{C_{ox}}$$



(EM) P-channel :- V_T is -ve

(DM) P-channel :- V_T is +ve

(EM) N-channel :- V_T is +ve

(DM) N-channel :- V_T is -ve

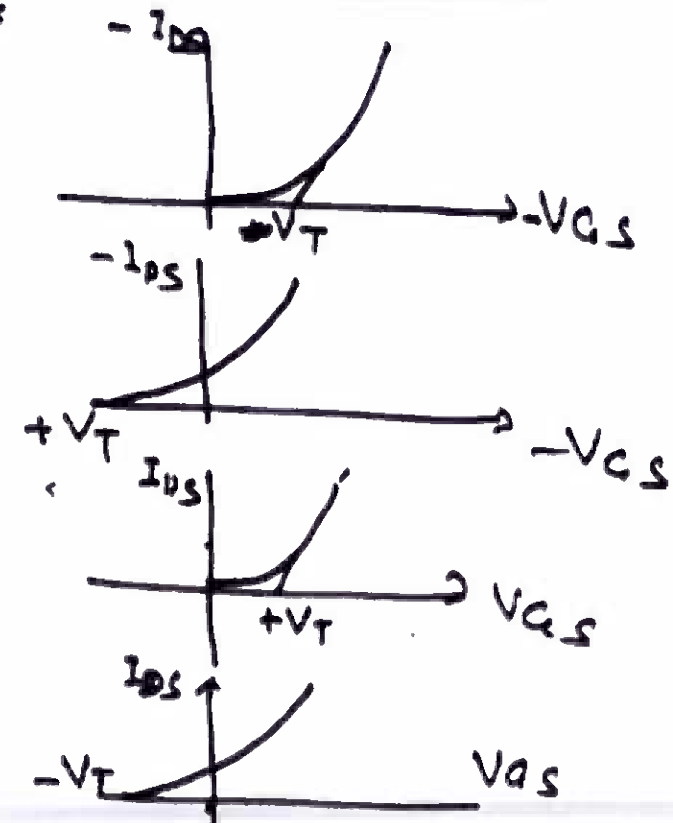

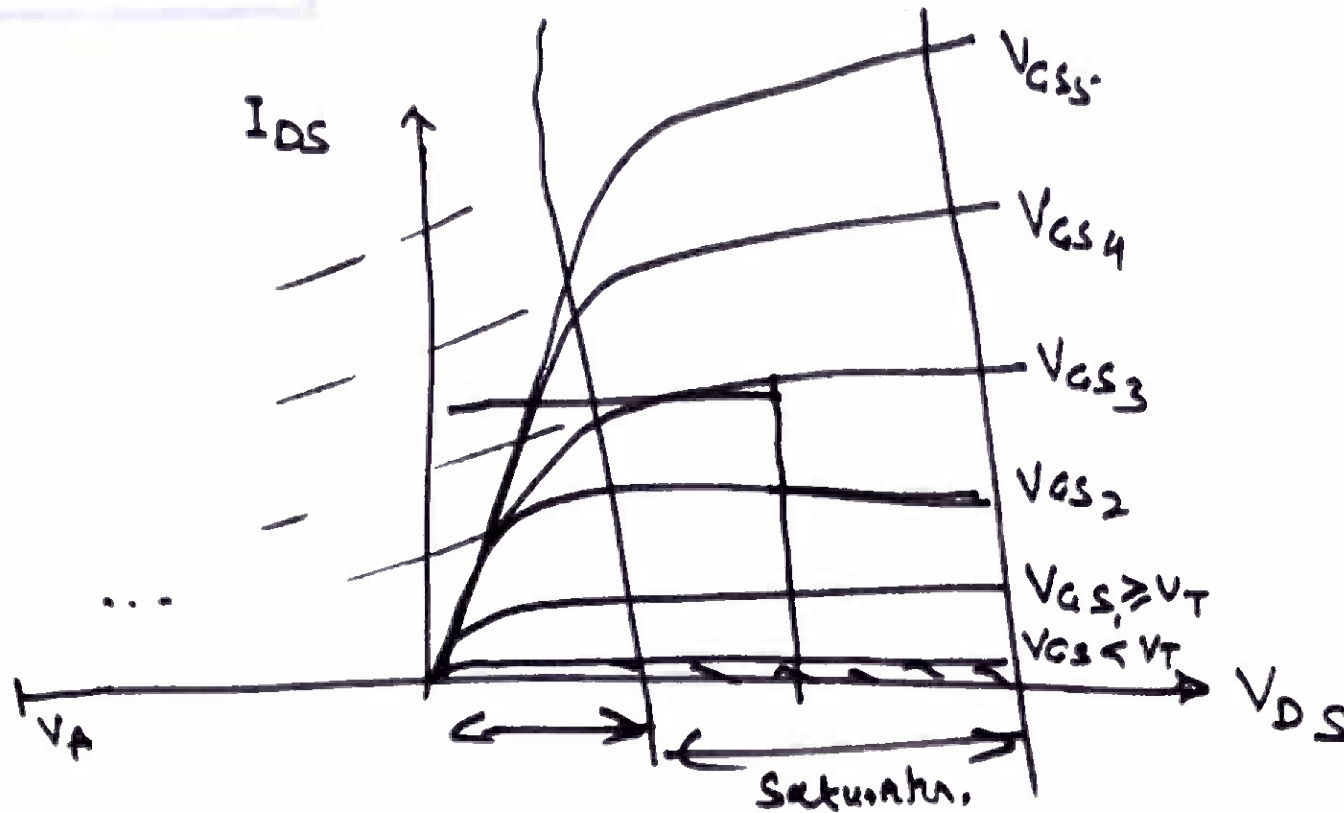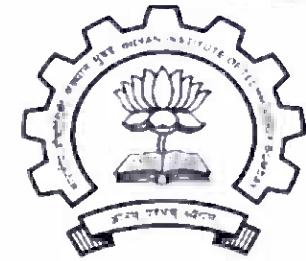

Output characteristics of NMOS (EM)



CDEEP
IIT Bombay

Slide No. 4

MOSFET Operation

$$I_{D_S} = \mu C_{ox} \left(\frac{W}{L} \right) \left[\underline{(V_{GS} - V_T)} V_{DS} - \frac{1}{2} V_{DS}^2 \right] \quad V_{GS} - V_T > V_{DS}$$

$$V_{GS} - V_T = V_{OV} = V_{Exc}$$

Linear Mode

$$I_{D_S} = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \quad V_{GS} - V_T < V_{DS}$$

$$\lambda = \frac{\lambda'}{L}$$

Also


$$\lambda = \frac{1}{V_A}$$

$$g_m r_o$$

$$\mu_n = 600 \text{ cm}^2/\text{V sec}$$

$$\mu_p = 200 \text{ cm}^2/\text{V sec}$$

Slide No. 5

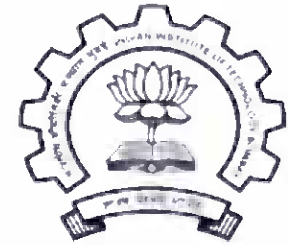

CDEEP
IIT Bombay




Course Name
Analog Circuits



Lecture No. 5

Instructor's Name
Prof. A. N. Chandorkar

Slide No: ✓

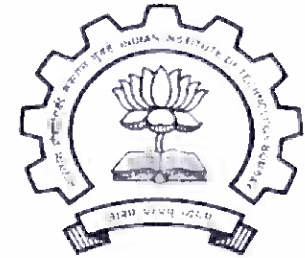

CDEEP
IIT Bombay

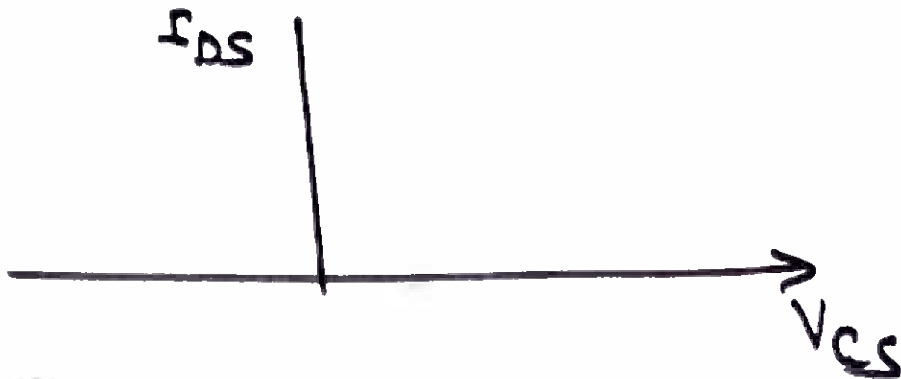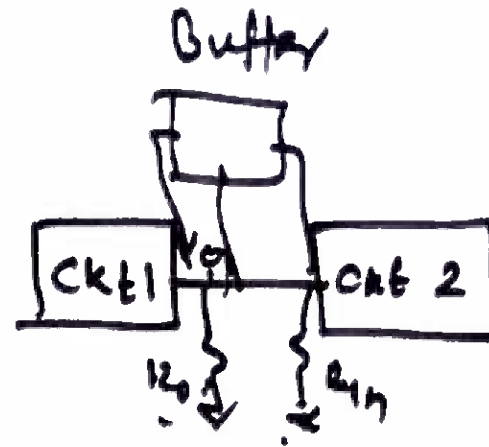

Course Name

Analog Circuits

Lecture No. 5

Instructor's Name

Prof. A. N. Chandorkar


Small Signal Model

(i) g_m (ii) Capacitances

(iii) Output Resistance



CDEEP
IIT Bombay

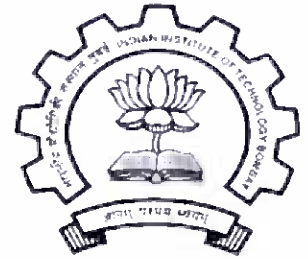

Major Small Signal Parameters for MOSFET

$$\textcircled{1} g_m = \text{Transconductance} = \frac{\partial I_{DS}}{\partial V_{GS}}$$


$$g_{m, \text{linear}} = \frac{\partial}{\partial V_{GS}} \left[\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) \left\{ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right\} \right]$$

As $V_{GS} - V_{DS} > V_{DS}$ $\therefore \frac{1}{2} V_{DS}^2$ can be neglected

$$g_{m, \text{linear}} = \frac{\partial}{\partial V_{GS}} \left[\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) V_{DS} \right]$$

We define $\beta'_n = \frac{\mu_n C_{ox}}{1}$, $\beta_n = \beta'_n \left(\frac{W}{L} \right)$

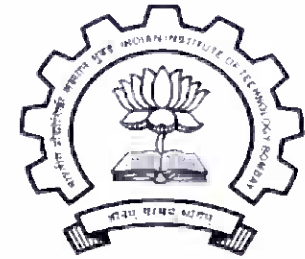Then $g_{m, \text{linear}} = \beta_n V_{DS}$



In Sat. Mode

$$g_m = \frac{\partial I_{Ds}}{\partial V_{Gs}} = \frac{\partial}{\partial V_{Gs}} \left[\frac{\beta_n}{2} (V_{Gs} - V_T)^2 (1 + \lambda V_{Ds}) \right]$$

Assume λ is very small, then $(1 + \lambda V_{Ds}) \rightarrow 1$


$$\therefore g_m = \beta_n' (V_{Gs} - V_T) (W/L)$$

$$g_m = \frac{\beta_n}{2} (V_{Gs} - V_T)^2 \frac{2}{(V_{Gs} - V_T)} = \frac{2 I_{Ds}}{(V_{Gs} - V_T)} = \frac{2 I_{Ds}}{V_{ov}}$$

$$\therefore \boxed{g_m = \frac{2 I_{Ds}}{V_{ov}}}$$

$$\therefore g_m = \sqrt{2 \beta_n I_{Ds}}$$
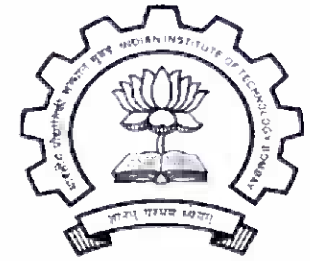
$$\textcircled{2} \text{ Output Resistance } r_o = \frac{1}{\lambda I_{Ds}} = \frac{V_A}{I_{Ds}} = \frac{L}{\lambda' I_{Ds}} \quad \lambda = \frac{\lambda'}{L}$$



Comparison between BJT & MOSFET

In MOS
$$\frac{g_m}{I_{DS}} = \frac{2}{V_{OV}}$$

Typically V_{OV} is of the order of 200 mV or so

$\therefore \frac{g_m}{I_{DS}} \approx \frac{2}{200 \text{ mV}} = \frac{2000}{200} = 10$. For higher V_{OV} , $\frac{g_m}{I_{DS}} < 10$

In BJT
$$\frac{g_m}{I_c} = \frac{q}{kT} = 38 \quad (T = 300^\circ\text{K})$$


clearly
$$\frac{g_m}{I_c} \gg \frac{g_m}{I_{DS}}$$

\therefore BJT is normally better than MOSFET for g_m values.

Limitation of MOSFET Small Signal Model.



CDEEP
IIT Bombay

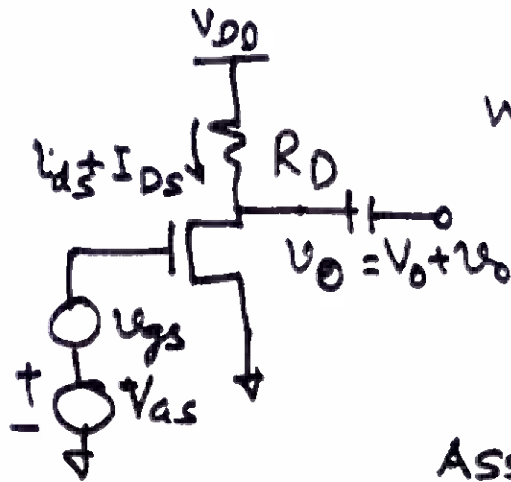

We have $v_{GS} = v_{gs} + V_{GS}$
oc + DC

$$\therefore i_{DS} = \frac{\beta_n}{2} [V_{GS} - V_T + v_{gs}]^2 [1 + \lambda V_{DS}]$$

Assuming λ v. small

We have $i_{ds} = i_{DS} - I_{DS}$

$$\begin{aligned} &= \frac{\beta_n}{2} [(V_{GS} - V_T) + v_{gs}]^2 - \frac{\beta_n}{2} [(V_{GS} - V_T)^2] \\ &= \frac{\beta_n}{2} [(V_{GS} - V_T)^2 + v_{gs}^2 + 2(V_{GS} - V_T)v_{gs}] - \frac{\beta_n}{2} [(V_{GS} - V_T)^2] \\ &= 2 \frac{\beta_n}{2} (V_{GS} - V_T) v_{gs} \left[1 + \frac{v_{gs}}{2(V_{GS} - V_T)} \right] \end{aligned}$$



CDEEP
IIT Bombay


Slide No. 12

$$\therefore i_{ds} = g_m v_{gs} \left[1 + \frac{v_{gs}}{2(V_{GS} - V_T)} \right]$$


If $v_{gs} \ll [2(V_{GS} - V_T)] \Rightarrow$ Small Signal

Then $i_{ds} = g_m v_{gs}$

Equivalent Model :

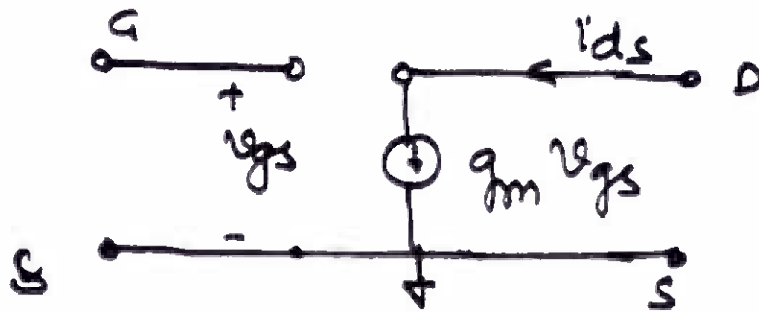

Equivalent Model with r_o

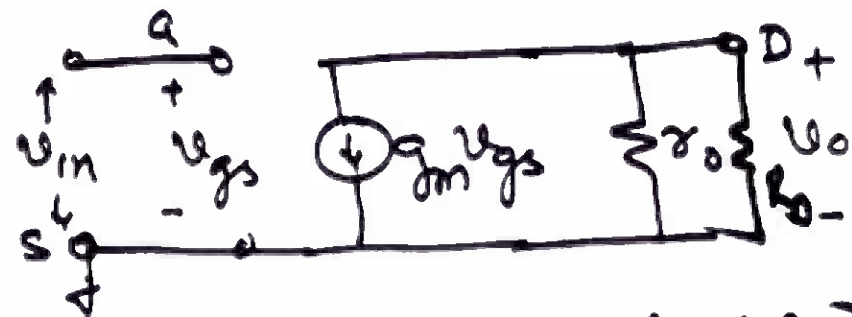

$$v_o = -g_m v_{gs} (r_o || R_D)$$

Slide No. 13


We see $v_{in} = v_{gs}$

$$\text{and } v_o = -g_m v_{gs} \cdot r_o = -g_m r_o v_{in}$$

$$\therefore \boxed{\frac{v_o}{v_{in}} = A_v = -g_m r_o}$$

$$g_m = \frac{2 I_{D_S}}{V_{OV}}, \quad r_o = \frac{1}{\lambda I_{D_S}}$$
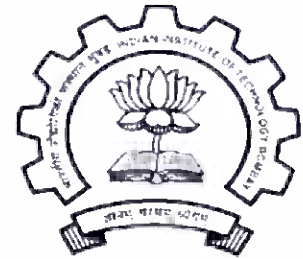
$$\therefore g_m r_o = \frac{2 I_{D_S}}{V_{OV}} \cdot \frac{1}{\lambda I_{D_S}} = \frac{2}{\lambda V_{OV}} = \frac{2}{\lambda (V_{GS} - V_T)}$$



CDEEP
IIT Bombay

Course Name

Analog Circuits

Lecture No. 5


Instructor's Name

Prof. A. N. Chandorkar


$$\omega_T = \frac{g_m}{C_{in}} \quad \text{or} \quad f_T = \frac{g_m}{2\pi C_{in}}$$

When Device is in Saturation we

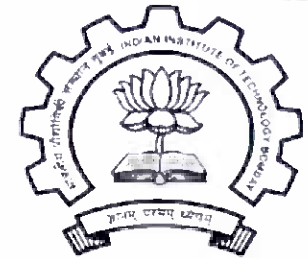
can say $C_{in} = C_{gs} + C_{gd} + C_{gb}$, but- $C_{gd} = C_{gb} = 0$
 $= C_{gs} = C_{ox} \cdot W \cdot L$



Capacitances in a MOSFET

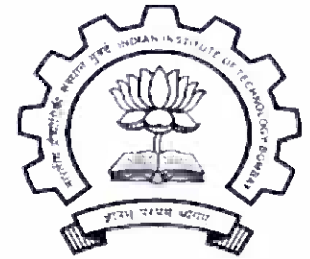

CDEEP
IIT Bombay

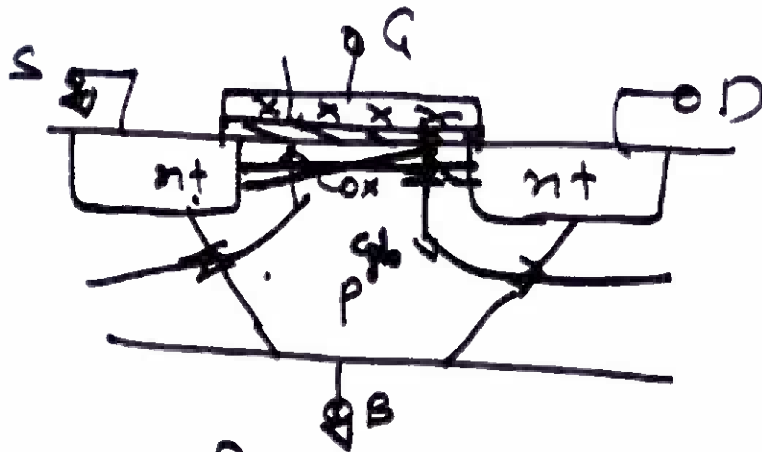

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$


In Saturation


$$\begin{cases} C_{gs} \approx \frac{1}{2} C_{ox} A_g \quad (\frac{2}{3} C_{ox}) \\ C_{gd} = \frac{1}{2} C_{ox} \cdot A_g \end{cases}$$

$$C_{sb} = \frac{C_{sbo}}{\left(1 + \frac{V_{SB}}{\phi_{sb}}\right)^{1/2}}$$

$$\begin{aligned} C_{in} &= C_{gs} + C_{gd} \\ &\approx C_{ox} \cdot A_g \\ &= C_{ox} W \cdot L \end{aligned}$$
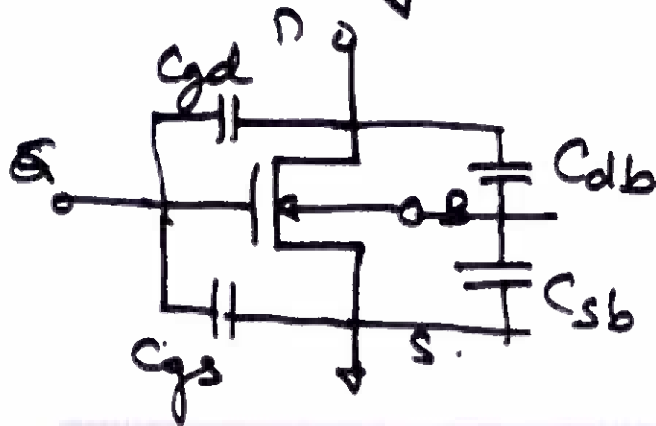
$$C_{db} = \frac{C_{dbo}}{\left(1 + \frac{V_{DB}}{\phi_{db}}\right)^{1/2}}$$



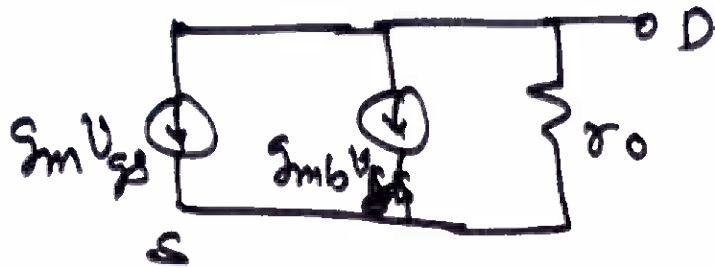Substrate Bias Effect on g_m 

Let V_{bs} be -ve bias on substrate ($V_s = 0$)

$$\text{Then } V_T = V_{T0} + \gamma \left[(2\phi_F + V_{SB})^{1/2} - (2\phi_F)^{1/2} \right]$$

$$\text{Since } I_{DS} = \frac{\beta}{2} \left[V_{GS} - V_{T0} - \gamma \left\{ (2\phi_F + V_{SB})^{1/2} - (2\phi_F)^{1/2} \right\} \right]^2$$

$$\frac{\partial I_{DS}}{\partial V_{SB}} = \text{is finite} = g_{mb}$$

$$\text{Evaluating } g_{mb} = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}} \cdot g_m = g_m \eta$$


$$\text{Typically } \eta = 0.6$$



CDEEP
IIT Bombay

Slide No: 17

Small Signal Model of MOSFET

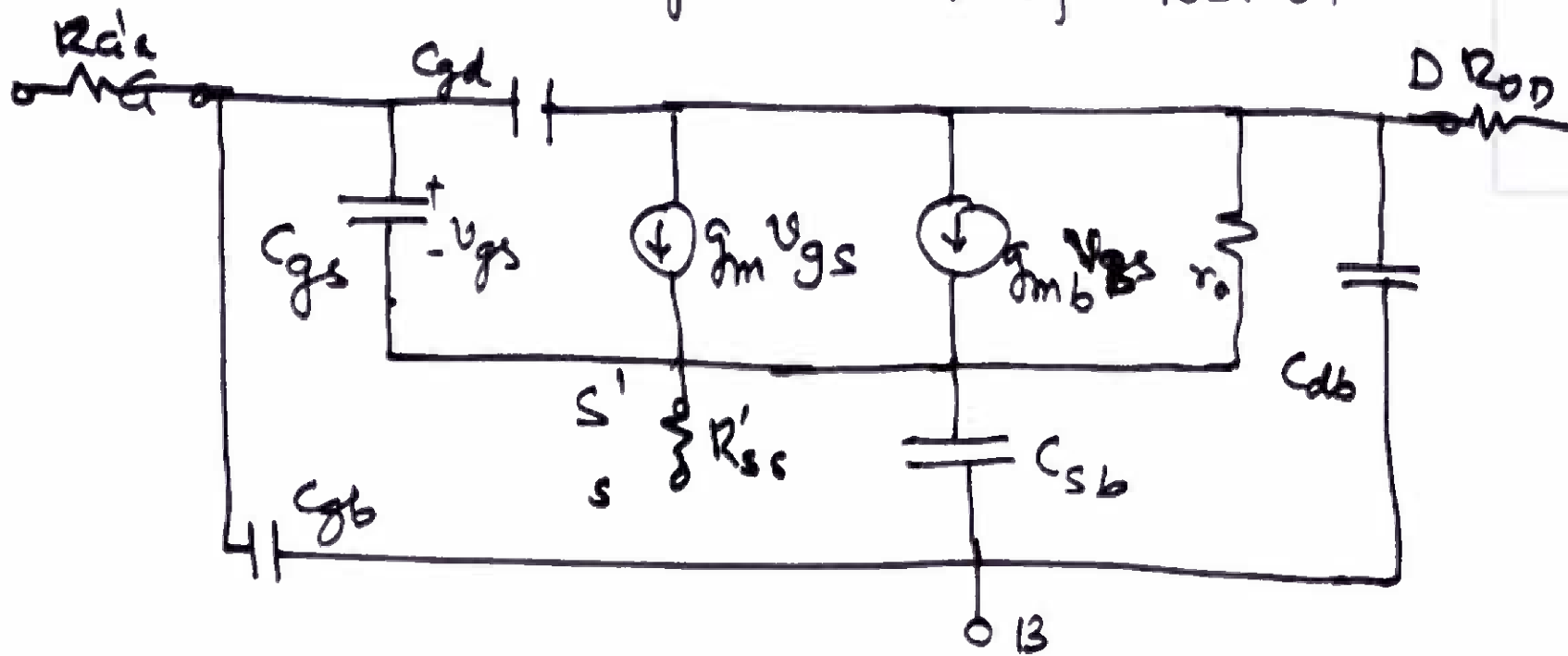



CDEEP
IIT Bombay

Course Name
Analog Circuits

Lecture No. 5

Instructor's Name
Prof. A. N. Chandorkar

Typical Common Source Amplifier

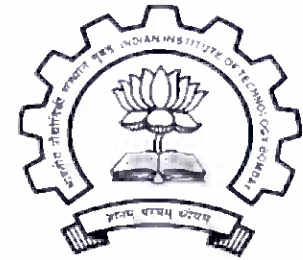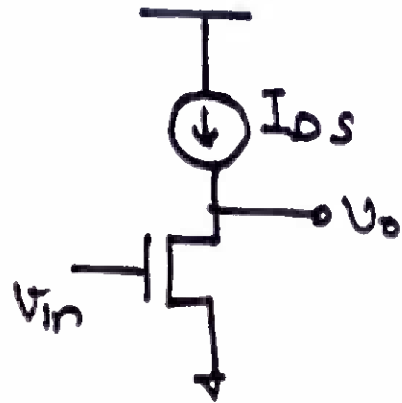CDEEP
IIT BombayCurrent Source
Biasing

From Two port eq. ckt

$$\Delta I_{D_s} = g_m v_{in} + g_o v_o$$



$$\therefore g_m = \left. \frac{\Delta I_{D_s}}{v_{in}} \right|_{v_o=0} \quad \& \quad g_o = \left. \frac{\Delta I_{D_s}}{v_o} \right|_{v_{in}=0}$$

Since I_{D_s} is Fixed $\Delta I_{D_s} = 0$

$$\therefore 0 = g_m v_{in} + g_o v_o \quad \text{or} \quad \frac{v_o}{v_{in}} = - \frac{g_m}{g_o} = -g_m r_o$$