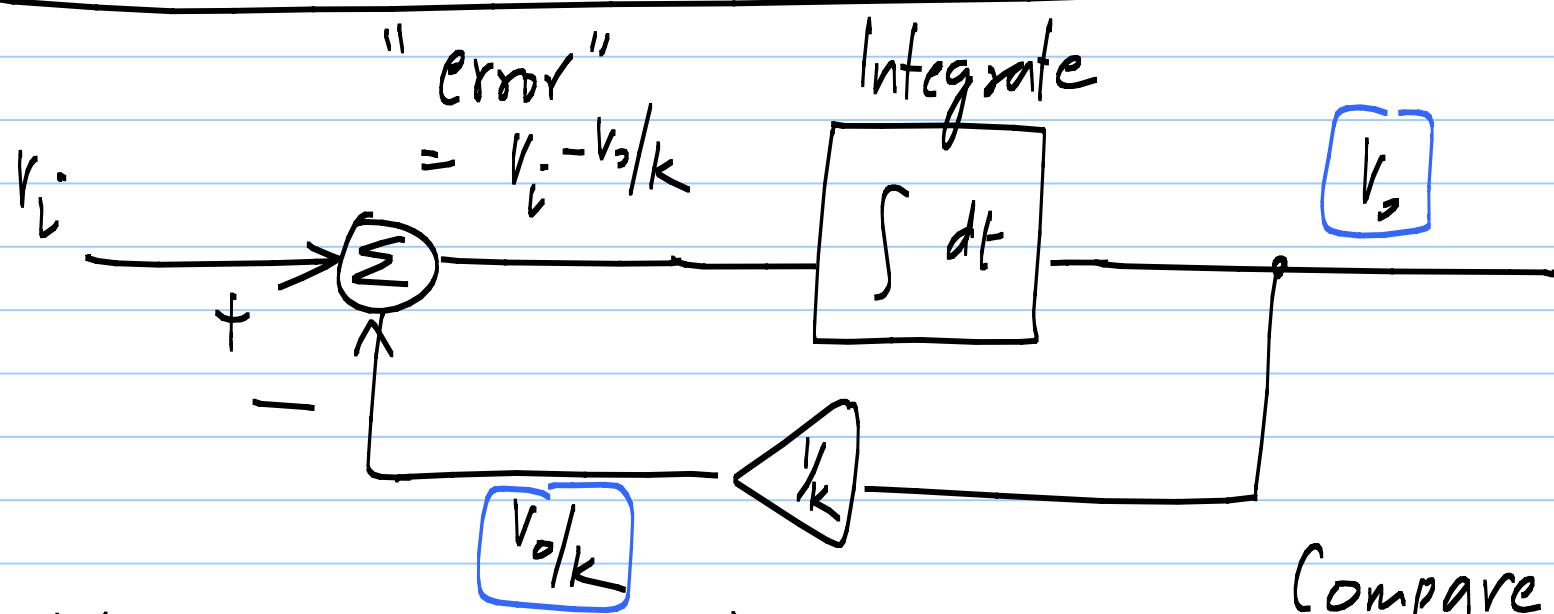


$\text{error} = 0 \Rightarrow$ integrator
o/p = constant

Amplifier using negative feedback

Note Title


12/22/2010



I'd like to make $V_o = kV_i$


Compare
actual o/p

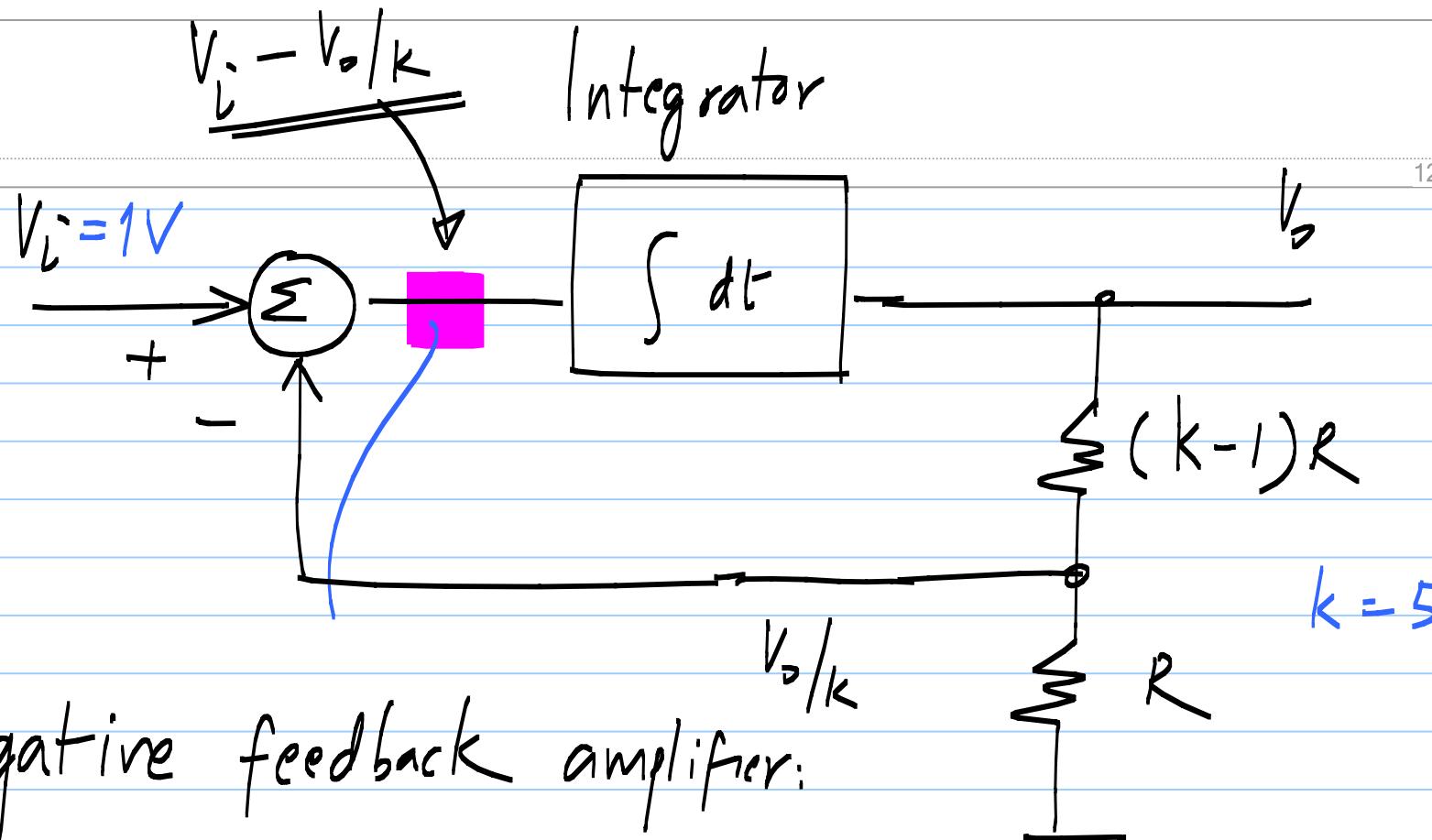\equiv I'd like to make $\frac{V_o}{k} = V_i$ to the
error: $\left(\frac{V_o}{k} - V_i \right)$ desired o/p.




Negative feedback amplifier:

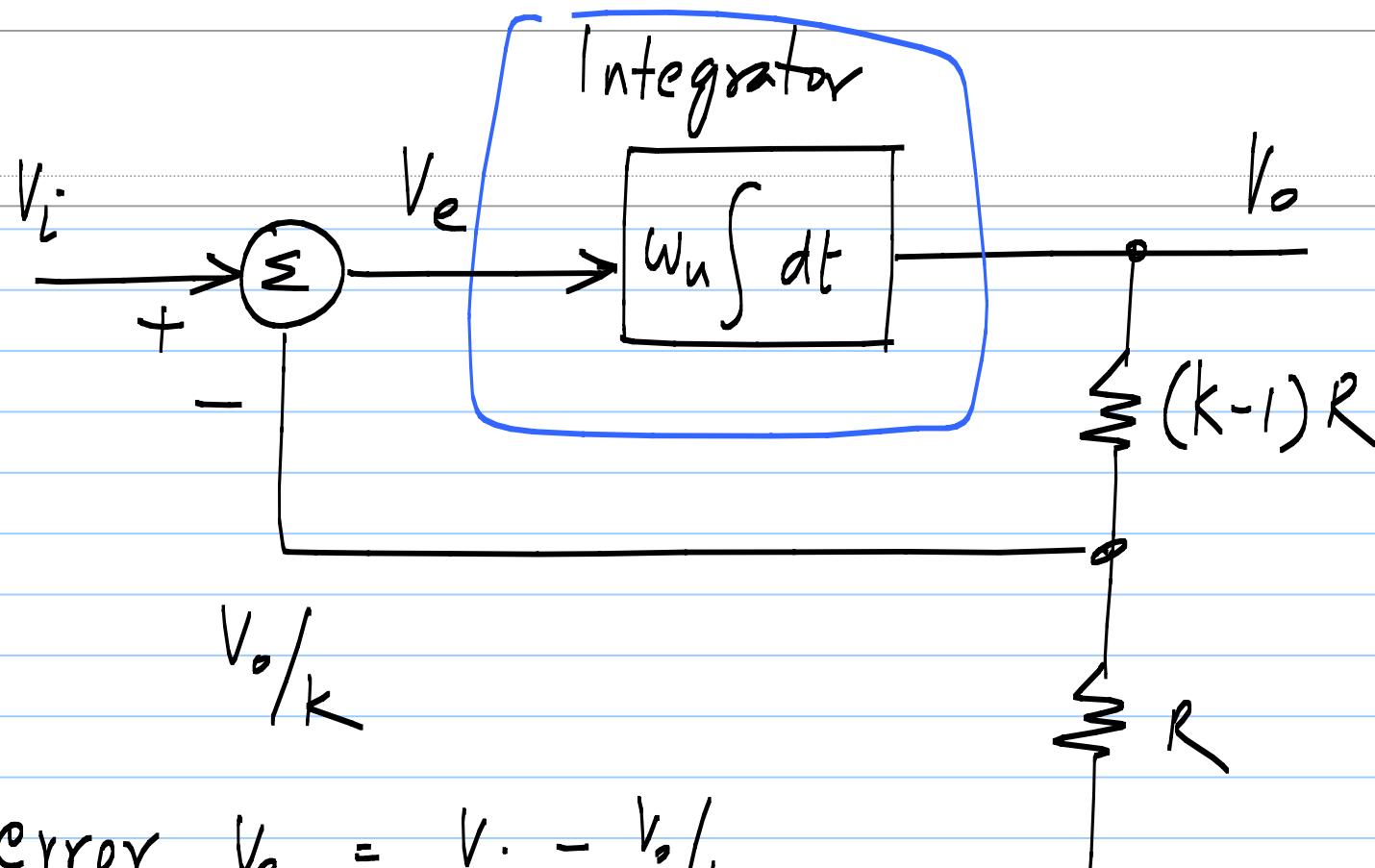- Integrate the error to drive the output



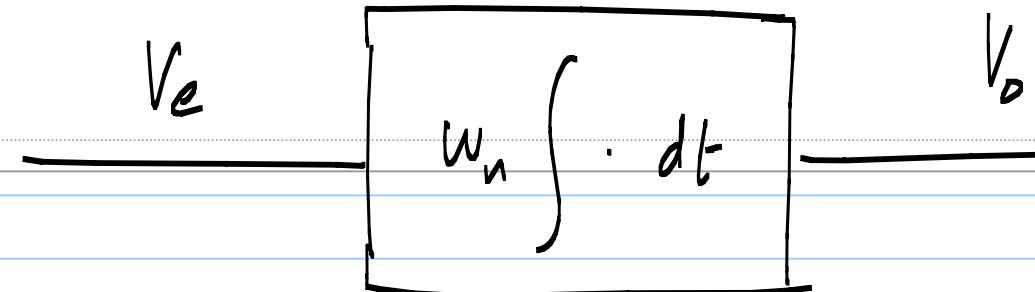
$$\text{Error } V_e = \underline{V_i - V_o/k}$$




$$V_o = w_n \int V_e \cdot dt$$

w_n : dimensions
of frequency

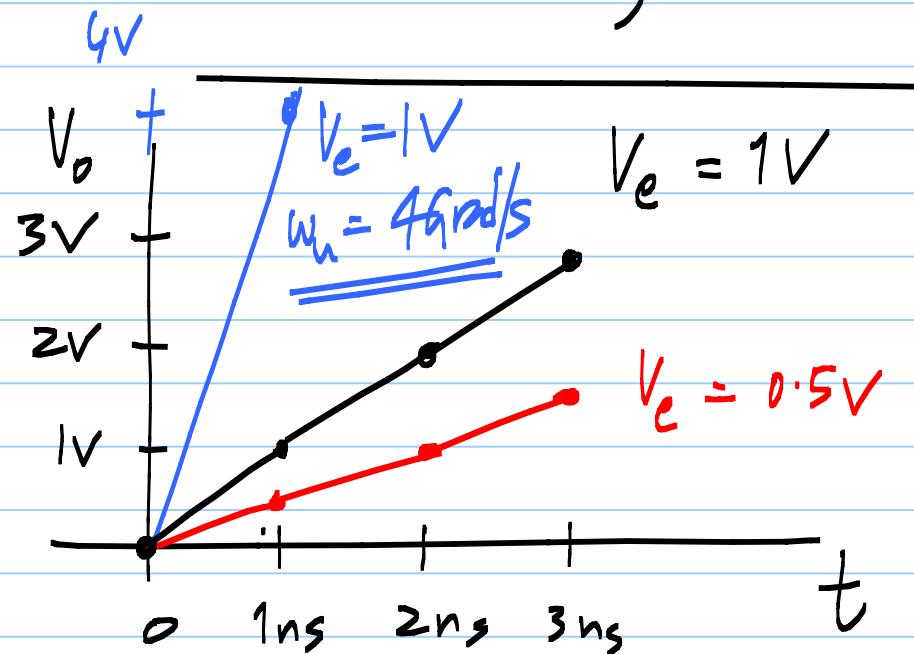

$$\begin{aligned} w_n &= 1 \text{ Grad/s} \\ &= 10^9 \cdot \text{rad/s} \end{aligned}$$
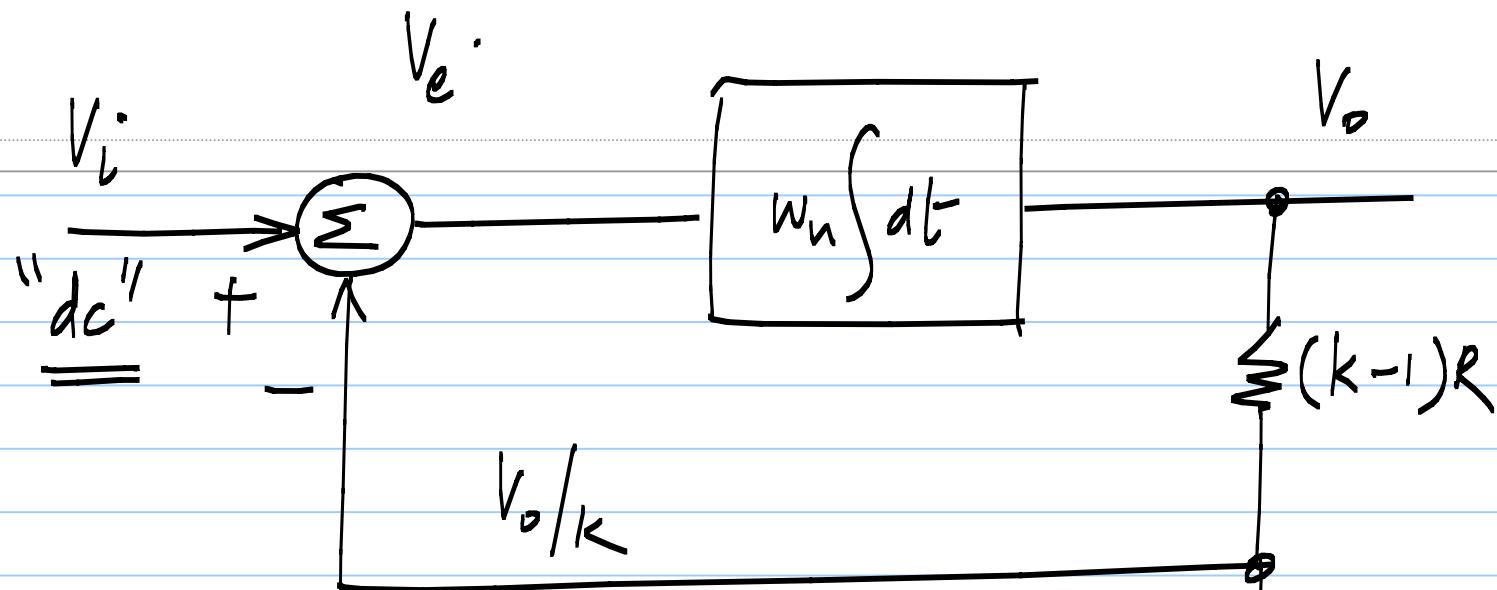
$$\begin{aligned} w_n &= 4 \text{ Grad/s} \\ &= 4 \times 10^9 \text{ rad/s} \end{aligned}$$



$$\frac{dV_o}{dt} = w_n \left(V_i - \frac{V_o}{k} \right)$$

$$\frac{dV_o}{V_i - \frac{V_o}{k}} = w_n \cdot dt$$

Integrate : $\int \frac{dV_o}{V_i - \frac{V_o}{k}} = \frac{w_n \cdot dt}{k}$

$V_i : \text{const}$

$$\frac{dV_o}{kV_i - V_o} = \frac{w_n \cdot dt}{k}$$


↓ Integrating

$$-\ln(kV_i - V_o) \Big|_{V_o(0)}^{V_o(t)} = \frac{w_n}{k} \cdot t \Big|_0^t$$

$$\ln \frac{kV_i - V_o(t)}{kV_i - V_o(0)} = -\frac{w_n}{k} \cdot t$$

$$V_o(t) = V_o(0) \cdot \exp\left(-\frac{\omega_n}{k} \cdot t\right)$$
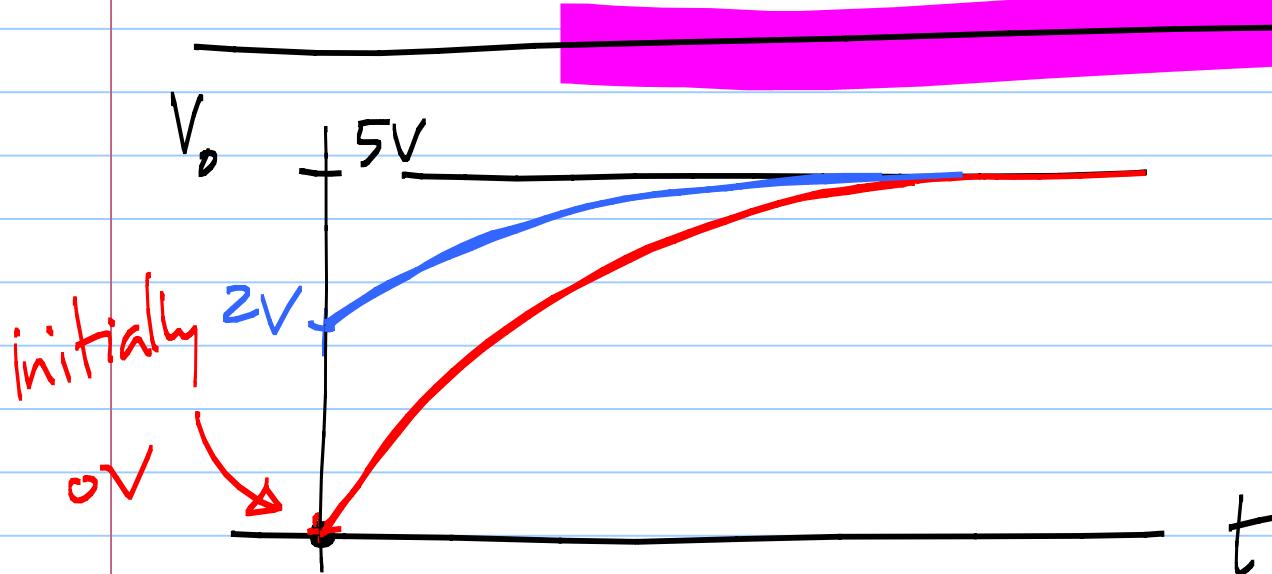
$$+ k \cdot V_i \left(1 - \exp\left(-\frac{\omega_n}{k} \cdot t\right) \right)$$




$$V_o(t) = k V_i$$

when $t = \infty$

$$V_o(t) = V_o(0) \exp\left(-\frac{w_n t}{k}\right) + k V_i \cdot \left(1 - \exp\left(-\frac{w_n t}{k}\right)\right)$$

12/22/2010

Note Title

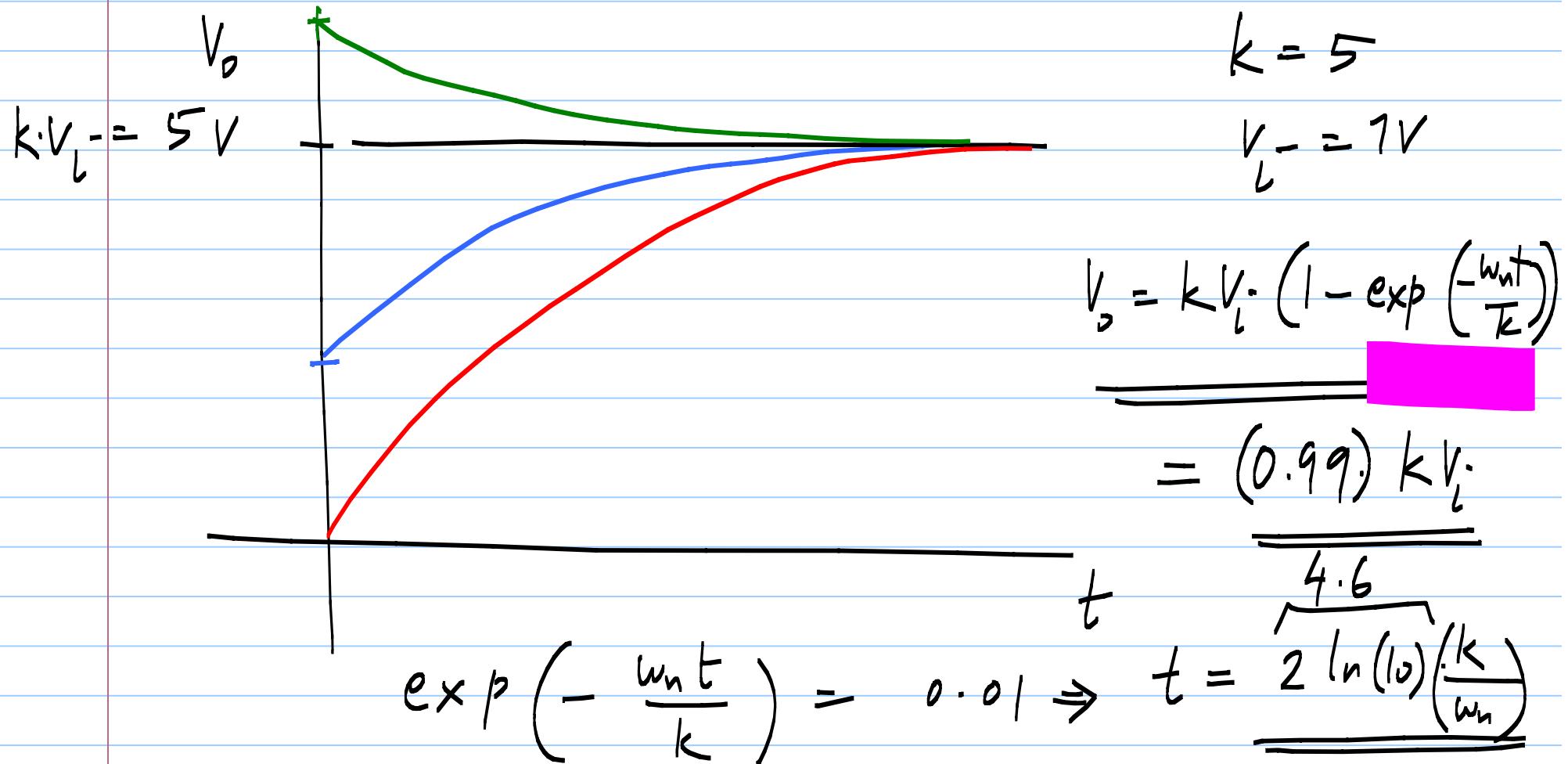

$$\exp\left(-\frac{\omega_n}{k} \cdot t\right) = 0.01$$

$$\Rightarrow t = \frac{2 \ln(10)}{4.6} \cdot \left(\frac{k}{\omega_n}\right)$$

$$\frac{k}{\omega_n} = \frac{5}{10^9 \text{ rad/s}} = \underline{\underline{5 \text{ ns}}}$$

$$t = 23 \text{ ns} \rightarrow \underline{\underline{4.6 \text{ ns}}}$$

reaches 99% of the steady state value kV_i . (zero initial condition)


$$\omega_n = 10^9 \text{ rad/s}$$

12/22/2010

$$k = 5$$

$$\boxed{\omega_n = 5 \times 10^9 \text{ rad/s}}$$
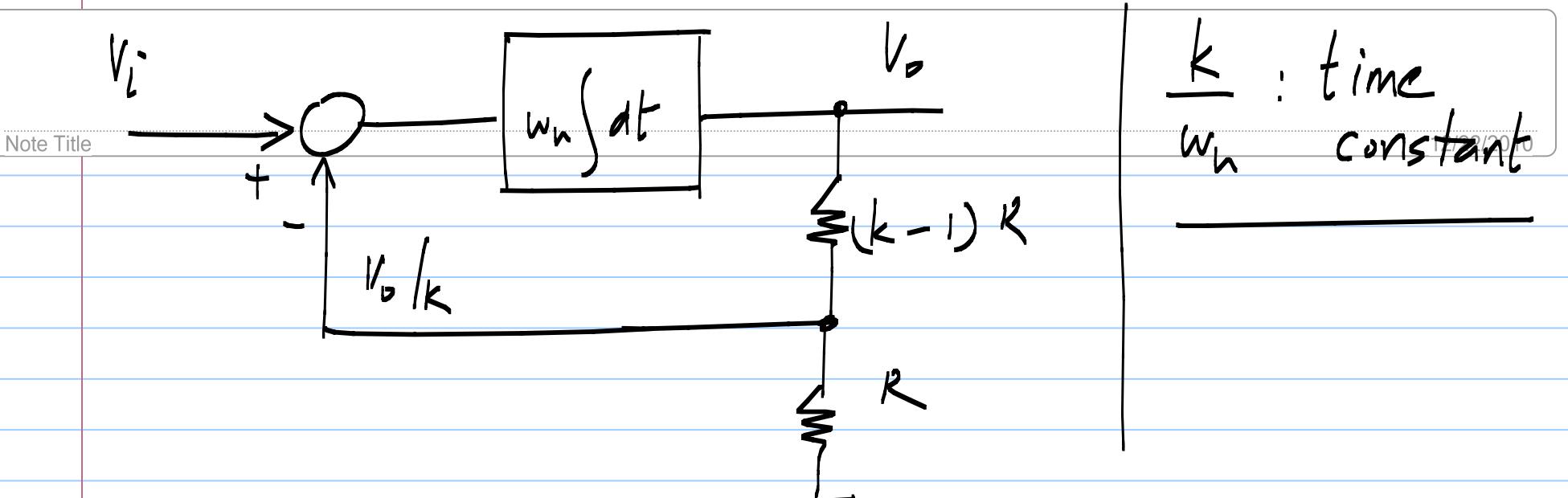
$$\frac{k}{\omega_n} = \frac{5}{5 \cdot 10^9 \text{ rad/s}} = \underline{\underline{1 \text{ ns}}}$$



- Compare divided output to the input & integrate the difference to drive the output
- Integrator: - w_n - speed of integration
- $\underline{\underline{V_o(t)}} \quad \begin{cases} \text{First order DE} \\ \exp\left(-\frac{w_n t}{k}\right) \end{cases}$