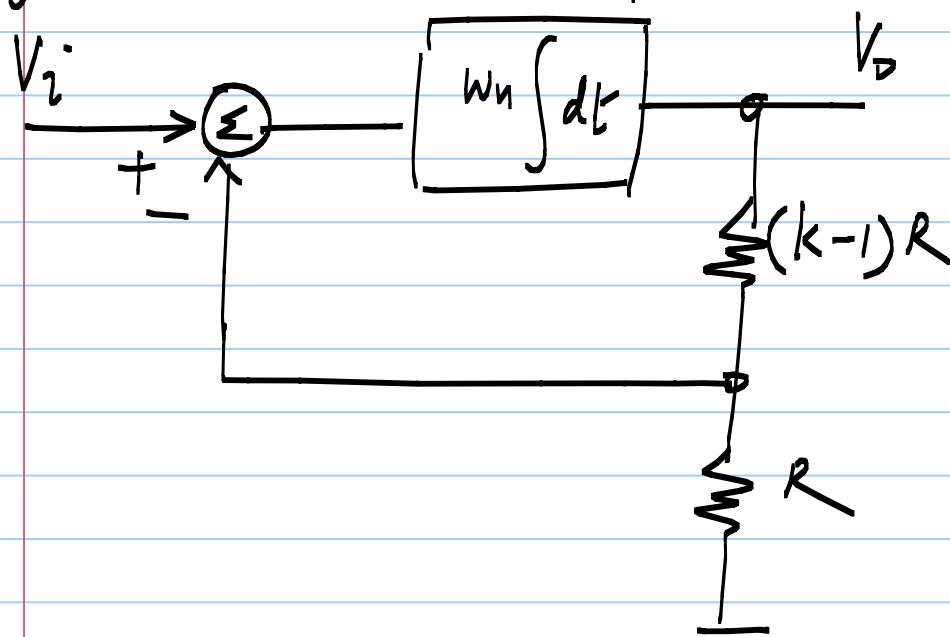


# Lecture #5, Analog IC Design

Note Title

12/24/2010

## Negative feedback amplifier



$$\text{time constant} = \frac{k}{\omega_n}$$


$$\text{bandwidth} = \frac{\omega_n}{k}$$

$$\boxed{\omega_{n,\text{loop}} = \frac{\omega_n}{k}}$$

# Operational amplifier: (opamp)


Note Title

12/24/2010

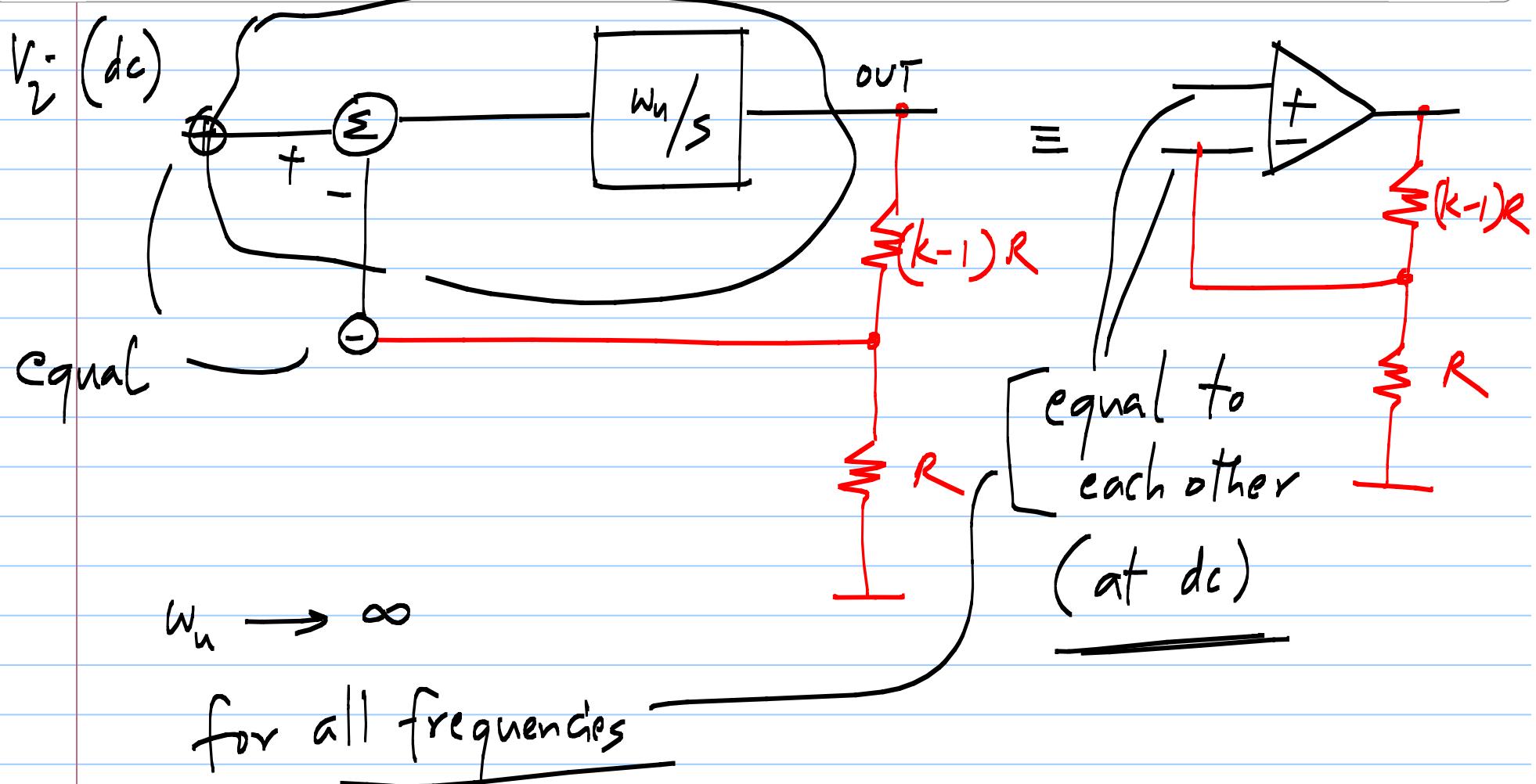

## Loop gain :

Note Title

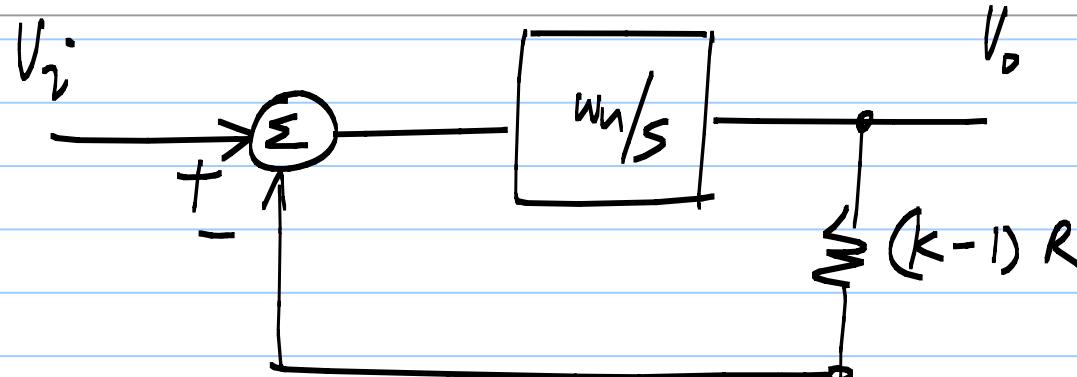


$$V_{\text{RETURN}} = -L(s) \cdot V_{\text{TEST}}$$

Loop gain

$$|L(s)| \gg 1$$

strong negative feedback

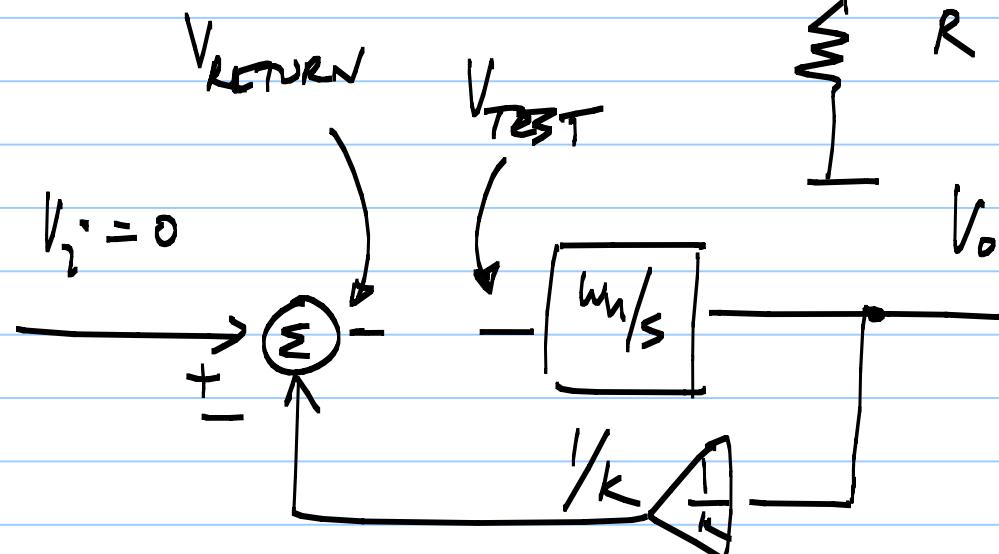


# Other amplifiers using an opamp.

Note Title


12/24/2010

V<sub>CVS</sub>:

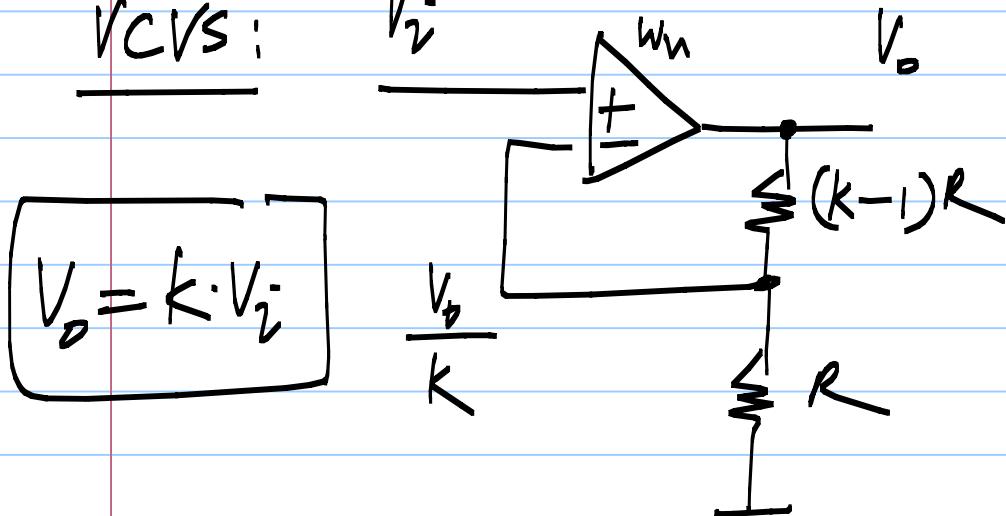

$$V_o = k \cdot V_i$$

$$\frac{V_o}{V_i} = k$$

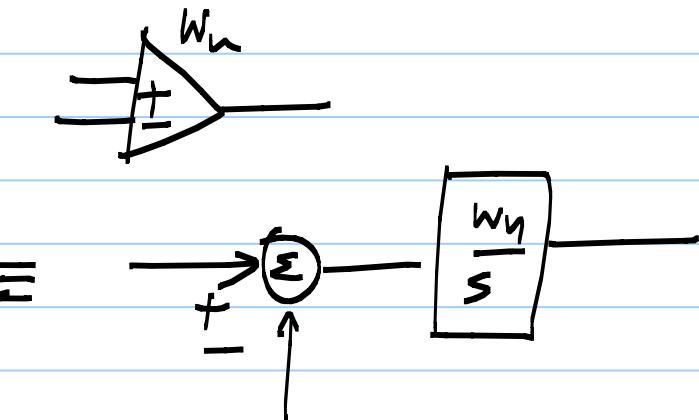

CCVS:



$$\underline{V_o = R_f \cdot I_i}$$

CCVS :

$$V_o = R_f \cdot I_i$$

Note Title

12/24/2010

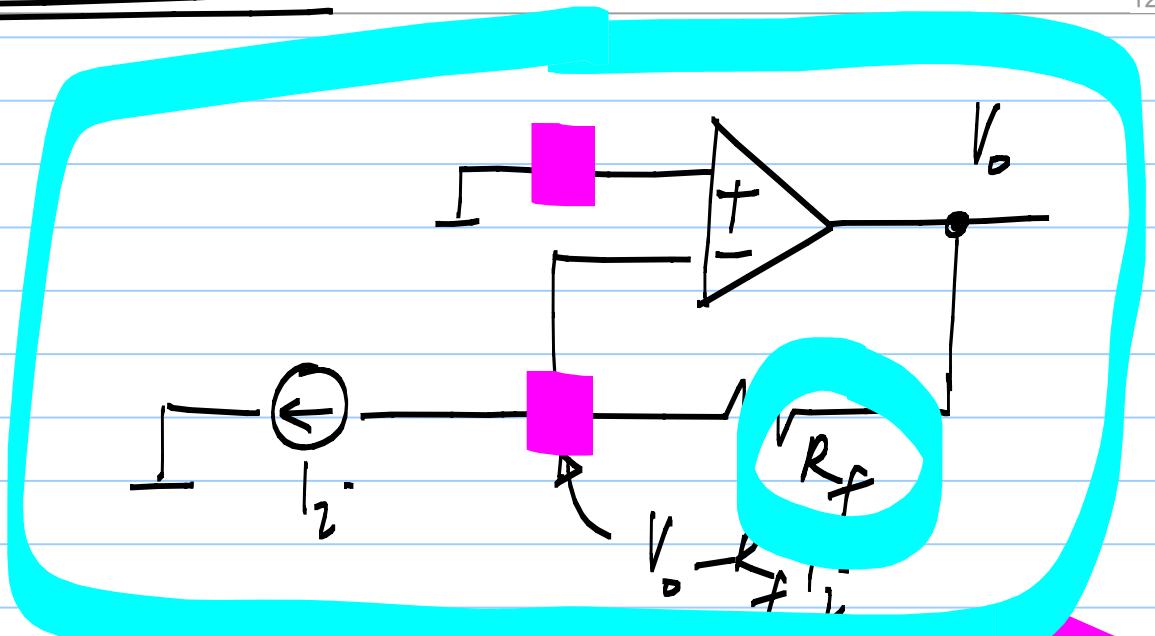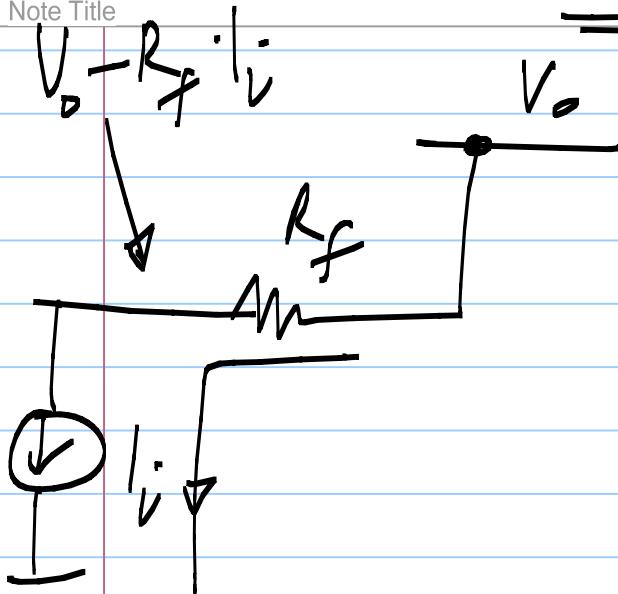

$$(V_o - R_f \cdot I_i) > 0 \quad \text{reduce } V_o$$


$$(V_o - R_f \cdot I_i) < 0 \quad \text{increase } V_o$$

CCVS :

$$V_o = I_i \cdot R_f$$

Note Title

12/24/2010

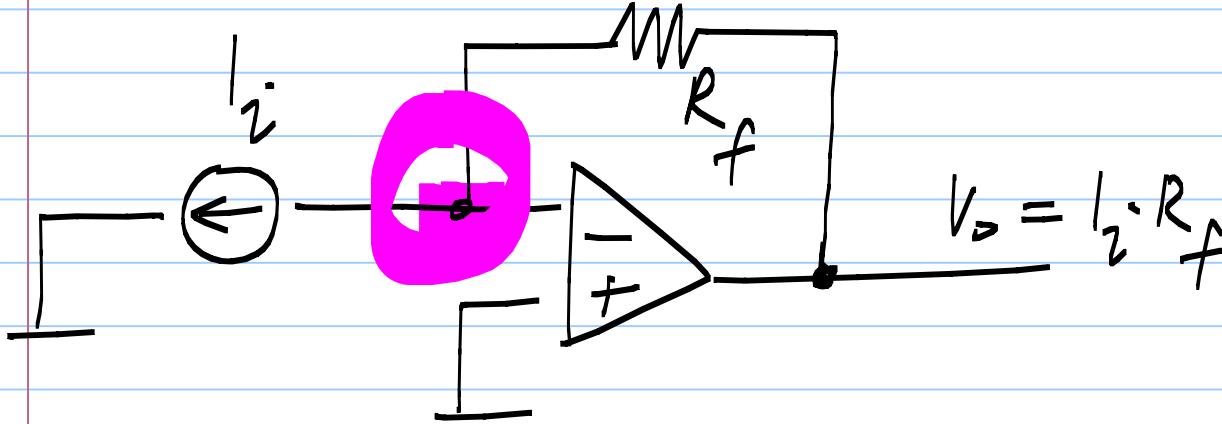


$$I_i \cdot (dc)$$

VCVS


Note Title

12/24/2010

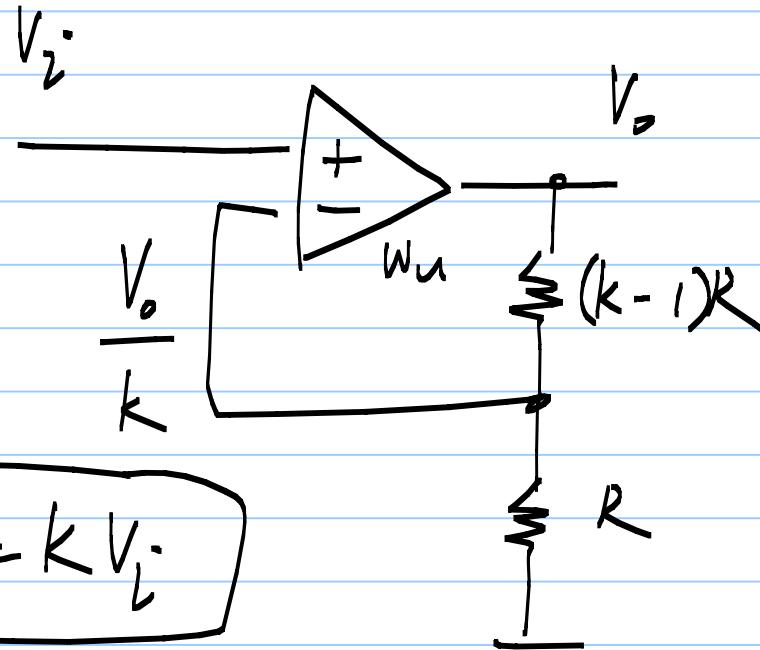

$$V_o = k V_i$$

CCVS

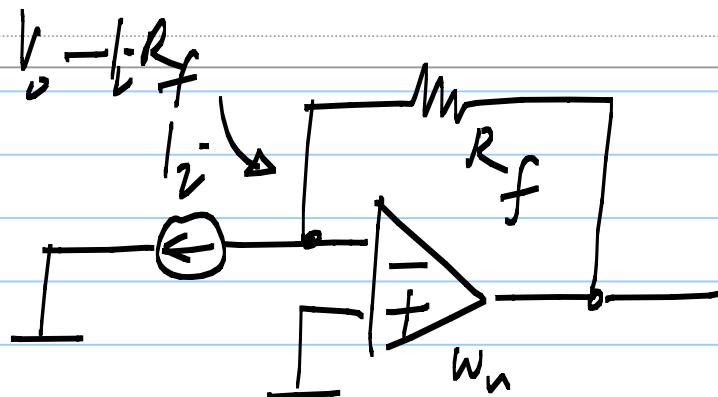

$$V_o = I_i \cdot R_f$$

$$dc: \quad V_o/k = V_i$$

$$V_o - I_i \cdot R_f = 0$$

$$w_n \rightarrow \infty \quad \text{for all freq.} \quad \frac{V_o}{k} = V_i$$

$$V_o - I_i \cdot R_f = 0 \quad \boxed{\text{IDEAL}}$$

# Integrator realization:


Note Title

12/24/2010

Integration using  $L$  or  $C$




Impractical

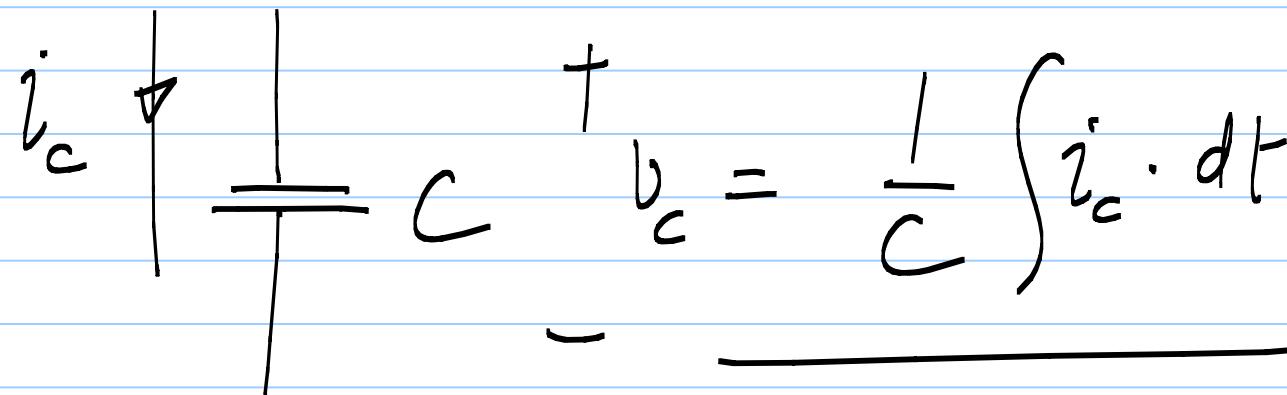
$$i_c \uparrow \quad \frac{+}{-} C \quad + b_c = \frac{1}{C} \int i_c \cdot dt$$


Note Title

12/24/2010

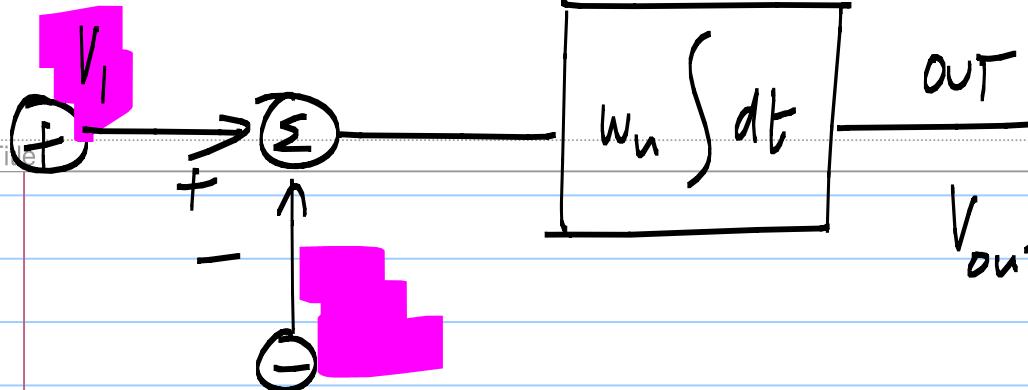

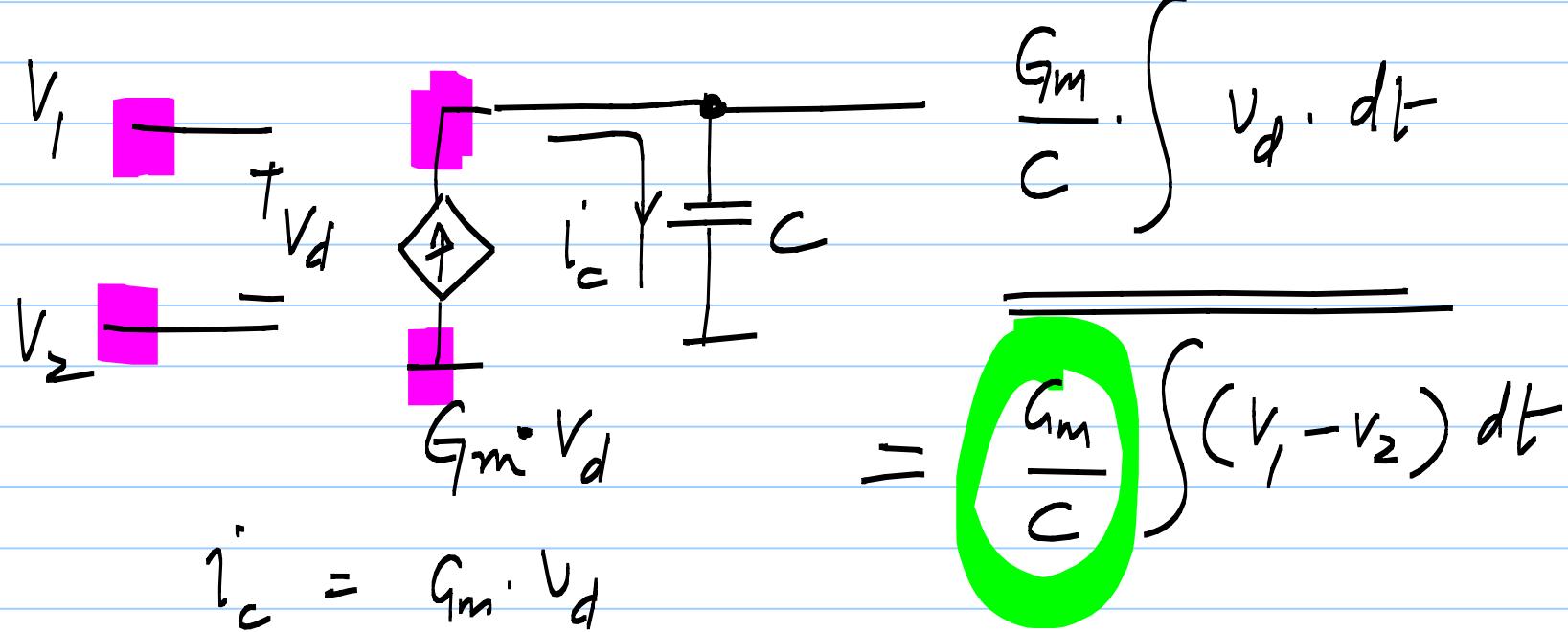
$$V_{\text{out}} = w_n \int (V_1 - V_2) dt$$



$$= \frac{G_m}{C} \int (V_1 - V_2) dt$$




$$i_c = G_m \cdot V_d$$

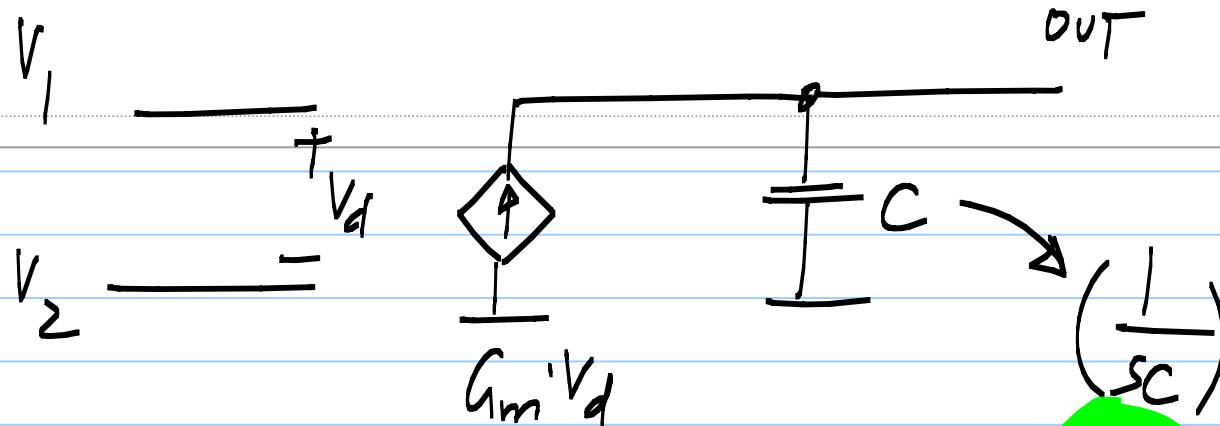


$$V_{\text{out}} = G_m \cdot V_d \cdot \frac{1}{sC} = \frac{G_m}{sC} (V_1 - V_2)$$

$$V_{\text{out}} = \frac{w_u}{s} (V_1 - V_2)$$


$w_u = \frac{G_m}{C}$

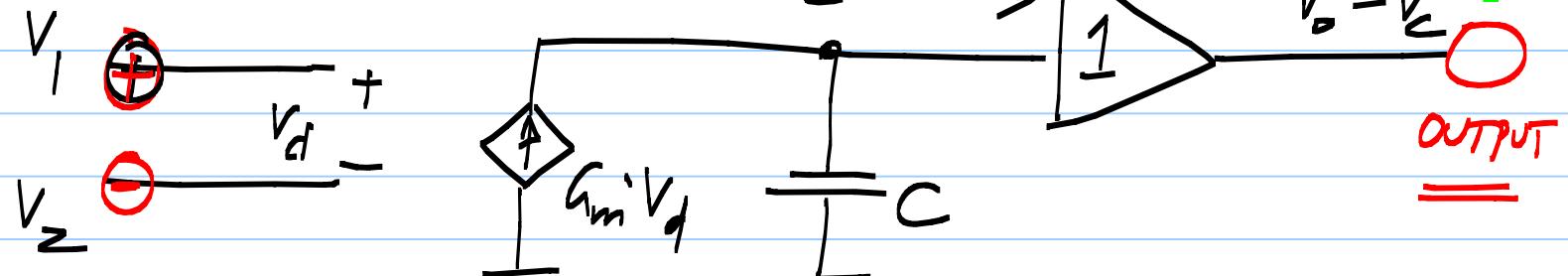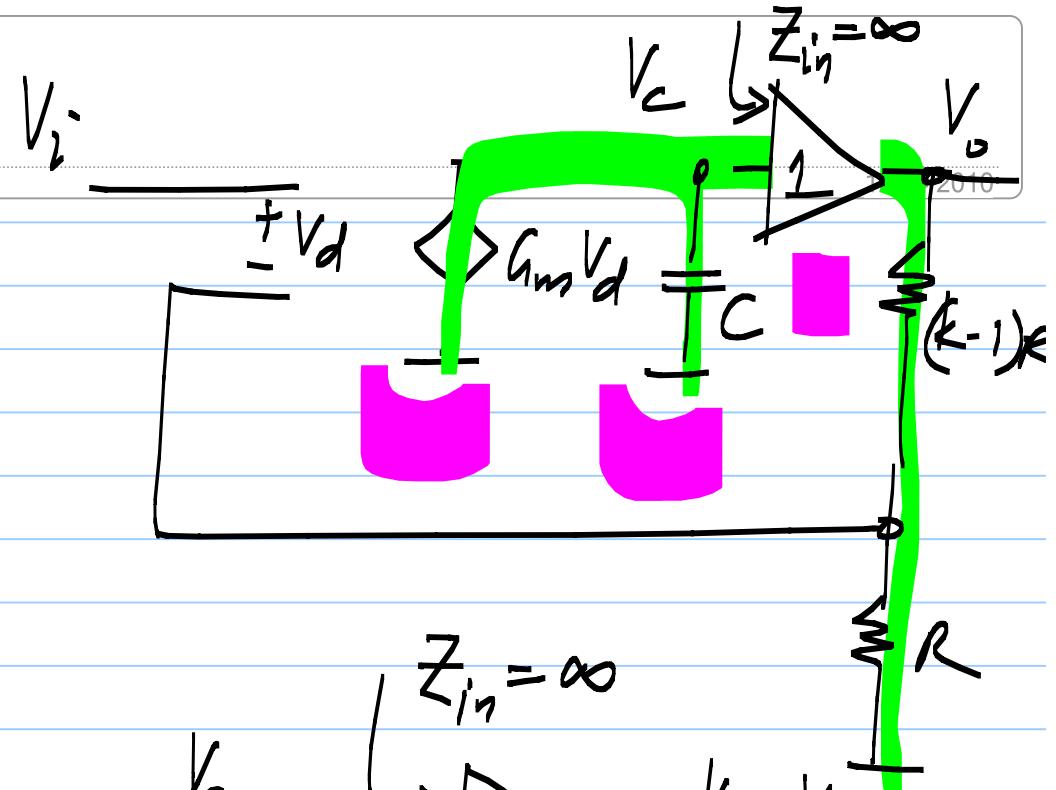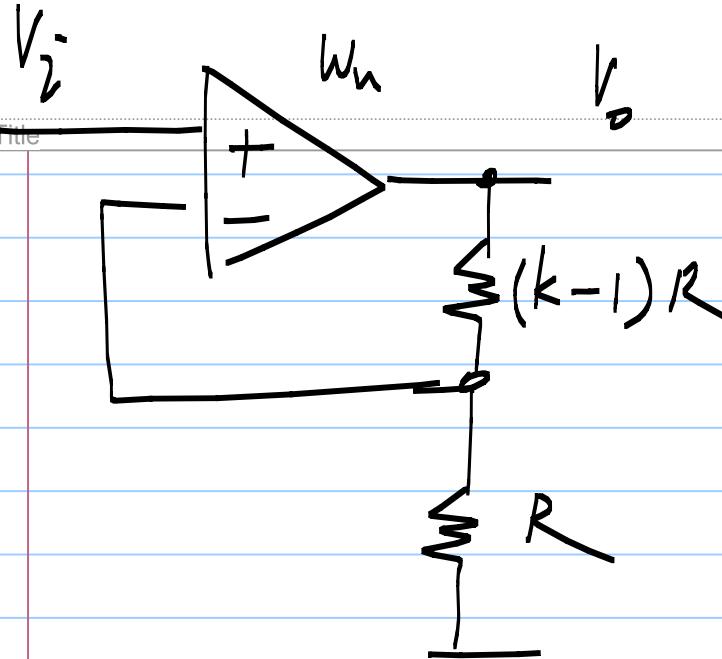

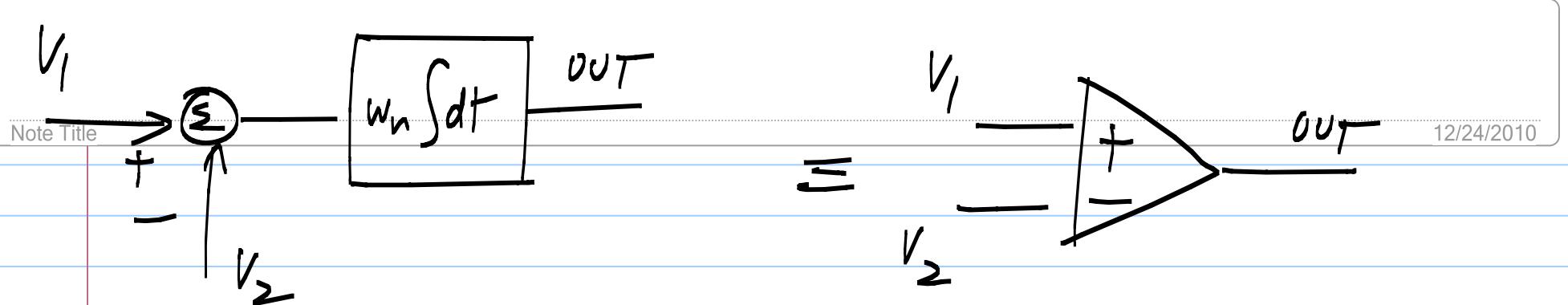

Take the difference  
& integrate


opamp

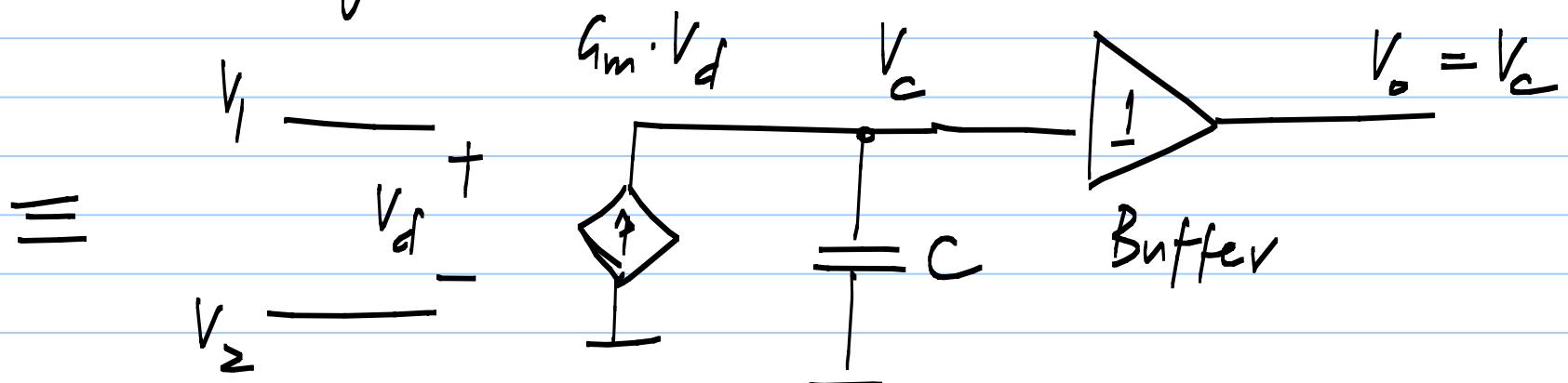

Realization

Desired

Specd

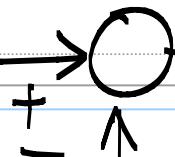

$$\int dt$$

12/24/2010

Actual  
Speed

Speed

50 km/h

Actual

5 seconds

time

$$\text{delay}$$

5 seconds