

# Negative feedback system with delay

Note Title


12/24/2010

- Feedback is delayed
- Comparison is with the actual output some time ago
- Don't know if actual output has reached the target → "overshoot"  
(go past the target)  
→ go below the target → "ringing"

# Negative feedback amplifier:

$$\frac{1}{\omega_n} \cdot \frac{dV_o}{dt}$$

1/18/2011

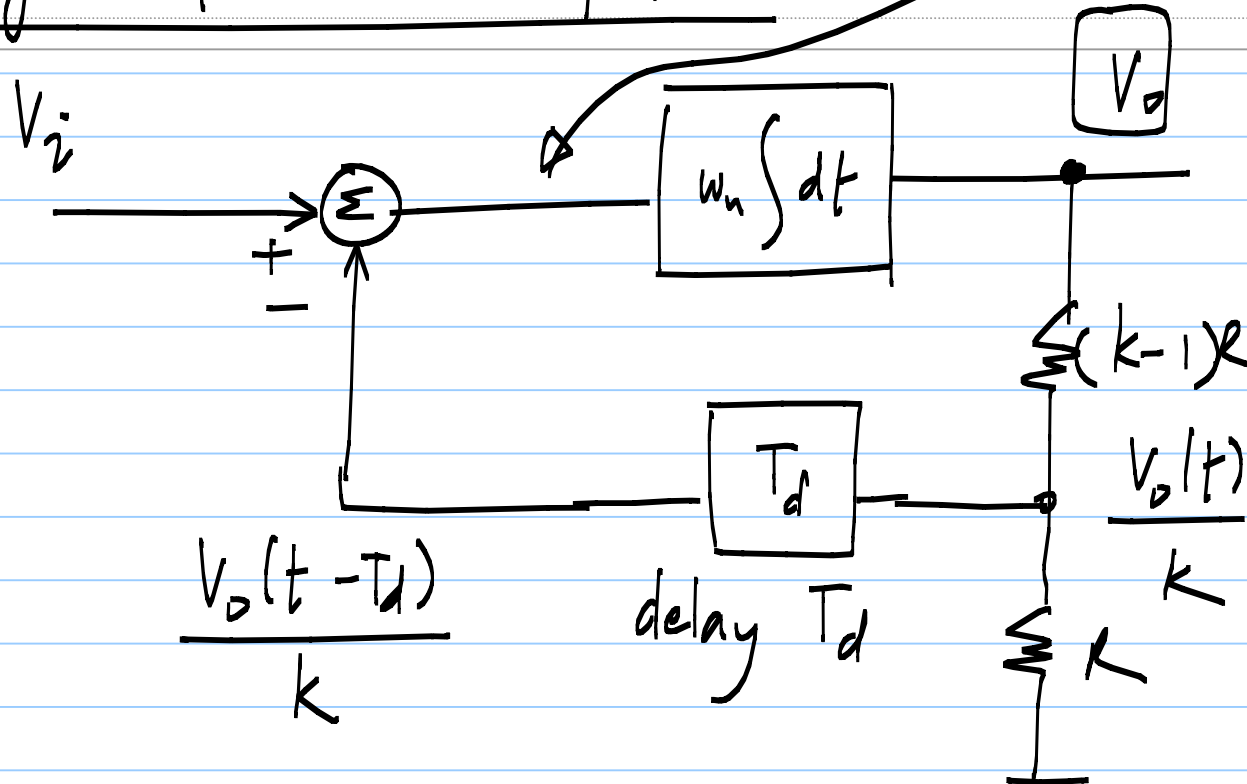

$$\frac{1}{\omega_n} \cdot \frac{dV_o(t)}{dt} = V_i(t) - \frac{V_o(t - T_d)}{k}$$

$$\frac{1}{w_n} \frac{dV_o}{dt} = V_i(t) - \frac{V_o(t - T_d)}{k}$$

Assume initially ( $t < 0$ )

$$V_i = 1V, \quad V_o = k \cdot V \Rightarrow \text{steady state}$$

$$\textcircled{a} \quad t = 0 \quad V_i \rightarrow 0$$

$$\frac{1}{w_n} \frac{dV_o}{dt} = - \frac{V_o(t - T_d)}{k}$$

$$\frac{1}{w_n} \cdot \frac{dv_o}{dt} = - \frac{v_o(t - T_d)}{k}$$

Assume an exponential form :  $v_o(t) = V_p \exp(\sigma t)$

$$\frac{1}{w_n} \cdot \cancel{V_p} \cdot \cancel{\sigma} \exp(\sigma t) = - \frac{V_p \exp(\sigma(t - T_d))}{k}$$

$$= - \frac{\cancel{V_p} \exp(\sigma t) \exp(-\sigma T_d)}{k}$$

$$\boxed{\frac{\sigma}{w_n} = - \frac{\exp(-\sigma T_d)}{k}}$$

$$\frac{\sigma}{\omega_u} = - \frac{\exp(-\sigma T_d)}{k}$$

$$\frac{\sigma}{\omega_u/k} + \exp(-\sigma T_d) = 0$$

$$\left(\frac{\sigma}{\omega_u/k}\right) \cdot \left(T_d \cdot \frac{\omega_u}{k}\right)$$

$$\sigma' + \exp(-\sigma' T) = 0$$


$$\sigma' = \frac{\sigma}{\omega_u/k}$$

$$T = \frac{T_d}{k/\omega_u}$$

Solve  $f(\sigma') = \sigma' + \exp(\sigma'/T) = 0$

Note Title

for  $\sigma'$

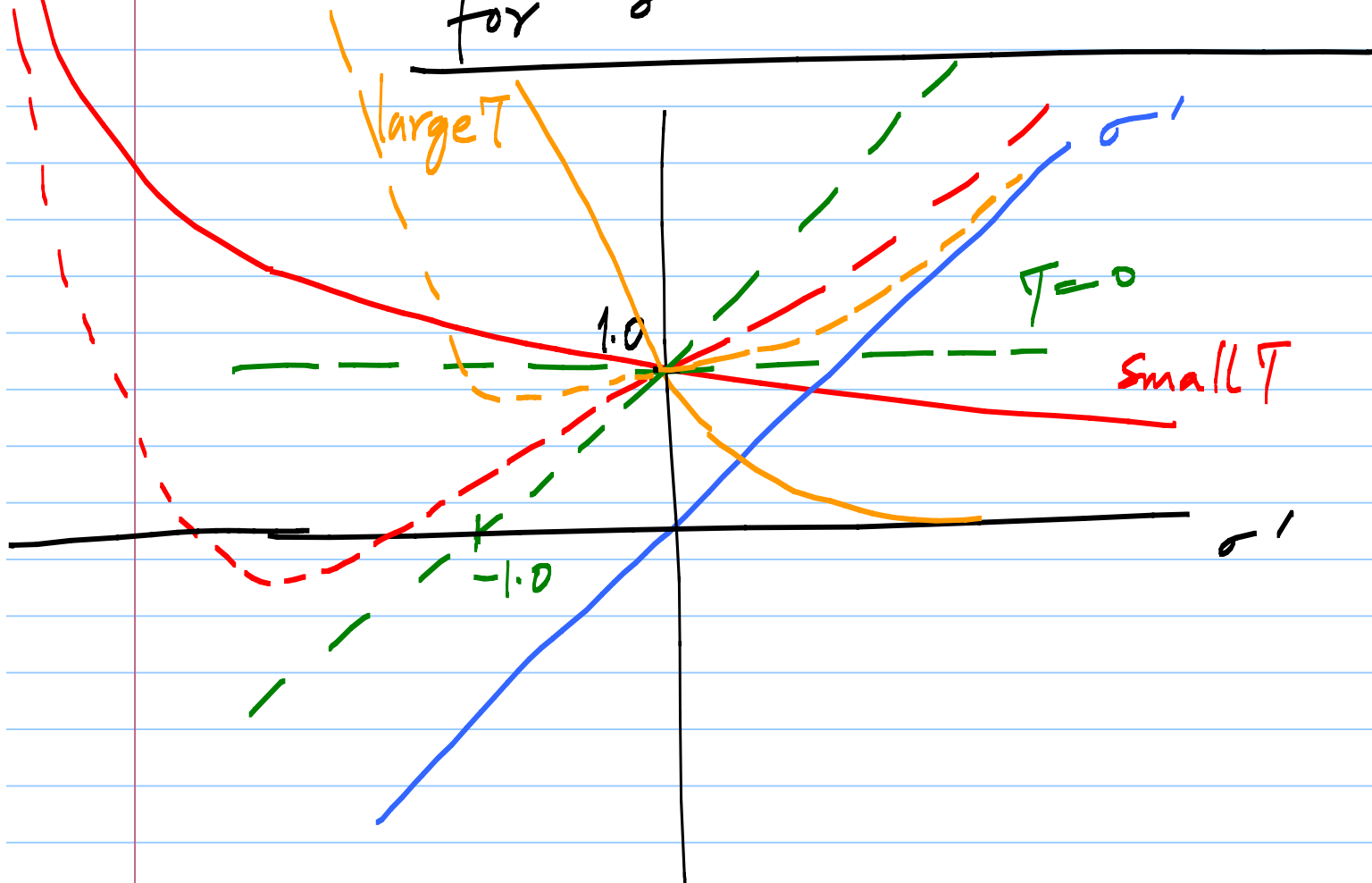

$$\sigma' = -1$$

$$\sigma = -\frac{w_n}{k}$$

for  $T_d = 0$

# Negative feedback with delay: $V_p \exp(\sigma t)$

Note Title

1/18/2011

$$\underline{\sigma' + \exp(\sigma' T) = 0}$$

$$\sigma' = \frac{\sigma}{\omega_n/k}$$

$$T = \frac{T_d}{k/\omega_n}$$

\* Has two solutions for small  $T$

$$\sigma'_1, \sigma'_2 \Rightarrow \sigma_1 \text{ \& \ } \sigma_2$$

\* Has no solutions for large  $T$

Two solutions  $\sigma_1, \sigma_2$

Note Title


1/18/2011

$\Rightarrow \exp(\sigma_1 t), \exp(\sigma_2 t)$  are solutions

$$to \quad \frac{1}{\omega_n} \frac{dv_o}{dt} = - \frac{v_o(t - T_d)}{k}$$

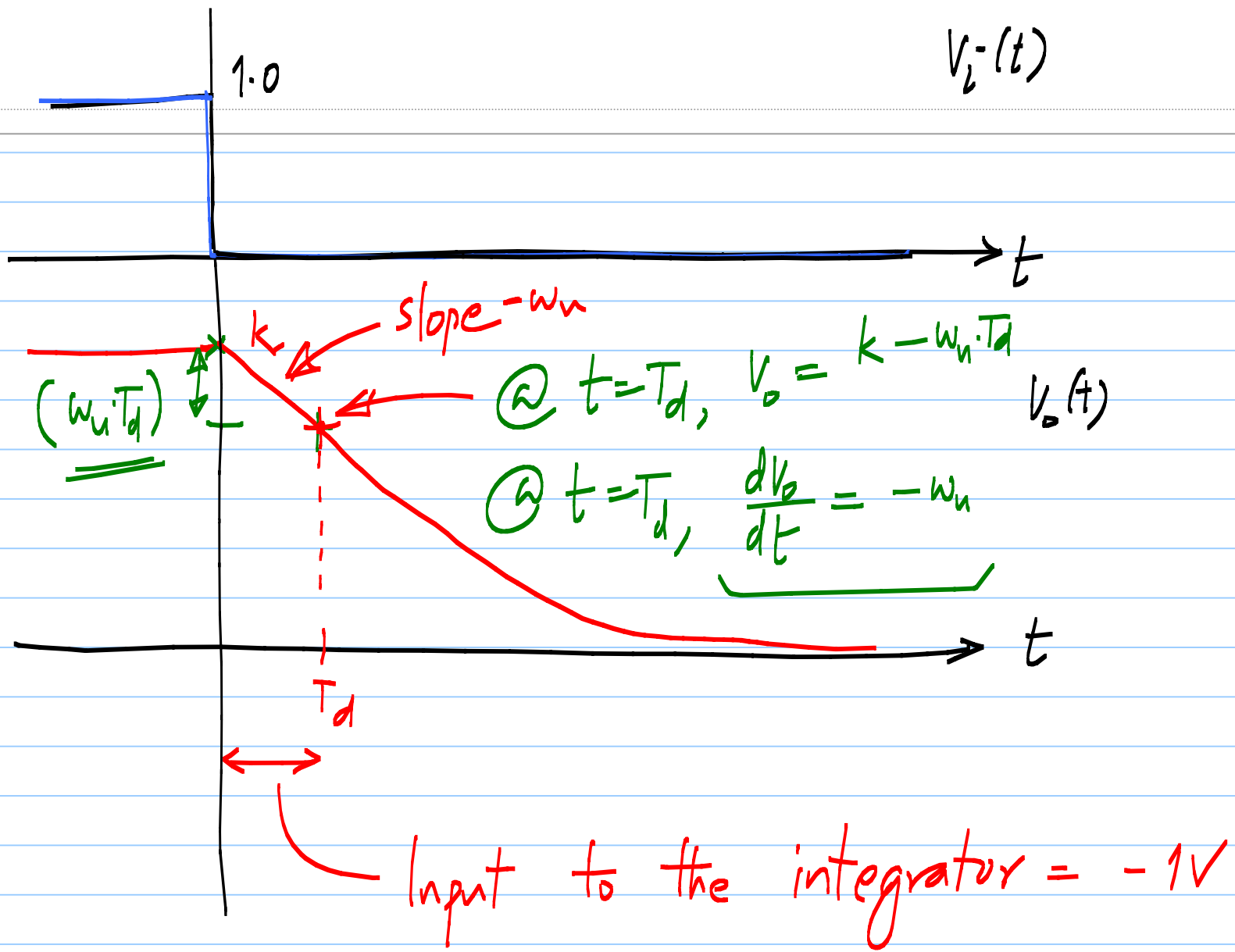Complete solution:  $v_o(t) = A_1 \cdot \exp(\sigma_1 t) + A_2 \cdot \exp(\sigma_2 t)$








$$\text{Solution } V_o(t) = A_1 \exp(\sigma_1 t) + A_2 \exp(\sigma_2 t)$$

$$\begin{aligned} V_o(T_d) &= k - \omega_n \cdot T_d \\ &= k \left( 1 - \frac{T_d}{\omega_n/k} \right) \\ &= \underline{k (1 - T)} \end{aligned}$$

$$\left. \frac{dV_o}{dt} \right|_{t=T_d} = -\omega_n$$

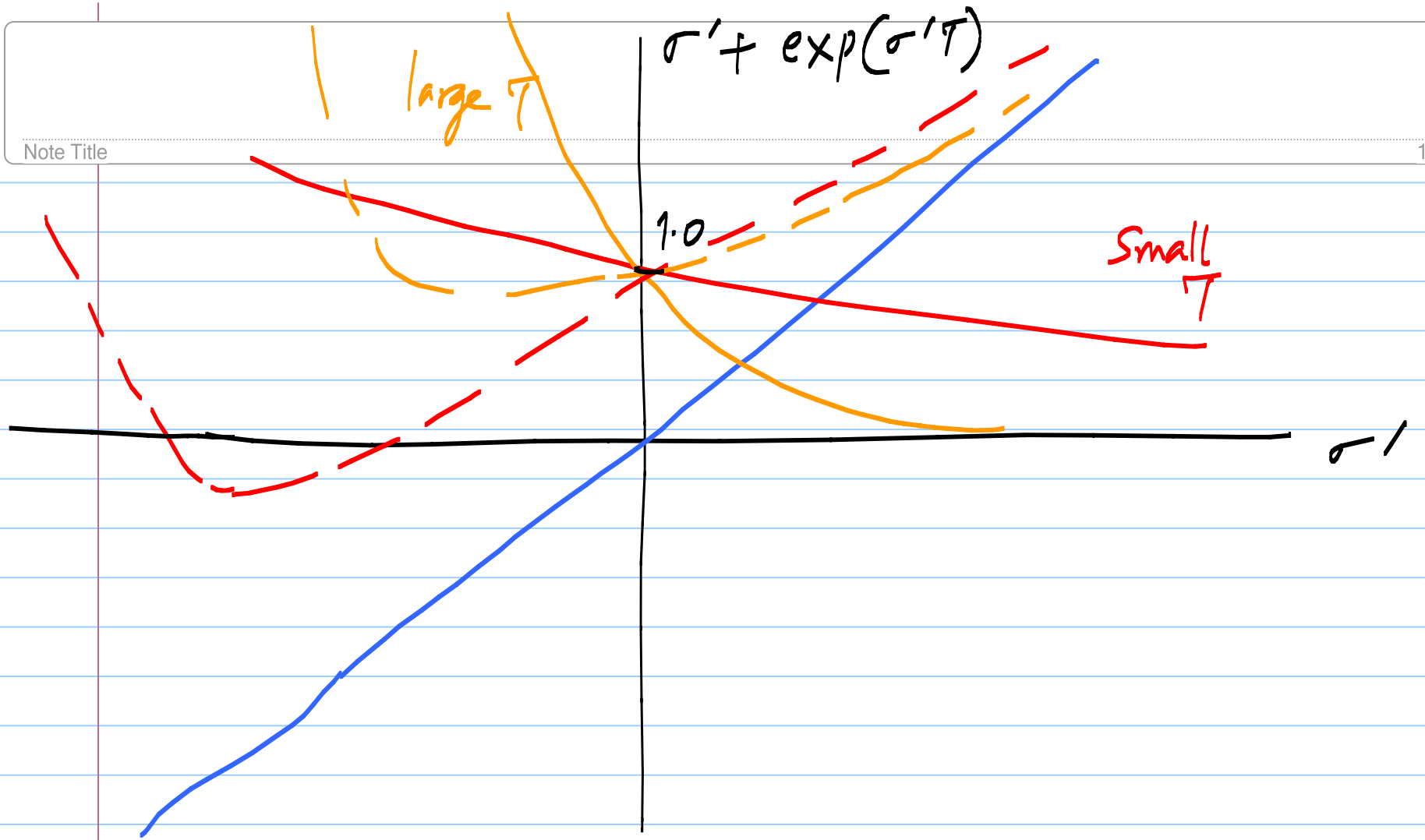

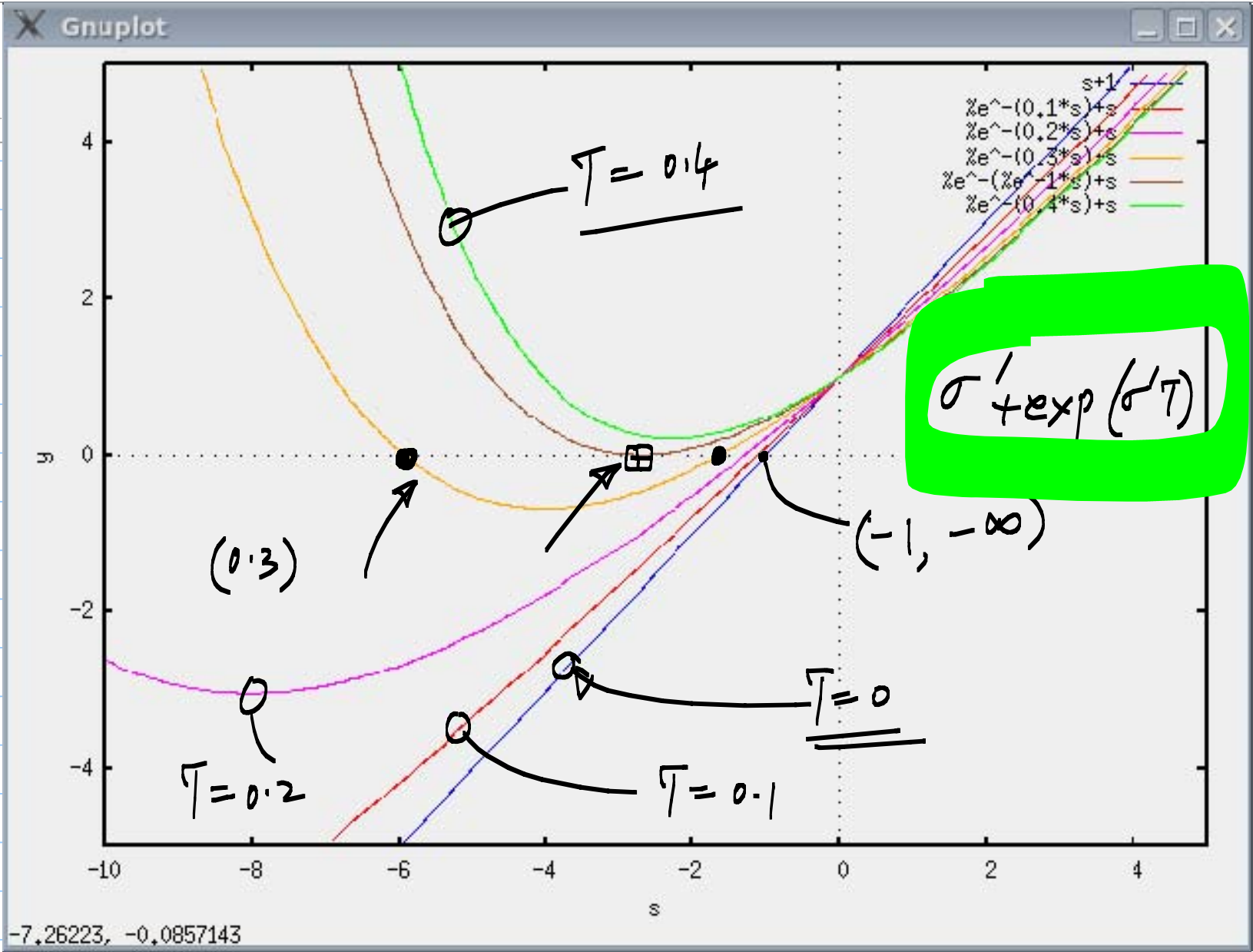

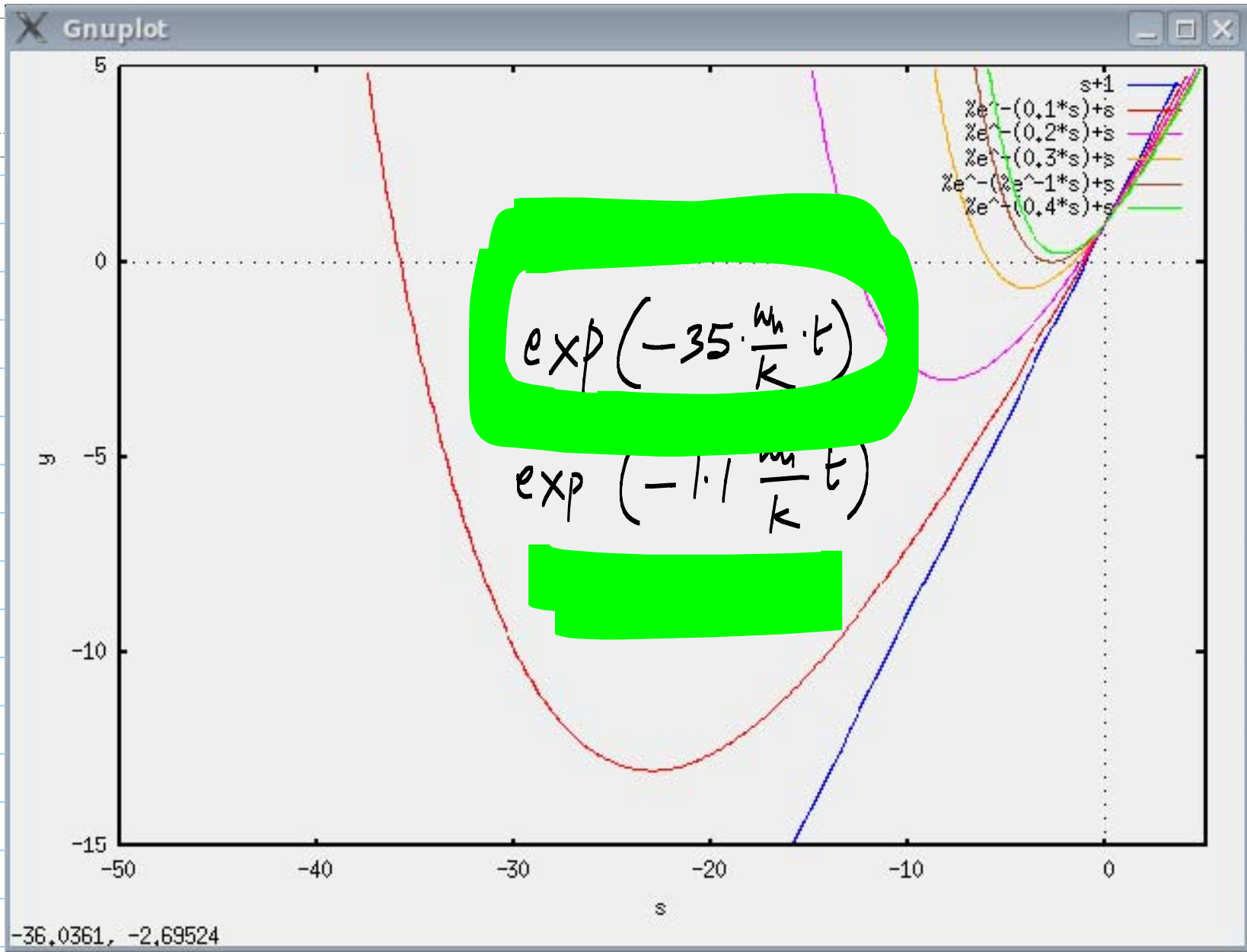


Note Title

1/18/2011


Note Title

2011

Transient Response

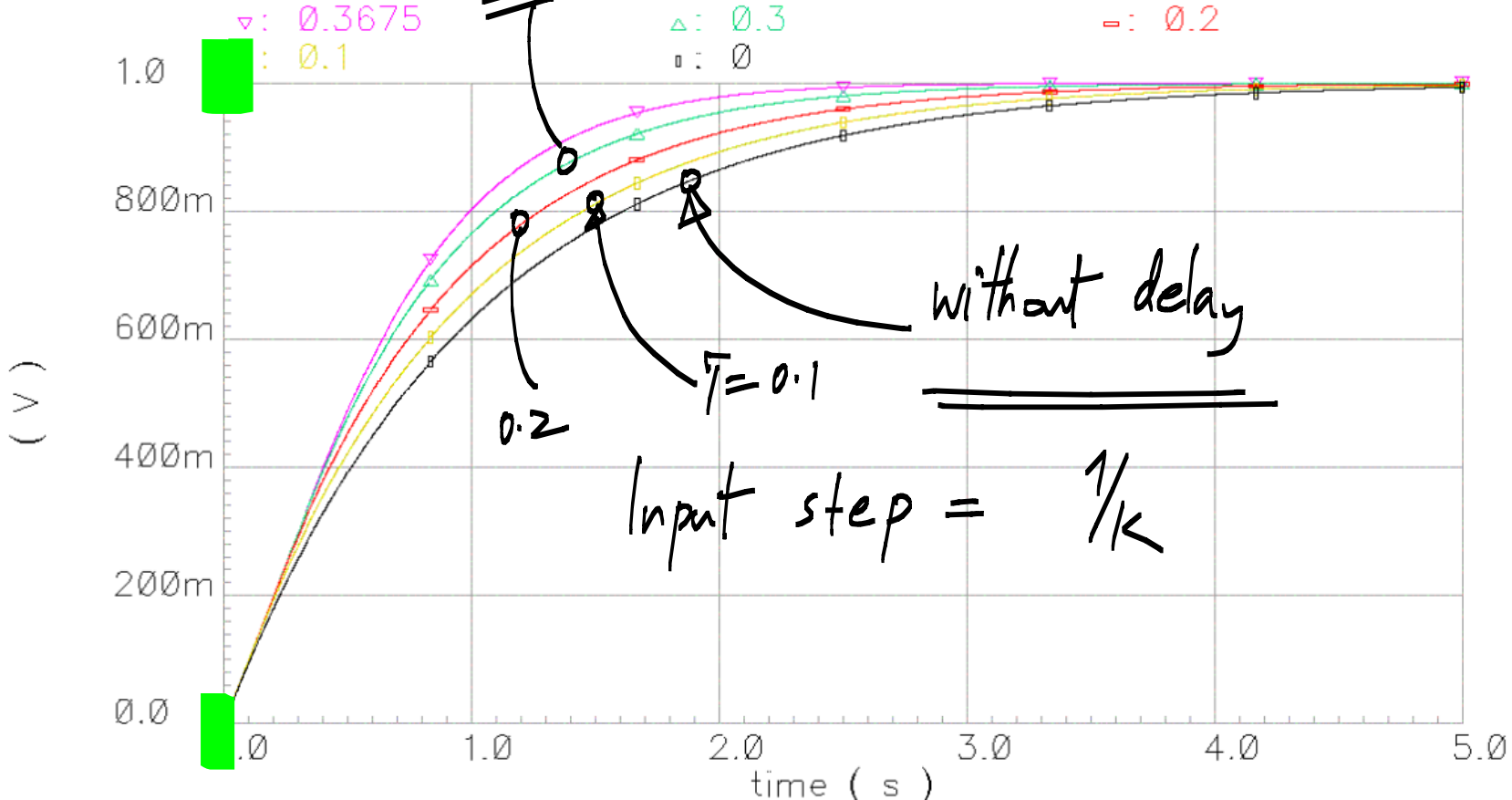

$$\frac{\omega_n}{K}$$

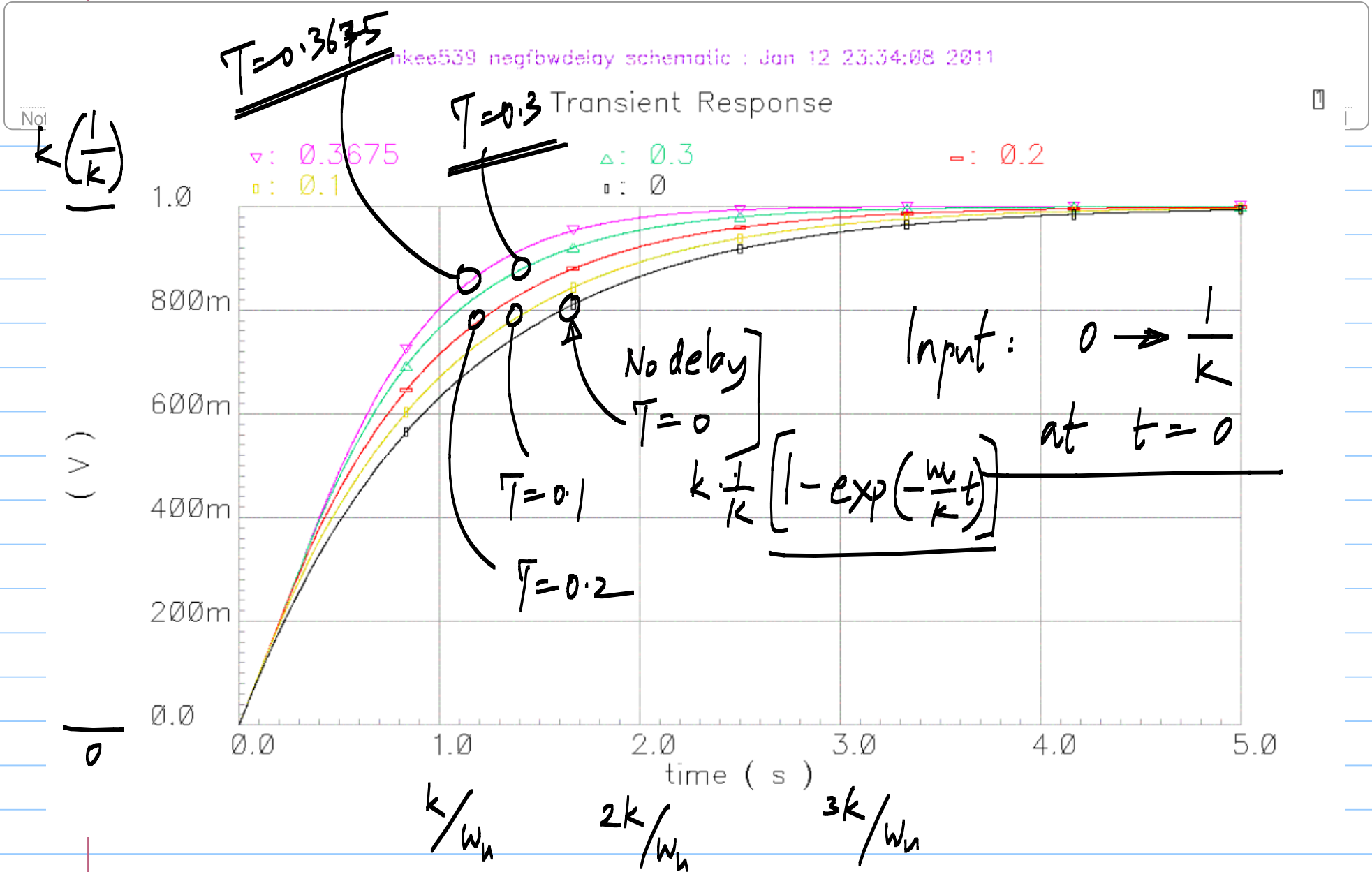

$$\sigma' + \exp(-\sigma'\tau)$$

Substitute

 $\sigma'$ 

$$\frac{d}{d\sigma'}$$




$$1 - \tau \exp(-\sigma'\tau) = 0$$

$$\exp(-\sigma'\tau) = \frac{1}{\tau}$$

$$\sigma'\tau = \ln(\tau)$$

$$\sigma' = \frac{\ln(\tau)}{\tau}$$

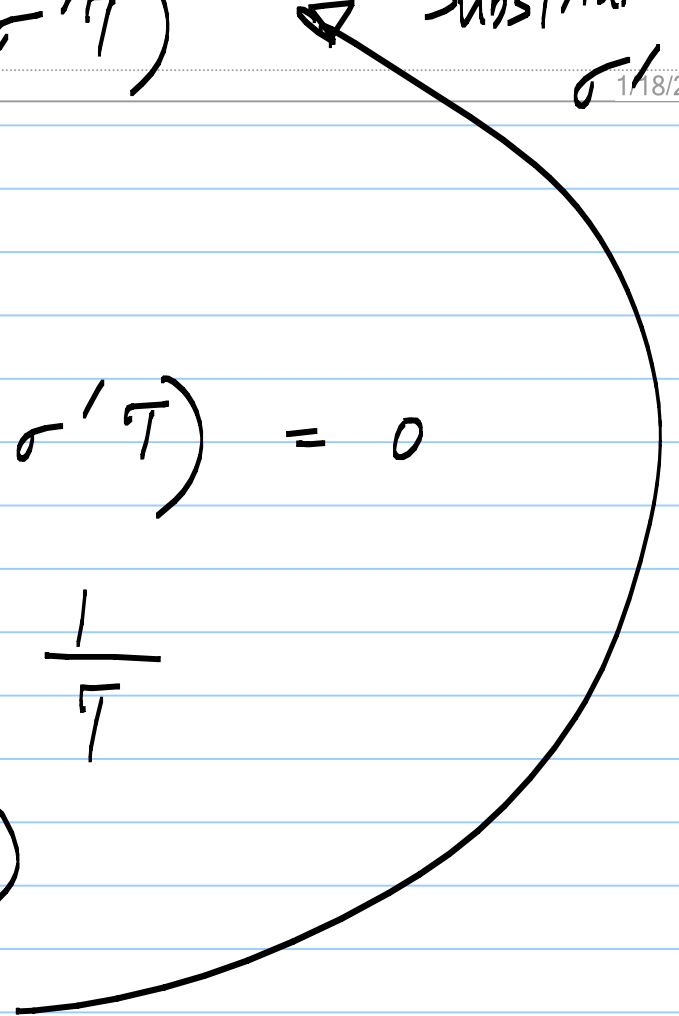



$$\frac{\ln(\tau)}{\tau} + \exp\left(-\frac{\ln(\tau)}{\tau} \cdot \tau\right) = 0$$

$$\frac{\ln(\tau)}{\tau} + \frac{1}{\tau} = 0$$

$$\ln(\tau) = -1$$

$$\tau = \frac{1}{e} = \underline{\underline{0.3675}}$$

$$\boxed{\tau > \frac{1}{e}}$$