
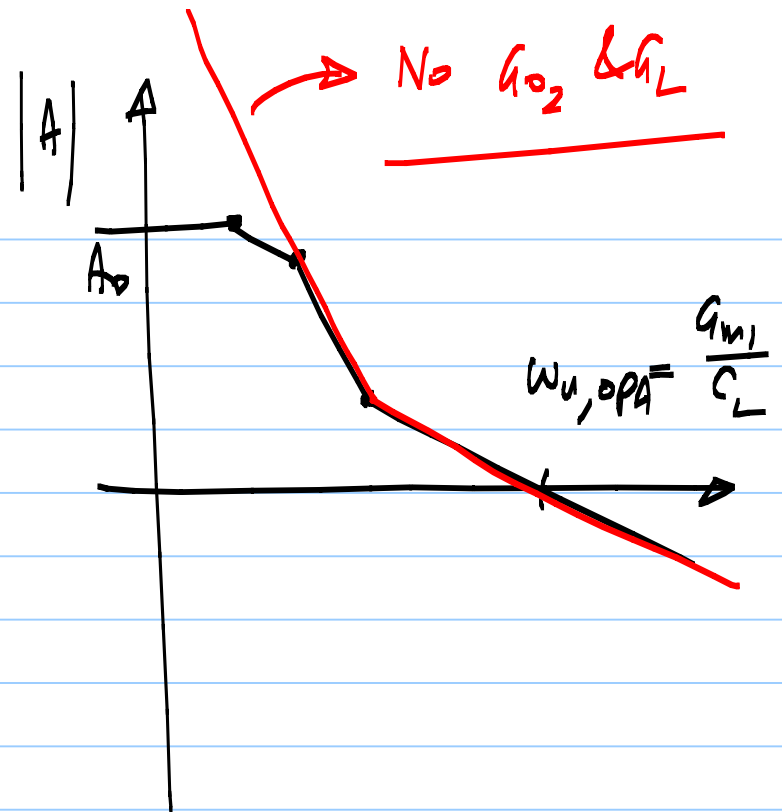



Lecture 18:

Two stage feed forward opamp:

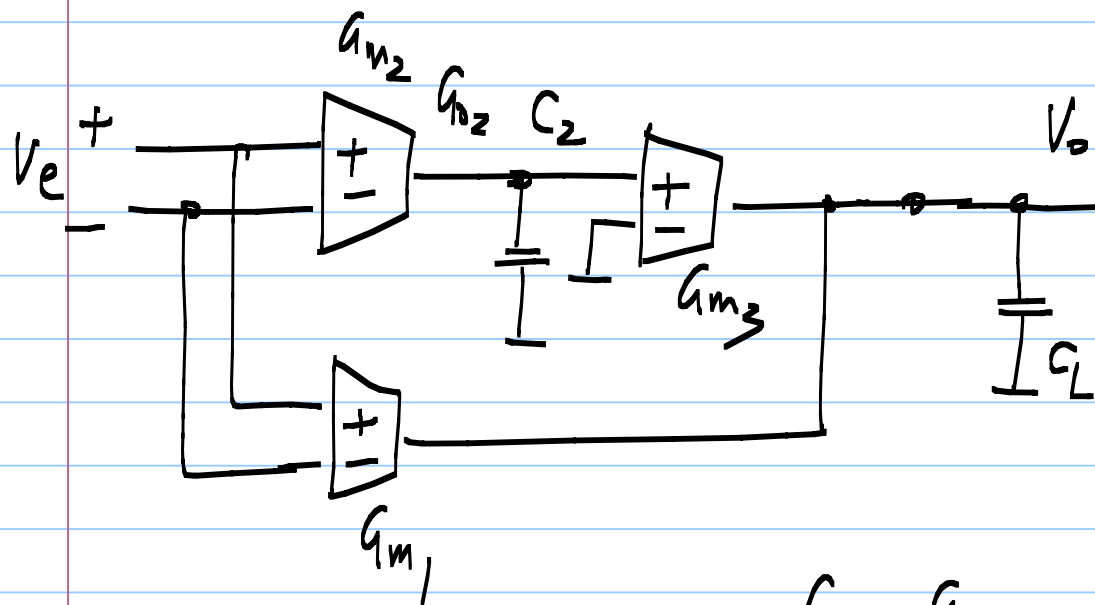

$$\frac{V_o}{V_e} = \frac{G_{m1} + \frac{G_{m2} \cdot G_{m3}}{sC_2}}{sC_L} = \frac{G_{m1}}{sC_L} \left(1 + \frac{G_{m2} G_{m3}}{G_{m1} sC_2} \right)$$
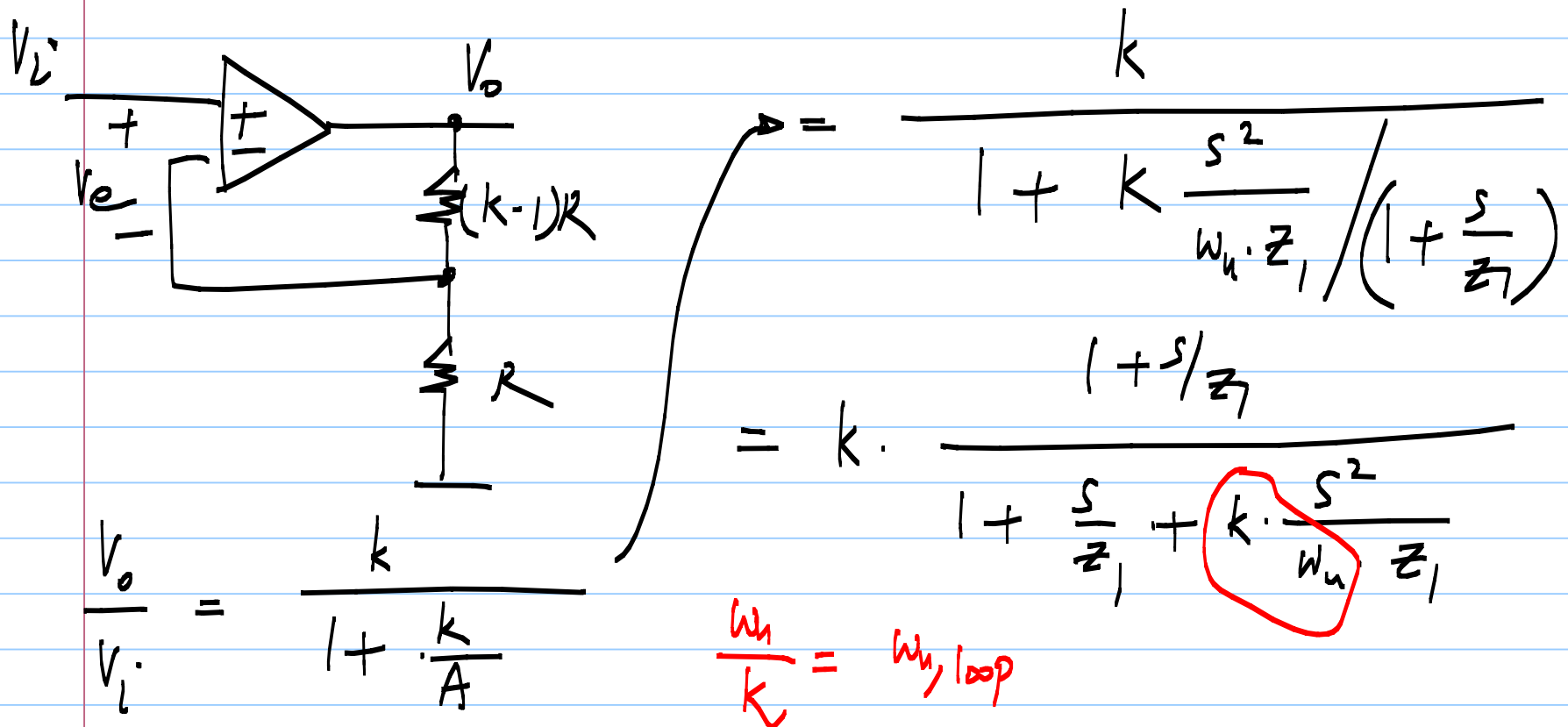
$$A(s) = \frac{V_o}{V_e} = \frac{\omega_u}{s} \left(1 + \frac{z_1}{s} \right) = \frac{\omega_u}{s} \cdot \frac{z_1}{s} \left(1 + \frac{s}{z_1} \right)$$



$$\frac{V_o}{V_e} = k \frac{(1 + s/z_1)}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{n,loop} \cdot z_1}}$$

$$\underbrace{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{n,loop} \cdot z_1}}_{\zeta} = \frac{1/z_1}{2/\sqrt{\omega_{n,loop} z_1}}$$

$$1 + 2\zeta \frac{s}{\omega_n} + \frac{s^2}{\omega_n^2} \quad \omega_n = \sqrt{\omega_{n,loop} z_1}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{n,loop}}{z_1}}$$

Damping factor $\zeta = \frac{1}{2} \sqrt{\frac{\omega_{n,loop}}{z_1}}$


Critical damping $\zeta = 1$, $\boxed{z_1 = \omega_{n,loop}/4}$

$$Z_1 = \frac{G_{m2} G_{m3}}{G_{m1} \cdot C_2} ; \quad \omega_n = \frac{G_{m1}}{C_L} ;$$

$$\omega_{n,loop} = \frac{G_{m1}}{k \cdot C_L}$$

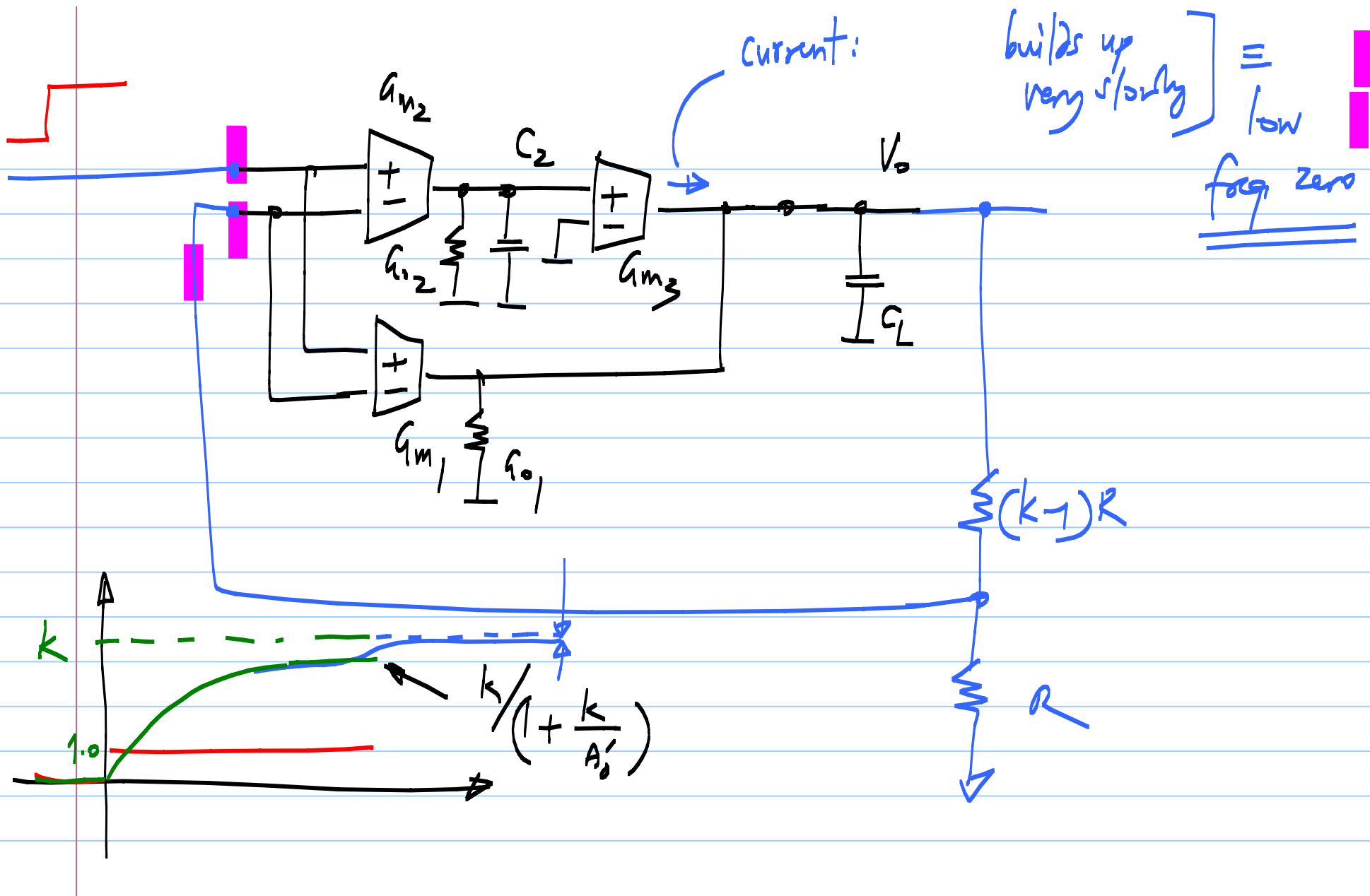Exercise: Evaluate the step response corresponding

$$\frac{V_o}{V_i} = k \cdot \frac{1 + s/z_1}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{n,loop} \cdot z_1}} ; \quad \boxed{\omega_{n,loop} = \frac{\omega_n}{k}}$$



Exercise;

$$\frac{V_o}{V_i} = K \cdot \frac{1 + s/z_1}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{u,loop} \cdot z_1}}$$

$\zeta = 1$
 $z_1 = \frac{\omega_{u,loop}}{4}$
 $p_2 = 4 \cdot \omega_{u,loop}$




$\left. \begin{array}{l} \frac{V_o}{V_i} \\ \text{vs. freq.} \end{array} \right\}$

} different values of z_1


$$\frac{V_o}{V_i} = K \frac{1}{1 + \frac{s}{\omega_{u,loop}} + \frac{s^2}{\omega_{u,loop} \cdot p_2}}$$

} different values of p_2

Single stage:

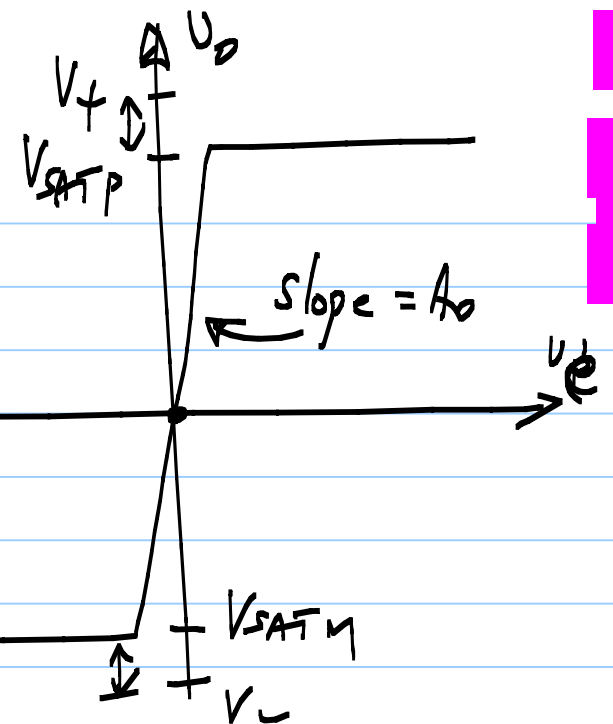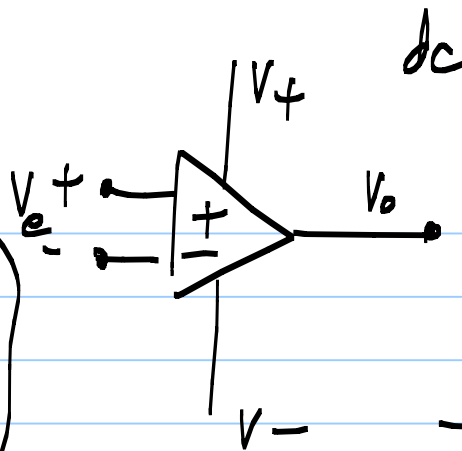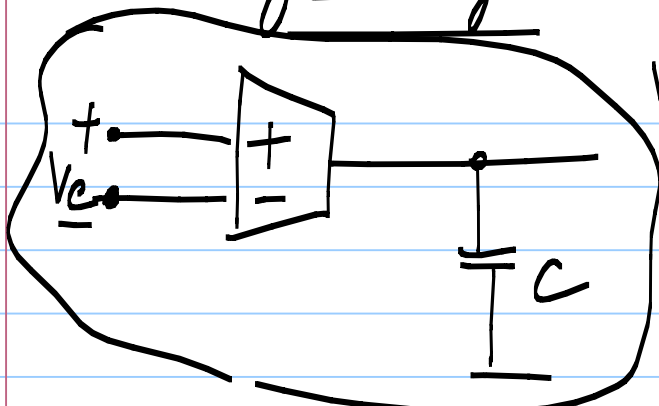


Two stage miller compensated opamp

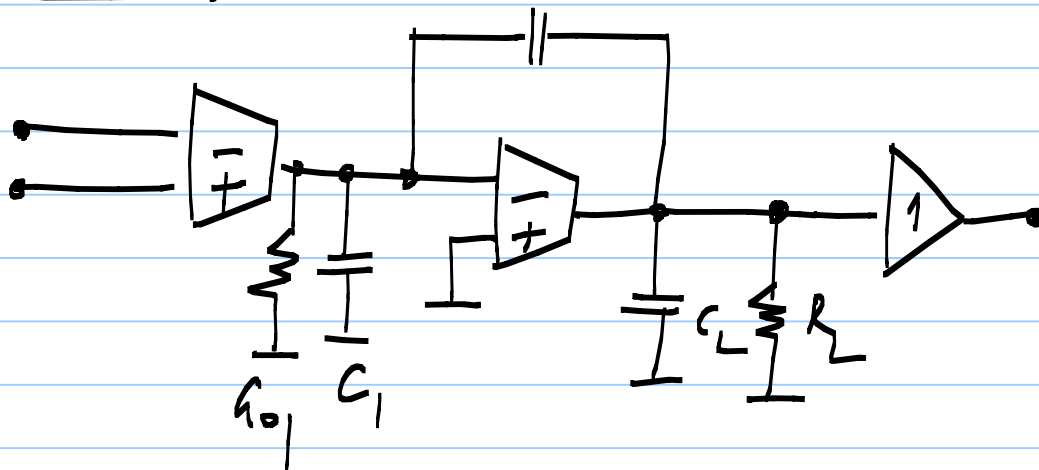

$$V_{SATP} = V_+$$


$$V_{SATM} = V_-$$


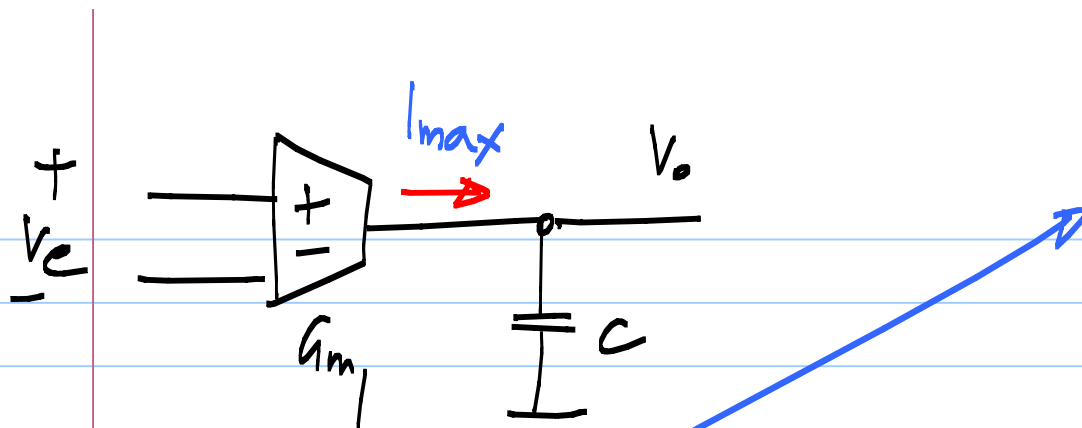


Slew rate limitation:

$$\boxed{\frac{I_{max}}{C}}$$


Max. rate
of change of
 V_o

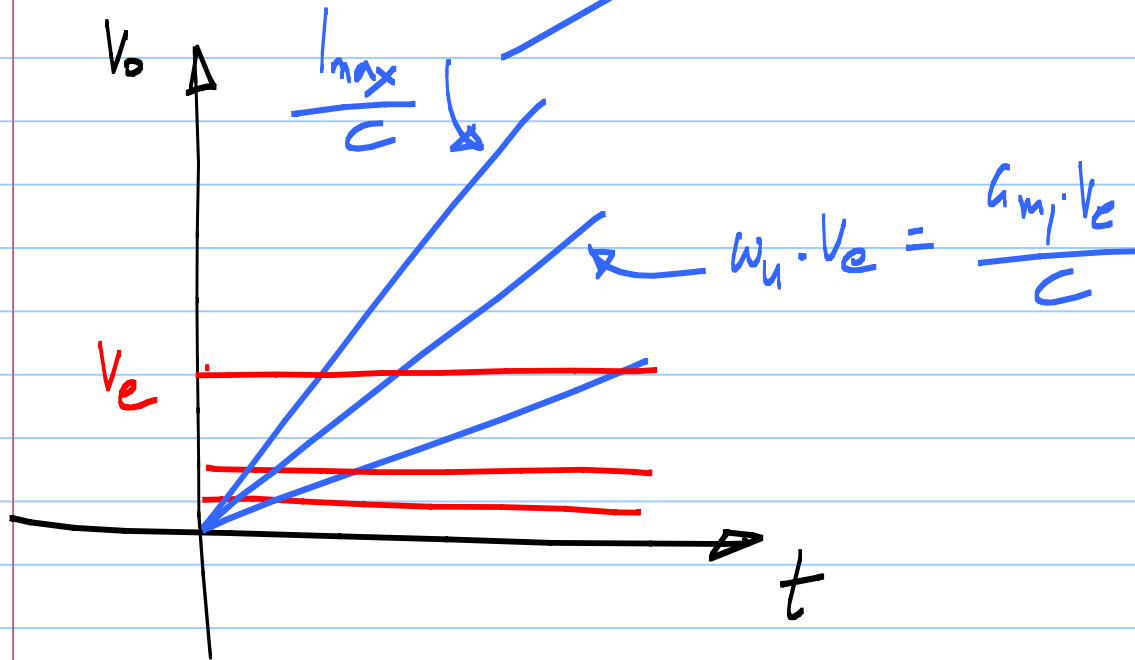

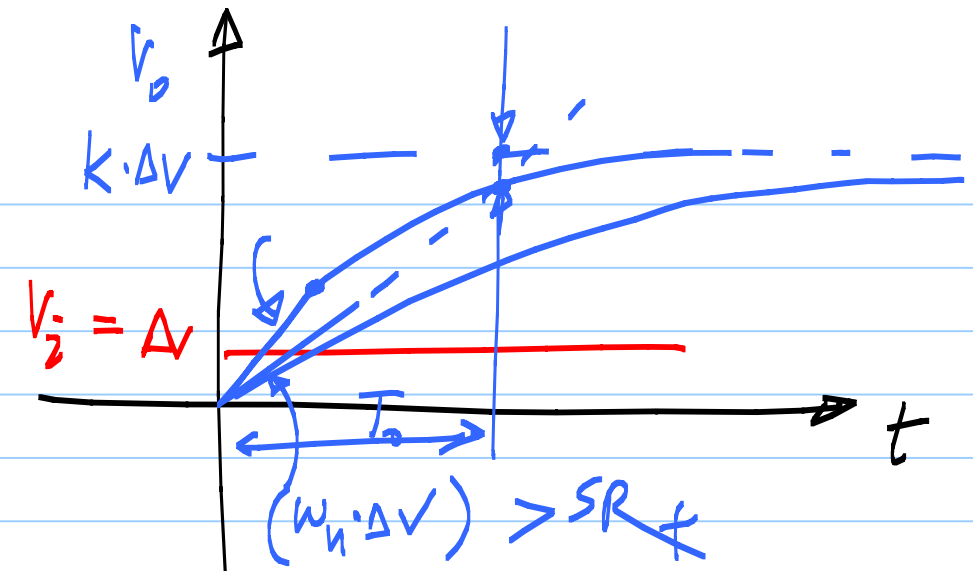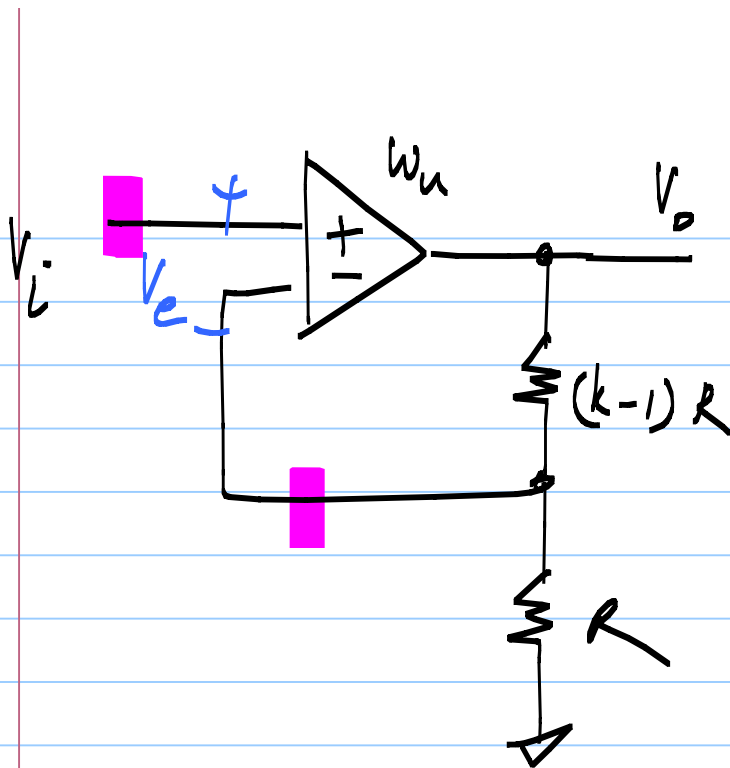

$$V_o = w_u \int (V_e + V_{off-} + V_n) dt$$

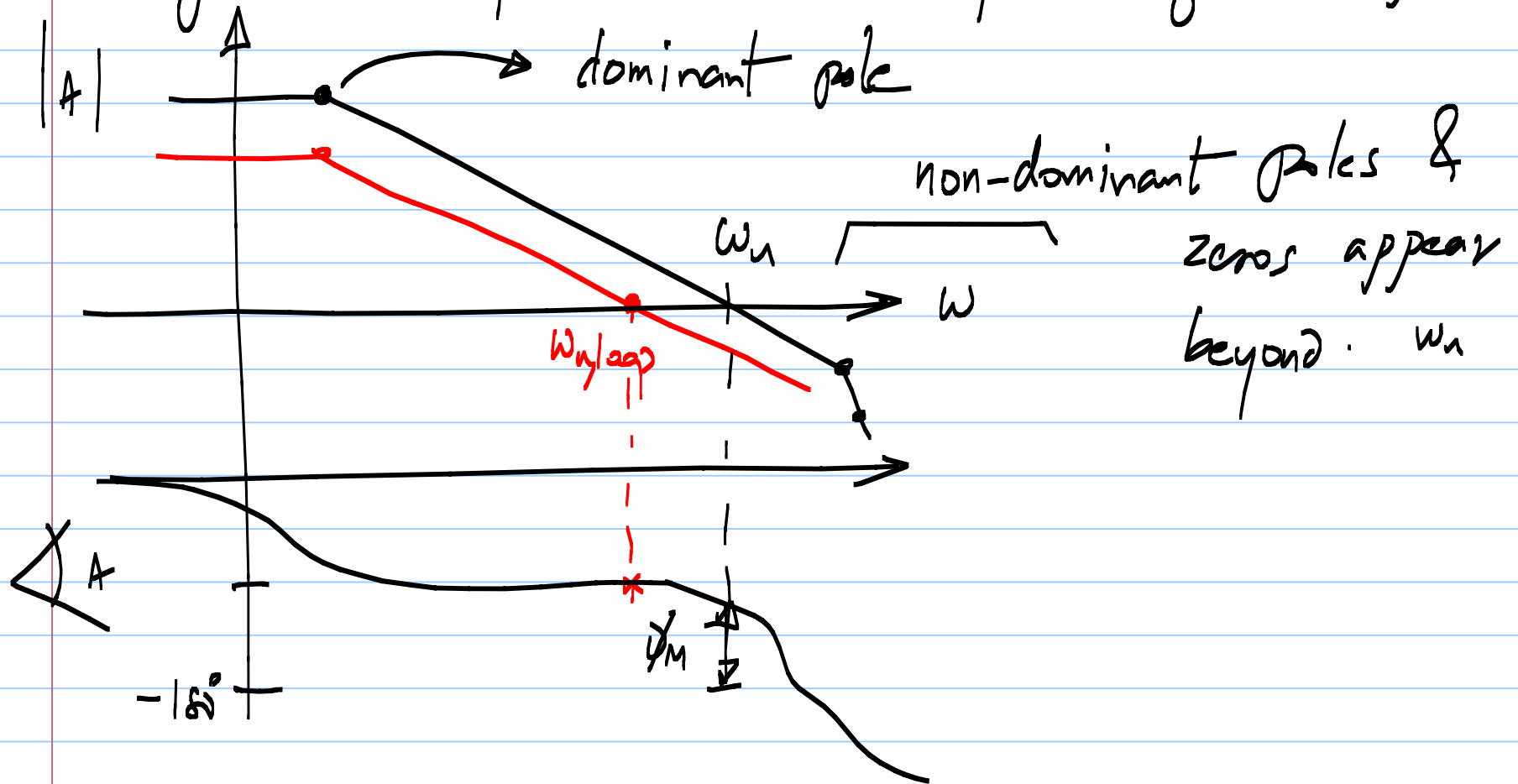Magnitude response & phase response of the opamp



OP amp data sheet:

* dc gain; dc v_o vs. v_e ; saturation voltages
(V_+ , V_-)

* ac magnitude response $\{ |A(j\omega)|, \angle A(j\omega) \}$


* slew rate

* offset & noise voltages


Dominant pole
compensated opamps

* Maximum supply voltage; Maximum load current

Unity gain compensated:

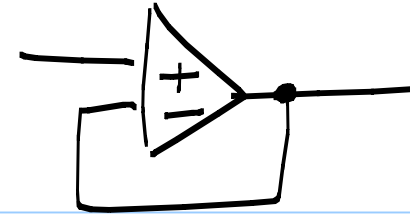

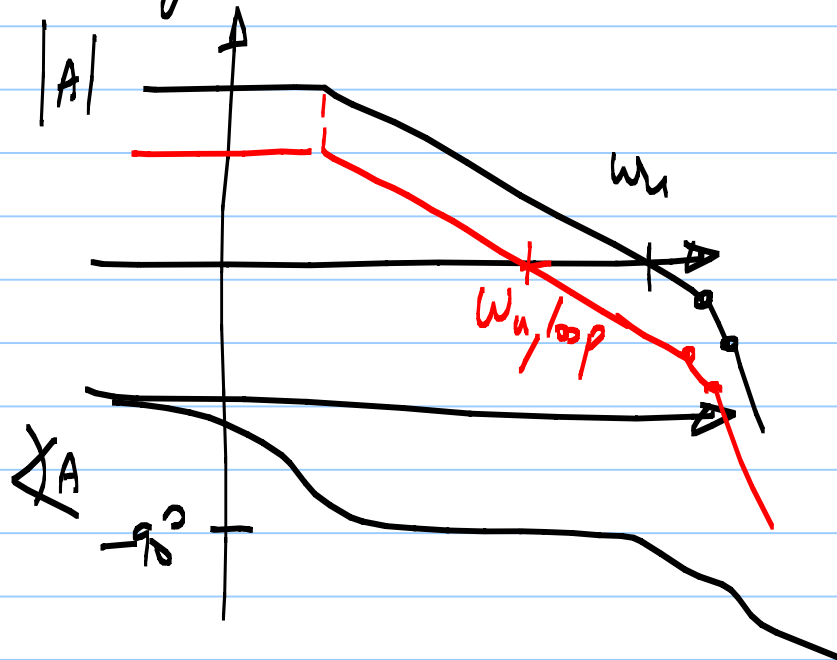* If the opamp is connected in unity negative feedback, it will be stable.



* For any gain $k > 1$ stability is guaranteed.

opamps not unity gain compensated; e.g. OPA657

(Compensated for $k > 10$)

