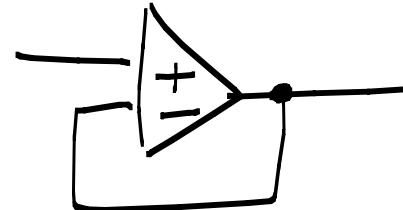


## OP amp data sheet:


- \* dc gain; dc  $V_o$  vs.  $V_e$ ; saturation voltages ( $V_+$ ,  $V_-$ )
- \* ac magnitude response  $\{ |A(j\omega)|, \angle A(j\omega) \}$
- \* slew rate
- \* offset & noise voltages
- \* Maximum supply voltage; Maximum load current

Dominant pole  
(compensated) opamps
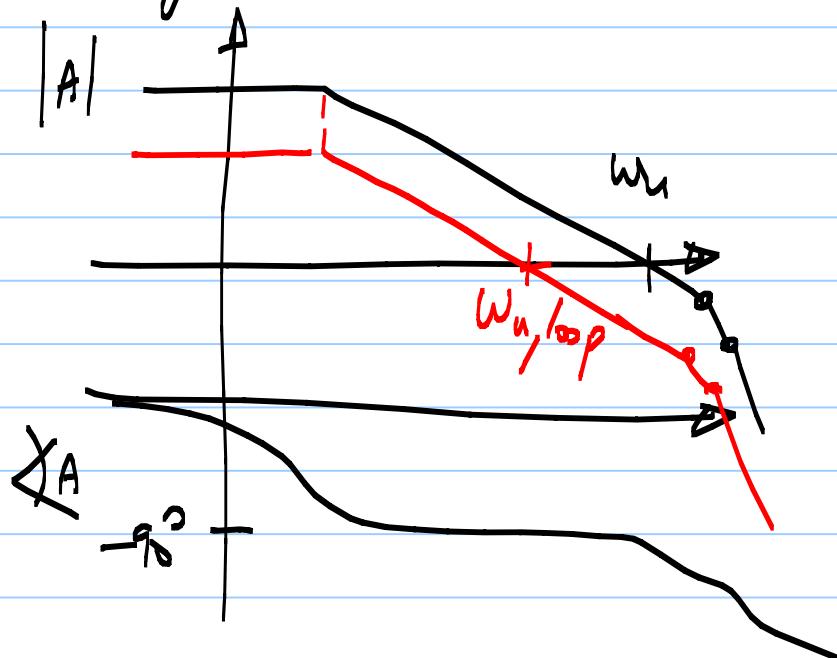
## Unity gain compensated:




- \* If the opamp is connected in unity negative feedback, it will be stable.





- \* For any gain  $k > 1$  stability is guaranteed.

opamps not unity gain compensated: e.g., OPA657



(Compensated fr  $k > 10$ )

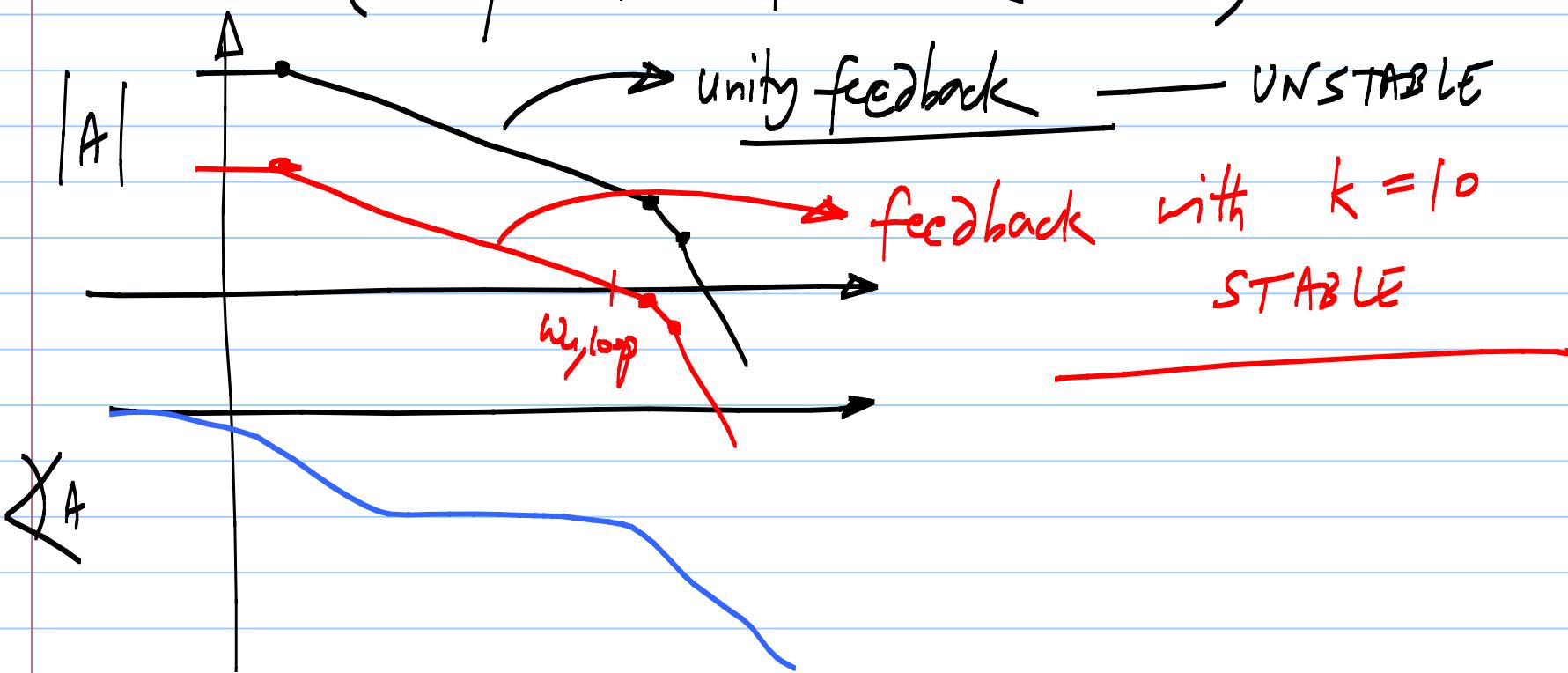

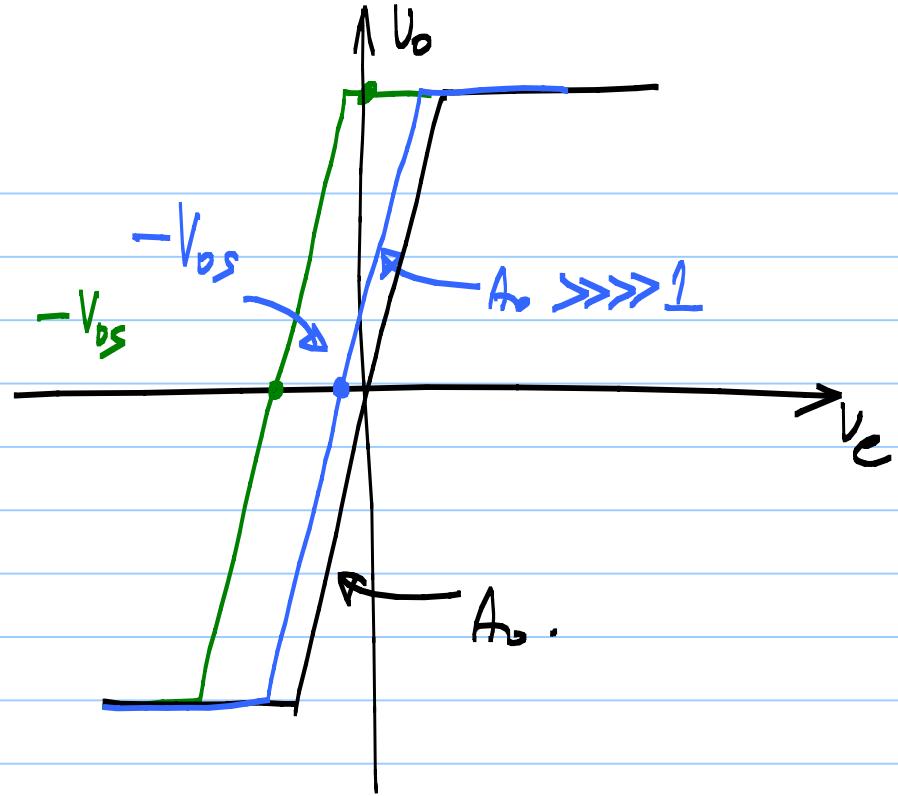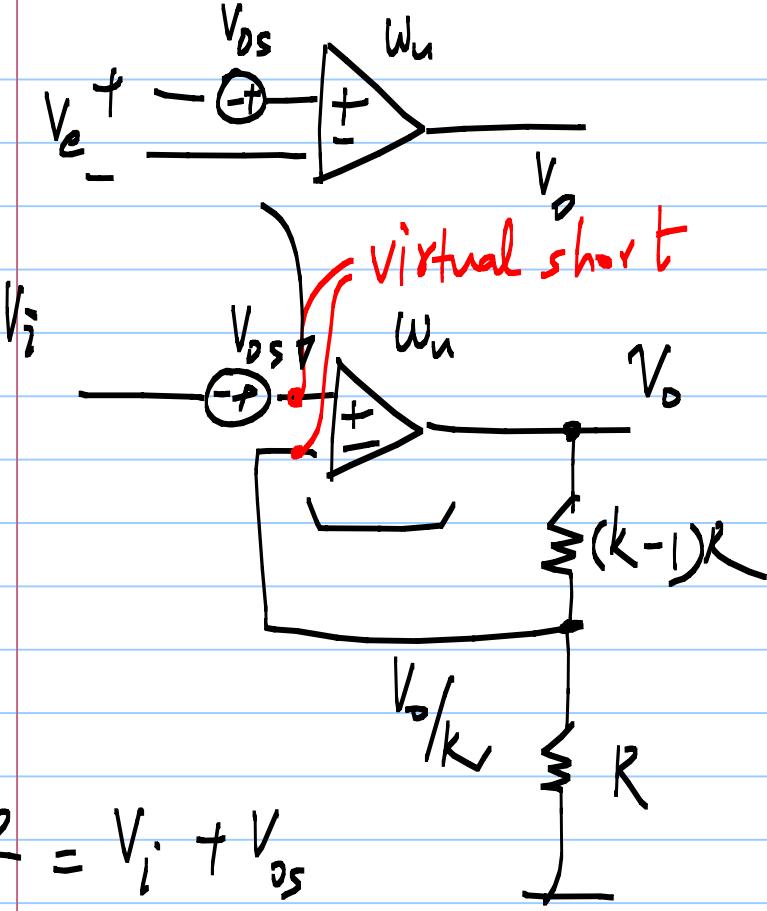

$$v_o = k v_i + k \cdot v_{ds}$$


## Inverting amplifier;

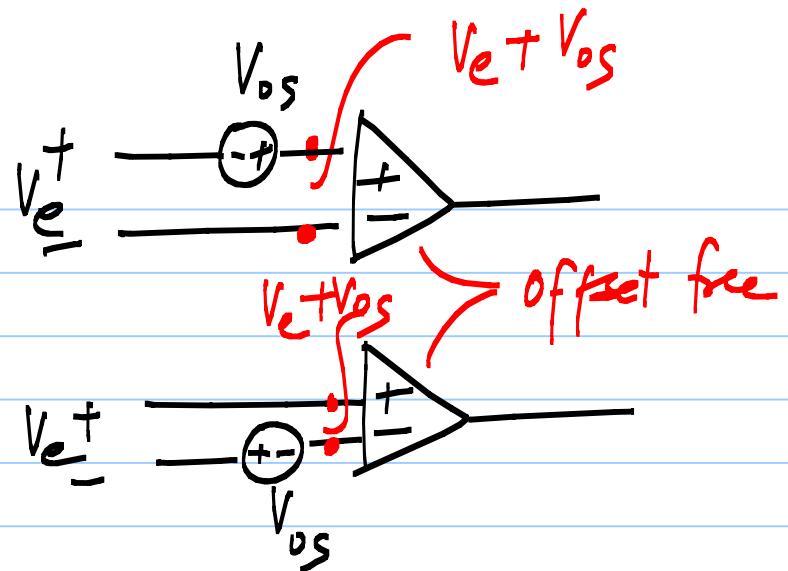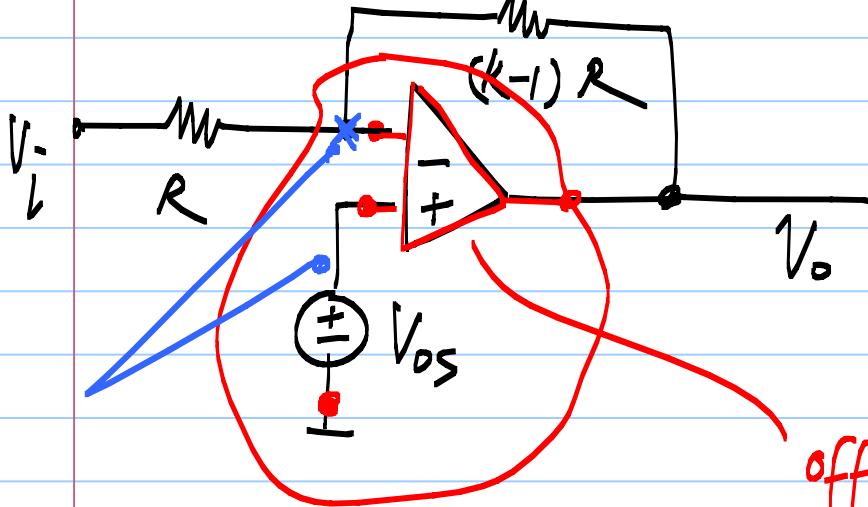

$$V_i \cdot \frac{k-1}{k} + V_o \cdot \frac{1}{k} = V_{os}$$

$$V_o = - (k-1) V_i + k \cdot V_{os}$$

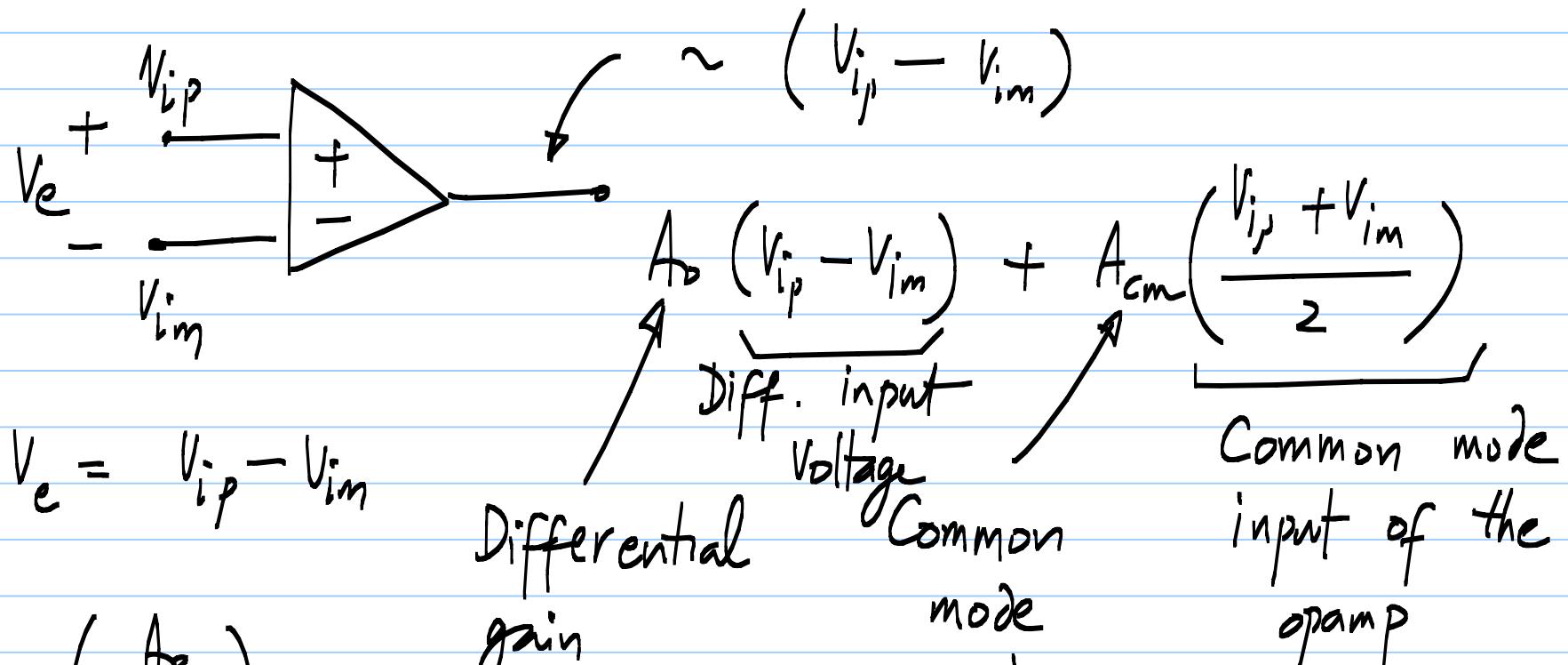Common mode gain — Common mode rejection ratio




$$20 \log_{10} \left( \frac{A_D}{A_{CM}} \right) = 20 \log_{10} \left( \frac{10^3}{0.1} \right) = \underline{\underline{80 \text{dB}}}$$

gain  
mode  
gain

## Effect of non-zero common mode gain $A_{cm}$

Non inverting amp:

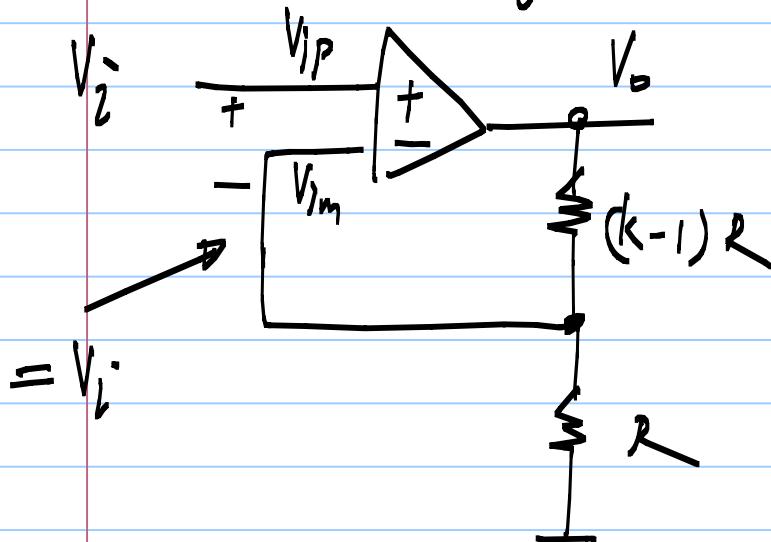

Differential gain is very large

$$V_{ip} = V_i; \quad V_{im} = V_i; \quad V_o = kV_i$$

$$V_o = \underbrace{kV_i}_{\text{ideal}} + \boxed{A_{cm} \cdot V_i}$$


Non (linearly)  
related to  $V_i$

$$V_o = A_v (V_{ip} - V_{im}) + A_{cm} \left( \frac{V_{ip} + V_{im}}{2} \right)$$

$$V_{im} = \frac{V_o}{k} \quad ; \quad V_{ip} = V_i$$

Calculate  $V_o$

## Inverting amplifier:

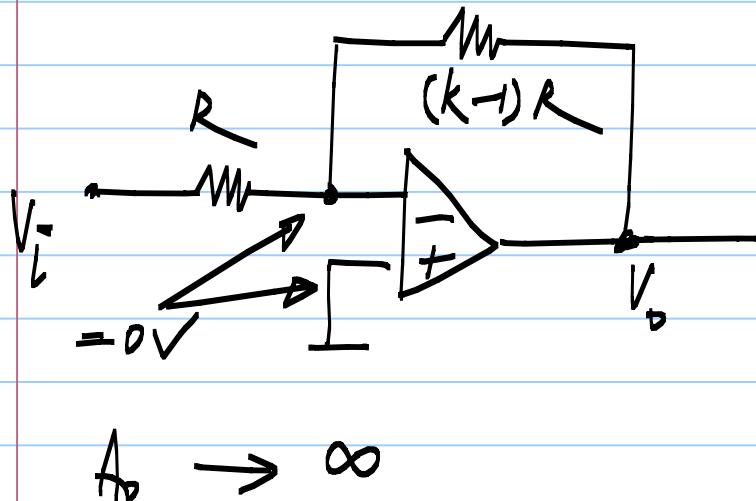

$$\frac{V_{ip} + V_{im}}{2} = 0$$

$\approx$  zero common mode input  
for the opamp.

$$V_o = \underbrace{-(k-1)V_i}_{\text{Ideal}} + \underbrace{A_{cm} = 0}_{\text{Error due to } A_{cm}}$$

## Transimpedance amplifier:


### Photodiode:

$$\text{Circuit Diagram: } \text{A photodiode (represented by a circle with a downward arrow) is connected in series with a current source } I_S \text{ through a resistor } R. \text{ A capacitor } C_S \text{ is connected between the output node and ground.}$$
$$\text{Equation: } V_o = I_s \cdot \frac{R}{C_S + 1/R} = I_s \cdot \frac{R}{1 + S_C R}$$

DC transimpedance :  $R$

Bandwidth :  $\frac{1}{S_C R} > \omega_{BW}$

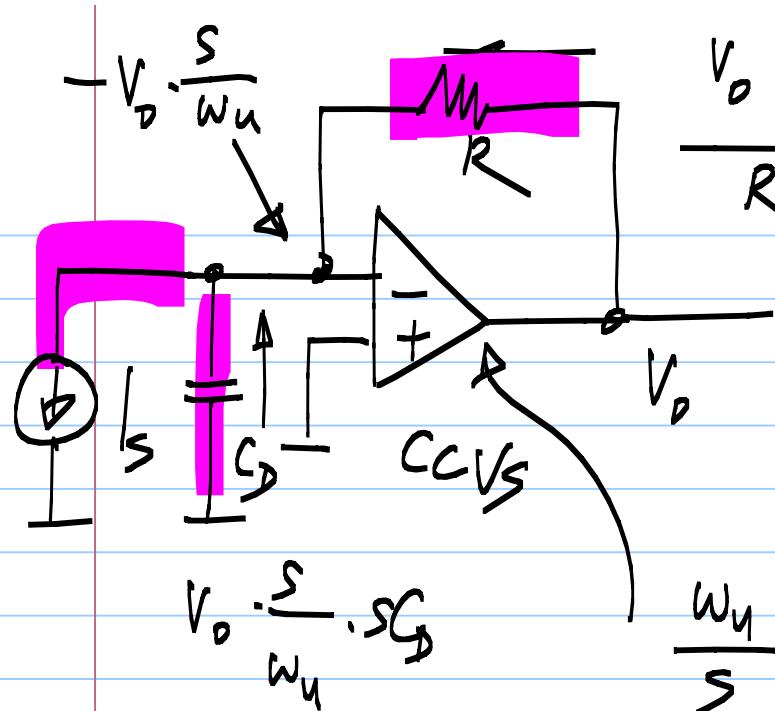For a given bandwidth :  $R$  is fixed.  $R < \frac{1}{S_C \omega_{BW}}$



$$\frac{V_o \left(1 + \frac{s}{\omega_n}\right)}{R}$$

$$I_s = \frac{V_o \left(1 + \frac{s}{\omega_n}\right)}{R} + V_o \cdot \frac{s}{\omega_n} \cdot s C_D$$

$$I_s R = V_o \left(1 + \frac{s}{\omega_n} + \frac{s^2 G_D R}{\omega_n}\right)$$

$$\omega_n = \sqrt{\frac{\omega_n}{G_D R}}$$

$$\frac{V_o}{I_s} = \frac{R}{1 + \frac{s}{\omega_n} + \frac{s^2 G_D R}{\omega_n}}$$

$\underbrace{1 + 2\zeta \frac{s}{\omega_n} + \frac{s^2}{\omega_n^2}}$

$$\frac{2\zeta}{\omega_n} = \frac{1}{\omega_n} \quad \zeta = \frac{1}{2} \frac{\omega_n}{\omega_n}$$

$$= \frac{1}{2} \sqrt{\frac{1}{\omega_n G_D R}}$$

Damping factor:  $\zeta$ ; Quality factor:  $Q$

$$\zeta = \frac{1}{2\varrho} ; Q = \frac{1}{2\zeta}$$

Underdamped system:  $\zeta < 1 ; Q > \frac{1}{2}$

Critically damped:  $\zeta = 1 ; Q = \frac{1}{2}$

Overdamped system:  $\zeta > 1 ; Q < \frac{1}{2}$

$$\frac{V_o}{Is} = \frac{R}{1 + \frac{s}{\omega_n} + \frac{s^2 \zeta R}{\omega_n}}$$

$$\left. \begin{array}{l} \zeta = \frac{1}{\sqrt{2}} \\ \frac{1}{2} \sqrt{\frac{1}{\omega_n \zeta R}} = \frac{1}{\sqrt{2}} \end{array} \right\}$$

$$\omega_n \zeta R = \frac{1}{2} ; \quad \omega_n = \frac{1}{2\zeta R}$$

$$\omega_n = \sqrt{\frac{1}{2\zeta R} \cdot \frac{1}{\zeta R}} = \frac{1}{\sqrt{2} \zeta R}$$

dc gain:  $R$

$$\omega_n = \sqrt{\frac{\omega_n}{\zeta R}}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{1}{\omega_n \zeta R}}$$

$$\frac{V_o}{Is} = \frac{R}{1 + \frac{s}{\omega_n} + \frac{s^2 \zeta R}{\omega_n}}$$

dc gain:  $R$



$$\omega_n = \sqrt{\frac{\omega_n}{\zeta R}}$$

$$\left\{ \right. = \frac{1}{\sqrt{2}} \quad ; \quad \frac{1}{2} \sqrt{\frac{1}{\omega_n \zeta R}} = \frac{1}{\sqrt{2}}$$

$$\left\{ \right. = \frac{1}{2} \sqrt{\frac{1}{\omega_n \zeta R}}$$


$$\omega_n \zeta R = \frac{1}{2} \quad ; \quad \omega_n = \frac{1}{2 \zeta R}$$
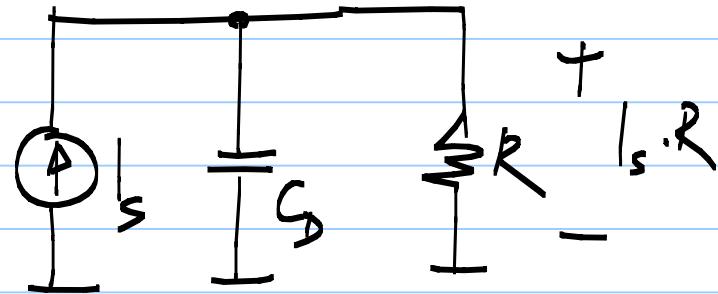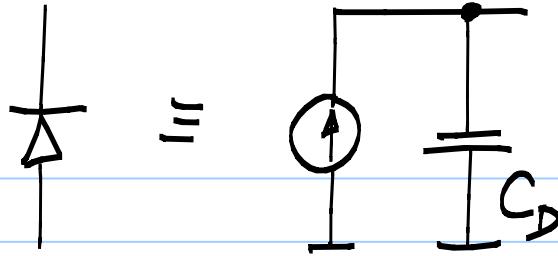
$$\omega_n = \sqrt{\frac{1}{2 \zeta R} \cdot \frac{1}{\zeta R}} = \frac{1}{\sqrt{2} \zeta R}$$



$$\text{DC Gain} : \cdot R$$

$$\text{BW} : \frac{1}{C_D \cdot R}$$

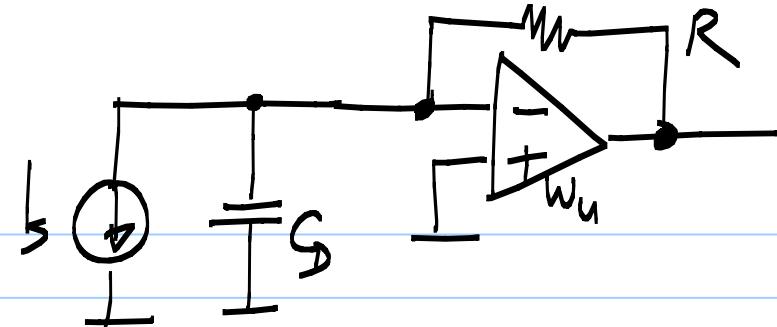


DC gain:  $R$



$$\text{BW: } \frac{1}{\sqrt{2} C_D \cdot R}$$

$$w_u = \frac{1}{2 C D \cdot R}$$

$$\left. \begin{array}{l} \text{ } \\ \text{ } \end{array} \right\} = 1/\sqrt{2}$$

$$\Rightarrow \omega_{-3dB} = w_u$$

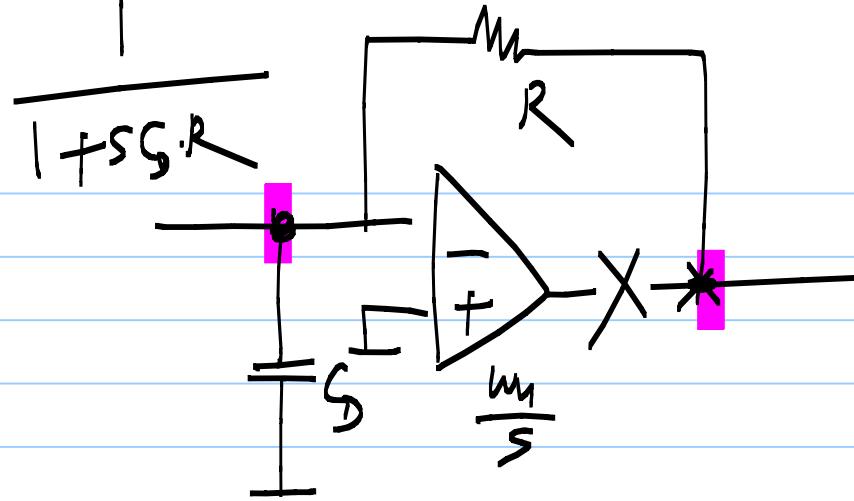

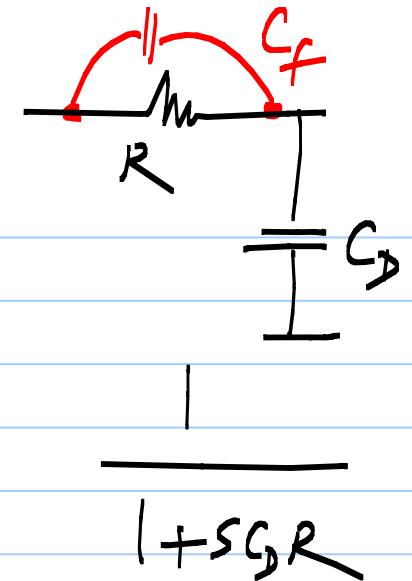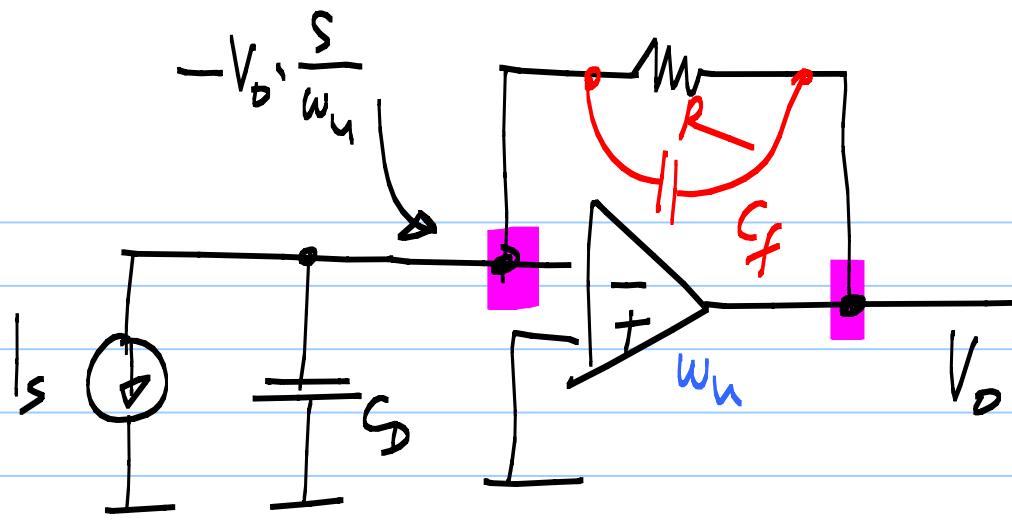

$$-V_o \cdot \frac{s}{w_n} (sC_f + \zeta + sC_D) - V_o (sC_f + \zeta) = I_s$$

$$\frac{V_o}{I_s} = \frac{R_f}{s^2 (C_D + C_f) R_f + s \left( \frac{1}{w_n} + C_f R_f \right) + 1}$$

$$\frac{1 + sC_f R}{1 + s(C_f + C_D)R}$$

$$\omega_n = \sqrt{\frac{\omega_u}{(\zeta + \zeta_f)R}}$$

$$\zeta = \frac{1}{\sqrt{2}}$$

$$w_{3dB} = \omega_n$$

$$\frac{2 \cdot \zeta}{\omega_n} = \frac{1}{\omega_u} + \zeta_f \cdot R$$

$$\left( \zeta_f R \right)^2 = \frac{2 \cdot G R \omega_n - 1}{\omega_n^2}$$

$$\sqrt{2} \cdot \sqrt{\frac{(\zeta + \zeta_f)R}{\omega_n}} = \frac{1}{\omega_u} + \zeta_f R$$

$$2 \cdot \frac{(\zeta + \zeta_f)R}{\omega_n} = \frac{1}{\omega_u^2} + \frac{2 \cdot \zeta_f R}{\omega_n} + (\zeta_f R)^2$$

$$\omega_{-3dB} = \omega_n$$

$$(\zeta_f \cdot R)^2 = \frac{2C_D \cdot R \cdot \omega_n - 1}{\omega_n^2}$$

$$= \sqrt{\frac{\omega_n}{\zeta_f \cdot R + \zeta_f \cdot R}}$$

$$= \sqrt{\frac{\omega_n}{\zeta_f \cdot R + \frac{\sqrt{2\zeta_f R \omega_n - 1}}{\omega_n}}} = \sqrt{\frac{\omega_n \cdot \zeta_f R + \sqrt{2\zeta_f R \omega_n - 1}}{\omega_n}}$$

$$\omega_{-3dB} = \sqrt{\omega_n \zeta_f R + \sqrt{2\zeta_f R \omega_n - 1}}$$

