
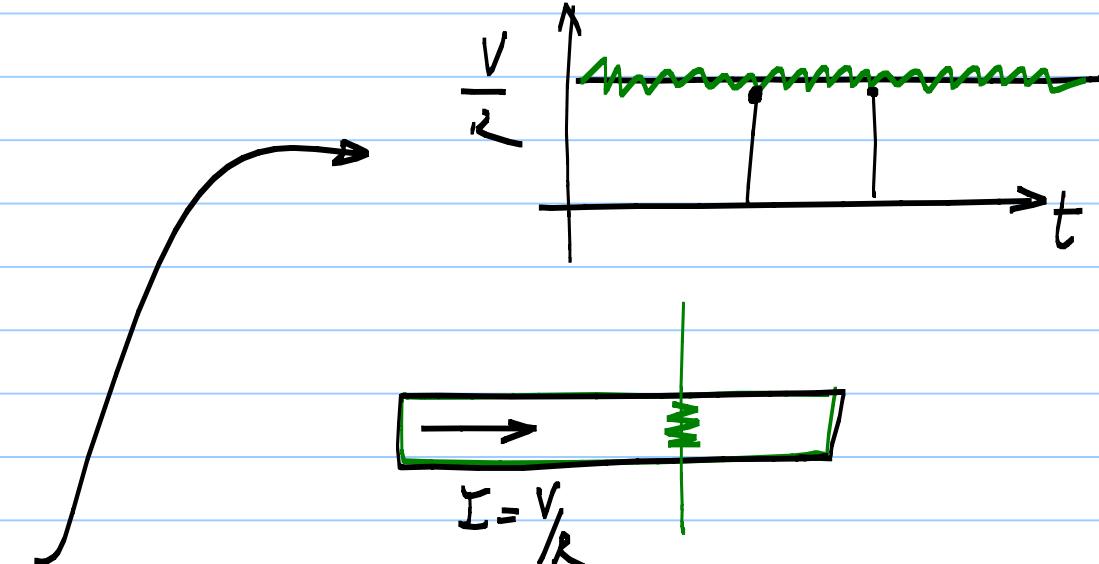
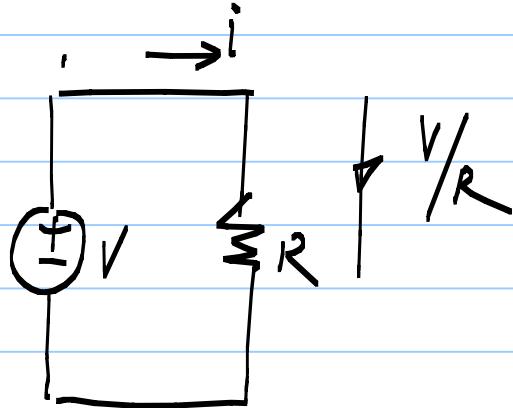


## Lecture 24


### Resistor noise

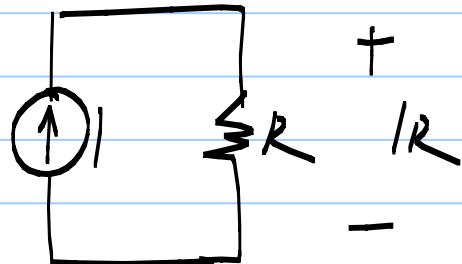


- \* Uncorrelated from one resistor to another
- \* Uncorrelated from one time instant to another

\* Power spectral density - distribution over frequency

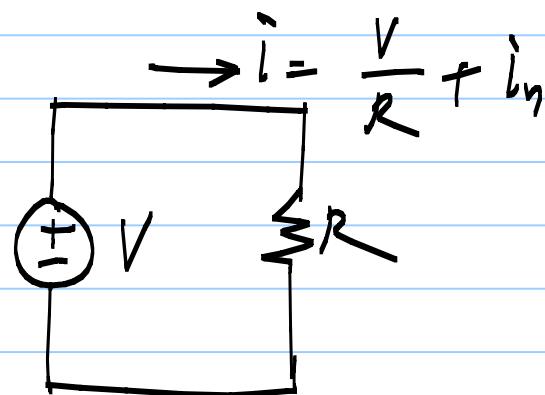
\* Mean squared value ] Variance  
(root mean square<sup>2</sup>) ] standard deviation




=

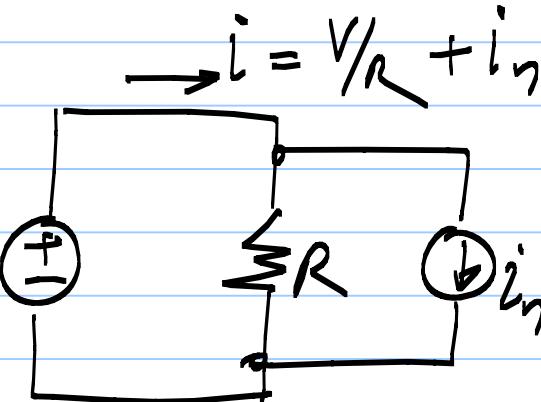

Noiseless

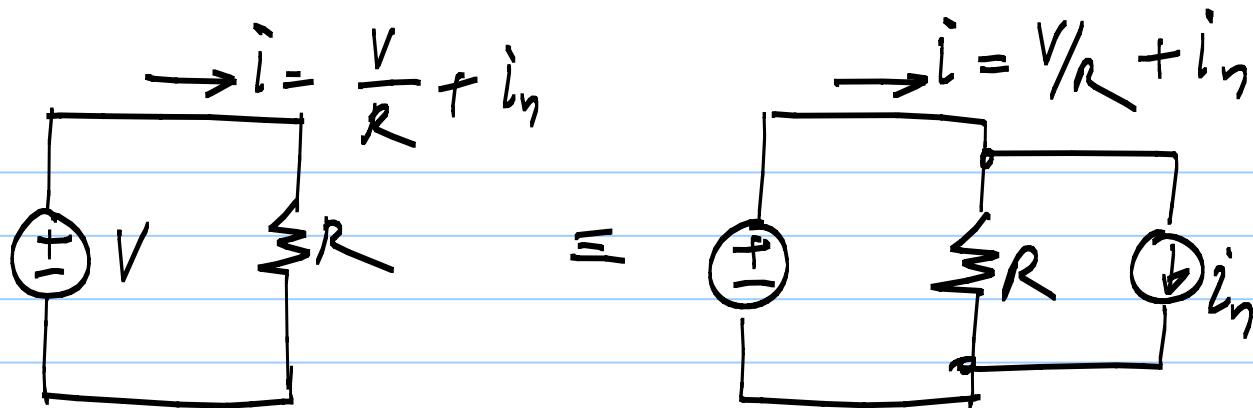


Noiseless


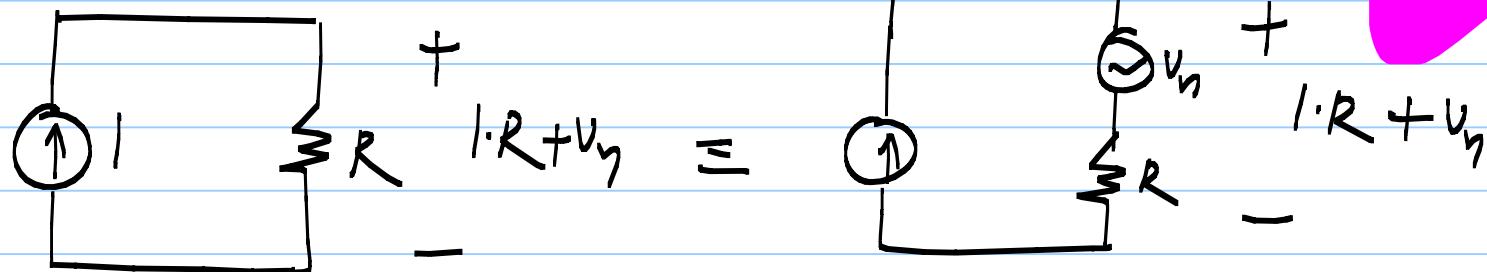


Noiseless


$$i_n \cdot R = v_n$$

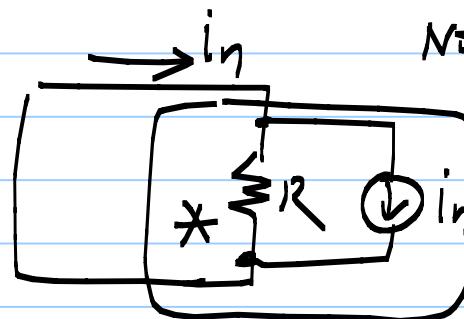

$$i_n \cdot R = v_n$$

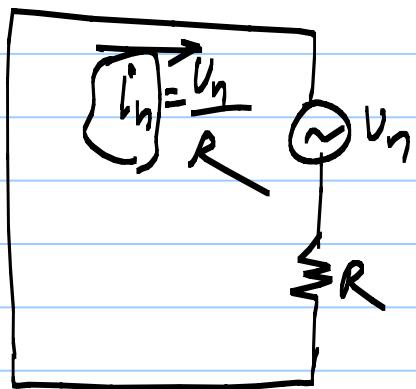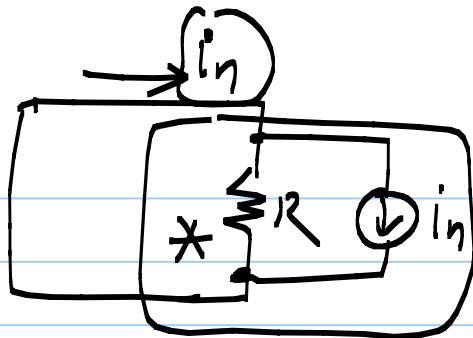

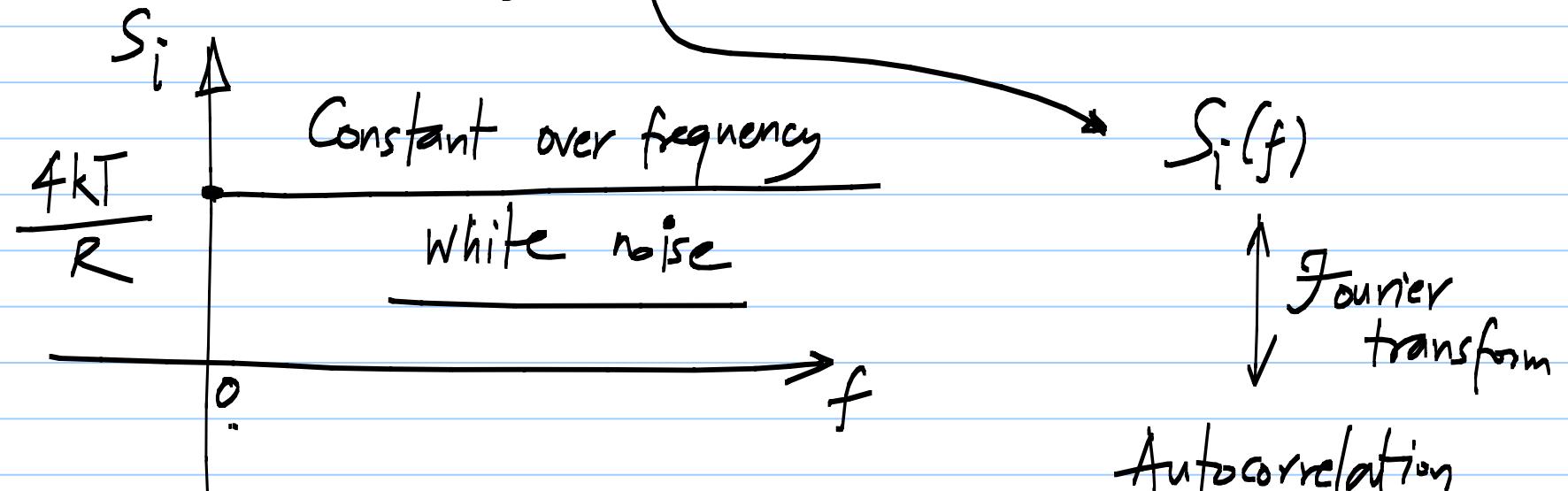Spectral density of  $i_n, v_n$  {noise in a resistor  $R$ }



$k$ : Boltzmann's constant


$$1.38 \times 10^{-23} \text{ J/K}$$

$T$ : Absolute temp. 300 K

$$\int_0^{\infty} S_i(f) df = \text{Variance} [v^2]$$

$$v_h = i_h \cdot R$$
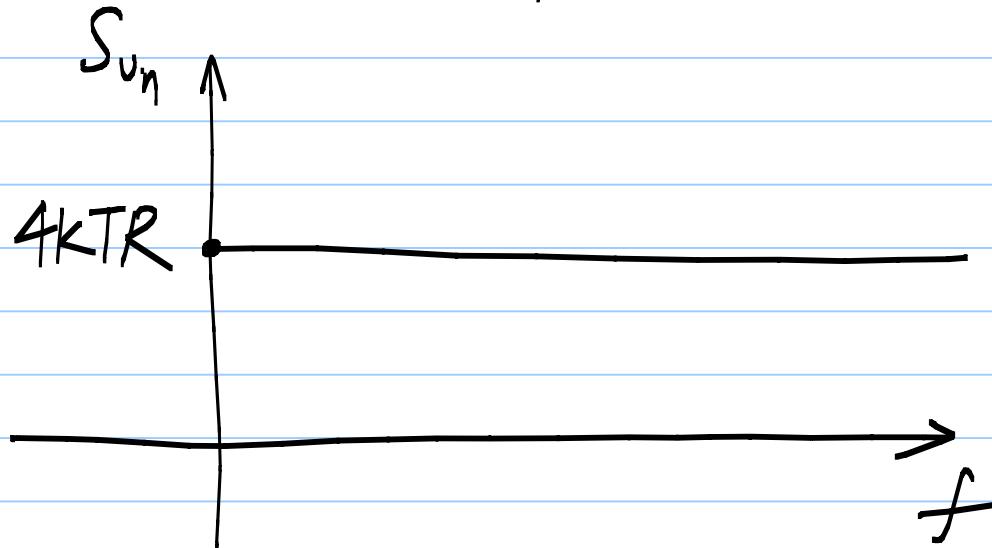
$$S_{v_h} = S_{\psi_h} \cdot R^2 = \frac{4kT}{R} \cdot R^2 = 4kT \cdot R$$



$$kT = 4 \times 10^{-21} \text{ J}$$

@ 300K

$$R = 1k\Omega$$

$$4 \times 4 \times 10^{-21} \text{ J} \times 10^3 \Omega \\ = 16 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$S_i = \frac{4kT}{R} A^2/\text{Hz}; S_v = 4kT \cdot R \frac{V^2}{\text{Hz}}$$

For a  $1\text{k}\Omega$  resistor  $S_i = 16 \times 10^{-24} A^2/\text{Hz}$   $S_v = 16 \times 10^{-18} \frac{V^2}{\text{Hz}}$




$$(4kT \cdot R) \cdot B = \text{Variance of } v_o$$

$$1 \text{ k}\Omega \text{ resistor: } S_v = 16 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$1 \text{ MHz BW: } B = 10^6 \text{ Hz}$$

$$\underline{S_v \cdot B} = 16 \times 10^{-12} \text{ V}^2 = \sigma_{v_o}^2$$
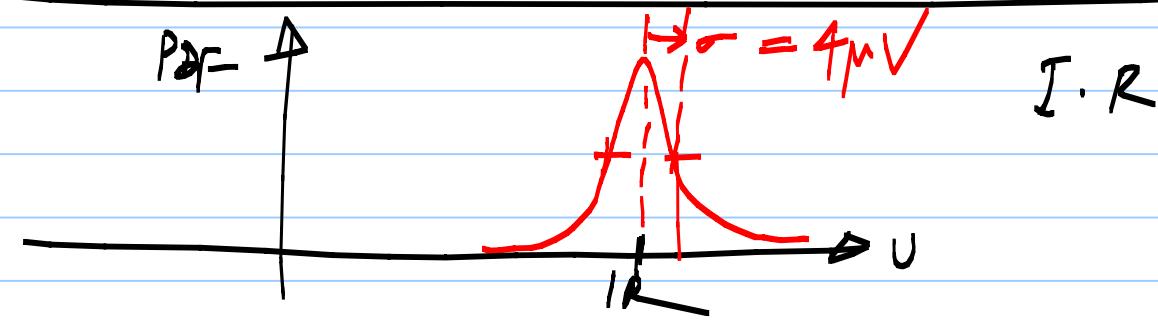
$$\boxed{\sigma_{v_o} = \sqrt{S_v \cdot B} = 4 \times 10^{-6} \text{ V} = 4 \mu\text{V}}$$



$$S_V = 4kTR \frac{V^2}{Hz} = \sqrt{4kTR} \frac{V}{\sqrt{Hz}}$$

$|k_2|:$


$$16 \times 10^{-18} \frac{V^2}{Hz} = 4 \times 10^{-9} \frac{V}{\sqrt{Hz}}$$

$|MHz\ BW$

$$= 4nV/\sqrt{Hz}$$

$$4nV/\sqrt{Hz} \cdot \sqrt{|MHz\ BW|} = 4nV$$
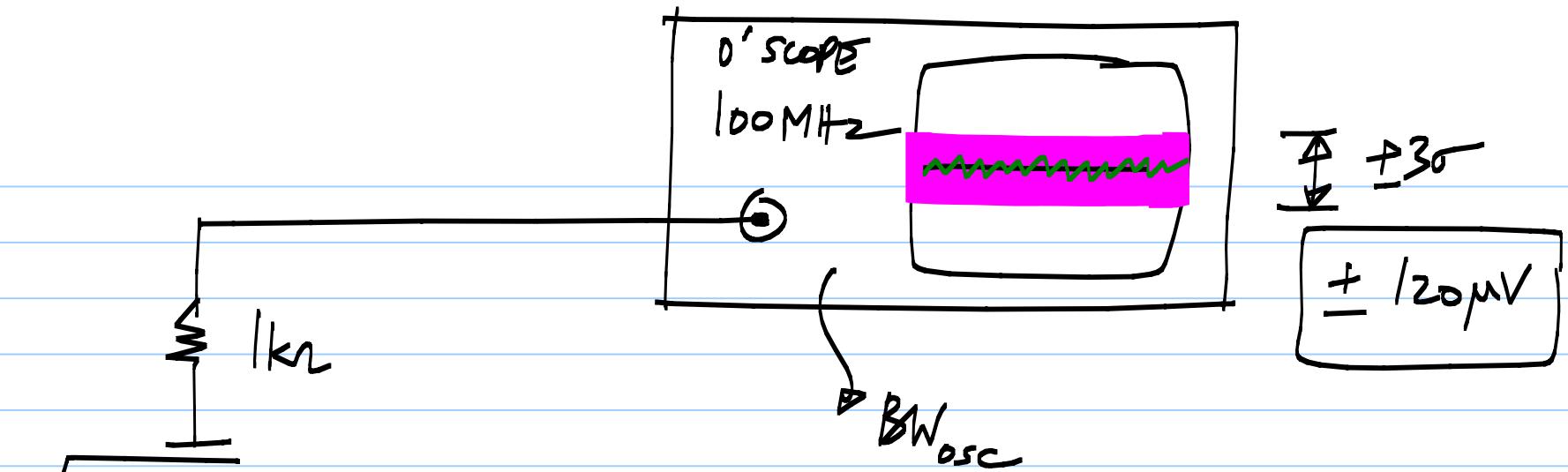
$$S_i = \frac{4kT}{R} \frac{A^2}{Hz} = \sqrt{\frac{4kT}{R}} \frac{A}{\sqrt{Hz}}$$



$$\sqrt{\overline{V_n^2}} = \sqrt{4kT R \cdot BW_{osc}}$$


$$16 \times 10^{-18} \frac{V^2}{Hz} \times 10^8 \text{ Hz}$$

$$\overline{V_n^2} = 4kT \cdot R \cdot BW_{osc}$$

$$= 16 \times 10^{-10} V^2 = \overline{V_n^2}$$

$$40 \mu V = \sqrt{\overline{V_n^2}}$$


$$S_{v_i} = \sqrt{V_n}$$

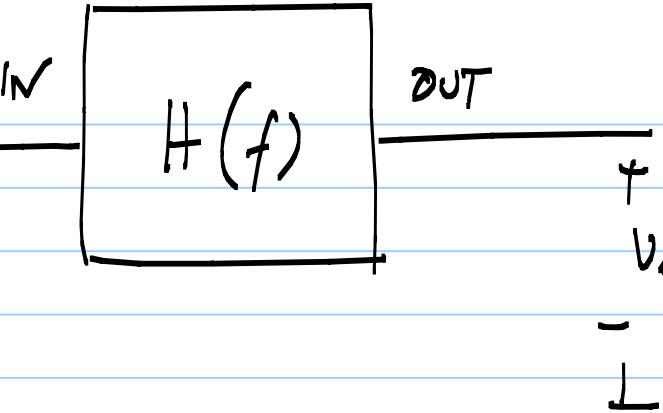

$$S_{v_o} = S_{v_i} |H(f)|^2$$


$$\int_{-\infty}^{\infty} S_{v_o}(f) \cdot df$$

$$S_{v_i} = 4kTR$$

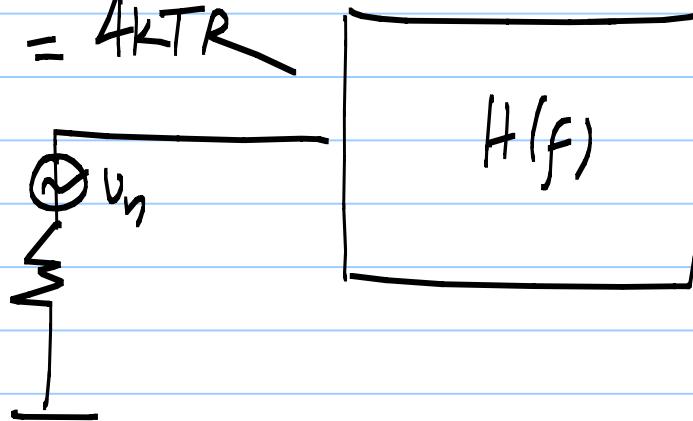



$$S_{v_o} = 4kTR |H(f)|^2$$

$$\sqrt{V_o^2} = 4kTR \int_0^{\infty} |H(f)|^2 \cdot df$$



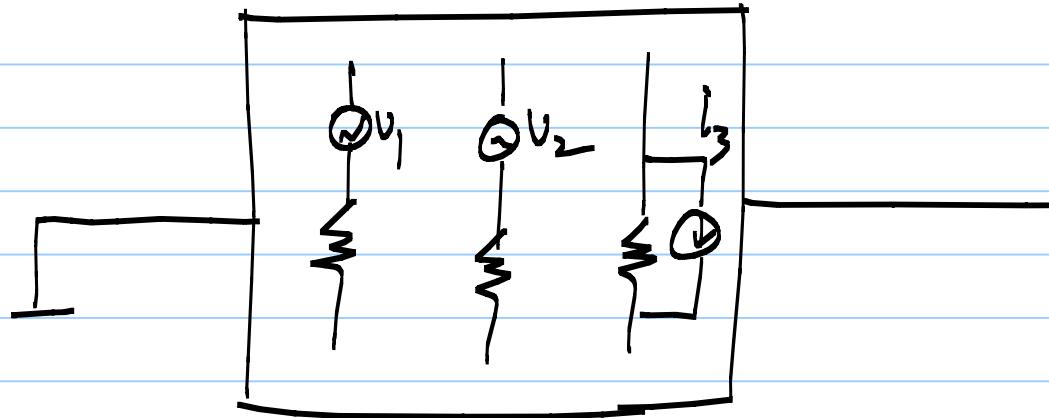


$$V_o = V_1 \cdot H_1(f) + V_2 \cdot H_2(f) + I_3 \cdot H_3(f) + \dots$$

$$S_{V_o} = S_{V_1} |H_1(f)|^2 + S_{V_2} |H_2(f)|^2 + S_{I_3} |H_3(f)|^2 + \dots$$

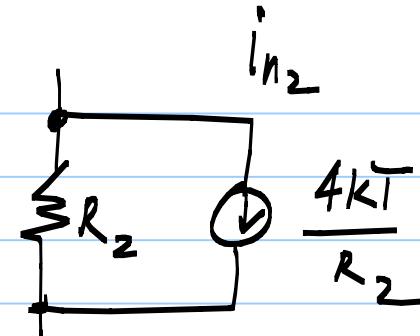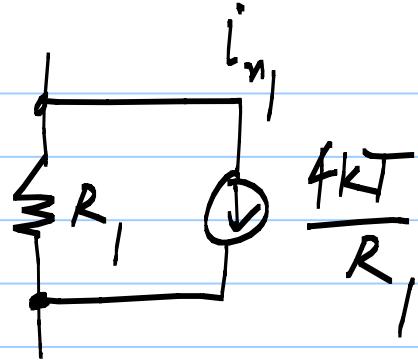

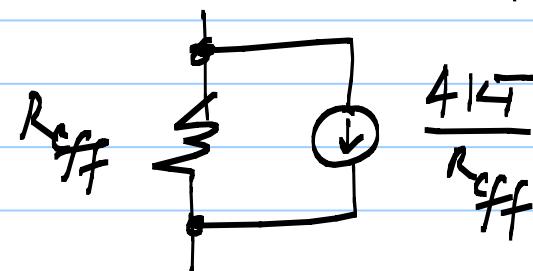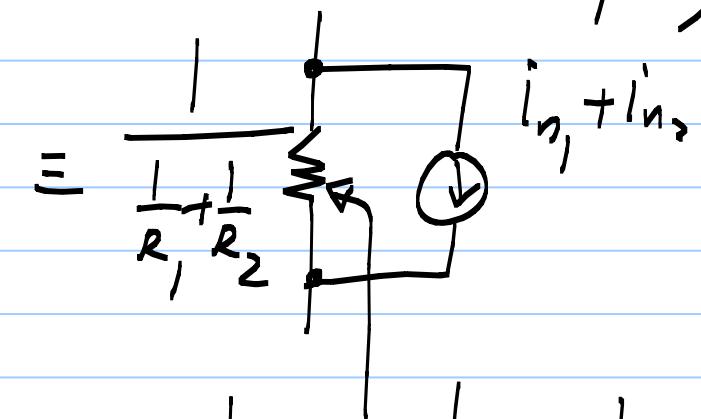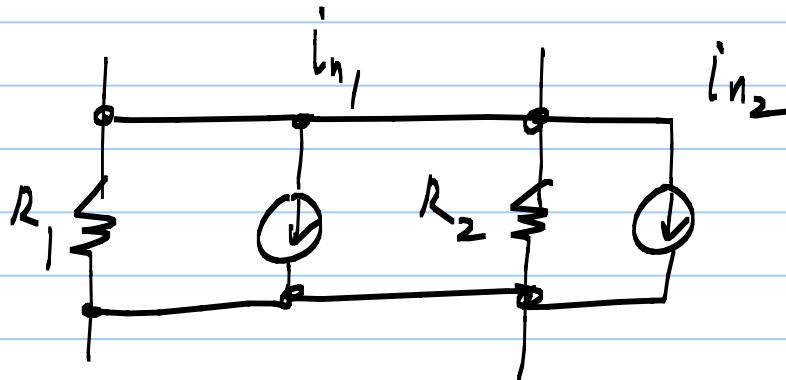
$$4kT \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$




$$\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2}$$

## First order RC lowpass filter:

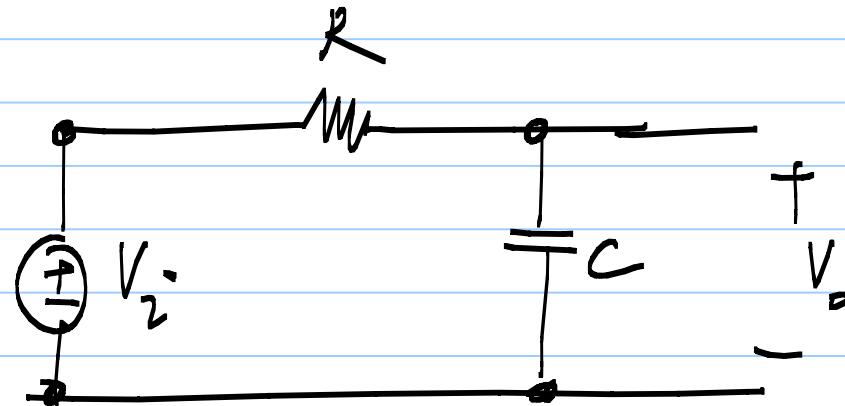
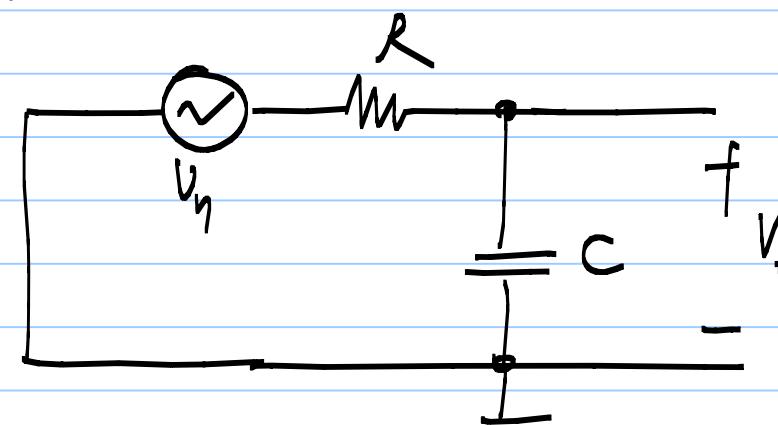
$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sCR}$$



$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sCR}$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{1 + j\omega CR}$$

$$S_{V_o} = S_{V_n} \cdot |H(f)|^2$$


$$\frac{1}{1 + j \frac{2\pi f C R}{}}$$

$$= \frac{4kTR}{1 + \frac{4\pi^2 f^2 C^2 R^2}{}}$$

$$f = \frac{1}{2\pi C R}$$

$$\overline{V_n^2} = \int_{0}^{\infty} S_{V_o} \cdot df$$


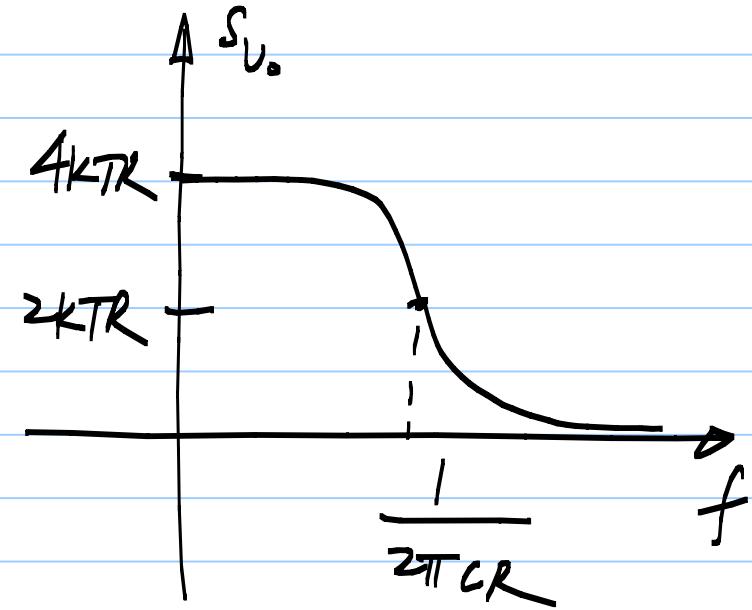
$$= \int_{0}^{\infty} \frac{4kTR}{1 + \frac{4\pi^2 f^2 C^2 R^2}{}} df$$



$$\int_0^{\infty} \frac{4kTR}{1 + 4\pi^2 f^2 C^2 R^2} df = 4kTR \cdot \left[ \frac{1}{2\pi CR} \cdot \tan^{-1}(2\pi f CR) \right]_{f=0}^{f=\infty}$$

$$= 4kTR \cdot \frac{1}{2\pi CR} \cdot \frac{\pi}{2} = \frac{kT}{C}$$

$$\boxed{\bar{U}_q^2 = \frac{kT}{C}}$$

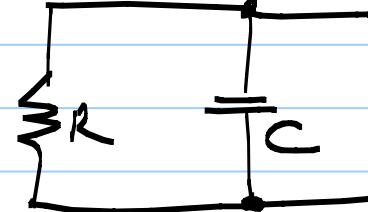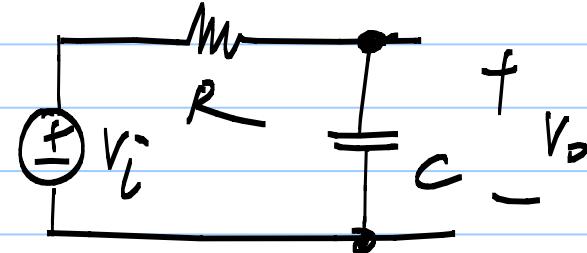

$$\frac{1}{V_1^2} = \frac{kT}{C}$$

$$C = 10 \text{ pF}$$


$$R = 100 \text{ k}\Omega$$

$$16 \times 10^{-16} V^2/\text{Hz}$$

$$\frac{1}{2\pi CR} = \frac{1}{2\pi \cdot 10^{-11} \cdot 10^5} = \frac{10^6}{2\pi} \text{ Hz}$$


$$R = 200 \text{ k}\Omega$$
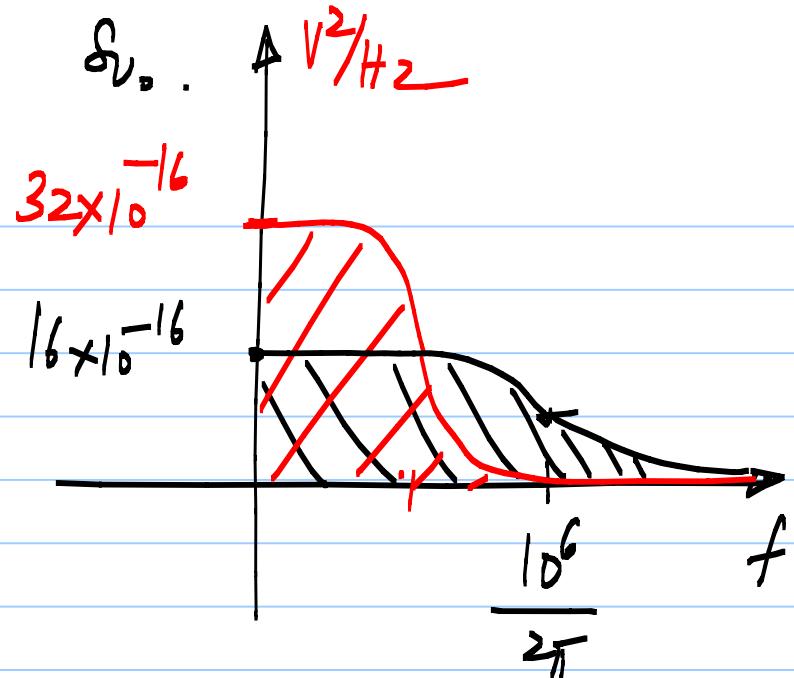
$$\frac{1}{2\pi CR} = \frac{10^6}{4\pi} \text{ Hz}$$



Equipartition theorem:

Each degree of freedom:  $\frac{kT}{2}$

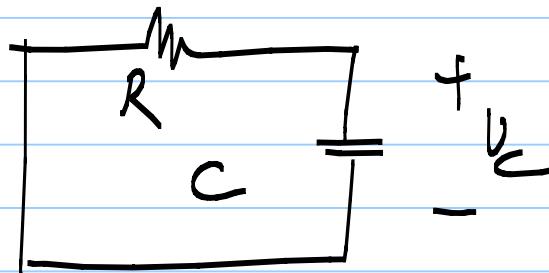

$$\frac{1}{2} C \bar{v_c^2} = \frac{kT}{2}$$
$$\boxed{\bar{v_c^2} = \frac{kT}{C}}$$

---

$$S_{v_n} = 4kTR \quad \text{for all frequencies}$$

$$kT \longleftrightarrow$$

$$\frac{hv}{\left[ \exp\left(\frac{hv}{kT}\right) - 1 \right]}$$