
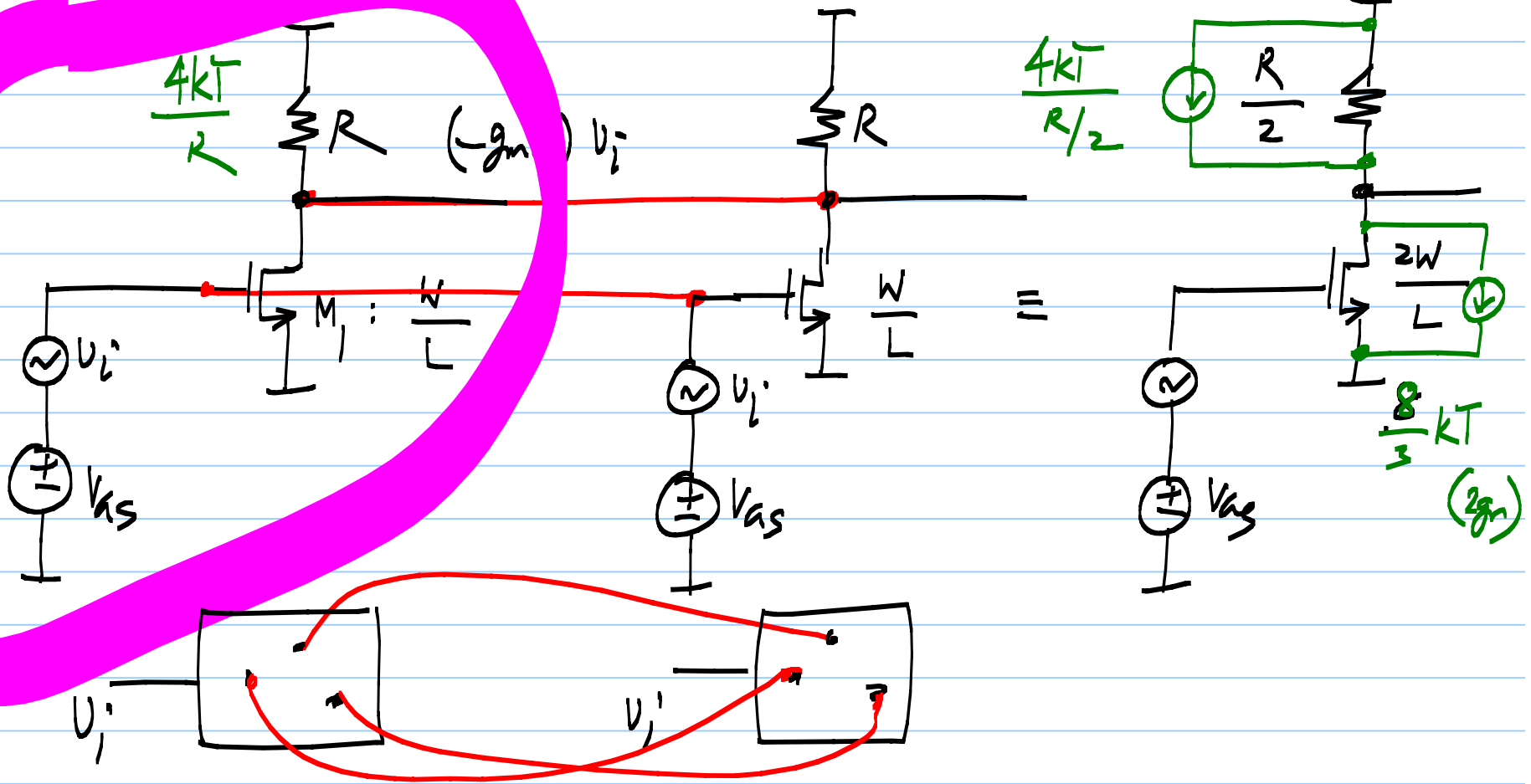


Lecture 26


Noise scaling

gain: $(-g_m R)$

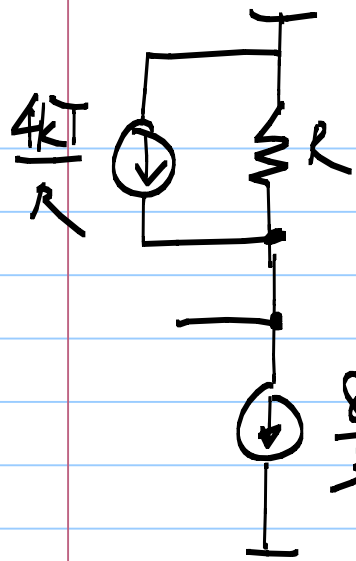





$$4kTR + \frac{8}{3}kT \cdot g_m R^2$$

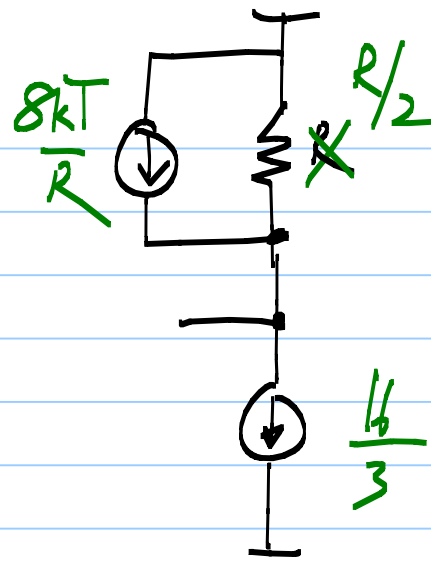
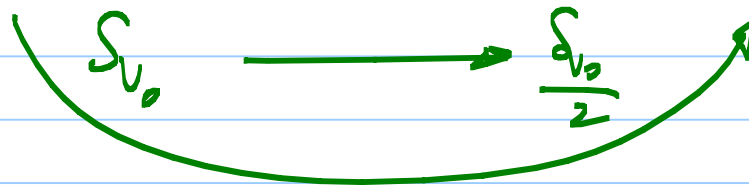
$$\frac{4kTR}{2} + \frac{8}{3}kT \cdot \frac{g_m R^2}{2}$$



Noise scaling:

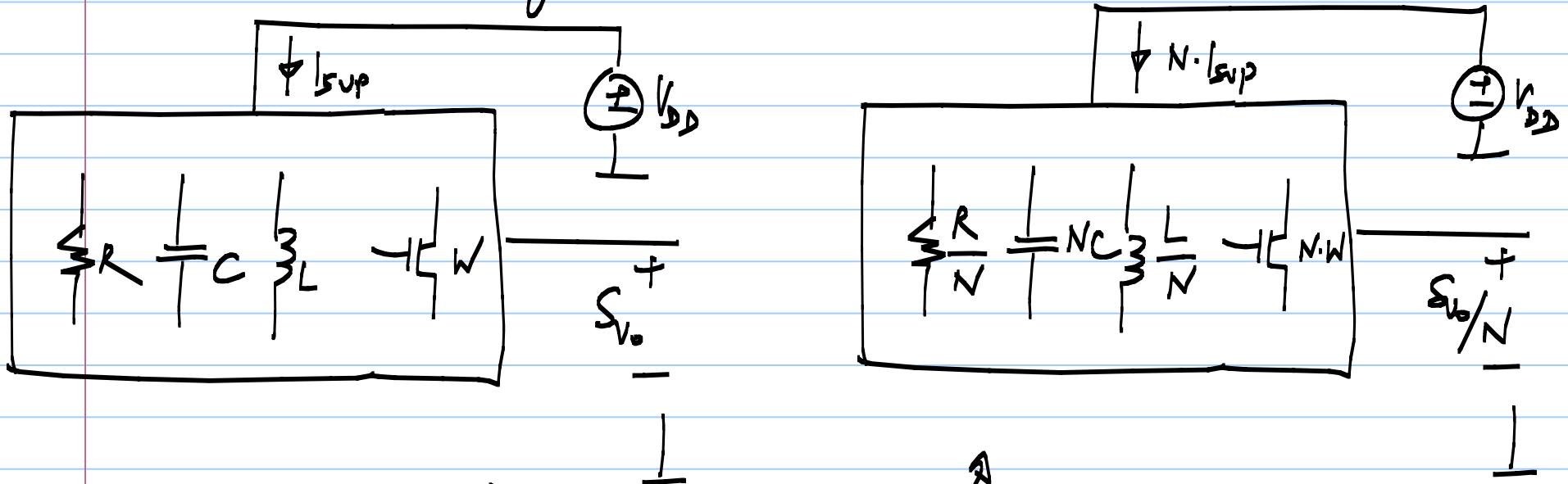


Scaling for noise:

- * $S_{v_0} \rightarrow S_{v_0}/N$
- * $P_D \rightarrow N \cdot P_D$
- * Voltages \rightarrow Identical

Thermal noise : $\frac{4KT}{R}$; $\frac{8}{3} kT gm$

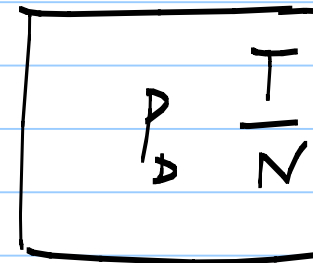$S_v \xrightarrow{\propto T} \frac{S_{v_0}}{N}$



$T_2 = T$

$P_{HEAT} = P_D$

Carnot ~~engine~~ refrigerator


$T_2 > T_1$

$\frac{P_{MECH}}{P_{MECH} + P_D} = \frac{T - T/N}{T}$


* input P_{MECH}

* transfers P_{HEAT} $T_1 \rightarrow T_2$

$P_{MECH} = (N-1) P_D$

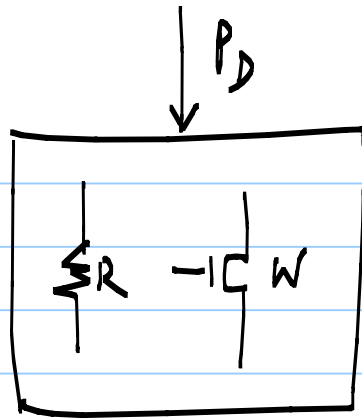


Circuit
Scaling

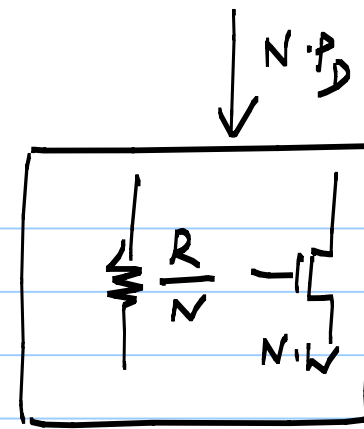

Refrigerate


$N \cdot P_D$

$$P_{MECH} = (N-1)P_D$$

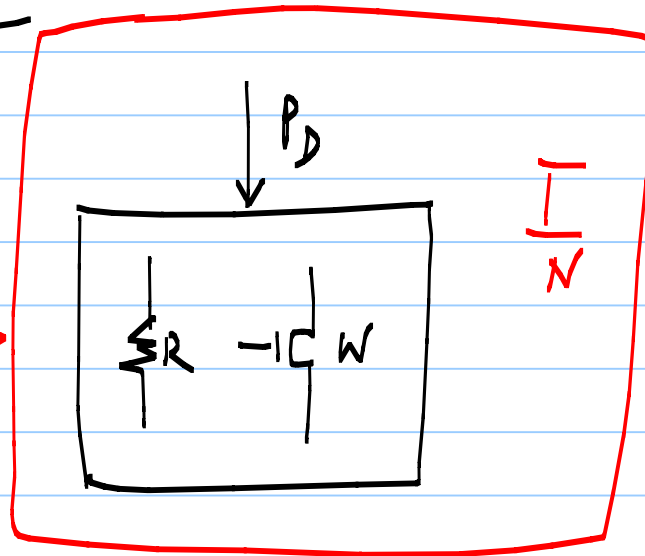

T


Frequency scaling:

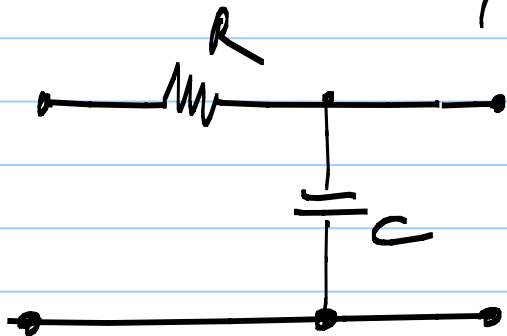

$$U_s^2 = \frac{KT}{C}$$

Const. R scaling


BW $\rightarrow \frac{1}{N}$

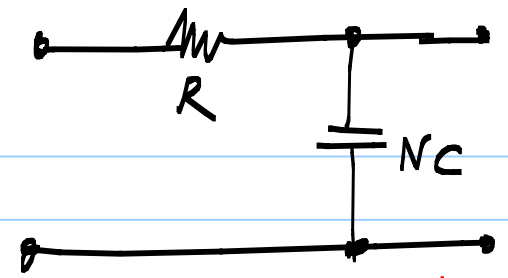

$$\left\{ \frac{KT}{NC} \right\}$$



BW $\rightarrow \frac{1}{N}$

Const. C scaling

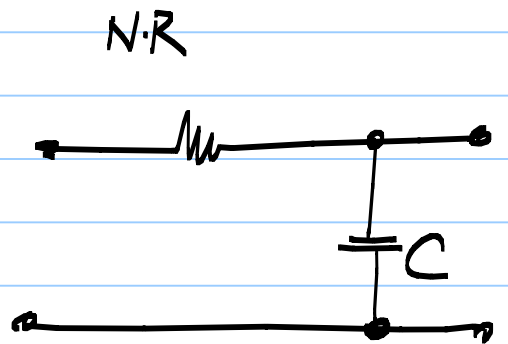

$$\left\{ \frac{KT}{C} \right\}$$

Scale the bandwidth by α

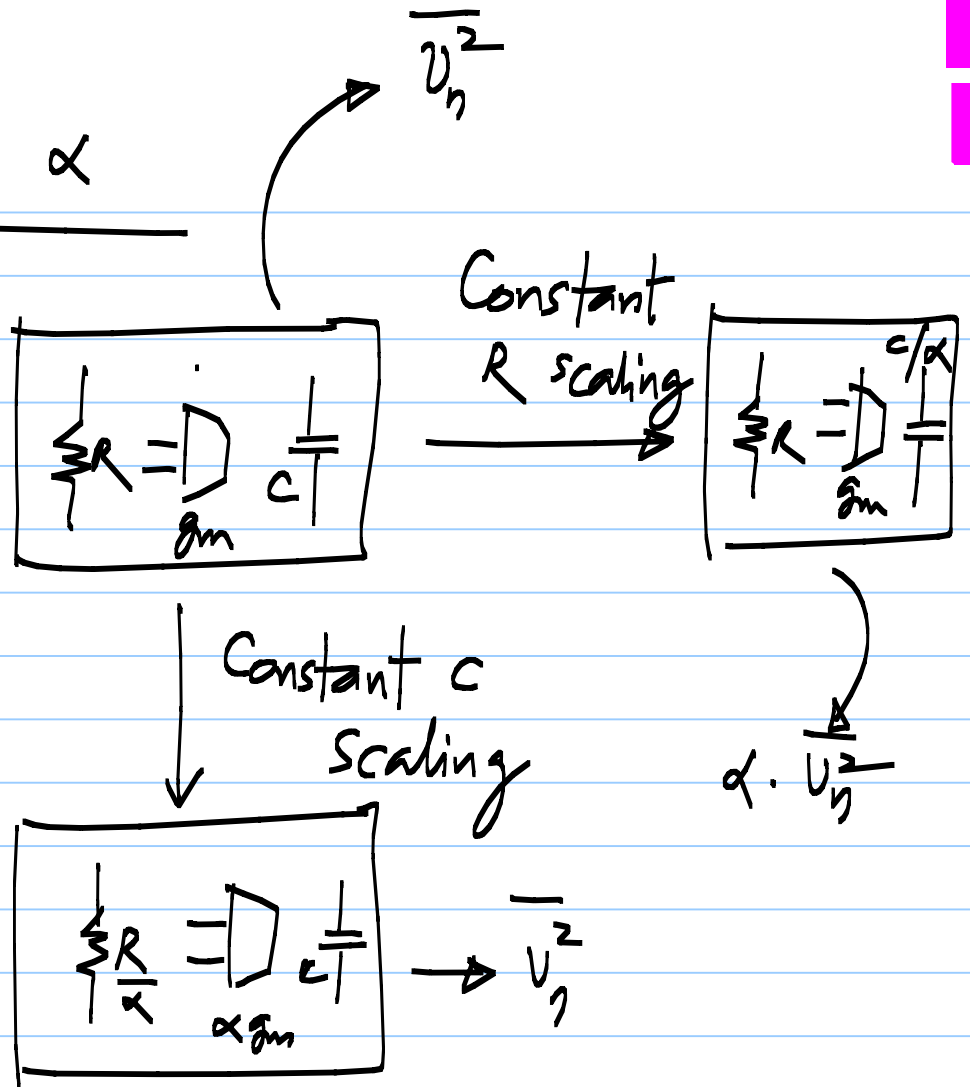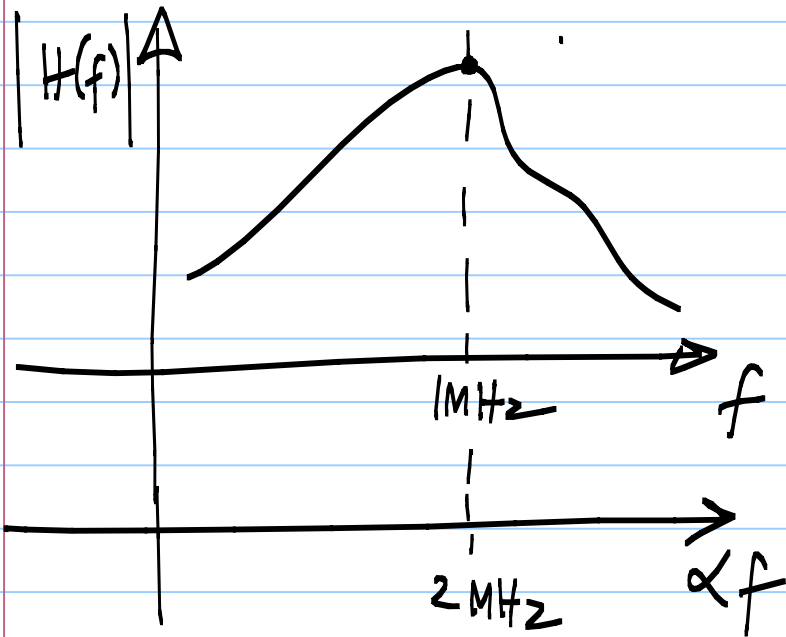

(Impedance) All branch impedances $Z_k \rightarrow Z_k/N$
Noise scaling: { without changing the transfer functions }

* Scale all elements by N

$$\begin{cases} G \rightarrow N \cdot G ; g_m \rightarrow N \cdot g_m ; L \rightarrow \frac{L}{N} ; C \rightarrow N \cdot C \\ R \rightarrow R/N \\ W \rightarrow N \cdot W \end{cases}$$

* $S_{v_o} \rightarrow S_{v_o}/N$

* Currents in the circuit $i_k \rightarrow N \cdot i_k$
 $P_s \rightarrow N \cdot P_s$

Bandwidth scaling: $H(f) \rightarrow H(f/\alpha)$

Constant C scaling

* $C \rightarrow C$

* $Q \rightarrow \alpha \cdot Q$

* $g_m \rightarrow \alpha \cdot g_m$

$\overline{V_n^2} \rightarrow \overline{V_n^2}$




Constant conductance scaling

* $C \rightarrow C/\alpha$

* $Q, g_m \rightarrow Q, g_m$


$\overline{V_n^2} \rightarrow \alpha \cdot \overline{V_n^2}$

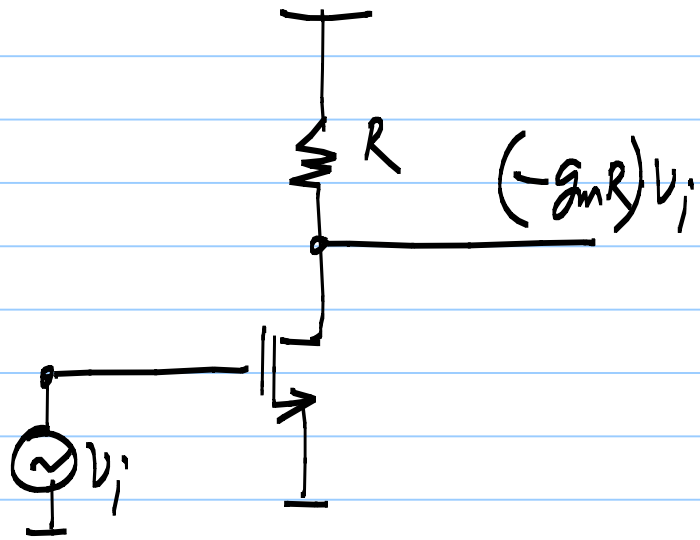Basic amplifier stages: CS, CG, CD
(Source follower)




$$(-g_m R)$$

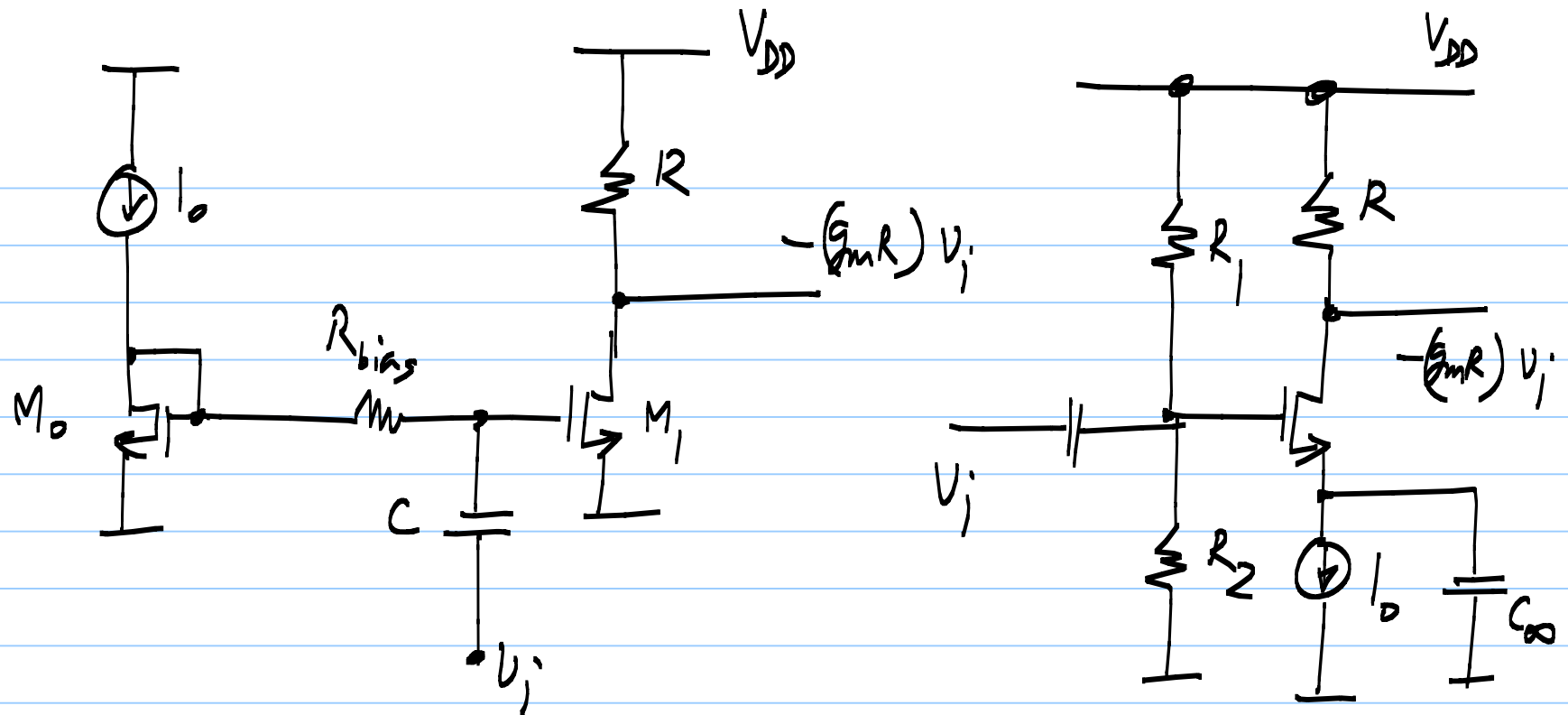* Constant current biasing preferred to constant V_{GS} biasing \rightarrow lower sensitivity of g_m



CS (common source amplifier)

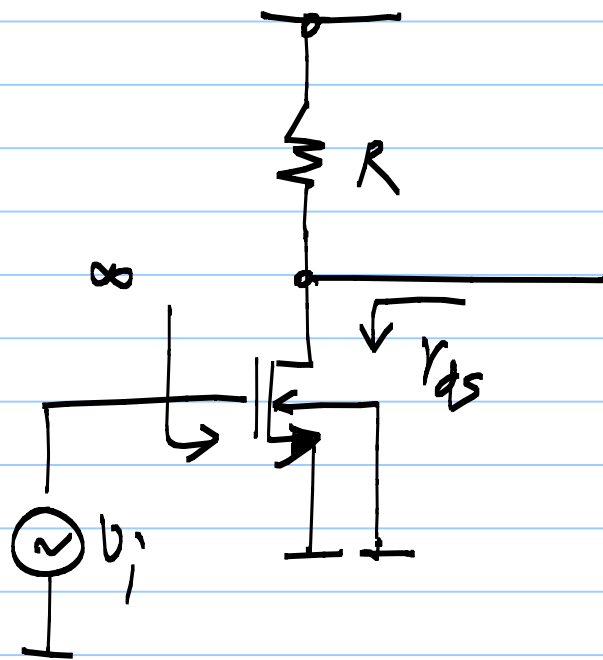

* Gain $\approx -g_m R$


* Gain = $-(g_m R) \cdot v_i = -g_m (R \parallel r_{ds})$

$$= \frac{-g_m}{g + g_{ds}}$$

* $V_{bs} = 0 \Rightarrow g_{mb} \cdot V_{bs} = 0$

Body effect doesn't influence the CS amp.

Common gate amplifier:

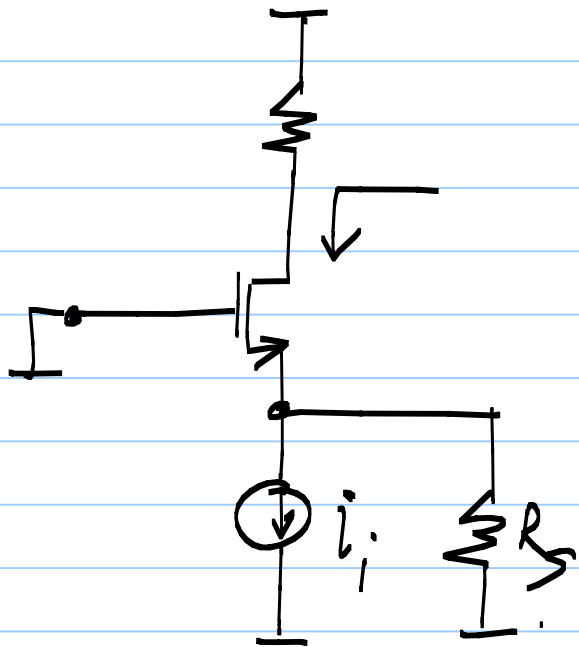

Current buffer

* $i_o = i_i$

* $r_{ds} = \infty ; (g_{ds} = 0)$

$R_{in} = 1/g_m$

$R_{out} = \infty$

* $r_{ds} \neq \infty ;$

Not true if $R \gg r_{ds}$

$R_{out} = g_m r_{ds} \cdot R_S + r_{ds} + R_S$
 $R_{in} \approx 1/g_m \quad R \sim r_{ds}$

