
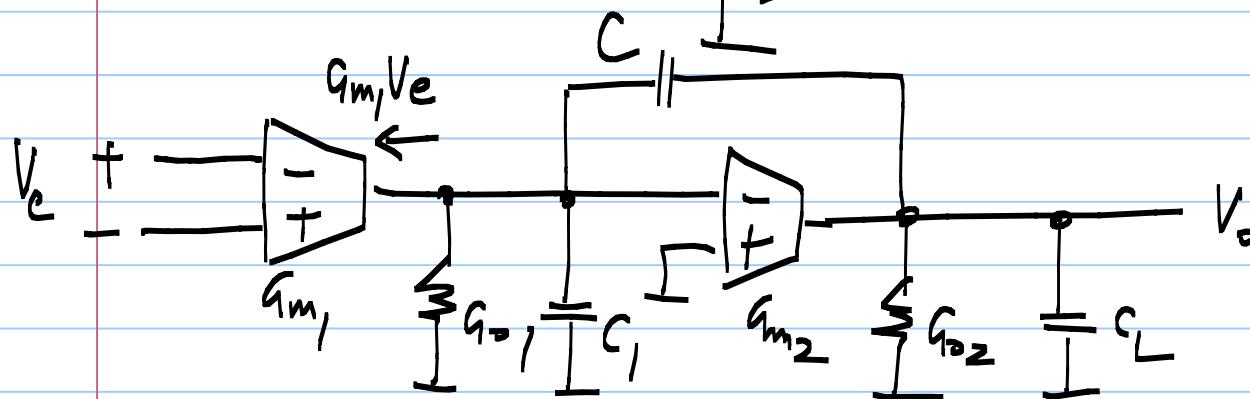


Lecture 28

Common source amplifier

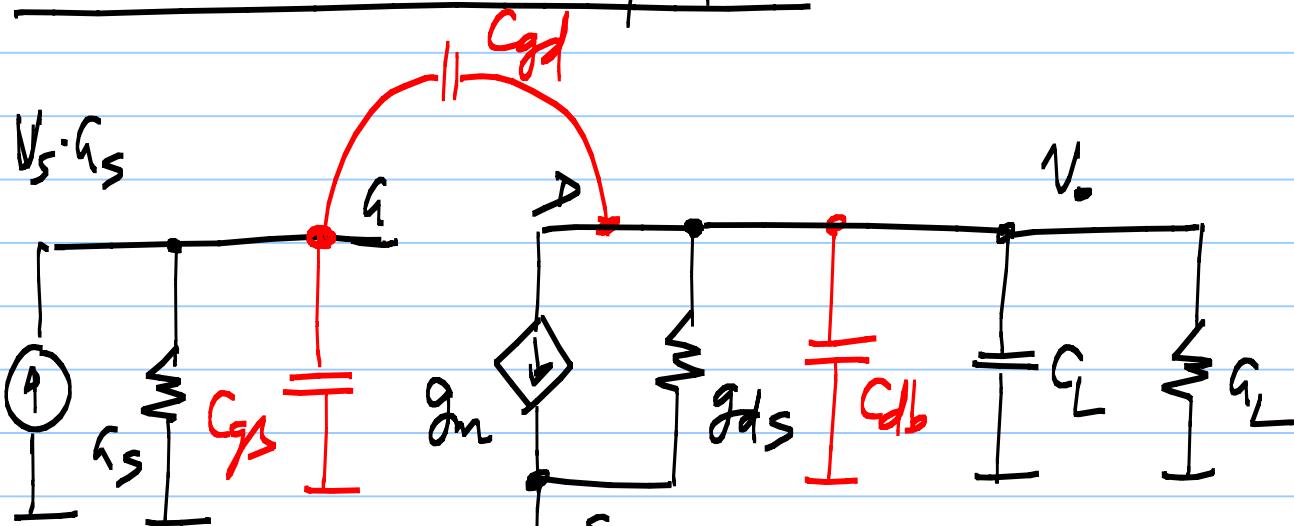

$$C'_L = C_L + C_{db}$$

$$G'_L = G_L + g_{ds}$$

$$\frac{V_o}{V_s} = \frac{-g_s (g_m - sC_{gd})}{s^2(C_{gs}C_{gd} + C_{gd}C_L' + C_L' \cdot C_{gs})}$$

$$+ s (C_{gd} (g_m + g_s + g_L') + C_L' \cdot g_s + C_{gs} g_L')$$

$$+ g_s g_L'$$

RHP pole: $+ \frac{g_m}{g_s} \rightarrow$ Extra phase shift

$V_s g_s$

C_L'

C_{gs}

C_{gd}

g_m

$-g_m, V_e$

C_L

C_I

C

g_{m_2}

$$P'_1 \approx -$$

$$g_s$$

$$C_{gd} \left(\frac{g_m}{C_L'} + 1 + \frac{g_s}{C_L'} \right) + C_{gs} + C_L' \cdot \frac{g_s}{C_L'}$$

lower freq.

w/o C_{gd}

$$- \frac{g_s}{C_{gs}}$$

$$P'_2 \approx -$$

$$C_L' + g_m \cdot$$

$$\frac{C_{gd}}{C_{gd} + C_{gs}} + g_s \cdot \frac{C_{gd} + C_L'}{C_{gd} + C_{gs}}$$

$$- \frac{C_L'}{C_L}$$


$$C_L' +$$

$$\frac{C_{gd} \cdot C_{gs}}{C_{gs} + C_{gd}}$$

higher freq.


POLE SPLITTING

CD amplifier:

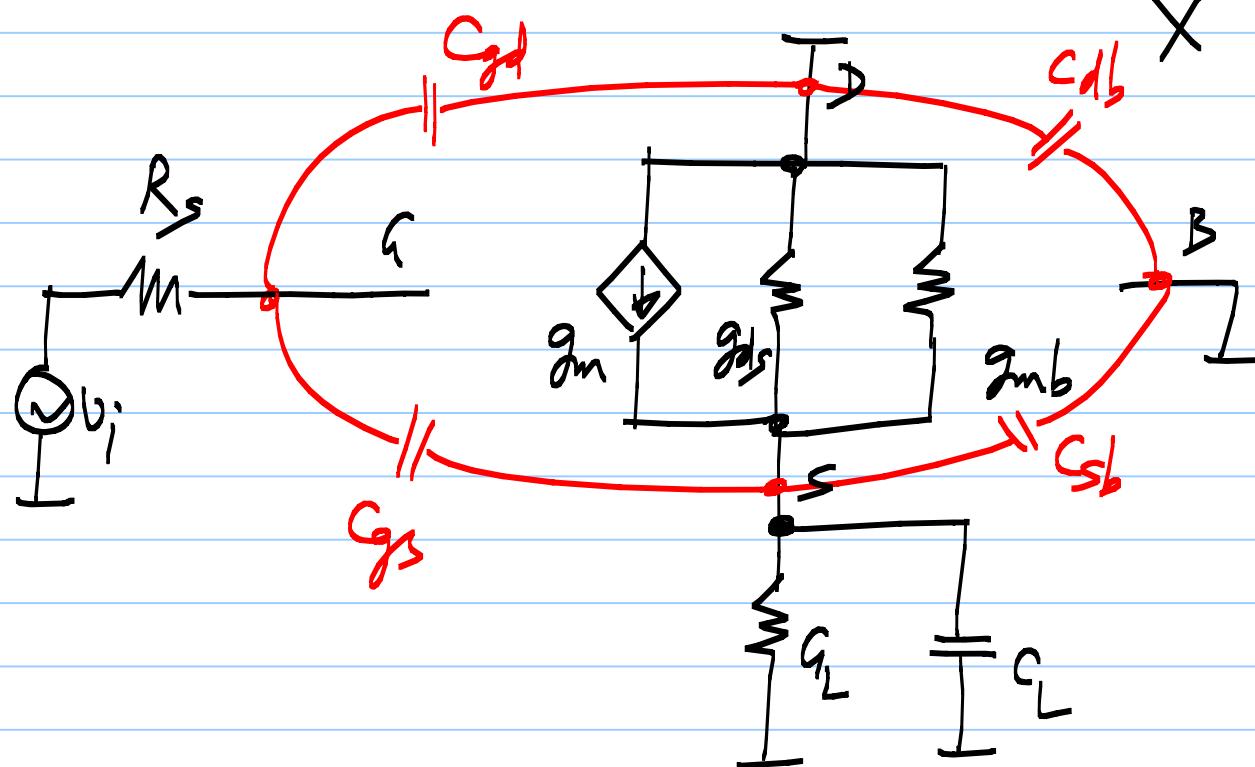

$$C_L' = C_{sb} + C_L$$

$$G_L' = G_L + g_{mb} + g_{ds}$$

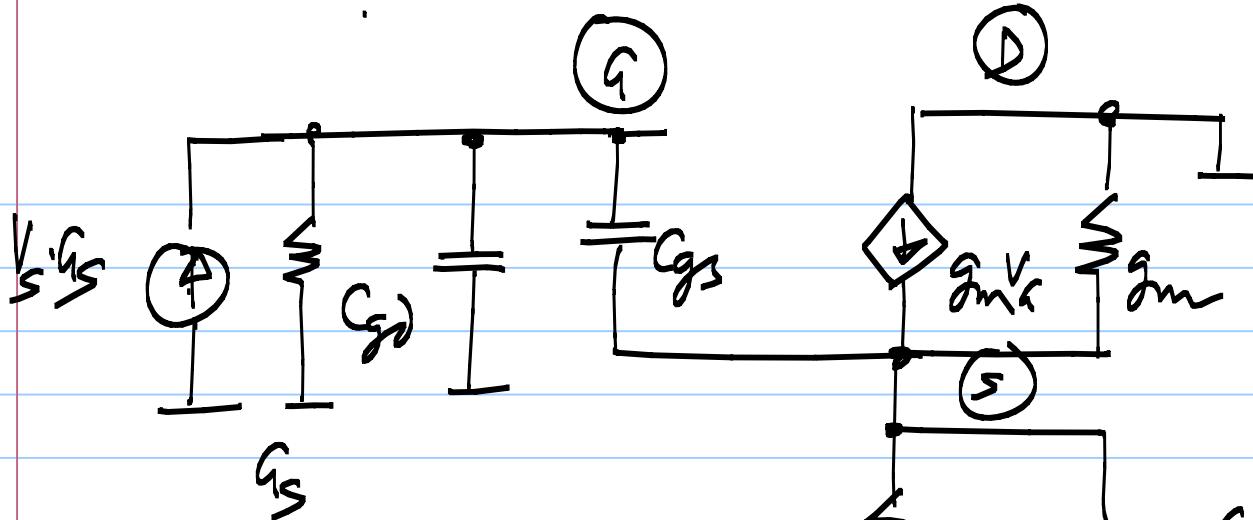

CD amp.


$$V_{GS} : -\hat{g}_m V_e$$





$$G_S : C_1$$


$$C_{GS} : C$$


$$C_L' : C_L$$
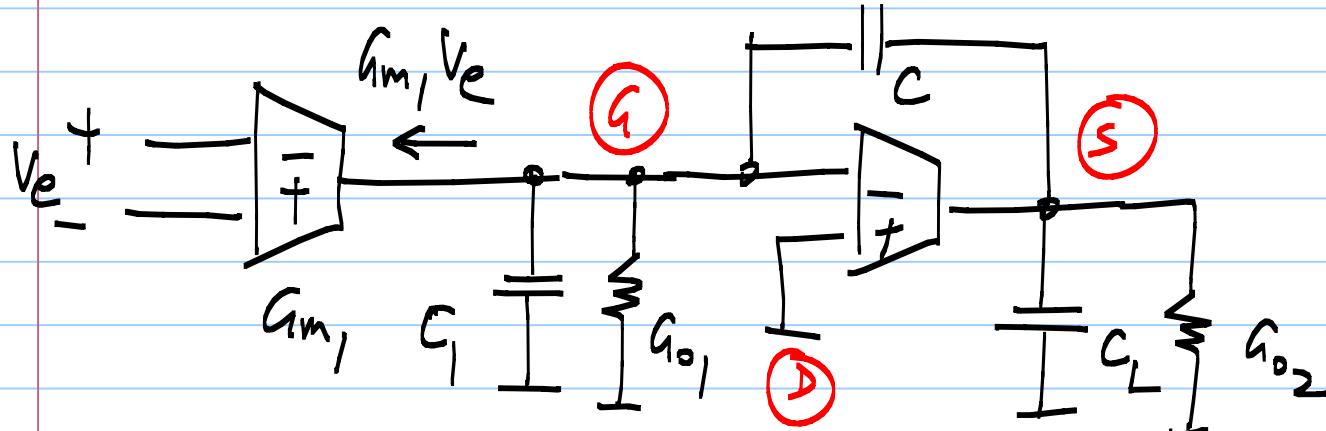
$$\begin{aligned} G_S &: g_{o1} \\ G_L' + \hat{g}_m &: g_{o2} \end{aligned}$$




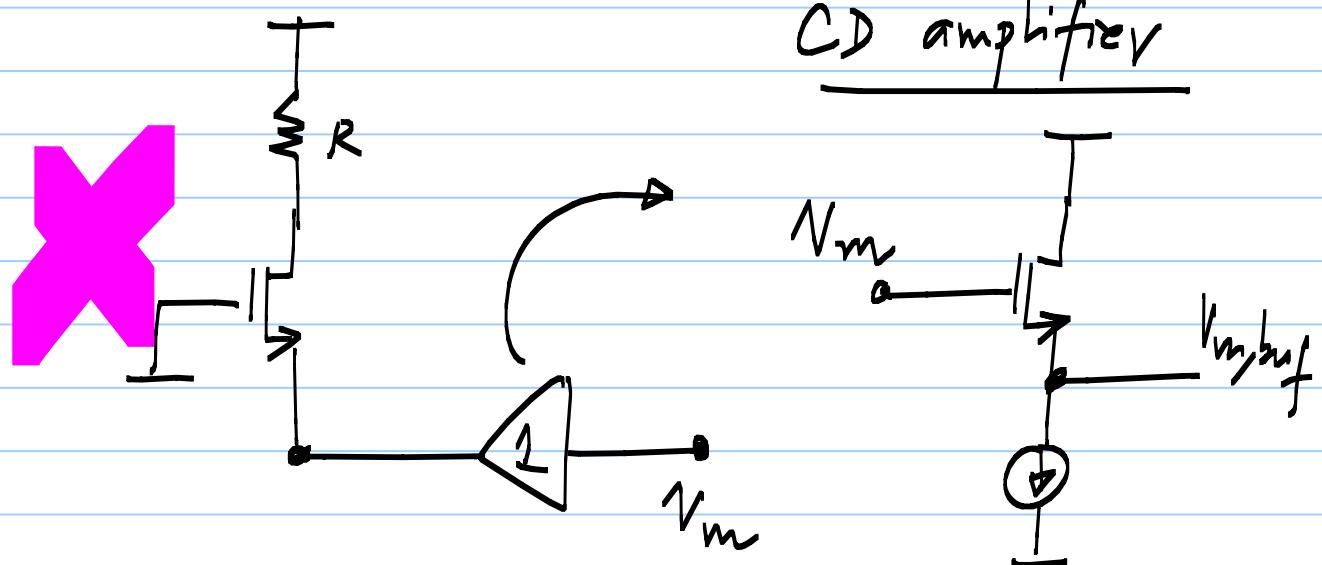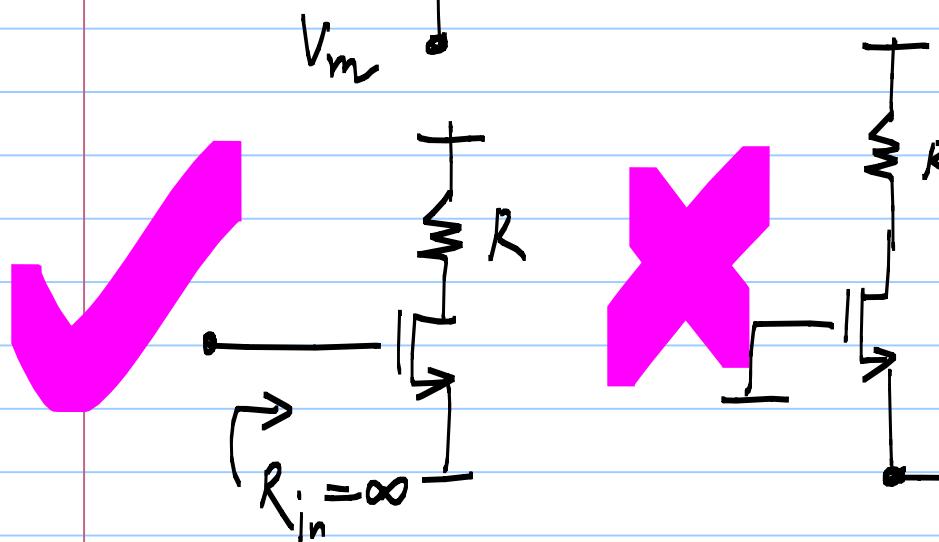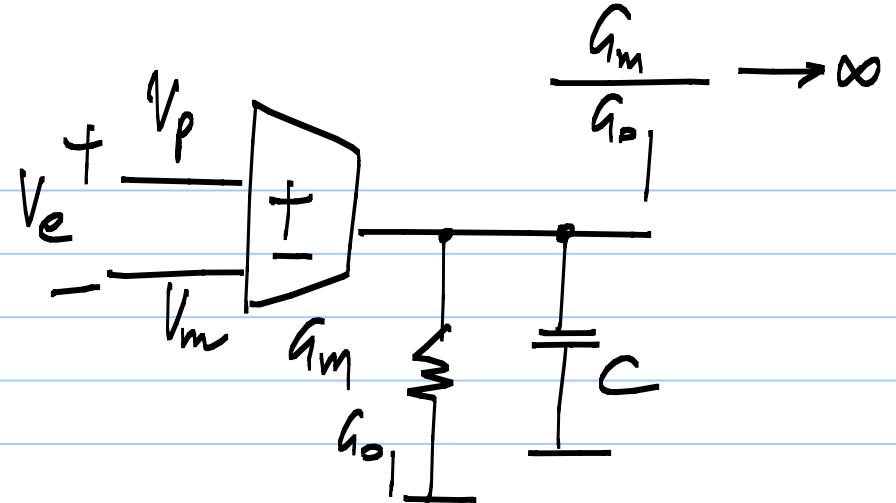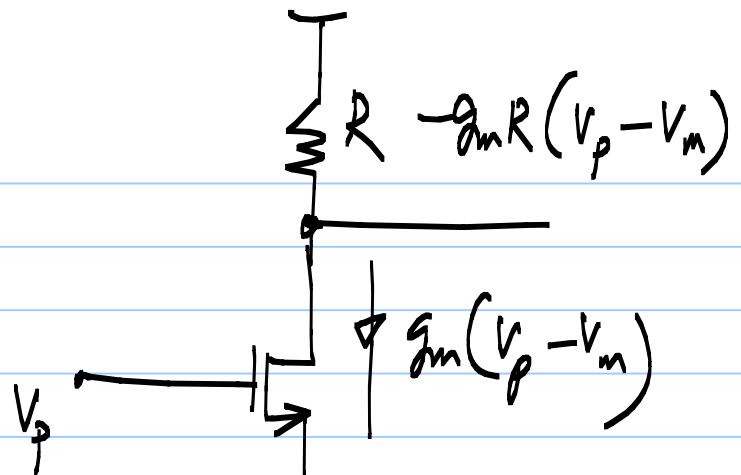

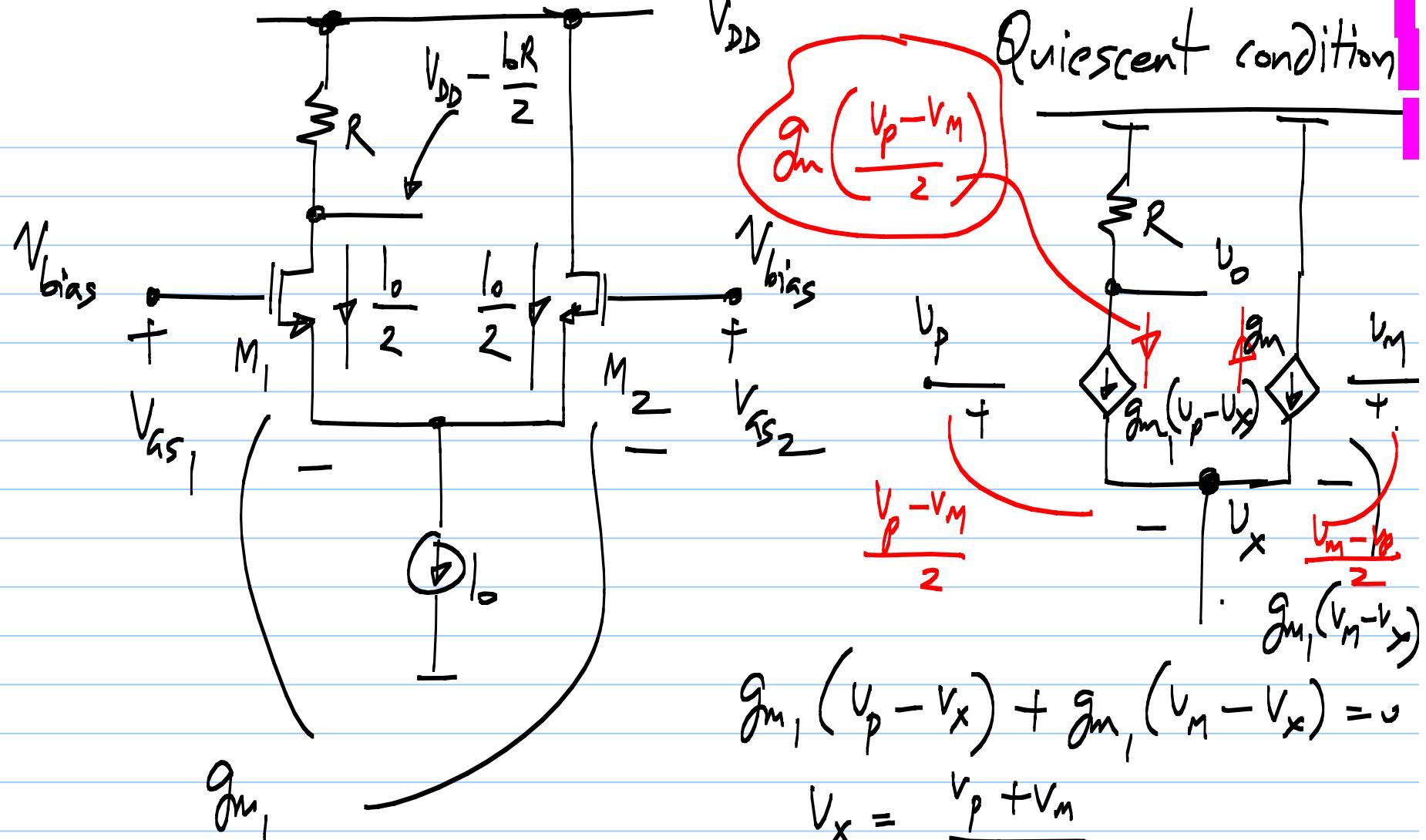

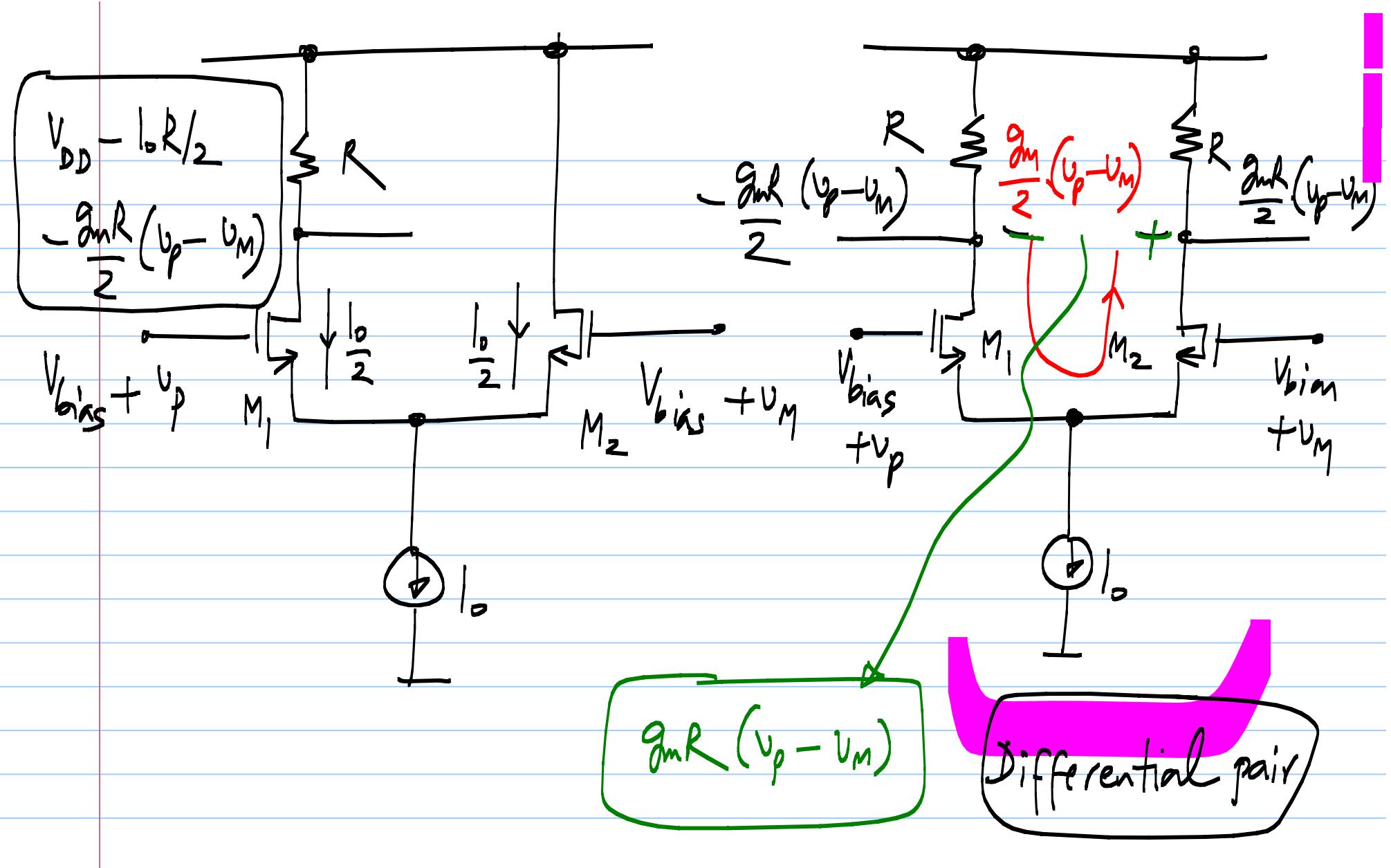

Differential pair:

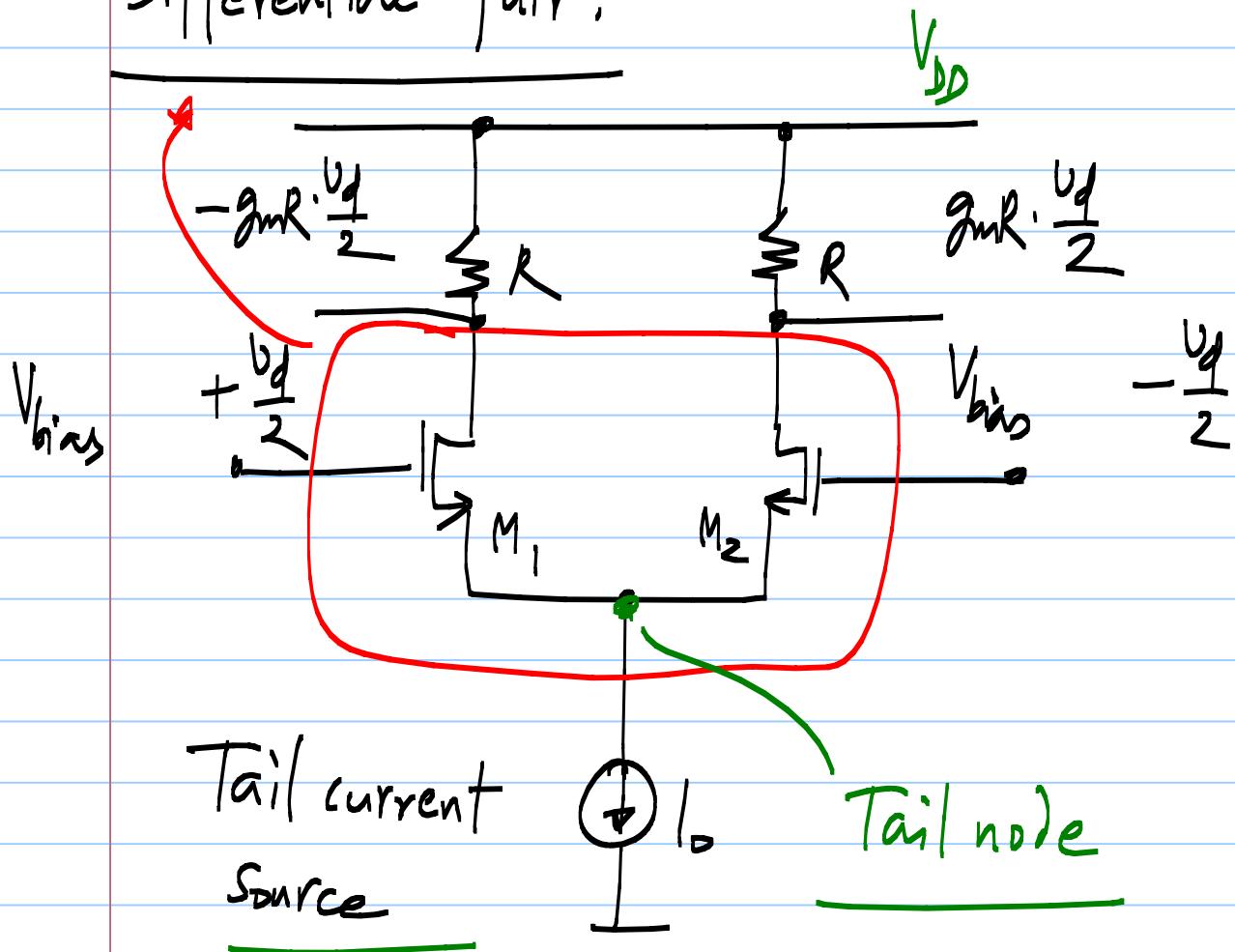


Large signal &
Small signal analysis

$$\frac{V_p + V_m}{2} \pm \left(\frac{V_p - V_m}{2} \right)$$

Common mode voltage $\frac{1}{2} \cdot \text{differential voltage}$

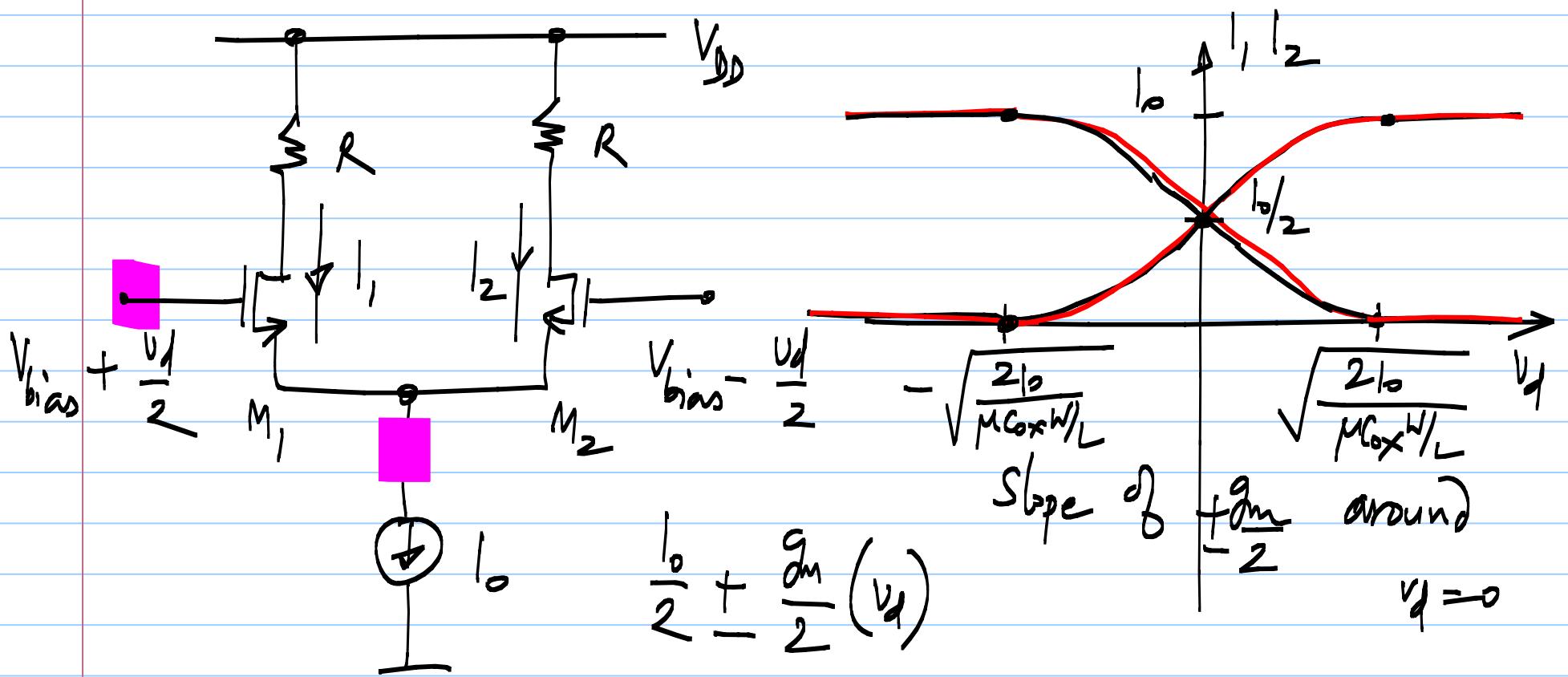Large signal analysis of the differential pair



Quiescent V_{as} of M_1 & M_2 :

$$V_T + \sqrt{\frac{2 \cdot I_o / 2}{\mu C_{ox} W/L}}$$

V_{as} of M_1 at a current:
of I_o

$$V_T + \sqrt{\frac{2 \cdot I_o}{\mu C_{ox} W/L}}$$

V_{as} of M_2 when M_1 is:
carrying I_o

$$V_T$$

$$V_T = \sqrt{\frac{2 I_o}{\mu C_{ox} W/L}}$$