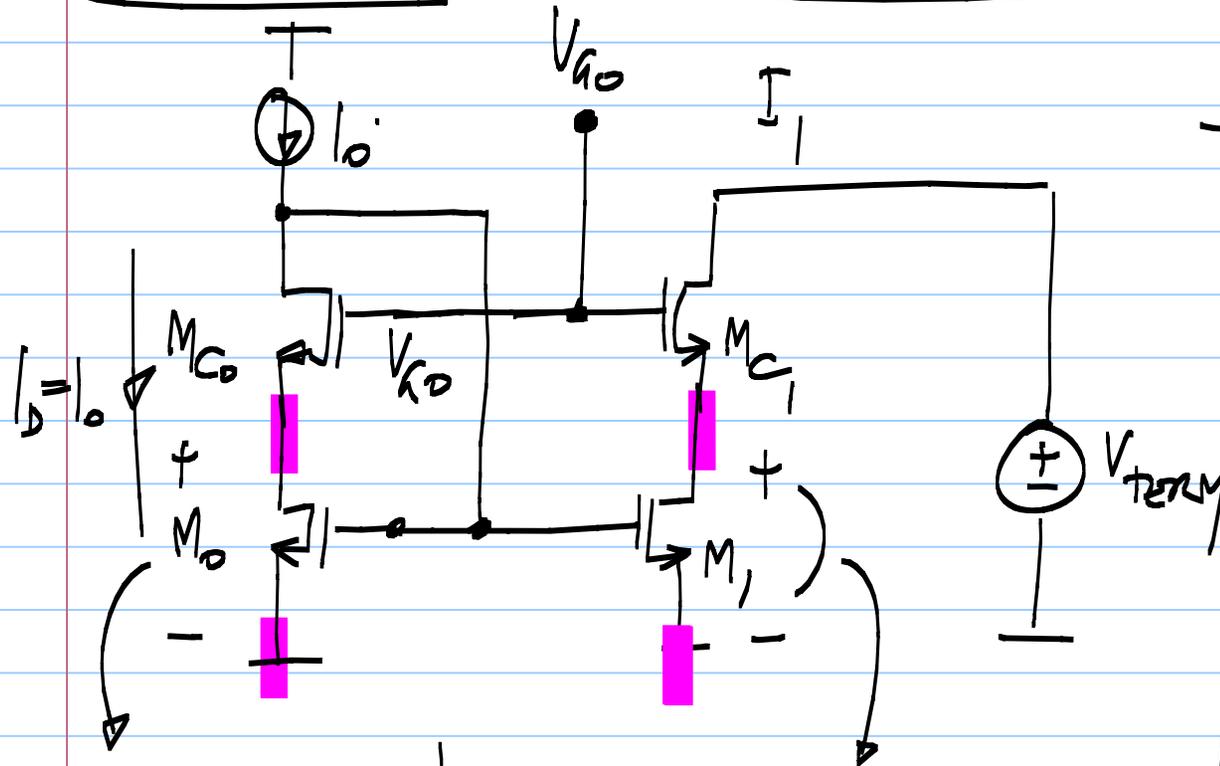


Lecture 33:

$$M_1 = M_0$$

$$M_C = M_{C0}$$

$$I_1 = I_0$$




$$\Delta V_{TERM} = g_{mC} \cdot g_{m1}^{-1}$$

$$\Delta V_{TERM} = g_{mC} \cdot \left(\frac{g_{mC0}}{g_{mC1}} \right)$$


Cascode
Current
mirror

$$V_{DS0} = V_{G0} - V_{ASCO} \Big|_{I_0}$$

$$V_{DS1} = V_{G1} - V_{ASC1} \Big|_{I_1}$$


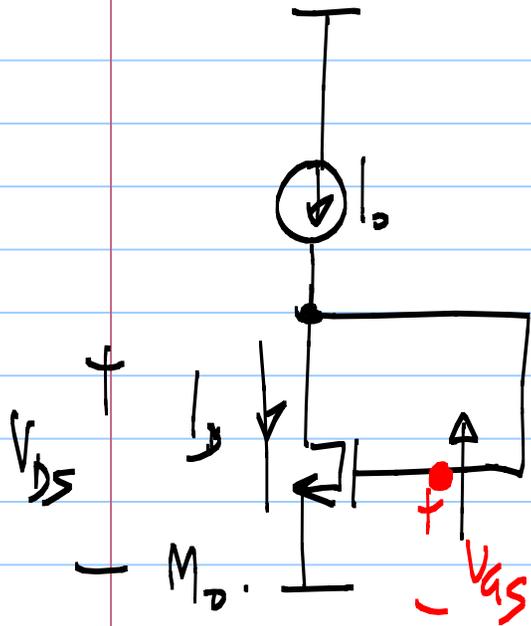


$$V_{DS0} = V_{GS0}$$

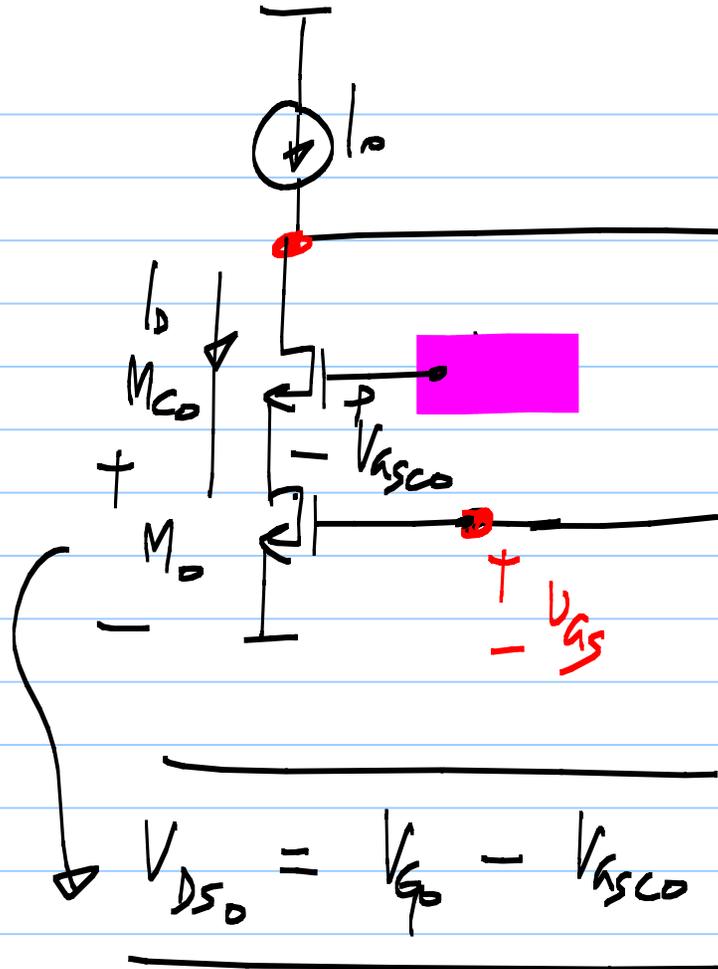

$$V_{DS0} = V_{G0} - V_{GS0}$$

High swing Cascode current mirror

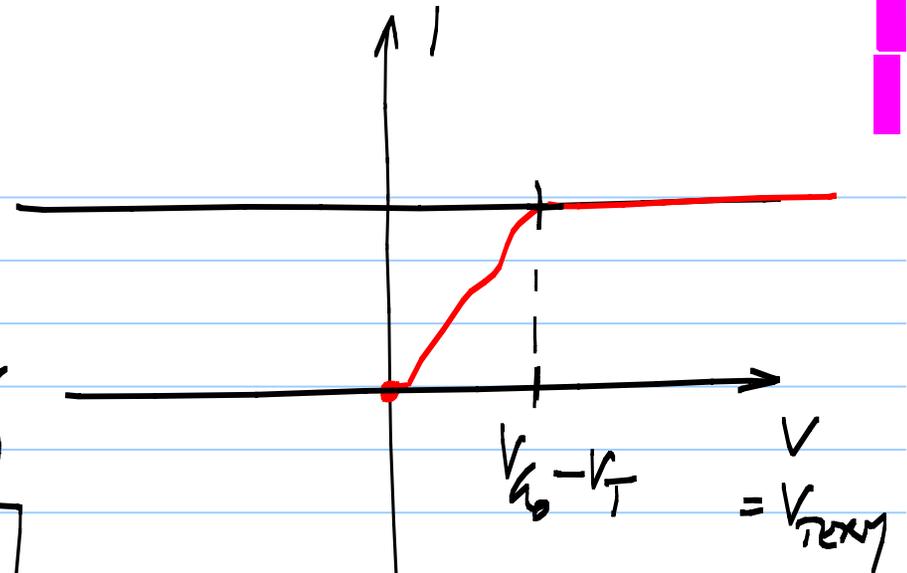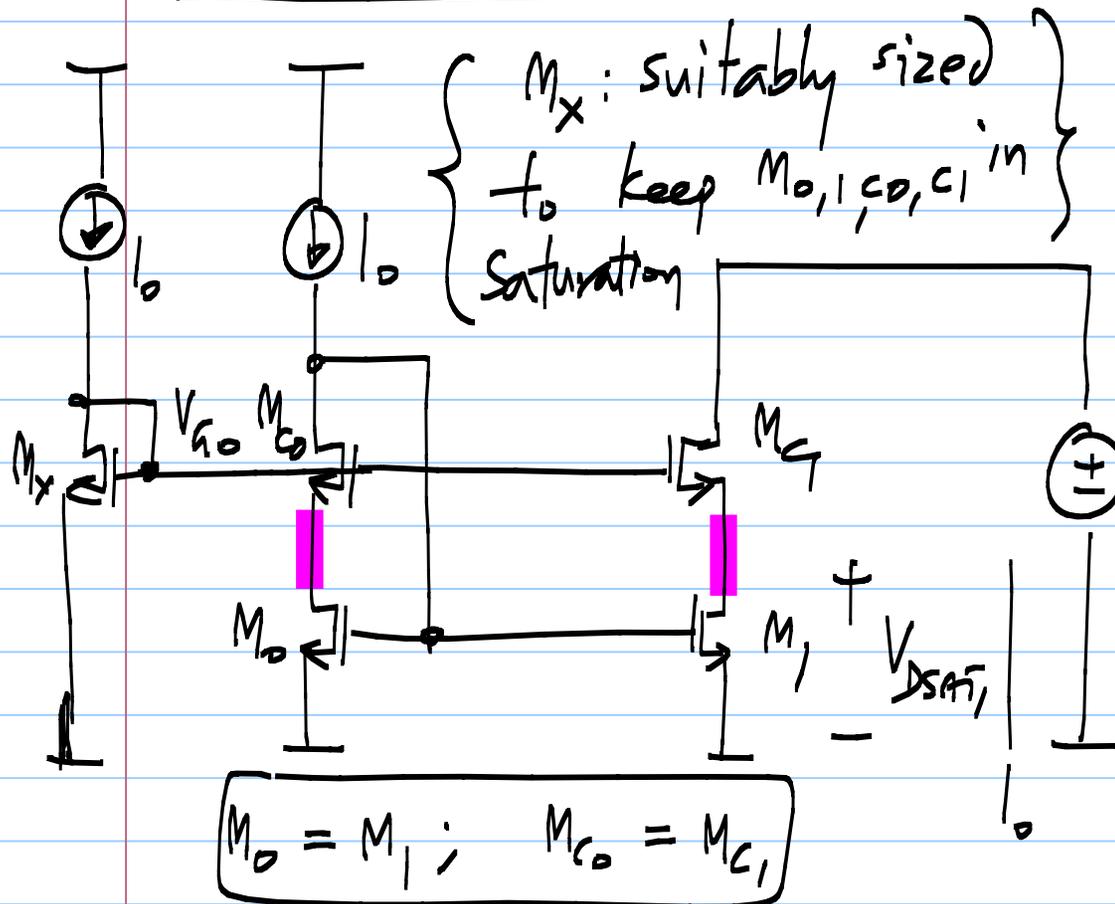



V_{TERM}

Minimize V_{G0}



$$V_{G0} > V_{DSAT0} + V_{T_{C0}} + V_{DSAT_{C0}}$$

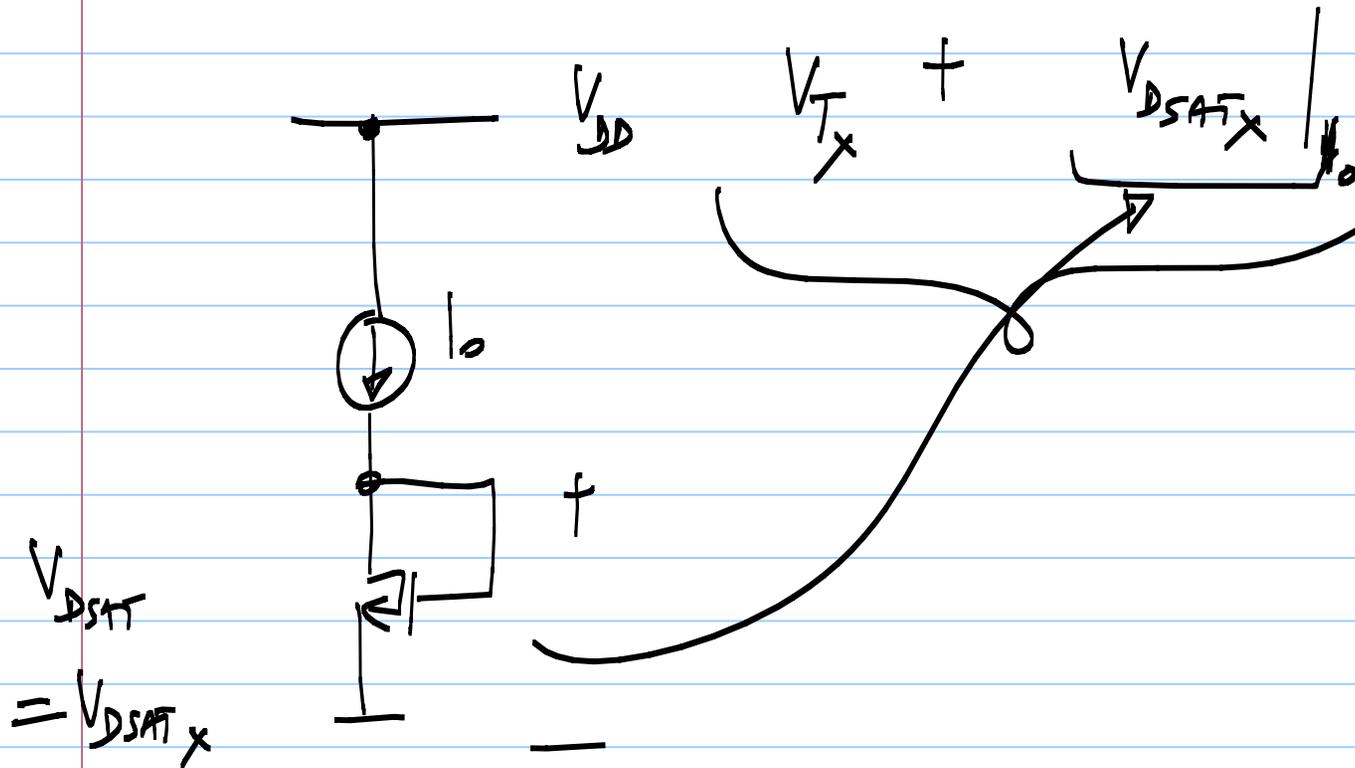
$$V_{fo,min} = \underbrace{V_{T_{E0}}}_{V_{T_x}} + \underbrace{V_{DSAT_{C0}} + V_{DSAT_{E0}}}_{V_{DSAT_x}} + I_0$$



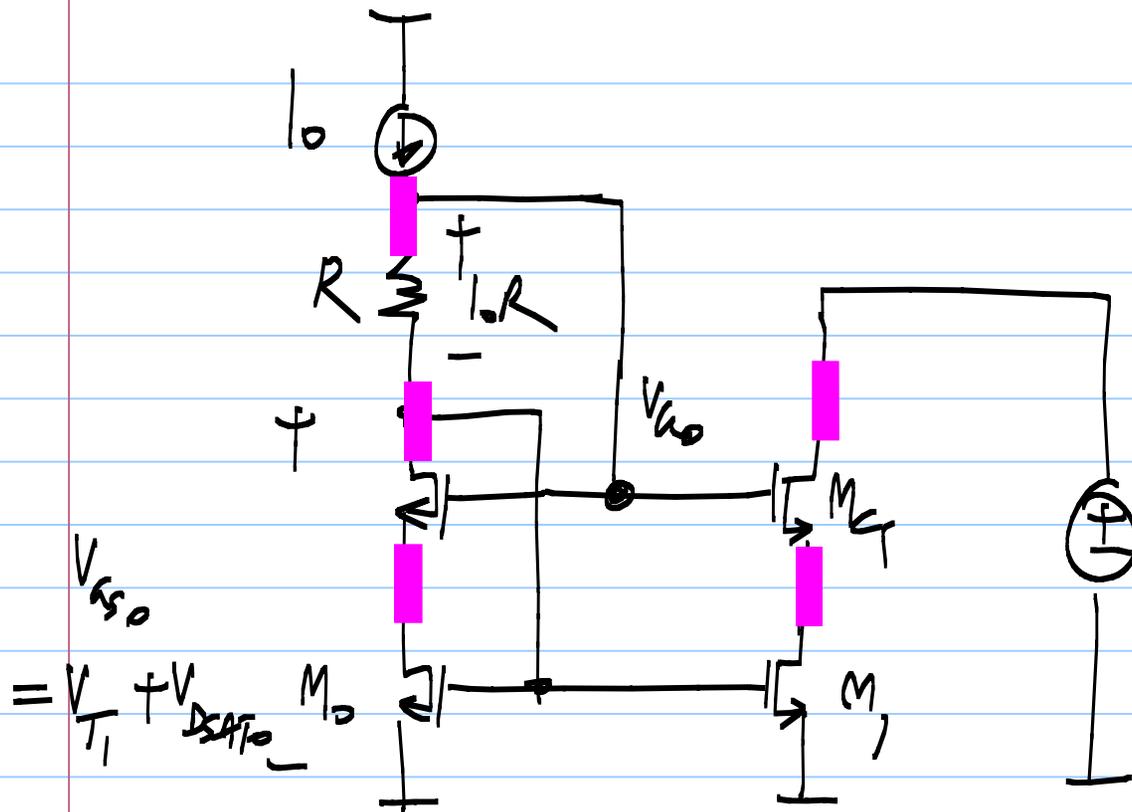


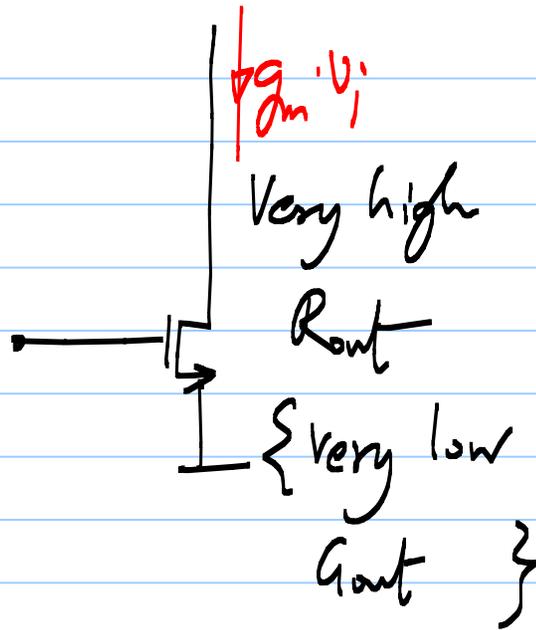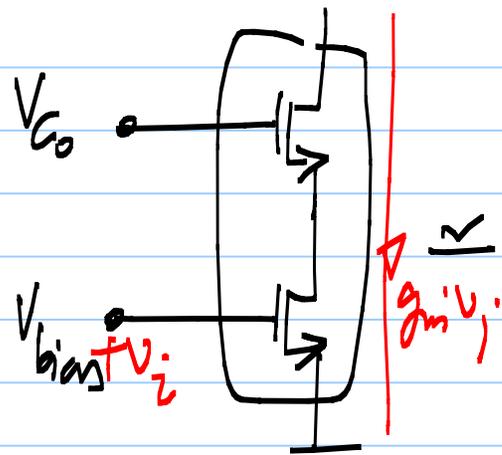- ① Calculate ΔV_{DS} , due to a change ΔV_{TERM}
- ② Range of V_{SS_0} so that all transistors are in saturation




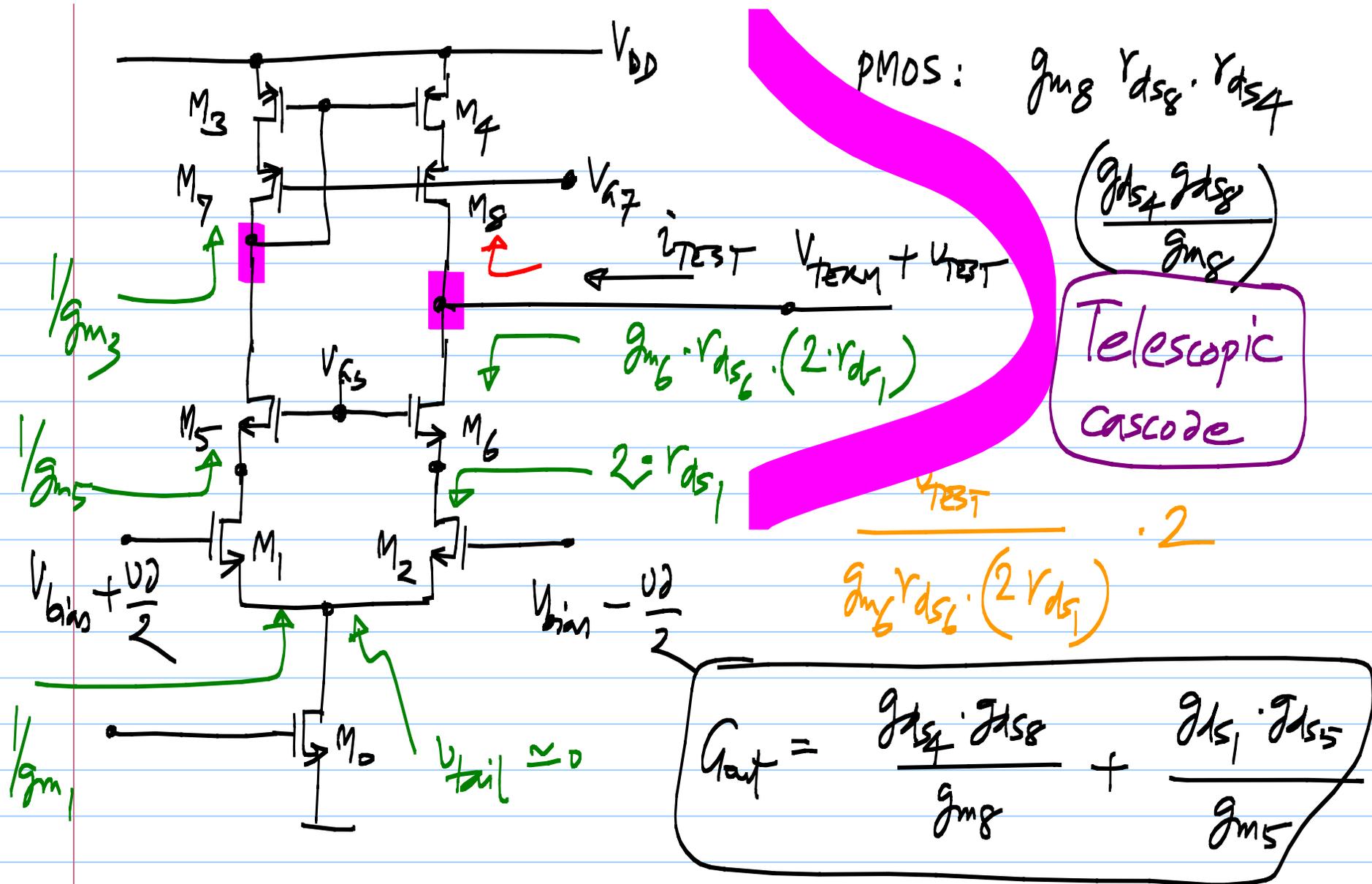


Single stage cascode opamp -

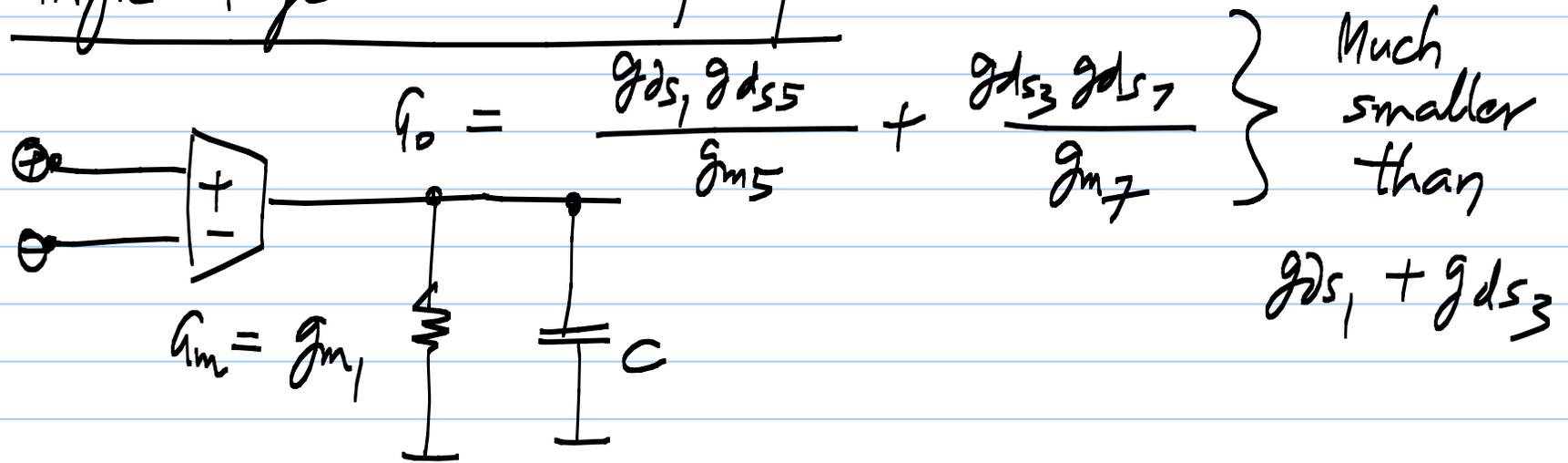
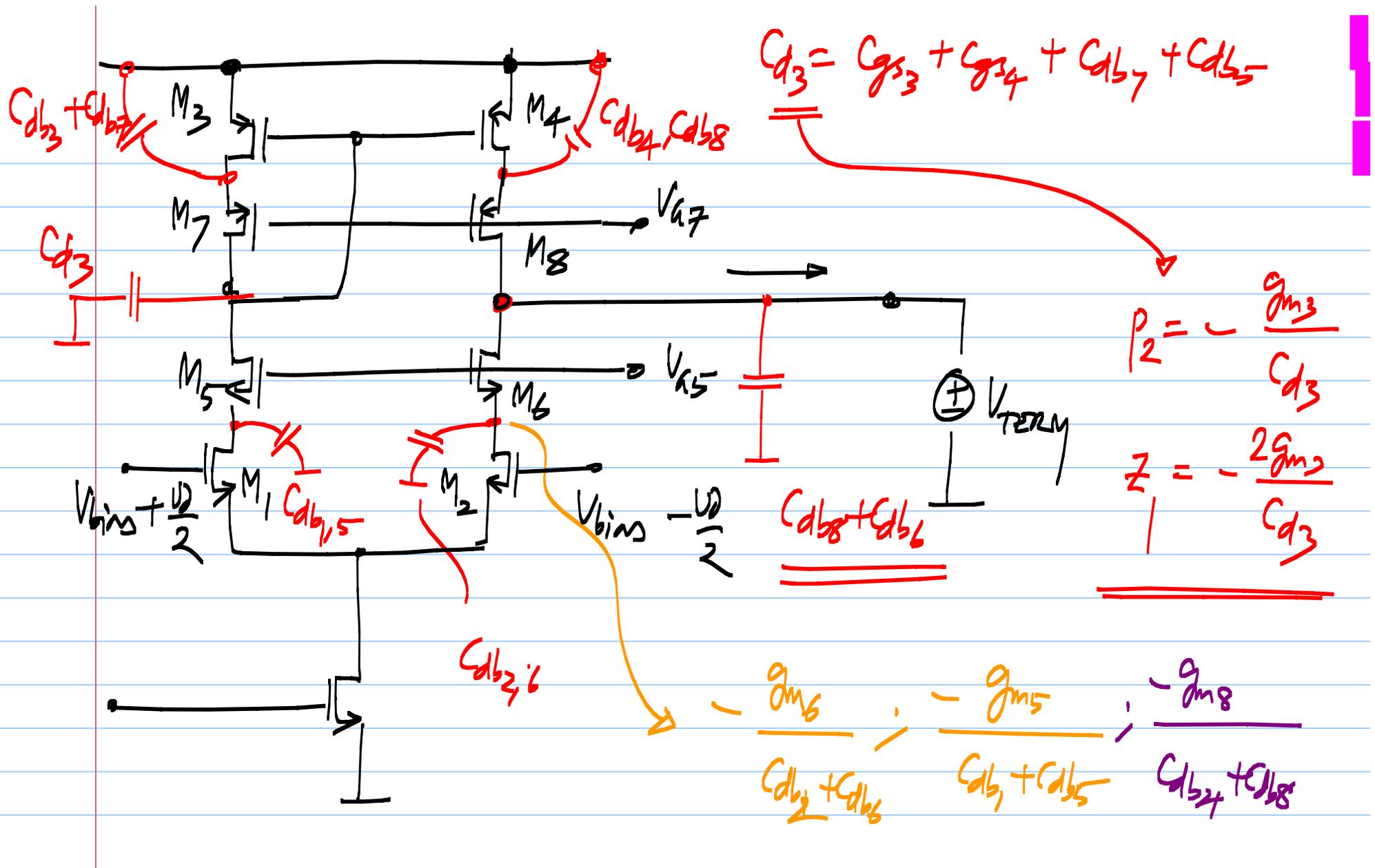
$$\frac{g_{m1}}{g_{ds1} + g_{ds3}} \sim \left(\frac{g_m}{g_{ds}} \right); \quad \frac{g_{m1}}{\frac{g_{ds1} g_{ds5}}{g_{m5}} + \frac{g_{ds3} g_{ds7}}{g_{m7}}} \sim \left(\frac{g_m}{g_{ds}} \right)^2$$



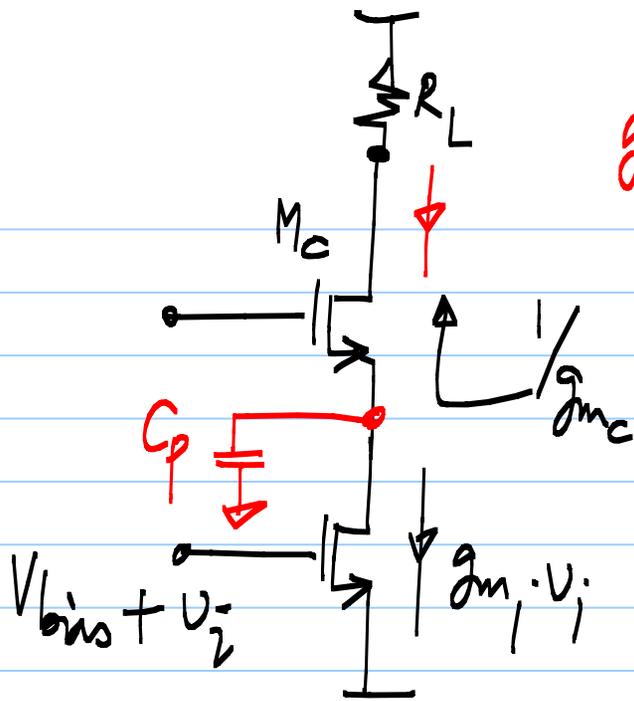

$$g_{m_i} \cdot v_i(s) \frac{g_{m_c}}{g_{m_c} + sC_p} = g_{m_i} \cdot v_i(s) \cdot \frac{1}{1 + \frac{sC_p}{g_{m_c}}}$$

Pole: $-\frac{g_{m_c}}{C_p}$