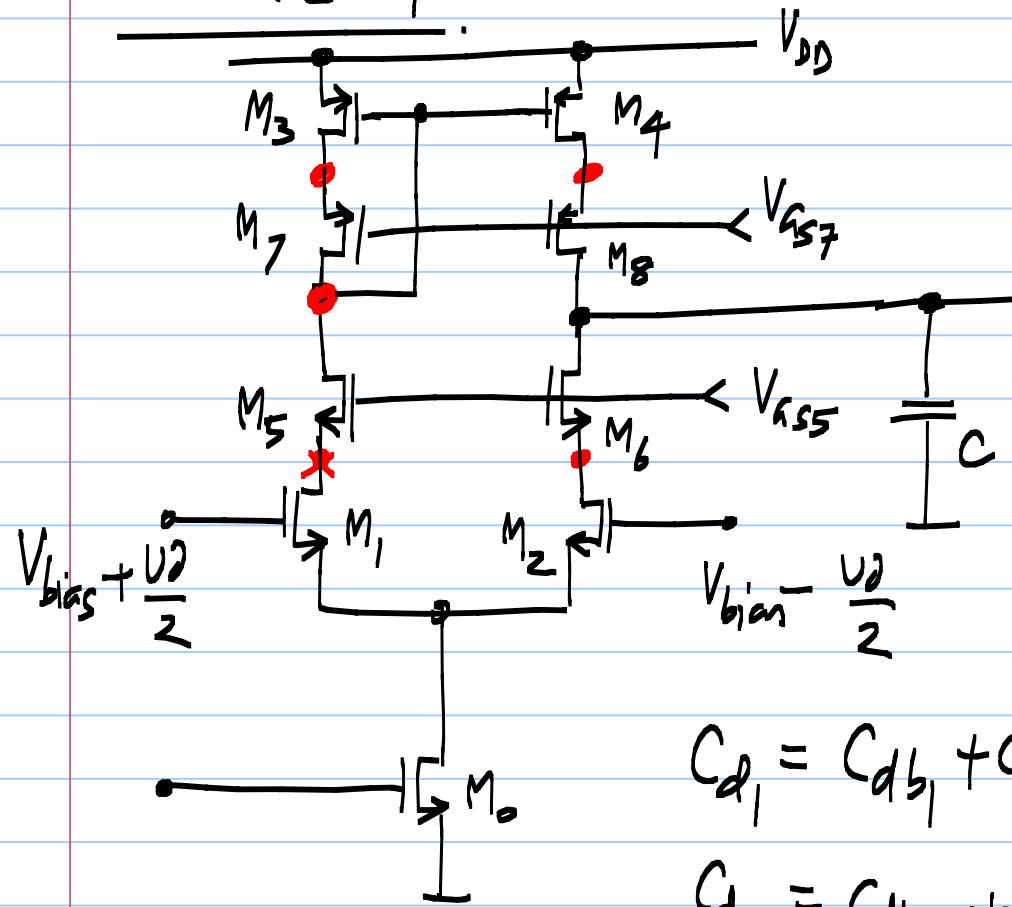


## Lecture 34



$$A_o = \frac{\frac{\partial v_o}{\partial v_i}}{\frac{\partial v_o}{\partial v_s} + \frac{\partial v_o}{\partial v_d}}$$

$$A_m = \frac{\partial v_o}{\partial v_i}$$

$$A_{out} = \frac{\frac{\partial v_o}{\partial v_s}}{\frac{\partial v_o}{\partial v_i}} + \frac{\frac{\partial v_o}{\partial v_d}}{\frac{\partial v_o}{\partial v_i}}$$


$$C_{d1} = C_{db1} + C_{sb5} + C_{gs5}$$

$$C_{d2} = C_{db2} + C_{sb6} + C_{gs6}$$

$$C_{d5} = C_{db5} + C_{db7} + 2 \cdot C_{gs3}$$

$$C_{d3} = C_{db3} + C_{sb7} + C_{gs7}$$
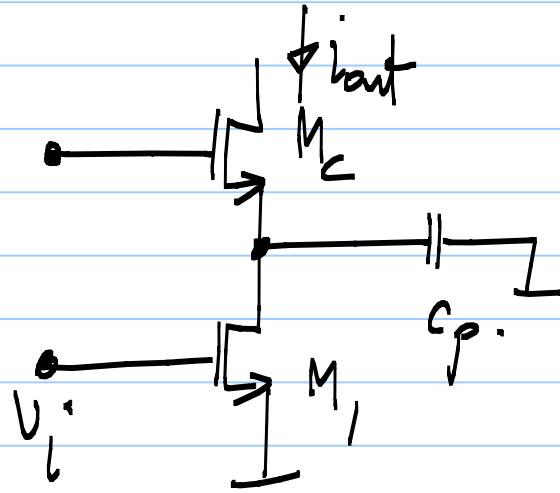
$$\text{Due to } C_{d5} : \quad p_2 = -\frac{g_{m3}}{C_{d5}} ; \quad z_1 = -\frac{2g_{m3}}{C_{d5}}$$




pole @  $-\frac{g_{mc} + g_{mbc}}{C_p}$

$$C_{d1} : -\frac{g_{m5}}{C_{d1}} ; \quad C_{d2} : -\frac{g_{m5}}{C_{d1}}$$

$$C_{d3} : -\frac{g_{m7}}{C_{d3}} ; \quad C_{d4} : -\frac{g_{m8}}{C_{d4}}$$

acts only  
on half of  
 $I_{out}$

## Noise & offset:


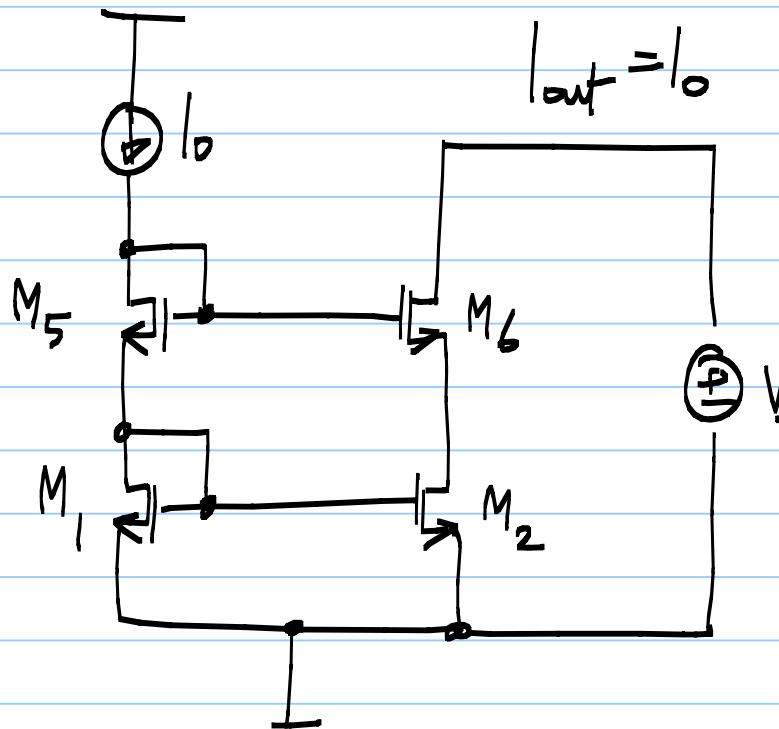



$$I_{out} = I_0$$
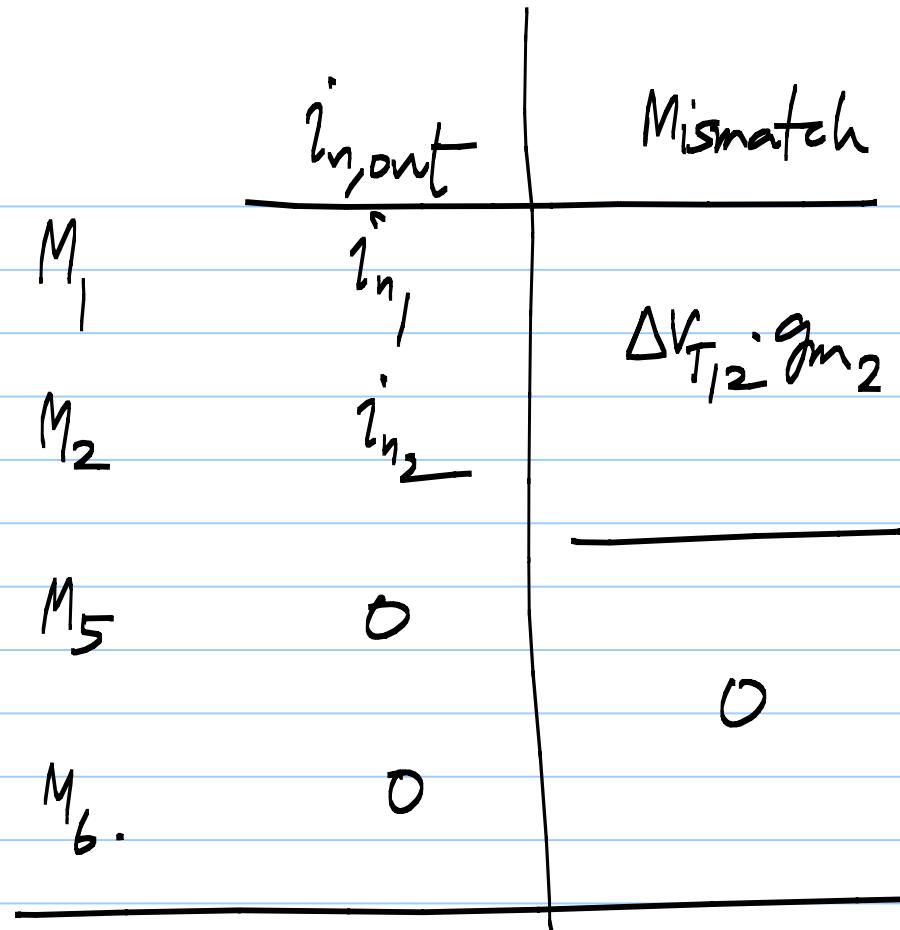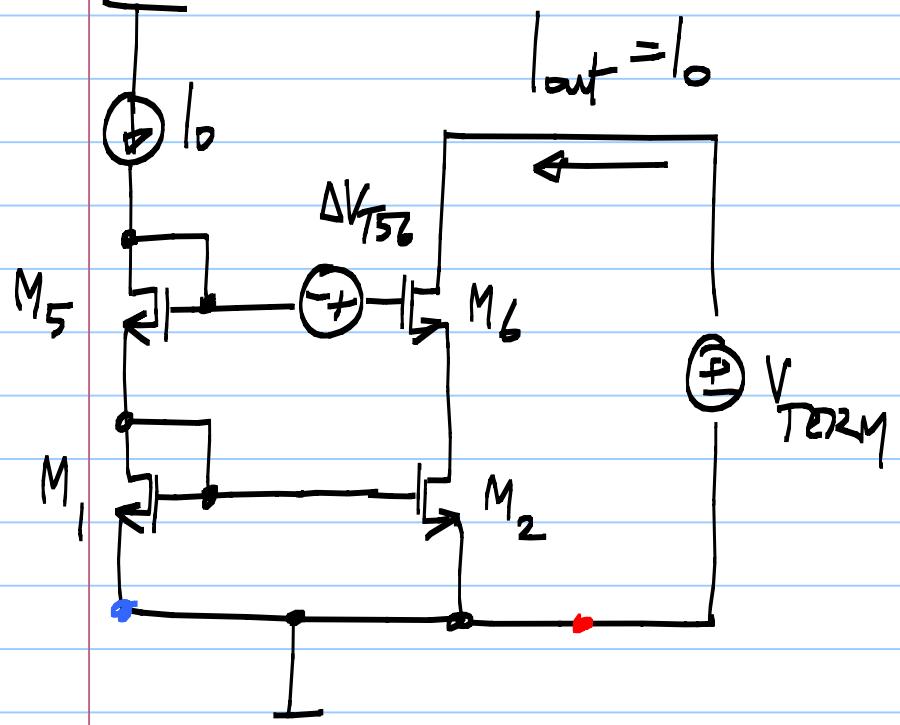
## Exercise:


- \* Calculate the total noise  $i_{in,out} \{ S_{in,out} \}$
- \* Calculate the mismatch induced error in  $I_{out}$

Identify the contribution of individual transistors



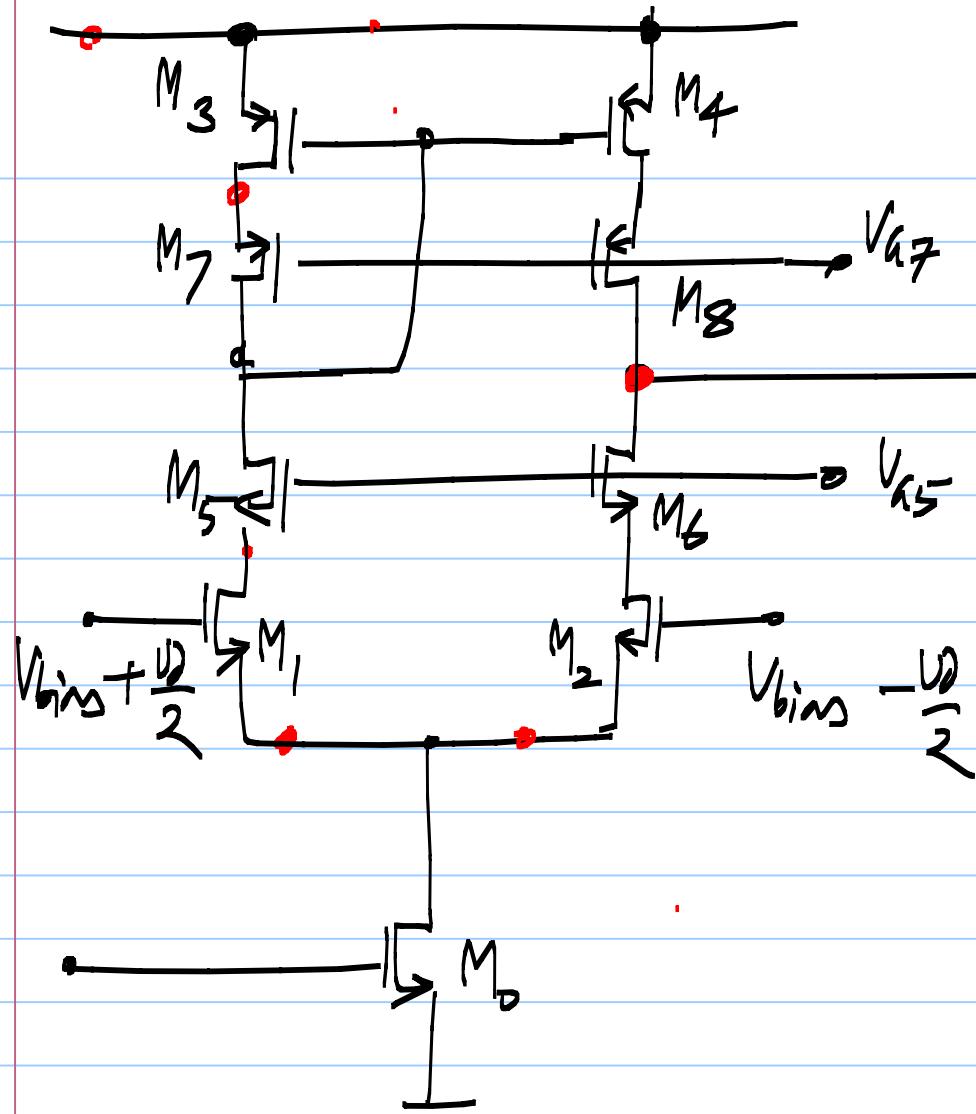

Noise, in, out	
$M_0$	0
$M_1$	$i_{n_1}$
$M_2$	$-i_{n_2}$
$M_3$	$i_{n_3}$
$M_4$	$-i_{n_4}$
$M_5$	0
$M_6$	0
$M_7$	0
$M_8$	0

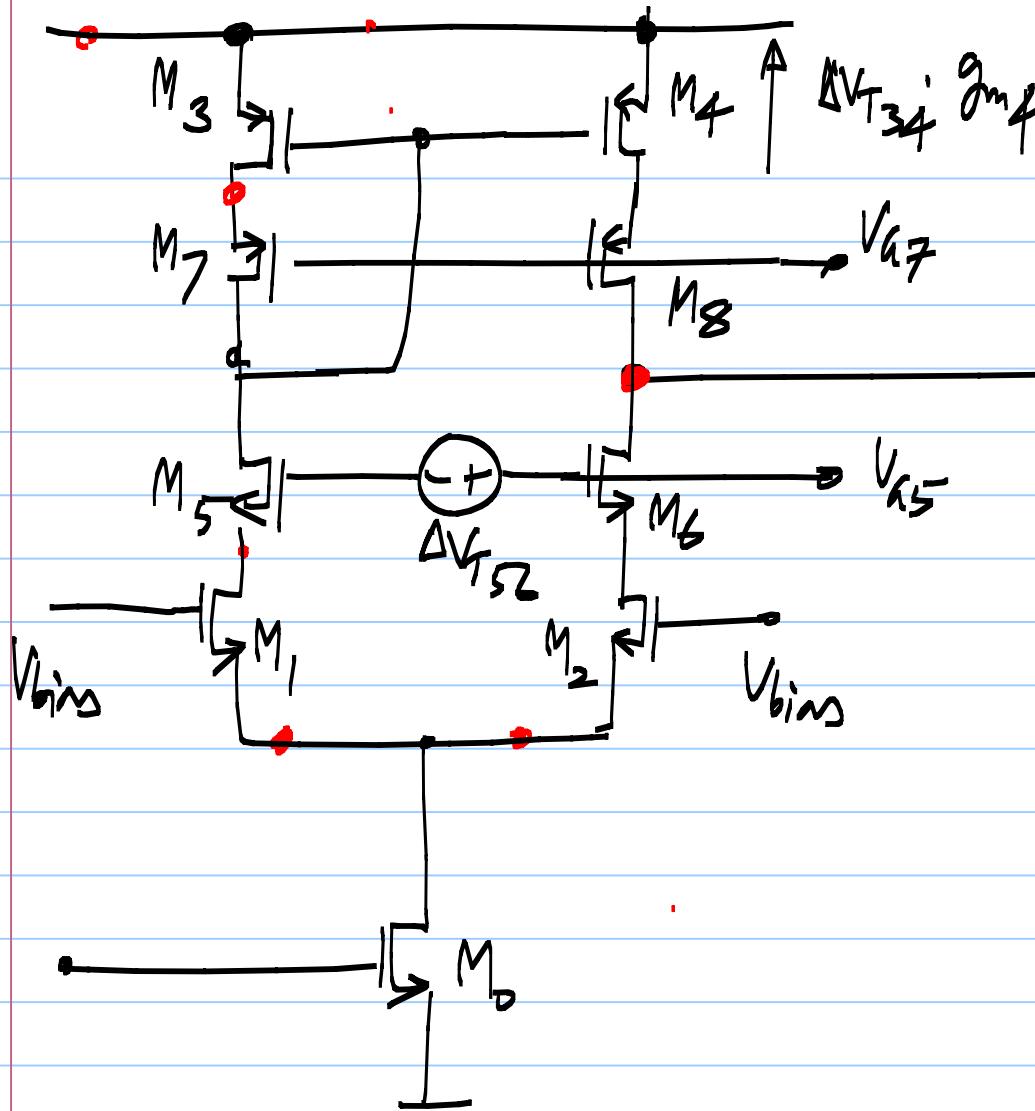

$$\Delta V_{T34} \cdot g_{m4}$$

$i_{out}$

$$\Delta V_{T12}$$

$$g_m \cdot \Delta V_{T12}$$

$$\Delta V_{T34}$$

$$- g_m \cdot \Delta V_{T34}$$

$$\Delta V_{T52}$$

0

$$\Delta V_{T78}$$

0

$$i_{out} = i_{n_1} - i_{n_2} + i_{n_3} - i_{n_4}$$



$$S_{i_{out}} = S_{i_{n_1}} + S_{i_{n_2}} + S_{i_{n_3}} + S_{i_{n_4}}$$


$$= \frac{16}{3} kT \cdot (g_{m_1} + g_{m_3})$$

$$S_{v_{in}} = \frac{S_{i_{out}}}{g_m^2} = \frac{16}{3} \frac{kT}{g_{m_1}} \left( 1 + \frac{g_{m_3}}{g_{m_1}} \right)$$

$$\underline{\sigma_{v_{os}}^2 = \sigma_{V_{T12}}^2 + \sigma_{V_{T34}}^2 \cdot \left( \frac{g_{m_3}}{g_{m_1}} \right)^2}$$

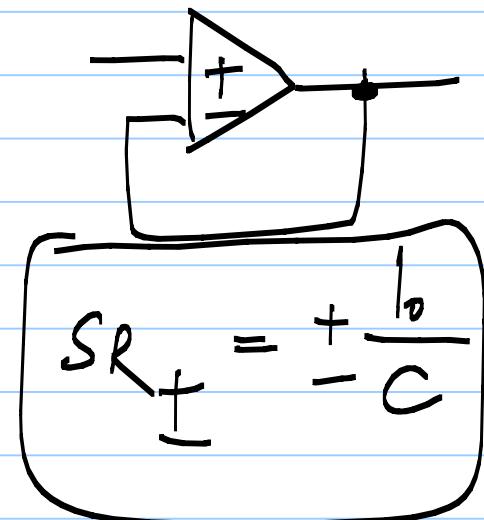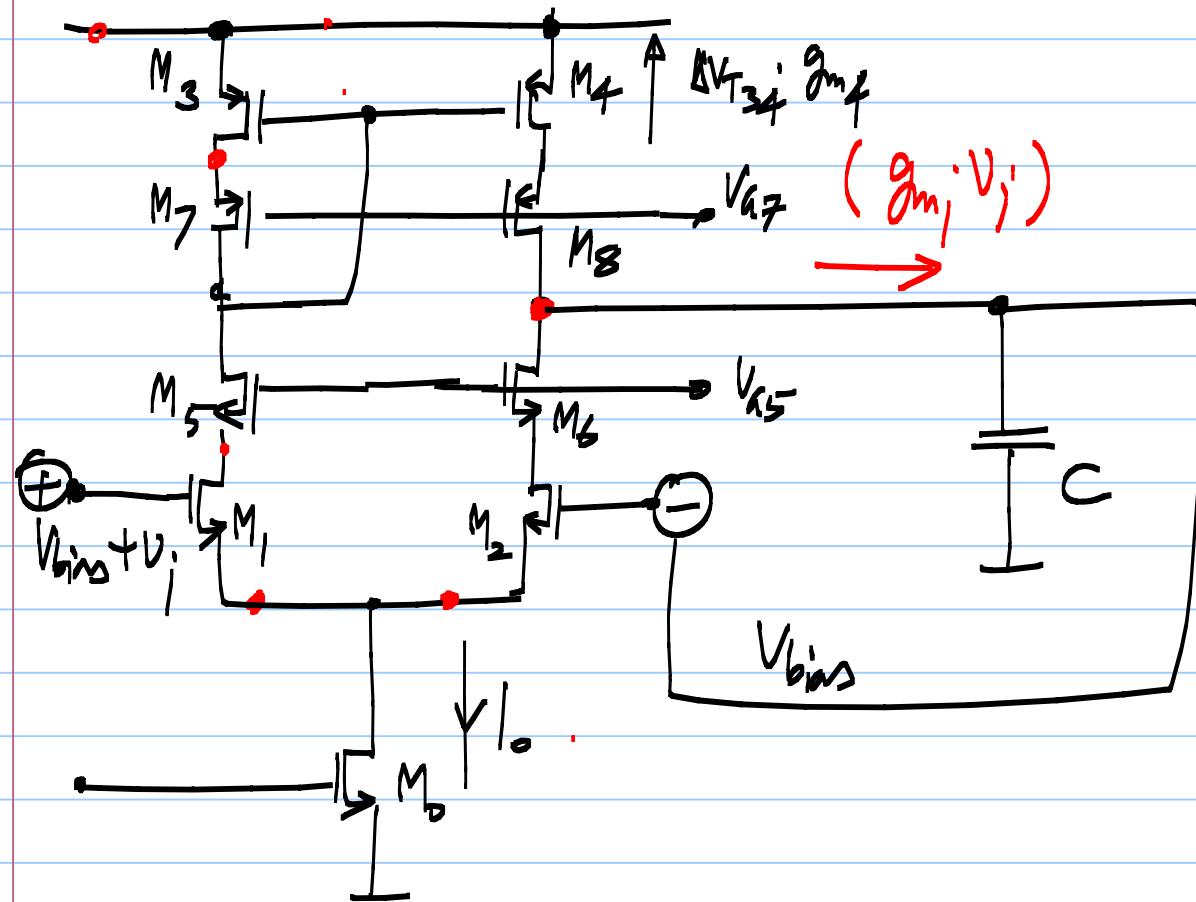Slew rate of the telescopic cascode opamp.



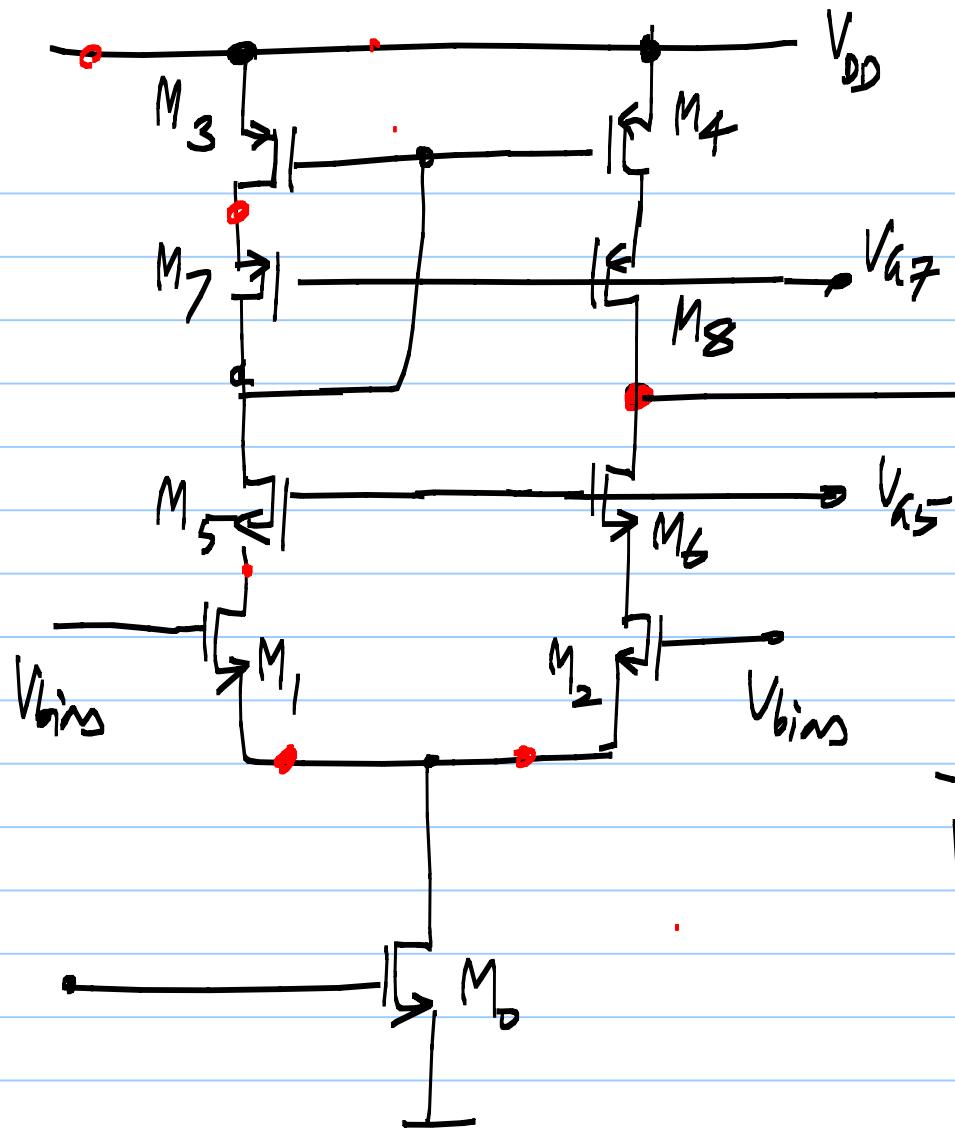

$$V_{G5} - V_{T5} < V_{out} < V_{G7} + V_{T7}$$

$V_{out}$

$$V_{G7,max} = V_{DD} - V_{DSAT_3}$$

$$- \frac{V_{G7}}{I_D/2}$$

$$V_{G5,min} = V_{bias} - V_T + V_{GS5} \Big|_{I_D/2}$$

$$V_{DSAT_0} + V_{T_1} < V_{bias} < V_{G_5} - V_{T_5} - V_{DSAT_5} + \frac{V_r}{2}$$

# Telescopic cascade vs. the Differential pair

- \* gain is higher
  - \* swing limit; smaller
  - \* Noise, offset,  $w_u$ , SR similar
  - \* Many more parasitic poles