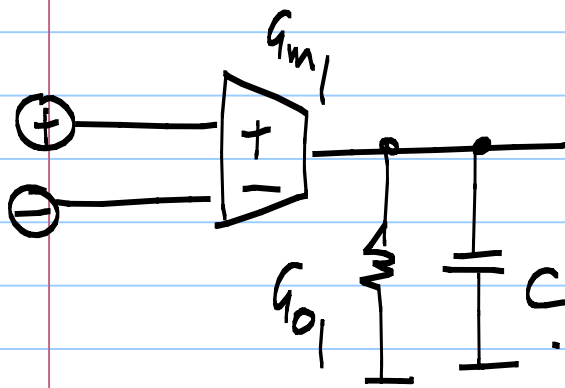



Lecture 36 : Two stage opamp

CCVS



$$A_D = \frac{g_{m1}}{g_{o1}}$$


$$\omega_u = \frac{g_{m1}}{C}$$

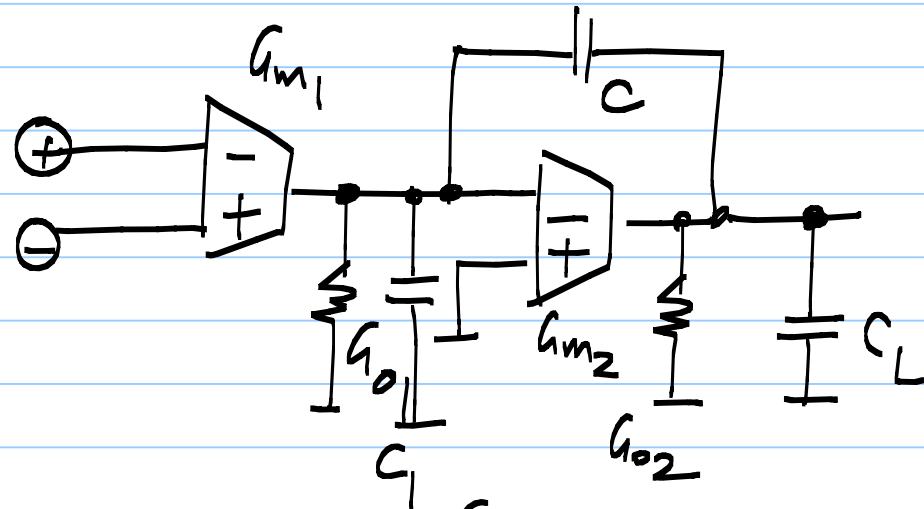


$$A_D = \frac{g_{m1}}{g_{o1}} \cdot \frac{g_{m2}}{g_{o2}}$$

$$\omega_u = \frac{g_{m1}}{C}, \quad |P_2| = -\frac{g_{m2}}{C_L + C}$$

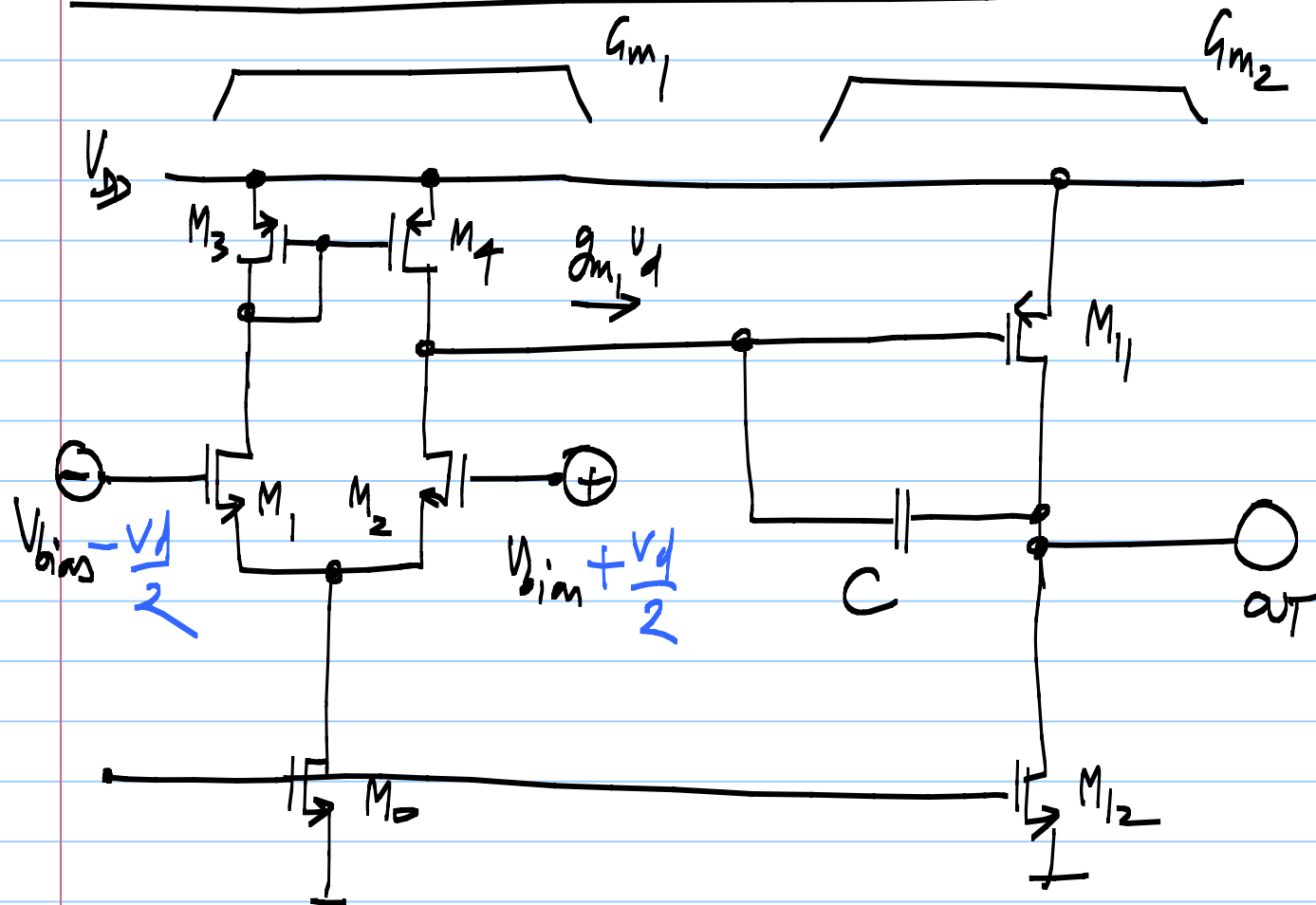First stage: G_{m1} : Differential pair transconductor



Two stage
miller -
compensated
opamp.

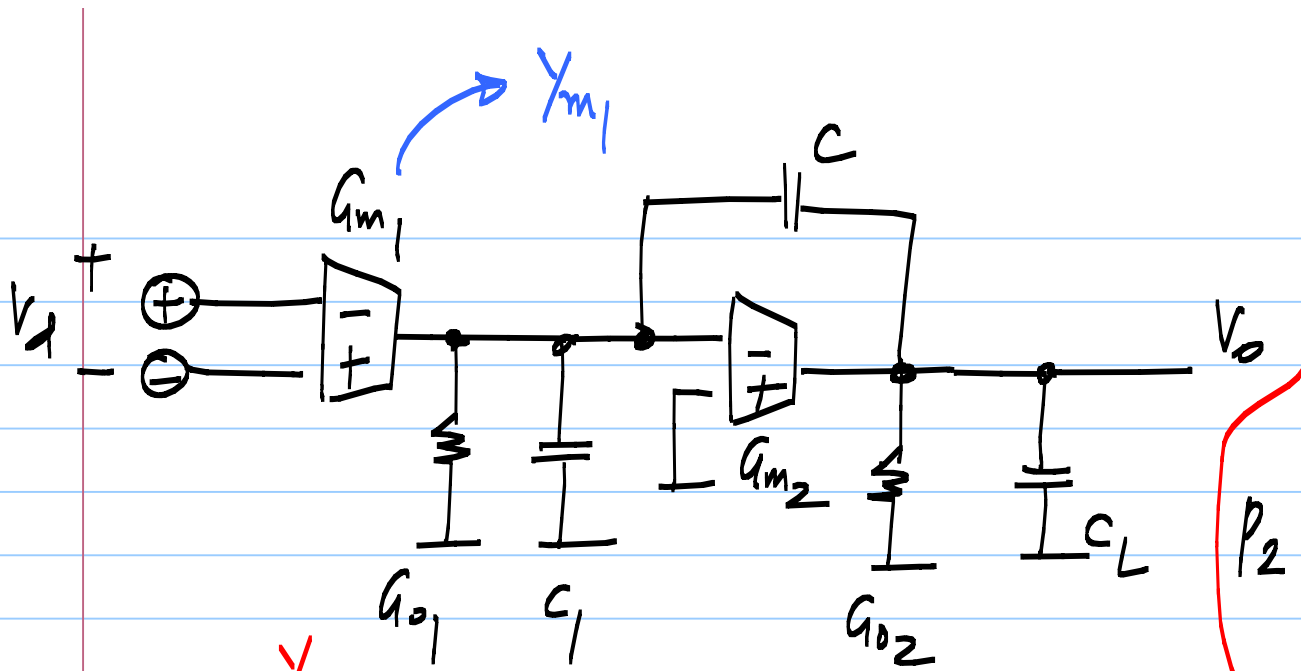


$$z_1 = g_{m2} / C$$

$$p_1 \approx \frac{g_{o1}}{C_1 + C \left(\frac{g_{m2}}{g_{o2}} + 1 \right)}$$

$$p_2 \approx \frac{g_{m2} \cdot \frac{C}{C+C_1} + g_{o2}}{C_L + \frac{CC_1}{C+C_1}}$$
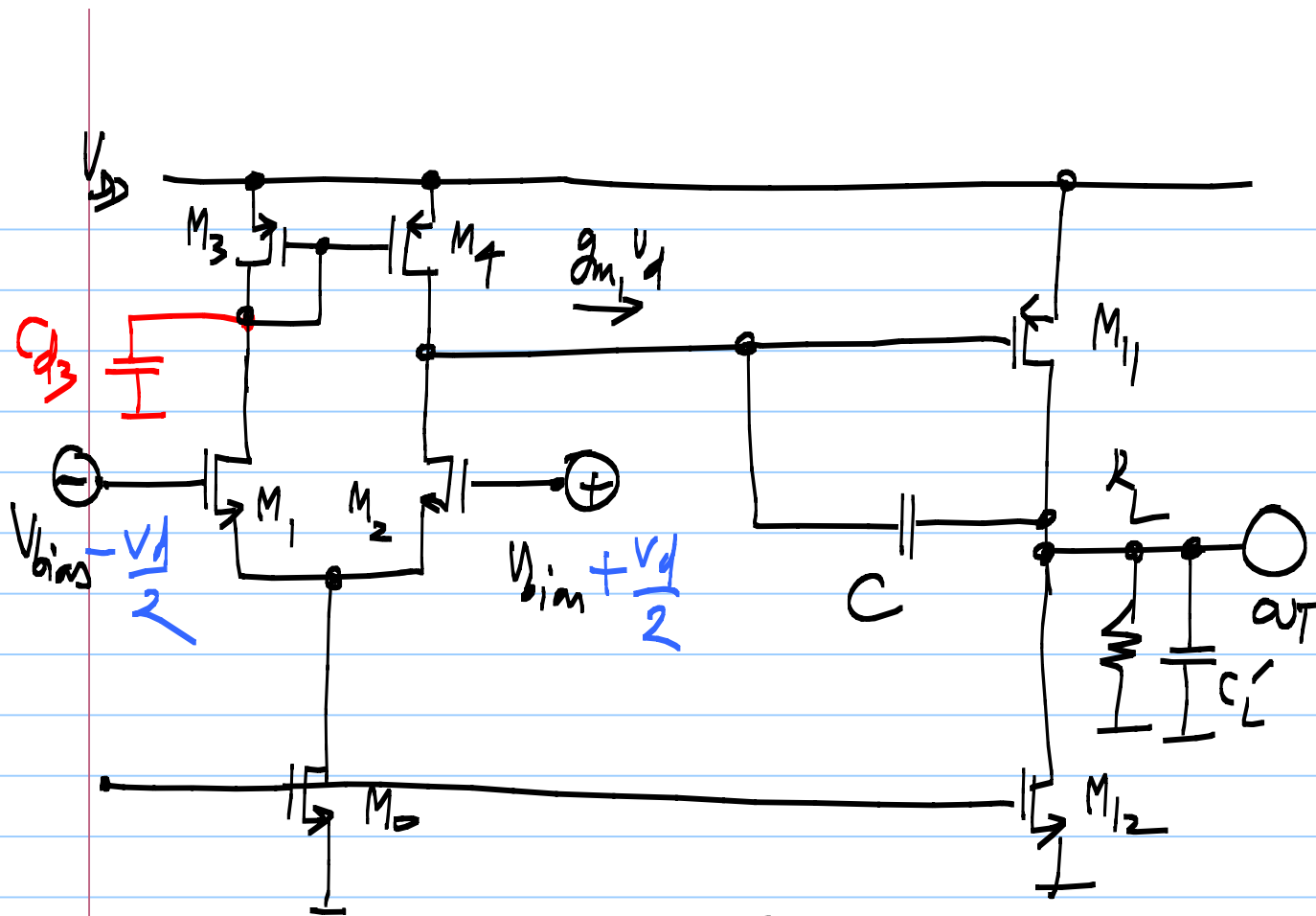
$$\frac{V_o}{V_d} = \frac{\cancel{g_{m1}} g_{m2}}{g_{o1} \cdot g_{o2}} \cdot \frac{(1 - s/z_1)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$



$$Y_m(s) = g_{m1} \cdot \frac{1 + s \cdot \frac{C_{d3}}{2g_{m3}}}{1 + s \cdot \frac{C_{d3}}{g_{m3}}}$$

$$C_1 = C_{db4} + C_{db2} + C_{gs11}$$

$$C_L = C'_L + C_{db11} + C_{db12}$$

$$G_{o1} = g_{ds9} + g_{ds3}$$

$$G_{o2} = g_{ds11} + g_{ds12} + G_L$$

$$G_{m2} = g_{m11}$$

$$A_0 = \frac{g_{m1}}{g_{ds1} + g_{ds3}} \cdot \frac{g_{m11}}{g_{ds11} + g_{ds12}}$$

$$\omega_u = \frac{g_{m1}}{C}$$

$$p_2 = - \frac{g_{m11} \cdot \frac{C}{C+C_1} + g_{o2}}{\frac{C \cdot C_1}{C+C_1} + C_L} ; \quad p_3 = - \frac{g_{m3}}{C_{d3}}$$

$$z_1 = + \frac{g_{m11}}{C} ; \quad z_2 = - \frac{2 \cdot g_{m3}}{C_{d3}}$$

$$A_b = 1000$$

$$R_L = 1k\Omega$$

$$G_L = 1mS$$

$$G_{m1} = 1000mS \\ = 1S$$

(single stage opamp)

$$1000mS$$

$$A_b = 100 \times 10$$


$$G_L = 1mS$$

$$G_{m2} = 10mS$$

$$\left\{ \frac{G_{m1}}{G_{o1}} = 100 \right\}$$


$$G_{m1} = 2mS$$

$$12mS$$

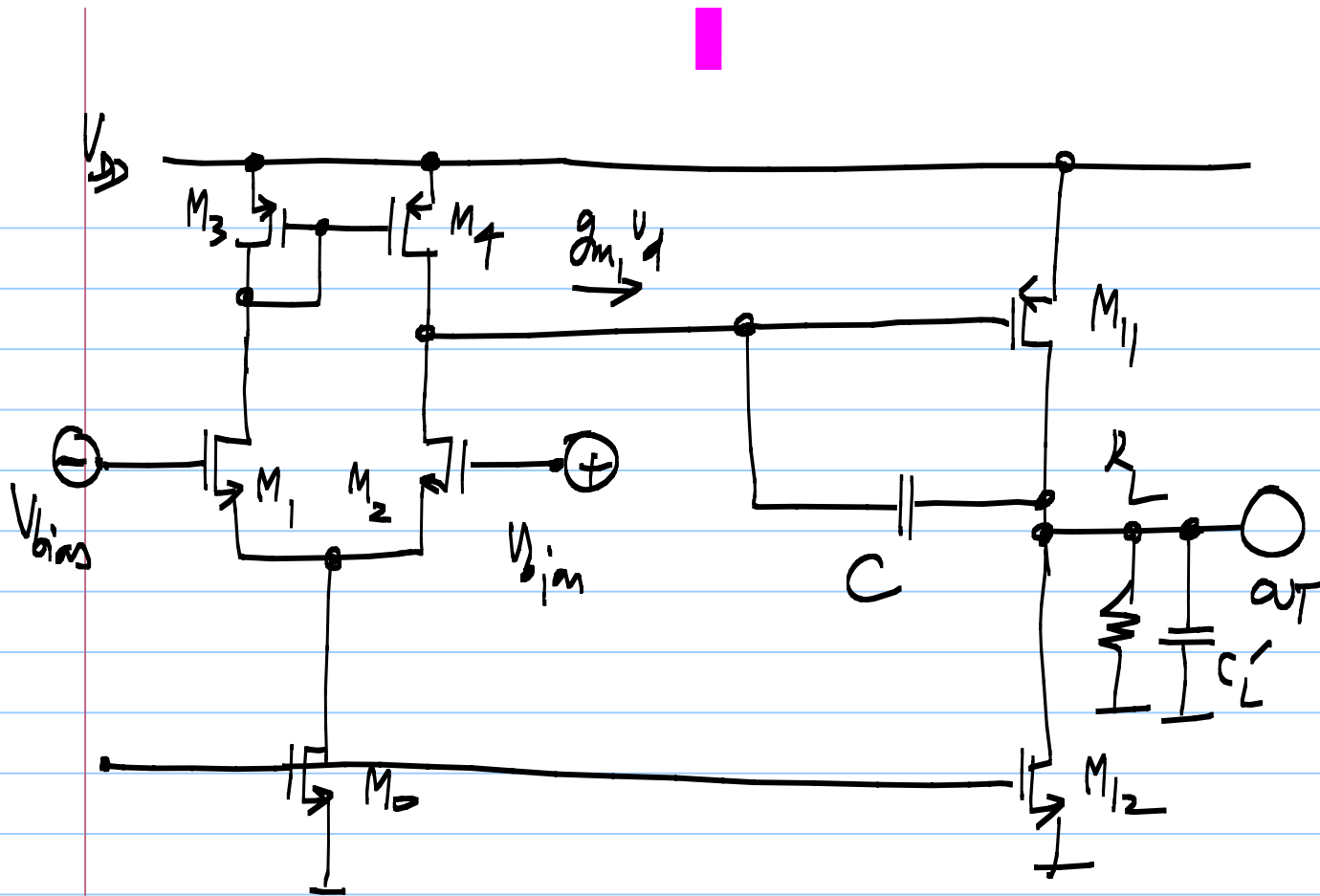

Noise
offset:
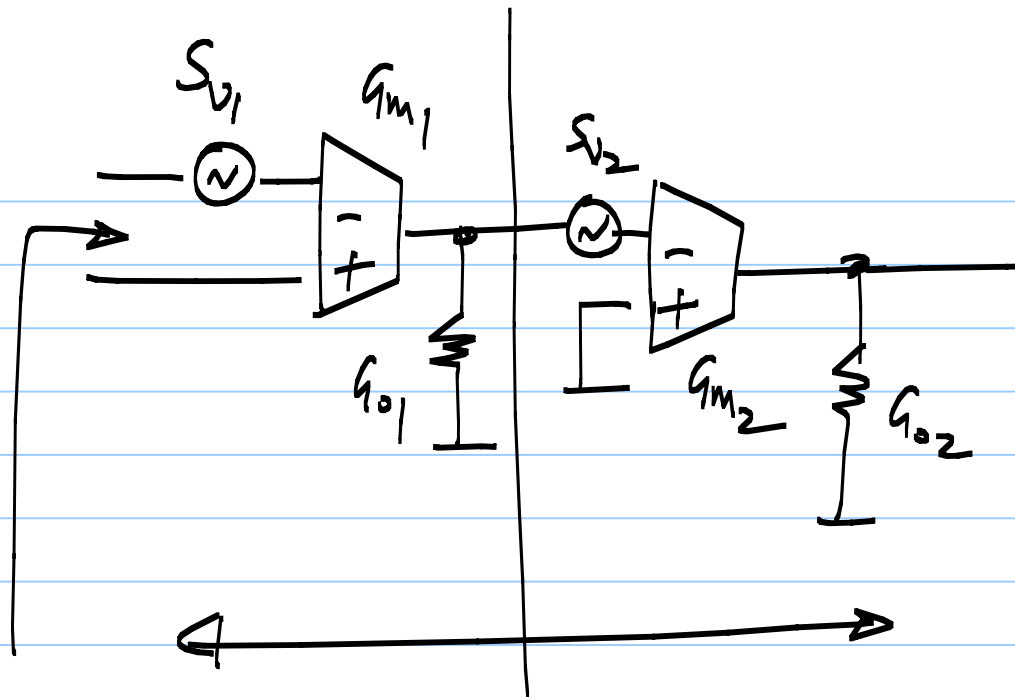
$$\frac{16}{3} \cdot \frac{kT}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right)$$



$$S_{v1} \left(\frac{g_{m1}}{g_{o1}} \cdot \frac{g_{m2}}{g_{o2}} \right)^2$$


$$+ S_{v2} \left(\frac{g_{m2}}{g_{o2}} \right)^2$$

$$\left(\frac{g_{m1}}{g_{o1}} \cdot \frac{g_{m2}}{g_{o2}} \right)^2$$



$$S_{v_{in}} = S_{v1} + S_{v2} \cdot \left(\frac{g_{o1}}{g_{m1}} \right)^2$$

$$S_{v_{in}} \approx \frac{16}{3} \cdot \frac{kT}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right)$$

(2 stage opamp)

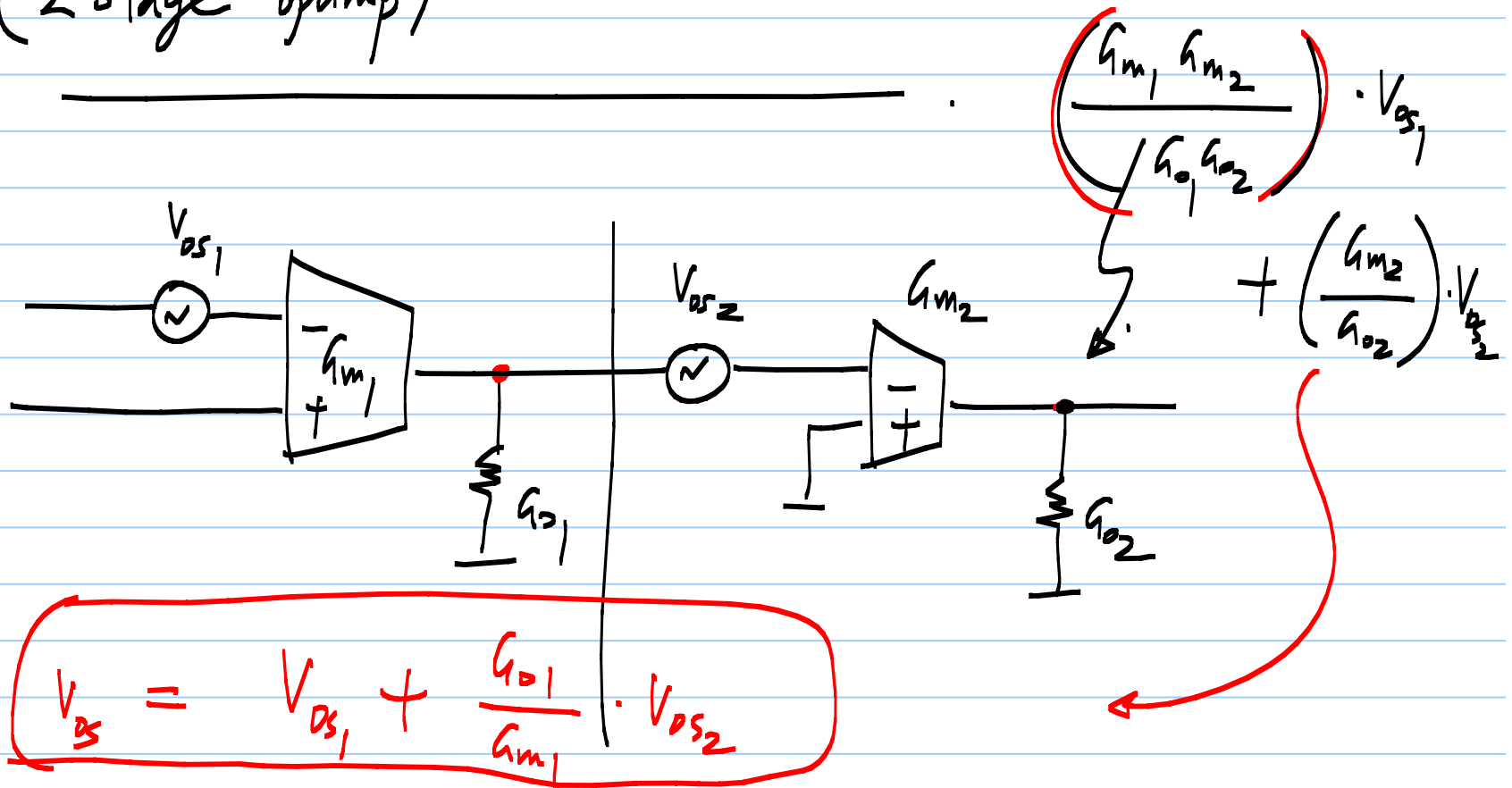
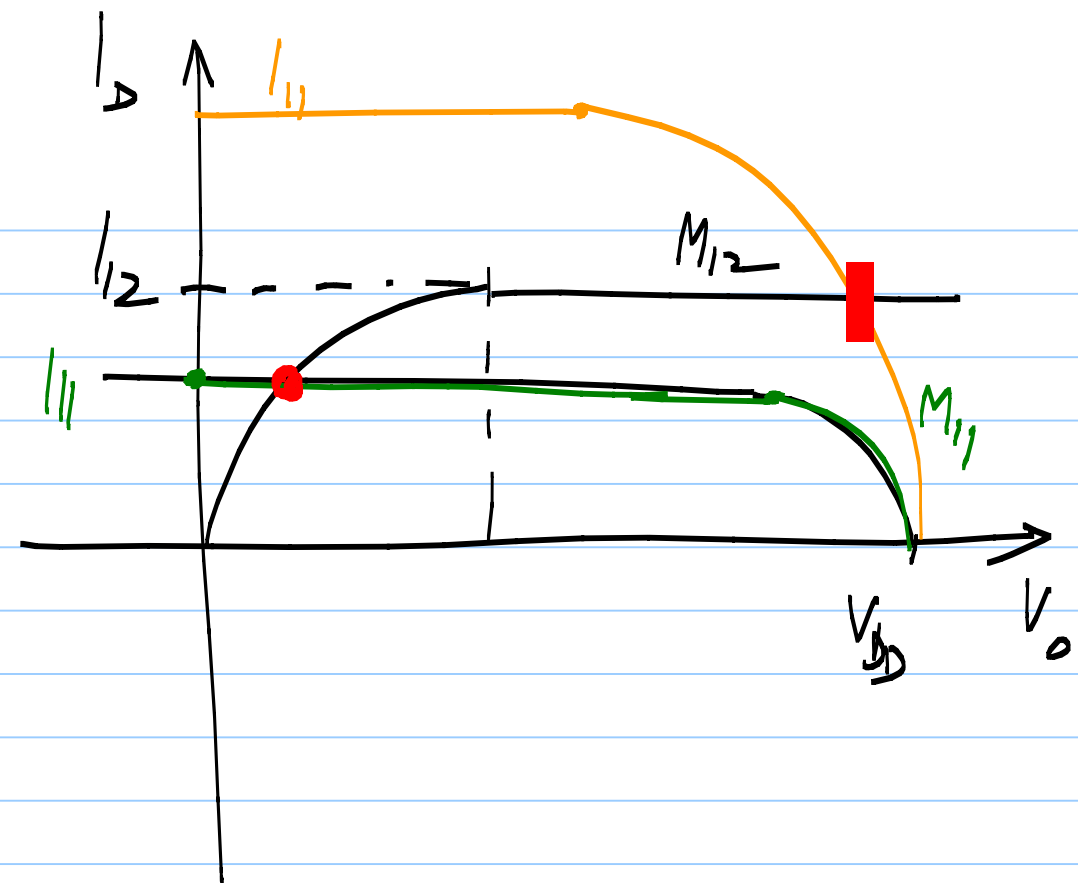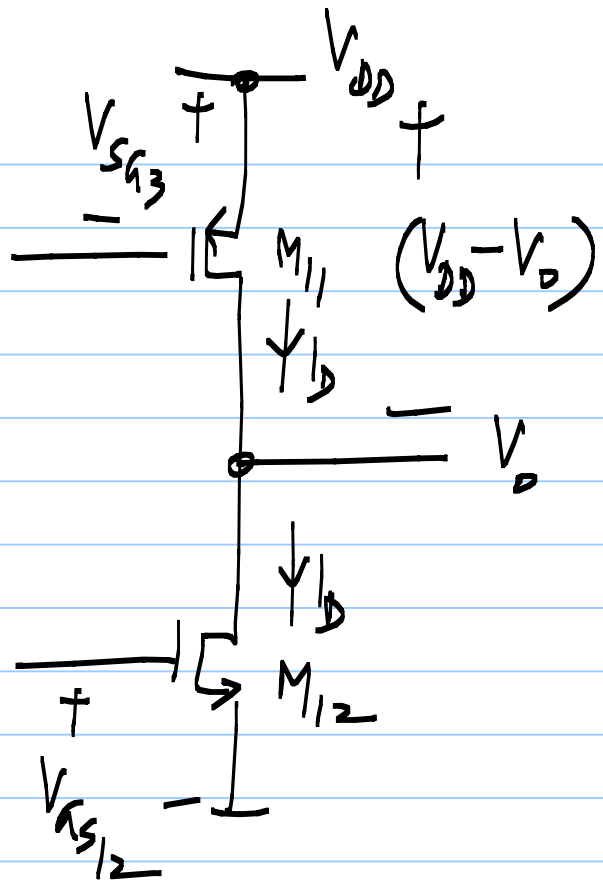
$$\sigma_{V_{05}}^2 = \sigma_{V_{T12}}^2 + \left(\frac{g_{m1}}{g_{m3}} \right)^2 \sigma_{V_{T34}}^2$$



Systematic offset if $V_{SG3}|_{\frac{1}{2}} \neq V_{SG11}|_{\frac{1}{2}}$

$$\left\{ \begin{array}{l} \text{o/p of 1}^{\text{st}} \text{ stage} = V_{DD} - V_{SG3}|_{\frac{1}{2}} \\ \text{i/p req. for 2}^{\text{nd}} \text{ stage} = V_{DD} - V_{SG11}|_{\frac{1}{2}} \end{array} \right.$$

To avoid this :

$$V_{SG11}|_{\frac{1}{2}} = V_{SG3}|_{\frac{1}{2}}$$

$$V_{TP} + \sqrt{\frac{2 \cdot I_{O/2}}{\mu_p C_{ox} W_3 / L_3}} = V_{TP} + \sqrt{\frac{2 \cdot I_{I_2}}{\mu_p C_{ox} W_{I_1} / L_{I_1}}}$$

$$\left[\frac{I_{O/2}}{W_3 / L_3} = \frac{I_{I_2}}{W_{I_1} / L_{I_1}} \right]$$
