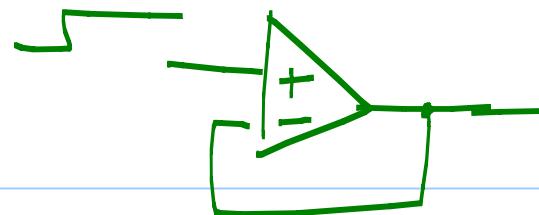




## Lecture 37:



Slew rate:

Rate of change of  
Voltage across C

$$(v_c) = \pm \frac{I_o}{C}$$

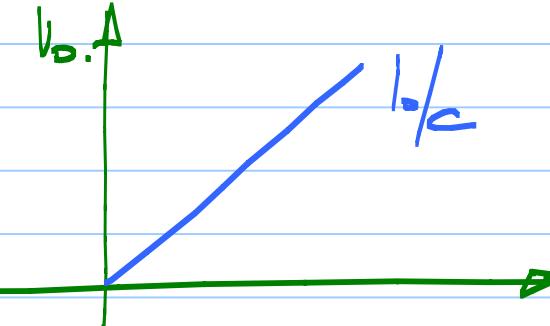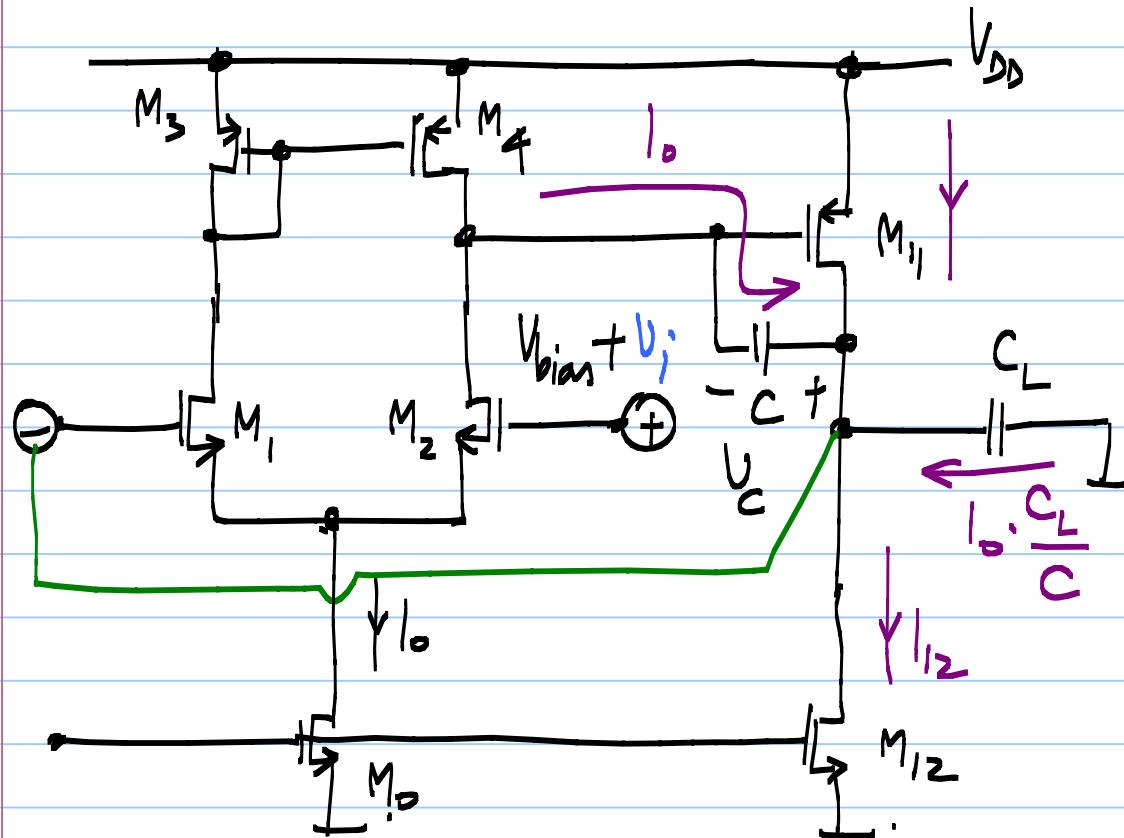

$$I_{D1} = I_{D2} - I_o \left( 1 + \frac{C_L}{C} \right)$$

$$I_{D1} = I_{L2} - I_o \left( 1 + \frac{C_L}{C} \right) > 0$$

If  $I_{L2} > I_o \left( 1 + \frac{C_L}{C} \right)$ ; output will reduce  
 @  $\frac{I_o}{\frac{C_L}{C}}$

$$I_{L2} < I_o \left( 1 + \frac{C_L}{C} \right) ?$$


output slew rate =  $\frac{I_{L2}}{C_L + C}$

Total current in  $C$  &  $C_L$   
 $= I_{L2}$

$$SR_+ = \frac{I_o}{C}$$
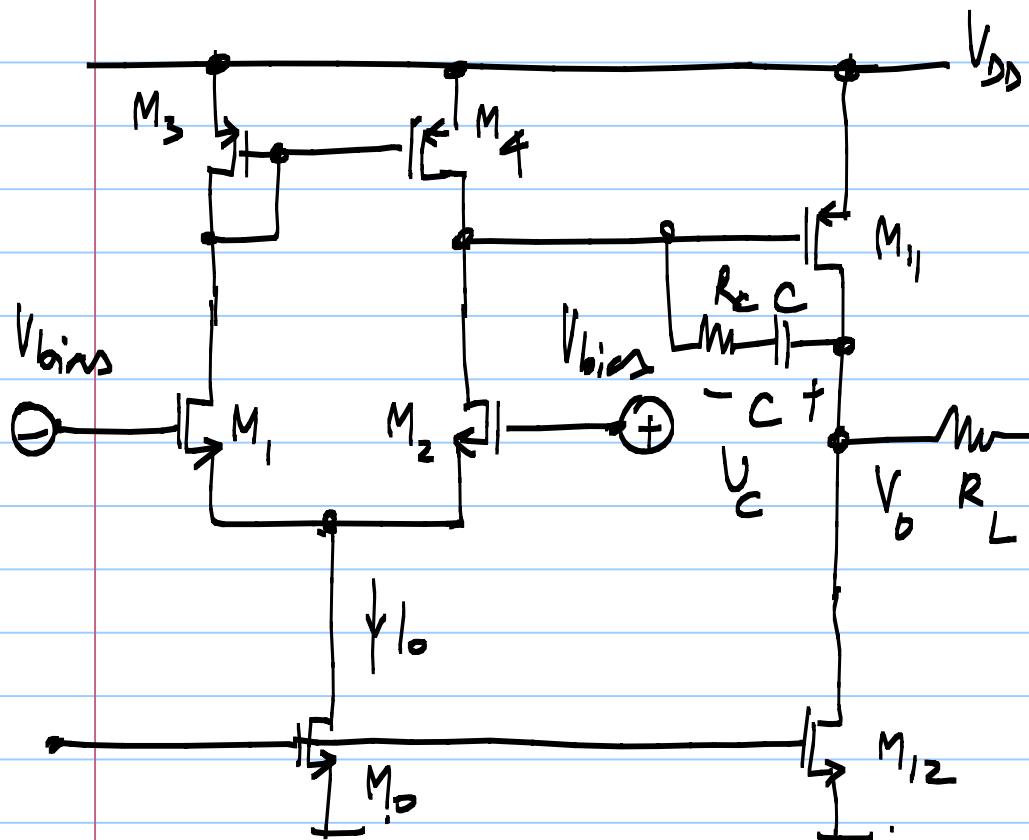
$$SR_- = \min \left[ \frac{I_o}{C}, \frac{I_2}{C_L + C} \right]$$





$$\left[ \begin{array}{l} V_{T_1} + V_{DSAT_1} < V_{bias} < V_{DD} - V_{SG3} + V_{T_1} \\ + V_{DSAT_0} \end{array} \right]$$

$$\left[ \begin{array}{l} V_{DSAT_{12}} < V_0 < V_{DD} - V_{DSAT_{11}} \end{array} \right]$$

$R_C$  in series with  $C$   
to cancel the  $R_H^0$   
zero

## Two stage opamp:

$$A_v = \frac{g_{m1}}{g_{ds1} + g_{ds3}} \circ \frac{g_{m11}}{g_{ds11} + g_{ds12} + g_L}$$

$$H(s) = A_v \left( \frac{1 + s \frac{g_B}{2g_{m3}}}{1 + s \frac{g_{ds3}}{g_{m3}}} \right) \cdot \frac{1 - s/z_1}{\left( 1 + \frac{s}{P_1} \right) \left( 1 + \frac{s}{P_2} \right)}$$

$$S_{V_{in}} = \frac{16}{3} \cdot \frac{kT}{g_{m1}} \left( 1 + \frac{g_{m3}}{g_{m1}} \right)$$


$$\sigma_{V_{BS}}^2 = \sigma_{V_{T12}}^2 + \left( \frac{g_{m3}}{g_{m1}} \right)^2 \sigma_{V_{T34}}^2$$

$$\omega_R = 1/C$$




$$\omega_L = \min \left( \frac{1}{C}, \frac{1}{L+C} \right)$$

$$V_{T1} + V_{DSAT0} < V_{bias} < V_D - V_{DSAT3} \\ + V_{DSAT1}$$
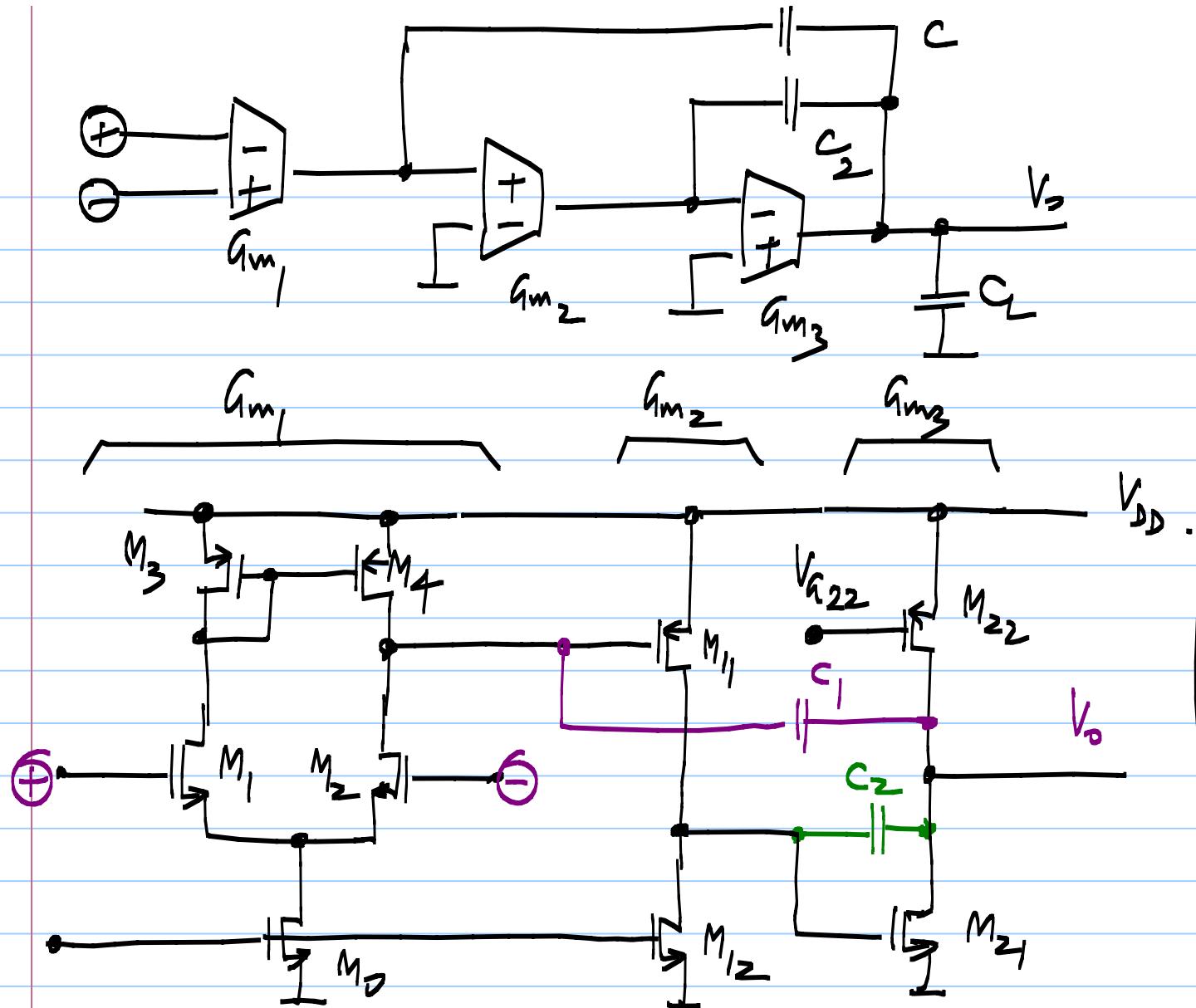
$$V_{DSAT2} < V_{out} < V_D - V_{DSAT1}$$




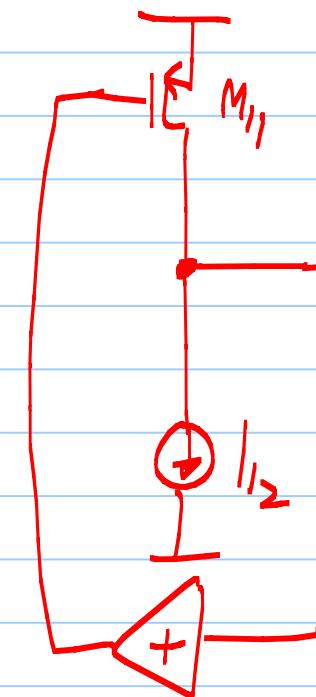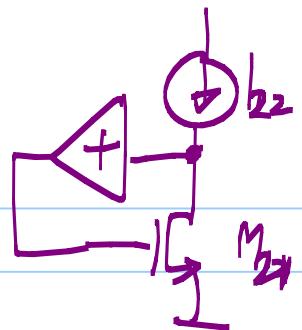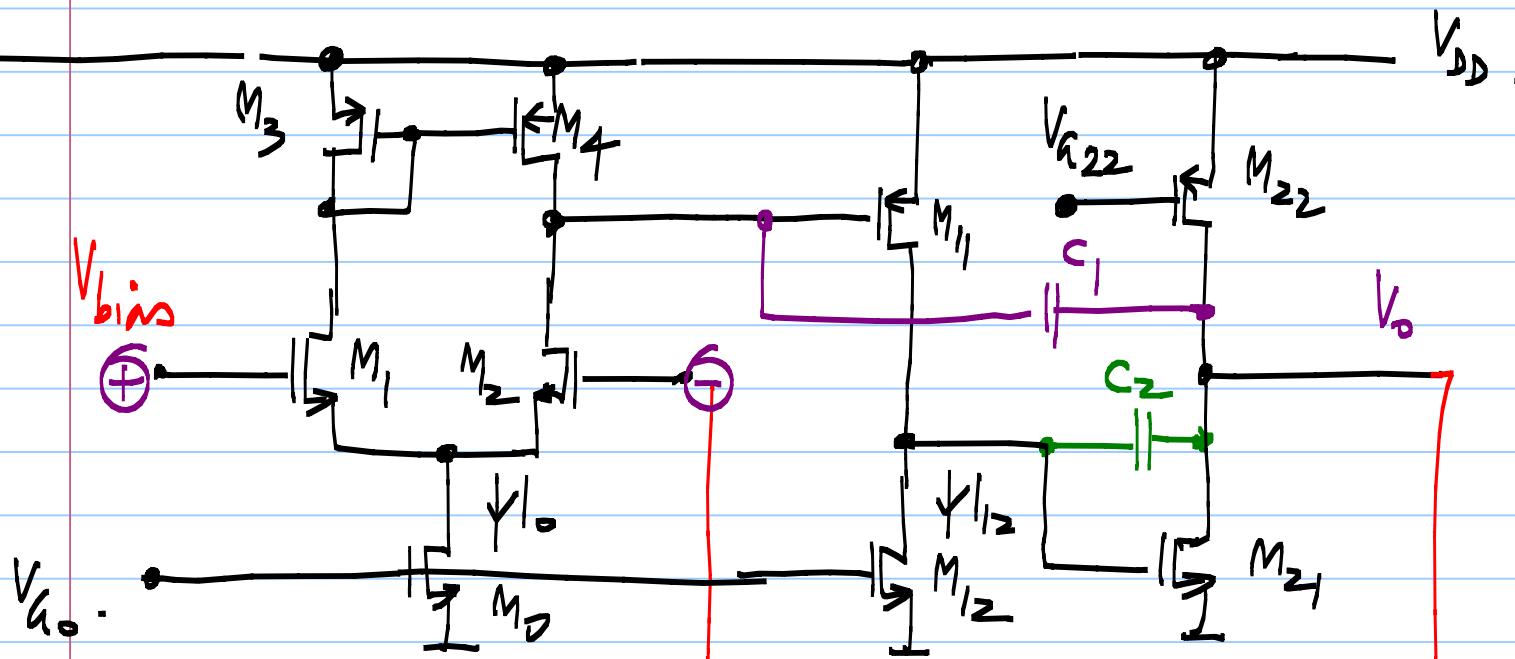Three  
stage  
nested  
Miller  
compensated  
opamp




$$\frac{I_o}{W_o} = \frac{I_2}{W_{12}} = \frac{I'_o}{W'_o} ; \quad L'_o = L_o = L_{12}$$

Single stage opamp

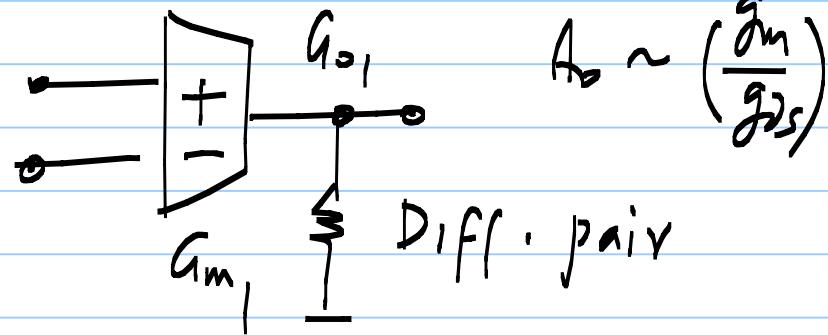


Two stage opamp

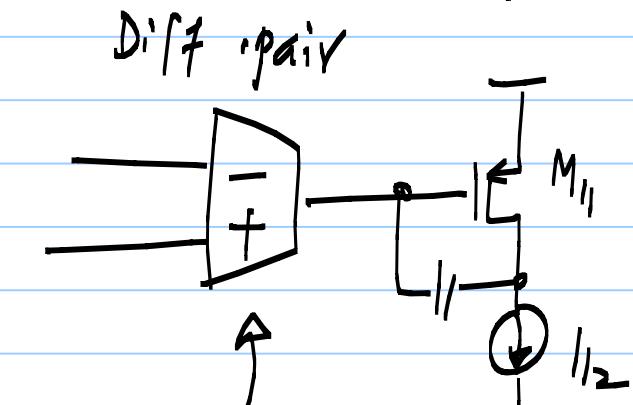

Telescopic /

Folded cascade

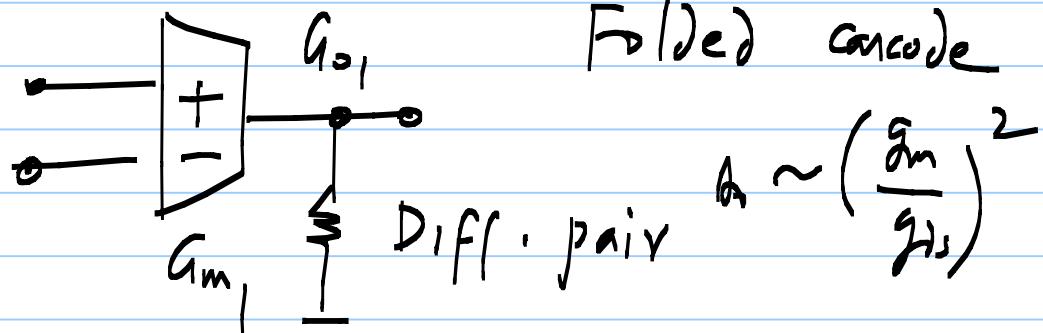

$$\left( \frac{g_m}{g_{D_s}} \right)^2 \left( \frac{g_{m11}}{g_{D_{s1}} + g_{D_{s2}} + g_{L2}} \right)$$

