

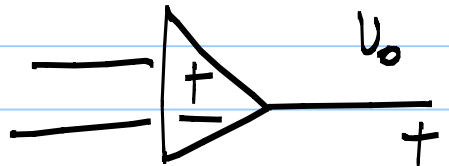


Lecture 39

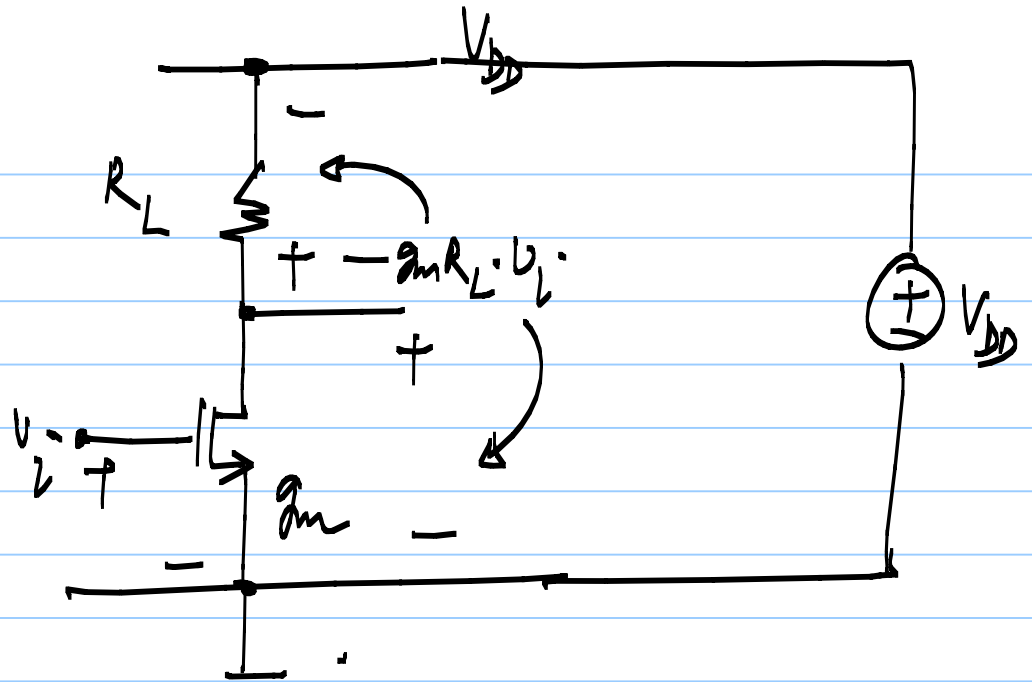

Com. ref.
point

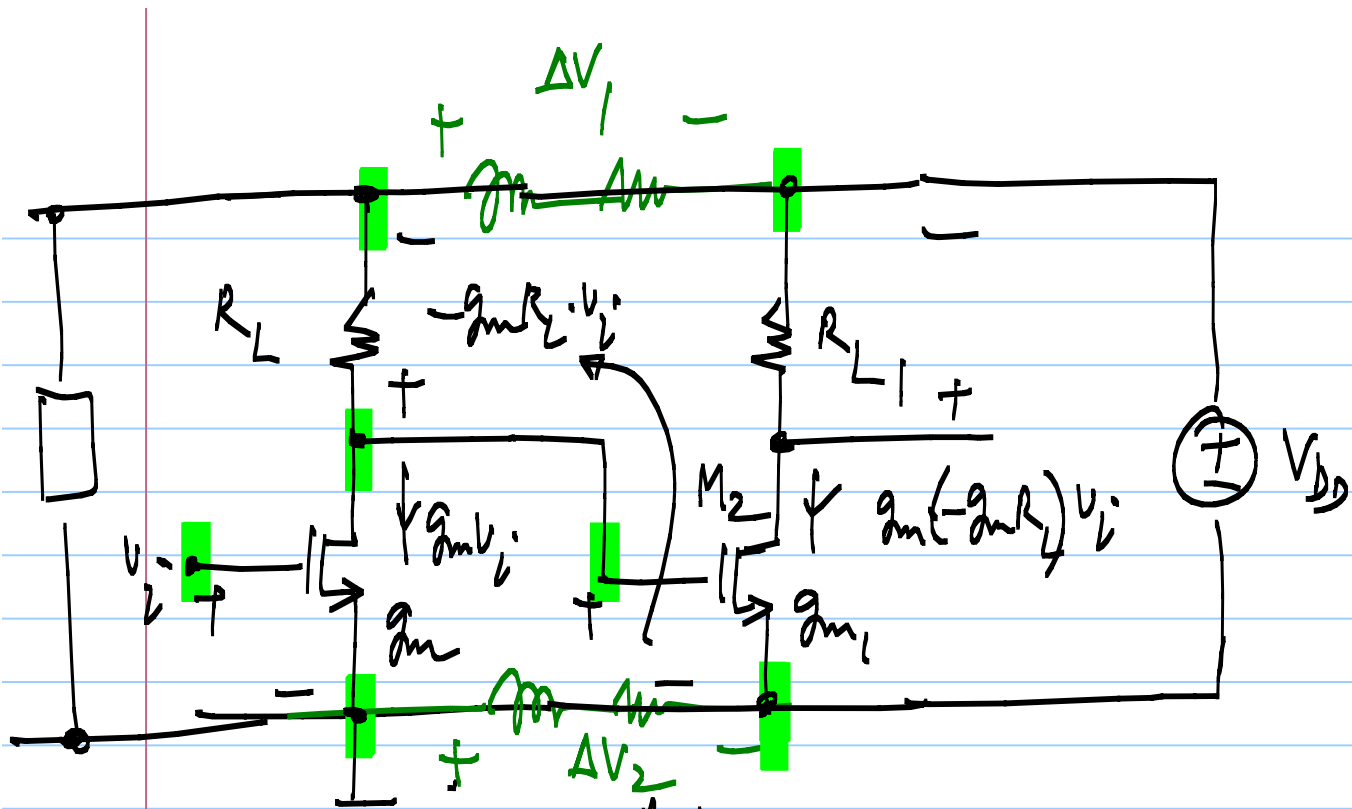





v_{as} of M_2 :

$$-g_m R_L v_i + \Delta V_1$$

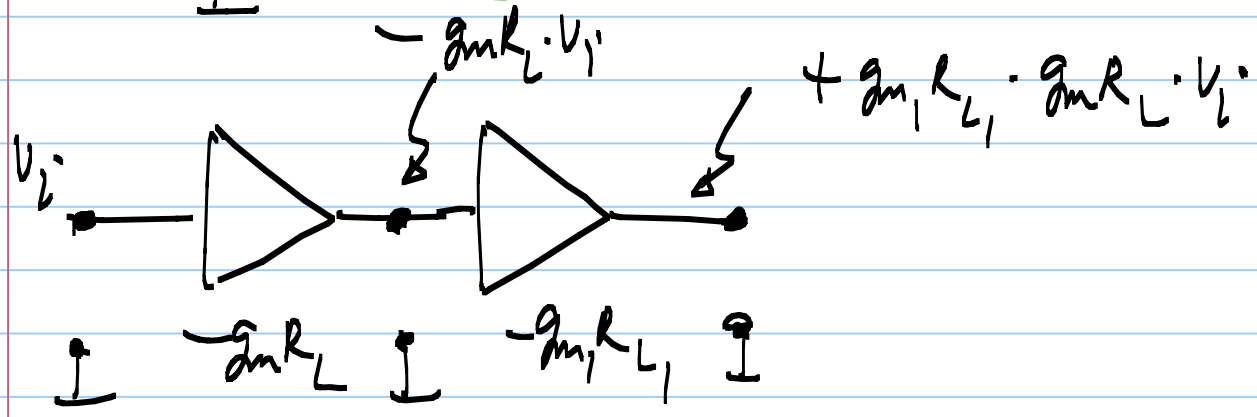depends on other circuits connected to the supply





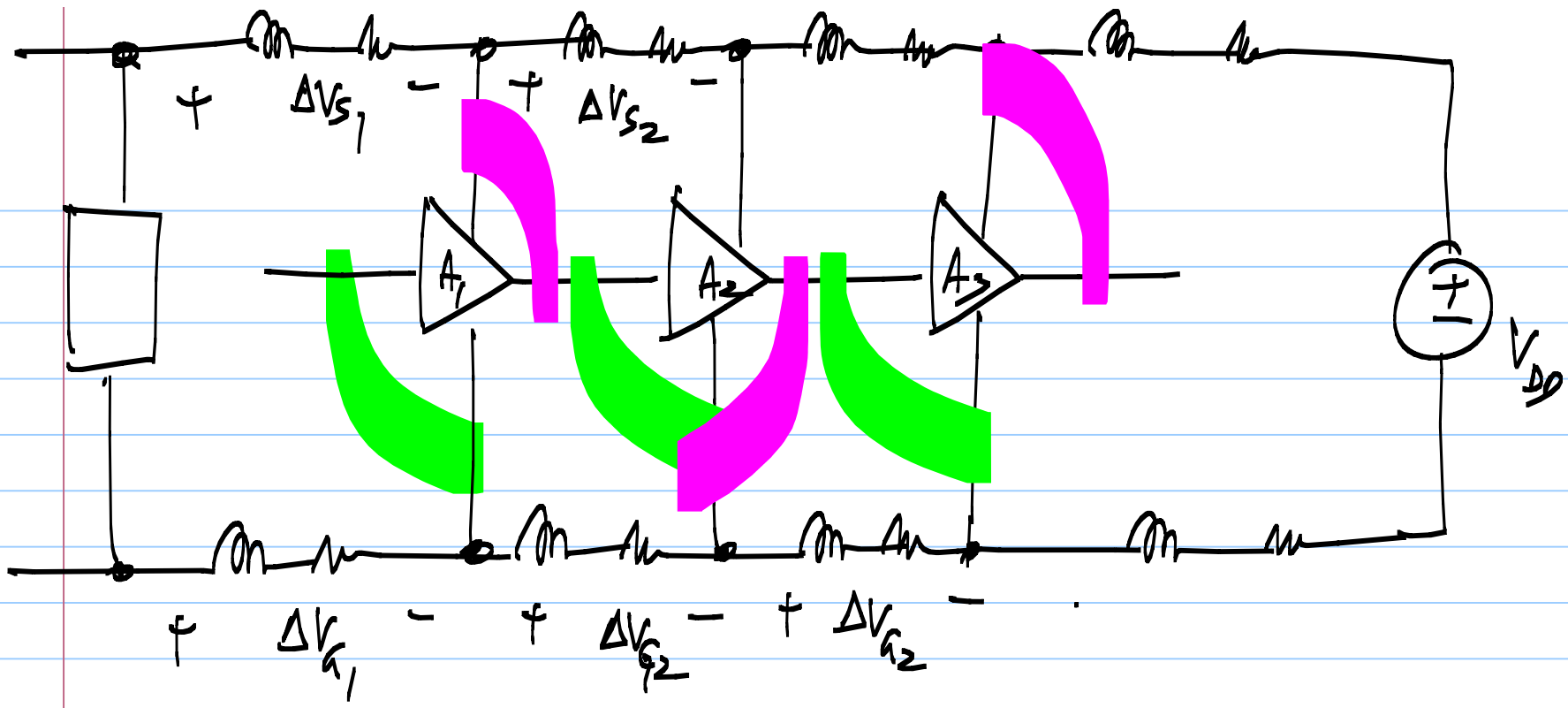



Problem:

defined
voltages between some node x
and common ground

Use two wires to define any signal
used only for the signal

Differential signalling

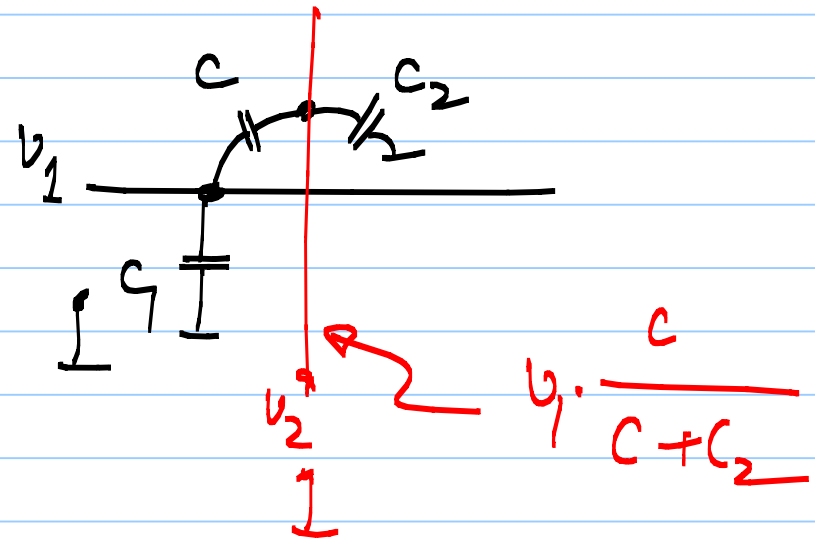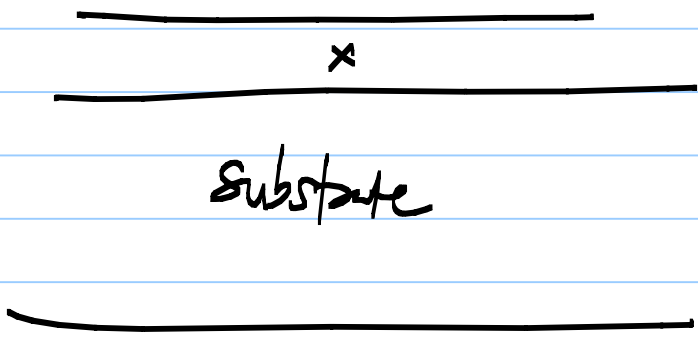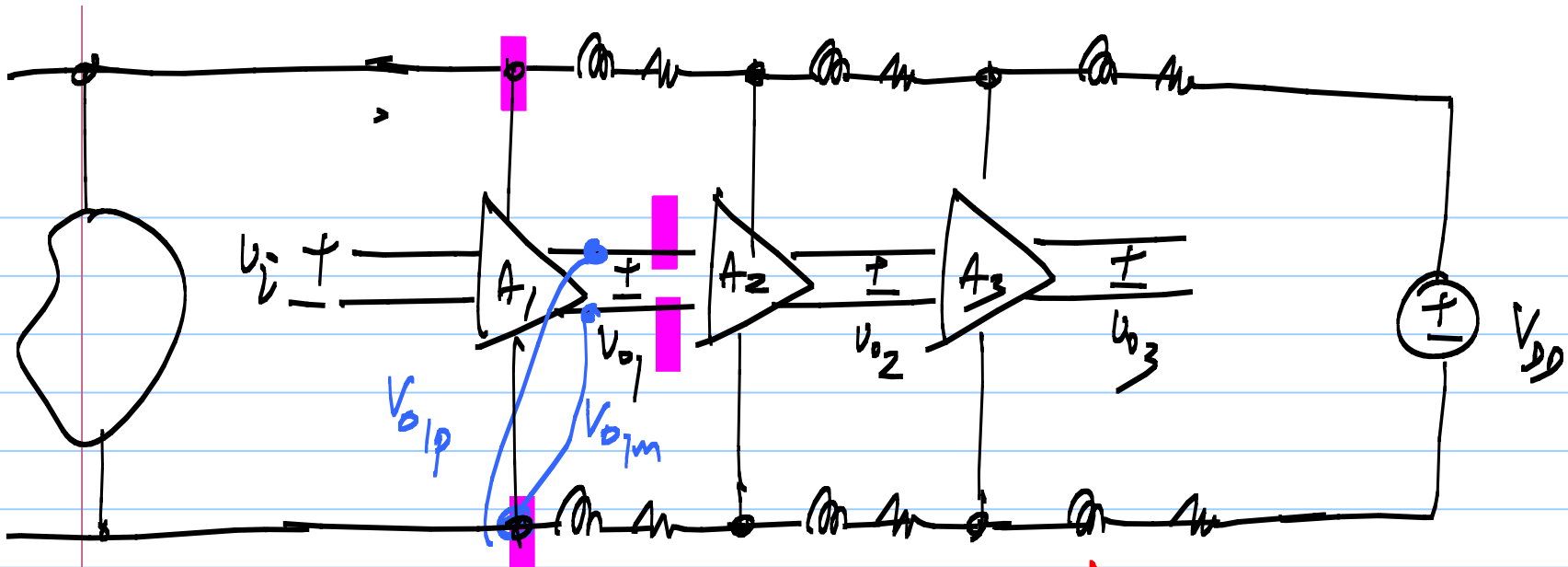


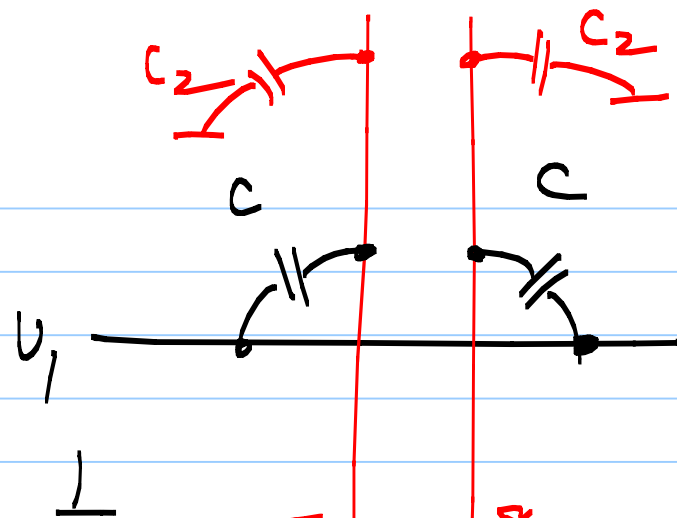

Cancelled out
in the difference

$$\frac{C_1}{C + C_2} \cdot v_1$$

$$\frac{C}{C + C_2} \cdot v_1$$

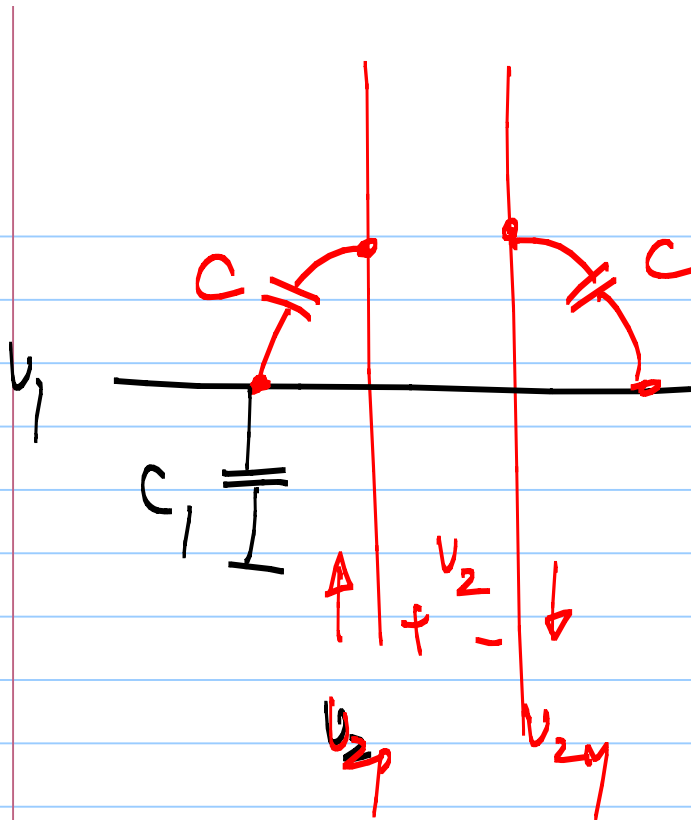

$$v_{2p} \cdot \frac{C}{C+C} + v_{2n} \cdot \frac{C}{C+C_1}$$



$$v_{2p} = -v_{2n} = \frac{v_2}{2}$$

Fully differential signalling:

* A pair of wires carry any given signal



* Each wire has a voltage $\frac{V}{2}$, $-\frac{V}{2}$ wrt common ground in the ckt.

* Less interference due to common voltage drops in supply & ground lines

* Less interference from other sources

* Lesser generation of interference.

Differential pair:

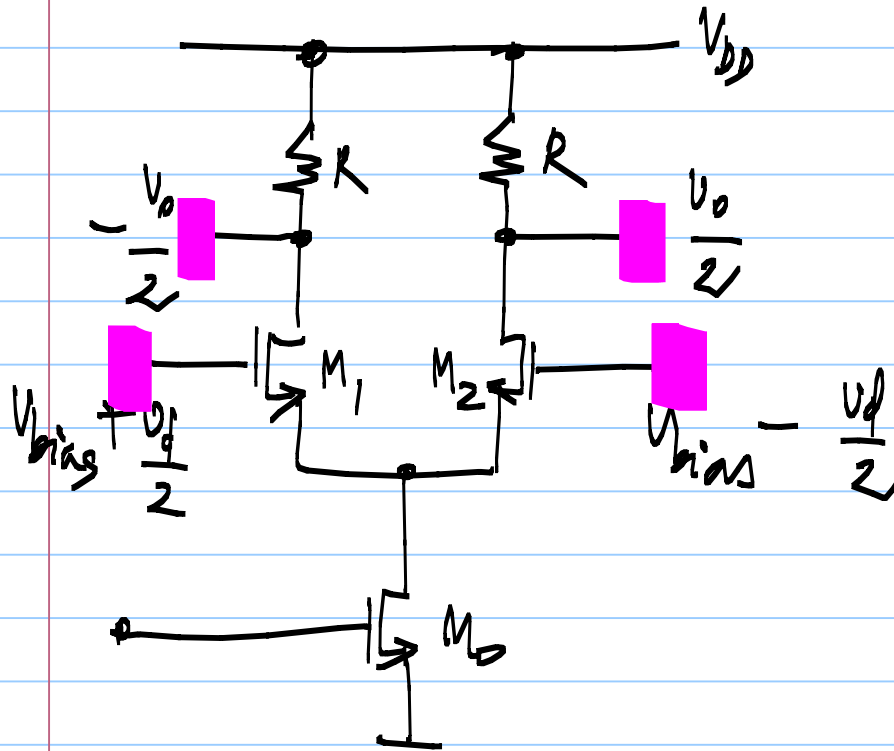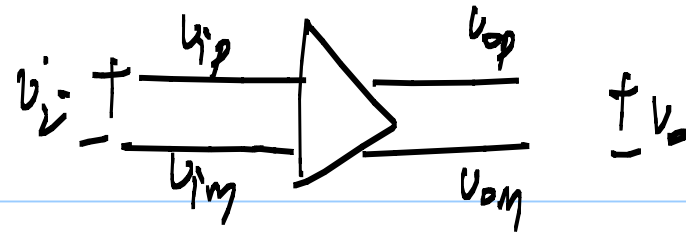



Fully differential signals
are handled by fully
differential circuits

Fully differential o/p


Differential i/p

Common mode i/p

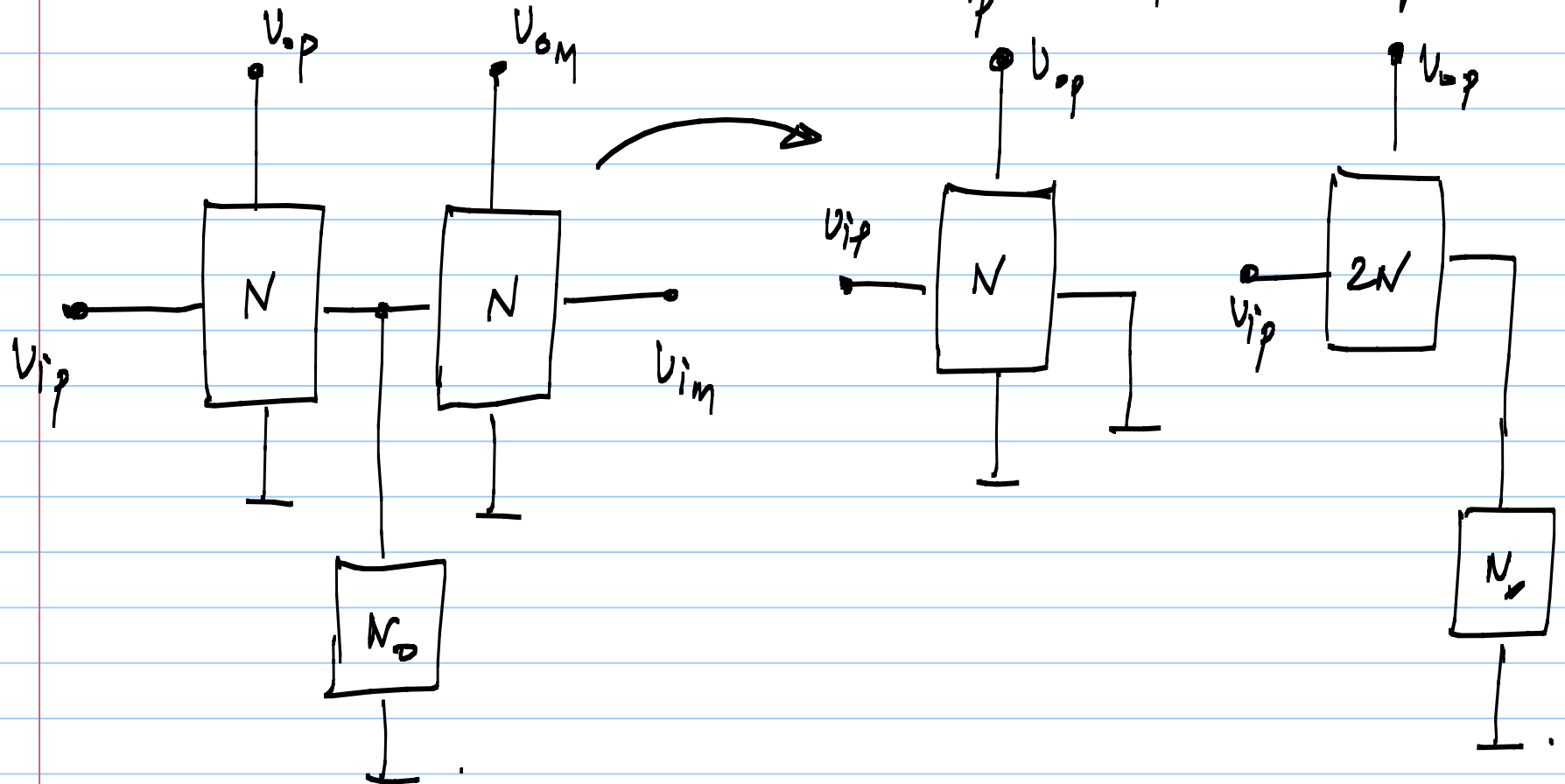

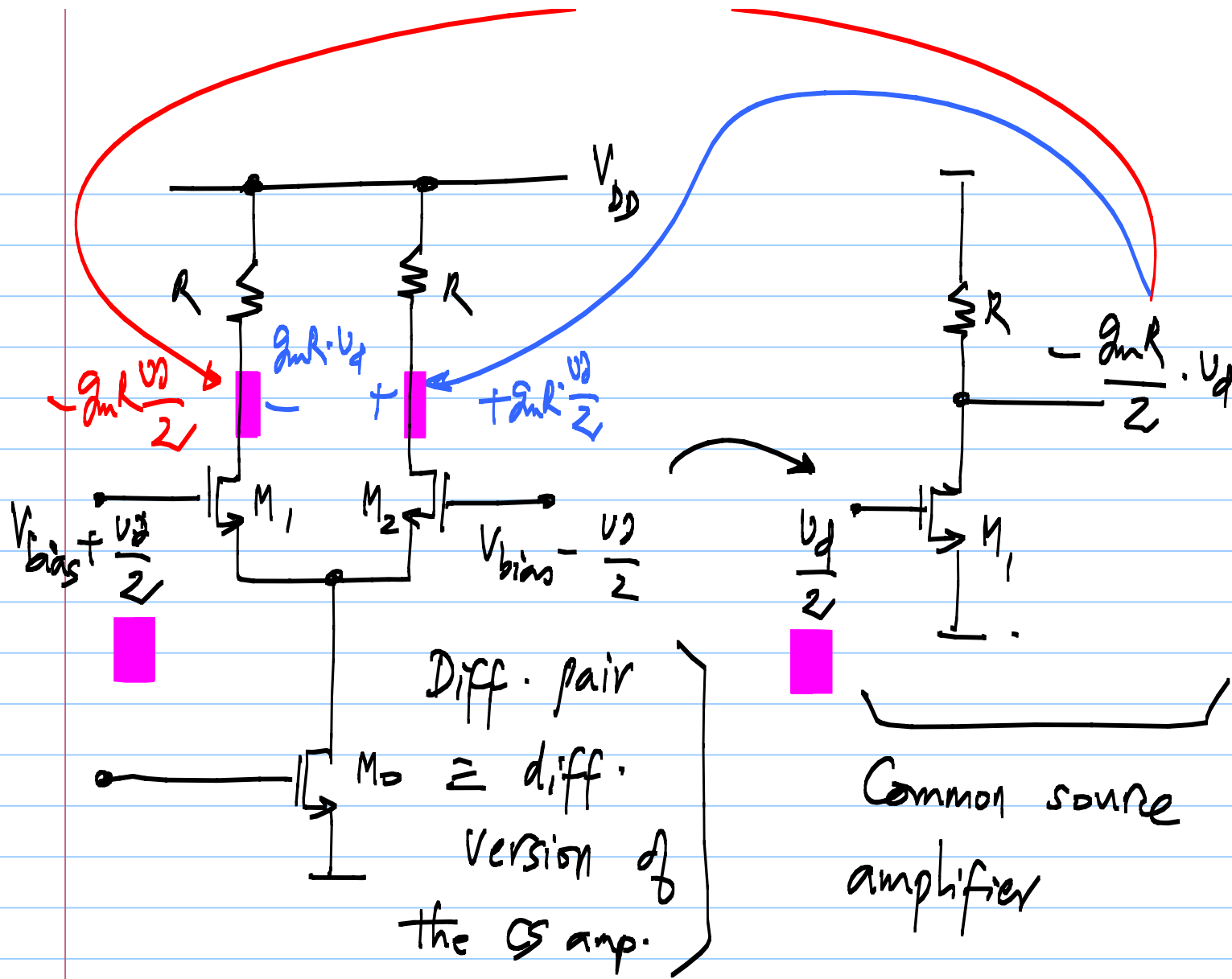


Fully differential circuits: noise

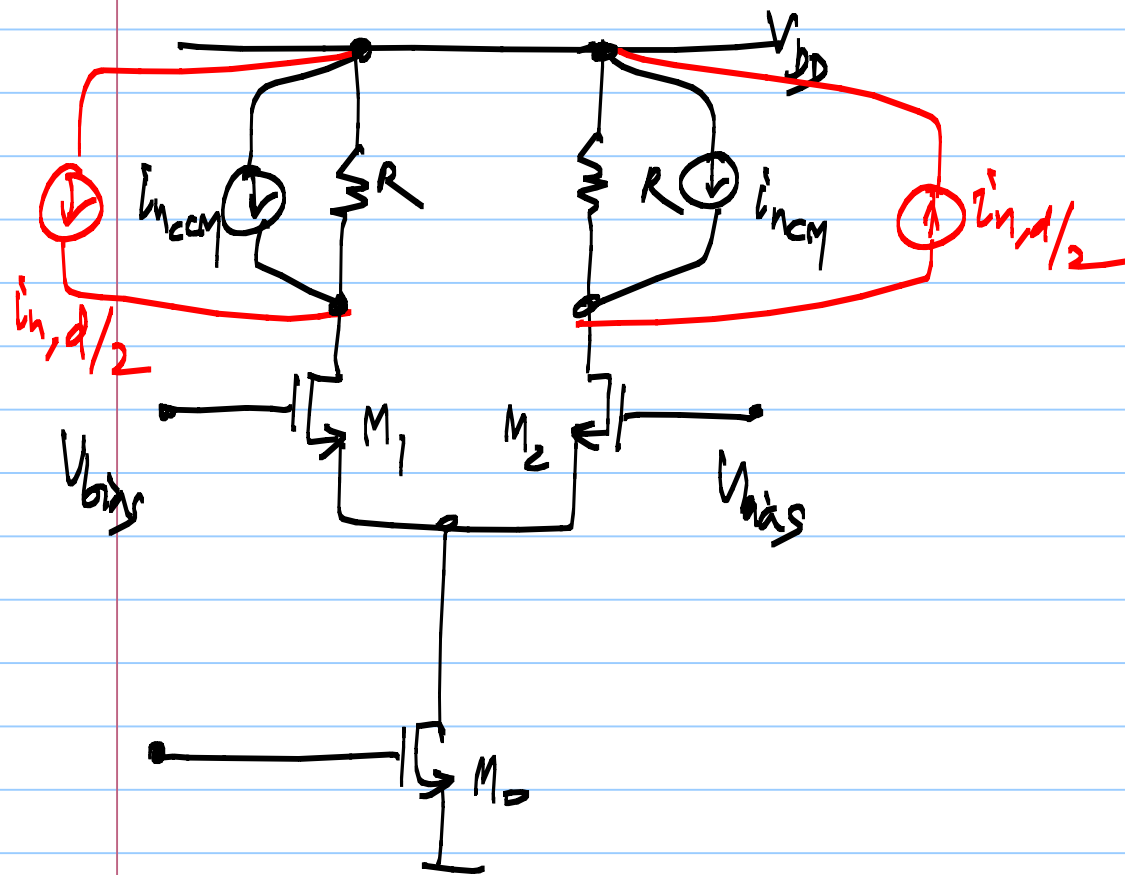

$$i_{n1} = \frac{i_{n1} + i_{n2}}{2} + \frac{i_{n1} - i_{n2}}{2}$$


$$i_{n2} = \frac{i_{n1} + i_{n2}}{2} - \frac{i_{n1} - i_{n2}}{2}$$
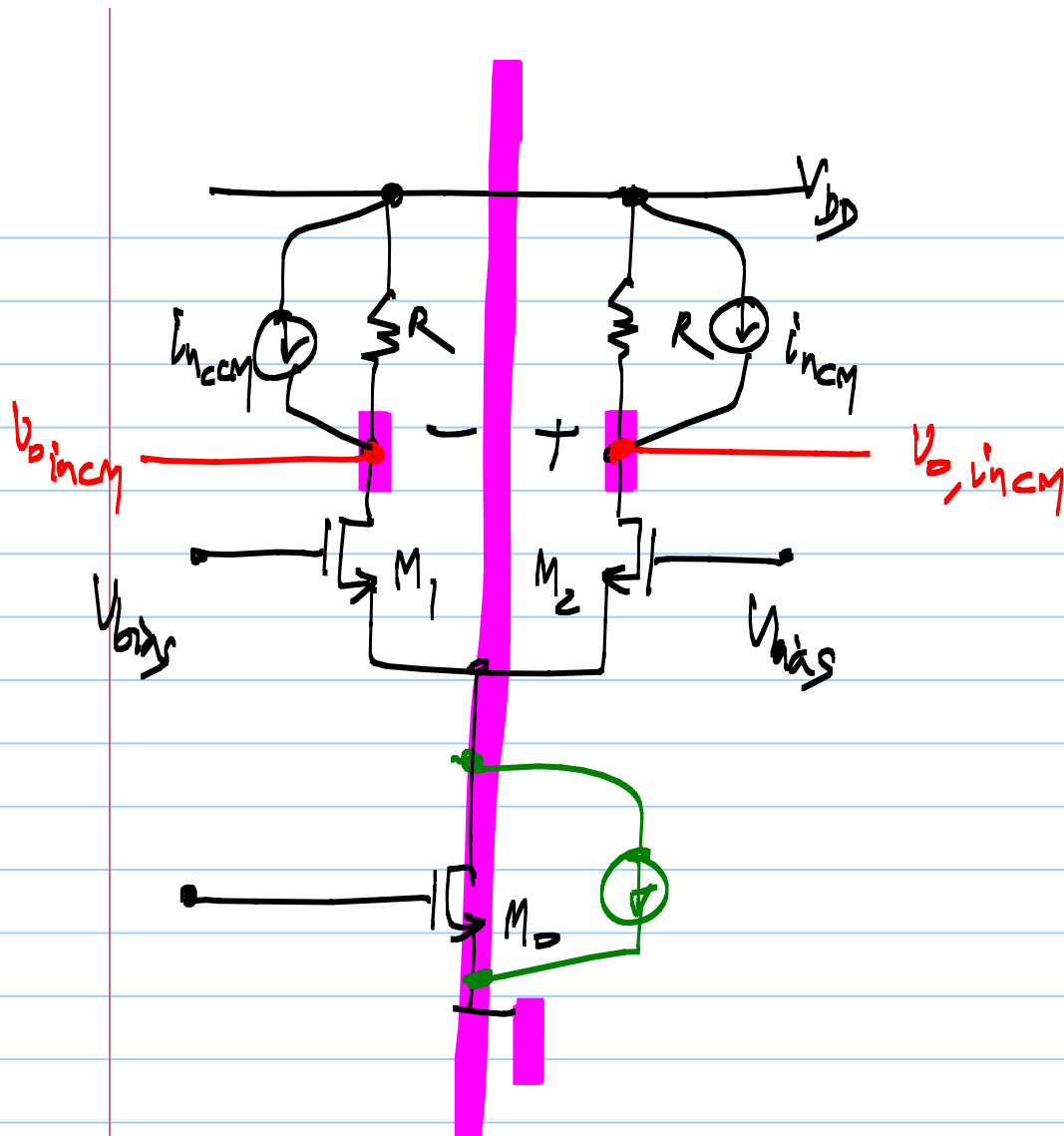
$$i_{n1,2} = i_{n,cm} + \frac{i_{n,d}}{2}$$




Effect of $i_{n,cm}$ on
the diff. o/p = 0

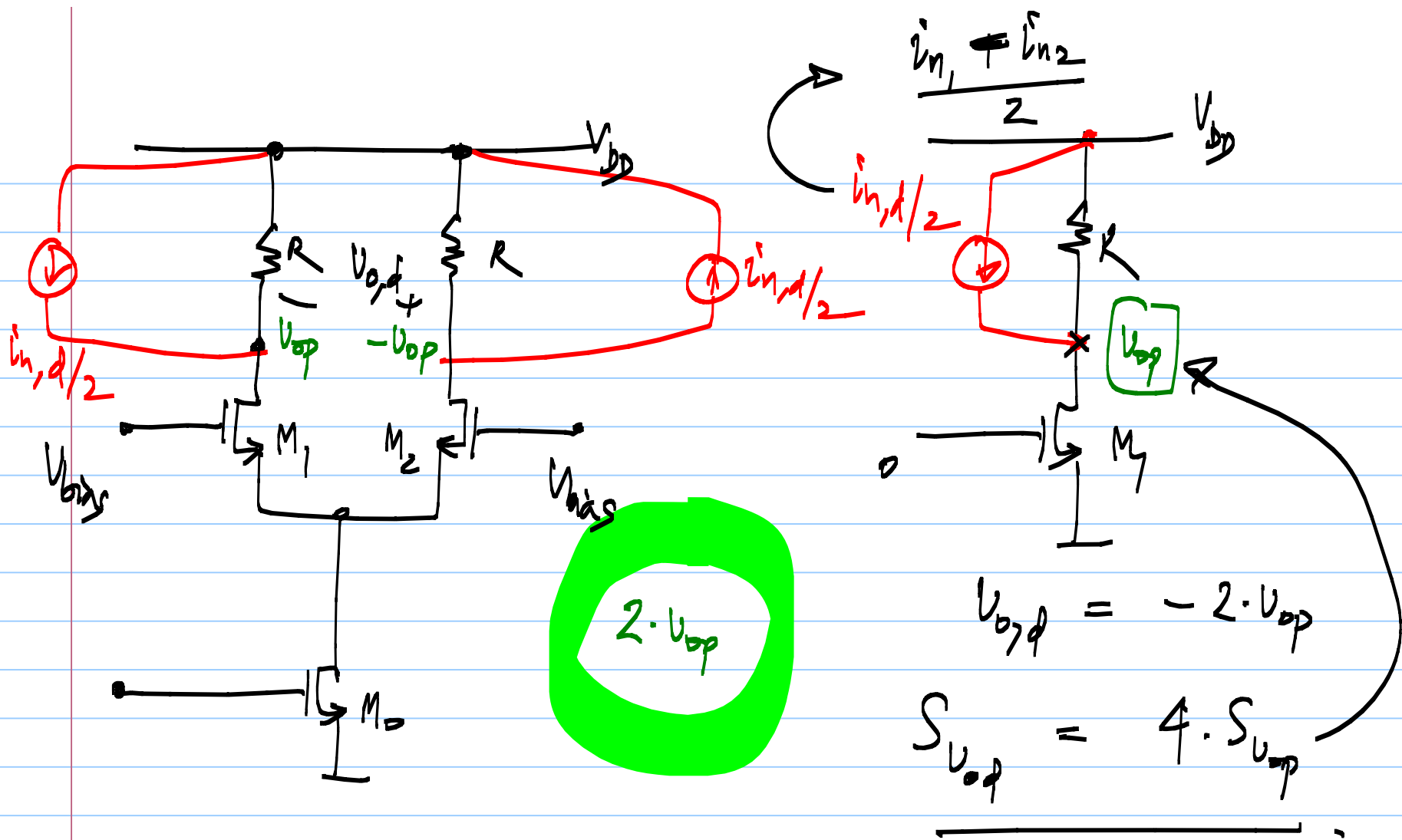Effect of noise from
common components = 0


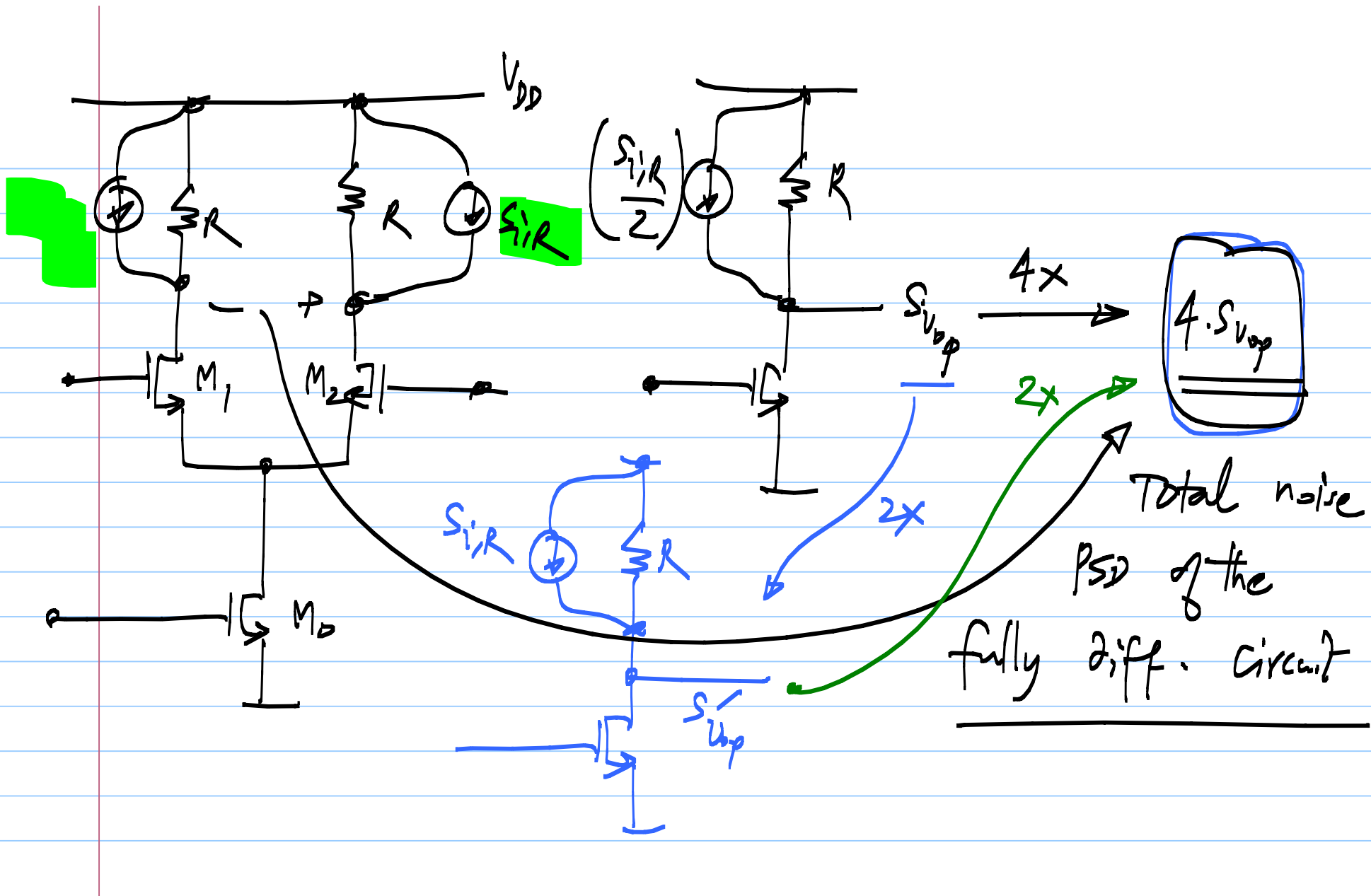
$$\begin{aligned} \left(\frac{i_{in}}{2} \right) &= \frac{i_{n1} - i_{n2}}{2} = S_{i,R} \\ &= \frac{S_{i,R} + S_{i,R}}{4} = \underline{\underline{\left(\frac{S_{i,R}}{2} \right)}} \end{aligned}$$



Fully differential circuit: noise analysis

* Analyze the noise of the half circuit

* Multiply the o/p noise PSD by 2x
to obtain the noise in the fully diff.
output
