

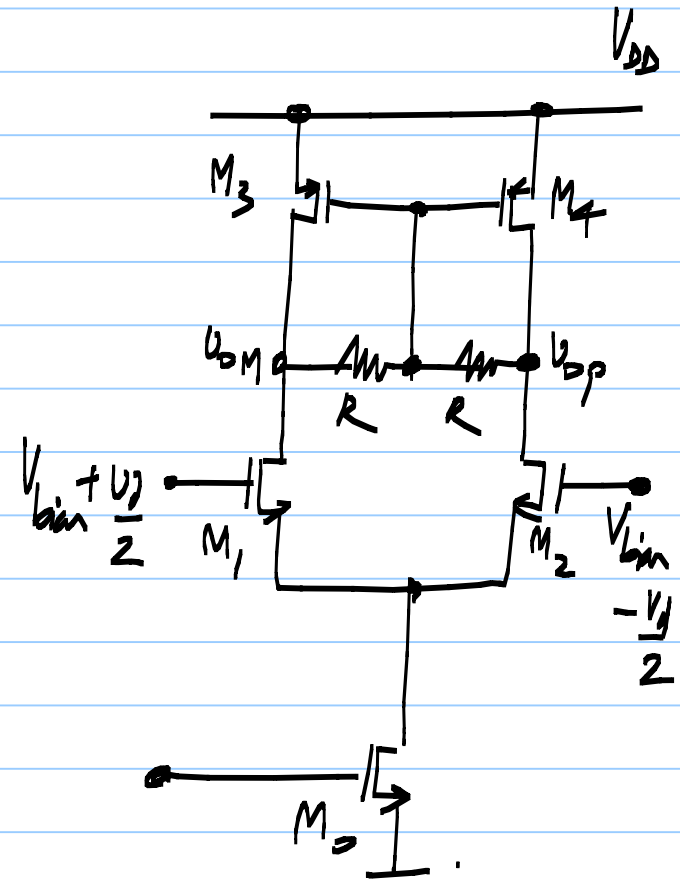

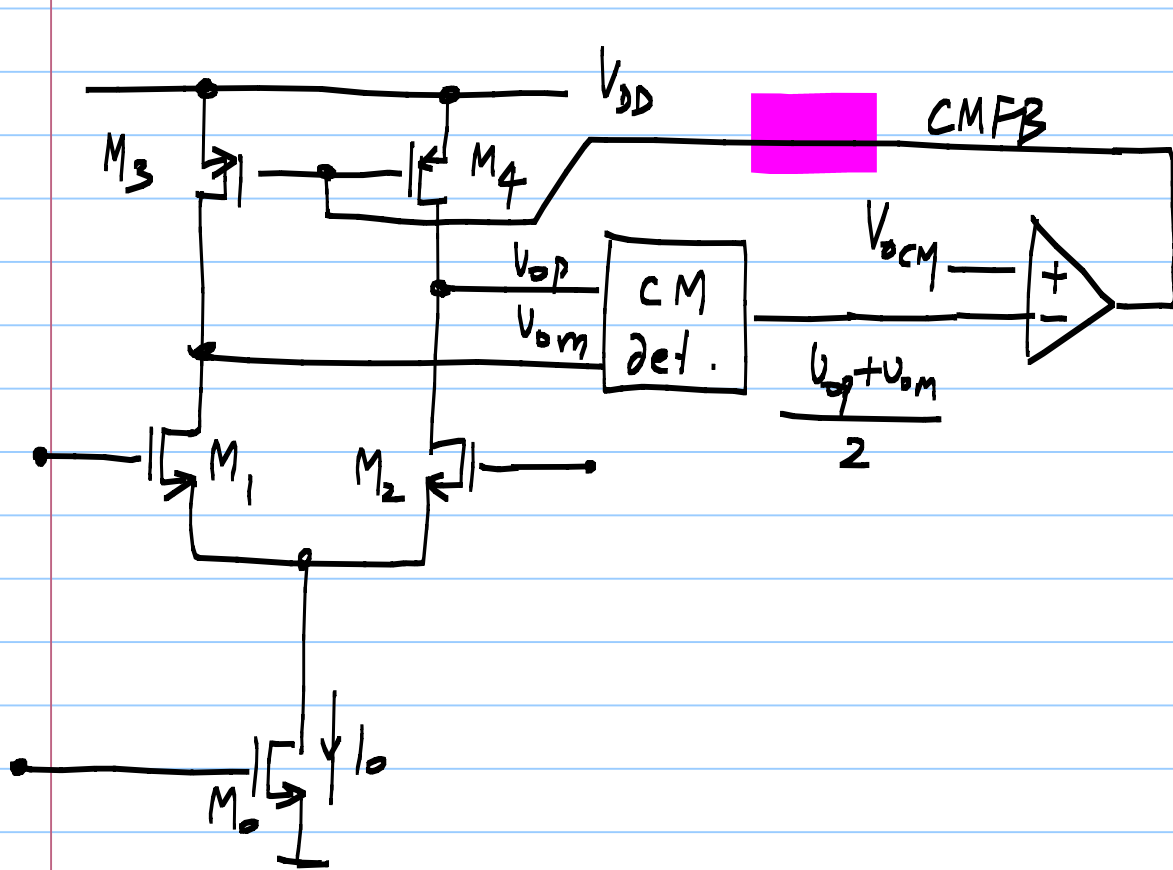
# Lecture 41: Common mode feedback circuits




# Resistive common mode detector:


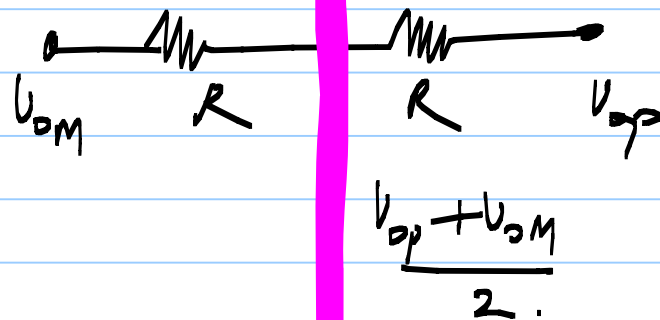


\* linear

\* Range unlimited

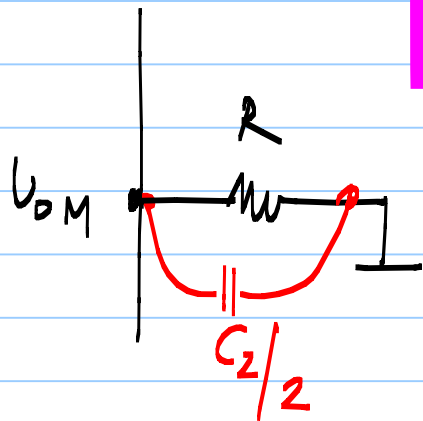

Diff. half ckt — Loads the diff circuit

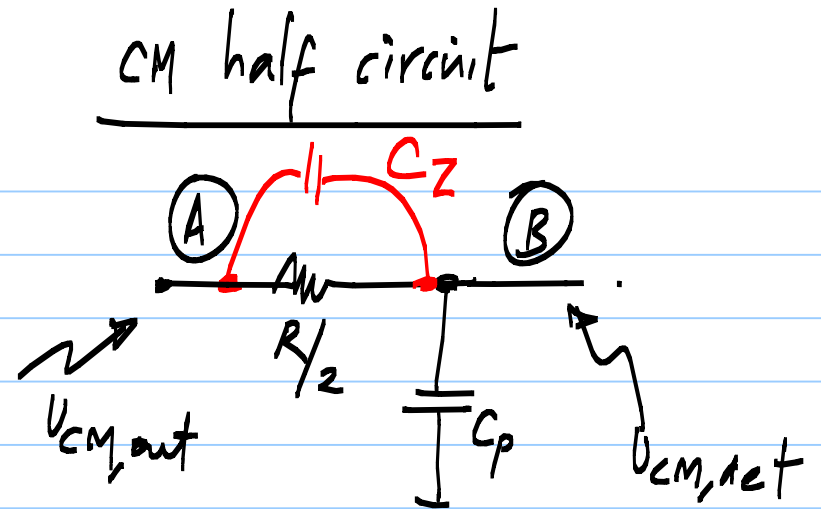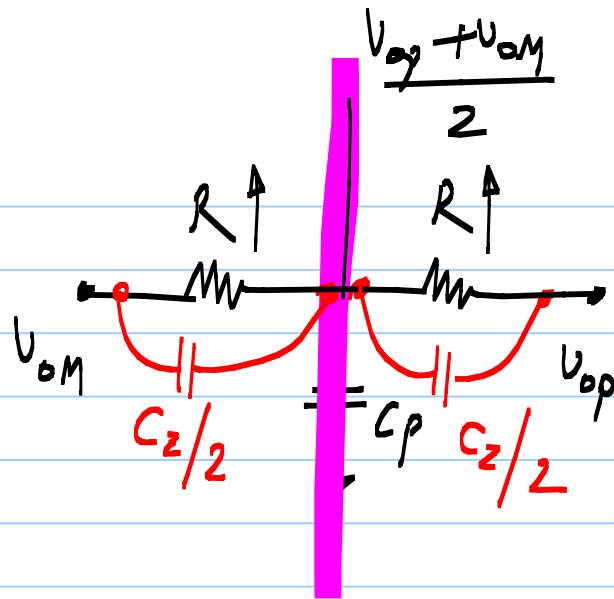


Introduce a zero

$$\frac{1}{1 + sC_p R/2} \cdot \frac{C_z}{C_z + C_p} \cdot \frac{1 + sC_z R/2}{1 + s(C_z + C_p) R/2}$$


@ h.f


# Buffered resistive CM det.

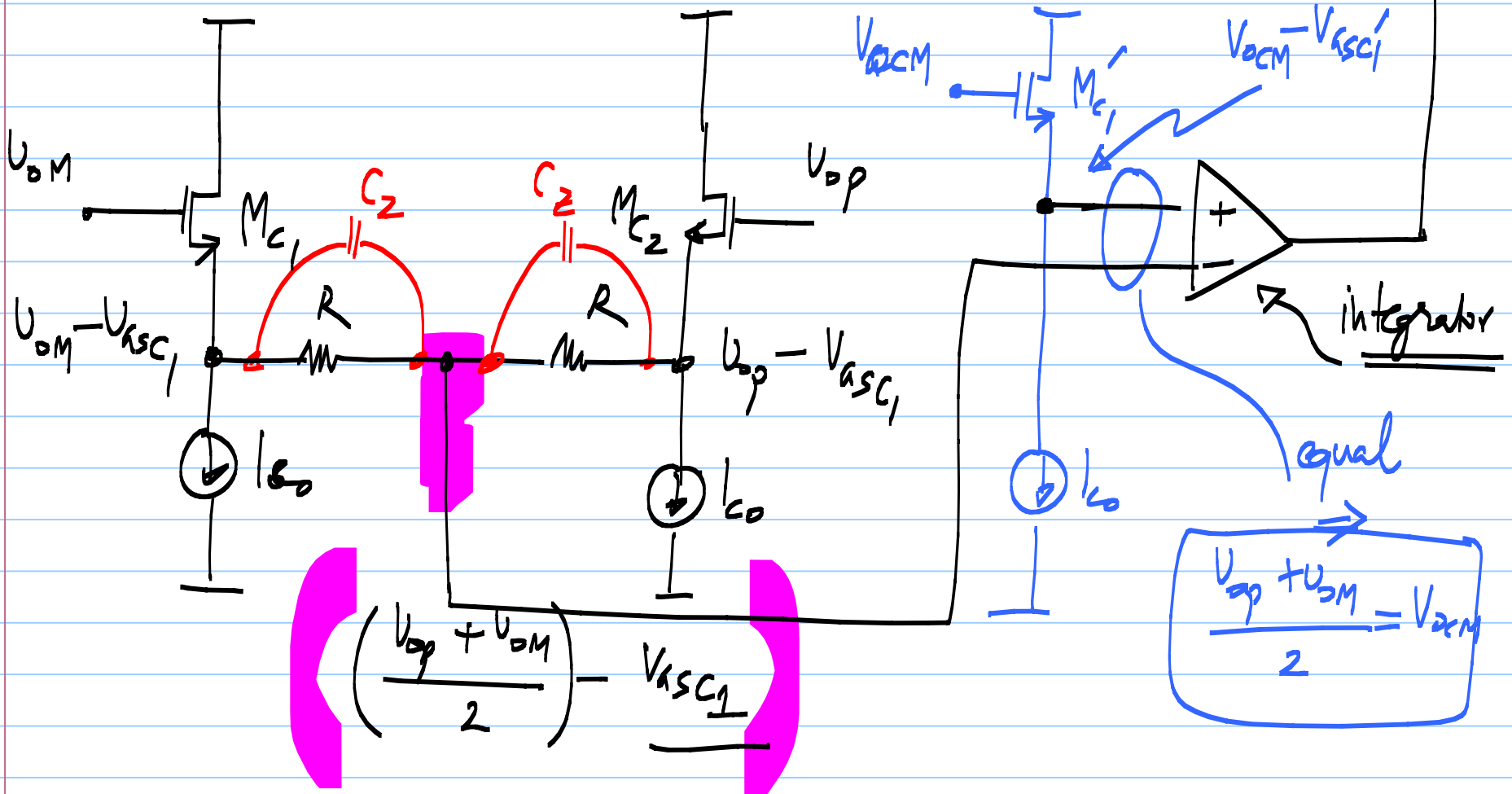

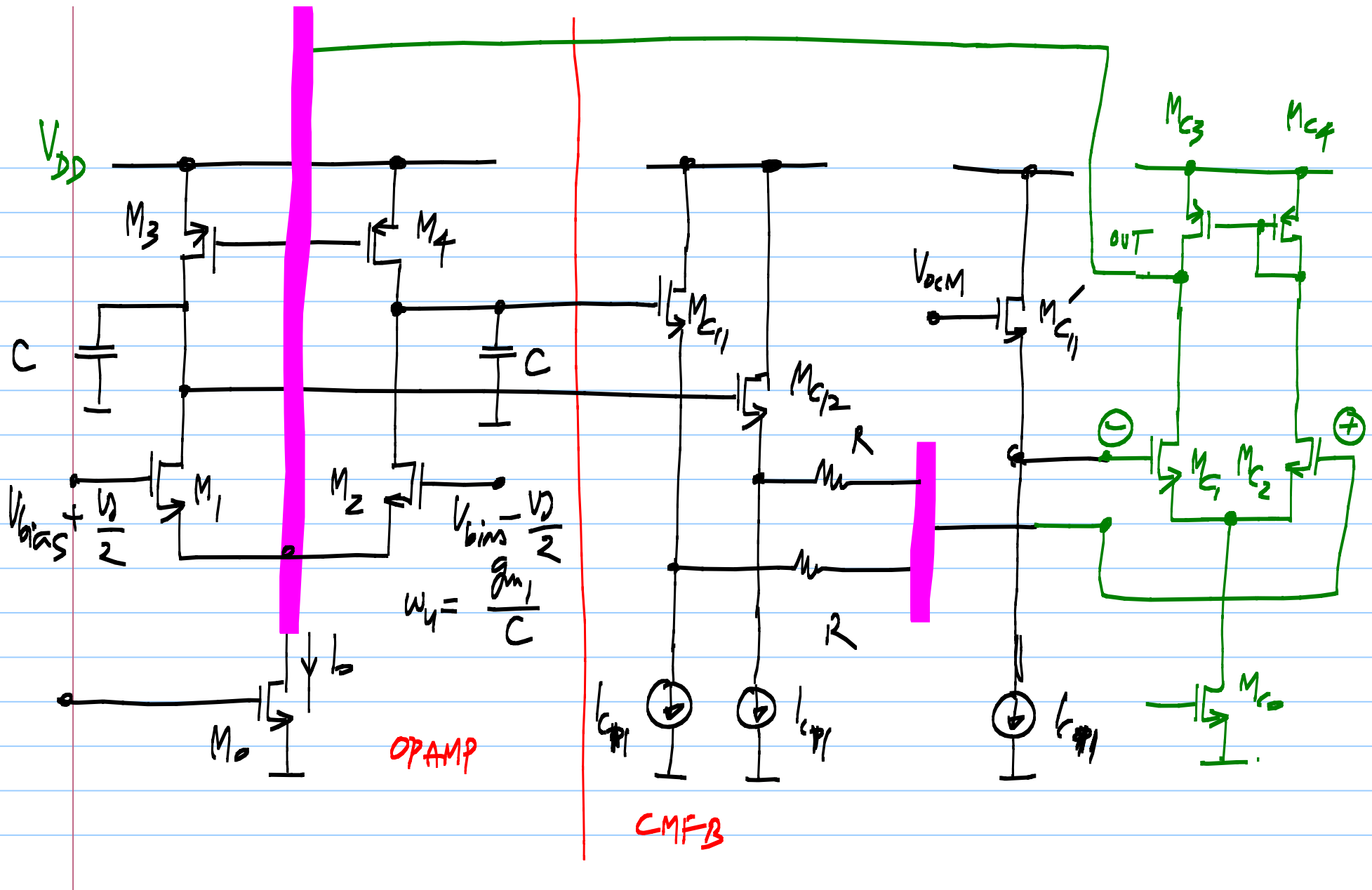
## Buffered resistive CM def.

- \* No loading
  - \* Swing limits
  - \* Nonlinearity ; body effect
-



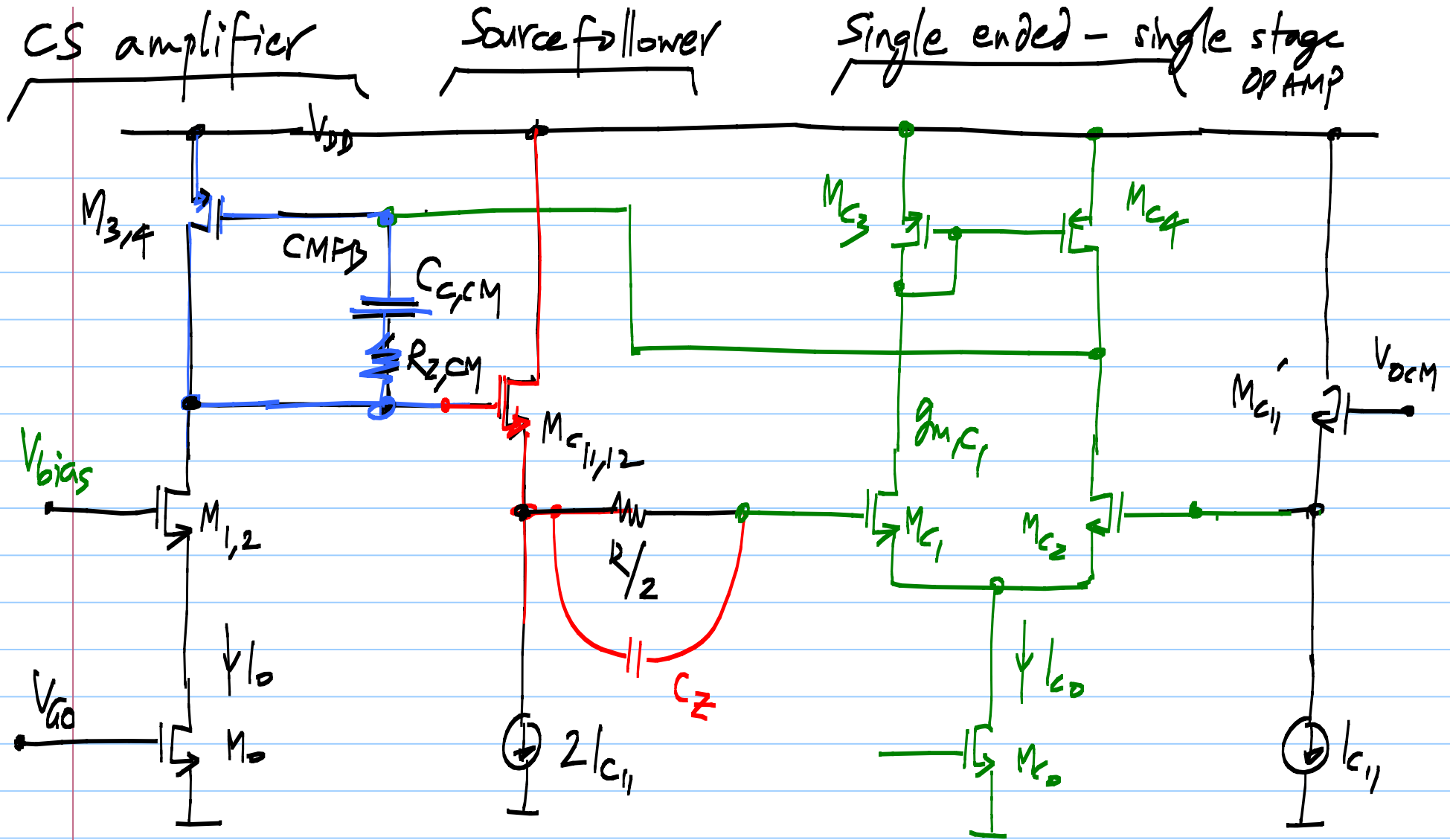

# Two stage opamp

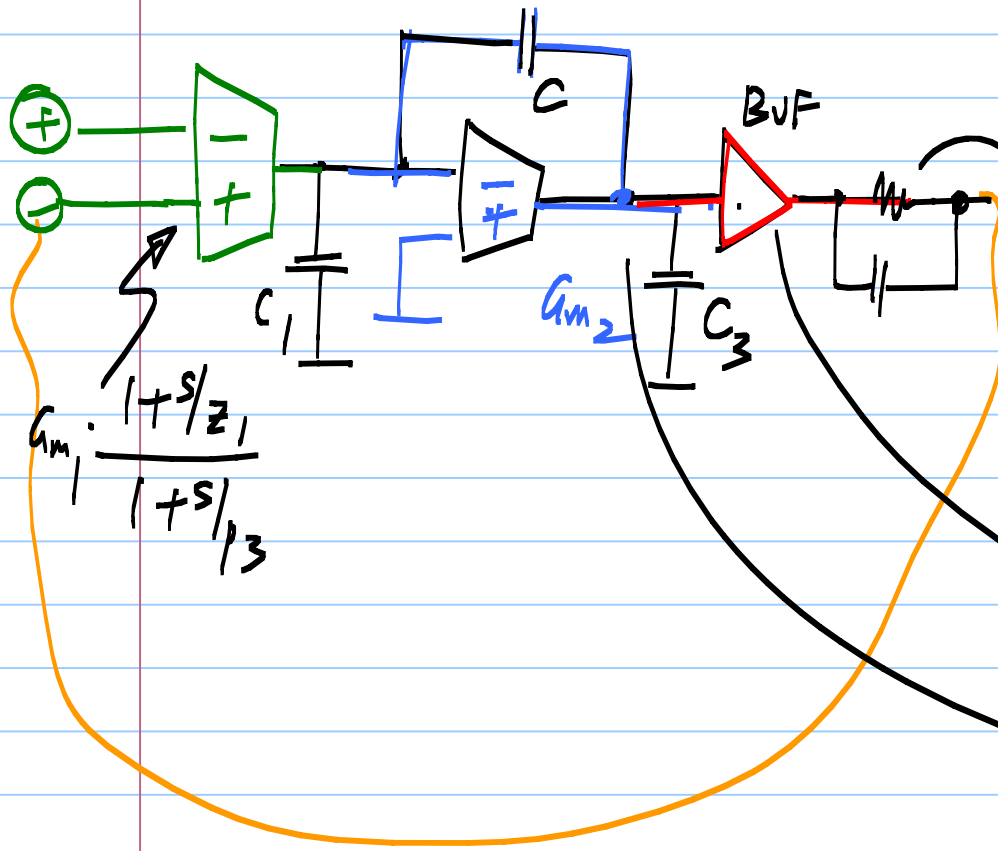

$$g_{m1} \cdot \frac{1+s/z_1}{1+s/p_3}$$

$$\omega_{u,loop,rcm} = \frac{g_{m1} C_1}{C_{c,cm}}$$

Mirror pole & zero:  $-\frac{g_{m3}}{C_1, C_3}$ ;  
 $-\frac{2g_{m3}}{C_{PF3}}$

poles & zeros





- Common mode feedback circuit is required to stabilize the o/p CM voltage of fully differential circuits

{ Common mode detector  
Transconductor / opAMP


≡ Two stage single ended opAMP

- CMFB loop { CM eq. circuit of the complete opAMP } must be stable [ single stage opamp + Buffered CM det. + single stage single-ended  $G_m$  - CMFB ]

CM eq. half ckt-

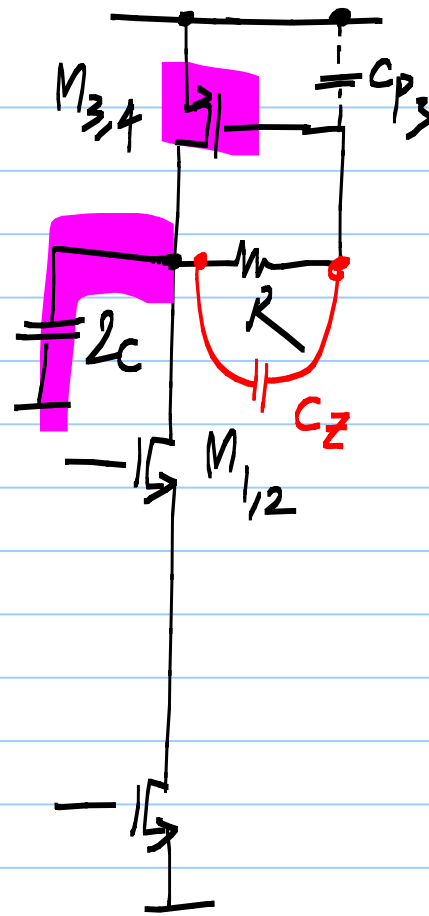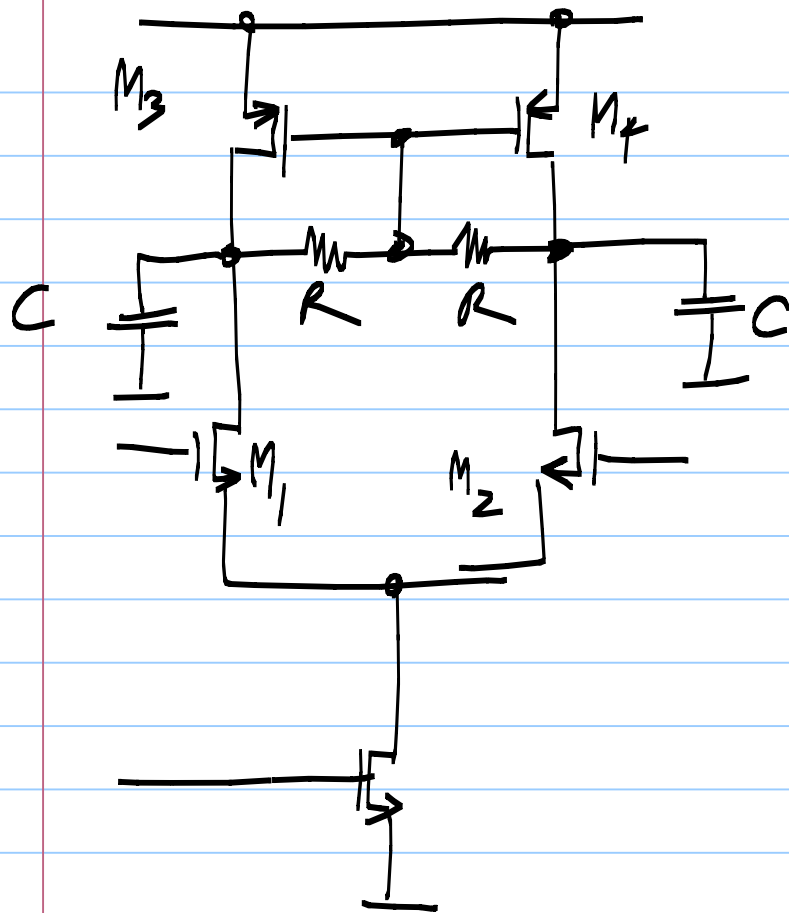
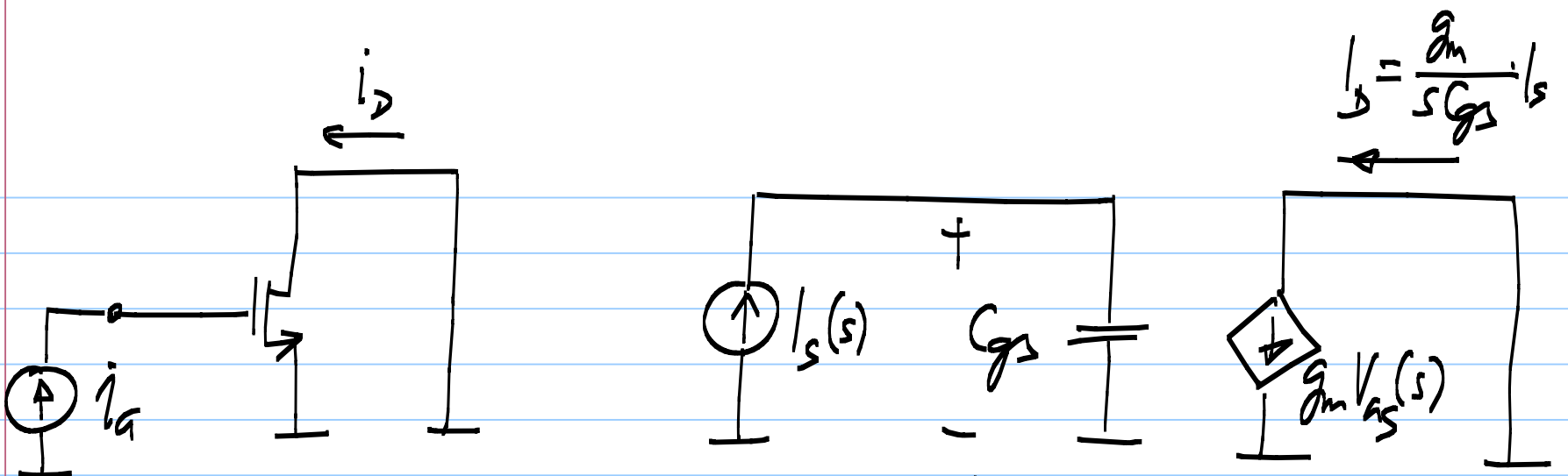
$$\frac{2g_{m3}}{2C} = \omega_{n,loop\ CM}$$




$$i_b = \frac{g_m}{s C_{gs}} i_s$$

MOS in Saturation

$$V_{gs} = \frac{i_s}{s C_{gs}}$$

$$\frac{i_b}{i_a} = \frac{g_m}{s C_{gs}} \Big|_{s=j\omega} \xrightarrow{\text{mag.}} \frac{g_m}{\omega C_{gs}}$$

Unity gain frequency  $\omega$

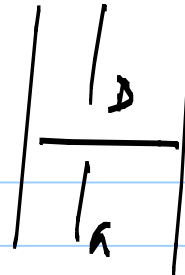

Velocity saturation  
 $\mu \frac{(V_{AS} - V_T)}{L} \rightarrow v_{SAT}$

Transit frequency

$$\omega_T = \frac{g_m}{C_{gs}}$$

$$f_T = \frac{g_m}{2\pi C_{gs}}$$

$$\omega_T = \frac{g_m}{C_{gs}} = \frac{\mu C_{ox} \frac{W}{L} \cdot (V_{AS} - V_T)}{\frac{2}{3} C_{ox} \cdot WL} = \frac{3}{2} \frac{\mu (V_{AS} - V_T)}{L^2}$$

$(V_{AS} - V_T)$

$\frac{3}{2} \cdot \frac{v_{SAT}}{L}$

$$* \quad w_T = \frac{3}{2} \frac{\mu (V_{GS} - V_T)}{L^2} \quad \text{OR} \quad \frac{3}{2} \frac{v_{SAT}}{L} \quad \text{has to be high}$$

Short channel  $L$ .

HIGH SPEED

High  $(V_{GS} - V_T)$ ; Small parasitic capacitances

$$* \quad r_o^2 = \frac{2\mu C_{ox}}{I_D} \cdot \frac{A_V^2}{L^2} + \frac{A_D^2}{wL}$$

HIGH PRECISION

Long channel  $L$ , large  $w \Rightarrow$  large parasitic cap.

$$* \quad \text{Low power} \quad I_D = \left( \frac{V_{GS} - V_T}{2} \right) g_m \quad \text{OR} \quad \eta V_T \cdot g_m$$

Low  $(V_{GS} - V_T)$