
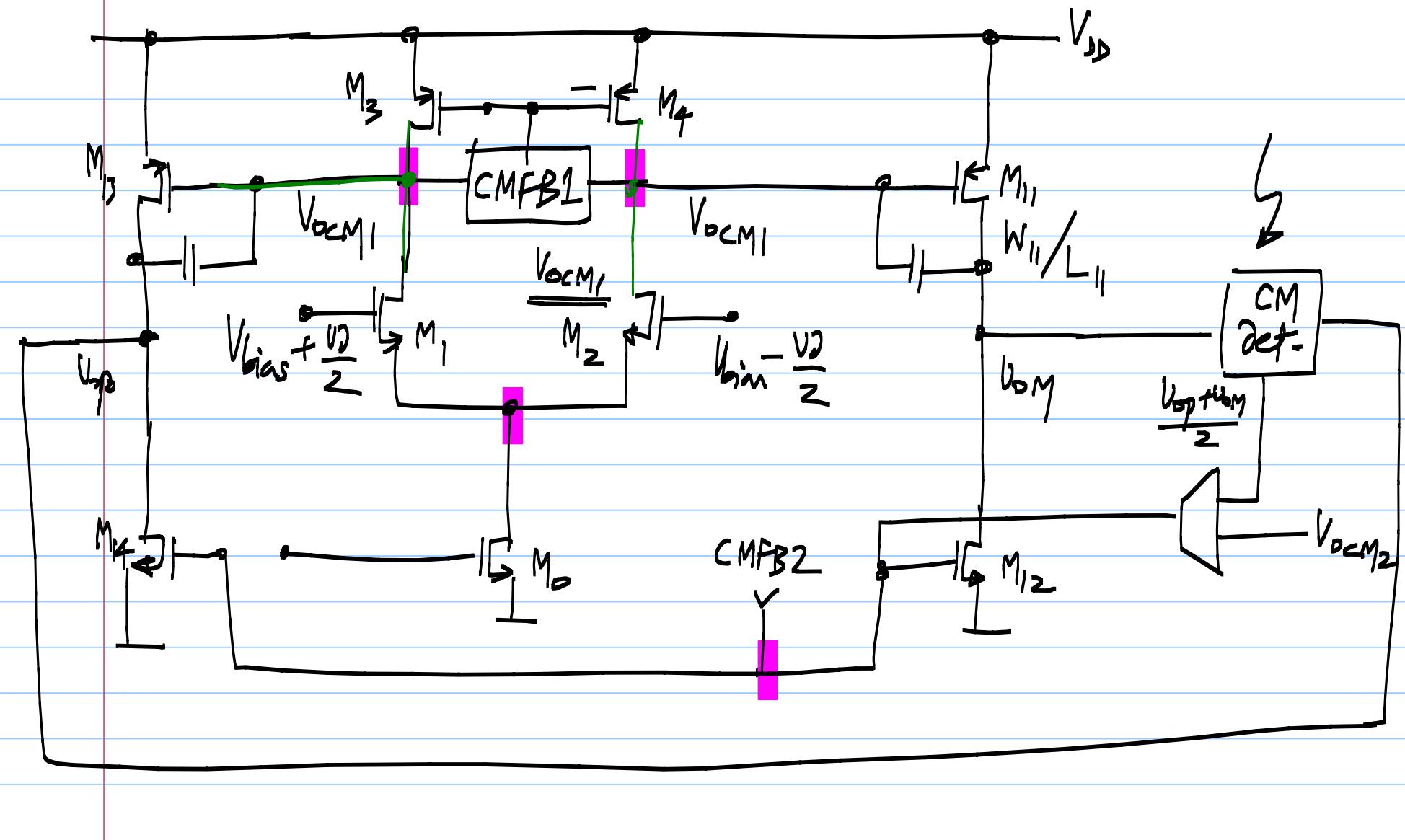



Lecture 43 :


Two stage fully differential opamp

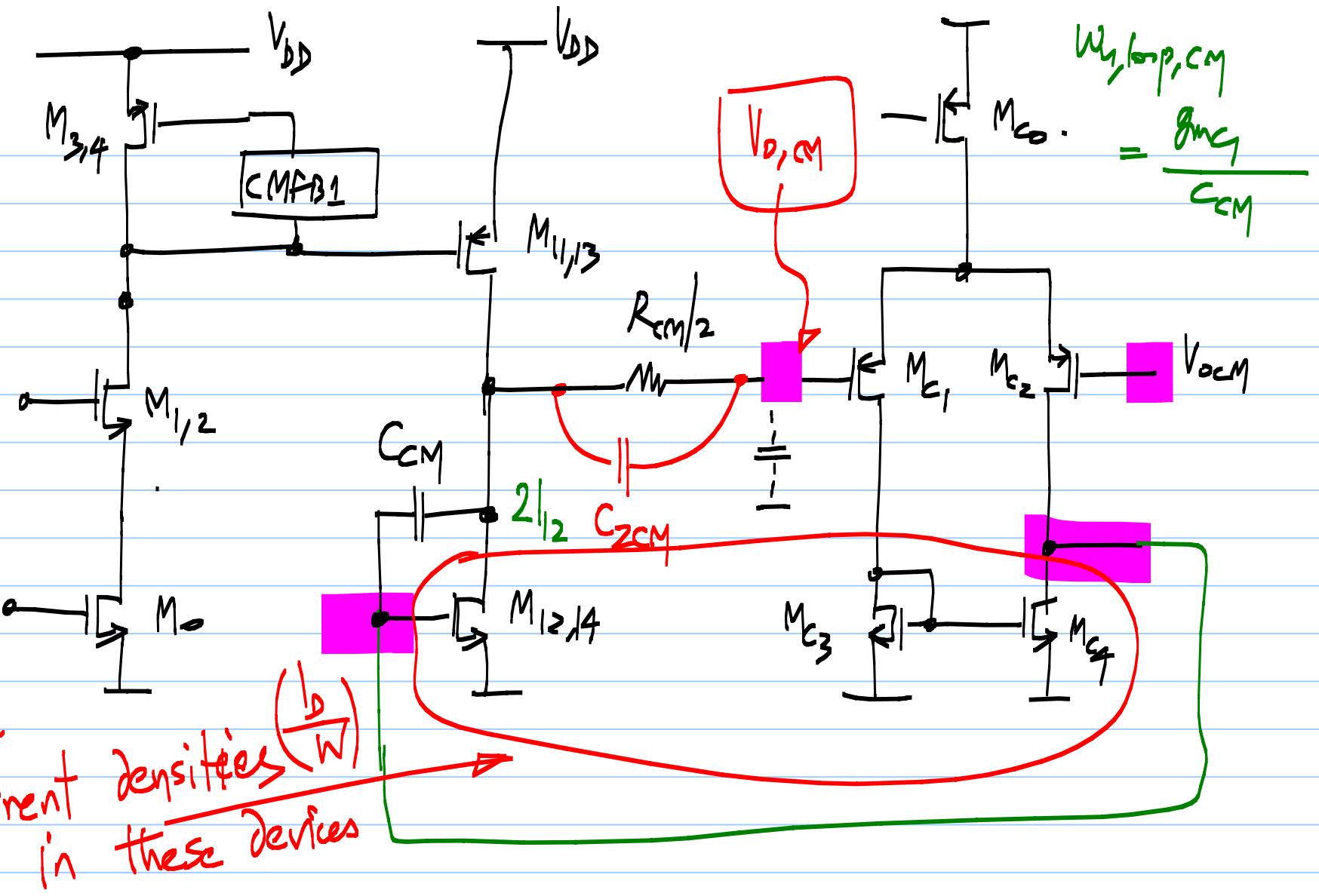
- DC gain, slew rate, noise, offset, signal swing limits
Similar to the single ended two stage opamp;
- $\omega_u = \frac{g_m}{C}$; $P_2 = \frac{g_{m3} \cdot \frac{C}{C+C_1}}{\frac{CC_1}{C+g} + C_L}$; Mirror pole/zero not present






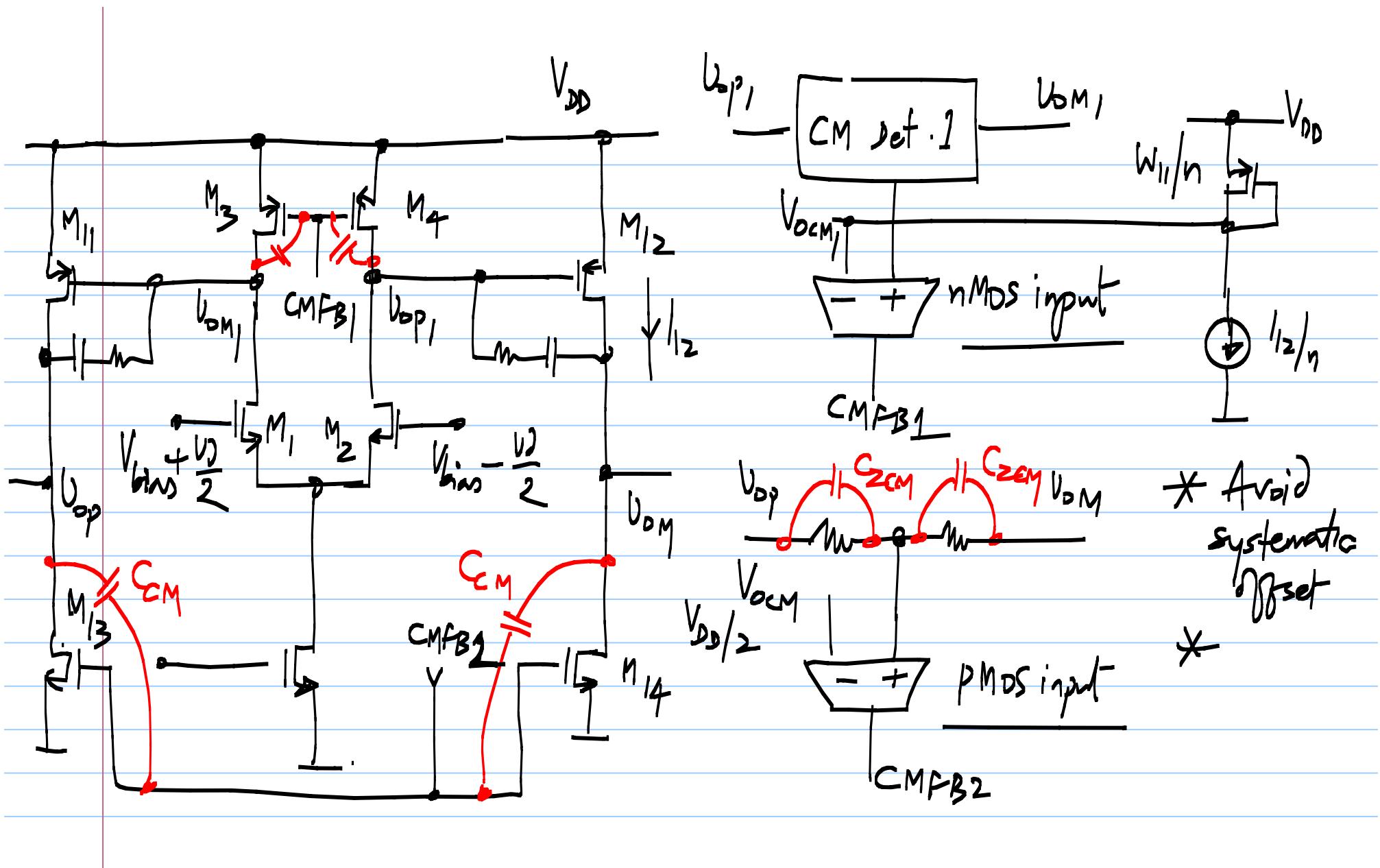


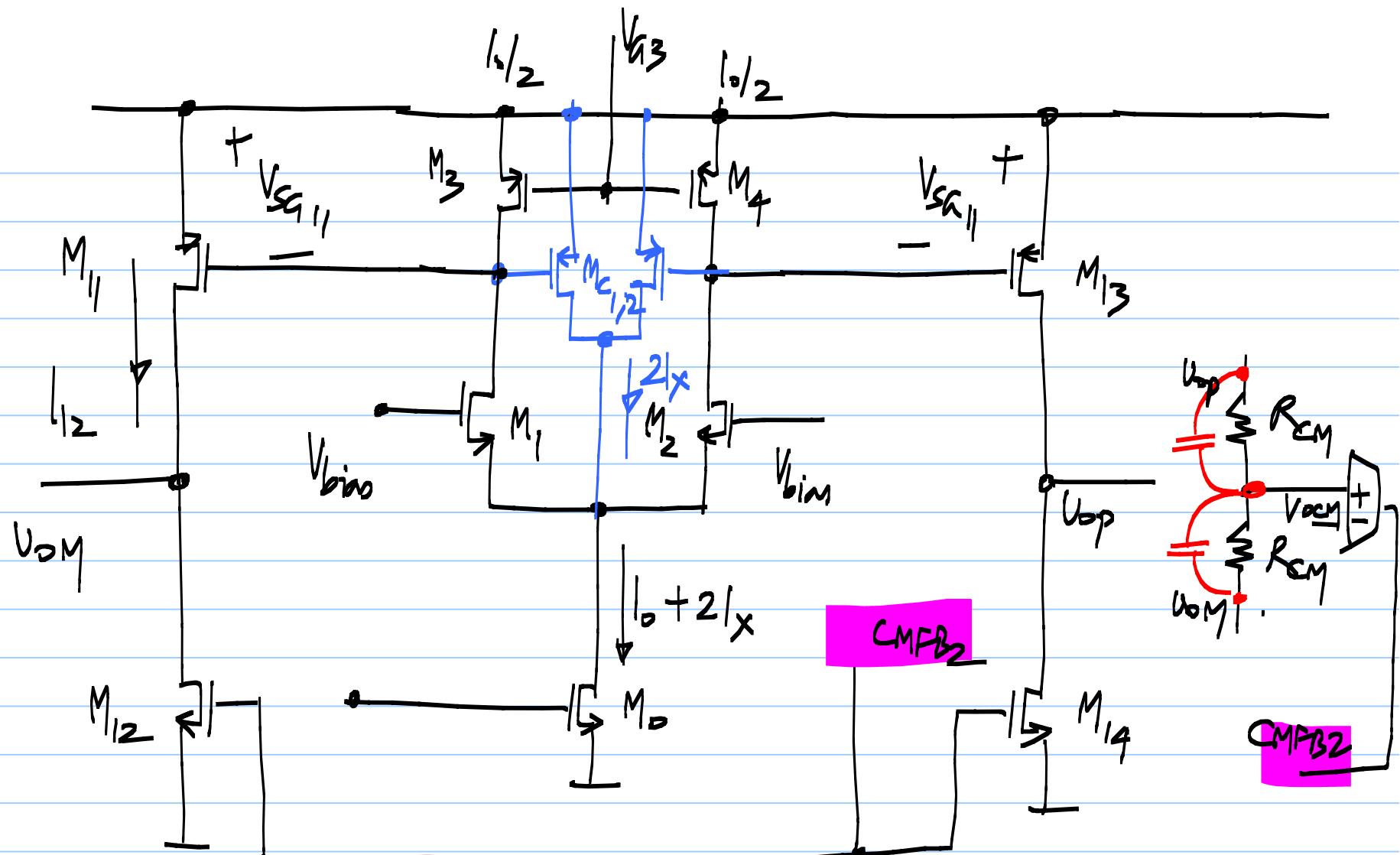

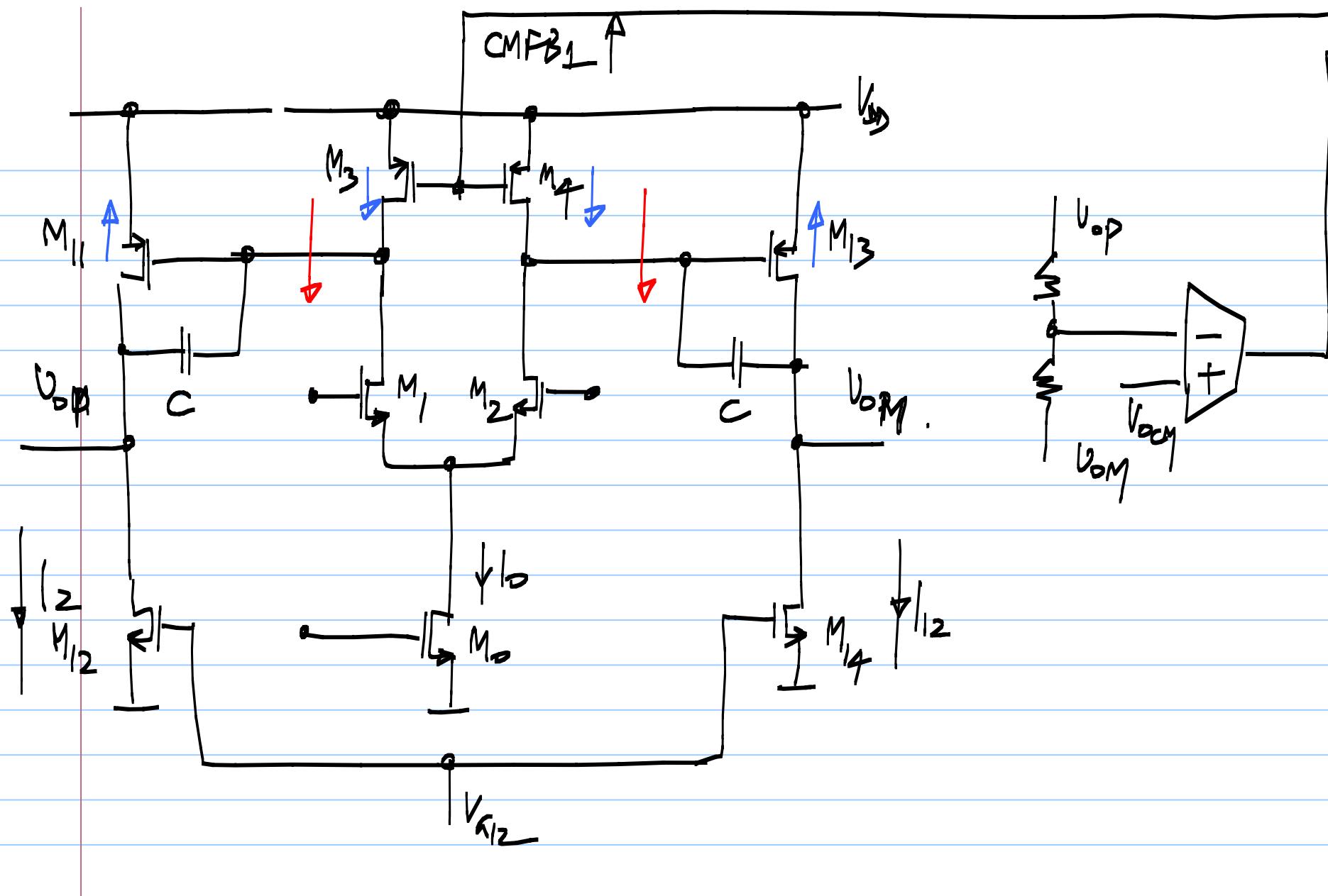

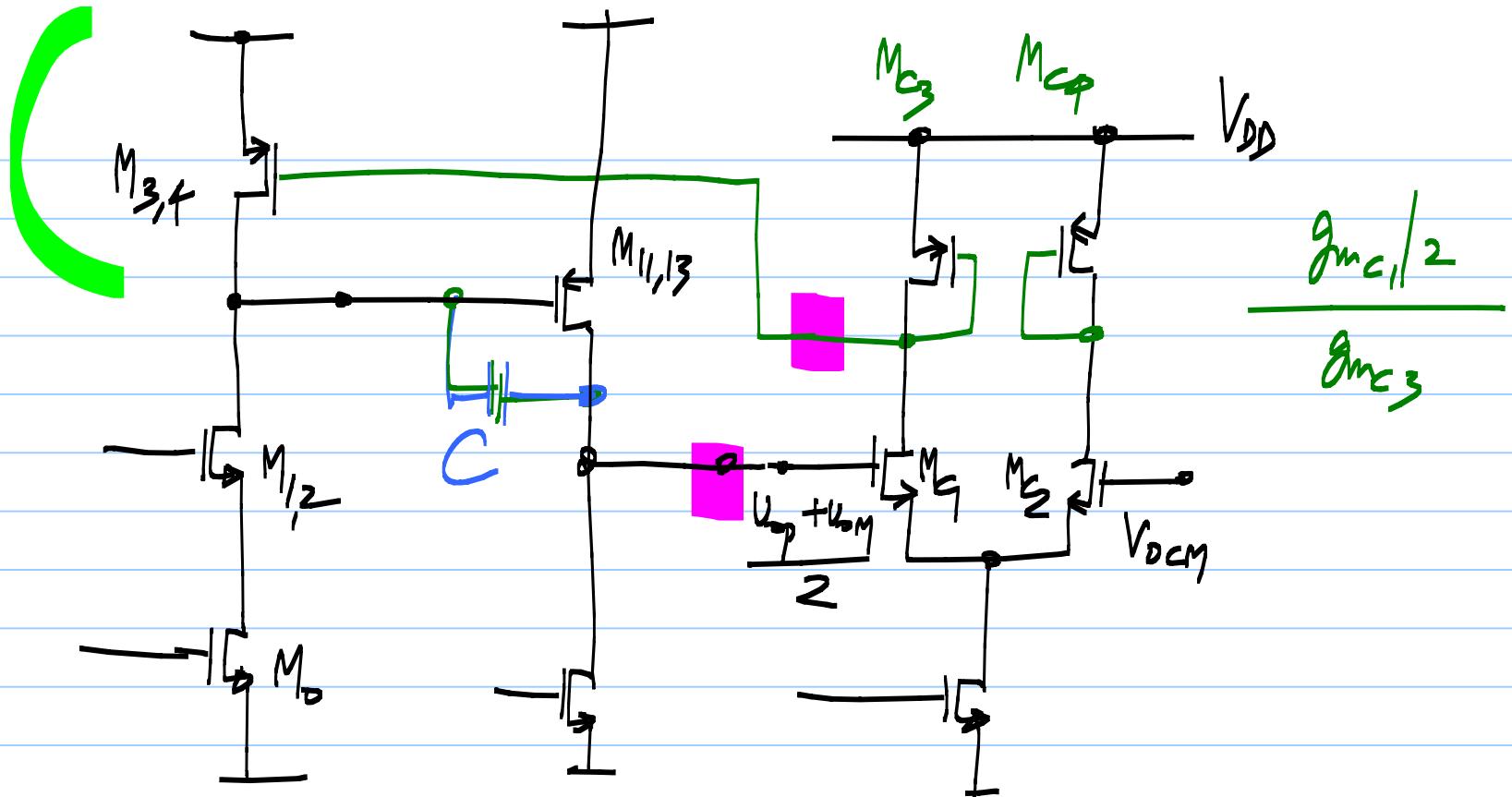


Single CMFB loop for a 2 stage opamp

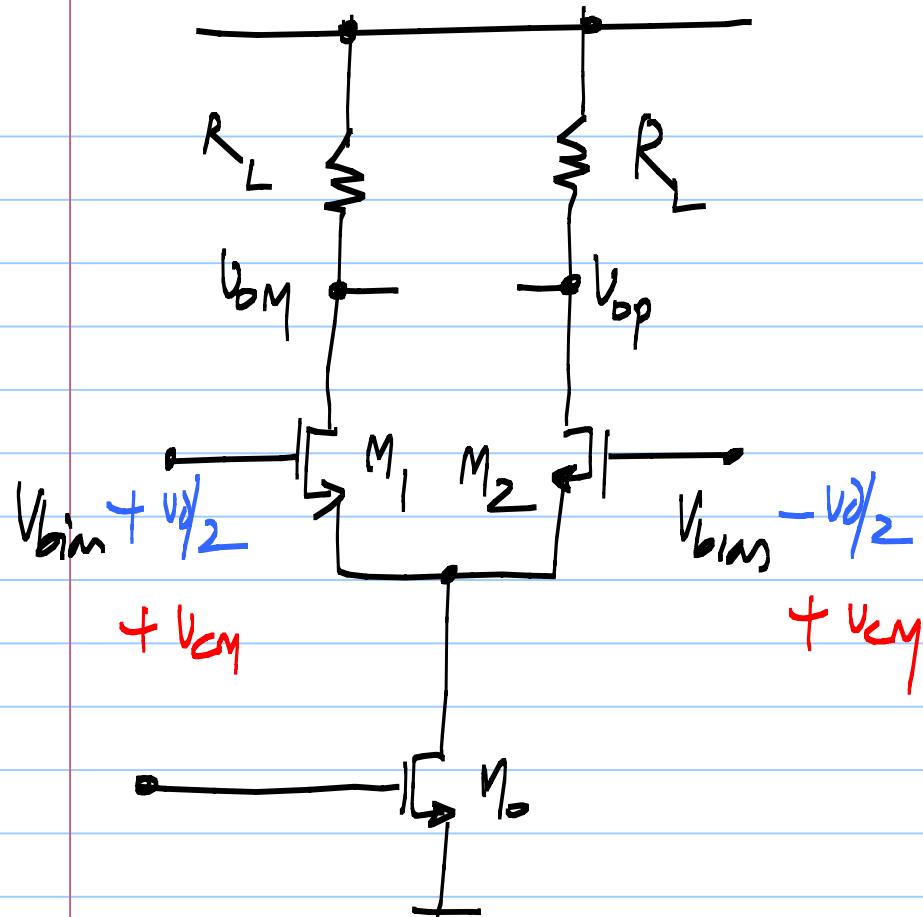

$$A_d = \frac{V_{op} - V_{oM}}{V_d} = g_m \cdot R_L$$

$$A_{CM} = \frac{(V_{op} + V_{oM})/2}{V_{cm}} = \frac{R}{2r_{ds0}}$$

$$A_{CM} \ll A_d \gg A_{CM} \ll 1$$

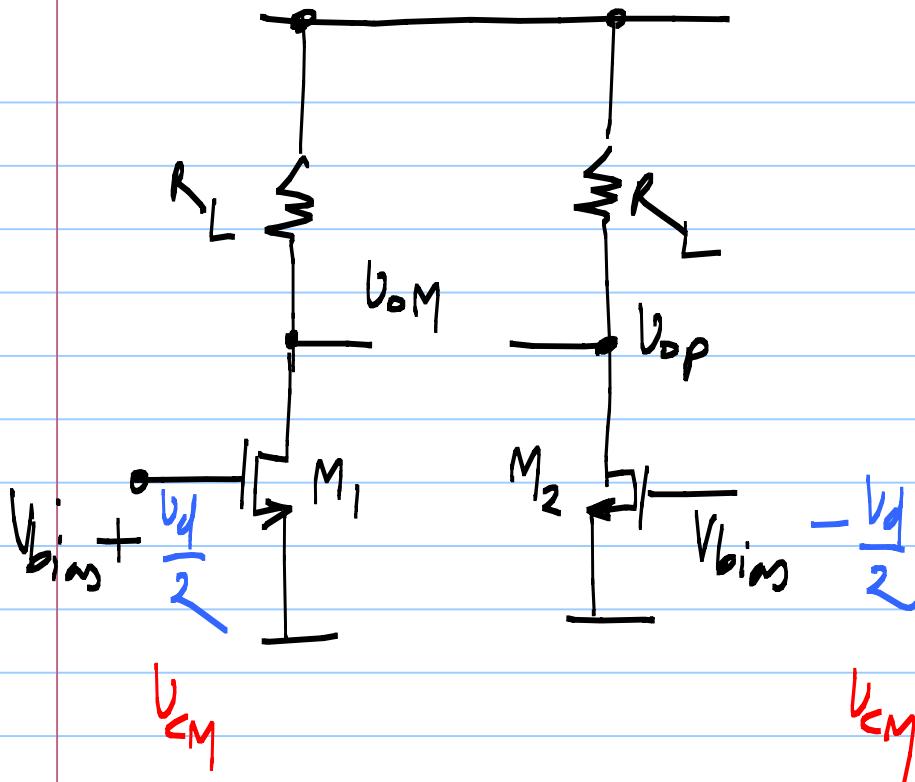

$$A_D = \frac{V_{op} - V_{oM}}{V_d} = g_m \cdot R_L$$

$$A_{CM} = \frac{(V_{op} + V_{oM})/2}{V_{CM}} = g_m \cdot R_L$$

$$A_{CM} = A_D$$

✗

With CMFB circuitry $A_{CM} \rightarrow 0$