
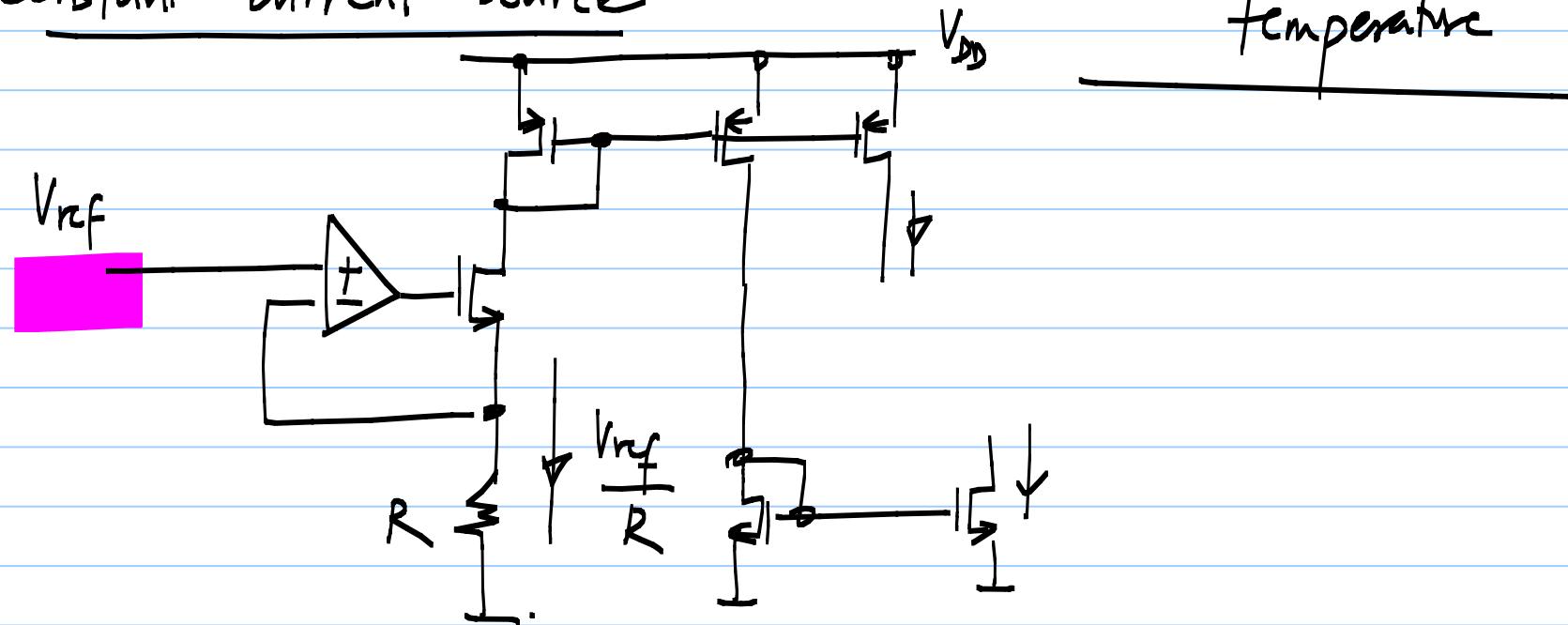


Lecture 53:

Constant current source

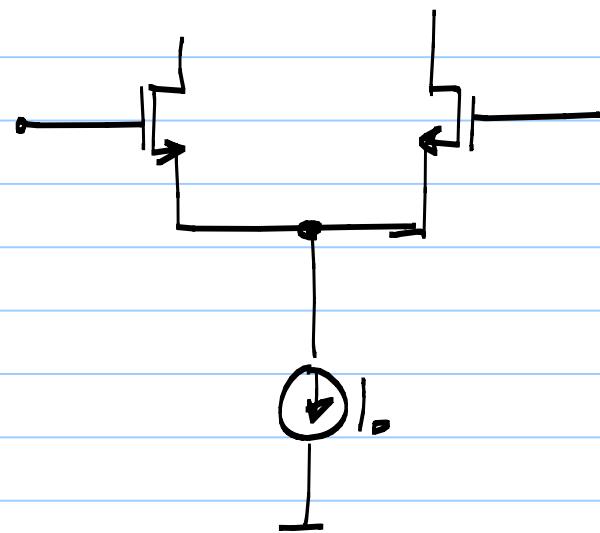Constant over
process, supply voltage &
temperature





b : constant over temp.

$$g_m = \sqrt{\frac{2 \cdot I_o / 2}{\mu C_{ox} W / L}}$$


reduces as $T \uparrow$

varies with temp

$$g_m = \frac{I_o/2}{V_t} = \frac{I_o/2}{kT/q}$$

To keep g_m constant,

$$I_o \propto T$$

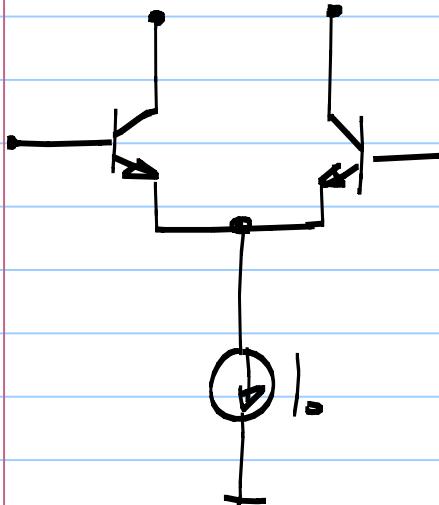



$$V_t = \frac{kT}{q} \propto T$$

$$V_{BE1} = V_t \ln\left(\frac{I_o}{I_s}\right) \propto T$$

depends on T
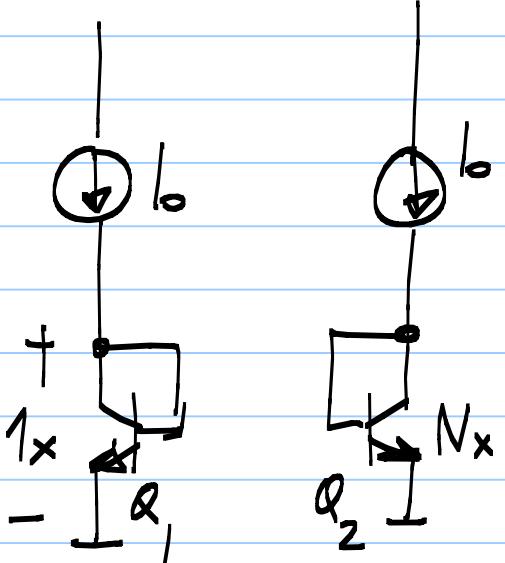
$$V_{BE2} = V_t \ln\left(\frac{I_o}{N \cdot I_s}\right)$$




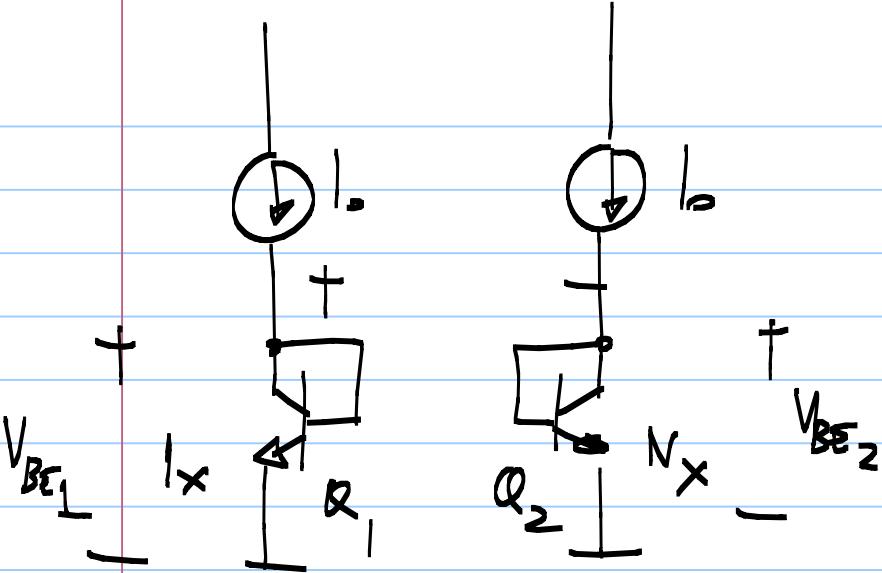


$V_{BE_1} - V_{BE_2}$ must appear across a resistor (must have zero T_C)


$$V_{BE_1} = V_t \ln \left(\frac{I_o}{I_s} \right) \quad V_{BE_1} - V_{BE_2} = V_t \cdot \ln(N)$$
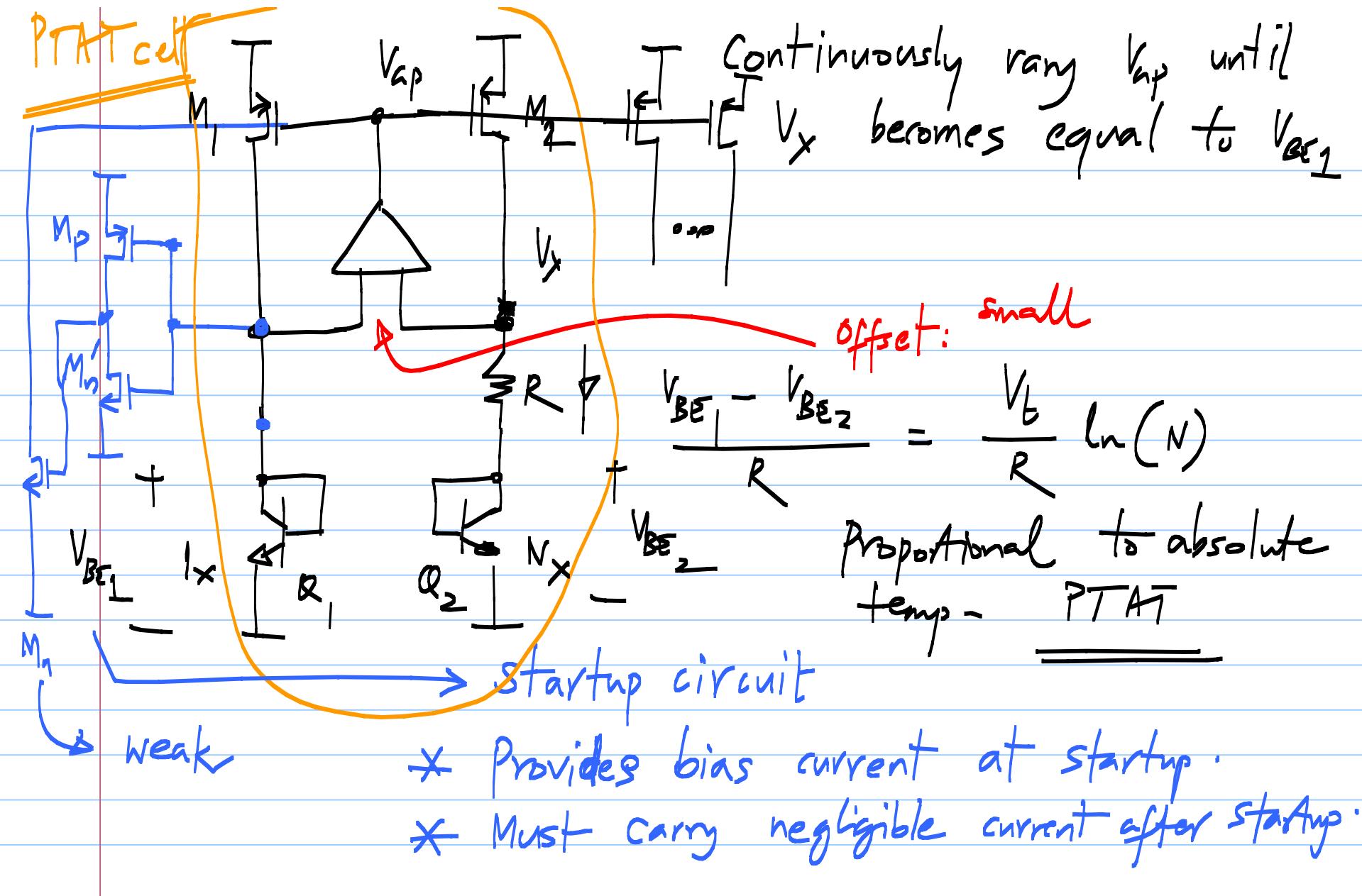
$$V_{BE_2} = V_t \ln \left(\frac{I_o}{NI_s} \right)$$



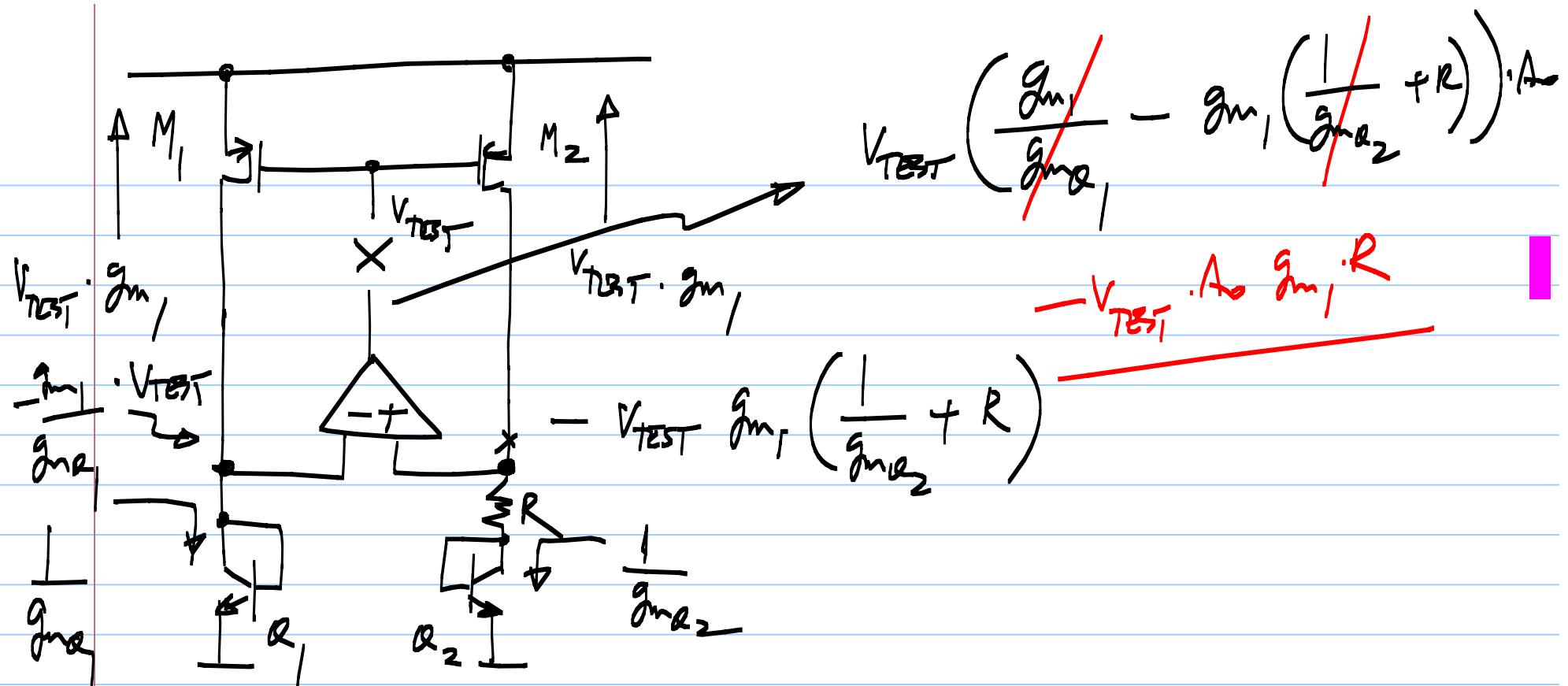


$$g_{m2} = g_{m1} = \frac{I_c}{V_t}$$

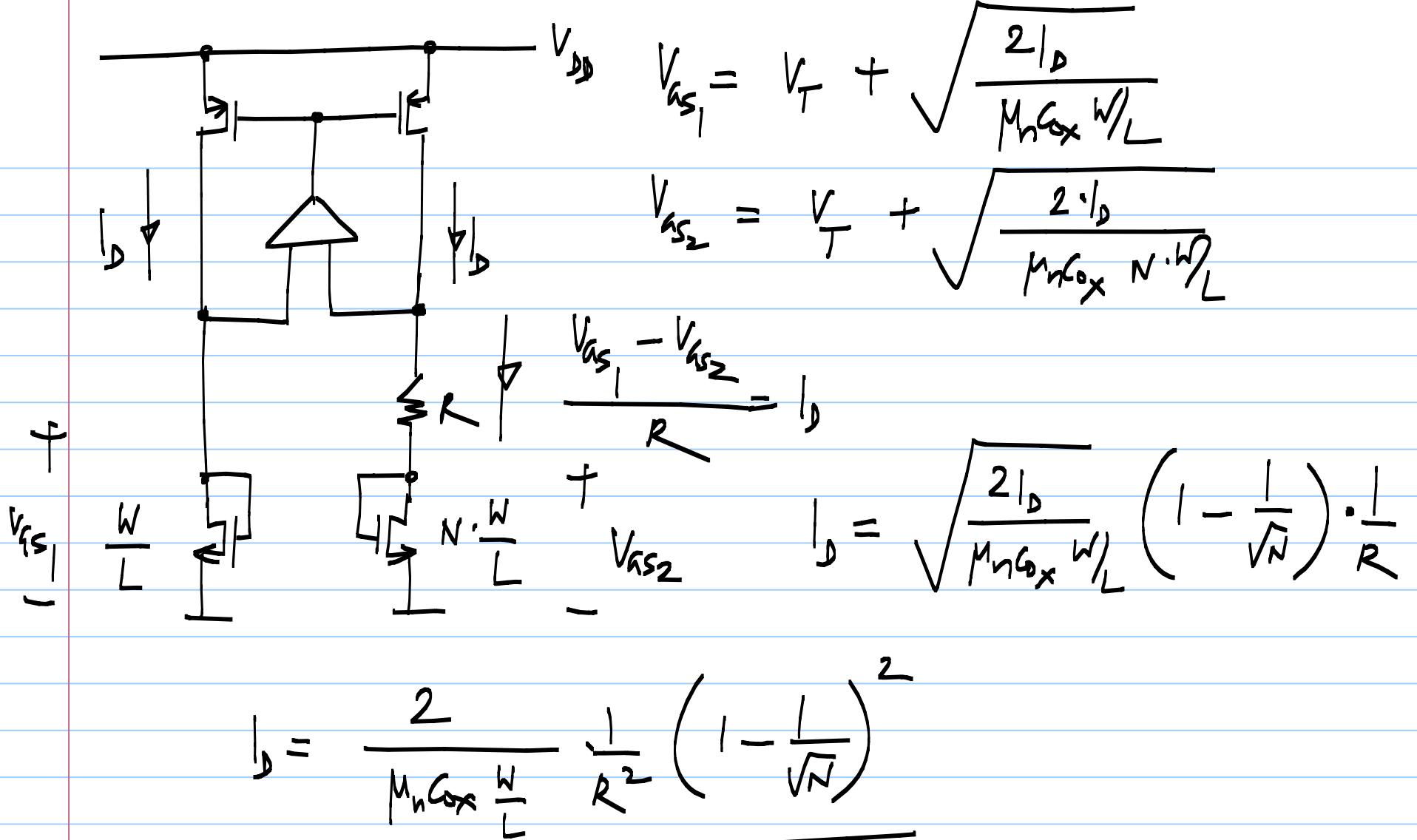


n Mos transistor biased at I_D :

$$g_m = \sqrt{2I_D \cdot M_n C_{ox} \frac{W_1}{L_1}} = 2 \sqrt{\frac{W_1/L_1}{W/L}} \cdot \frac{1}{R} \left(1 - \frac{1}{\sqrt{N}}\right)$$
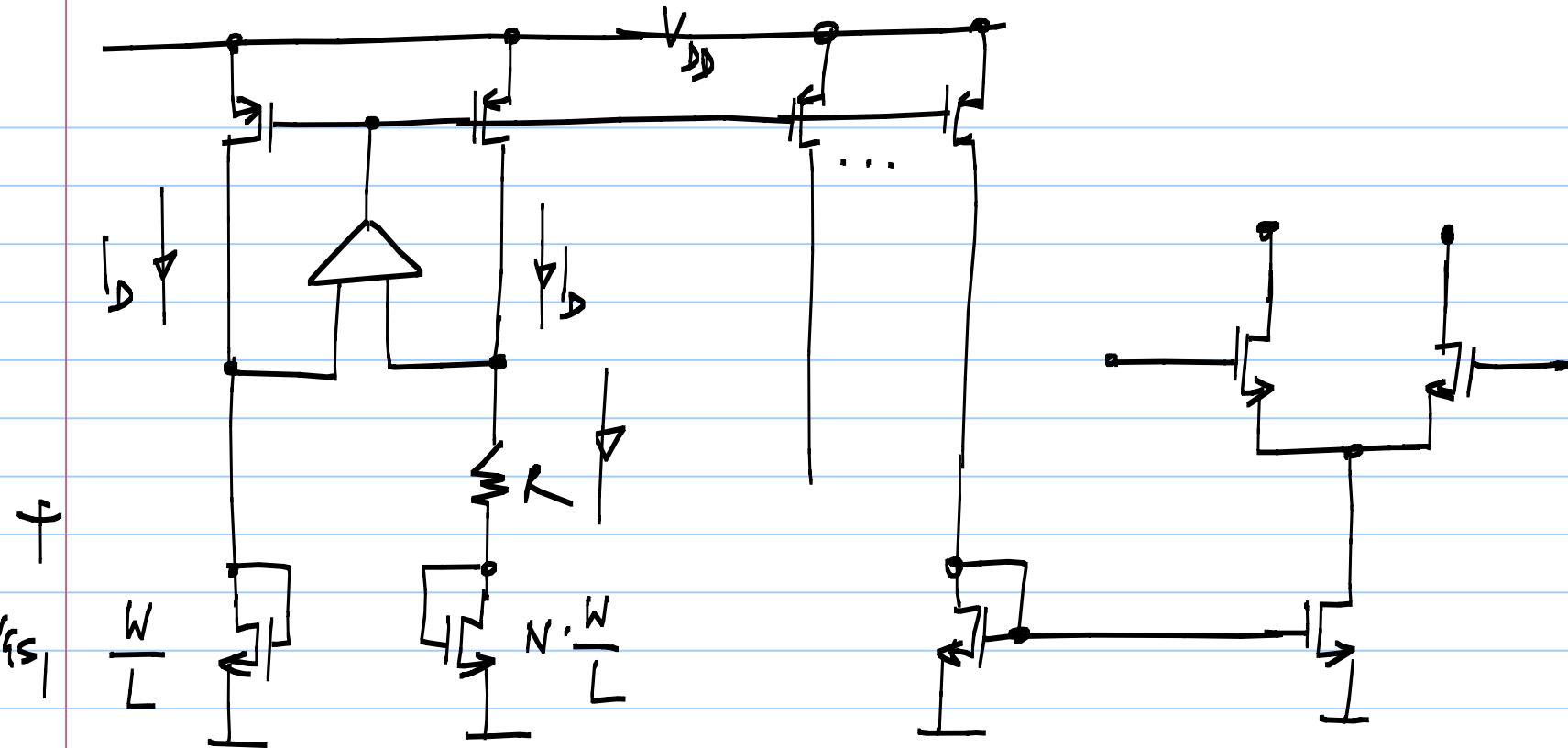
$$\sqrt{I_D} = \sqrt{\frac{2}{M_n C_{ox} \frac{W}{L}}} \frac{1}{R} \left(1 - \frac{1}{\sqrt{N}}\right)$$



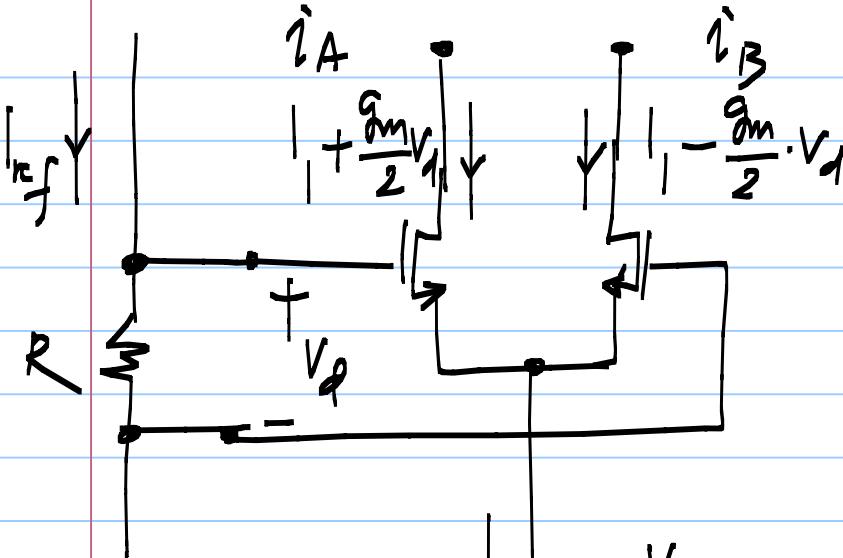


$$i_A = I_1 + \frac{g_m}{2} \cdot V_d = I_1 + \frac{g_m}{2} I_{ref} R$$

$$i_B = I_1 - \frac{g_m}{2} V_d = I_1 - \frac{g_m}{2} I_{ref} R$$

$$V_d = I_{ref} \cdot R$$

constant with
temp.

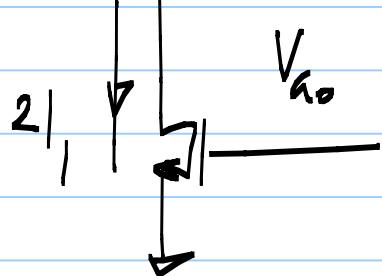


$$i_A - i_B = g_m R \cdot I_{ref}$$

$$\text{If } i_A - i_B = I_{ref} \Rightarrow g_m R = 1$$

$$g_m = \frac{1}{R}$$

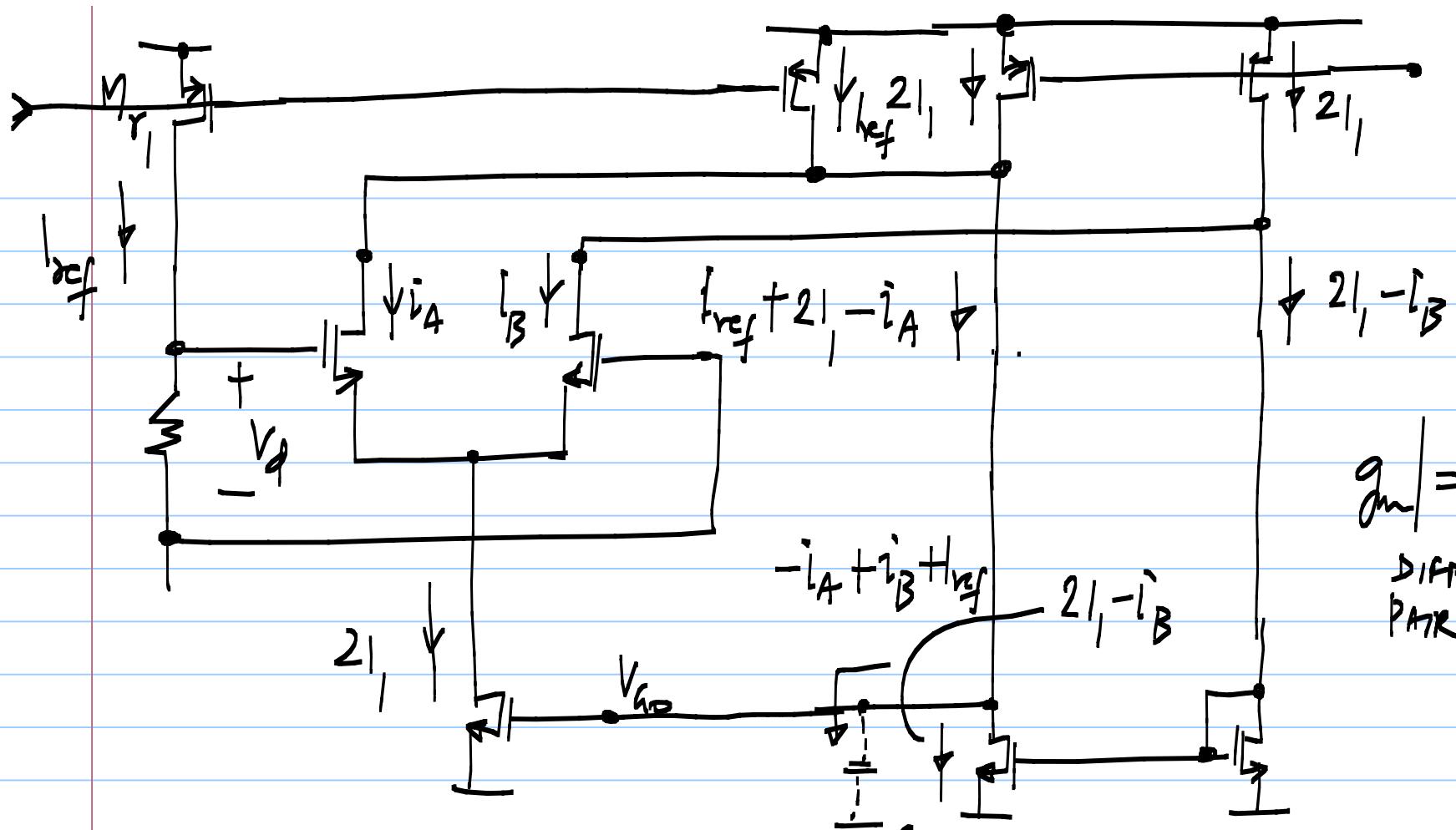* Vary g_m (\Rightarrow vary $2I_o \Rightarrow$ vary V_o)
until $i_A - i_B$ equals I_{ref}



If $i_A - i_B > |V_{REF}|$, reduce g_m (reduce V_{AO})
 $[i_A - i_B - |V_{REF}| > 0]$

