

Lecture 59:



Discrete-time filters

$$y(t) = w_p \int x(t) dt$$

$$x_d[n] = x(nT_s)$$

$$y_d[n] - y_d[n-1]$$

$$\frac{T_s}{2} (x_d[n] + x_d[n-1])$$

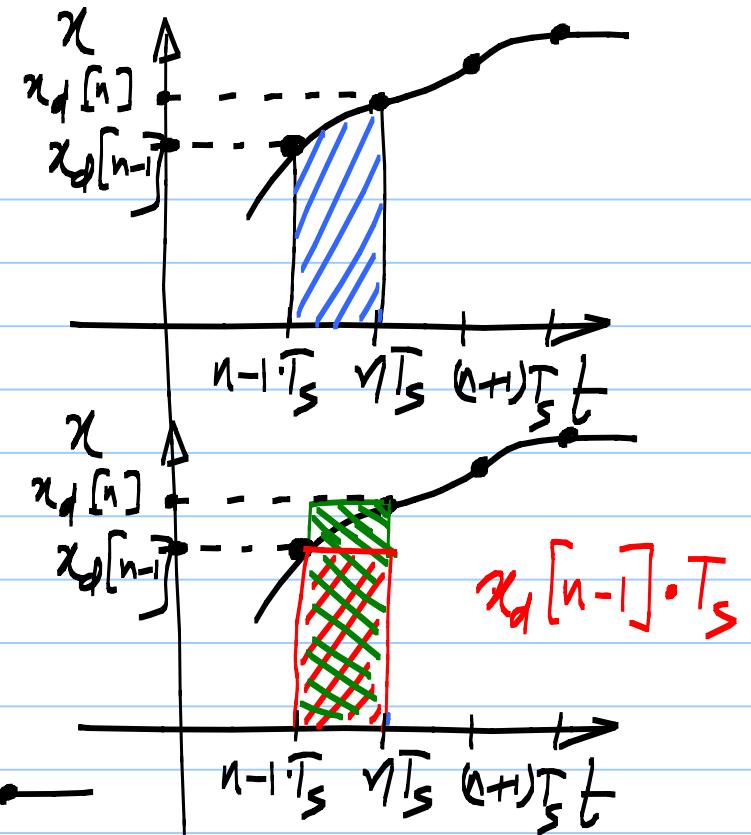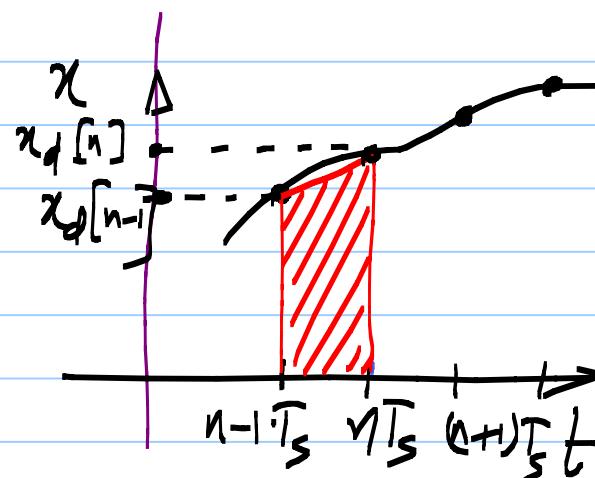

$$y(t) = w_p \int x(t) dt$$

$$y_d[n] - y_d[n-1] = w_p^T s \cdot x_d[n-1]$$

Forward Euler
Approximation

$$y_d[n] - y_d[n-1] = w_p^T s \cdot x_d[n]$$

Backward Euler

$$y_d[n] - y_d[n-1] = \frac{w_p^T s}{2} (x_d[n] + x_d[n-1])$$

Bilinear

$$y_d[n] - y_d[n-1] = \frac{w_p T_s}{2} (x_d[n] + x_d[n-1])$$

Bilinear


$$\left(y(t) = w_p \int x(t) dt \rightarrow Y(s) = \frac{w_p}{s} X(s) \right)$$

$$Y_d(z) (1 - z^{-1}) = \frac{w_p T_s}{2} (1 + z^{-1})$$


$$Y_d(z) = \frac{w_p T_s}{2} \cdot \frac{1 + z^{-1}}{1 - z^{-1}} \cdot X_d(z)$$

$$\frac{w_p T_s}{2} \cdot \frac{1 + z^{-1}}{1 - z^{-1}} \leftrightarrow \frac{w_p}{s} ; \quad s \leftrightarrow \frac{2}{T_s} \left(\frac{1 - z^{-1}}{1 + z^{-1}} \right)$$

Integrator:

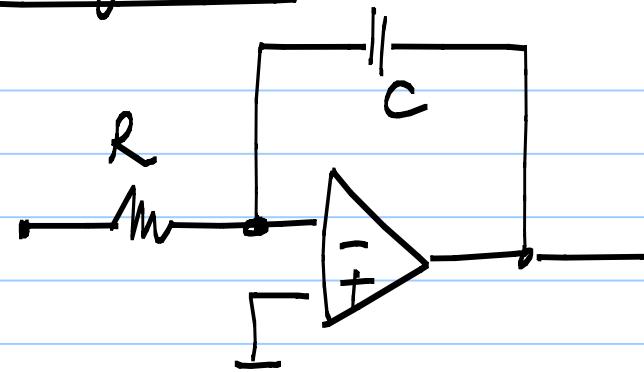

DT Integrator:

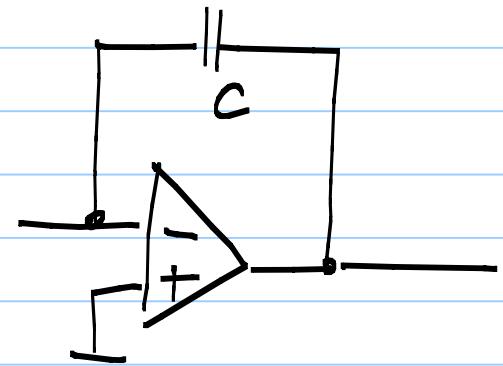


$$\frac{Y_d(z)}{X_d(z)} = \frac{2}{T_s} \cdot \frac{1+z^{-1}}{1-z^{-1}}$$

$$= \frac{2}{T_s} \left(\frac{1}{1-z^{-1}} + \frac{z^{-1}}{1-z^{-1}} \right)$$

Bkwd Euler ↗ Fwd Euler


$$y_d[n] - y_d[n-1] = \frac{2}{T_s} \cdot x_d[n]$$
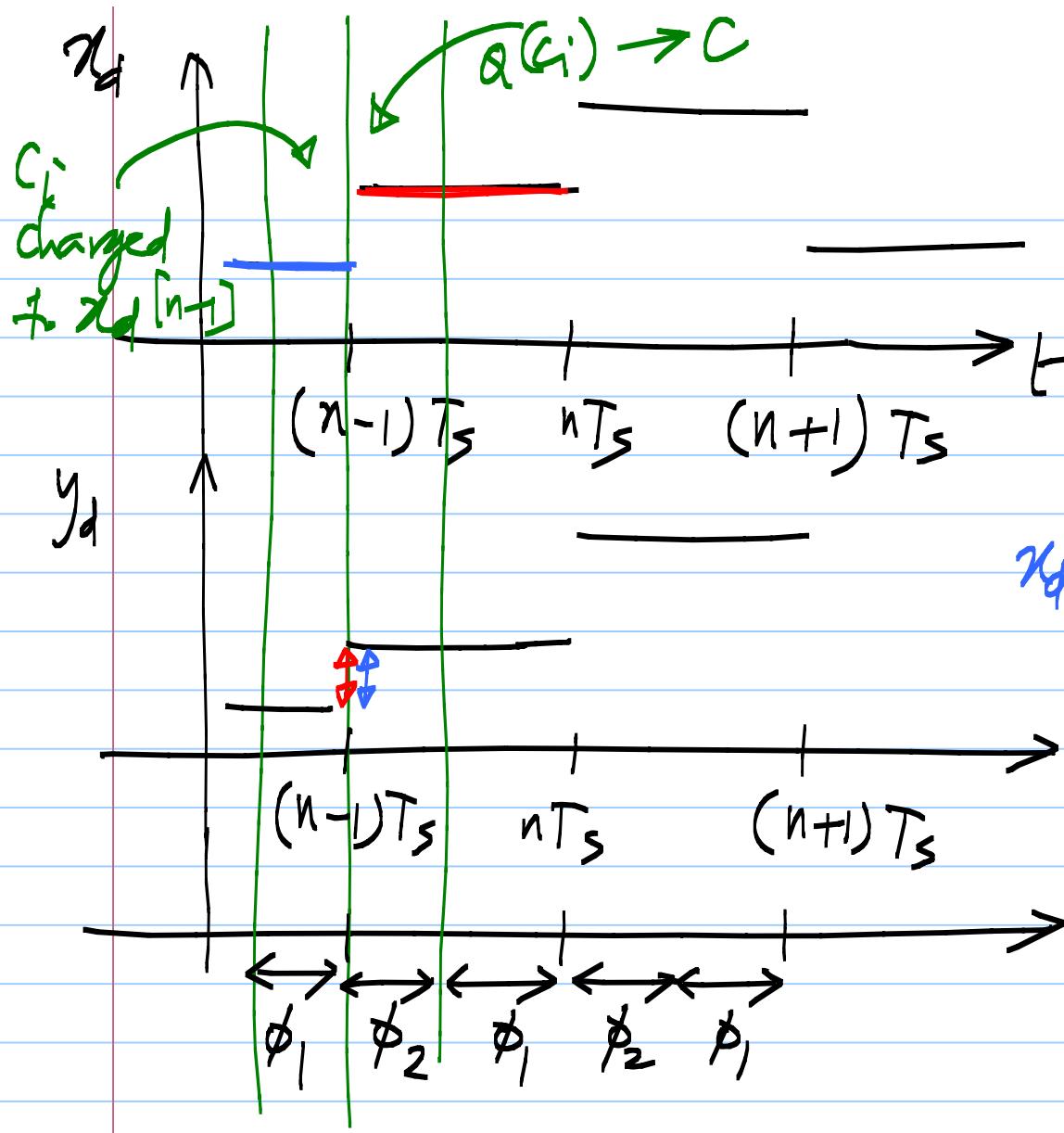
$$y_d[n] - y_d[n-1] = \frac{2}{T_s} \cdot x_d[n-1]$$




$$y_d[n] - y_d[n-1] = \frac{2}{T_s} \cdot x_d[n]$$
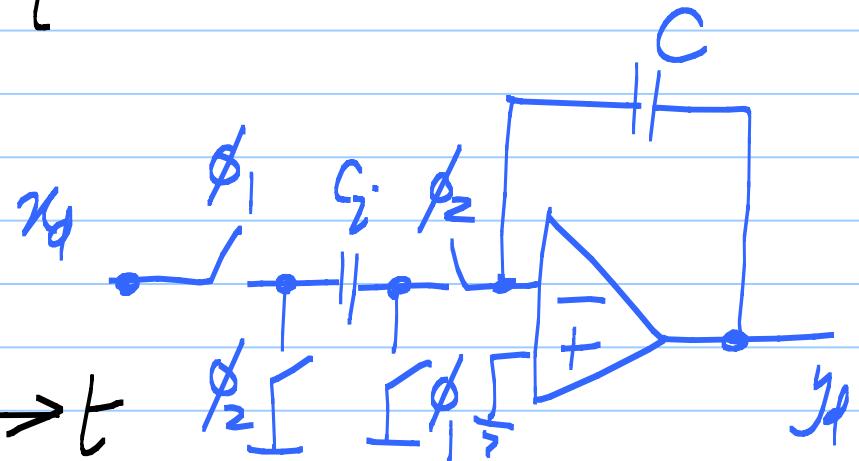
$$y_d[n] - y_d[n-1] = \frac{2}{T_s} \cdot x_d[n-1]$$



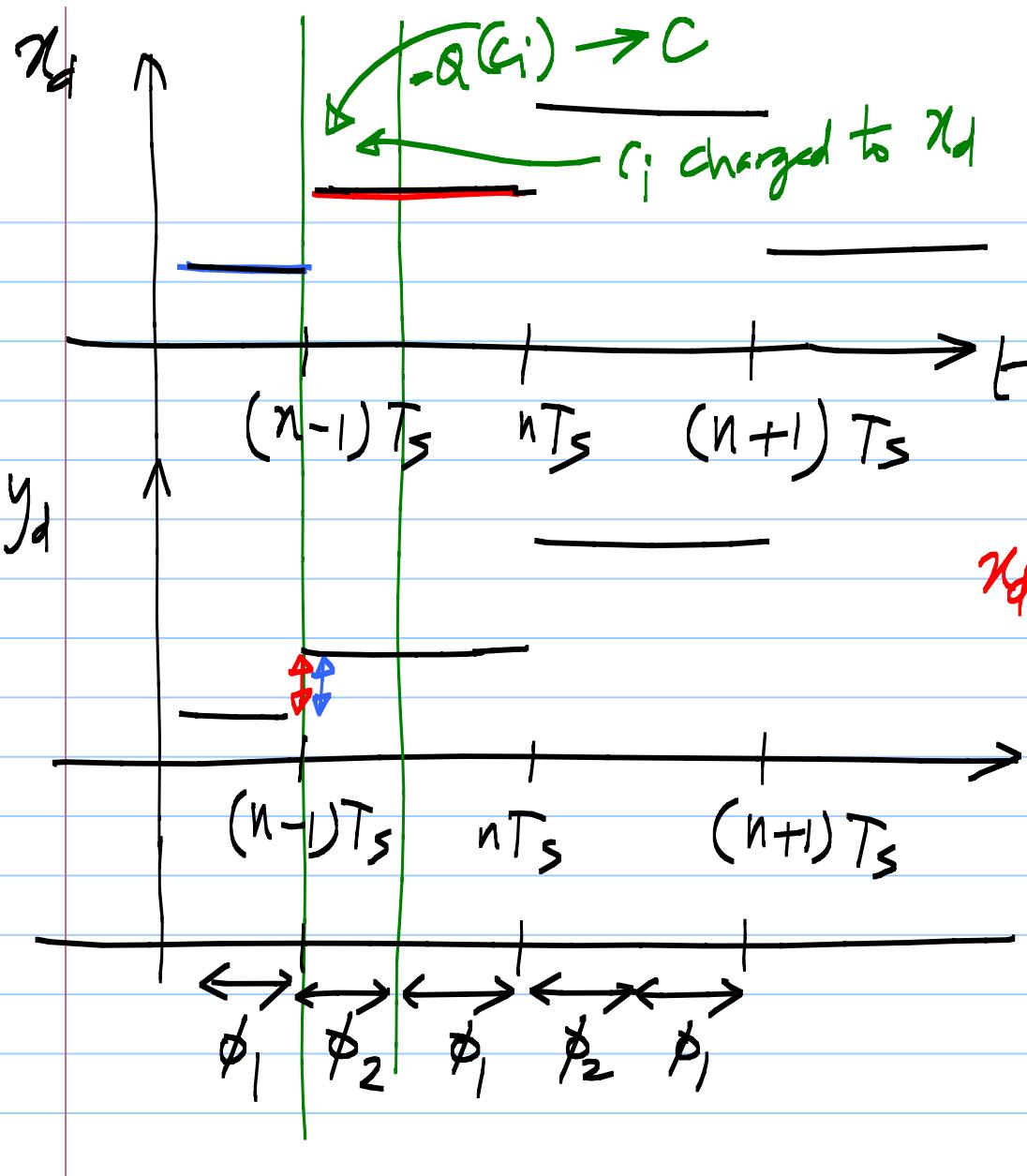
$$y_d[n] - y_d[n-1] = \frac{G_i}{C} \cdot x_d[n-1]$$




$$y_d[n] - y_d[n-1] = \frac{2}{T_s} \cdot x_d[n]$$
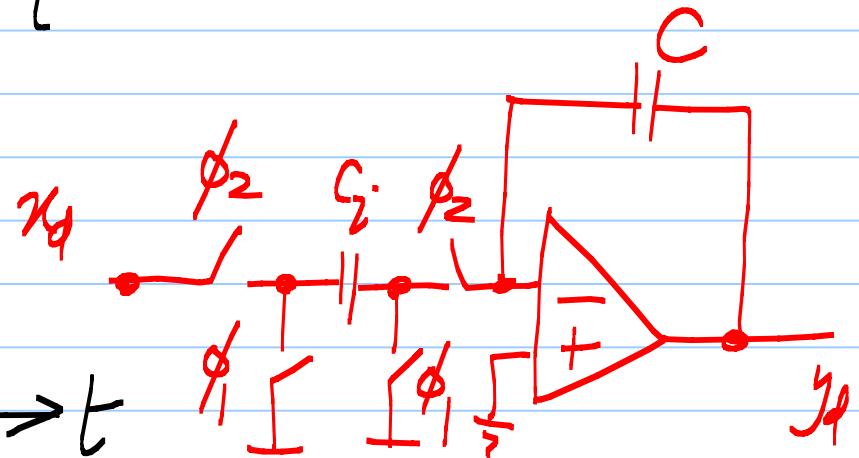
$$y_d[n] - y_d[n-1] = \frac{2}{T_s} \cdot x_d[n-1]$$



$$y_d[n] - y_d[n-1] = -\frac{C_1}{C} \cdot x_d[n]$$


Switched capacitor integrators

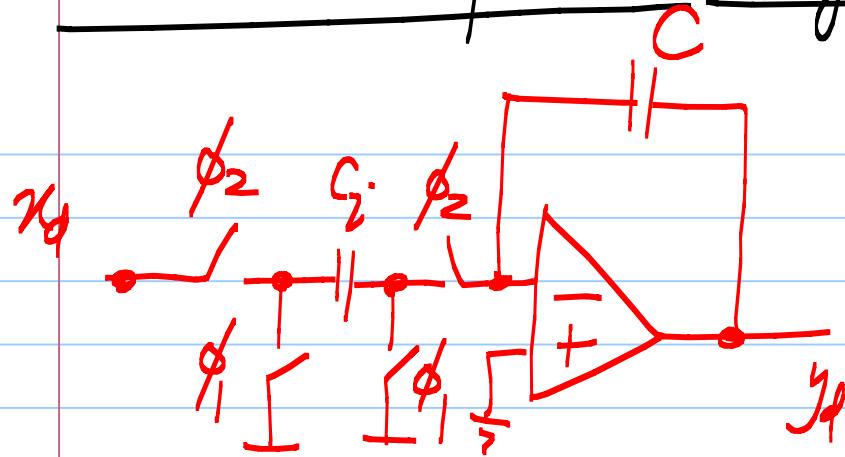

$$y_d[n] - y_d[n-1] = -\frac{C}{C} \cdot x_d[n]$$

$$\frac{Y_d(z)}{X_d(z)} = -\frac{C}{C} \cdot \frac{1}{1-z^{-1}}$$

Delay-free, inverting
integrator

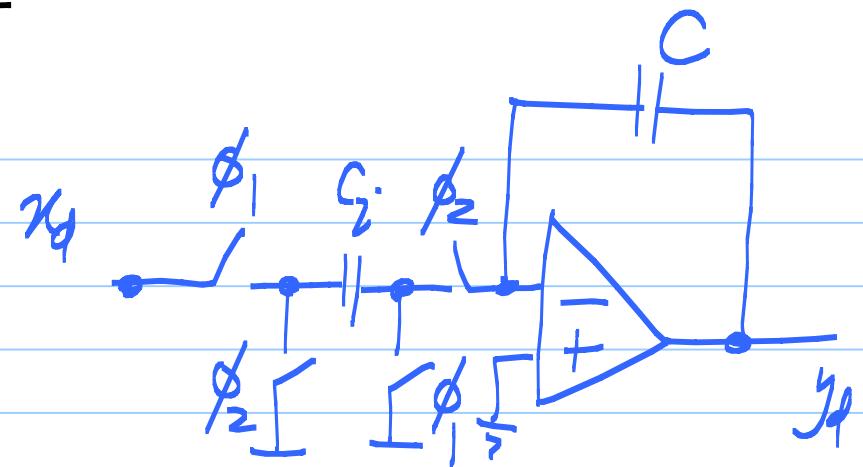


$$y_d[n] - y_d[n-1] = \frac{C}{C} \cdot x_d[n]$$

$$\frac{Y_d(z)}{X_d(z)} = +\frac{C}{C} \cdot \frac{z^{-1}}{1-z^{-1}}$$

Delayed, non-inverting
integrator

Bilinear transformed integrator:

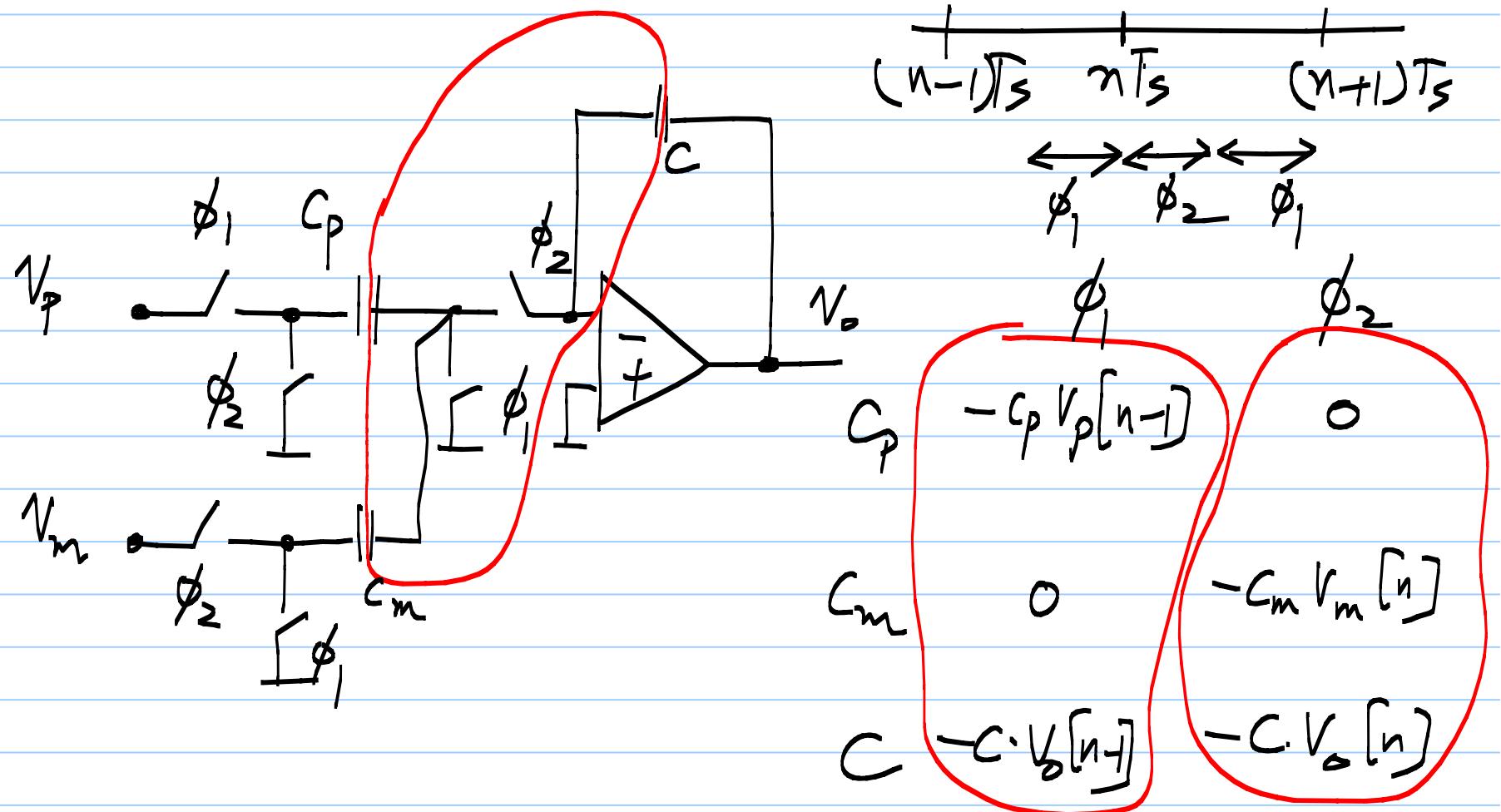

$$-C_p V_p[n-1] - 0 = C V_o[n-1]$$


$$= 0 - C_m V_m[n-1] - C V_o[n]$$

$$V_o[n] - V_o[n-1] = \frac{C_p}{C} V_p[n-1] - \frac{C_m}{C} V_m[n]$$

For bilinear transformed integrator,


$$V_p = V_i ; \quad V_m = -V_i ; \quad C_p = C_m$$

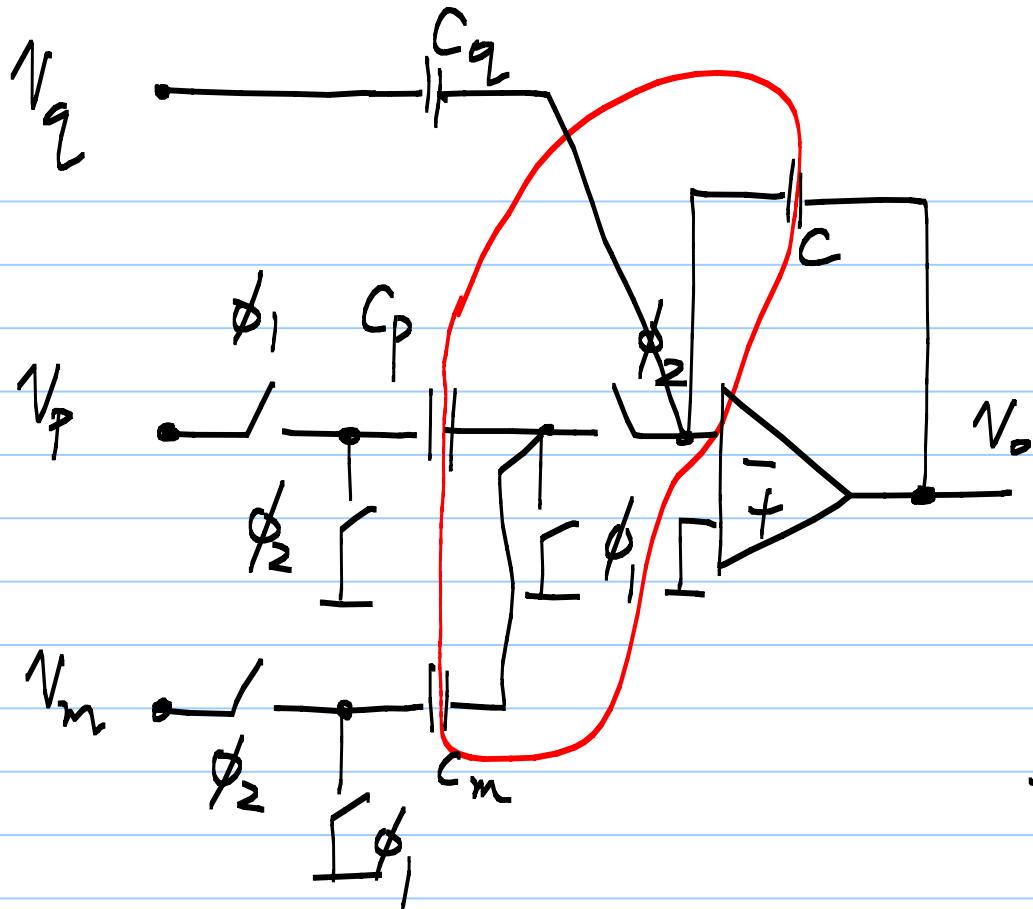
$$V_o[n] - V_o[n-1] = \frac{C_p}{C} \cdot (V_i[n-1] + V_i[n])$$



$$+ \frac{C_Q}{C} (V_Q[n-1] - V_Q[n])$$
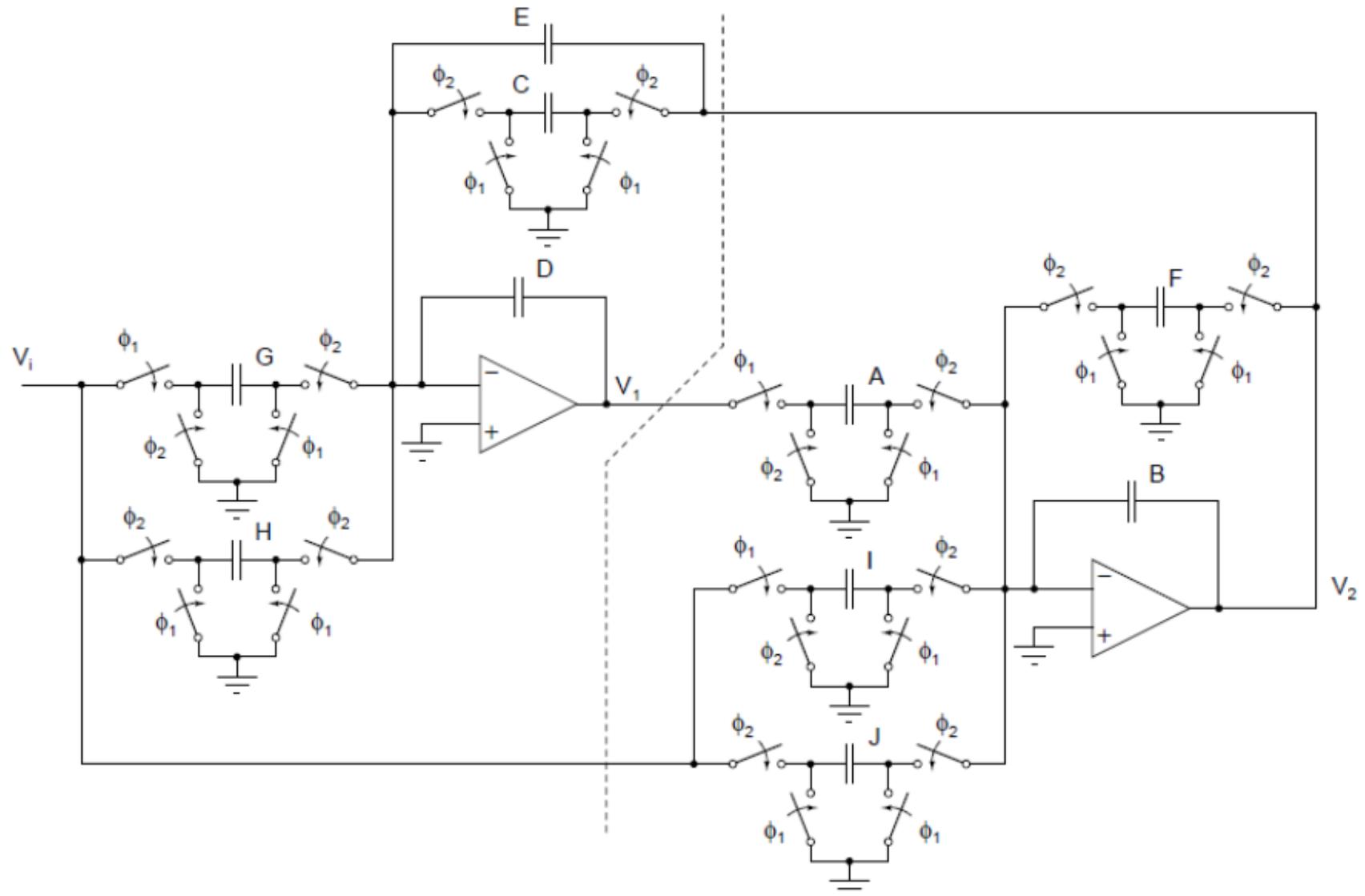
$$V_o[n] - V_o[n-1] = \frac{C_P}{C} V_P[n-1] - \frac{C_m}{C} V_m[n]$$



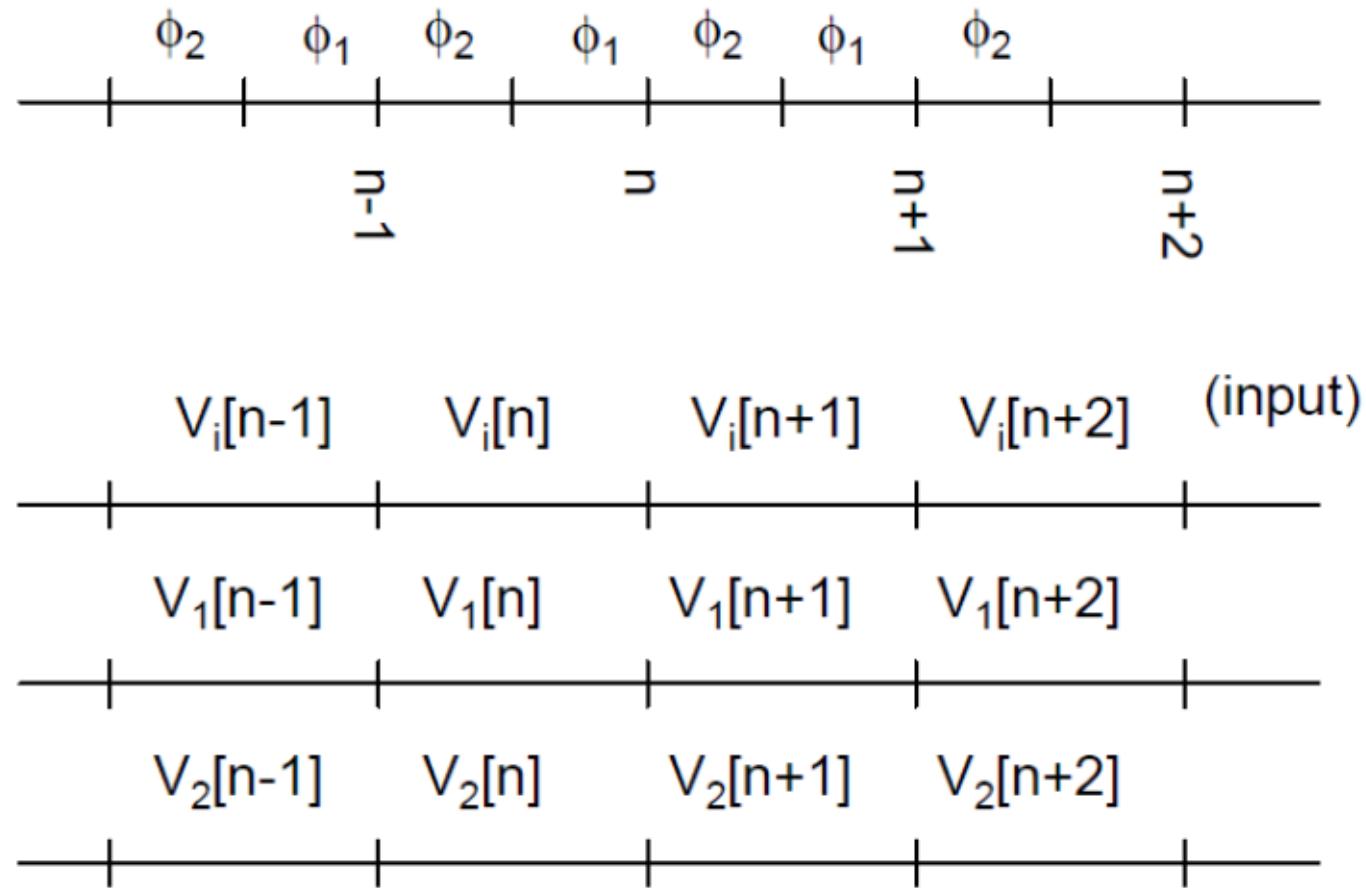

$$\begin{aligned}
 & D(V_1[n] - V_1[n-1]) + G(0 - V_i[n-1]) + \\
 & H(V_i[n] - 0) + C(V_2[n] - 0) + E(V_2[n] - V_2[n-1]) = 0 \\
 & B(V_2[n] - V_2[n-1]) + F(V_2[n] - 0) + A(0 - V_1[n-1]) + \\
 & I(0 - V_i[n-1]) + J(V_i[n] - 0) = 0
 \end{aligned}$$

$$\frac{V_2}{V_{in}} = \frac{-DJ + (ID + DJ - HA)z^{-1} + (GA - ID)z^{-2}}{D(B + F) + (-2BD - DF + AC + AE)z^{-1} + (BD - AE)z^{-2}}$$

$B = D = 1$; Any one of $G, H, I, J = 0$; $A = C$


2nd order lowpass filter:

$$s \leftrightarrow \frac{2}{T_s} \cdot \frac{1-z^{-1}}{(1+z^{-1})}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + \frac{s}{Q\omega_p} + \frac{s^2}{\omega_p^2}}$$

$$\begin{aligned}\frac{V_o(z)}{V_i(z)} &= \frac{1}{1 + \frac{2}{Q\omega_p T_s} \cdot \frac{1-z^{-1}}{(1+z^{-1})} + \frac{4}{(\omega_p T_s)^2} \cdot \frac{(1-z^{-1})^2}{(1+z^{-1})^2}} \\ &= \frac{(1+z^{-1})^2}{(1+z^{-1})^2 + \frac{2}{Q\omega_p T_s} (1-z^{-1})(1+z^{-1}) + \frac{4}{(\omega_p T_s)^2} (1-z^{-1})^2}\end{aligned}$$

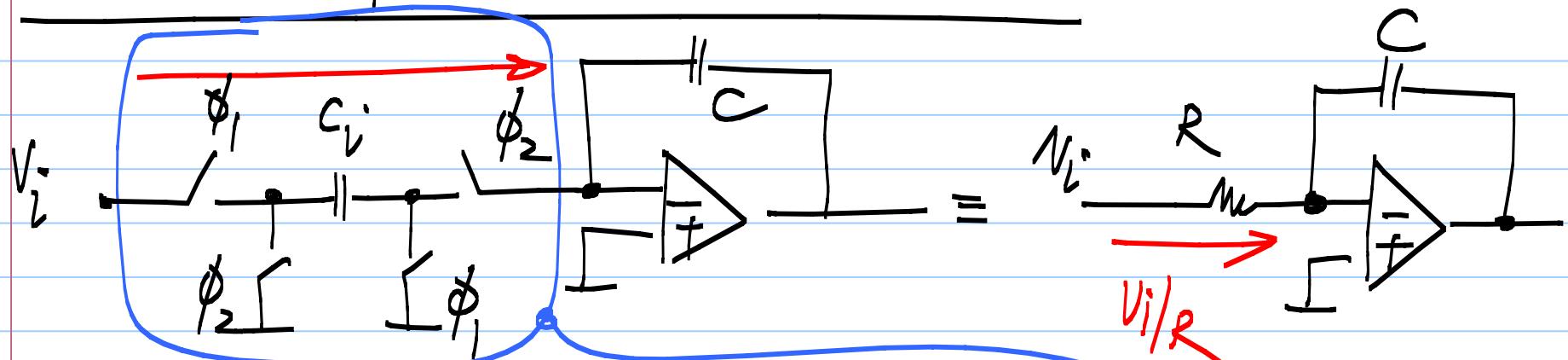Switched capacitor \longleftrightarrow resistor :



In each cycle ($\approx T_s$), a charge $C_i V_i$ is transferred to C

$$R = \frac{T_s}{C_i} = \frac{1}{f_s C_i}$$

$$\therefore \text{Average current} = \frac{C_i V_i}{T_s} = \frac{V_i}{\underline{\underline{(T_s/C_i)}}} = \frac{V_i}{\underline{\underline{f_s C_i}}}$$