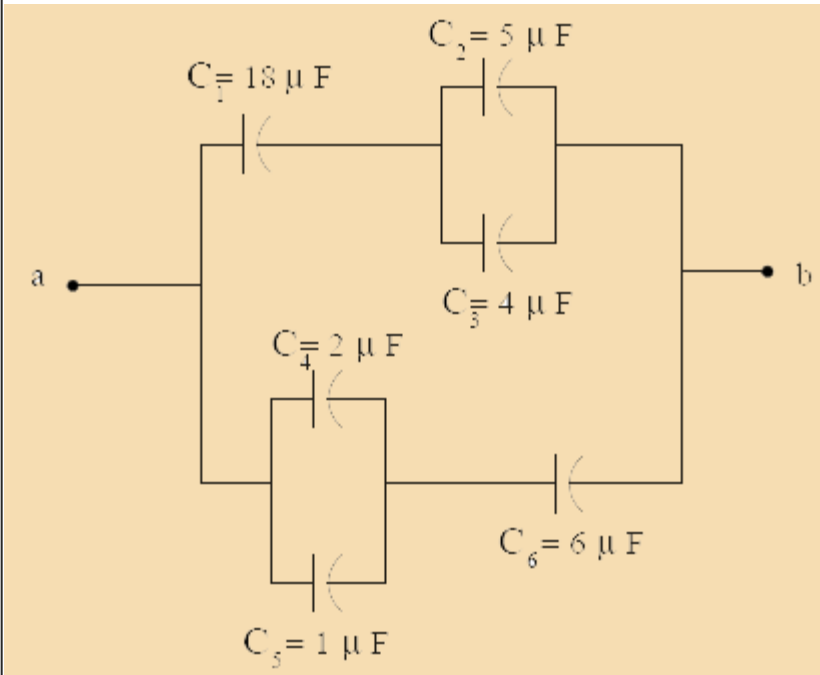


Exercise 1

Determine the effective capacitance of the following capacitance circuit and find the voltage across each capacitance if the voltage across the points a and b is 300 V.



[Ans. $8 \mu\text{F}$., 100V,200V,200V,200V,200V,100V]

Exercise 2

Two parallel, infinite plates made of material of perfect conductor, carry charges Q_1 and Q_2 . The plates have finite thickness. Show that the charge densities on the two adjacent inside surfaces are equal and opposite while that on the two outside surfaces are equal.

(Hint : Field inside the plates due to four charged surfaces must be zero.)